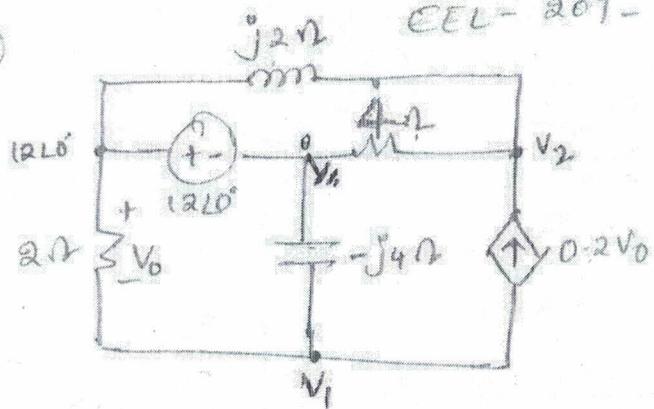


(1)

①

CEL - 209 - LNT (END - Exam)



$$V_0 = 12L^{\circ} - V_1 \rightarrow ① \Rightarrow \text{from } ②$$

Apply nodal analysis at V_1 :

$$\frac{V_1 - 12L^{\circ}}{2} + \frac{V_1}{j4} = -0.2V_0, \rightarrow ② \Rightarrow \frac{2(V_1 - 12L^{\circ})}{2+2} + \frac{V_1 j}{-j4(j)} = -0.2V_0$$

$$\frac{V_2 - 12L^{\circ}}{j2} + \frac{V_2}{4} = 0.2V_0 \rightarrow ③ \Rightarrow \frac{2V_1 - 24L^{\circ}}{4} + \frac{V_1 j}{4} = -0.2V_0 \rightarrow ④ \quad \text{from } ③$$

$$\text{from } ② \quad 2V_1 - 24 + jV_1 = -0.8V_0 \rightarrow ④$$

$$\text{Sub } ① \text{ in } ④ \quad (2+j)V_1 = -0.8(12 - V_1) + 24$$

$$(2+j)V_1 = -9.6 + 0.8V_1 + 24$$

$$V_1(1.2+j) = 14.4$$

$$V_1 = \frac{14.4}{1.2+j} = 9.081 - 5.901j \rightarrow ⑤$$

1M


$$\text{From } ①, \text{ sub } ⑤ \text{ in } ① \quad V_0 = 12L^{\circ} - 7.081 + 5.901j$$

$$V_0 = 4.918 + 5.901j$$

$$V_0 = 7.682 \angle 50.194^\circ$$

1M

②

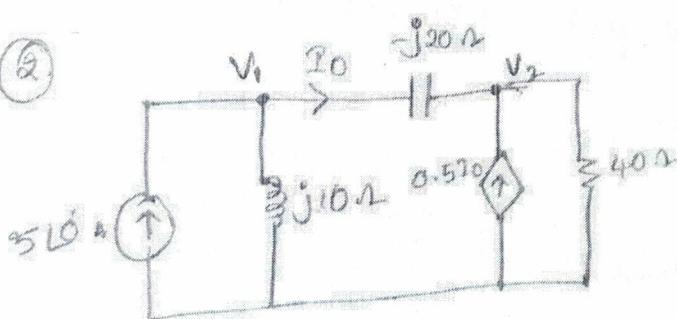Nodal at V_1

$$\frac{V_1 - V_2}{-j20} + \frac{V_1}{j10} = 5L^{\circ}$$

$$jV_1 - jV_2 - 2jV_1 = 100$$


$$V_1 = j100 - V_2 \rightarrow ①$$

Nodal at V_2

$$\frac{V_2}{40} + \frac{V_2 - V_1}{-j20} = 0.5V_1, \rightarrow ②$$

$$\frac{V_1 - V_2}{-j20} = 10 \rightarrow ③$$

1M

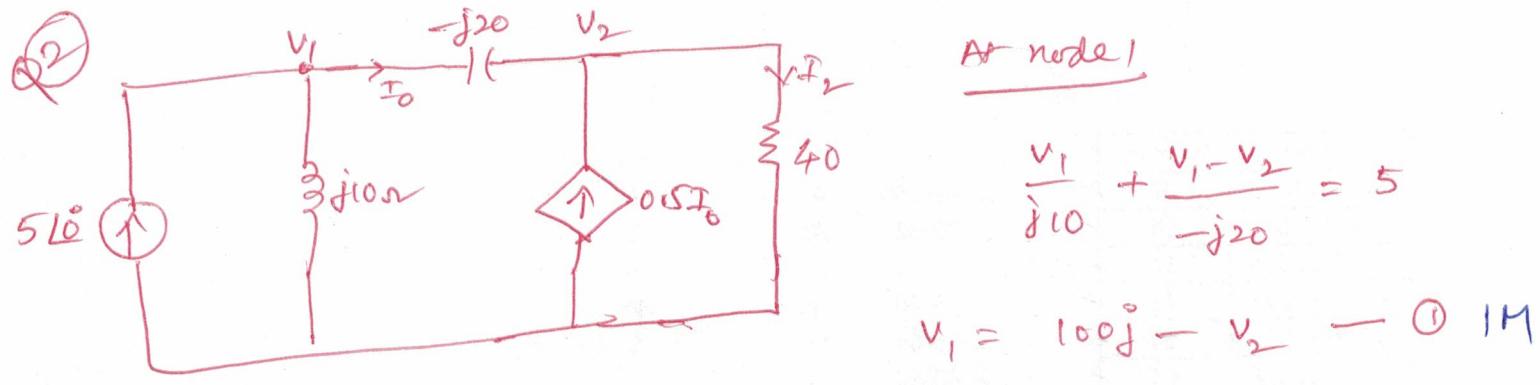

At node 1

$$\frac{V_1}{j10} + \frac{V_1 - V_2}{-j20} = 5$$

$$V_1 = 100j - V_2 \quad \text{--- (1) IM}$$

At node 2:

$$0.5I_0 + I_0 = \frac{V_2}{40}, \text{ but } I_0 = \frac{V_1 - V_2}{-j20}; \text{ hence}$$

$$1.5 \left(\frac{V_1 - V_2}{-j20} \right) = \frac{V_2}{40} \Rightarrow 3V_1 = (3-j)V_2 \quad \text{--- (2) IM}$$

Substituting (1) in (2)

$$300j - 3V_2 = 3V_2 - jV_2 \Rightarrow 300j = V_2(6-j)$$

$$\therefore V_2 = \frac{300j}{6-j} = -8.1 + j48.6 \text{ or } \underline{\underline{49.32}} \angle \underline{\underline{99.46}}$$

$$I_2 = \frac{49.32}{40} = \underline{\underline{1.23A}}$$

$$P_{avg} = \frac{1}{2} \left| \frac{V^2}{R} \right| \text{ or } \frac{1}{2} |I_2|^2 R. = \underline{\underline{30.25W}} \rightarrow 2M$$

(2)

$$\text{From (2)} \quad \frac{V_2}{40} + \frac{2j(V_2 - V_R)}{40} = 0.5 \left(\frac{V_1 - V_2}{-j20} \right)$$

$$V_2 + 2jV_2 - 2jV_1 = \frac{V_1 - V_2}{-j} \quad \boxed{j_2 = -1}$$

$$-V_2 j + 2V_2 + 2V_1 = V_1 - V_2$$

$$-3V_1 = -V_2 - 2V_2 + V_2 j$$

$$-3V_1 = -V_2(3+j) \Rightarrow V_1 = V_2 \left(\frac{3+j}{3} \right) \rightarrow (4) \rightarrow 1M$$

$$\text{from (1)} \quad V_1 = 100j - V_2$$

$$\text{Sub (1) in (4)} \quad 100j - V_2 = V_2 \left(\frac{3+j}{3} \right)$$

$$300j - 3V_2 = 3V_2 - 3jV_2$$

$$300j + 3jV_2 = 6V_2 \rightarrow$$

$$V_2 = 50j + 0.5jV_2$$


$$3V_2 - 3jV_2 + 3V_2 = 300j$$

$$V_2 = \frac{300j}{6+3j} = \frac{100j}{2-j}$$

$$I_2 = \frac{V_2}{40} = \frac{2.5j}{2-j} \rightarrow 1M$$

$$P_{avg} = \frac{1}{2} (I_2)^2 R = \frac{1}{2} \left(\frac{2.5}{\sqrt{5}} \right)^2 (40) = \cancel{25} \text{ Watt} \quad \rightarrow 2M$$

(3)

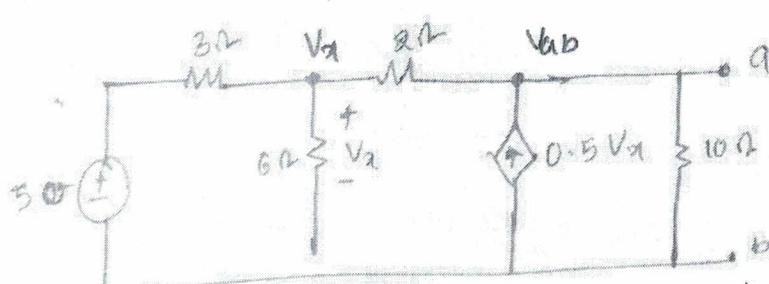

Thevenin's equivalent at point "a b". $\rightarrow (V_{AB} = V_{AB})$

$$\frac{V_A - 50}{3} + \frac{V_A - V_{AB}}{2} + \frac{V_A}{6} = 0$$

$$2V_A - 100 + 3V_A - 3V_{AB} + V_A = 0$$

$$6V_A - 3V_{AB} = 100 \rightarrow (1)$$

$$\frac{V_{AB}}{10} + \frac{V_{AB} - V_A}{2} = 0.5V_A \Rightarrow V_{AB} + 5V_{AB} - 5V_A = 5V_A$$

$$6V_{AB} = 10V_A \Rightarrow V_A = 0.6V_{AB} \rightarrow (2)$$


(3)

Sub ② In ①

$$6(0.6 V_{ab}) - 3 V_{ab} = 10V$$

$$3 \cdot 6 V_{ab} - 3 V_{ab} = 10V$$
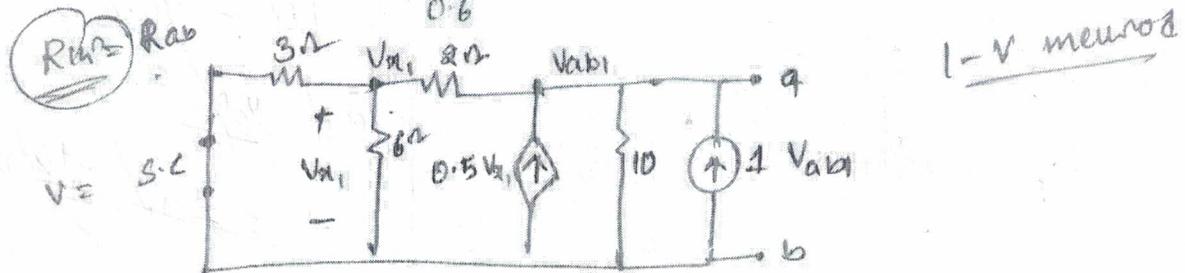
$$V_{ab} = \frac{10V}{0.6} = 166.67 \text{ volt} \quad \rightarrow 2M$$



$$R_{in} = R_{ab} = \frac{V_{ab1}}{1} \rightarrow ⑤$$

calculate V_{ab1}

$$\frac{V_{x_1}}{3} + \frac{V_{x_1}}{6} + \frac{V_{x_1} - V_{ab1}}{2} = 0$$

$$2V_{x_1} + V_{x_1} + 3V_{x_1} - 3V_{ab1} = 0$$

$$6V_{x_1} = 3V_{ab1} \rightarrow ③ \Rightarrow V_{x_1} = 0.5V_{ab1}$$

$$\frac{V_{ab1} - V_{x_1}}{2} + \frac{V_{ab1}}{10} = 1 + 0.5V_{x_1}$$

$$5V_{ab1} - 5V_{x_1} + V_{ab1} = 10 + 5V_{x_1}$$

$$6V_{ab1} = 10 + 10V_{x_1} \rightarrow ④$$


Sub ③ in ④

$$6V_{ab1} = 10 + 5V_{ab1}$$


$$V_{ab1} = 10$$

Sub V_{ab1} in ⑤

$$R_{in} = R_{ab} = \frac{10}{1} = 10\Omega \rightarrow 2M$$

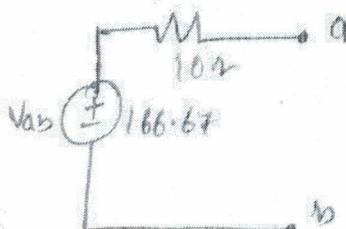Equivalent of thevenin
 R_{ab} ↓
1M

Equivalent of Norton

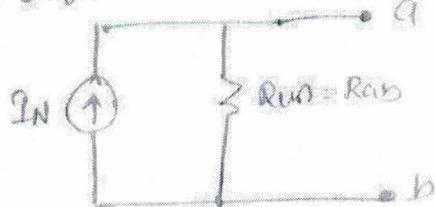


→ 1M

$$I_N = \frac{V_{ab} = V_{ab}}{R_{in} = R_{ab}} = \frac{166.67}{10}$$


$$I_N = 16.667 \text{ Amp}$$

(4)

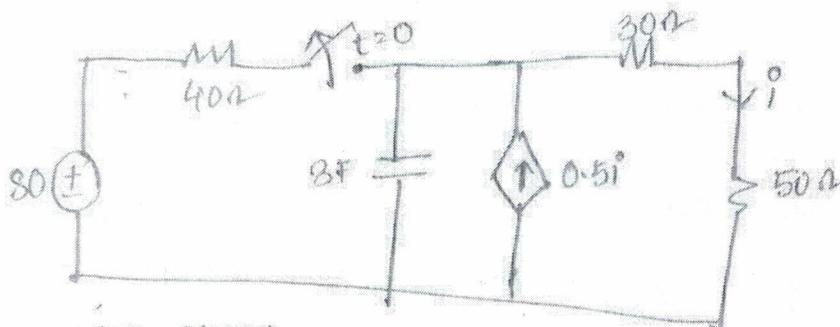

(4)

$$\begin{aligned}
 v_c(t) &= v_a - v_o - (v_a - v_o)e^{-t/480} \\
 &= 160 - 96 \cdot e^{-t/480} \\
 i(t) &\equiv \frac{v_c(t)}{80} \\
 &= 2 - 1.2e^{-t/480}
 \end{aligned}$$

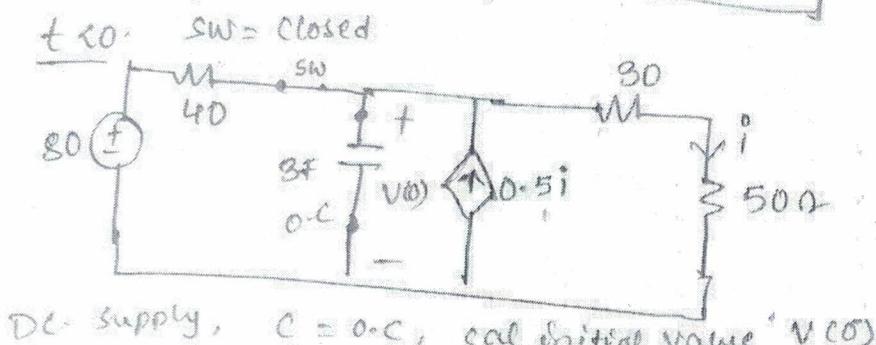DC supply, $C = 0.0\text{C}$, calc initial value 'V(0)'

$$\frac{V(0)}{40} + \frac{V(0)}{80} = 0.5i \rightarrow (1) \quad i = \frac{V(0)}{80} \rightarrow (2)$$


$$\frac{2V(0) - 160}{80} + \frac{V(0)}{80} = \frac{0.5 \cdot V(0)}{80}$$

$$2V(0) + V(0) - 0.5V(0) = 160$$

$$2.5V(0) = 160$$


$$V(0) = 64 \text{ volt}$$

from (2), sub $V(0) = 64$: $\Rightarrow i(0) = \frac{64}{80} = 0.8 \text{ Amp}$ $\Rightarrow 1M$

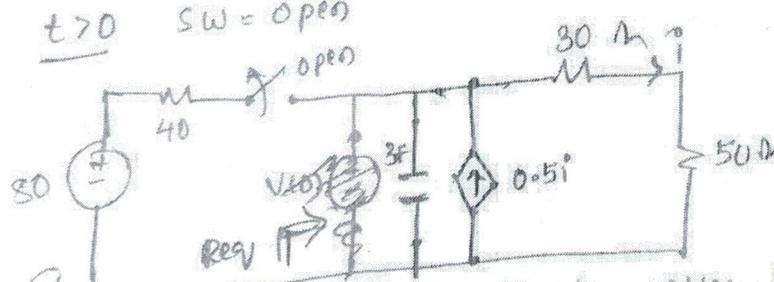 $t > 0$ SW = open

$$i(t) = i(0) e^{-t/480}$$

The circuit is source free circuit. After SW operation Q.P. 3 occurs.

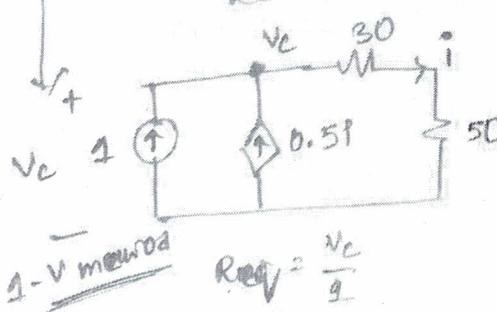RC circuit, $\tau = R_{eq} C$ 

$$\frac{V_c}{80} = 1 + 0.5i$$

$$V_c = 80 + 0.5V_c$$

$$V_c = 160$$


$$i = \frac{V_c}{80}$$

$$R_{eq} = \frac{160}{1} = 160$$

$$R_P = R_{eq} \cdot C = 160 \times 3 = \frac{480}{\text{sec}}$$



$$i(t) = 0.8 e^{-t/480} \text{ AMP}$$

 $\hookrightarrow 2M$

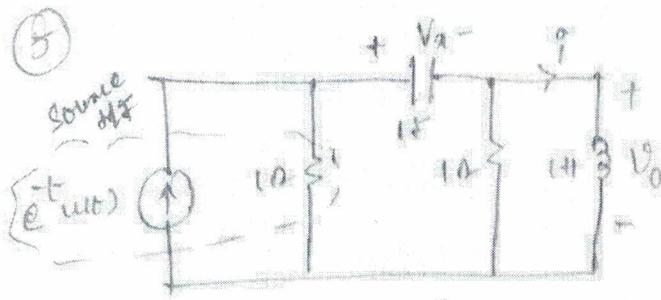

Assume
 $V_s(0) = 0 \text{ volt}$
 $i(0) = 1 \text{ amp}$

using initial condition [C],

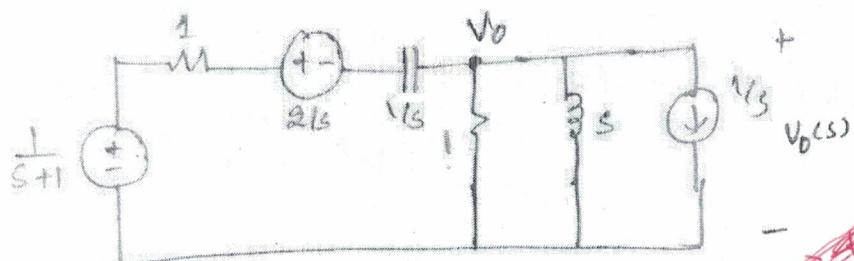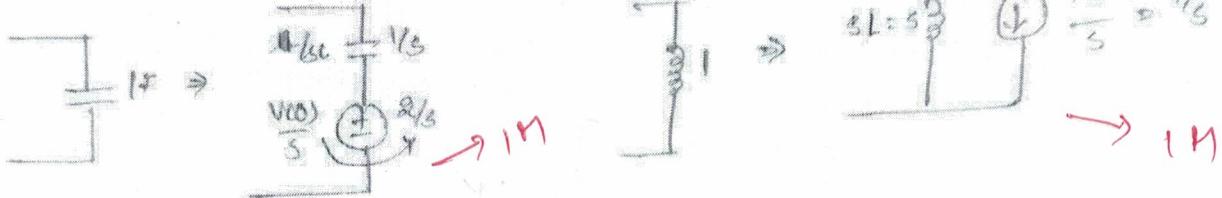

$$\frac{V_o}{s} + \frac{V_o}{s} + \frac{(V_{s+1}) - 2/s - V_o}{1 + V_s} = -\frac{1}{s} \Rightarrow \frac{s}{s+1} - 2 - sV_o = (s+1)(s+1/s)V_o + \frac{s+1}{s}$$

~~$$V_o(1 + \frac{1}{s} + \frac{1}{s}) \quad (V_{s+1}) - \frac{2/s - V_o}{1 + V_s} \quad \frac{s}{s+1} - \frac{s+1}{s} - 2 = (2s + 2 + 1/s)V_o$$~~

$V_o(1 + \frac{1}{s} + \frac{1}{s})$

$$V_o = \frac{-2s^2 - 4s - 1}{(s+1)(2s^2 + 2s + 1)} \rightarrow 1M$$

$$V_o = \frac{-s^2 - 2s - 0.5}{(s+1)(s^2 + s + 0.5)} = \frac{A}{s+1} + \frac{Bs + C}{s^2 + s + 0.5}$$

$$\text{Sub } s = -1, \Rightarrow -s^2 - 2s - 0.5 = A(s^2 + s + 0.5) + B(s^2 + s) + C(s+1)$$

$\rightarrow A = 1$

Equating coeff:

$$s^2 \Rightarrow -1 = A + B \Rightarrow B = -2$$

$$s^1 \Rightarrow -2 = A + B + C \Rightarrow C = -1$$


$$V_o = \frac{-s^2 - 2s - 0.5}{(s+1)(s^2 + s + 0.5)} = \frac{1}{s+1} - \frac{2(s+0.5)}{(s+0.5)^2 + (0.5)^2}$$

$$V_o(s) = \left[e^{-t} - 2e^{-t/2} \cos(1/2)t \right] \text{ unit} \rightarrow 2M$$

(5) 2M

L = $\int 4 \cdot 2^t dt$

(6)

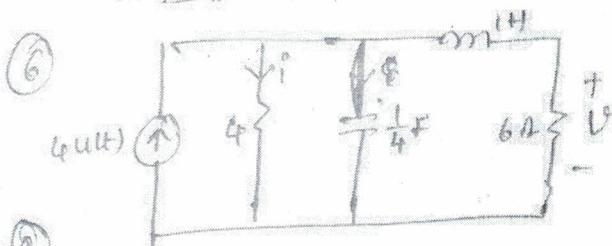


(a) for $t < 0$, $i_{L(0)} = 0$
so that the circuit is
not active.

Initial conditions = 0.


$$\left. \begin{aligned} i_{L(0^-)} &= i_{L(0^+)} = 0 \Rightarrow i_{L(0^+)} \\ V_c(0^-) &= V_c(0^+) = 0 \Rightarrow V_c(0^+) \end{aligned} \right\} -1M$$

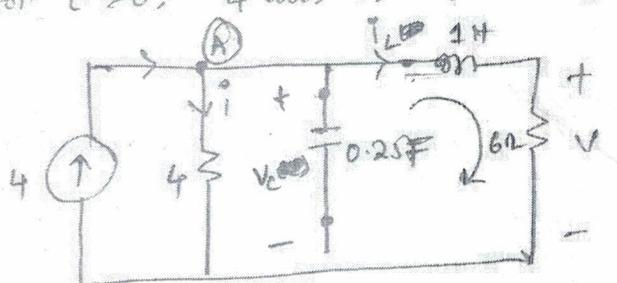for $t > 0$, $i_{L(0^+)} \rightarrow i_L$ (Supply), circuit is active



$$\left. \begin{aligned} \frac{di_{L(t)}}{dt} &= 4 \text{ Amp/sec} \\ \frac{dv_{c(t)}}{dt} &= 0 \text{ volt/sec} \\ \frac{dv_{L(t)}}{dt} &= 0 \text{ volt/sec} \end{aligned} \right\}$$

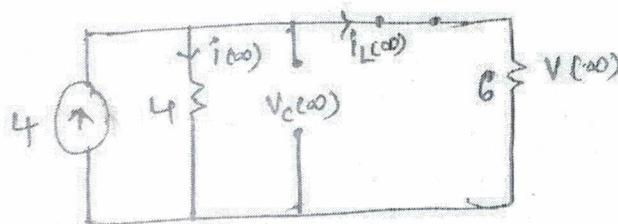(b) for $t > 0$, SW is closed for long time $t \rightarrow \infty$, $C \rightarrow 0 \cdot C$, $L \rightarrow 5 \cdot L$



$$\text{Current division} \quad i(0) = \frac{4 + 6}{10} = 1.0 \text{ Amp}$$

$$i_{L(\infty)} = \frac{4 + 4}{10} = 1.6 \text{ Amp} \quad \checkmark 1M$$

$$V(0) = i_{L(0)} + 6$$

$$V(\infty) = 1.6 + 6 = 7.6 \text{ Volts} \quad \checkmark 1M$$

$$V_c(0) = i(0) * 4 = 4.0 \text{ Volts.}$$

(c) We know that

$$C \frac{dv_{c(0^+)} - v_{c(0^+)} - i_{c(0^+)} \cdot C}{dt} = i_c(0^+) \Rightarrow \frac{dv_{c(0^+)} - i_{c(0^+)} \cdot C}{dt} = \frac{0}{C} = 0 \text{ Volt/sec (0-C).}$$

$$L \frac{di_{L(0^+)} - v_{c(0^+)} - i_{L(0^+)} \cdot L}{dt} = v_{c(0^+)} \Rightarrow \frac{di_{L(0^+)} - i_{L(0^+)} \cdot L}{dt} = \frac{0}{L} = 0 \text{ Amp/sec (0-L) } \checkmark 1M$$

$$V(0^+) = i_{L(0^+)} \cdot (6) \Rightarrow \text{diff} \Rightarrow$$

$$\frac{dv_{c(0^+)} - i_{c(0^+)} \cdot C}{dt} = \frac{di_{L(0^+)} - i_{L(0^+)} \cdot L}{dt} = 0 \text{ (6)} = 0 \text{ (6)}$$

At Point A (Supply KCL)


$$4 = 4 + \frac{di_{L(0^+)} - i_{L(0^+)} \cdot L}{dt} = 4$$

$$\frac{dv_{c(0^+)} - i_{c(0^+)} \cdot C}{dt} = 0 \text{ Volt/sec} \rightarrow 1M$$

$$\frac{di_{L(0^+)} - i_{L(0^+)} \cdot L}{dt} = 4 \text{ Amp/sec} \rightarrow 1M$$

(7)

Q

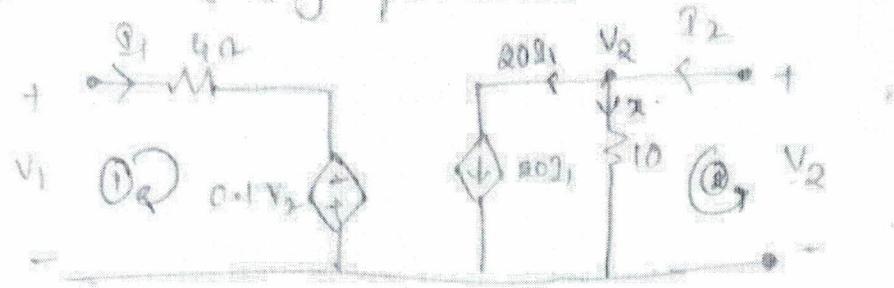 \bar{Z} + \bar{G} - parameters

$$20I_1 + 2 = I_2$$

$$2 = I_2 - 20I_1$$

Apply loop (1)

$$4I_1 - 0.1V_2 - V_1 = 0 \rightarrow (1)$$

loop (2)

$$-V_2 + (I_2 - 20I_1)10 = 0$$

From (1), $V_1 = 4I_1 - 0.1(20I_1 - I_2)$

$$\cancel{V_1 = 4I_1 - 2I_1 + 0.1I_2} \Rightarrow -V_1 = \cancel{2I_1 + 0.1I_2} \rightarrow (3)$$

$$\begin{aligned} V_2 &= 20I_1 - I_2 \rightarrow (2) \\ I_2 &= 20I_1 + \frac{V_2}{10} \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} 1M$$

 \bar{Z} -parameters

$$V_1 = I_1 Z_{11} + I_2 Z_{12}$$

$$V_2 = I_1 Z_{21} + I_2 Z_{22}$$

$$V_2 = -200I_1 + 10I_2 \rightarrow (4)$$

From (1) & (4)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 24 & -10 \\ -200 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

→ 2M

 \bar{g} -parameters

$$g_{11} = g_{11}V_1 + g_{12}I_2$$

$$g_{21} = g_{21}V_1 + g_{22}I_2$$

From (3)

$$V_1 - 0.1I_2 = 2I_1 \rightarrow 0.05$$

$$I_1 = \frac{1}{2}V_1 = \frac{0.1}{2}I_2 \rightarrow (4)$$

$$V_2 = 20I_1 - I_2 \rightarrow (2)$$


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0.5 & -0.05 \\ 20 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \rightarrow 2M$$

From (2) & (3)

$$h = \begin{bmatrix} 4 & -0.1 \\ 20 & 0.1 \end{bmatrix} \Rightarrow g = \begin{bmatrix} \frac{1}{24} & \frac{1}{24} \\ -\frac{25}{3} & \frac{5}{3} \end{bmatrix}$$

(8)

(8)

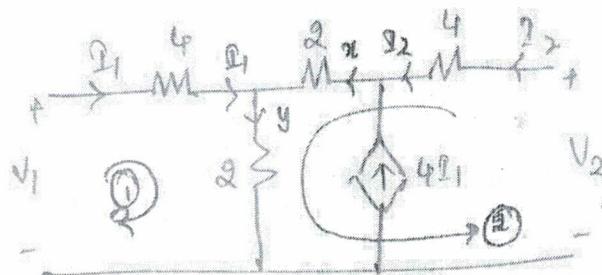

$$I_1 = I_2 + 4I_1, \quad V = I_1 + 2 = I_2 + 5I_1$$

 γ -parameter

loop ①

$$4I_1 + 2(I_2 + 5I_1) - V_1 = 0 \quad \text{---}$$

$$9I_1 + 2I_2 = V_1 \rightarrow \textcircled{2} \rightarrow 0.5V_1$$

$$I_1' = Y_{11}V_1 + Y_{12}V_2$$

$$I_2' = Y_{21}V_1 + Y_{22}V_2$$

loop ②

$$4I_2 + 2(I_2 + 5I_1) + 2(I_2 + 4I_1) = V_2 = 0$$

$$4I_2 + 2I_2 + 8I_1 + 2I_2 + 10I_1 = V_2$$

$$18I_1 + 8I_2 = V_2 \rightarrow \textcircled{3} \rightarrow 0.5V_2$$

$$Z = Y^{-1} \quad \text{or} \quad Y = Z^{-1}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 9 & 2 \\ 18 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Y = Z^{-1} = \begin{bmatrix} 8 & -2 \\ -18 & 9 \end{bmatrix} \cdot \frac{1}{9 \times 8 - 2 \times 18} \cdot \begin{bmatrix} 1 \\ -18 \end{bmatrix} \rightarrow Y_{36}$$

$$Y = \begin{bmatrix} 0.22 & -0.055 \\ -0.5 & 0.25 \end{bmatrix} = \begin{bmatrix} 9/18 & -1/18 \\ -1/2 & 1/4 \end{bmatrix} \rightarrow 2Y$$

 h -parameter

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow \begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

$$\text{from } \textcircled{3} \quad I_2 = \frac{1}{8}V_2 - \frac{18}{8}I_1 \rightarrow \textcircled{4}$$

$$\text{Sub } \textcircled{4} \text{ in } \textcircled{2} \cdot 9I_1 + \frac{2}{8}V_2 - \frac{2}{8} \cdot 18I_1 = V_1 \Rightarrow V_1 = 4.5I_1 + 0.25V_2 \rightarrow \textcircled{5}$$


$$\text{from } \textcircled{5} \quad I_2 = -2.25I_1 + 0.125V_2 \rightarrow \textcircled{6},$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 4.5 & 0.25 \\ -2.25 & 0.125 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \rightarrow 2Y$$

$$\frac{1}{Z_1} \approx \frac{1}{R_{in}}$$

(9)

P-parameters:

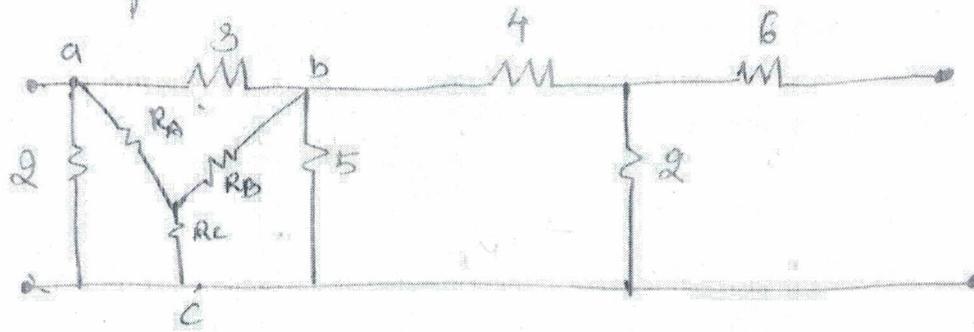

Convert $\Delta(abc)$ to $Y(ABC)$

$$R_A = \frac{3 \times 2}{10} = 0.6 \Omega$$


$$R_B = \frac{15}{10} = 1.5 \Omega$$

$$R_C = \frac{10}{10} = 1 \Omega$$


$Y(ABC)$

0.6

M

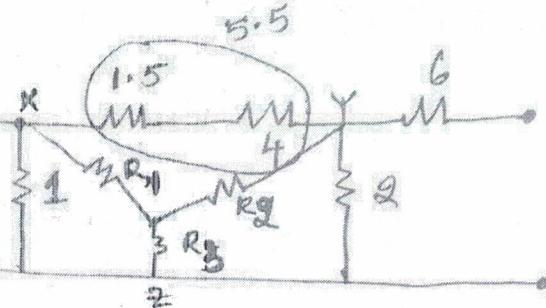

Convert $\Delta Y_Z(A)$ to $Y(123)$

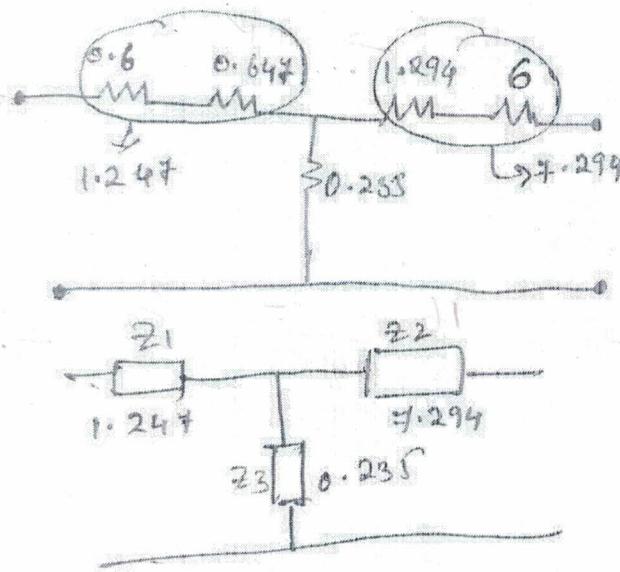

P-parameters

$$V_1 = AV_2 - BV_2 \quad \{ 1 \text{M}$$

$$I_1 = CV_2 - DV_2$$

from (3) sub I_1 in (1)

$$V_1 = 1.482 (4.25) V_2 - (1.482) (32.03) I_2 + 0.235 I_2$$

$$V_1 = 6.306 V_2 - 47.24 I_2 \rightarrow (4)$$

Based on
(3) & (4)

$$\{T\} = \begin{bmatrix} 6.306 & 47.24 \\ 4.25 & 32.03 \end{bmatrix}, \rightarrow 2 \text{M}$$

$$R_1 = \frac{5.5 * 1}{8.5} = 0.64 \Omega$$

$$R_2 = \frac{5.5 * 2}{8.5} = 1.294 \Omega$$

$$R_3 = \frac{1 * 2}{8.5} = 0.235 \Omega$$

$$\begin{aligned} [Z] &= \begin{bmatrix} Z_{11} + Z_{13} & Z_{13} \\ Z_{13} & Z_{22} + Z_{33} \end{bmatrix} \\ [Z] &= \begin{bmatrix} 1.482 & 0.235 \\ 0.235 & 7.529 \end{bmatrix} \rightarrow 2 \text{M} \end{aligned}$$

$$V_1 = 1.482 I_1 + 0.235 I_2 \rightarrow (1)$$

$$V_1 = 1.482 I_1 + 7.529 I_2 \rightarrow (2)$$

$$I_1 = 0.235 I_1 + 7.529 I_2 \rightarrow (3)$$

$$I_1 = \frac{1}{0.235} V_2 - \frac{7.529}{0.235} I_2$$

$$I_1 = 4.25 V_2 - 32.03 I_2 \rightarrow (3)$$

$$V_1 = 6.306 V_2 - 47.24 I_2 \rightarrow (4)$$

$$(10) \quad I_s(t) = 2 + \frac{16}{\pi^2} \sum_{n=1}^{\infty} \frac{1}{n^2} \cos nt, \quad n = 2K-1$$

$$i(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

$$a_0 = 2, \quad a_n = -\frac{16}{\pi^2 n^2}, \quad \omega_0 = n\omega_0 \rightarrow 1M$$

$$|A_n| = \sqrt{a_n^2 + b_n^2}, \quad \phi_n = -\tan^{-1}(\frac{b_n}{a_n})$$

$$|A_n| = \frac{16}{\pi^2 n^2}, \quad \phi_n = -\tan^{-1}(\frac{b_n}{a_n}) = 0$$

$$I_s(\omega) = |I_s(\omega)| \underline{|A_n|} = \frac{16}{\pi^2 n^2} (10)$$

From circuit find $I(s)$. (For AC Supply).

Current division rule.

$$I(s) = \frac{I_s(s) + 1}{1 + 2 + 2s} = \frac{1}{2 + 2 + 2s} I_s(s) \rightarrow 1M$$

$$I(s) = \frac{1}{\sqrt{9 + 4s^2}} -\tan^{-1}\left(\frac{2s}{3}\right) + \frac{16}{\pi^2 n^2} 10$$

$$I(s) = \frac{1}{2\sqrt{1+4s^2}} + \frac{16}{\pi^2 n^2} -\tan^{-1}\left(\frac{2s}{3}\right) = \frac{16}{\pi^2 n^2 \sqrt{9 + 4s^2}} -\tan^{-1}\left(\frac{2s}{3}\right) \quad \text{Ans} \rightarrow 1M$$

For DC Supply.

$$V_s = 2 \quad \begin{array}{c} M \\ | \\ 2 \\ | \\ 1 \end{array} \quad i(t) \Rightarrow I_{DC}(s) = \frac{2+1}{2+1} = \frac{2}{3} = 0.66 \text{ Amp} \rightarrow 1M$$

$\rightarrow 1M$


Amplitude + phase form:

$$i(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(n\omega_0 t + \phi_n)$$

$$i(t) = 0.66 + \sum_{n=1}^{\infty} \frac{8}{\pi^2 n^2 \sqrt{1+w_n^2}} \cos(nt + \tan^{-1}(w_n))$$

$$n = 2K-1$$

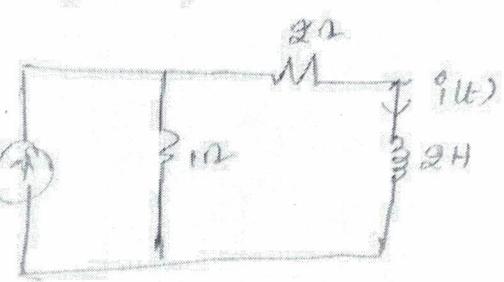
$$i(t) = 0.66 + \sum_{n=1}^{\infty} \frac{16}{\pi^2 n^2 \sqrt{9+4n^2}} \cos(nt + \tan^{-1}\frac{2}{3}) \rightarrow 2M$$



$$\begin{aligned} L &\rightarrow sL = 2S \\ R &\rightarrow R \\ P(t) &\rightarrow 2(s) \rightarrow 2W \\ Q(t) &\rightarrow 2(s) \end{aligned}$$

Evaluate the $H(s) = \frac{V_o(s)}{V_s(s)}$
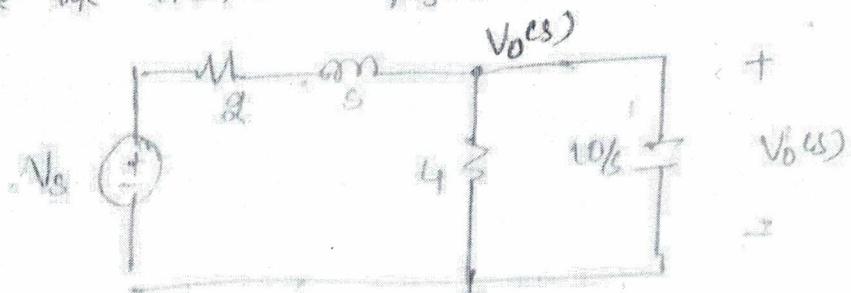
$$\begin{aligned} L &\rightarrow sL \\ C &\rightarrow \frac{1}{sC} \\ R &\rightarrow R \\ V_s &\rightarrow \frac{V_s(s)}{s} \\ V_o &\rightarrow V_o(s) \end{aligned}$$



using nodal analysis

$$\frac{V_o(s) - V_s(s)}{s+5} + \frac{V_o(s)}{4} + \frac{V_o(s)}{10s} = 0$$

$$40V_o(s) - 40V_s(s) + 10(2+s)V_o(s) + V_o(s)s(2+s)4 = 0$$

$$40V_o(s) + (20 + 10s)V_o(s) + (8s + 4s^2)V_o(s) = 40V_s(s)$$

$$(40 + 20 + 10s + 8s + 4s^2)V_o(s) = 40V_s(s)$$

$$\frac{V_o(s)}{V_s(s)} = \frac{40}{4s^2 + 18s + 60} = \frac{20}{2s^2 + 9s + 30}$$

$$H(s) = \frac{V_o(s)}{V_s(s)} = \frac{20}{2s^2 + 9s + 30} \quad \rightarrow 1M$$

$$s = j\omega \quad H(j\omega) = \frac{20}{2(j\omega)^2 + 9(j\omega) + 30} = \frac{20}{(30 - 2\omega^2) + j9\omega}$$

$$|H(j\omega)| = \frac{20}{\sqrt{(30 - 2\omega^2)^2 + (9\omega)^2}}$$

$$|H(0)| = \frac{20}{\sqrt{(30)^2}} = \frac{20}{30} = \frac{2}{3} = 0.66 \approx 0 \quad \left. \right\} 1M$$

$$|H(\infty)| = \frac{20}{\sqrt{(30 - \infty)^2 + 9(\infty)^2}} = 0$$

Filter is Band pass

$\rightarrow 1M$

$$1 = \frac{20^2}{(30 - 2\omega_c^2)^2 + (9\omega_c)^2} \Rightarrow 30^2 - 700 + 4\omega_c^4 + 100\omega_c^2 + 81\omega_c^2 = 400$$

$$4\omega_c^4 - 39\omega_c^2 + 500 = 0$$

$$\omega_c^2 = 9.818 \pm 10.86j$$