
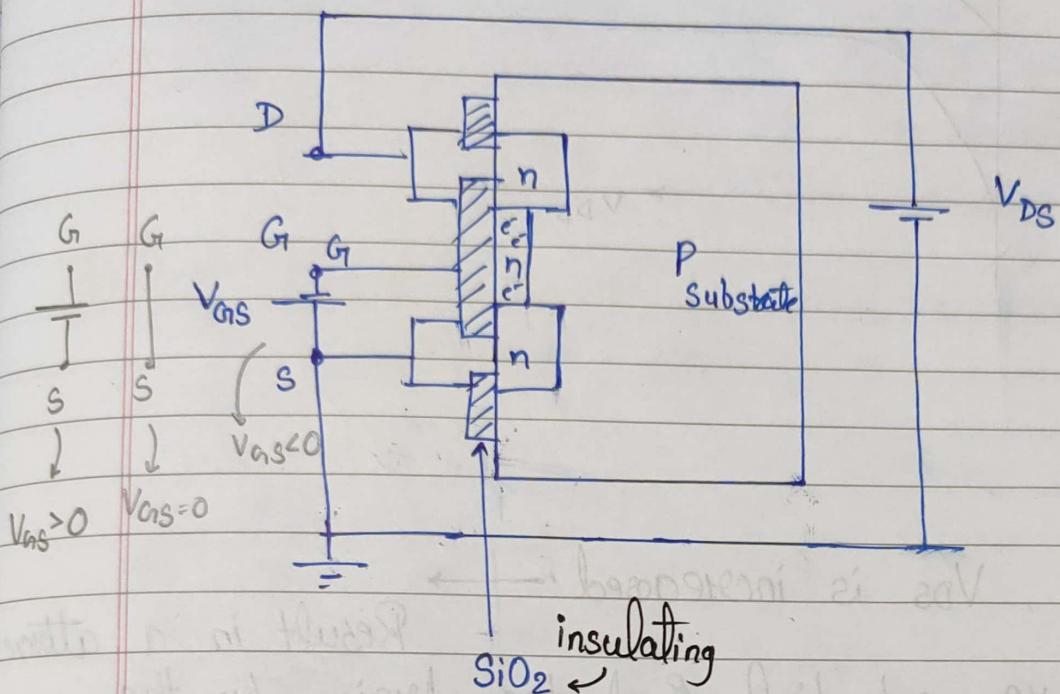


Depletion Type MOSFET \Rightarrow

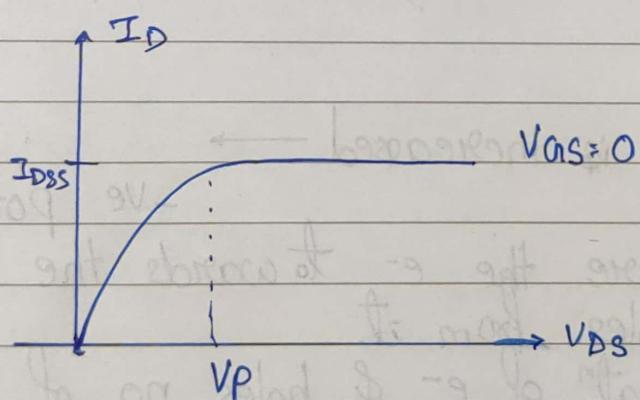
Metal oxide semiconductor
Field effect transistor



Case-1) $V_{GS} = 0 \text{ V}$




Deplet Region

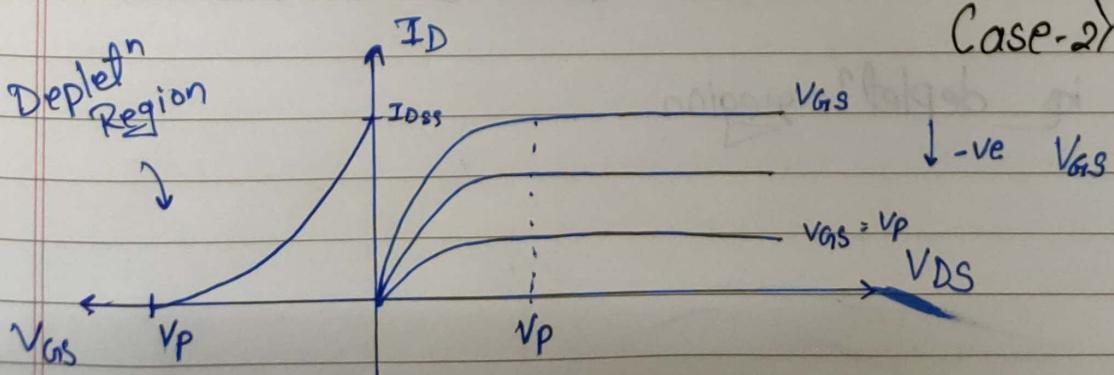

Case-2) $V_{GS} < 0 \text{ V}$

Case-3) $V_{GS} > 0V$

I_D inc. rapidly
Enhancement

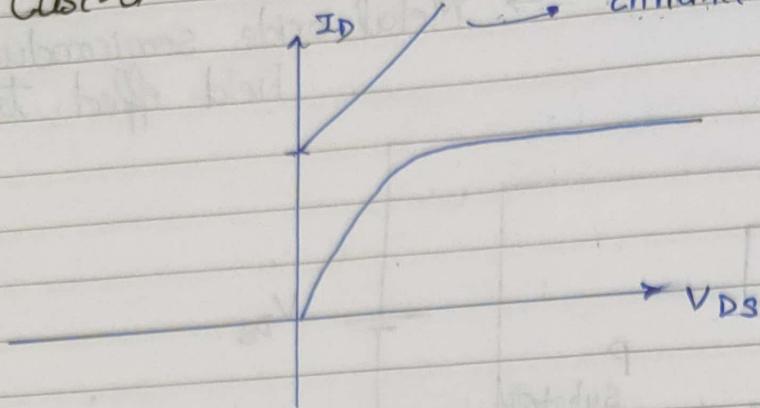

i) $V_{GS} = 0V$, V_{DS} is increased →

Result in a attraction of free electrons of n-channel and current flows similar to J-FET

ii) $V_{GS} < 0V$, V_{DS} is increased →

-ve potential at gate will pressure the e- towards the substrate & attract holes from it.

Due to recombination of e- & holes no. of free carriers will reduce so I_D is reduced.

This is depletion region.

i) $V_{GS} > 0V$, V_{DS} inc. \rightarrow

This is at the Enhancement region of the +ve depletion type MOSFET. The +ve potential will attract e^- and establish new carriers due to accelerating particle. So the current increases rapidly.

ii) Shockley's eqn is valid in both Deplet'n & Enhancement region.

i) $I_D = I_S$

ii) $I_G = 0$

iii) $V_{DS} = V_P \Rightarrow I_D = I_{DSS}$


iv) $V_{GS} = V_P \Rightarrow I_D = 0$

v) $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$

Que.) Sketch the transfer Curve for n-channel depletion type MOSFET having $I_{DSS} = 12 \text{ mA}$ $V_p = -6 \text{ V}$.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$
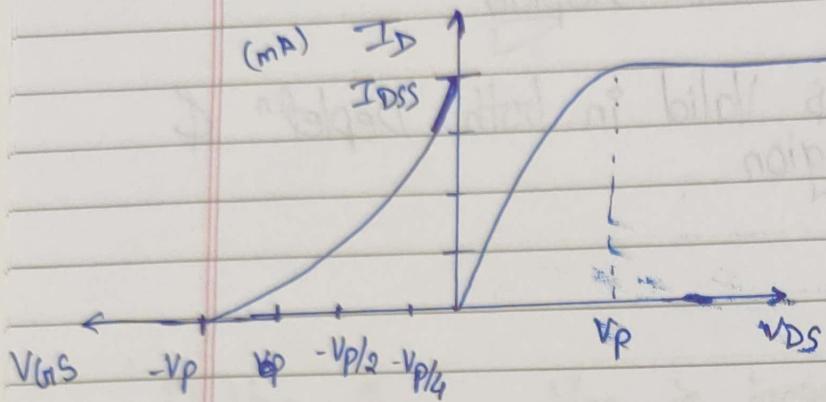
$$\boxed{V_{GS} = V_p} \quad \text{Depletion}$$



$$\text{i)} V_{GS} = V_p$$

$$I_D = 0$$

$$\text{ii)} V_{GS} = V_p/2$$

$$I_D = 3 \text{ mA}$$

$$\text{iii)} V_{GS} = V_p/4$$

$$I_D = \frac{9}{4} \text{ mA}$$

④ Enhancement \rightarrow

$$V_{GS} = -\frac{V_p}{2} = +3 \text{ V}$$

$$\text{i)} V_{GS} = V_p$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

Shockley's Egn is not valid


classmate

Date _____

Page _____

Enhancement Type MOSFET \Rightarrow

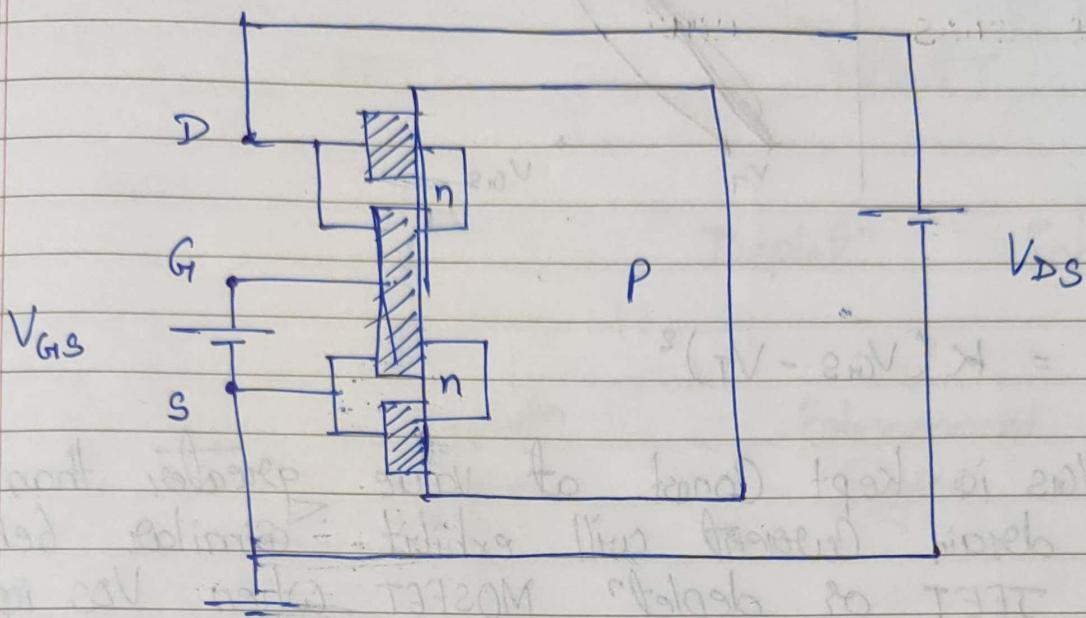There is only
Enhancement
Region &
No Deplet
Region.



Case-1) $V_{GS} = 0$ v, V_{DS} is increased \rightarrow

n-channel makes $I_D = 0$.

Absence of


Case-2) $V_{GS} > 0$ v, V_{DS} is inc. \rightarrow

e⁻ from Substrate. but

If will attract



- Both Gate & drain are +ve w.r.t. Source, +ve potential at Gate will repel holes & attract e⁻. When V_{GS} reaches V_T (Threshold Voltage). Then Current is established in FET
- Channel is enhanced by +ve Gate to Source.
- Once V_{GS} inc. beyond V_T , current I_D will inc.

11/Oct/24

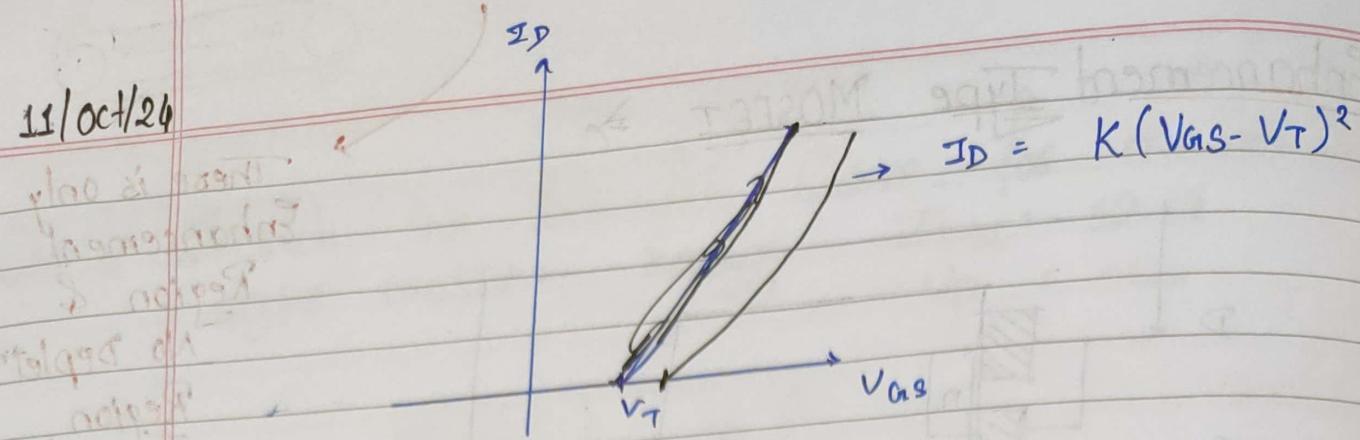

$$I_D = K(V_{GS} - V_T)^2$$

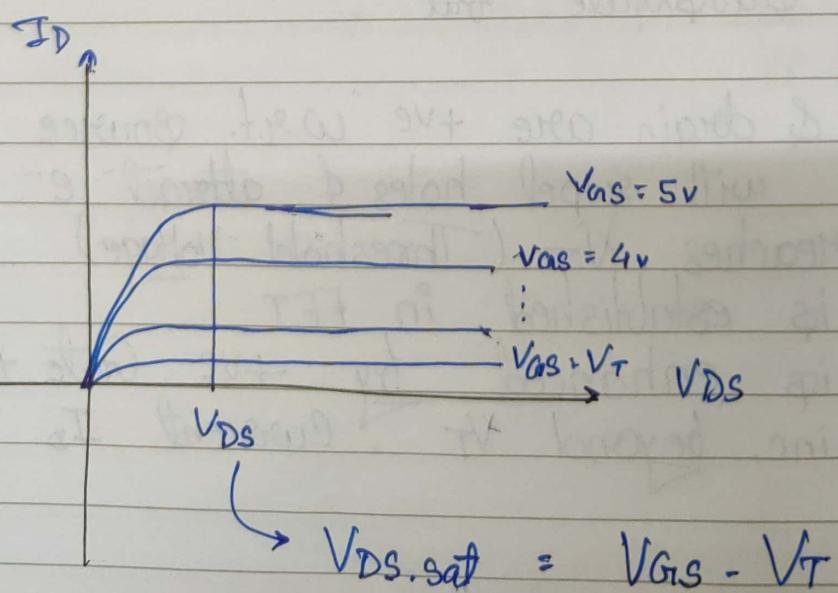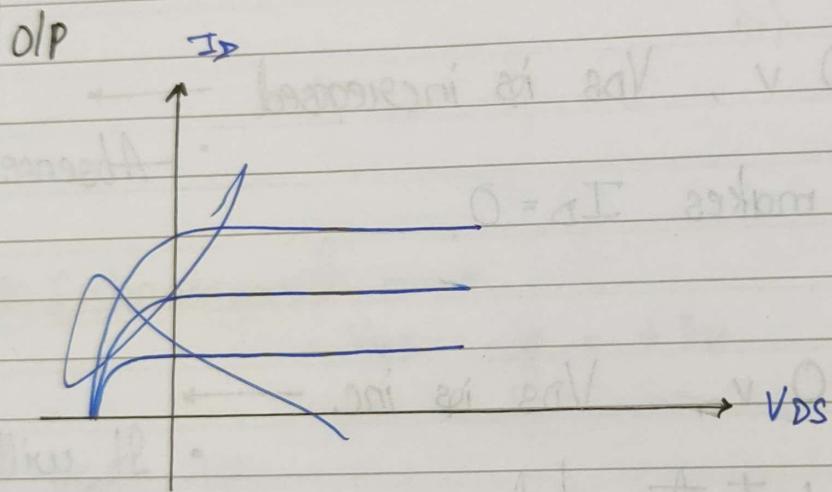- If V_{GS} is kept Const. at value greater than V_T , The drain current will exhibit similar behaviour as JFET or depletion MOSFET when V_{DS} is inc.



n-channel

P-channel

JFET

FET

MOSFET


Depletⁿ

Enhancement

Depletⁿ
RegionEnhancement
RegionOnly enhancement
Region


DC Biasing of FET \Rightarrow

i) Fixed Bias Configuration \rightarrow

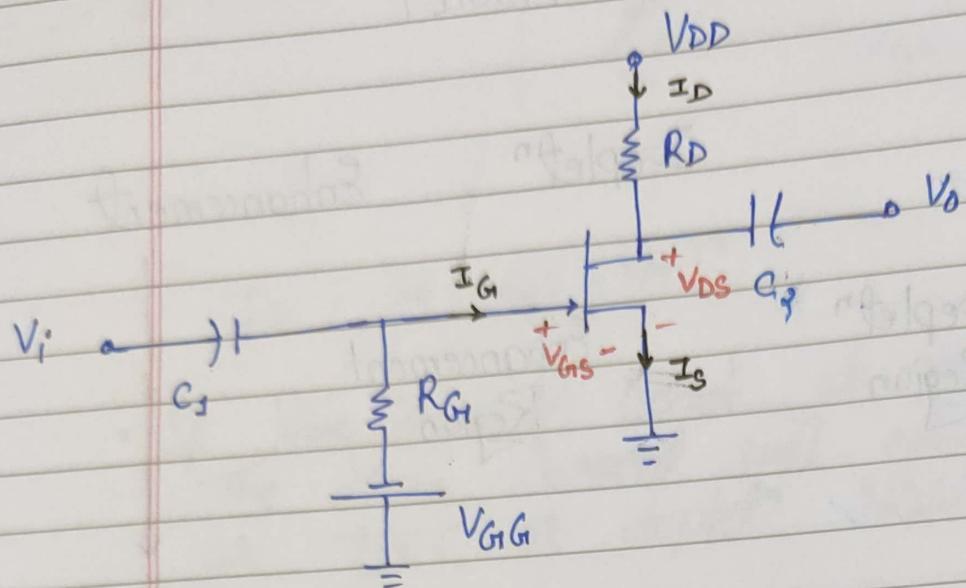

i) DC Equivalent Circuit \Rightarrow

$$f = 0 \\ X_C = \infty$$

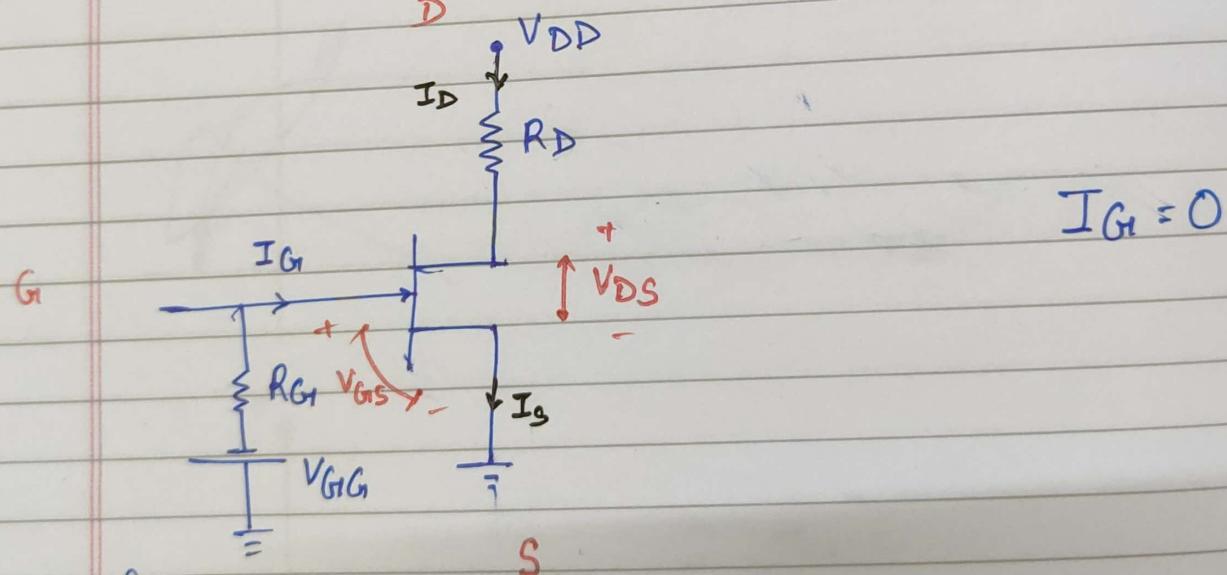

KVL \rightarrow for DS Loop \Rightarrow

$$V_{DD} - I_D R_D - V_{DS} = 0 \quad \text{--- (1)}$$

for G_S loop $\Rightarrow 0$

$$-V_{GIG} - I_G R_{GS} - V_{GS} = 0 \quad \text{--- (2)}$$

$$\boxed{V_{GS} = -V_{GIG}}$$

$\hookrightarrow V_{GSQ}$

QW

$$\textcircled{i} \quad V_{GS} \checkmark$$

$$\textcircled{ii} \quad I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2 \checkmark$$

$$\textcircled{iii} \quad V_{DS} = V_{DD} - I_D R_D \checkmark$$

I_{DSS}, V_p (Given)

Ques. 1) In a fixed bias configuration $V_{DD} = 16V$, $V_{GG} = 2V$
 $R_D = 2k\Omega$, $R_G = 1M\Omega$, $I_{DSS} = 10mA$, $V_p = -8V$.
 Calculate $\textcircled{i} V_{GS_Q}$ $\textcircled{ii} I_{DQ}$ $\textcircled{iii} V_{DSQ}$ $\textcircled{iv} V_S$
 $\textcircled{v} V_{G1}$ $\textcircled{vi} V_D$

⇒

$$V_S = 0V$$

$$I_{G1} = 0$$

$$V_{G1S} = -V_{GG} \Rightarrow V_{GS_Q} = -2V$$

$$\textcircled{ii} \quad I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2 = 10 \left(1 - \frac{(-2)}{(-8)} \right)^2 = 10 \times \frac{9}{16}$$

$$I_D = \frac{45}{8} mA$$

$$\boxed{\textcircled{ii} \quad I_{DQ} = 5.625 mA}$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$\boxed{\textcircled{iii} \quad V_{DSQ} = 4.75V}$$

$$V_{DS} = V_D - V_S$$

$$\boxed{V_D = V_{DS} = 4.75V}$$


$$V_{G1} = V_{GS} = -2V$$

$$\boxed{V_{G1} = V_{GS} = -2V}$$

14/0ct/24


CLASSMATE
Date _____
Page _____

2) Self Bias Configuration

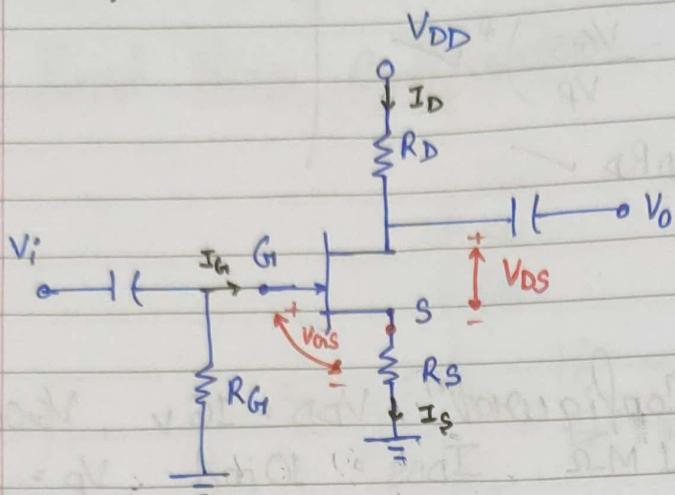

DC Equivalent ckt \Rightarrow

$$I_{Gt} = 0$$

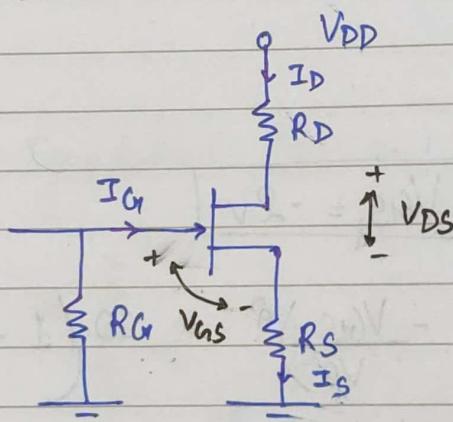

i) KVL in DS loop \rightarrow

$$V_{DD} - I_D R_D - V_{DS} - I_S R_S = 0$$

$$V_{DS} = V_{DD} - I_D R_D - I_S R_S$$


ii) KVL in GIS loop \rightarrow

$$-V_{GIS} - I_S R_S = 0$$

$$V_{GIS} = -I_S R_S$$

iii) \checkmark $I_D = I_{DSS} \left(1 - \frac{V_{GIS}}{V_P} \right)^2$

\checkmark $V_{GIS} = -I_D R_S$

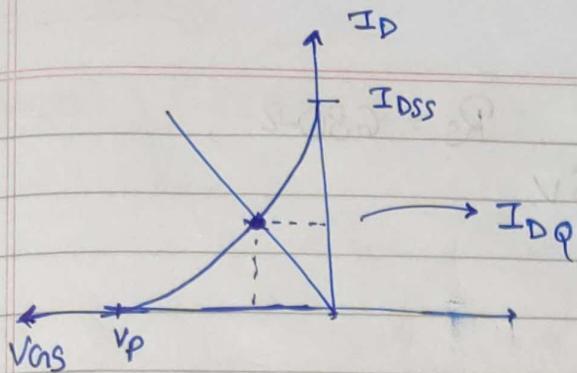

$\checkmark \boxed{V_{DS} = V_{DD} - I_D(R_D + R_S)}$

Que.) For a self bias config. $V_{DD} = 20V$, $R_D = 3.3k\Omega$, $R_S = 1k\Omega$,
 $R_G = 1M\Omega$, $I_{DSS} = 8mA$, $V_P = -6V$.

\Rightarrow

$\rightarrow V_{G_S} = -I_S R_S = -I_D R_S$

$$I_D = I_{DSS} \left(1 - \frac{V_{G_S}}{V_P} \right)^2 = I_{DSS} \left(1 + \frac{I_D R_S}{(-6)} \right)^2$$

$$I_D = 8 \left(1 - \frac{10^3 I_D}{6} \right)^2 \Rightarrow I_D = 5.83 \times 10^{-3}$$

$$I_D = 2.587 \text{ mA}, 13.9 \text{ mA}$$

$$I_{DSS} = 8 \text{ mA} \Rightarrow I_D = 2.587 \text{ mA} \checkmark$$

$\boxed{V_{G_S} = -2.587 \text{ V}}$

$$V_{DS} = 20 - 2.587 \times 3.3 - 2.587 \times 1$$

$\boxed{V_{DS} = 8.876 \text{ V}}$

$$V_{DS} = V_D - V_S \Rightarrow \boxed{V_D = 11.468 \text{ V}} \checkmark$$

$$V_D = 11.46 \text{ V}$$

$$V_S = +I_D R_S$$

$\boxed{V_S = +2.587 \text{ V}} \checkmark$

$$V_{G_S} = V_G - V_S$$

$$V_G = -5.174 \text{ V} \checkmark$$

Self Bias

Q. 2) $V_{DD} = 12V$, $R_D = 1.5k\Omega$, $R_S = 680\Omega$,
 $I_{DSS} = 12mA$, $V_P = -6V$

$$\Rightarrow V_{GS} = -I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 12 \times 10^{-3} \left(1 - \frac{680}{6} \frac{I_D}{10^3} \right)^2$$

$$I_D = 3.83 \times 10^{-3} mA, 20.29 mA$$

$$I_{DSS} \quad I_D < I_{DSS} \Rightarrow I_D = 3.83 mA$$

$$V_{GS} = -2.6 V$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_{DS} = 3.65 V$$

$$V_S = I_D R_S$$

$$V_S = 2.6 V$$

$$V_S = -I_D R_S$$

$$V_S = -2.6 V$$

$$V_{DS} = V_D - V_S$$

$$V_D = 1.05 V$$

$$V_{GS} = V_G - V_S$$


$$V_G = V_{GS} + V_S$$

$$V_{DS} = V_D - V_S$$

$$V_D = V_{DS} + V_S$$

$$V_D = 6.25 V$$

Ques #1 Voltage Divider Bias

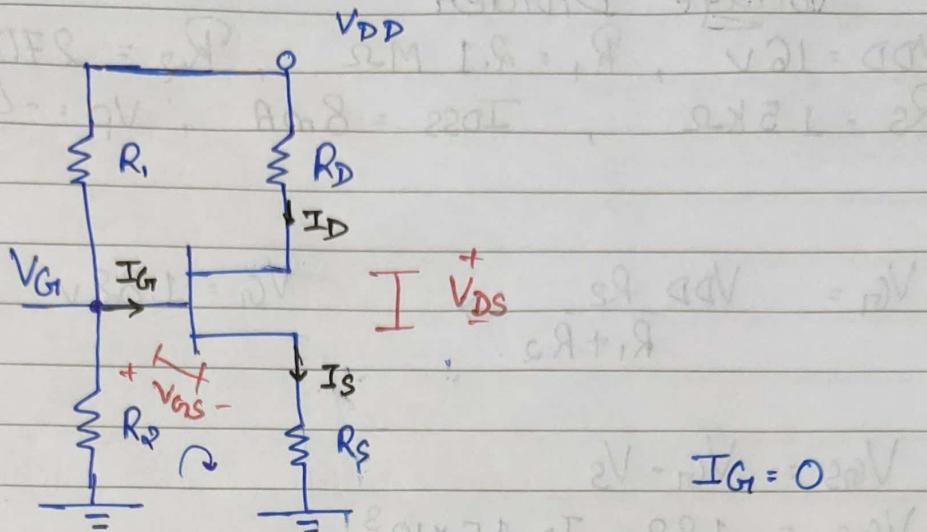

i) DC Equivalent ckt

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$$

ii) KVL in G-S loop \Rightarrow

$$V_{GS} = V_G - V_S$$

$$V_{GS} = \frac{V_{DD} R_2}{R_1 + R_2} - I_D R_S$$

iii) $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$

iv) KVL in DS loop \Rightarrow

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

Que.1)

Voltage Divider

$$V_{DD} = 16V, R_1 = 2.1M\Omega, R_2 = 270k\Omega, R_D = 2.4k\Omega$$
$$R_S = 1.5k\Omega, I_{DSS} = 8mA, V_P = -4V$$

⇒

$$V_{G1} = \frac{V_{DD} R_2}{R_1 + R_2} \Rightarrow$$

$$V_{G1} = 1.82V$$

$$V_{GS} = V_{G1} - V_S$$

$$V_{GS} = 1.82 - I_D 1.5 \times 10^3$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 8 \times 10^{-3} \left(1 + \frac{1.82 - I_D \times 1.5 \times 10^3}{4} \right)^2$$

$$I_D = 6.23mA, 2.414mA$$


Both values are less than I_{DSS}

$$V_{GS} = 1.82 - I_D (1.5 \times 10^3)$$

$$I_D = 0 \Rightarrow V_{GS} = 1.82$$

$$V_{GS} = 0 \Rightarrow I_D = 0.0012$$

Use Graphical method to select I_D

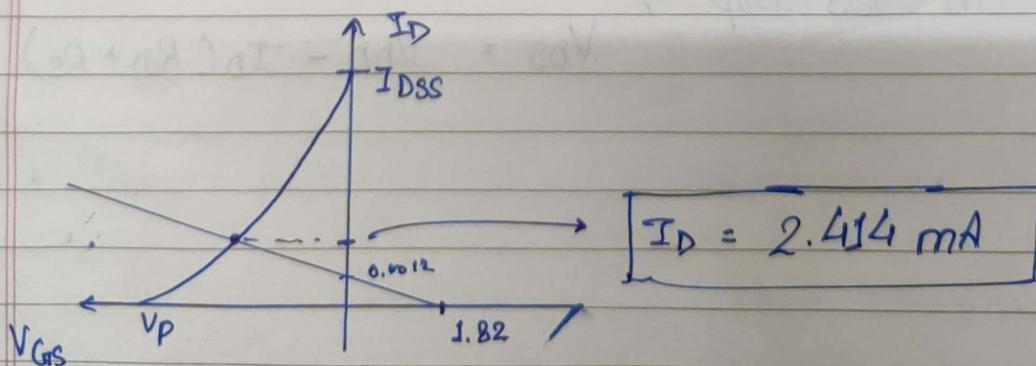

$$V_{GS} = 1.82 - 2.414 \times 1.5$$

$$\boxed{V_{GS} = -1.801 \text{ V}}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$\boxed{V_{DS} = 6.58 \text{ V}}$$

$$V_S = I_D R_S$$

$$\boxed{V_S = 3.621 \text{ V}}$$

$$V_{GS} = 1.82 - 2.414 \times 1.5$$

$$V_S = I_D R_S$$


$$V_{GS} = -1.801 V$$

$$V_S = 3.621 V$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$V_{DS} = 6.58 V$$

Ques. 2)

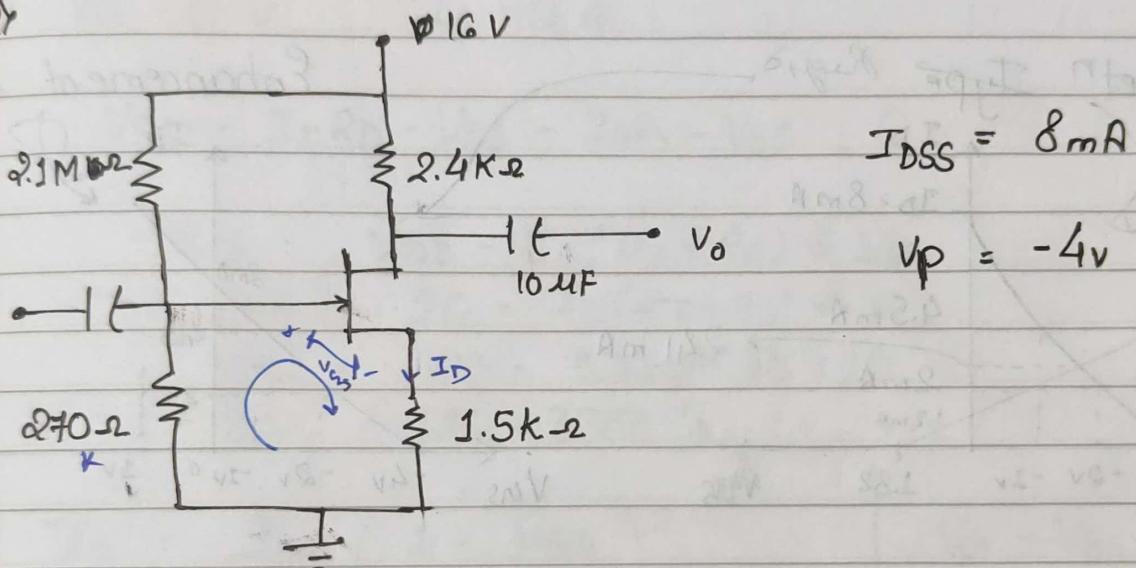

$$V_G = V_{DD} \frac{R_2}{R_2 + R_1} = \frac{16 \times 270 \times 10^3}{270 \times 10^3 + 2.1 \times 10^6} = 2.05 \times 10^{-3} V = 1.82 V$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = 2.05 \times 10^{-3} - I_D \times 1.5 \times 10^3$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 8 \times 10^{-3} \left(1 + \frac{1.82 V}{4} \right)^2$$


$$I_D = 6.23 \text{ mA}, 2.414 \text{ mA}$$

$$\text{then } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

i) $V_{GS} = -1 \Rightarrow I_D = 8 \times 10^3 \left(1 - \frac{(-1)}{(-4)}\right)^2 = 4.5 \text{ mA}$

ii) $V_{GS} = -2 \Rightarrow I_D = 2 \text{ mA}$

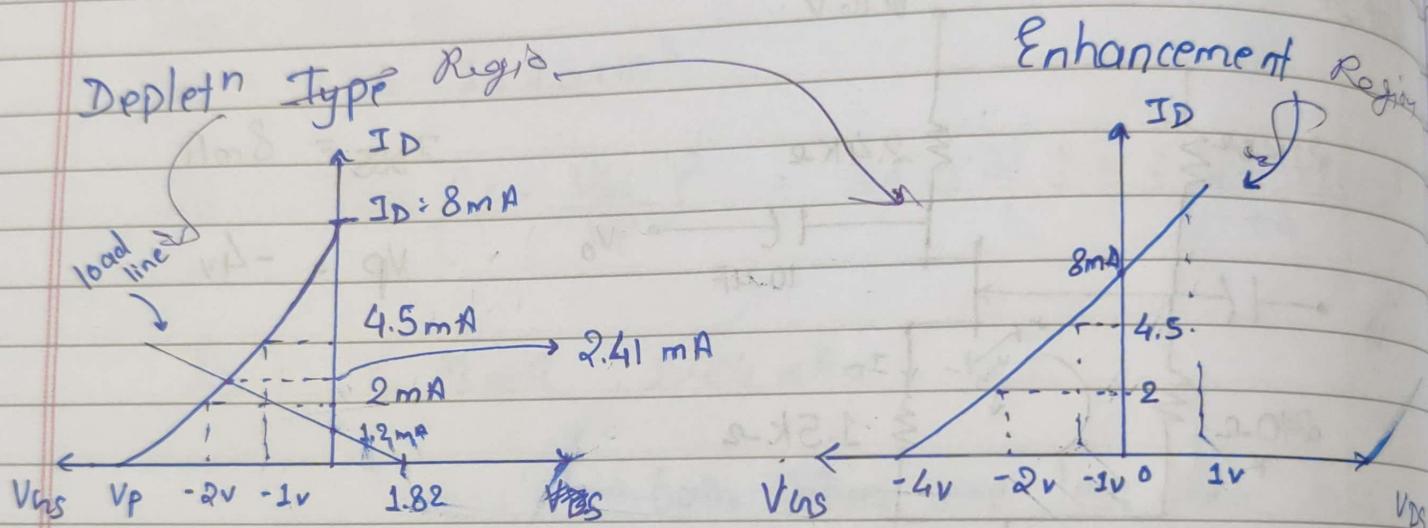iii) $V_{GS} = 1 \Rightarrow I_D = 12.5 \text{ mA}$




$$I_{DQ} = 2.41 \text{ mA}$$

$$V_{GSIQ} = V_G - V_S = 1.82 - 2.41 \times 1.5$$

$$V_{GSIQ} = -1.795 \text{ V}$$

Question

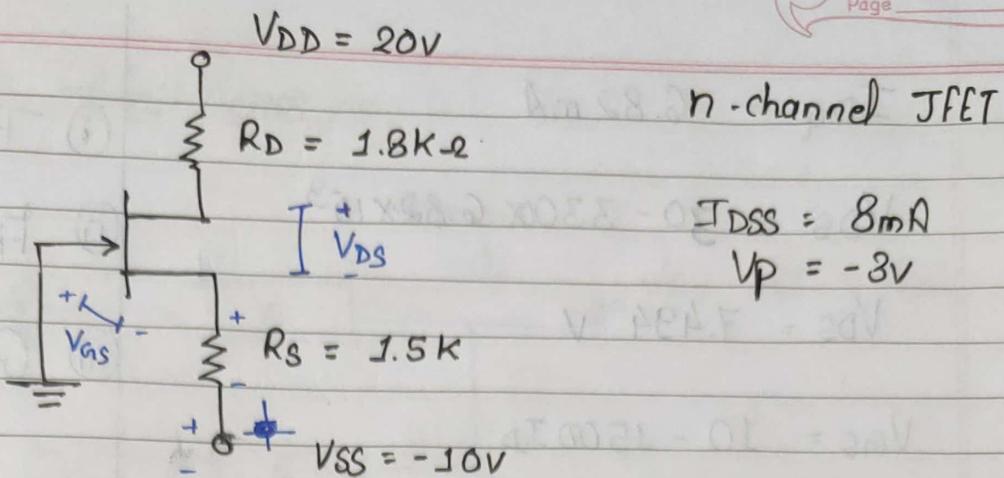

$$I_{DSS} = 8mA$$

$$V_P = -8V$$

⇒

$$V_G = 0V \quad , \quad I_G = 0A$$

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S - V_{SS} = 0$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) - V_{SS}$$

$$V_{DS} = 20 - I_D (1.8k\Omega + 1.5k\Omega) - 10$$

$$V_{DS} = 20 - 3.3 \times 10^3 I_D + 10$$

$$V_{DS} = 30 - 3300 I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_G - V_{GS} - I_D R_S - V_{SS} = 0$$

$$V_{GS} = -(V_{SS} + I_D R_S)$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{GS} = -(-10 + I_D \times 1500)$$

$$V_{GS} = 10 - 1500 I_D$$

$$I_D = 8 \times 10^{-3} \left(1 - \frac{10 - 1500 I_D}{-3} \right)^2$$

$$I_D = 6.82mA, 11.01mA$$


$$I_{DQ} = 6.82 \text{ mA}$$

$$V_{DS} = 30 - 3300 \times 6.82 \times 10^{-3}$$

$$V_{DS} = 7.494 \text{ V}$$

$$V_{GS} = 10 - 1500 I_D$$

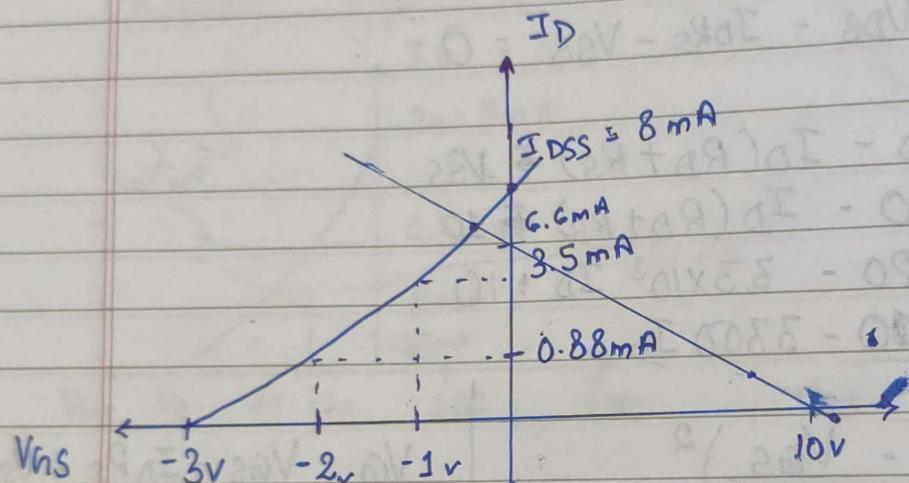
$$\begin{aligned} \text{For } I_D = 0 &\Rightarrow V_{GS} = 10 \text{ V} \\ V_{GS} = 0 &\Rightarrow I_D = 6.6 \text{ mA} \end{aligned}$$



V_{GS}

$$I_D = 8 \left(1 - \frac{V_{GS}}{(-3)} \right)^2$$

#) Feedback Amplifiers

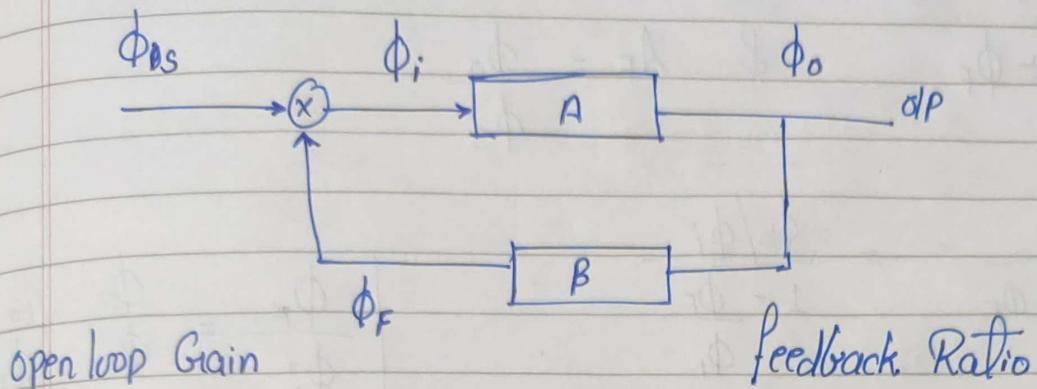

\hookrightarrow A : Gain of Basic Amp.
B : feedback Ratio

$$B = \frac{\Phi_F}{\Phi_o}$$

Φ_s : Source Signal

Φ_F : Feedback Signal

Φ_i : Input Signal to the Amp.

$$A_F = \frac{\Phi_o}{\Phi_s}$$

$$A = \frac{\Phi_o}{\Phi_i}$$

Overall
Gain

AC Oscillator

★ Positive Feedback (Regenerative feedback) :-

$$\phi_i = \phi_s + \phi_f \quad \& \quad A_F = -\frac{\phi_o}{\phi_s}$$

$$A_F = \frac{\phi_o}{\phi_i - \phi_f} = \frac{\phi_o / \phi_i}{1 - \frac{\phi_f}{\phi_i}}$$

$$\left[\frac{\phi_f}{\phi_i} = \frac{\phi_f}{\phi_o} \cdot \frac{\phi_o}{\phi_i} \right]$$

$$A_F = \frac{A}{1 - \frac{\phi_f}{\phi_i}}$$

$$A_F = \frac{A}{1 - BA}$$

✓ $|A| < |A_F|$

A_F → Closed loop Gain

→ Disadvantage :-

Amplify noise also

Degenerative feedback

classmate
Date _____
Page _____
18/0ct/24

★ -ve Feedback \Rightarrow

$$\phi_i = \phi_s - \phi_f \quad \& \quad A_F = \frac{\phi_o}{\phi_s}$$

$$A_F = \frac{\phi_o}{\phi_i + \phi_f} = \frac{\phi_o / \phi_i}{1 + \phi_f / \phi_i}$$

$$A_F = \frac{A}{1 + \frac{\phi_f}{\phi_i}}$$

$$\frac{\phi_f}{\phi_i} = \frac{\phi_f}{\phi_o} \cdot \frac{\phi_o}{\phi_i}$$

\downarrow \downarrow
 B A

$$A_F = \frac{A}{1 + AB}$$

(AB)

$$|A_F| < |A|$$

Highly stable than +ve F.B.

Effect of -ve F.B. \downarrow

$$A_F = \frac{A}{1 + AB}$$

$$\frac{\partial A_F}{\partial A} = \frac{(1+AB) - BA}{(1+AB)^2} = \frac{1}{(1+AB)^2}$$

$$\frac{dA_F}{dA} = \frac{1}{(1+AB)^2} \times \frac{A_F}{A_F}$$

Amplifier with feedback

$$\frac{dA_F}{A_F} = \frac{1}{(1+AB)^2} \times \frac{dA}{A_F}$$

$$\frac{dA_F}{A_F} = \frac{(1+AB)}{(1+AB)^2} \times \frac{dA}{A}$$

★ $\frac{dA_F}{A_F} = \frac{1}{(1+AB)} \cdot \frac{dA}{A}$

fractional change in Gain of the Amp. with feedback


$$\frac{dA}{A} = \text{---} \rightarrow \text{without feedback}$$

$$K = \frac{1}{1+AB} < 1, K < 1$$

$$\frac{dA_F}{A_F} = K \frac{dA}{A}$$

$$\frac{1}{1+AB} \rightarrow \text{Sensitivity}$$

Depletion MOSFET \rightarrow

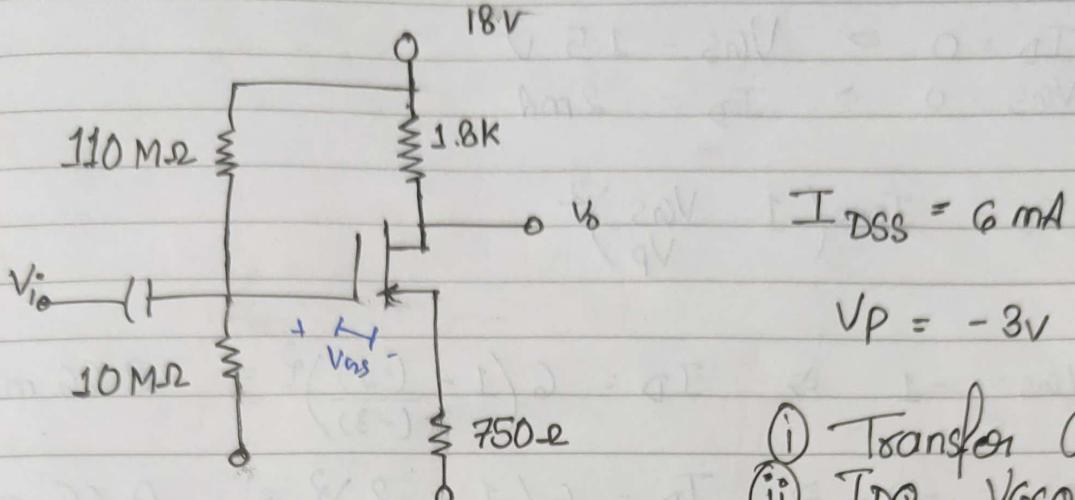

- i Transfer Curve
- ii I_{DQ} , V_{GSQ} , V_{DS}
- iii Verify Graphically.

$$\Rightarrow I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$V_G = V_{DD} \frac{R_2}{R_2 + R_1} = 18 \times \frac{10}{110 + 10} = 1.5$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = V_G - I_{DRS} \cdot 750 = 1.5 - I_D \cdot 750$$

$$I_D = 6 \times 10^{-3} \left(1 - \frac{1.5 - 750 I_D}{-3} \right)^2$$

$$I_D = 3.117 \text{ mA}, 11.5 \text{ mA}$$

V_{GS}

$$V_{GS} = 1.5 - I_D(750)$$

$$I_D = 0 \Rightarrow V_{GS} = 1.5 \text{ V}$$


$$V_{GS} = 0 \Rightarrow I_D = 2 \text{ mA}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$V_{GS} = -1 \Rightarrow I_D = 6 \left(1 - \frac{(-1)}{(-3)} \right)^2 = 2.66 \text{ mA}$$

$$V_{GS} = -2 \Rightarrow I_D = 6 \left(1 - \frac{2}{3} \right)^2 = 0.66 \text{ mA}$$
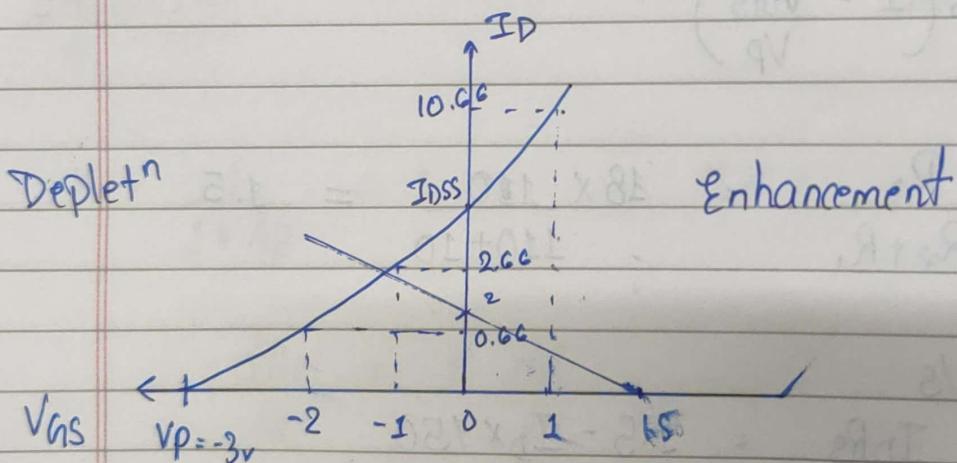
$$V_{GS} = 1 \Rightarrow I_D = 6 \left(1 + \frac{1}{3} \right)^2 = 10.66 \text{ mA}$$



$$I_{DQ} = 3.117 \text{ mA}$$

$$V_{GSQ} = 1.5 - 3.117 \times 10^{-3} \times 750$$

$$V_{GSQ} = -0.8325 \text{ V}$$


$$V_{DS} = 18 - 1.8 \times 10^3 I_D \quad V_{DS} - I_D R_S = 0$$

$$V_{DS} = 18 - 1.8 \times 10^3 (3.117)$$

$$V_{DS} = 18 - I_D (R_D + R_S)$$

$$V_{DS} = 10.05 \text{ V}$$

Ques.2


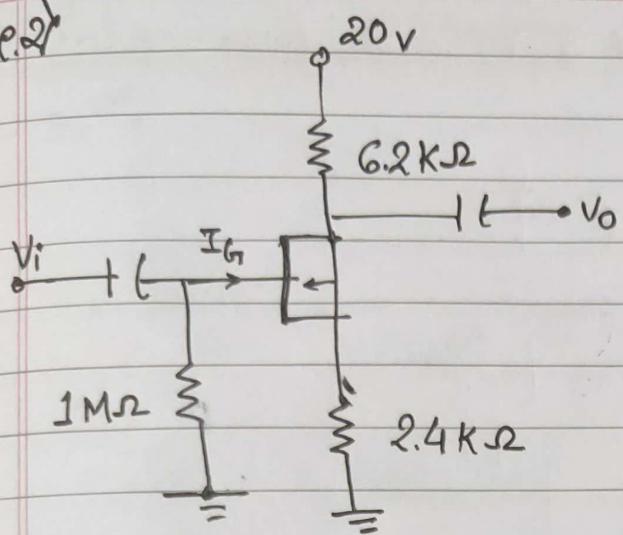


$$I_{DSS} = 8mA$$

$$V_P = -8V$$

$$Ct_9 + V$$

Enhancement MOSFET \Rightarrow

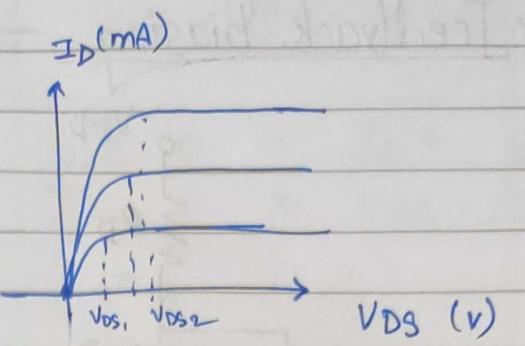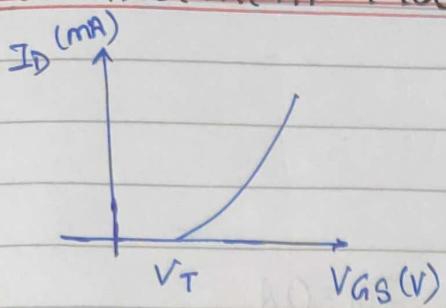

$$I_D = K (V_{GS} - V_T)^2$$

$$V_{DS,sat} = V_{GS} - V_T$$

Q.1) Draw a transfer Curve for n-channel Enhancement type MOSFET

$$V_T = 3V$$

$$I_{D(on)} = 6 \text{ mA}$$

$$V_{GS(on)} = +8V$$

\Rightarrow

$$I_D = K (V_{GS} - V_T)^2$$

$$6 \times 10^{-3} = K (8 - 3)^2$$



$$K = \frac{6 \times 10^{-3}}{25} \Rightarrow K = 2.4 \times 10^{-4} \text{ A/V}^2$$

$$K = 0.24 \text{ mA/V}^2$$


$$I_D = 0.24 (V_{GS} - 3)^2$$

$$V_{GS} = 4 \Rightarrow I_D = 0.24 \text{ mA}$$

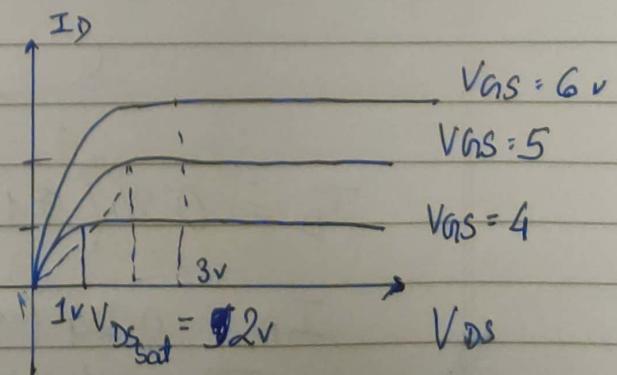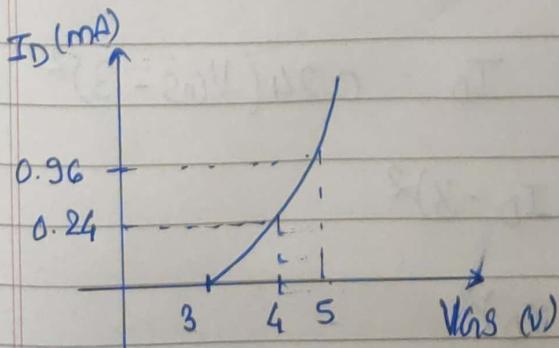
$$V_{GS} = 5 \Rightarrow I_D = 0.96 \text{ mA}$$



★ Feedback Biasing

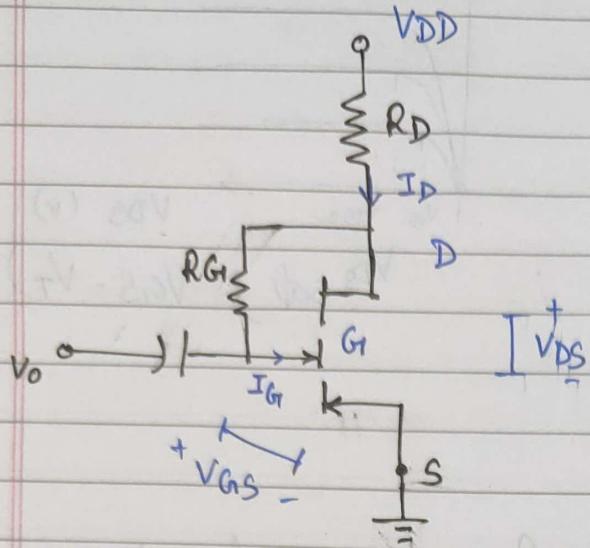

$$I_{G1} = 0$$

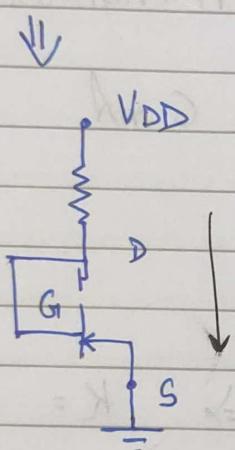

As $I_{G1} = 0$
 $R_{G1} I_{G1} = 0$

$$\textcircled{1} \quad V_{G1} = V_D$$

$$\textcircled{2} \quad V_{GS} = V_{DS}$$

$$\textcircled{3} \quad V_{DS} = V_{DD} - I_D R_D$$

$$\textcircled{4} \quad V_{GS} = V_{DD} - I_D R_D$$

Ques. 1) $\Rightarrow R_D = 2k\Omega$, $V_{DD} = 12V$, V_{DS} ?

Given
 $K = 0.24$
 $V_T = 3V$

$$V_{GS} = V_{DS} = V_{DD} - I_D R_D \quad | \quad I_D = K(V_{GS} - V_T)^2$$

$$I_D = 0.24(V_{GS} - 3)^2$$

$$I_D = 0.24(12 - 2 \times 10^3 I_D - 3)^2$$

$$I_D = 0.24(9 - 2 \times 10^3 I_D)^2$$

$$I_D = 4.43 \text{ mA}, \quad 4.56 \text{ mA}$$

$$2.79 \text{ mA}, \quad 7.24 \text{ mA}$$

$$I_D = 0.24(V_{GS} - 3)^2$$

$$V_{GS} = 12 - 2 \times 10^3 I_D$$

$$V_{GS} = 3 \Rightarrow I_D = 0$$



$$V_{GS} = 4 \Rightarrow I_D = 0.24 \text{ mA}$$

$$V_{GS} = 5 \Rightarrow I_D = 0.96 \text{ mA}$$

$$V_{GS} = 6 \Rightarrow I_D = 2.16 \text{ mA}$$

$$V_{GS} = 0 \Rightarrow I_D = 6 \text{ mA}$$
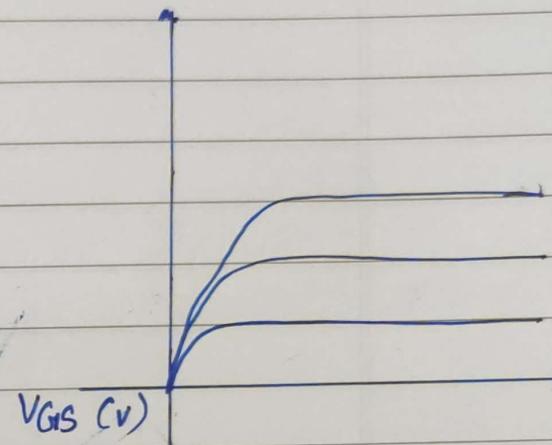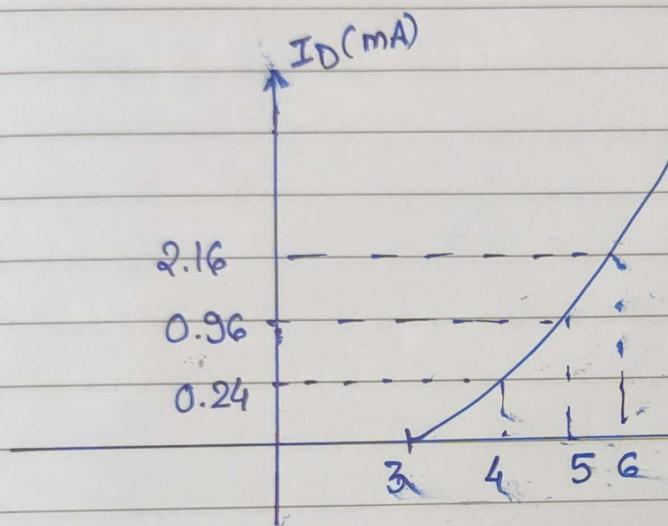
$$I_D = 0 \Rightarrow V_{GS} = 12 \text{ V}$$




$$I_{DQ} = 2.79 \text{ mA}$$

$$V_{GS} = V_{DS} = 6.42 \text{ V}$$

Small Signal Analysis of FET

$$\Delta I_D = g_m \Delta V_{GS}$$

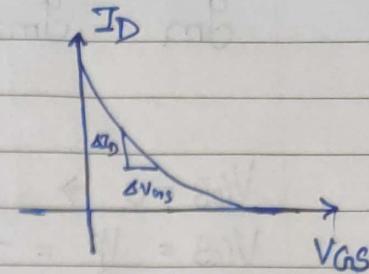* $\frac{\Delta I_D}{\Delta V_{GS}} = g_m \Rightarrow \text{Transconductance}$



$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$g_m = \frac{dI_D}{dV_{GS}} = I_{DSS} \times 2 \left(\frac{-1}{V_p}\right) \left(1 - \frac{V_{GS}}{V_p}\right)$$

✓
$$g_m = + \frac{2 I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p}\right)$$

Transconductance can not be -ve

$$V_{GS} = 0 \Rightarrow g_{m0} = \frac{2 I_{DSS}}{V_p}$$

✓
$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_p}\right)$$

$g_{m0} \rightarrow \text{max value}$

Ques.) Calc. the Value of ① max value of g_m ② Plot g_m vs V_{GS} A JFET has $I_{DSS} = 8 \text{ mA}$
 & $V_{GS} = 4 \text{ V}$, $V_p = -4 \text{ V}$

⇒


$$g_{m0} = \frac{2 I_{DSS}}{V_p} = \frac{2 \times 8 \times 10^{-3}}{4} = 4 \text{ mA/V} = 4 \text{ mS}$$

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p} \right)$$

$$V_{GS} = 0 \Rightarrow g_m = g_{mo}$$

$$V_{GS} = \frac{V_p}{2} = -2 \Rightarrow g_m = \frac{g_{mo}}{2}$$
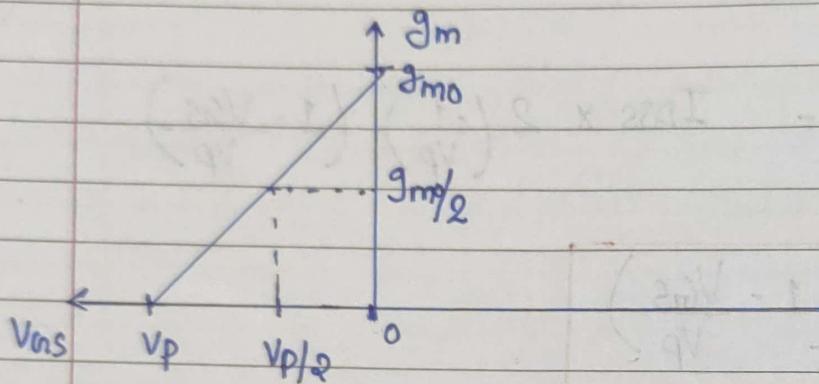
$$V_{GS} = V_p = -4 \Rightarrow g_m = 0$$



★ Relation b/w I_D & g_m →

$$g_m = \frac{I_D}{V_{GS}}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$


$$\frac{V_{GS}}{V_p} = 1 - \sqrt{\frac{I_D}{I_{DSS}}}$$

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p} \right)$$

$$g_m = g_{mo} \sqrt{\frac{I_D}{I_{DSS}}}$$

$$I_D = I_{DSS} \frac{g_m^2}{g_{mo}}$$

$$n = y^2 \rightarrow \text{Parabola}$$

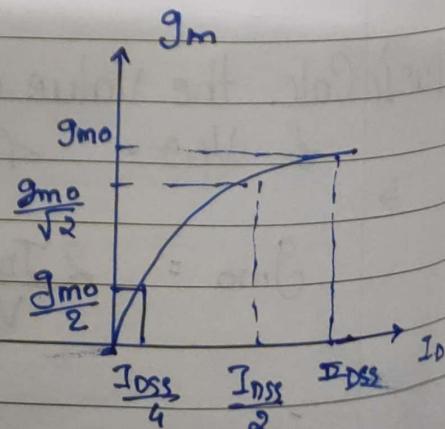


$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = g_{mo} \left(1 - \frac{V_{GS}}{V_P}\right) = g_{mo} \sqrt{\frac{I_D}{I_{DSS}}}$$


$$r_{dl} = \frac{\Delta V_{DS}}{\Delta I_D}$$

↓
drain
resistance


$r_{dl} \rightarrow$ Very large

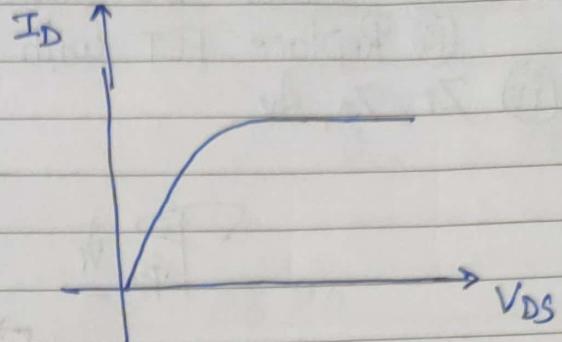

* AC equivalent ckt →

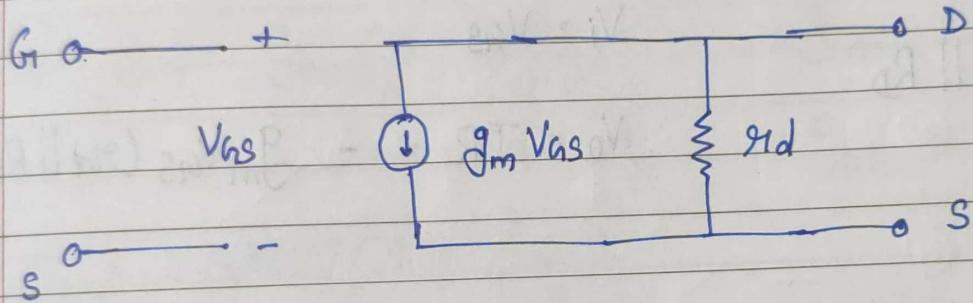


AC Equivalent of Fixed Biased FET ⇒

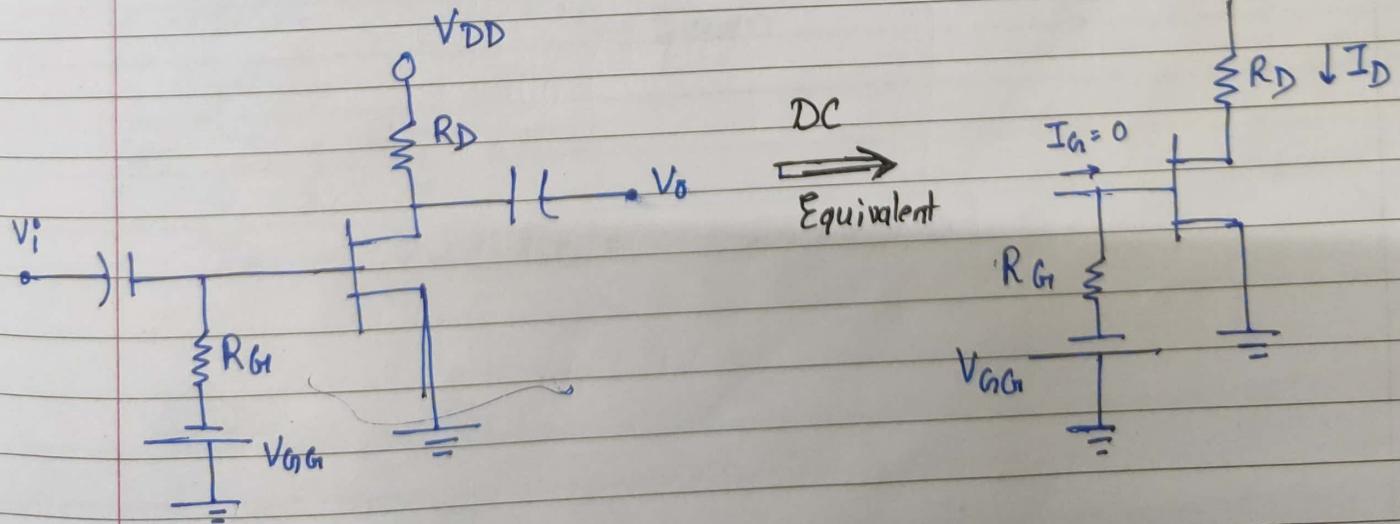

for AC equiv. CK →

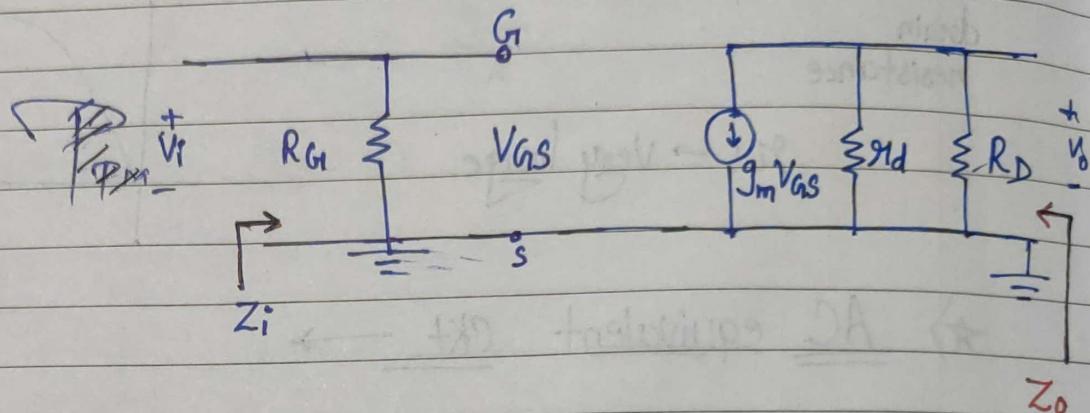- (i) Short ckt Capacitor
- (ii) Make DC Source Zero.
- (iii) Replace FET with Small Signal model.
- (iv) Z_i, Z_o, A_v



$$\checkmark Z_i = R_{G1}$$

$$Vi = V_{GS}$$

$$\checkmark Z_o = R_D \parallel R_D$$

$$V_o = IR = - g_m V_{GS} (R_D \parallel R_D)$$

$$A_v = \frac{V_o}{V_i}$$

$$\checkmark A_v = - g_m (R_D \parallel R_D)$$

Ques.) A Fixed bias Config. has $V_{DD} = 20V$, $R_D = 2K\Omega$,
 $R_{in} = 1M\Omega$, $V_{GS} = 2V$, $I_{DSS} = 10mA$, $V_p = -8V$

i) Draw equiv. Ckt

ii) Calc. eq Q point

iii) Verify graphically

iv) Calc. g_m & g_{mo}

Q (V_{GSQ} , I_{DQ})

$-2V$

$5.625mA$

v) Calc. Z_i , Z_o , A_v given $r_{ld} = 25K\Omega$
 (drain Resist.)

vi) D —, — ignoring r_{ld} .

$$iv) g_m = g_{mo} \left(1 - \frac{V_{GSQ}}{V_p} \right)$$

$$g_{mo} = \frac{2 I_D}{V_p}$$

$$g_{mo} = \frac{2 \times 10}{8} = 2.5 \text{ mS}$$

$$g_m = 2.5 \times 10^{-3} \left(1 - \frac{(-2)}{(-8)} \right)$$

$$= 2.5 \times 10^{-3} \left(1 - \frac{1}{4} \right) = \frac{2.5 \times 3 \times 10^{-3}}{4}$$

$$g_m = 1.875 \text{ mS}$$

\hookrightarrow Simen

$$v) Z_i = R_D = 1M\Omega$$

$$Z_o = r_{ld} || R_D = \frac{25 \times 2 \times 10^3}{27} = 1.85 K\Omega$$

$$A_v = - g_m Z_o$$

$$= - 1.875 \times 1.85$$

$$A_v = -3.468$$

(vi) Ignoring r_d

$$Z_i = R_{G1} = 1 \text{ M}\Omega$$

$$Z_o = R_D = 2 \text{ k}\Omega$$

$$A_v = -g_m Z_o = 1.875 \times 2$$

$$A_v = -3.75$$

(using $r_d = 0$)

$$\frac{\Delta I_S}{\Delta V} = \text{m}\Omega$$

$$\left(\frac{0.05V - 1}{9V}\right) \text{ m}\Omega = \text{m}\Omega \quad (vi)$$

$$2m \text{ m}\Omega = 0.1 \times 8 = \text{m}\Omega$$

$$\left(\frac{(8-1)}{8}\right)^{8.01 \times 2.8} = \text{m}\Omega$$

$$8.01 \times 2.8 = \left(\frac{7}{8}\right)^{8.01 \times 2.8} =$$

$$2m \text{ m}\Omega = \text{m}\Omega$$

simply ↪

$$2m \Omega = 0.9 \times 10^3 \quad (v)$$


$$2m \Omega = 0.9 \times 10^3 = \frac{0.9 \times 10^3}{F_0} = 0.9 / R_D = 0.5$$

$$0.5 \text{ m}\Omega = \text{m}\Omega$$

$$2.8 \times 2.8 = \text{m}\Omega$$


$$\Rightarrow g_d = \frac{\Delta V_{DS}}{\Delta I_D} = \frac{1}{Y_{OS}}$$

Y_{OS} = Admittance o/p
Common Source

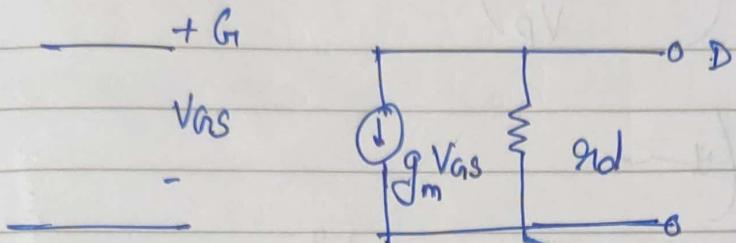

\Rightarrow Self Bias Configuration \Rightarrow

JFET

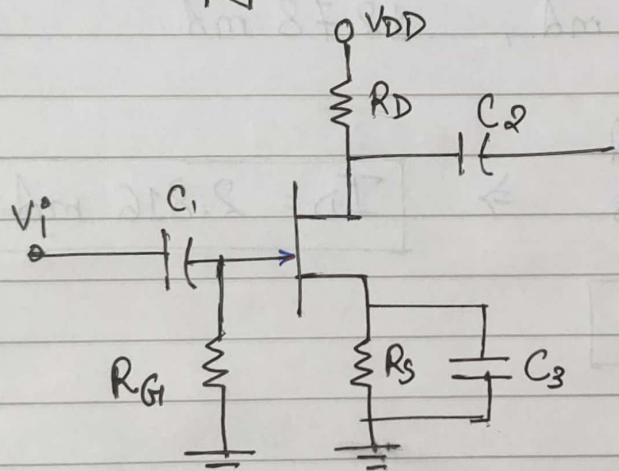

The self bias Configuration has $V_{DD} = 20V$, $R_D = 3.3 k\Omega$

$R_S = 1 k\Omega$, $R_G = 1 M\Omega$, $I_{DSS} = 10mA$, $V_p = -6V$

$\therefore Y_{OS} = 20 \mu S$.

\Rightarrow Small Signal Model

$\rightarrow C_{tr} + C$

i) Draw the transfer ckt.

ii) Find the Q point.

iii) Verify graphically.

iv) Draw the small signal equivalent model.

v) Calc. Z_i , Z_o , A_v taking g_d into consideration ignoring g_d .

⇒

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 10 \times 10^{-3} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = - I_D R_S$$

$$I_D = 10 \times 10^{-3} \left(1 - \frac{I_D \times 10^3}{6} \right)^2$$

$$I_D = 2.816 \text{ mA}, 12.78 \text{ mA}$$

$$I_{DSS} = 10 \text{ mA}$$

$$I_D < I_{DSS}$$

$$\Rightarrow I_D = 2.816 \text{ mA}$$


$$V_{GS} = - 2.816 \text{ V}$$

$$\text{If } V_{GS} = 0 \Rightarrow I_D = I_{DSS} = 10 \text{ mA}$$

$$V_{GS} = \frac{V_P}{2} \Rightarrow I_D = \frac{I_{DSS}}{4} = 2.5 \text{ mA}$$

$$V_{GS} = \frac{V_P}{4} \Rightarrow I_D = \frac{9}{16} I_{DSS} = 5.625 \text{ mA}$$

①

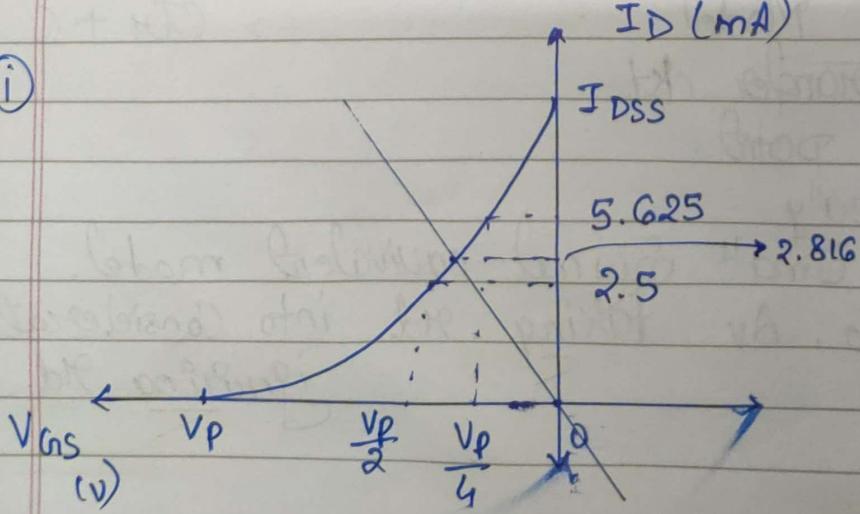


ii) Q point $(V_{G1S}, I_D) = (-2.816, 2.816)$

iii) $V_{G1S} = -10^3 I_D$

$$V_{G1S} \quad y = m \quad I_D = -\frac{1}{10^3} V_{G1S}$$

$$y = mx$$

iv) Now for AC Analysis \rightarrow

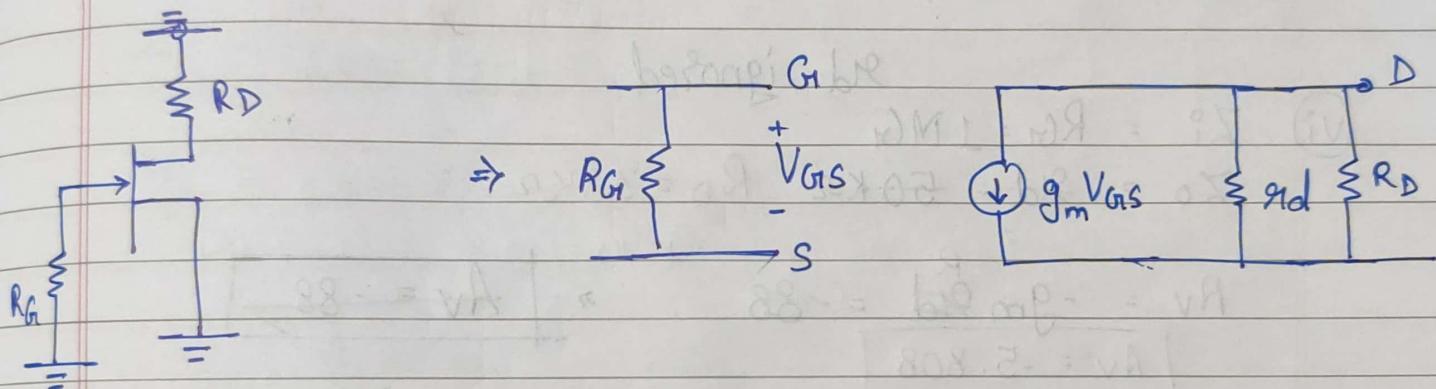

$$g_d g_m = \frac{1}{20} \quad g_d = \frac{1}{g_m} = \frac{1}{20 \times 10^{-6}} = 50 \text{ k}\Omega$$

$$g_m = \frac{2 I_{DSS}}{V_P} = \frac{2 \times 10 \times 10^{-3}}{6} = 3.33 \times 10^{-3}$$

$$g_m = g_m \left(1 - \frac{V_{G1S}}{V_P}\right) = 3.33 \times 10^{-3} \left(1 - \frac{-2.816}{6}\right)$$

$$g_m = 1.76 \times 10^{-3} = 1.76 \text{ mS}$$

$$g_m V_{G1S} = 4.97 \text{ mA}$$

(188, 2188) - (part, part) thing

$$\textcircled{V} \quad Z_i = 1M\Omega = R_G$$

$$Z_o = g_d \parallel R_D = 50k \parallel 3.3k$$

$$Z_o = 3.09k\Omega$$

$$A_V = -g_m (g_d \parallel R_D)$$

$$= -1.76 \times 3.09$$

$$\boxed{A_V = -5.448}$$

\textcircled{Vi} $Z_i = R_G = 1M\Omega$


$Z_o = g_d = 50k\Omega \quad R_D = 3.3k\Omega$


g_d ignored

$$A_V = -g_m \frac{R}{g_d} = -88 \quad \Rightarrow \boxed{A_V = -88}$$

$$\boxed{A_V = -5.808}$$

Que.) Voltage Divider

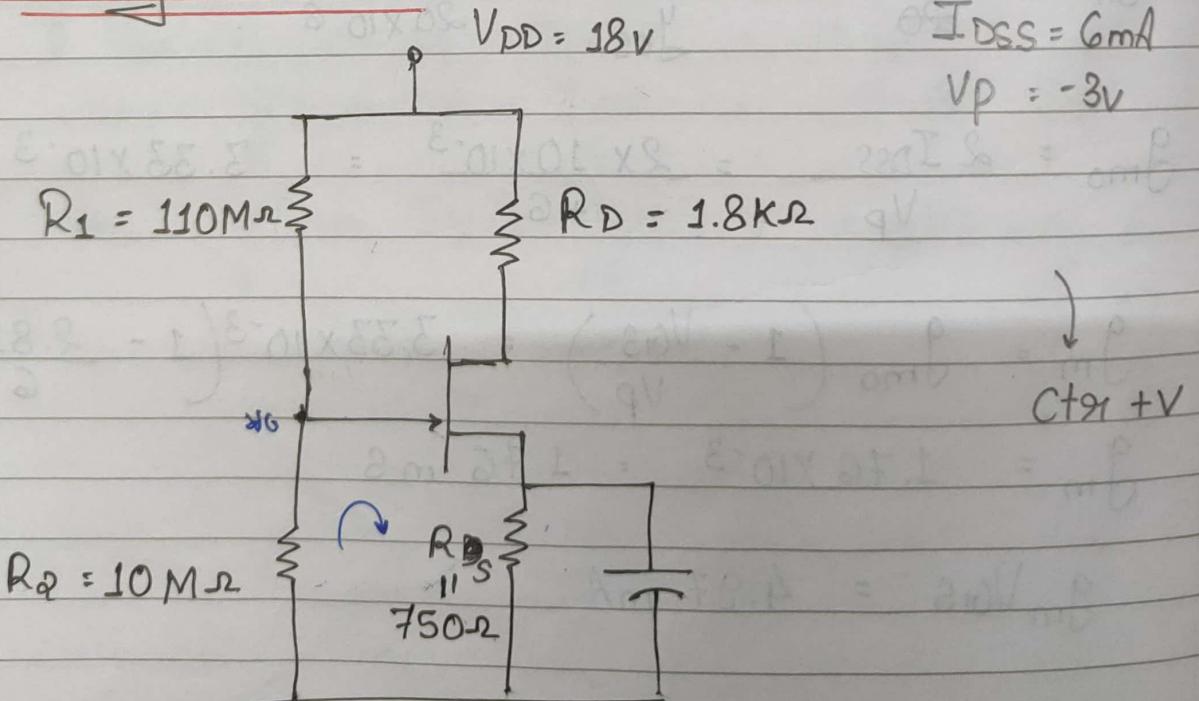

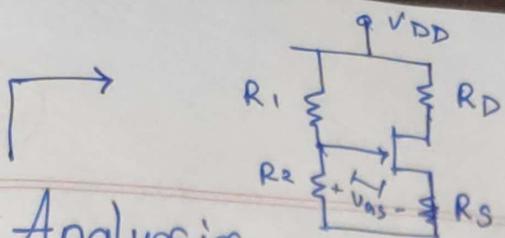

classmate
Date 24/0ct/24
Page

DC Analysis

$$V_{G1} = \frac{V_{DD} R_2}{R_1 + R_2} = \frac{18 \times 10 \times 10^6}{120}$$

$$V_{G1} = 1.5 \text{ V}$$

$$V_{G1S} = V_{G1} - V_S$$

$$V_{G1S} = V_{G1} - I_D R_S \Rightarrow V_{G1S} = 1.5 \text{ V}$$

$$I_D = V_{G1S} = 1.5 - I_D \times 750$$

$$I_D = I_{DSS} \left(1 - \frac{V_{G1S}}{V_p} \right)^2$$

$$I_D = 6 \times 10^{-3} \left(1 + \frac{1.5 - 750 I_D}{3} \right)^2$$

$$I_D = 3.12 \text{ mA}, 11.55 \text{ mA}$$

$$I_D < I_{DSS} \Rightarrow I_D = 3.12 \text{ mA}$$


$$V_{G1S_Q} = -0.84 \text{ V}$$

$$\text{Q-point} \rightarrow (V_{G1S_Q}, I_{D_Q}) = (-0.84 \text{ V}, 3.12 \text{ mA})$$

$$V_{G1S} = 0 \Rightarrow I_D = I_{DSS} = 6 \text{ mA}$$

$$V_{G1S} = \frac{V_p}{2} \Rightarrow I_D = \frac{I_{DSS}}{4} = 1.5 \text{ mA}$$

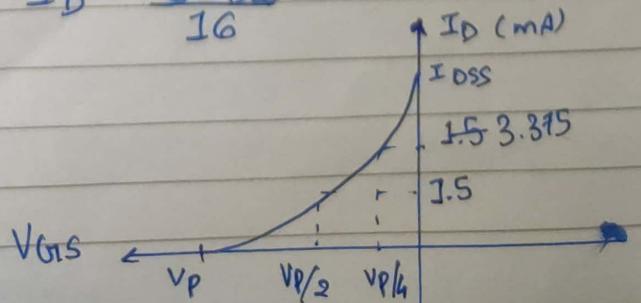
$$V_{G1S} = \frac{V_p}{4} \Rightarrow I_D = \frac{9 I_{DSS}}{16} = 3.375 \text{ mA}$$



$$g_{m0} = \left| \frac{2 I_{DSS}}{V_p} \right| = \left| \frac{2 \times 6 \times 10^{-3}}{-3} \right| = 4 \times 10^{-3}$$

$$g_m = g_{m0} (1 -$$

for AC

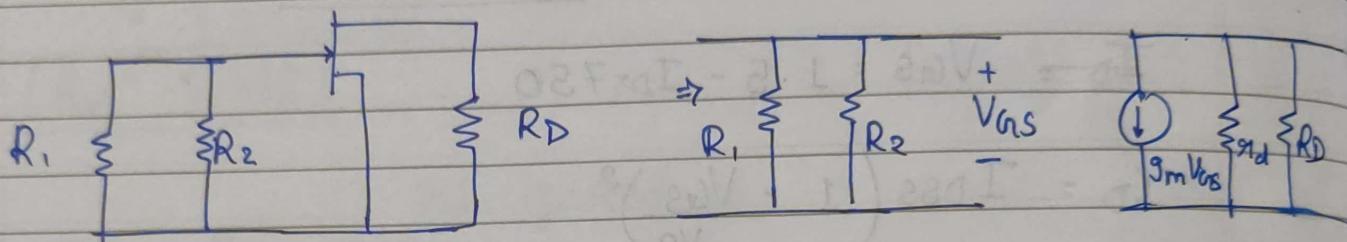

$$g_m = g_{m0} \left(1 - \frac{V_{os}}{V_p} \right) = 4 \times 10^{-3} \left(1 - \frac{(-0.84)}{(-3)} \right)$$

$$g_m = 2.88 \text{ mS}$$

$$r_d = 50 \text{ k}\Omega$$

$$Z_i = R_1 || R_2 = 9.16 \text{ M}\Omega$$

$$Z_o = r_d || R_D = 1.737 \text{ k}\Omega$$


$$A_v = -g_m (r_d || R_D)$$

$$\boxed{A_v = -5.004}$$

classmate
Date _____
Page _____

DC eq. Ckt

1) Fixed Biases

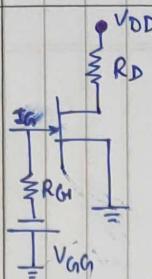

$I_G = 0$



$V_{GS} = V_G - V_S$

$V_{GS} = +V_{GGS}$

$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$

$V_{DS} = V_{DD} - I_D R_D$

AC eq. Ckt

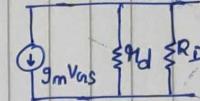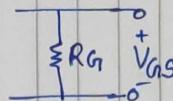

$Z_i = R_G$

$Z_o = R_d || R_D$

$A_v = -g_m Z_o$

$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p}\right)$

$g_{mo} = \frac{2I_{DSS}}{V_p}$

$g_d = \frac{\Delta V_{DS}}{\Delta I_D}$

$g_d = \frac{1}{I_{DS}}$

$g_{mo} = \frac{2I_{DSS}}{V_p}$



$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p}\right)$

$Z_i = R_G$

$Z_o = R_d || R_D$

$A_v = -g_m Z_o$



2) Self Biases

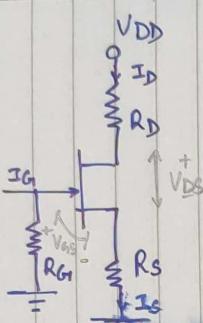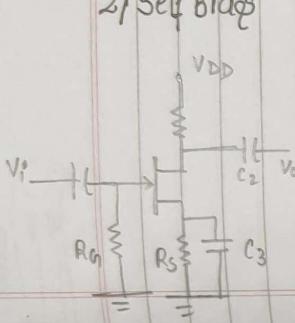



$V_{GS} = -I_S R_S = I_D R_S$

$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$

$V_{DS} = V_{DD} - I_D (R_D + R_S)$

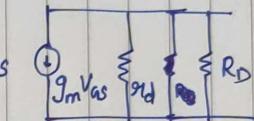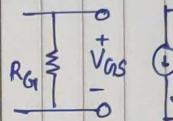

3) Voltage Divider

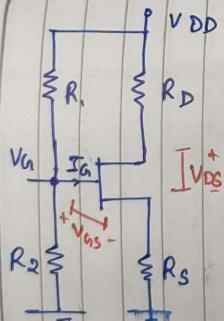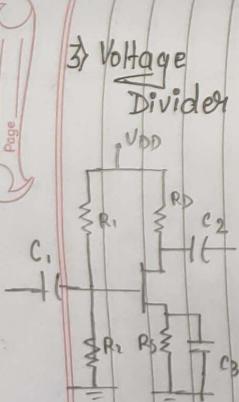



$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$

$V_{GS} = V_G - V_S$

$V_{GS} = V_{DD} \left(\frac{R_2}{R_1 + R_2}\right) - I_D R_S$

$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$

$V_{DS} = V_{DD} - I_D (R_D + R_S)$

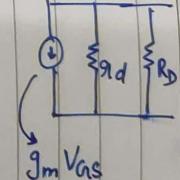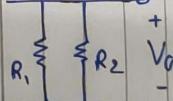

$Z_i = R_1 || R_2$


$Z_o = R_d || R_D$

$A_v = -g_m (R_d || R_D)$

$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p}\right)$

DC eq. Ckt

1) Fixed Bias

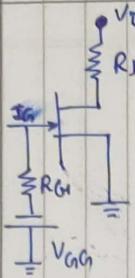

$$I_{G1} = 0$$



$$V_{GS} = V_G - V_S$$

$$V_{GS} = +V_{GG}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_{DS} = V_{DD} - I_D R_D$$

AC eq. Ckt

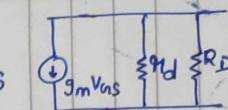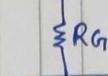

$$Z_i = R_G$$

$$Z_o = g_d || R_D$$

$$A_v = -g_m Z_o$$

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$g_{mo} = \frac{2I_{DSS}}{V_P}$$

$$g_d = \frac{\Delta V_{DS}}{\Delta I_D}$$

$$g_d = \frac{1}{j_{DS}}$$

$$g_{mo} = \frac{2I_{DSS}}{V_P}$$


$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$Z_i = R_G$$

$$Z_o = g_d || R_D$$

$$A_v = -g_m Z_o$$



2) Self Bias

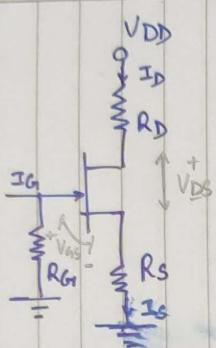

$$V_{GS} = -I_S R_S = I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

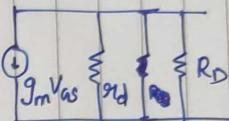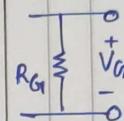

$$g_d = \frac{1}{j_{DS}}$$

$$g_{mo} = \frac{2I_{DSS}}{V_P}$$


$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$Z_i = R_G$$

$$Z_o = g_d || R_D$$

$$A_v = -g_m Z_o$$

3) Voltage Divider

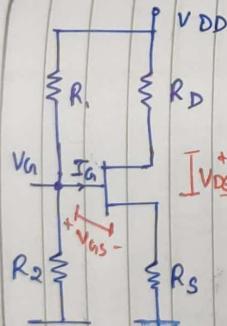



$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = V_{DD} \left(\frac{R_2}{R_1 + R_2}\right) - I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

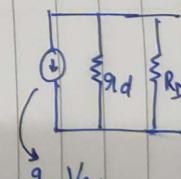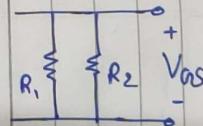


$$Z_i = R_1 || R_2$$

$$Z_o = g_d || R_D$$

$$A_v = -g_m (g_d || R_D)$$

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_P}\right)$$

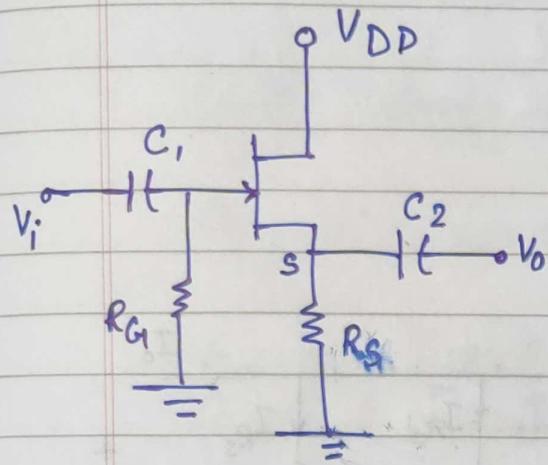Source Follower (Common Drain) \Rightarrow



Op is taken at
Source

AC equivalent \rightarrow

(Small Signal Analysis)

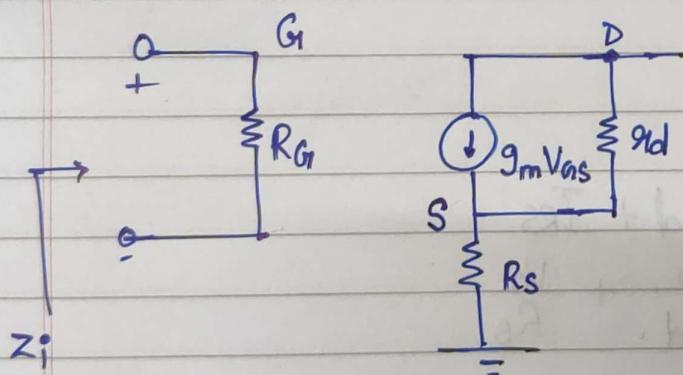


Fig-2


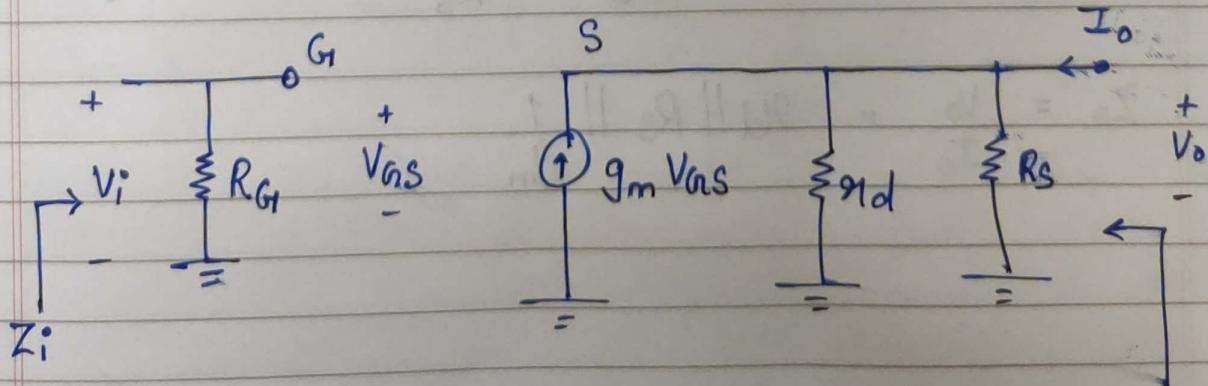


Fig-3

$$\textcircled{i} \quad Z_i = R_G$$

$$\textcircled{ii} \quad Z_o = \frac{V_o}{I_o} \quad |_{V_i=0}$$

\hookleftarrow

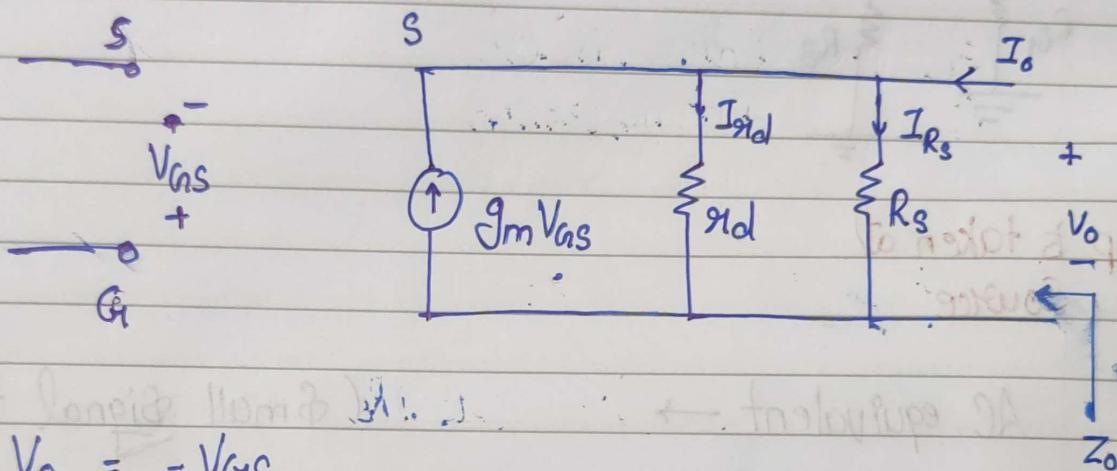

$$\textcircled{a} \quad V_o = -V_{GS}$$

\textcircled{b} Applying KCL at S

$$\begin{aligned} g_m V_{GS} + I_o &= I_{RD} + I_{RS} \\ &= \frac{V_o}{R_D} + \frac{V_o}{R_S} \end{aligned}$$

$$I_o - g_m V_o = \frac{V_o}{R_D} + \frac{V_o}{R_S} \Rightarrow I_o = V_o \left(g_m + \frac{1}{R_D} + \frac{1}{R_S} \right)$$

$$Z_o = \frac{V_o}{I_o} = R_D \parallel R_S \parallel \frac{1}{g_m}$$

(iii) Voltage Gain $A_v = \frac{V_o}{V_i}$

fig ③ Apply KVL in loop

$$\textcircled{a} \quad V_i = V_{gs} + V_o \Rightarrow V_{gs} = V_i - V_o$$

$$\frac{V_o}{V_i} = \frac{g_m(\text{r}_d \parallel R_s)}{1 + g_m(\text{r}_d \parallel R_s)}$$

$$\textcircled{b} \quad \underline{V_o} = g_m V_{gs} (\text{r}_d \parallel R_s)$$

$$V_o = g_m (V_i - V_o) (\text{r}_d \parallel R_s)$$

Que.) A Source follower Ckt has $V_{GSQ} = -2.86V$
 $I_{DQ} = 4.56mA$, $I_{DSS} = 16mA$, $V_p = -4V$
 $Y_{OS} = 25\mu S$, $R_S = 2.2k\Omega$, $R_G = 1M\Omega$
 $V_{DD} = 9V$

Determine

$$\textcircled{i} \quad g_m$$

$$\textcircled{ii} \quad g_d$$

$$\textcircled{iii} \quad Z_i^o$$

$\textcircled{iv} \quad Z_o$ with & without g_d
 Compare the result.

v) Determine A_v with & without g_d .

Ans

$$\textcircled{i} \quad g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p} \right)$$

$$g_{mo} = \left| \frac{2I_{DSS}}{V_p} \right| = \frac{2 \times 16 \times 10^{-3}}{4} = 8mS$$

$$g_m = 8 \times 10^{-3} \left(1 - \frac{2.86}{4} \right)$$

$$g_m = 2.28 mS$$

$$\textcircled{ii} \quad g_d = \frac{1}{Y_{OS}} = \frac{10^6}{25} = 40k\Omega$$

$$\textcircled{iii} \quad Z_i^o = R_G = 1M\Omega$$

\textcircled{iv} with g_d

$$Z_o = g_d || R_S || \frac{1}{g_m}$$

$$Z_o = 362.378 \Omega$$

(without r_d .)

$$Z_0 = R_s \parallel \frac{1}{g_m} = \frac{1}{\frac{R_s + 1}{R_s} + g_m}$$

$$Z_0 = 365.69 \Omega$$

v) with r_d


$$A_v = \frac{g_m (r_d \parallel R_s)}{1 + g_m (r_d \parallel R_s)} = \frac{1}{1 + \frac{1}{g_m (r_d \parallel R_s)}}$$

$$A_v = 0.826$$

without r_d

$$A_v = 0.83$$

07/NOV/24

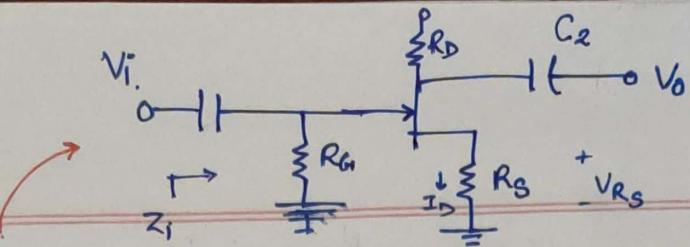


classmate

Date _____
Page _____

FET Self Bias Unby Passed Rs

(i)

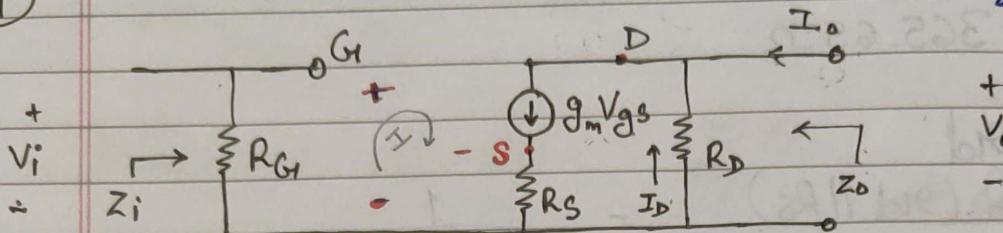

(i) when R_D is not included in ckt

$$i) Z_i = R_{g1}$$

$$ii) Z_o = \left. \frac{V_0}{I_o} \right|_{V_i=0} = -\frac{I_o R_D}{I_o}$$

Applying KCL at node D $\Rightarrow I_o + I_D = g_m V_{gs}$ — (i)

—, KVL \rightarrow GS loop $\Rightarrow V_{gs} = -(I_o + I_D) R_S$ — (ii)

$$V_{gs} + V_{RS} = 0 \quad \hookrightarrow V_i = 0 \Rightarrow V_{gs} + (g_m V_{gs}) R_S = 0$$

Substituting (ii) in (i)

$$I_D + I_o = -g_m (I_o + I_D) R_S$$

$$(I_o + I_D)(1 + g_m R_S) = 0$$


$$\Rightarrow I_o = -I_D$$

Hence,

$$Z_o = R_D$$

11

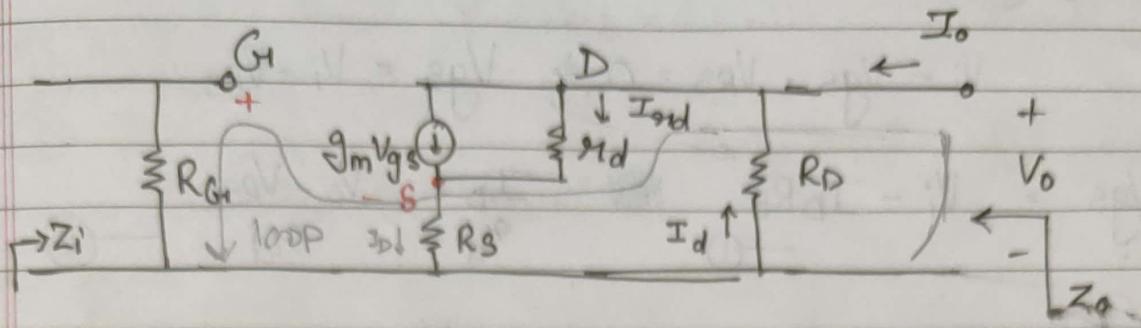When r_{id} is included in the ckt \rightarrow



$$\text{Applying KCL at Drain } D \Rightarrow I_o = g_m V_{gs} + I_{r_{id}} - I_D \quad \text{--- i}$$

$$\text{Applying KVL at DSG loop} \Rightarrow V_{r_{id}} = V_o + V_{gs} \quad \text{--- ii}$$

$V_o - V_{r_{id}} + V_{gs} = 0$

Substituting (ii) in (i)

$$I_o = g_m V_{gs} + \frac{V_o + V_{gs}}{I_{r_{id}} r_{id}} - I_D \quad \text{--- iii}$$

$$I_{r_{id}} = \frac{V_{r_{id}}}{R_{id}}$$

$$\text{Substituting } V_o = -I_D R_D \text{ and } V_{gs} = -(I_o + I_D) R_S$$

$$\checkmark I_o = -I_D \left[1 + g_m R_S + \frac{R_S}{r_{id}} + \frac{R_D}{r_{id}} \right] \quad \text{--- iv}$$

in (ii)
and rearranging

$$Z_o = \frac{V_o}{I_o}$$

$$Z_o = -\frac{I_D R_D}{I_o}$$

Substituting I_o from (iv) we get

$$\checkmark Z_o = \frac{1 + g_m R_S + \frac{R_D}{r_{id}}}{1 + g_m R_S + \frac{R_S}{r_{id}} + \frac{R_D}{r_{id}}} \times R_D$$

$$V_o = -I_D R_{SD}, V_{RS} = I_D R_S$$

III

Applying KVL in IP

$$V_i - V_{GS} - V_{RS} = 0 \Rightarrow V_{GS} = V_i - V_{RS}$$

$$V_{GS} = V_i - I_D R_S \quad \text{--- (1)}$$

$$I_D = \frac{V_o - V_{RS}}{R_D} \quad \text{--- (2)}$$

$$\text{Apply KCL at } S \Rightarrow I_D = g_m V_{GS} + \frac{V_o - V_{RS}}{R_D}$$

$$I_D = g_m (V_i - V_{RS}) + \frac{V_o - V_{RS}}{R_D}$$

$$I_D = \frac{g_m V_i}{1 + g_m R_S + R_D + R_S} \quad \text{--- (3)}$$

$$A_v = \frac{V_o}{V_i} = -\frac{I_D R_D}{V_i}$$

Substituting I_D from (3)

$$A_v = -\frac{g_m R_D}{1 + g_m R_S + R_D + R_S}$$

Que. 1) A Self bias Configuration has a operating point $V_{GSQ} = -2.6V$
 $I_{DSS} = 8mA$, $V_p = -6V$, $y_{os} = 20\mu S$.

- ① Determine g_m , r_d , Z_i ,
- ② Calc. Z_o , A_v with & without effect of r_d .
 Compare the result.

$$R_G = 1M\Omega, R_D = 3.3k\Omega, R_S = 1k\Omega$$

 \Rightarrow

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_p} \right)$$

$$g_{m0} = \left| \frac{2I_{DSS}}{V_p} \right| = \left| \frac{2 \times 8 \times 10^{-3}}{6} \right| = 2.66 \times 10^{-3} \text{ S}$$

$$\textcircled{i} \quad g_m = 2.66 \times 10^{-3} \left(1 - \frac{2.6}{6} \right) =$$

$$g_m = 1.5 \text{ mS}$$

$$r_d = \frac{1}{y_{os}} = \frac{10^6}{20} = 5 \times 10^4 \Omega$$

$$Z_i = R_G = 1M\Omega$$

$$\textcircled{ii} \quad Z_o = -\frac{I_D R_D}{I_0} \Rightarrow Z_o = R_D = 3.3k\Omega \quad (\text{ignoring } r_d)$$

$$\text{without } r_d \rightarrow A_v = -\frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

$$A_v = -\frac{1.5 \times 10^{-3} \times 3.3 \times 10^3}{1 + 1.5 \times 1 + \frac{(3.3 + 1) \times 10^3}{5 \times 10^4}}$$

$$A_v = -1.914$$

ctrl
if $g_{ld} > 10(R_D + R_S)$ \Rightarrow ignore g_{ld}

CLASSMATE
Date _____
Page _____

Considering g_{ld} , \Rightarrow

$$Z_0 = \frac{1 + g_m R_S + \frac{R_D}{g_{ld}}}{1 + g_m R_S + \frac{R_S}{R_D} + \frac{R_D}{g_{ld}}} \times R_D$$

$$Z_0 = 3.299 \text{ k}\Omega$$


without $g_{ld} \Rightarrow$

$$A_v = -1.9$$




Sinusoidal i/p 1V peak-peak . Draw o/p Sinusoidal

1Hz

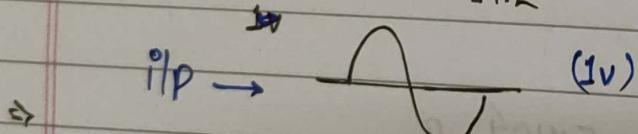

(1v)


waveform.

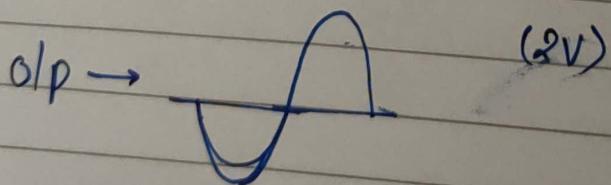

(2v)

Ques.

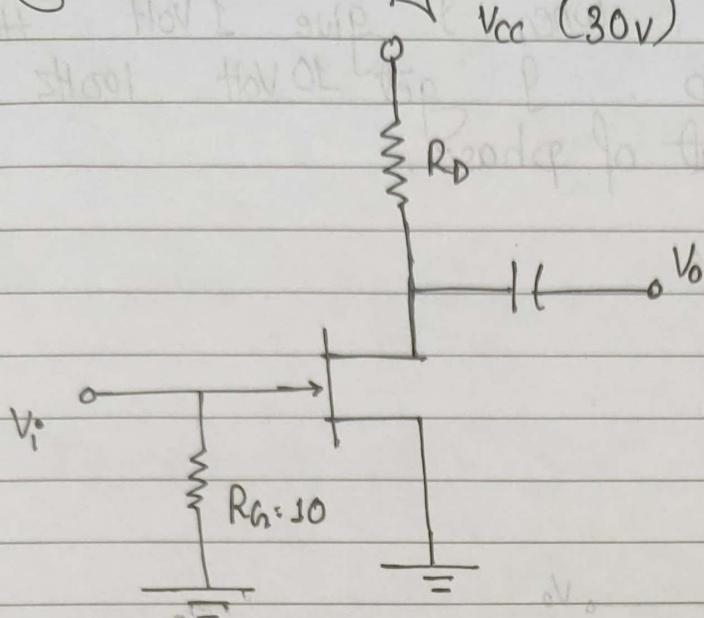Design a fixed bias ckt having a voltage gain of 10 as given in a fig.



AC

$$I_{DSS} = 10 \text{ mA}$$

$$V_p = -4 \text{ V}$$

$$Y_{OS} = 20 \mu\text{s}$$

⇒

$$V_{GS} = 0 \text{ V}, R_s = 0$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_p} \right) \Rightarrow g_m = g_{m0}$$

$$g_{m0} = \left| \frac{2 I_{DSS}}{V_p} \right| = \left| \frac{2 \times 10}{4} \right| = 5 \text{ ms}$$

$$\Rightarrow g_m = 5 \text{ ms}$$

$$r_d = \frac{1}{Y_{OS}} \Rightarrow \boxed{r_d = 5 \times 10^4 \Omega}$$

$$\text{AC Gain} = -10 \Rightarrow A_V = \frac{-g_m R_D}{1 + g_m R_s + \frac{R_D + R_s}{r_d}}$$

$$R_D = r_d \left(\frac{-g_m R_D}{g_m} \right)$$

$$A_V = -g_m (r_d || R_D) + \frac{\frac{1}{r_d}}{\frac{1}{r_d} + \frac{1}{R_D}} = -\frac{A_V}{g_m}$$


$$\frac{1}{r_d} + \frac{1}{R_D} = -\frac{g_m}{A_V} = \frac{10^{-3}}{2} \Rightarrow \frac{1}{R_D} = \frac{10^{-3}}{2} - 20 \times 10^{-6}$$

$$\boxed{R_D = 2 \text{ k}\Omega}$$

Que.1

Design a fixed bias network using JFET having $I_{DSS} = 10\text{mA}$, $V_p = -4\text{V}$, $R_G = 10\text{M}\Omega$, $y_{os} = 20\mu\text{s}$ Supply Volt $< 30\text{V}$. when I give 1 volt $H \rightarrow 100\text{Hz}$ Sinosoidal i/p. I get 10 volt 100Hz Sin o/p with o/p 180° out of phase.

Que.2

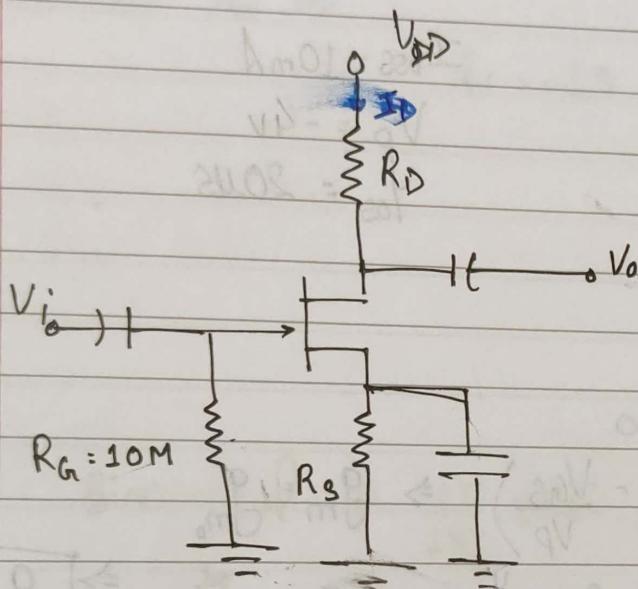

$$I_{DSS} = 10\text{mA}$$

$$V_p = -4\text{V}$$

$$y_{os} = 20\mu\text{s}$$

$$A_v = 8$$

$$V_{GQ} = \frac{1}{4} V_p = -1\text{V}$$

$$g_{mo} = ? \quad g_m$$

$$\Rightarrow g_{mo} = \left| \frac{2 I_{DSS}}{V_p} \right| = \left| \frac{2 \times 10 \times 10^{-3}}{-4} \right| = 5 \text{ mS}$$

$$g_m = g_{mo} \left(1 - \frac{V_{G.S.}}{V_p} \right) = 5 \left(1 - \frac{1}{4} \right) = 3.75 \text{ mS}$$

$$A_v = -g_m (\frac{g_d}{R_D} || R_D) \Rightarrow \frac{1}{g_d} + \frac{1}{R_D} = -\frac{g_m}{A_v} = 4.68 \times 10^{-4}$$

$$\frac{1}{R_D} = 4.68 \times 10^{-4} - 20 \times 10^{-6} = 4.48 \times 10^{-4}$$

$$R_D = 2.2 \text{ k}\Omega$$

DC Analysis →

$$V_{GS_Q} = -I_D R_S$$


$$R_S = \frac{1}{I_D}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \left(1 - \frac{1}{4} \right)^2 = 10 \times \frac{9}{16}$$


$$\checkmark I_D = 5.625 \text{ mA}$$

Enhancement MOSFET

* Drain Feedback Configuration →

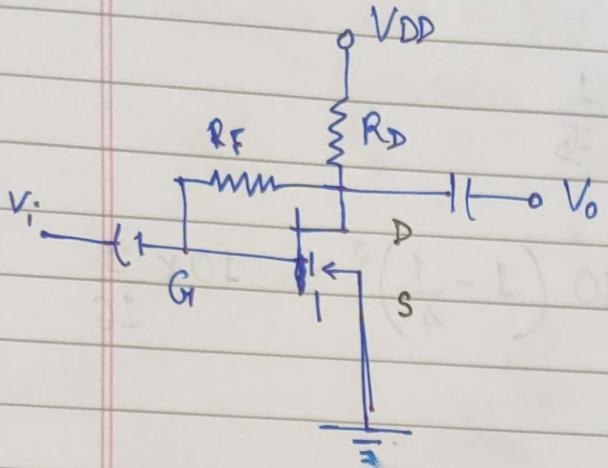

Small Signal Equivalent model

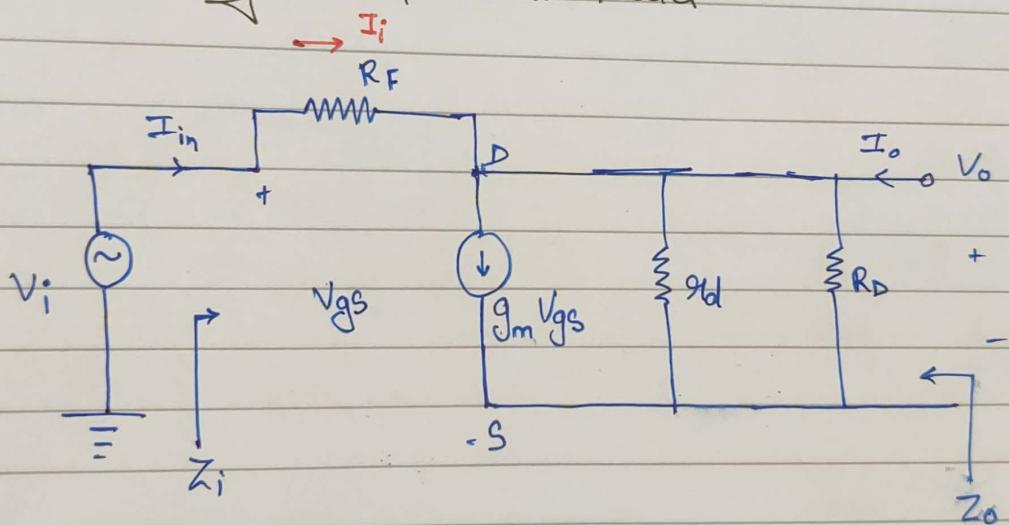

~~Drain~~
KCL at D

$$I_i = g_m V_{gs} + \frac{V_o}{r_{ds} \parallel R_D} \quad |_{R_L = \infty}$$

$$[V_{gs} = V_i]$$

$$\frac{V_i - V_o}{R_F} = g_m V_i + \frac{V_o}{r_{ds} \parallel R_D}$$

$$A_v = \frac{V_o}{V_i} = \frac{\frac{1}{R_F} - g_m}{\left[\frac{1}{r_{ds} \parallel R_D} + \frac{1}{R_F} \right]}$$

$$A_V = -g_m (R_F \parallel r_{d\text{L}} \parallel R_D)$$

$$A_V = \frac{-g_m R_D}{1 + g_m R_F} \quad \text{and} \quad \frac{g_f}{R_F} \parallel \frac{1}{r_{d\text{L}} \parallel R_D} = \frac{1}{R_F \parallel r_{d\text{L}} \parallel R_D}$$

(and $g_m \gg \frac{1}{R_F}$)

$$A_V = -g_m R_D$$

Drain feedback Configuration →

$$Z_i = \frac{V_i}{I_i}$$

Applying KCL at D

$$I_i = g_m V_{GS} + \frac{V_o}{r_{d\text{L}} \parallel R_D}$$

$[V_{GS} = V_i]$

$$I_i - g_m V_i = \frac{V_o}{r_{d\text{L}} \parallel R_D} \Rightarrow V_o = r_{d\text{L}} \parallel R_D (I_i - g_m V_i)$$

$$I_i = \frac{V_i - V_o}{R_F} = \frac{V_i - (r_{d\text{L}} \parallel R_D)(I_i - g_m V_i)}{R_F}$$

$$Z_i^0 = \frac{V_i}{I_i} = \frac{R_F + r_{d\text{L}} \parallel R_D}{1 + g_m (r_{d\text{L}} \parallel R_D)}$$

$$g_f \quad R_F \gg r_{d\text{L}} \parallel R_D$$

$$Z_i^0 = \frac{R_F}{1 + g_m (r_{d\text{L}} \parallel R_D)}$$

$$Z_0 = \left. \frac{V_o}{I_o} \right|_{V_i=0} \Rightarrow Z_0 = R_F \parallel r_{d\text{L}} \parallel R_D$$

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} = \frac{\partial I_D}{\partial V_{GS}}$$

$$I_D = k(V_{GS} - V_T)^2$$

$$\frac{\partial I_D}{\partial V_{GS}} = 2k(V_{GS} - V_T)$$

$$g_m = 2k(V_{GS} - V_T)$$

→ Enhancement MOSFET

Ques) For a Enhancement type MOSFET Connected in drain feedback Configuration ($K = 0.24 \times 10^{-3} \text{ A/V}^2$)

$$V_{GSO} = 6.4 \text{ V}, V_T = 3 \text{ V}, g_{OS} = 20 \mu\text{s}, R_D = 2 \text{k}\Omega$$

$R_F = 10 \text{ M}\Omega$. Calculate

\Rightarrow ① $g_m, r_{id}, Z_i, Z_o, A_v$

$$g_m = 2K(V_{GSO} - V_T)$$

$$\sqrt{g_m} = 2 \times 0.24 \times 10^{-3} (6.4 - 3) = 1.6 \times 10^{-3} \text{ S}$$

$$\sqrt{r_{id}} = \frac{1}{g_{OS}} = 50 \text{ k}\Omega$$

$$Z_i = \frac{R_F + r_{id} \parallel R_D}{1 + g_m(r_{id} \parallel R_D)} = \frac{10 \times 10^6 + (50 \times 10^3 \parallel 2 \times 10^3)}{1 + 1.6 \times 10^{-3} (50 \times 10^3 \parallel 2 \times 10^3)}$$

$$\sqrt{Z_i} = 2.4 \text{ M}\Omega$$

$$Z_o = R_F \parallel r_{id} \parallel R_D = \frac{1}{\frac{1}{R_F} + \frac{1}{r_{id}} + \frac{1}{R_D}}$$

$$\sqrt{Z_o} = 1.9 \text{ k}\Omega$$


$$A_v = -\frac{g_m R_D}{r_{id}} = -1.6 \times 10^{-3} \times 2 \times 10^3$$

$$A_v = -3.2 \quad A_v = -g_m (R_F \parallel r_{id} \parallel R_D)$$

$$A_v = -1.6 \times 10^{-3} \times \frac{1.9}{2.4 \times 10^3}$$

$$\sqrt{A_v} = -3.04 - 3.04$$

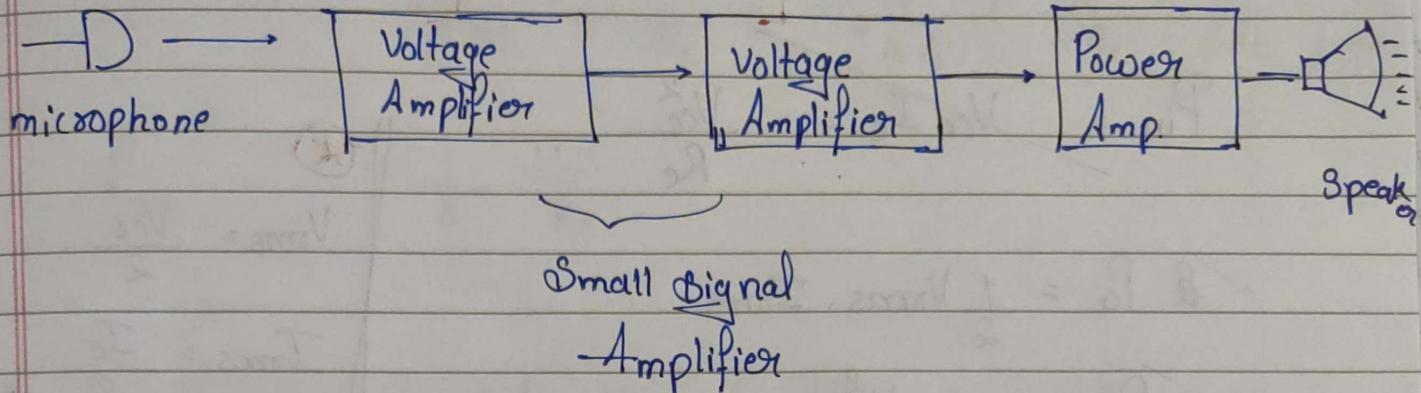
Large Signal Amplifier (Power Amplifier) \Rightarrow




Common Collector $\rightarrow Z_o = \text{Low}$

Types of Power Amplifier \rightarrow

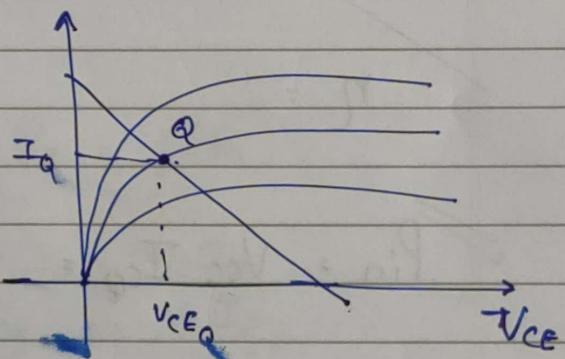- ① Class A \rightarrow Conductn angle is 360°
- ② Class B \rightarrow 180°
- ③ Class AB \rightarrow b/w π to 2π
- ④ Class C \rightarrow conductn $< \pi$



i) Class A \Rightarrow

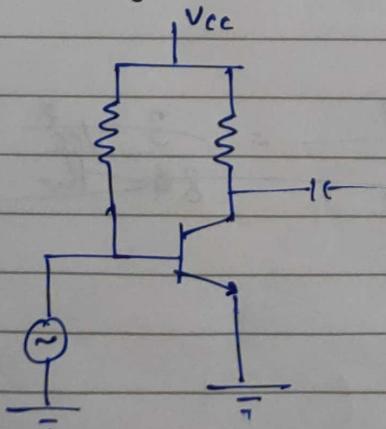

$$P_{in} = V_{cc} (I_c + I_B)$$

$$P_o = \frac{V_{oms}}{\sqrt{2}} \times \frac{I_{oms}}{\sqrt{2}} = \frac{1}{2} V_{oms} I_{oms}$$

$$I_{CQ} \Rightarrow I_B$$

$$\boxed{I_C = \frac{V_{CC}}{R_C}}$$

$$\cancel{P_{in} = V_{CC} I_C = \frac{V_{CC}^2}{R_C}}$$



$$V_{oms} = \frac{V_{CC}}{2}$$

$$\checkmark P_o = \frac{1}{2} V_{oms} \cdot I_{oms}$$

$$I_{oms} = \frac{I_C}{2}$$

$$\checkmark P_o = \frac{1}{8} \frac{V_{CC}^2}{R_C}$$

$$= \frac{V_{CC}}{2R_C}$$

$$\eta = \frac{P_o}{P_i} = \frac{1}{8}$$



$$\eta =$$

$$\cancel{\checkmark P_{in} = V_{CC} I_{CQ} = \frac{V_{CC}^2}{2R_C}}$$

$$\checkmark I_{CQ} = \frac{I_C}{2}$$

$$\eta = \frac{P_o}{P_i} = \frac{1}{4} \Rightarrow \boxed{\eta = 25\%}$$

$$P_{diss.} = P_{in} - P_o = \frac{V_{CC}^2}{2R_C} - \frac{V_{CC}^2}{8R_C} = \frac{3}{8} \frac{V_{CC}^2}{R_C}$$

$$\checkmark P_{R_C} = I_{CQ}^2 R_C = \frac{I_C^2 R_C}{4}$$


$$\frac{1}{2} - \frac{\text{Date}}{\text{Page}} - \frac{1}{4} = \frac{4-1}{8}$$

$$P_{\text{dissipation}} = P_{\text{in}} - P_0 - P_{R_C}$$

$$= \frac{V_{CC}^2}{2R_C} - \frac{V_{CC}^2}{8R_C} - \frac{I_C^2 R_C}{4} = \frac{V_{CC}^2}{2R_C} - \frac{V_{CC}^2}{8R_C} - \frac{V_{CC}^2}{4R_C}$$

$$P_{\text{diss.}} = \frac{1}{8} \frac{V_{CC}^2}{R_C}$$
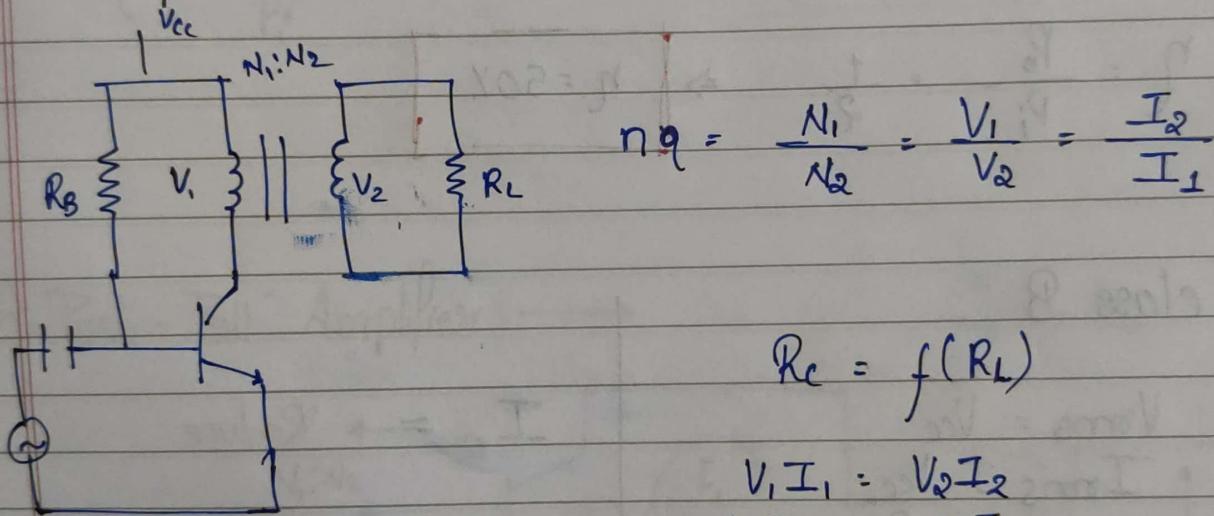
#) Transformer Coupled class A Power Amplifier \Rightarrow



$$nq = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$$

$$R_C = f(R_L)$$

$$V_1 I_1 = V_2 I_2$$

$$\frac{V_1 I_1}{I_1^2} = \frac{V_2 I_2}{I_2^2}$$

$$-\frac{V_1}{I_1} = \frac{V_2}{I_2} \times \frac{I_2}{I_1}$$

$$R_C = \frac{V_2}{I_2} n^2$$

$$R_C = n^2 R_L$$

$$V_{CEQ} \approx V_{CC}$$

$$V_{RMS} = V_{CC}$$

$$I_{RMS} = \frac{V_{CC}}{R_C}$$

$$P_{in} = V_{CC} \cdot I_{RQ} = V_{CC} \cdot \frac{V_{CC}}{R_C}$$

$$P_{in} = \frac{V_{CC}^2}{2R_C}$$

$$P_{out} = \frac{1}{2} V_{RMS} I_{RMS} = \frac{V_{CC}^2}{2R_C}$$

$$\eta = \frac{P_o}{P_i} = \frac{1}{2} \Rightarrow \boxed{\eta = 50\%}$$

A class B

$$V_{RMS} = V_{CC}$$

$$I_{RMS} = \frac{V_{CC}}{R_C}$$

$I_e \rightarrow$ Reduce

$$P_{in} = V_{CC} \cdot I_{RQ}$$

$$P_{in} = \frac{V_{CC}^2}{2R_C}$$

$$P_o = \frac{1}{2} V_{RMS} I_{RMS}$$

$$P_o = \frac{1}{2} V_{CC} \cdot \frac{V_{CC}}{R_C} = \frac{V_{CC}^2}{2R_C}$$

$$\eta = \frac{P_o}{P_i} = \frac{1}{2}$$

$$P_{out} = \frac{1}{2} (V_{rms} \cdot I_{rms})$$


Half wave

$$P_0 = \frac{1}{2} (V_m \cdot I_m) \quad P_0 = \frac{1}{2} \left(\frac{V_{rms}}{\sqrt{2}} \cdot \frac{I_{rms}}{\sqrt{2}} \right) = \frac{1}{4} V_{rms} I_{rms}$$


$$P_0 = \frac{1}{4} \frac{V_{cc}^2}{R_c}$$


$$\eta = -\frac{P_0}{P_i} = -\frac{\pi}{4} \Rightarrow [\eta = 78.54\%]$$

A) Push-Pull Amplifier →

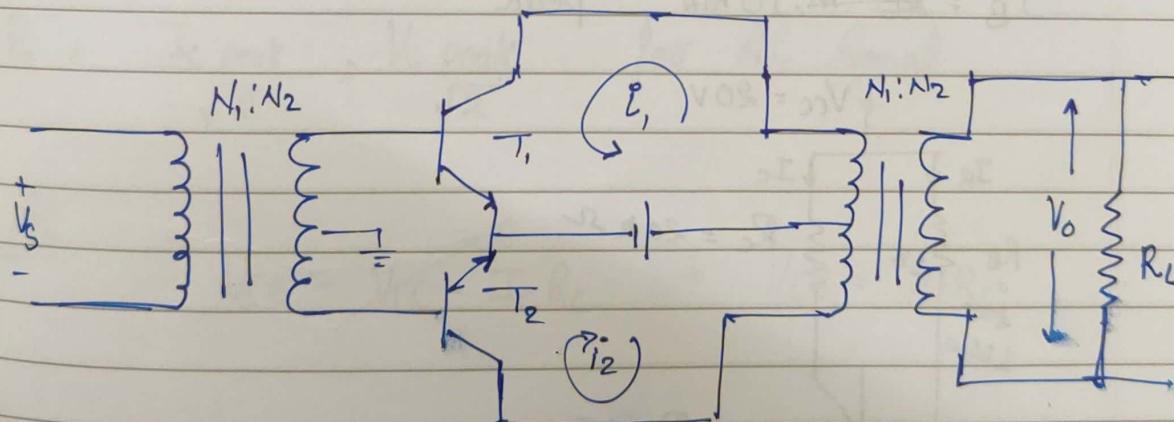


Cross over Dis Distortion

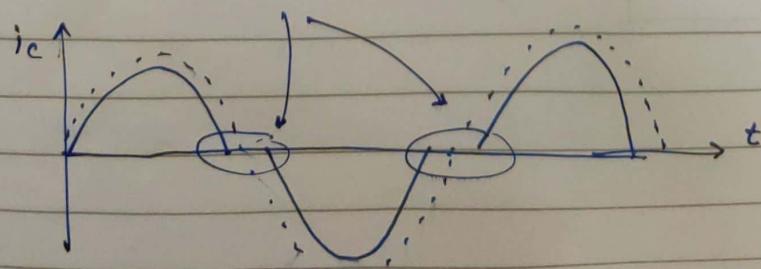

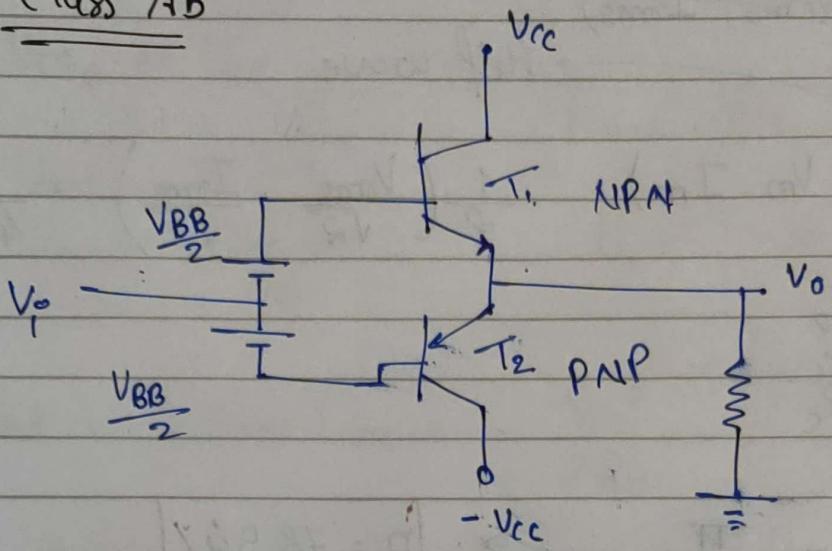Class AB

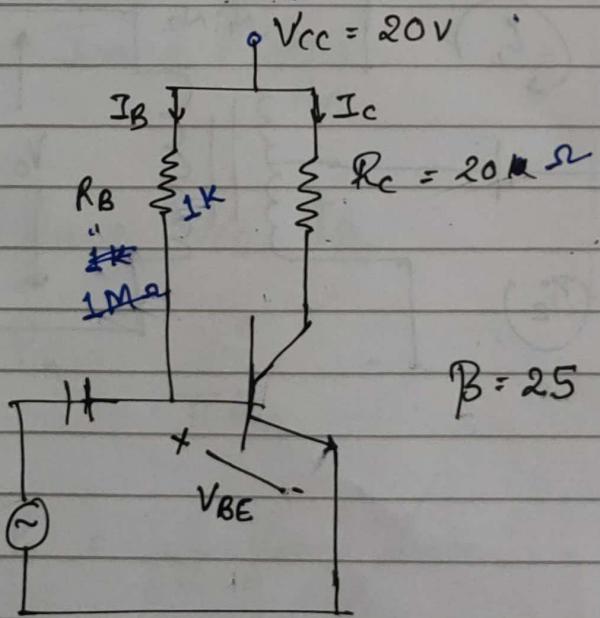Ques.) P_{in} , P_o , η & max. value of these quantities
 $I_B = 20 \text{ mA}$ peak



$$P_i = V_{cc} I_{cQ}$$

$$V_{cc} - I_c R_c - V_{CE} = 0$$

$$V_{CE} = 20 - 20 \times 10^3 I_c$$

$$V_{CEQ} = 20 \left(1 - \frac{I_c}{10^3} \right)$$

$$V_{cc} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{20 - 0.7}{10^3} = 19.3 \text{ mA}$$

$$I_{cQ} = \beta I_B = 482.5 \text{ mA}$$

$$V_{CEQ} = 20 \left(1 - \frac{482.5}{10^3} \right)$$

$$V_{CEQ} = 10.35 \text{ V}$$

$$I_{cQ} = 482.5 \text{ mA}$$

$$I_{cQ} = 0.48 \text{ mA}$$


$$P_i = 20 \times 0.482 \Rightarrow P_i = 9.64 \text{ W}$$

$$P_o = \frac{I_c \text{ peak}}{\sqrt{2}} \times \frac{V_c \text{ peak}}{\sqrt{2}} \quad \text{for AC Signal}$$

AC

$$V_{CE} = V_{cc} - I_c R_c \Rightarrow V_{CE} = I_c R_c$$

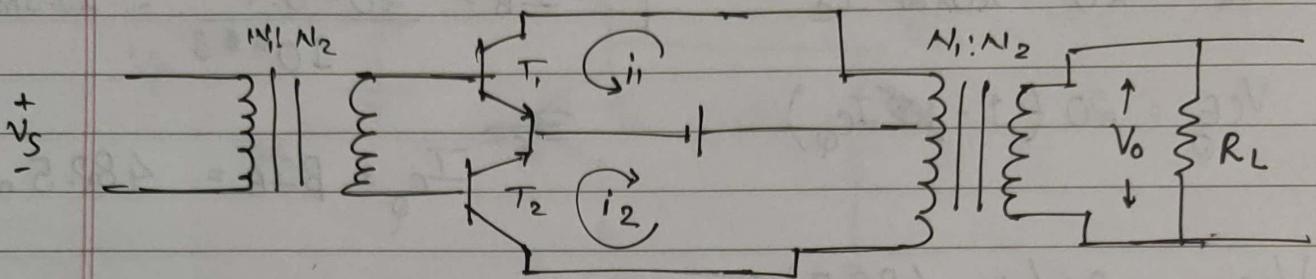Ques) Determine P_i , P_o , η & maximum value of these quantities for push pull amplifier shown below?



$$V_{cc} = 30V, R_L = 16\Omega, \frac{N_1}{N_2} = 2, I_{peak} = 1A$$

\Rightarrow

$$P_{in} = V_{cc} I_{CQ}$$

$$\eta = \frac{N_1/2}{N_2} = 0.1$$

$$P_{in} = \frac{2V_{cc}}{\pi} I_{peak}$$

for

$$P_{in\ max} = \frac{2V_{cc}}{\pi} I_{peak(max)}$$

$$R'_L = n^2 R_L$$

$$R'_L = 16$$


$$P_o(ac) = \frac{I_p^2 R'_L}{2} = 8W$$

Combination Network \Rightarrow

Ques. 1) Find V_D & V_C , $V_B \approx 3.62 V$, $B = 180$

$$I_{DSS} = 12 \text{ mA}$$

$$V_P = -6V$$

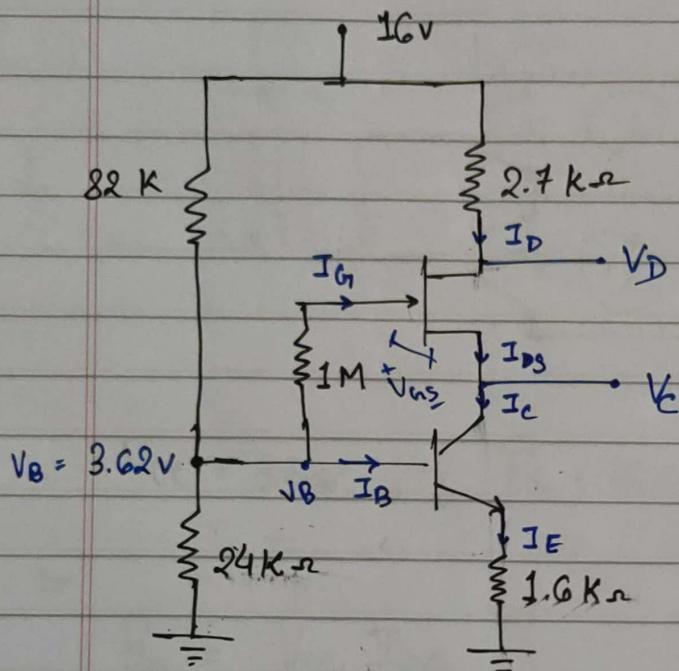

$$I_D = I_S$$

$$I_S = I_C$$

$$I_E = I_C + I_B$$

\Rightarrow

$$I_G = 0$$

$$\begin{aligned} V_{GS} &= V_G - V_S \\ &= V_G - V_C \end{aligned}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



$$3.62 - V_{BE} - I_E R_E = 0$$

$$I_E = \frac{3.62 - 0.7}{1.6 \times 10^3}$$

$$\checkmark I_E = 1.14 A \quad 1.82 \text{ mA}$$

$$I_C = I_E = 1.82 \text{ mA}$$

$$I_E = \frac{V_E}{R_E} =$$

$$I_C = I_S$$

$$I_S = I_D = 1.82 \text{ mA}$$

$$\begin{aligned} V_D &= V_{DD} - I_{DRD} \\ &= 16 - 1.82 \times 2.7 \\ \checkmark V_D &= 11.086 \text{ V} \end{aligned}$$

$$I_c = \beta I_B \Rightarrow I_B = 10.1 \text{ mA}$$

$$V_B - R_G I_G - V_{G_S}^o = V_C \Rightarrow V_C = V_B - V_{G_S}$$


$$I_D = I_{DSS} \left(1 - \frac{V_{G_S}}{V_P} \right)^2$$

$$V_{G_S} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) = -6 \left(1 - \sqrt{\frac{1.82}{12}} \right)$$

$$V_{G_S} = -3.66 \text{ V}$$

$$V_{as} < \begin{cases} -3.66 \text{ V} \\ -8.33 \text{ V} \end{cases}$$

$$V_C = 3.62 - ($$

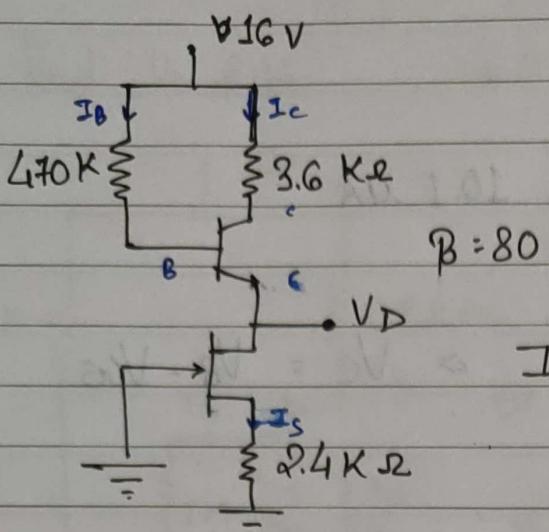Que.2) V_D ?

$$I_{DSS} = 8\text{ mA}$$

$$V_P = -4\text{ V}$$

→

$$16 - 3.6 \times 10^3 I_D - V_{CE} = V_D$$

$$I_E = I_D = I_S \quad \left| \quad -V_{GS} - R_S I_S = 0 \right.$$

$$V_{GS} = -I_S R_S$$

$$V_{GS} = -I_D R_S$$

$$I_D = I_{DD} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 8 \times 10^{-3} \left(1 + \frac{I_D \times 2.4 \times 10^3}{(-4)} \right)^2$$

$$I_D = 1.1 \text{ mA}, 2.62 \text{ mA} \quad \left| \quad I_E = 1.1 \text{ mA} \right.$$

$$V_{GS} = -1.1 \times 2.4$$

$$V_{GS} = -2.64$$


$$I_E = (\beta + 1) I_B$$

$$I_B = 13.5 \mu\text{A}$$

$$16 - 470 \times 10^3 I_B - V_{BE} = V_D$$

$$V_D = 16 - 470 \times 10^3 \times 13.5 \times 10^{-6} - 0.7$$

$$V_D = 8.955 \text{ V}$$

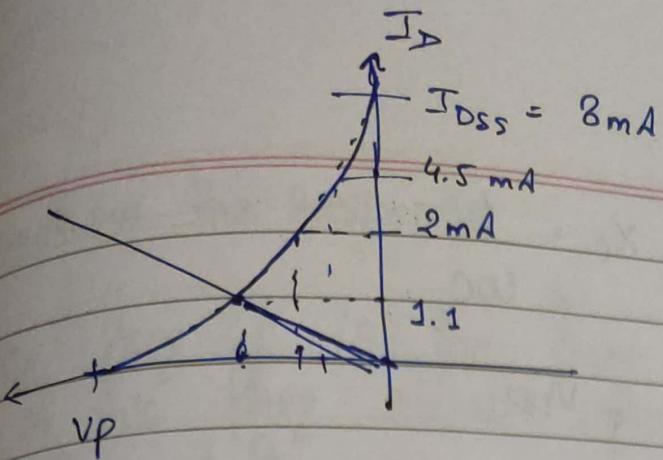

classmate


Date 21 Nov/24
Page

$$V_{DS} = \frac{V_P}{2} \Rightarrow I_D = 2 \text{ mA}$$

$$V_{GS} = \frac{V_P}{4} \Rightarrow I_D = 4.5 \text{ mA}$$

Frequency Response of JFET \Rightarrow

- Low freq.
High freq.

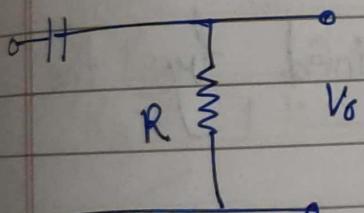

$$V_o = \frac{R}{R + X_C} V_i$$

$$|V_o| = \frac{RV_i}{\sqrt{R^2 + X_C^2}}$$


$$\text{where } X_C = R, \quad V_o = \frac{1}{\sqrt{2}} V_i$$

the frequency of at which $X_C = R$

$$X_C = R \Rightarrow \frac{1}{2\pi f C} = R \Rightarrow f = \frac{1}{2\pi R C}$$

i) Low Frequency $\Rightarrow X_C = \frac{1}{\omega C}$

① $C_G \Rightarrow$

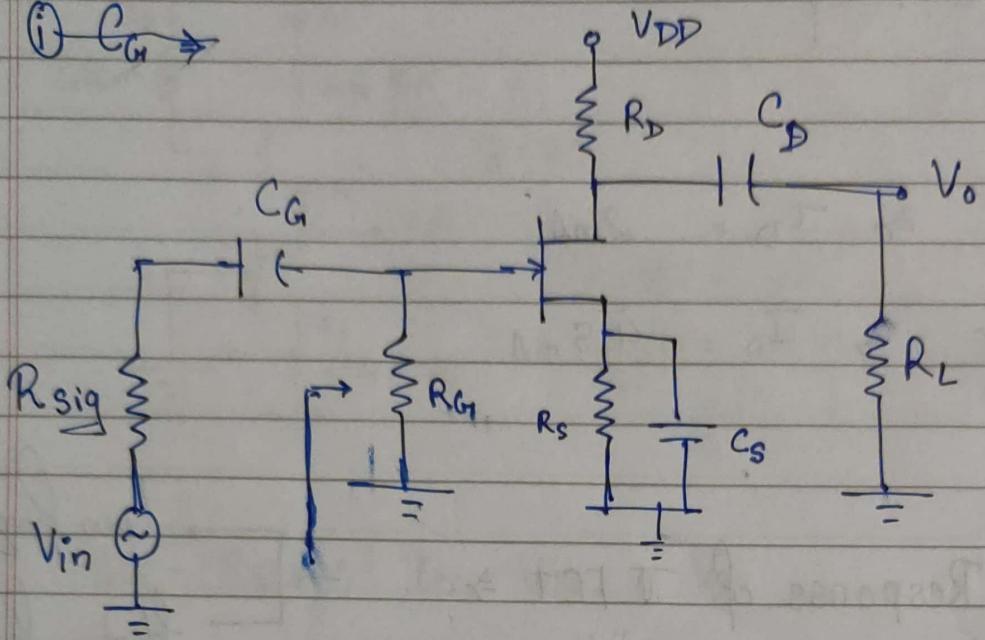

The low freq. Response is determined by the Coupling & Bypass Capacitor.

① $C_G \Rightarrow$

$$f_{CG} = \frac{1}{2\pi(R_{sig} + Z_i)C_G}, \quad Z_i = R_G$$

② $C_D \Rightarrow$

$$f_{CD} = \frac{1}{2\pi(R_L + Z_o)C_D}, \quad Z_o = R_D$$

③ $C_S \Rightarrow Z_o = R_s \parallel \frac{1}{g_m}$

$$f_{CS} = \frac{1}{2\pi(R_s \parallel \frac{1}{g_m})C_S}$$

measure the response

The freq. of this freq. output voltage $V_o = 0.707 V_i$ &
 $P_o = \frac{1}{2} P_i$.

or in terms of Gain, Gain is 3dB less.

Ques.) Determine lower cutoff freq. using low freq. response
 given $C_G = 0.01 \mu F$, $C_D = 0.5 \mu F$, $C_S = 0.2 \mu F$
 $R_{sig} = 10 k\Omega$, $R_G = 1 M\Omega$, $R_D = 4.7 k\Omega$,
 $R_S = 1 k\Omega$, $R_L = 2.2 k\Omega$, $I_{DSS} = 8 mA$, $V_P = -4V$

\Rightarrow

$$\checkmark f_{C_G} = \frac{1}{2\pi(10 \times 10^3 + 10^6) \times 0.01 \times 10^{-6}} = \cancel{1.57 \text{ Hz}} \quad 15.7 \text{ Hz}$$

$$\checkmark f_{C_D} = \frac{1}{2\pi(2.2 \times 10^3 + 4.7 \times 10^3) 0.5 \times 10^{-6}} = 46 \text{ Hz}$$

$$g_{mo} = \left| \frac{2 I_{DSS}}{V_P} \right| = \left| \frac{-16}{4} \right| = 4 mA$$

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$V_{GS} = - I_D R_S$$

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{(-4)} \right)^2$$

$$I_D = 8 \times 10^{-3} \left(1 - \frac{I_D \times 10^3}{4} \right)^2$$

$$I_D = 2 \text{ mA}, 8 \text{ mA}$$

$$V_{GS} = -2 \text{ V}$$



$$g_m = 4 \left(1 - \frac{2}{4} \right) = 2 \text{ mS}$$

$$f_{CS} = \frac{1}{2\pi \left(R_S \parallel \frac{1}{g_m} \right) C_S} = \frac{1}{2\pi \left(10^3 \parallel \frac{10^3}{2} \right) 2 \times 10^{-9}}$$

$$\checkmark f_{CS} = 238.73 \text{ Hz}$$

Lower Cutoff freq = $f_L = f_{CS} = 238.73 \text{ Hz}$
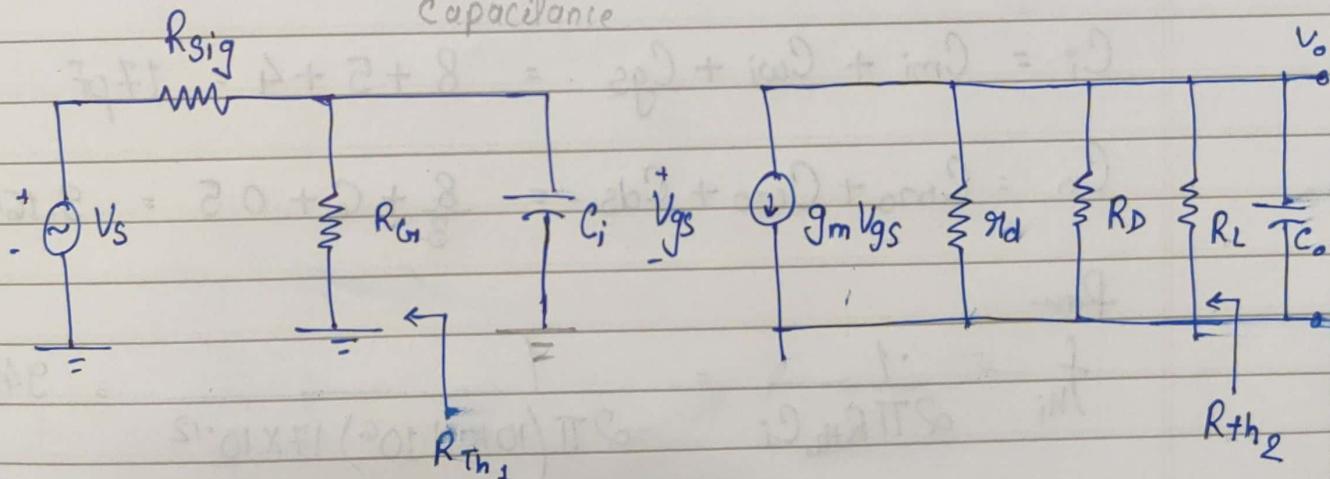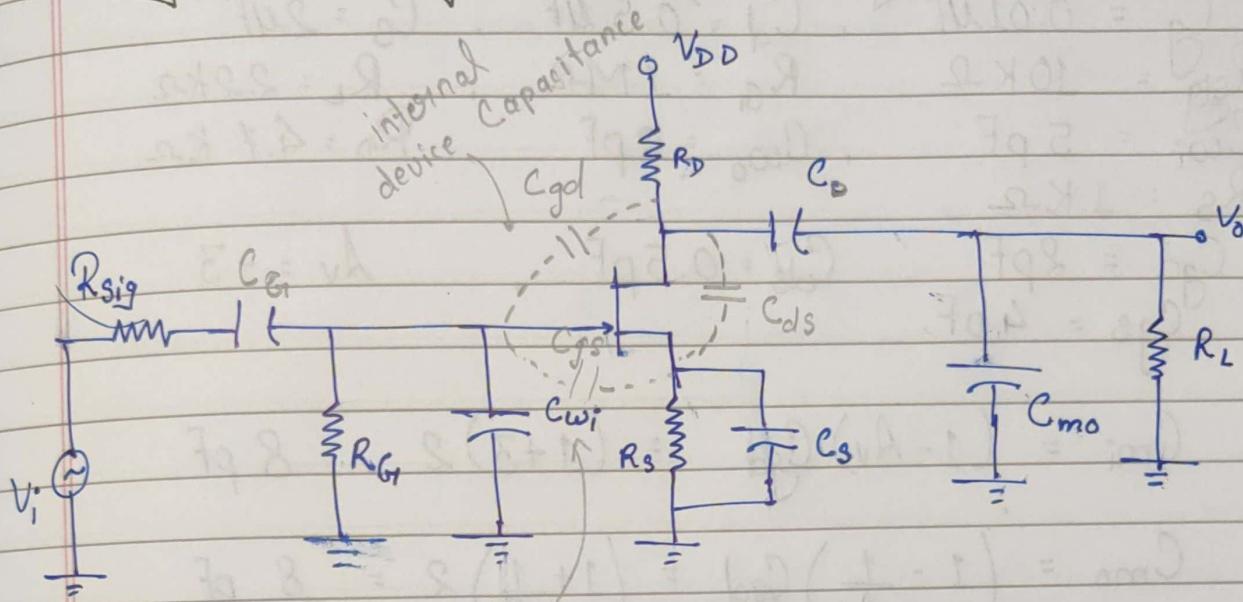
#) High Frequency Response of FET \Rightarrow



$$f_{Hi} = \frac{1}{2\pi R_{Th_1} C_i}$$

$$R_{Th_1} = R_{sig} \parallel R_{Gf}$$

$$C_i = C_{wi} + C_{gs} + C_m$$

$$C_m = (1 - A_v) C_{gd}$$

$$f_{Ho} = \frac{1}{2\pi R_{Th_2} C_o}$$

$$R_{Th_2} = r_d \parallel R_D \parallel R_L$$

$$C_o = C_{wi} + C_{ds} + C_{m0}$$

$$C_{m0} = \left(1 - \frac{1}{A_v}\right) C_{gd}$$

Que.) Determine High Cutoff freq for the fig.

$$C_g = 0.01 \mu F, C_d = 0.5 \mu F, C_s = 2 \mu F$$

$$R_{sig} = 10 k\Omega, R_G = 1 M\Omega, R_L = 2.2 k\Omega$$

$$C_{wi} = 5 \text{ pF}, C_{wo} = 6 \text{ pF}, R_D = 4.7 k\Omega$$

$$R_S = 1 k\Omega$$

$$C_{gd} = 2 \text{ pF}, C_{ds} = 0.5 \text{ pF}, A_v = -3$$

$$C_{gs} = 4 \text{ pF}$$

\Rightarrow

$$C_{mi} = (1 - A_v) C_{gd} = (1 + 3) 2 = 8 \text{ pF}$$

$$C_{mo} = \left(1 - \frac{1}{A_v}\right) C_{gd} = \left(1 + \frac{1}{3}\right) 2 = \frac{8}{3} \text{ pF}$$

$$C_i = C_{mi} + C_{wi} + C_{gs} = 8 + 5 + 4 = 17 \text{ pF}$$

$$C_o = C_{mo} + C_{wo} + C_{ds} = \frac{8}{3} + 6 + 0.5 = 9.166 \text{ pF}$$

f_{Hi}

$$f_{Hi} = \frac{1}{2\pi R_{th} C_i} = \frac{1}{2\pi (10k \parallel 10^6) 17 \times 10^{-12}} = 945.5 \text{ kHz}$$

$$= 0.94 \text{ MHz}$$

$$f_{Ho} = \frac{1}{2\pi R_{th} C_o} = \frac{1}{2\pi (\frac{1}{R_d} \parallel \frac{1}{R_D} \parallel \frac{1}{R_L}) C_o}$$

$$= \frac{1}{2\pi \left(\frac{1}{9.166 \times 10^{-12}} \right)} = 11.6 \text{ MHz}$$

✓ Higher Cutoff = $\min(f_{Hi}, f_{Ho}) = 0.94 \text{ MHz}$