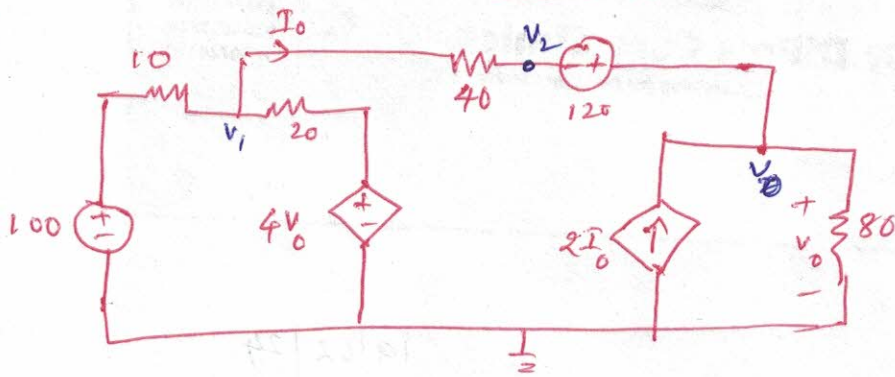


LNT - Key

①

Q1



Let V_1, V_2 be the non-reference voltages.

Applying KCL at Node 1:

$$\frac{V_1 - 100}{10} + \frac{V_1 - 4V_0}{20} + \frac{V_1 - V_2}{40} = 0$$

But $V_2 = V_0 - 120$

\therefore

$$7V_1 - 9V_0 = 280 \quad \text{--- ①} \rightarrow 0.5M$$

At node 2:

$$-I_0 - 2I_0 + \frac{V_0}{80} = 0 \Rightarrow 3I_0 = \frac{V_0}{80}$$

but $I_0 = \frac{V_1 + 120 - V_0}{40}$

$$\Rightarrow 3 \left(\frac{V_1 + 120 - V_0}{40} \right) = \frac{V_0}{80}$$

$$6V_1 - 7V_0 = -720 \quad \text{--- ②} \rightarrow 0.5M$$

From ① & ②

$$\begin{bmatrix} 7 & -9 \\ 6 & -7 \end{bmatrix} \begin{bmatrix} V_1 \\ V_0 \end{bmatrix} = \begin{bmatrix} 280 \\ -720 \end{bmatrix}$$

$$\Delta = 5$$

$$\Delta_1 = -8440$$

$$\Delta_2 = -6720$$

} 1M


$$V_1 = \frac{\Delta_1}{\Delta} = -1688V. \quad \text{--- 1}$$

$$V_0 = \frac{\Delta_2}{\Delta} = -1344V. \quad \text{--- 1}$$

$$I_0 = -5.6A. \quad \text{--- 1}$$

Handwritten notes at the bottom right, including a date '4/5/2024' and some illegible text.

Q2:

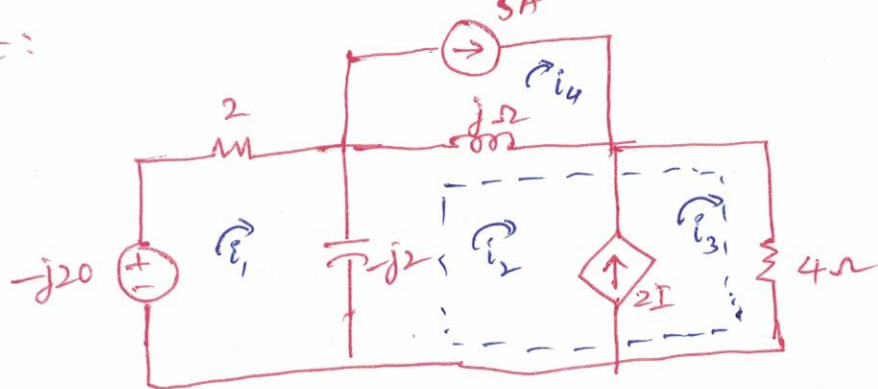

For Mesh 1: $-j20 - 2i_1 + j2(i_1 - i_2) = 0$

$$(-1 + j)i_1 - (j)i_2 = j10 \quad \text{--- (1) --- IM}$$

For Super Mesh: $-(-j2)(i_2 - i_1) - 1j(i_2 - i_4) - 4i_3 = 0$

$$i_4 = 5A, \quad i_3 - i_2 = 2I = 2(i_1 - i_2) \Rightarrow i_3 = 2i_1 - i_2$$

$$\therefore (-8 - j2)i_1 + (4 + j)i_2 = -5j \quad \text{--- (2) --- IM}$$

$$\begin{bmatrix} -1 + j & -1j \\ -8 - j2 & 4 + j \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} j10 \\ -5j \end{bmatrix}, \quad \left. \begin{array}{l} \Delta = -3 - 5j \\ \Delta_1 = -5 + 40j \\ \Delta_2 = -15 + 85j \end{array} \right\} 1.5M$$

$$I = I_1 - I_2 = \frac{\Delta_1 - \Delta_2}{\Delta} = 5.7 + j5.4 \text{ or } 7.9 \angle 43.4^\circ A$$


→ 1.5M

Q3: By using Super position theorem, V_0 can be expressed

as

$$V_0 = V_1 + V_2 + V_3$$

With 10V:

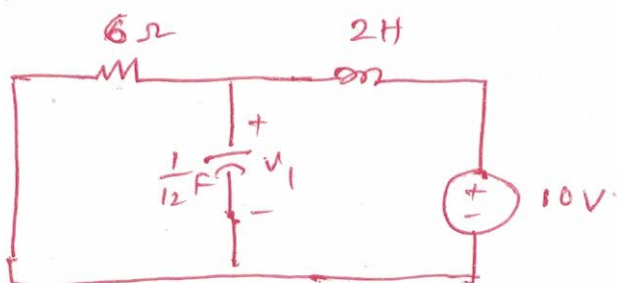


$$V_1 = 10V \quad \text{--- IM}$$

with $4A$:

$$\omega = 2, \quad j\omega L = j4 \Omega$$

$$\frac{1}{j\omega C} = -j6 \Omega$$

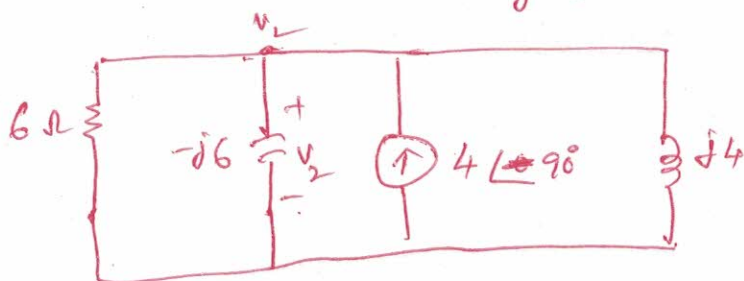


Apply in KCL,

$$\frac{v_2}{6} + \frac{v_2}{-j6} + \frac{v_2}{j4} = -4j$$

$$(0.16 - 0.083j) v_2 = -4j \Rightarrow v_2 = 9.6 - 19.2j$$

or
 $= 21.4 \angle -63^\circ$

12V Source:

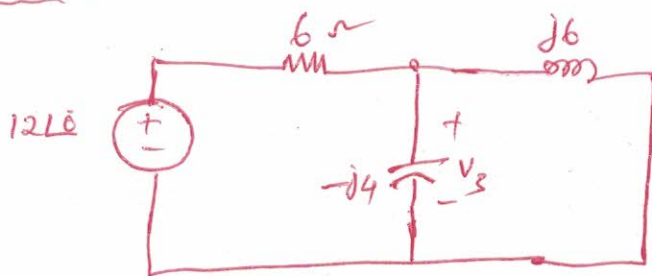

$$\omega = 3,$$

$$j\omega L = j6$$

$$\frac{1}{j\omega C} = -j4$$


$$\frac{v_3 - 12}{6} + \frac{v_3}{-j4} + \frac{v_3}{j6} = 0 \Rightarrow v_3 \left(\frac{1}{6} + \frac{1}{-j4} + \frac{1}{j6} \right) = 2$$

$$v_3 = 9.6 - 4.8j \quad \text{or} \quad 10.73 \angle -26.56^\circ$$

$$v_o = 10 + 21.45 \cos(2t - 63^\circ) + 10.73 \cos(3t - 26.56^\circ) \text{ V.}$$

Q4: — Transform all elements to frequency domain.

Zth. calculation:

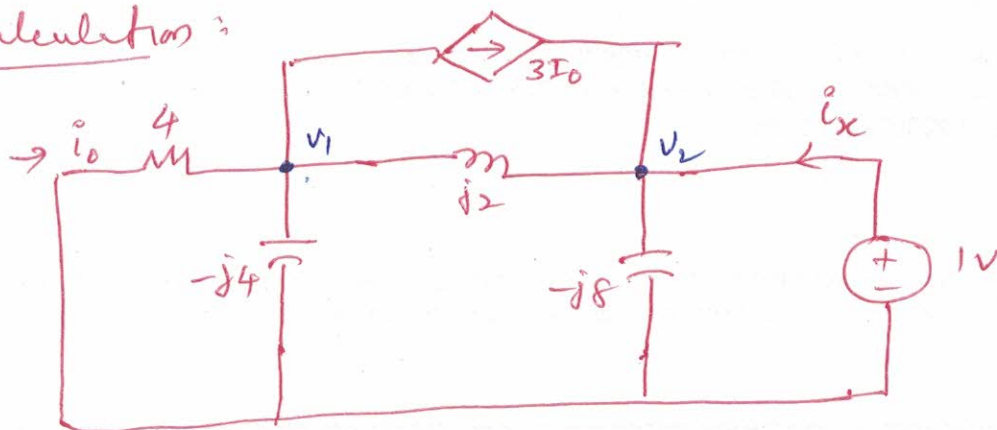

Apply KCL at node 1

$$\frac{V_1}{4} + \frac{V_1}{-j4} + 3\vec{i}_0 + \frac{V_1 - 1}{j2} = 0 \quad \text{where } \vec{i}_0 = \frac{-V_1}{4}$$

$$\therefore \frac{V_1}{-j4} - \frac{2V_1}{4} = \frac{1 - V_1}{j2} \Rightarrow V_1 \left(\frac{1}{-j4} - \frac{1}{2} + \frac{1}{j2} \right) = \frac{1}{j2}$$

$$\boxed{V_1 = 0.4 + j0.8}$$


At node 2:

$$I_x + 3I_0 = \frac{1}{-j8} + \frac{1 - V_1}{j2}$$

$$I_x = (0.75 + j0.5)V_1 - j\frac{3}{8} = -0.1 + j0.425$$

$$\therefore Z_{th} = \frac{1}{I_x} = -0.52 - j2.2 = \text{or } \underline{2.29 \angle -103.2^\circ \Omega} \quad - 2M$$

V_{th} Calculation:

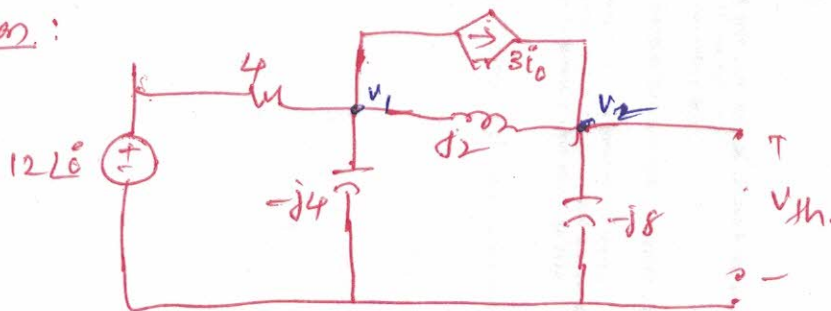

At node 1:

$$\frac{12 - V_1}{4} = 3\vec{i}_0 + \frac{V_1}{-j4} + \frac{V_1 - V_2}{j2} \quad \text{where } \vec{i}_0 = \frac{12 - V_1}{4}$$

$$(2 + j)V_1 - j2V_2 = 24 \quad \text{--- (1)}$$

At node 2:

$$\frac{V_1 - V_2}{j2} + 3\vec{i}_0 = \frac{V_2}{-j8} \Rightarrow (6 + j4)V_1 - j3V_2 = 72 \quad \text{--- (2)}$$

$$\begin{bmatrix} 2+j & -j2 \\ 6+j4 & -j3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 24 \\ 72 \end{bmatrix}$$

$$\Delta = -5 + j6$$


$$A_2 = -j24; \quad V_{th} = V_2 = 3 \angle -219.8^\circ \quad \rightarrow 2M$$

$$V_0 = \frac{2}{2 + Z_{th}} \cdot V_{th} = \underline{2.3 \angle -163.3^\circ \text{ V}} \quad - 1M$$

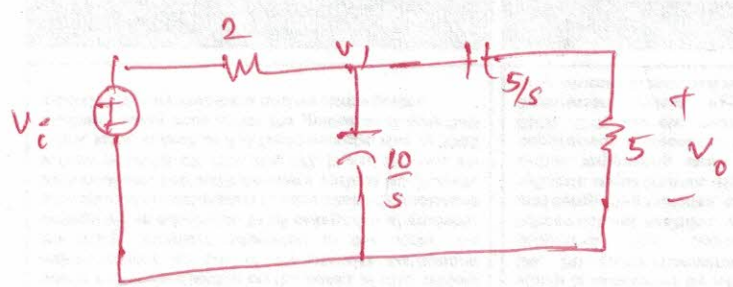Q5: Transform all elements to Freq. Domain.

$$0.2F \rightarrow \frac{1}{s\omega C} = \frac{1}{s(0.2)} = \frac{5}{s}$$

$$0.1F = \frac{1}{s(0.1)} = \frac{10}{s}$$



$$\text{Let } Z = \frac{10}{s} \parallel (5 + \frac{5}{s}) = \frac{10(s+1)}{s(s+3)} \quad \text{--- IM}$$

$$V_1 = \frac{Z}{Z+2} V_i \quad ; \quad V_o = \frac{5}{5 + \frac{5}{s}} V_1 = \frac{s}{s+1} \cdot \frac{Z}{Z+2} V_i \quad \text{--- IM}$$

$$H(s) = \frac{V_o}{V_i} = \frac{5s}{s^2 + 8s + 5} \quad \rightarrow \text{2M.}$$