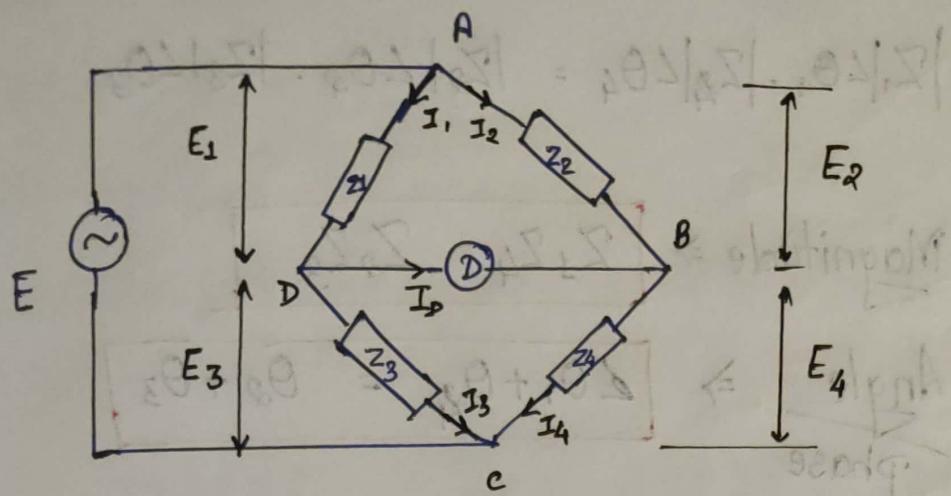


A.C. Bridges

08/0ct/24



Detector (D) →

↳ Head phones : 100 Hz - 4 kHz

↳ Vibrational Galvanometers : 10 Hz - 1 kHz → for low frequency ($f \leq$)

↳ Tunable ckt : 100 Hz - 10 kHz

↳ CRO : High frequency

• Bridge Balanced →

$$\text{i) } I_D = 0$$

$$\text{ii) } V_B = V_D$$

$$\text{iii) } E_1 = E_2 \quad \& \quad E_3 = E_4$$

$$E_1 = E_2 \\ Z_1 I_1 = Z_2 I_2$$

$$Z_1 \frac{E}{Z_1 + Z_3} = Z_2 \frac{E}{Z_2 + Z_4}$$

$$Z_1 Z_2 + Z_1 Z_4 = Z_2 Z_3 + Z_2 Z_4$$

$$\boxed{Z_1 Z_4 = Z_2 Z_3}$$

↳ for bridge to be balanced

$$Z = R + jL$$

$$Z = M \angle \theta$$

$$= M e^{j\theta}$$

$$Z_1 Z_4 = Z_2 Z_3$$

$$|Z_1| \angle \theta_1 \cdot |Z_4| \angle \theta_4 = |Z_2| \angle \theta_2 \cdot |Z_3| \angle \theta_3$$

Magnitude $\Rightarrow Z_1 Z_4 = Z_2 Z_3$

Angle $\Rightarrow \angle \theta_1 + \theta_4 = \theta_2 + \theta_3$
phase

Eg $\Rightarrow Z_1 = 400 \angle 50^\circ, Z_3 = 800 \angle -50^\circ$

$$Z_2 = 200 \angle 40^\circ, Z_4 = 400 \angle 20^\circ$$

$$\Rightarrow Z_1 Z_4 = 160000$$

$$\theta_1 + \theta_4 = 70^\circ$$

$$Z_2 Z_3 = 160000$$

$$\theta_2 + \theta_3 = -10^\circ$$

Bridge if $\theta_1 + \theta_4 \neq \theta_2 + \theta_3$
 \hookrightarrow imbalance

Eg) An A.C. bridge ckt working at 1000Hz as shown in fig

Arm AB is $0.2 \mu F$ (Pure Capacitance), arm BC = 500Ω

Arm CD contain Unknown impedance & arm DA = 300Ω (Pure Resistance)

in parallel with $0.1 \mu F$ Capacitor. Find R & C for R_C

constants of arm CD. Consider it is a series ckt.

(Balanced)

08/0ct/24

$$\Rightarrow f = 1000\text{Hz}$$

$$\omega = 2\pi f$$

$$AB \rightarrow Z_2 = 0.2\mu F \Rightarrow Z_2 = \frac{1}{j\omega C} = -7957.7j$$

$$BC \rightarrow Z_4 = 500\Omega$$

$$CD \rightarrow Z_3$$

~~$$DA \rightarrow Z_6 = 300 \parallel 0.1\mu F = 300 \parallel \frac{1}{j\omega C} = 300 \parallel -15915.5j$$~~

$$Z_2 = -7957.7j, Z_1 = 299.95 \angle -1.079^\circ \\ = 7957.7 \angle -90^\circ$$

$$Z_1 Z_4 = Z_2 Z_3$$

~~$$149973 \angle -1.0798^\circ = Z_3 \cdot (-7957.7 \angle 7957.7 \angle -90^\circ)$$~~

~~$$Z_3 = 18.846 \angle 88.92^\circ$$~~


$$Z_2 = -7957.7j, Z_1 = 300 \parallel 0.1\mu F = 300 \parallel \frac{1}{j\omega C}$$

~~$$= 300 \parallel -15915.5j$$~~

$$Z_1 =$$

$$= R$$

Maxwell's Inductance Bridge

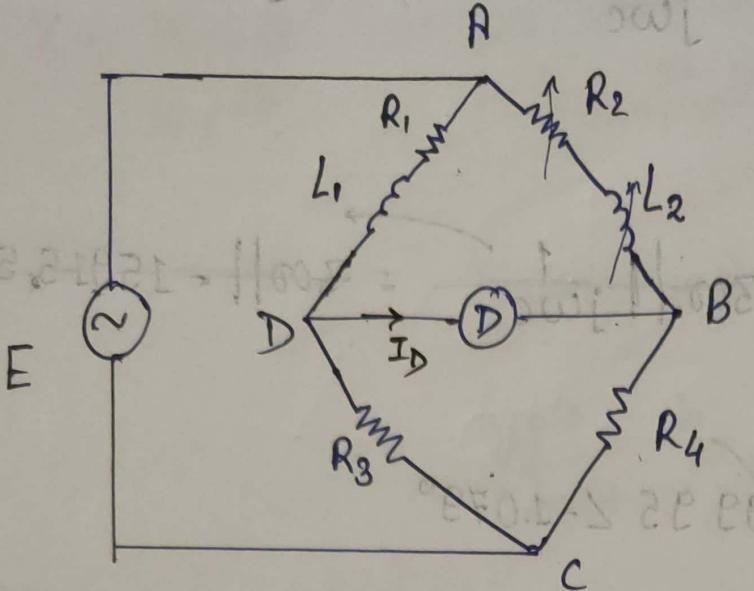

$$Z_1 Z_4 = Z_3 Z_2$$

$$(R_1 + j\omega L_1) R_4 = R_3 (R_2 + j\omega L_2)$$

$$R_1 R_4 + j\omega R_4 L_1 = R_2 R_3 + j\omega R_3 L_2$$

Equating real & imaginary Part

$$R_1 R_4 = R_2 R_3 \quad | \quad R_4 L_1 = R_3 L_2$$


$$R_1 = \frac{R_3}{R_4} \cdot R_2$$

$$L_1 = \frac{R_3}{R_4} \cdot L_2$$

08/Oct/24

Schering Bridge \Rightarrow (capacitance Measuring)

R_4, C_4 are Unknowns

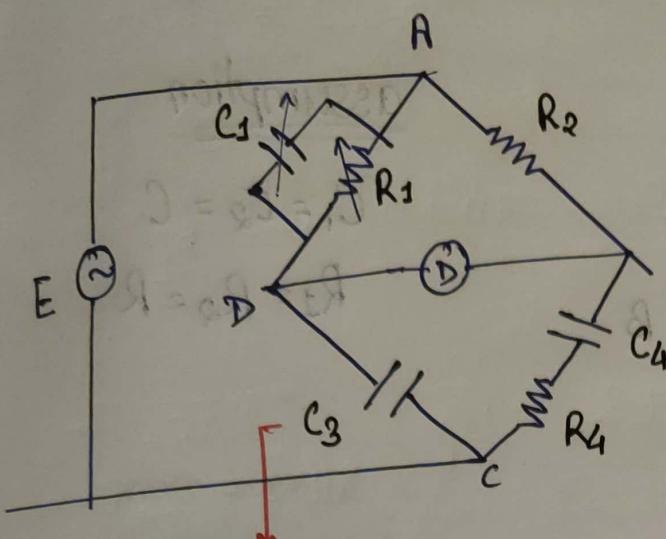

Standard Capacitor

Balanced Bridge

opposite arm
Should have parallel
& series combination
of R & C.

$$Z_1 Z_4 = Z_2 Z_3$$

$$\frac{R_1}{1 + j\omega R_1 C_1} \cdot \left(R_4 + \frac{1}{j\omega C_4} \right) = R_2 \left(\frac{1}{j\omega C_3} \right)$$

$$R_1 R_4 + \frac{R_1}{j\omega C_4} = \frac{R_2 (1 + j\omega R_1 C_1)}{j\omega C_3}$$

Real

$$\frac{R_1 R_4}{R_1 R_4} = \frac{R_1 R_2 C_1}{C_3}$$


imag

$$\frac{R_1}{j\omega C_4} = \frac{R_2}{j\omega C_3}$$

$$R_4 = \frac{C_1}{C_3} \cdot R_2$$

$$C_4 = \frac{R_1}{R_2} \cdot C_3$$

Measurement of freq. Using Wein's Bridge

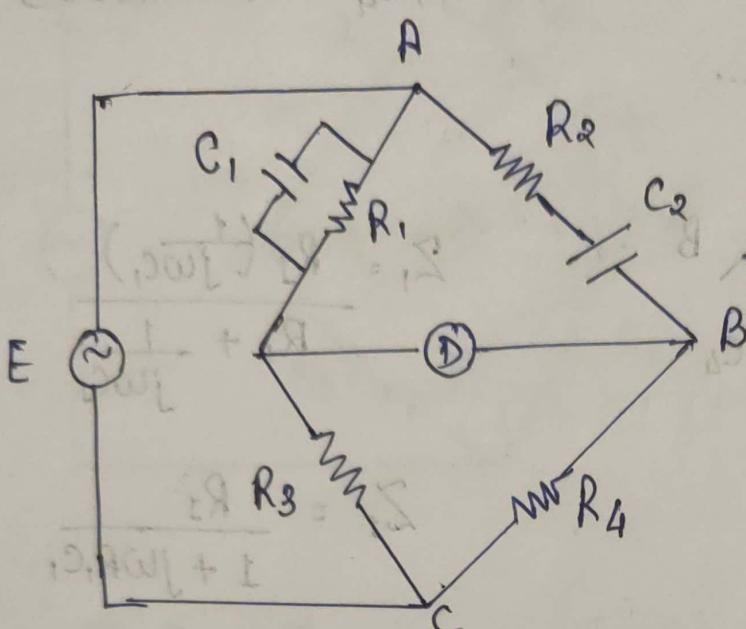

assumption

$$C_1 = C_2 = C$$

$$R_1 = R_2 = R$$

Adjacent arm
Series & parallel
Combination of R & C
rectangle

Balanced Bridge

$$Z_1 Z_4 = Z_2 Z_3$$

$$\frac{R_1}{1 + j\omega R_1 C_1} \cdot R_4 = \left(R_2 + \frac{1}{j\omega C_2} \right) R_3$$

$$\frac{R_1 R_4}{1 + j\omega R C} = R_2 R_3 + \frac{R_3}{j\omega C}$$

$$RR_4 = RR_3 + j\omega R^2 R_3 C + \frac{R_3}{j\omega CR} + \frac{RR_3}{R}$$

Real

$$RR_4 = RR_3 + \frac{R_3}{R}$$

$$RR_4 = 2RR_3$$

$$R_4 = 2R_3$$

$$\text{imag } j\omega R^2 R_3 C + -j\frac{R_3}{\omega RC} = 0$$

$$\omega R^2 C = \frac{1}{\omega RC}$$

$$\omega^2 R^2 C^2 = 1$$

$\Rightarrow \text{emf} = \text{current} \times \text{resistance}$


$\Rightarrow \text{mmf} = \text{flux} \times \text{reluctance} = \phi \cdot R$

$$\phi = \frac{ni}{R}$$

$$R = \frac{l}{\mu A}$$

$$\mu = \mu_a \mu_0$$

#> Maxwell Inductance Bridge \Rightarrow

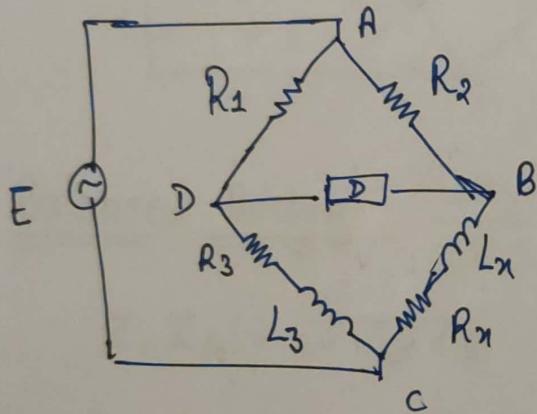

$$Z_1 Z_4 = Z_2 Z_3$$

$$E_{AD} = E_{AB}$$

$$\frac{R_1}{R_3 + j\omega L_3} = \frac{R_2}{R_x + j\omega L_x}$$

$$R_1[R_x + j\omega L_x] = R_2[R_3 + j\omega L_3]$$

Equating



Real Part $\rightarrow R_1 R_x = R_2 R_3$

$$R_x = \frac{R_2 R_3}{R_1}$$

Imag Part $\rightarrow j\omega R_1 L_x = j\omega R_2 L_3$

$$L_x = \frac{R_2 L_3}{R_1}$$

10 Oct 12

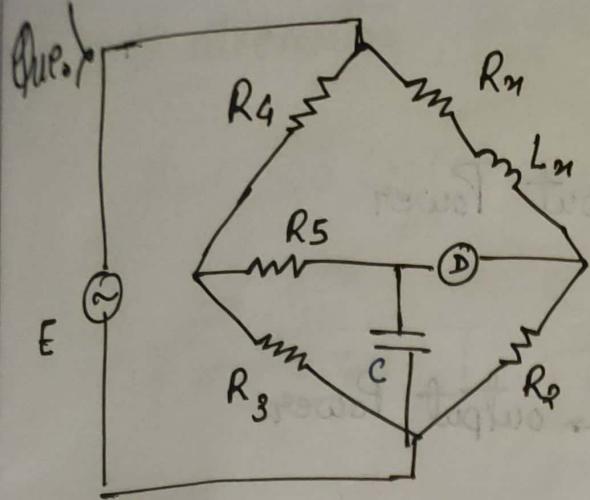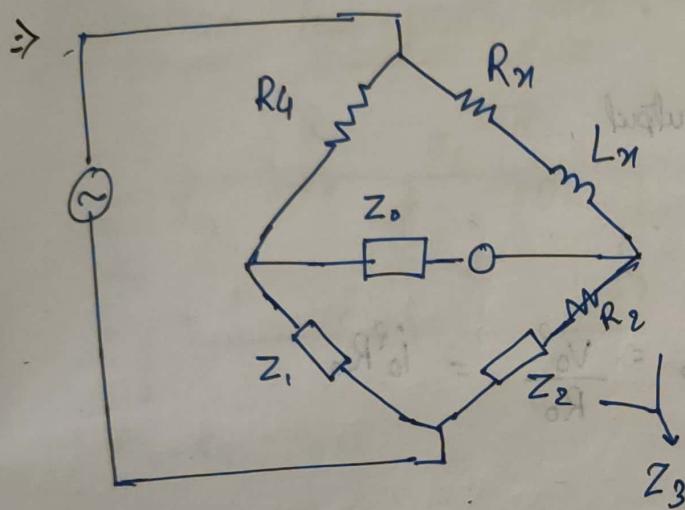 $R_n, L_n ?$ 

$$Z_0 = \frac{R_5 X_C}{R_5 + R_3 + X_C}$$

$$Z_1 = \frac{R_3 R_5}{R_3 + R_5 + X_C}$$

$$Z_2 = \frac{R_3 X_C}{R_3 + R_5 + X_C}$$

$$Z_3 R_4 = (R_n + L_n) Z_1$$

$$\left(R_2 + \frac{R_3 X_C}{R_3 + R_5 + X_C} \right) R_4 = (R_n + L_n) \frac{R_3 R_5}{R_3 + R_5 + X_C}$$


$$X_C = \frac{1}{j\omega C}$$

$$\frac{mV}{90^\circ} = \frac{mV}{90^\circ} \times \frac{1}{j\omega C}$$


17/10/24

Attenuator \Rightarrow
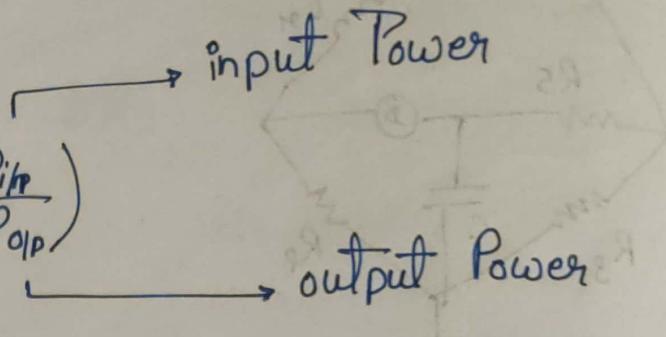
$$\text{Attenuation} = 10 \log \left(\frac{P_{\text{in}}}{P_{\text{out}}} \right)$$




Matched

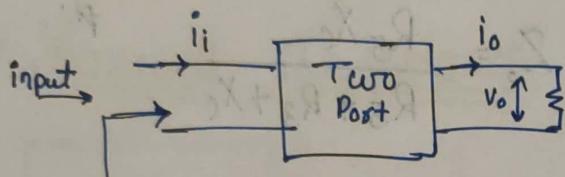

$$R_i = R_o \quad \text{for matched}$$
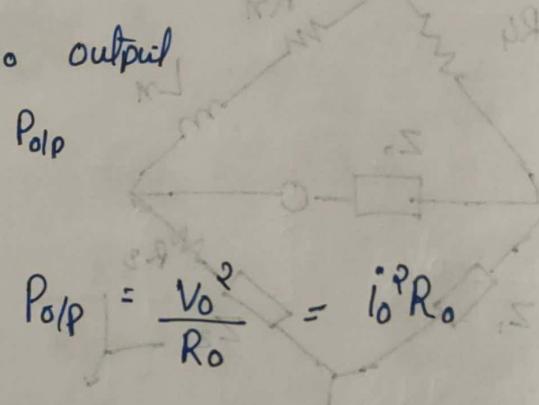
$$P_{\text{in}} = \frac{V_{\text{in}}^2}{R_o} = i_i^2 R_o$$



$$P_{\text{out}} = \frac{V_o^2}{R_o} = i_o^2 R_o$$

$$\frac{P_i}{P_o} = \left(\frac{V_{\text{in}}}{V_o} \right)^2 = \left(\frac{i_i}{i_o} \right)^2$$

$$\begin{aligned} \text{Attenuation} &= 10 \log_{10} \left(\frac{V_{\text{in}}^2}{V_{\text{out}}^2} \right) = 10 \log \left(\frac{i_i^2}{i_o^2} \right) \\ &= 20 \log \left(\frac{V_{\text{in}}}{V_{\text{out}}} \right) = 20 \log \left(\frac{i_i}{i_o} \right) \end{aligned}$$

$$K = \frac{V_{\text{in}}}{V_{\text{out}}} = \frac{i_i}{i_o}$$

Ex) 10dB attenuator, find K ?

17/0ct/24

$$10 = 20 \log_{10}(K)$$


$$\boxed{K = e^{\frac{1}{2}}}$$

$$\boxed{K = 1.64}$$

$$K = 10^{1/2}$$

$$\boxed{K = 3.162}$$

i) T-Section Two-port N/K :-

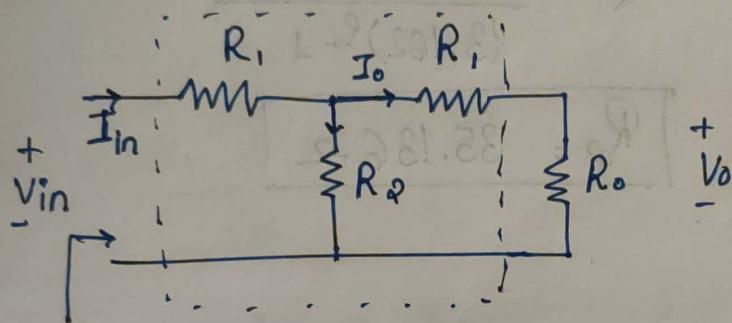

$$R_{in} = R_0$$

find R_1 & R_2 in terms of K & R_0 .

$$\textcircled{i} \quad (I_{in} - I_o) R_2 = I_o (R_1 + R_0)$$

$$I_{in} R_2 = I_o (R_1 + R_2 + R_0)$$

$$\frac{I_{in}}{I_o} = K = \frac{R_1 + R_2 + R_0}{R_2} \quad \text{--- } \textcircled{1}$$

$$\textcircled{ii} \quad R_{in} = R_1 + R_2 \parallel (R_1 + R_0)$$

$$\hookrightarrow R_0 = R_1 + \frac{R_2(R_1 + R_0)}{R_1 + R_2 + R_0} \Rightarrow R_0 = R_1 + \frac{R_1 + R_0}{K}$$

$$(1 - \frac{1}{K}) R_0 = (1 + \frac{1}{K}) R_1$$

$$\boxed{R_2 = \frac{2K R_0}{K^2 - 1}}$$

$$\Leftrightarrow \boxed{R_1 = \left(\frac{K-1}{K+1}\right) R_0}$$

Q.1 For a 10dB loss attenuator T-network find R_1, R_2

\Rightarrow

$$10 = 20 \log_{10}(K)$$

$$K = 10^{1/2} \Rightarrow K = 3.162$$

$$R_o = 50\Omega$$

$$R_1 = \left(\frac{K-1}{K+1} \right) R_o$$

$$R_2 = \frac{2KR_o}{K^2-1}$$


$$R_1 = \frac{2.162}{4.162} \times 50$$

$$R_2 = \frac{2 \times 3.162 \times 50}{(3.162)^2 - 1}$$


$$\boxed{R_1 = 25.974 \Omega}$$

$$\boxed{R_2 = 35.136 \Omega}$$

II-Section Attenuator \Rightarrow

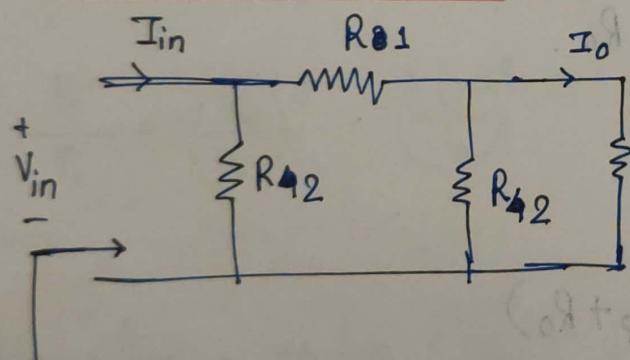


$$R_{in} = R_o$$

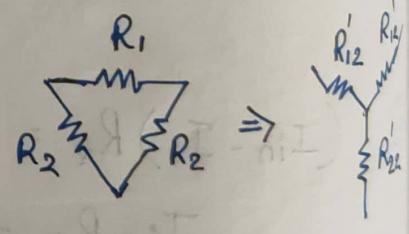

$$R'_{12} = \frac{R_1 R_2}{R_1 + 2R_2}$$

$$, R'_{22} = \frac{R_2^2}{R_1 + 2R_2}$$

0

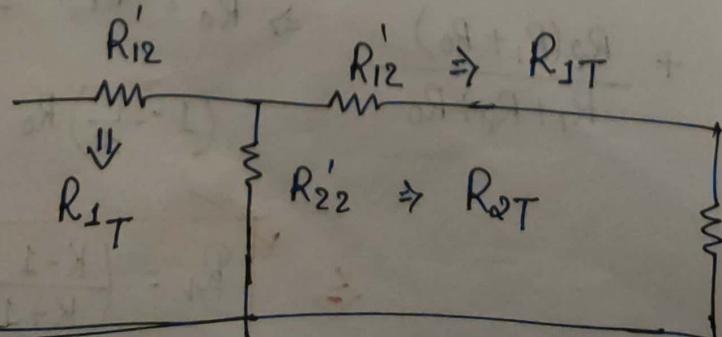

$$R_{oT}$$

$$R'_{12} = \left(\frac{K-1}{K+1} \right) R_0$$

$$\frac{R_1 R_2}{R_1 + 2R_2} = \left(\frac{K-1}{K+1} \right) R_0$$

$$\frac{R_1}{R_2} = \left(\frac{K-1}{K+1} \right) \times \frac{(K^2-1)}{2K} \Rightarrow \frac{R_1}{R_2} = \frac{(K-1)^2}{2K}$$

$$R_1 = \frac{R_0(K^2-1)}{2K}$$

$$R_2 = \frac{R_0(K+1)}{K-1}$$

$$\frac{(R_1 + 2R_2)R_0}{R_1 + 2R_2} = \left(\frac{K-1}{K+1} \right) R_0$$

$$R_1 + 2R_2 = R_1 = \left(\frac{(K-1)^2 + 2}{2K} \right) \left(\frac{K-1}{K+1} \right) R_0$$

$$\left[\frac{R_0}{R_0 + R_0} = \frac{R_0}{2R_0} = \frac{1}{2} \right]$$

$$\frac{R_0}{K-1} = R_0 \cdot \frac{1}{K-1}$$

$$K-1 = K$$

$$\left[\frac{R_0}{K-1} = R_0 \right]$$

$$R'_{22} = \frac{2KR_0}{K^2-1}$$

$$\frac{R_2^2}{R_1 + 2R_2} = \frac{2KR_0}{K^2-1}$$

$$\frac{R_1}{R_2} = \frac{(K-1)^2}{2K}$$

$$(R_1 + 2R_2)R_0 = R_0$$

$$\frac{(R_1 + 2R_2)R_0}{R_1 + 2R_2} = R_1 = \left(\frac{(K-1)^2 + 2}{2K} \right) \left(\frac{K-1}{K+1} \right) R_0$$

$$R_1 + 2R_2 = R_1 = \left(\frac{(K-1)^2 + 2}{2K} \right) \left(\frac{K-1}{K+1} \right) R_0$$

$$R_2 = \frac{R_0}{2}$$


$$\left[\frac{R_0}{2R_0} = \frac{1}{2} \right]$$

$$\frac{R_0}{K-1} = \left(\frac{1}{2} + \frac{1}{2} \right) R_0$$

$$K = \frac{R_0}{R_0} + 1$$

$$\left[\frac{R_0}{K-1} = \frac{1}{2} R_0 \right]$$

L - Section Attenuator

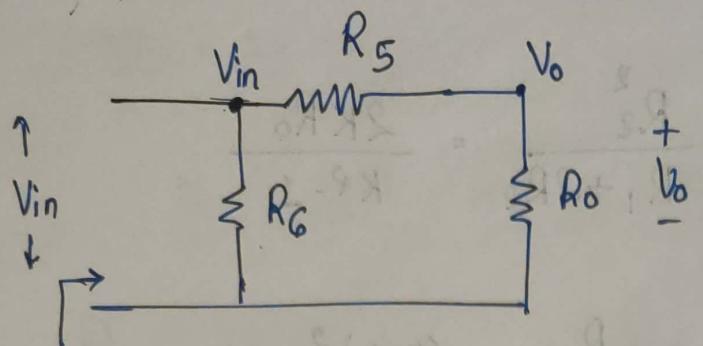

$$R_{in} = R_0$$

$$R_{in} = R_6 \parallel (R_5 + R_0)$$

$$R_0 = \frac{R_6(R_5 + R_0)}{R_5 + R_6 + R_0}$$

$$(R_5 + R_6)R_0 + R_0^2 = R_6R_5 + R_6R_0$$

$$R_0R_5 + R_0R_6 + R_0^2 = R_6R_5 + R_6R_0$$

$$R_5 = \frac{R_0R_6 + R_0^2 - R_6R_0}{R_6 - R_0}$$

$$R_5 = \frac{R_0^2}{R_6 - R_0}$$

Nodal Analysis

$$\frac{V_o - V_{in}}{R_5} + \frac{V_o}{R_0} = 0$$

$$V_o \left(\frac{1}{R_5} + \frac{1}{R_0} \right) = -\frac{V_{in}}{R_5}$$

$$1 + \frac{R_5}{R_0} = K$$


$$R_5 = (K-1)R_0$$

$$(R_6 - R_0)(K-1)R_0 = R_0^2$$

$$R_6 - R_0 = \frac{R_0}{K-1}$$


$$R_6 = R_0 + \frac{R_0}{K-1}$$

$$R_6 = \frac{K R_0}{K-1}$$

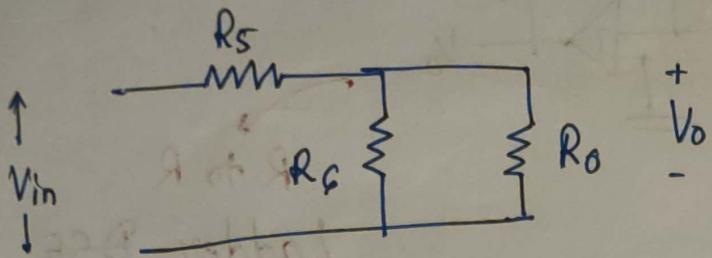

$$\frac{a(1-\delta^m)}{1-\delta^m}$$


Analog to digital Converter

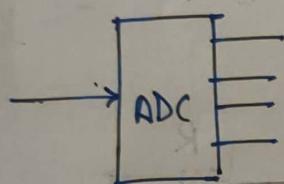

DAC $V_o = V_{ref} (b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + \dots + b_n 2^{-n})$

4bit $\rightarrow V_o = V_{ref} \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} \right) = 0.94 V_{ref}$


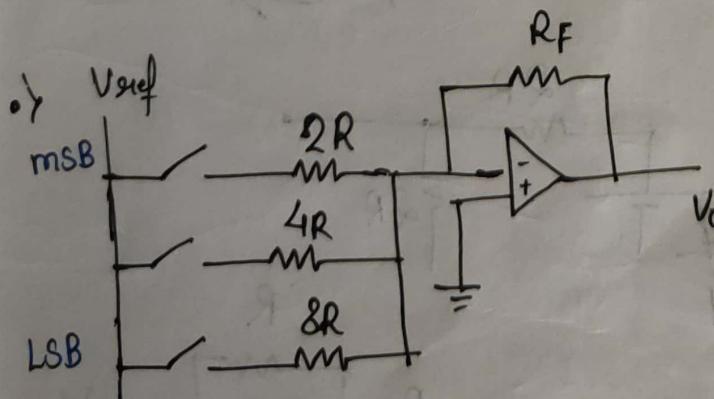
8bit $\rightarrow V_o = \frac{\frac{1}{2}(1 - \frac{1}{2^8})}{\frac{1}{2}} = 1 - \frac{1}{2^8} = 0.996 V_{ref}$



Digital to Analog


Binary weighted
DAC
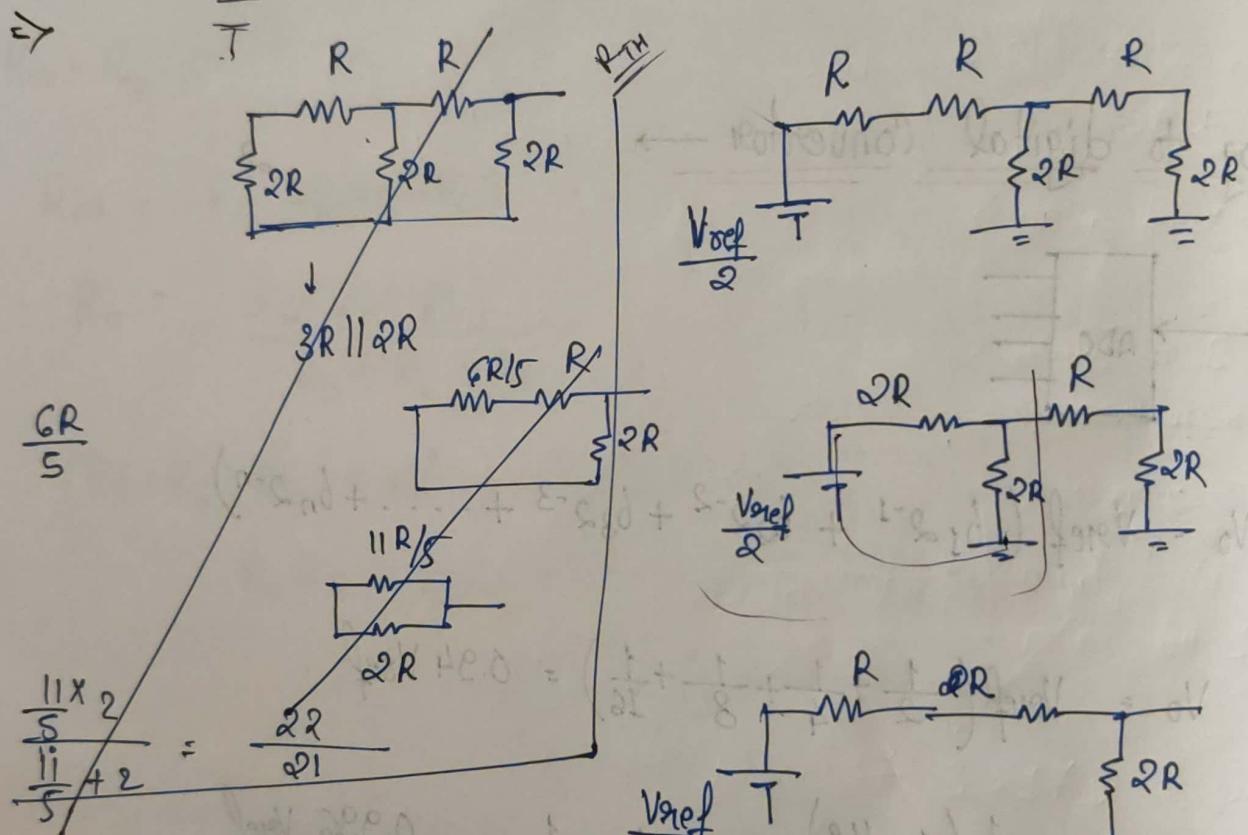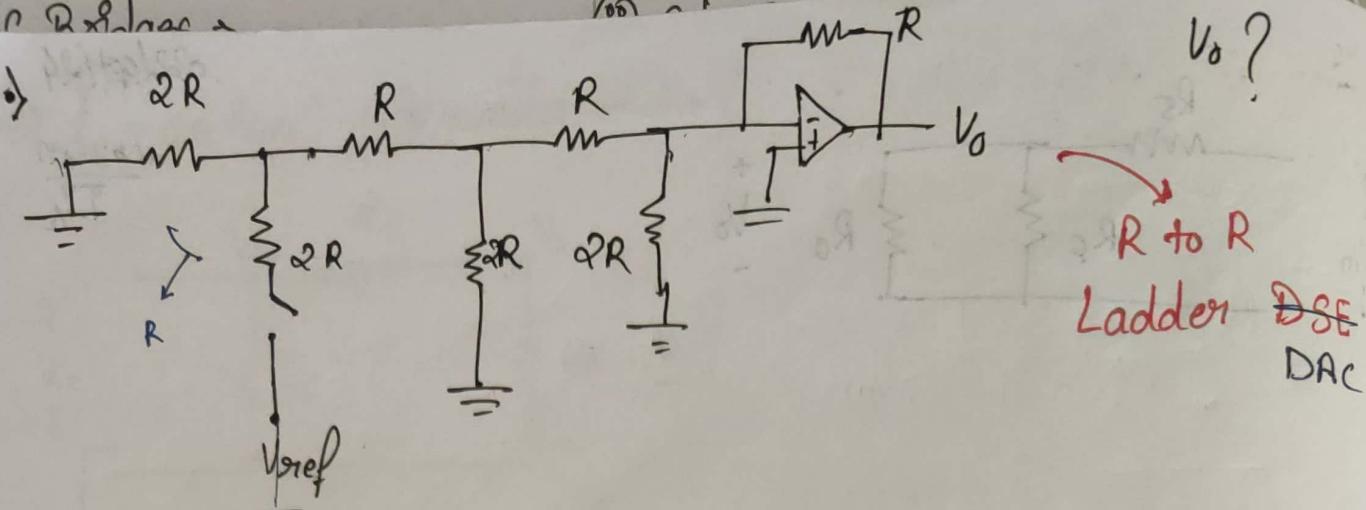
$$V_o = - \left(\frac{R_F}{2R} + \frac{R_F}{4R} + \frac{R_F}{8R} \right) V_{ref}$$



$$\frac{V_{ref}}{2} \xrightarrow[2R]{} \frac{V_{ref}}{8} : V_{TH}$$

R_{TH}

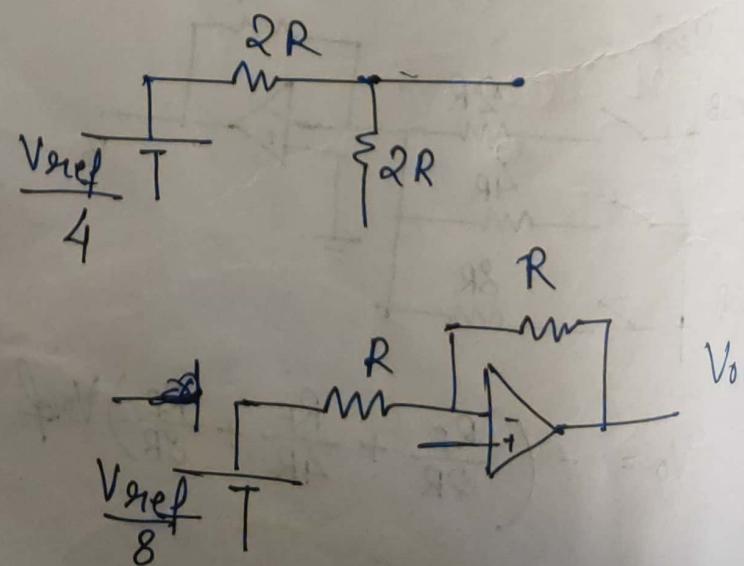

Ques) Find O/p Voltage for 1010, 0111

22/0ct/24

V_{ref} = 5V

~~BS~~ ~~DSE~~ DAC

8bit

$$V_o = -V_{ref} \left(\frac{R_1}{2} + 0 + \frac{1}{8} + 0 \right)$$

$$= -5 \times \frac{3}{8}$$

$$V_o = +V_{ref} \left(\frac{1}{2} + 0 + \frac{1}{8} + 0 + \frac{1}{2^6} + \frac{1}{2^7} + \frac{1}{2^8} \right)$$

$$V_o = +5 \times$$

$$V_o = 3.26 V$$


$$\text{Alternate} \rightarrow V_o = \frac{D}{2^n} V_{ref}$$

~~D = Decimal of (10100111)₂~~

$$D = 167$$


$$n=8 \quad 8\text{bit}$$
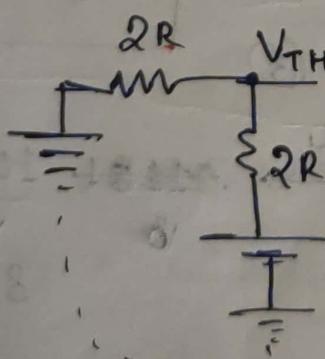
$$V_o = \frac{167 \times 5}{2^8} = 3.26 V \quad \checkmark$$



$$\underline{\underline{R_{TH}}}$$

$$V_{TH} = \frac{V_{ref}}{2}$$

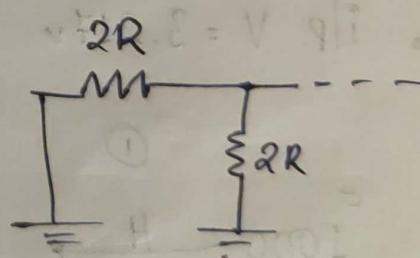

$$\frac{V_{ref}}{2}$$


$$\frac{V_o}{V_{ref}} = -\frac{R_f}{R}$$

LCS → Logic Control Sequential
 SAR → Successive Approx.
 Resistor

★ ADC

i) SAR →

(S)

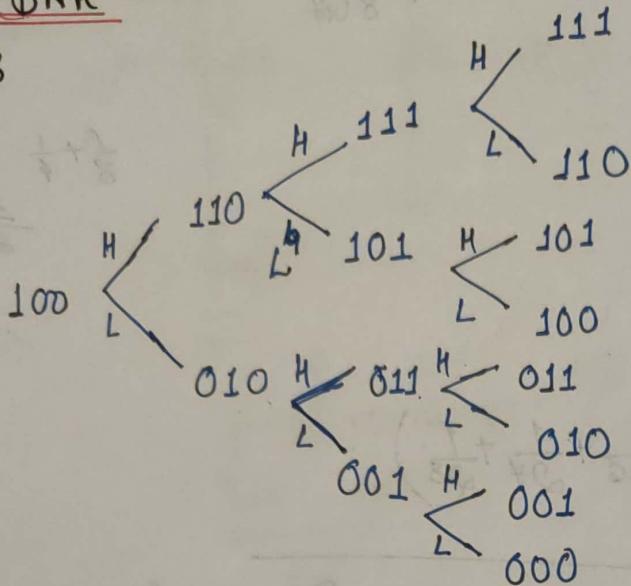

Given ilp $\frac{1}{16}$
 if High ↓

make add 1 to next msb

if ilp is Low ↓

make msb 0 & next msb 1. low


make 1st (1) (High)
 from right 0 & next bit 1.

Ques. 1)

SAR of 4 bit $V_{ref} = 5V$, ilp is 3.17 mV . Show me the o/p for each step

$$\Rightarrow \text{ilp V} = 3.217 \text{ V}$$

4-Cycle (6C4 4bit)

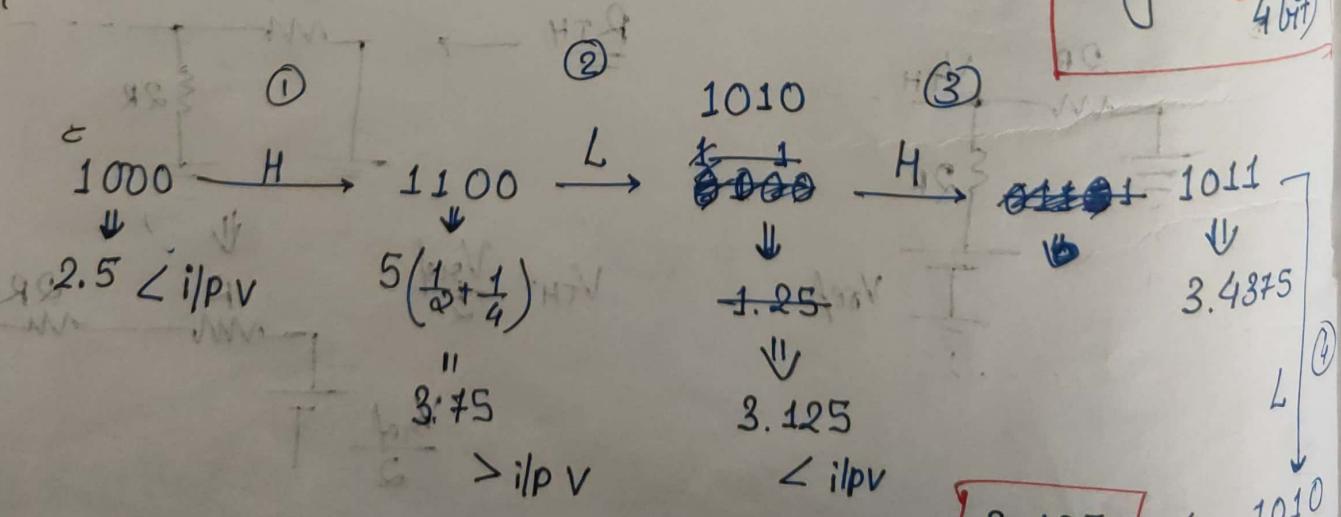

3.125

Ans

Single Slope ADC

+ve is higher \Rightarrow O/P of Comparator 1
 -ve \Rightarrow O/P = 0.

Que.) A 5 bit DAC with ref. of 10V, O/I/P (OB5)_H

to Q) O/P is 6.5V, what I/P should be applied.

\Rightarrow

$$V_{ref} = 10V$$

$$(OB5)_H \rightarrow 0010110101$$

$$\rightarrow (265)_D$$

$$(181)_D$$

$$D = 265\ 181$$

$$V_o = \frac{2 \cdot D}{2^n} V_{ref} = \frac{\frac{181}{265}}{2^{10}} \times 10V$$

$$V_o = 2.58V$$

$$\textcircled{1} \underline{\text{Ans}} \quad V_o = 1.767V$$

$$\textcircled{ii} \Rightarrow V_o = \frac{D V_{ref}}{2^n}$$

$$D = 6.5 \times 2^{10}$$

$$D = 665.2$$

$$665.6$$

$$\textcircled{4} \quad O/I/P = H = 299 + \frac{12}{16}$$

$$= (299)_H \quad \underline{\text{Ans}}$$


$$V_o = -\frac{1}{Rc} \int_0^T -V_{ref} dt$$

$$V_o = -\frac{V_{ref}}{Rc} T$$

$$V_o \propto T$$

28/0ct/24

* Dual slope ADC \Rightarrow

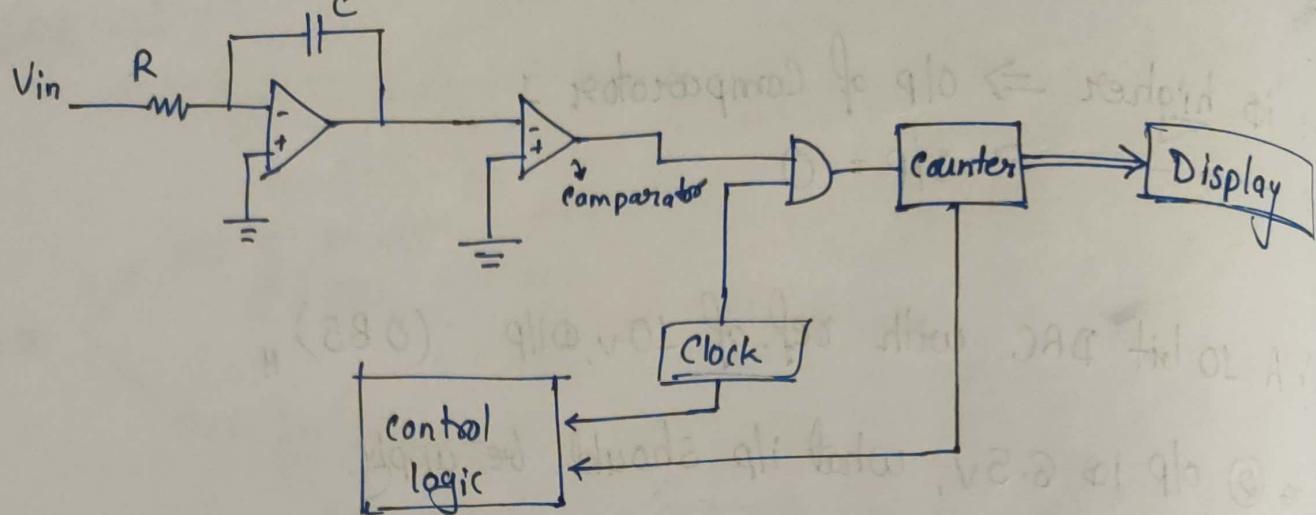

$$V_o = -\frac{1}{RC} \int_0^{T_2} -V_{ref} dt + V_{initial}$$

$$V_o = \frac{T_2}{RC} V_{ref} - \frac{T_1}{RC} V_{in}$$

$$V_o = 0$$


$$\hookrightarrow T_2 = T_1 \cdot \frac{V_{in}}{V_{ref}}$$

$$V_{initial} = \int_{-T_1}^0 \frac{V_{in}}{RC} dt$$


$$= -\frac{T_1}{RC} V_{in}$$

\hookrightarrow It overcomes the disadvantage
of Single Slope ADC \rightarrow as RC term is
not there

Flash Type \Rightarrow

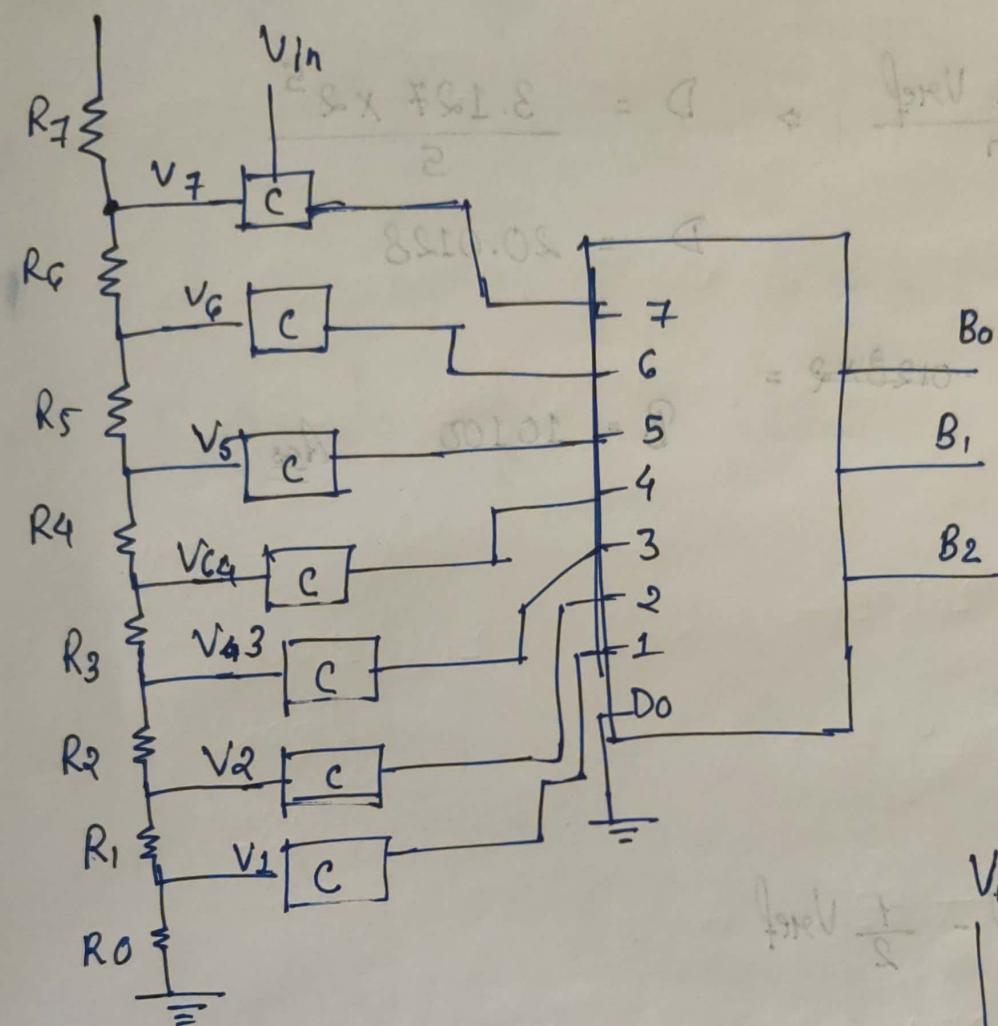

$$V_1 = \frac{R}{R+7R} \times V_{ref}$$

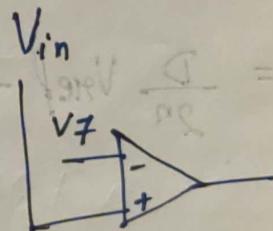

$$V_{ref} = 8V$$

$$\text{if } V_7 =$$

$$V_7 < V_{in} \xrightarrow{\text{O/P}} 1$$

$$V_7 \geq V_{in} \xrightarrow{\text{O/P}} 0$$

↪ Comparators

$$\begin{aligned} V_1 &< V_{in} \xrightarrow{\text{O/P}} 1 \\ V_1 &> V_{in} \xrightarrow{\text{O/P}} 0 \end{aligned}$$

| $N = \text{no. of bits.}$

↪ In flash type Comparator $2^N - 1$ comparators

2^N Registers

Ques) Ref \rightarrow 5 V

5 bit ADC

3.127 V

$$V_o = \frac{D \times V_{ref}}{2^n}$$

$$D = \frac{3.127 \times 2^5}{5}$$

$$D = 20.0128$$

2	20
2	10 0
2	5 0
2	2 1
1	0 1 0


$$\begin{array}{r} 0.128 \times 2 = \\ \hline 0.8 \\ \hline 1.8 \\ \hline 0.8 \\ \hline 1.0100 \end{array}$$

$$B = 10100$$

Ans

• Bipolar
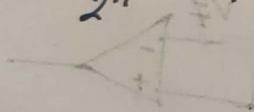
$$V_o = \frac{D}{2^n} V_{ref} - \frac{1}{2} V_{ref}$$



$$D = 2^{n-1} \text{ (most significant bit)}$$

$$V_o = \frac{2^n - 1}{2^n} V_{ref} - \frac{V_{ref}}{2}$$

$$V_o = V_{ref} - \frac{V_{ref}}{2^n} - \frac{V_{ref}}{2}$$

$$V_o = V_{ref} \left(\frac{1}{2} - \frac{1}{2^n} \right) V_{ref}$$

Ques) 10 bit ~~DAC~~ DAC

$$V_{ref} = 5 V$$

④ Digital i/p

① 0_H

② (04F)_H

$$V_o = \frac{0 \cdot V_{ref}}{2^{10}} - \frac{V_{ref}}{2}$$

$$V_o = -\frac{5}{2}$$

$$V_o = -2.5$$