

Introduction

Evaluation:

25 → midsem

55 → Endsem

20 → Teacher's assessment

10 Assignment

10 vivo

Additivity } Linear Network


Homogeneity }

If any ckt satisfies superposition principle it is linear ~~circuit~~ circuit.

Non-linear: diodes & transistor

↳ exponential, logarithm, trigonometric terms

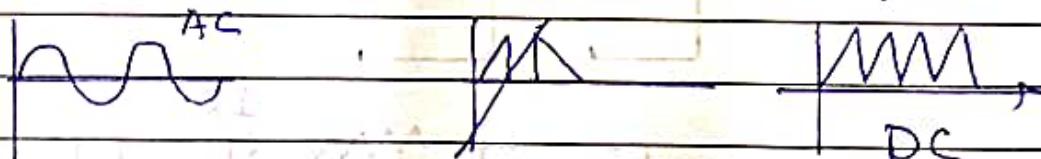Refer: Network Analysis → Von Volkenberg,
Network & System → Roy Chaudhury



DC → unidirectional

Elements -

- Active : supply power/energy
battery, generator, op-amp


→ Passive do not supply energy

e.g.: R, L, C

Sources



→ dependent

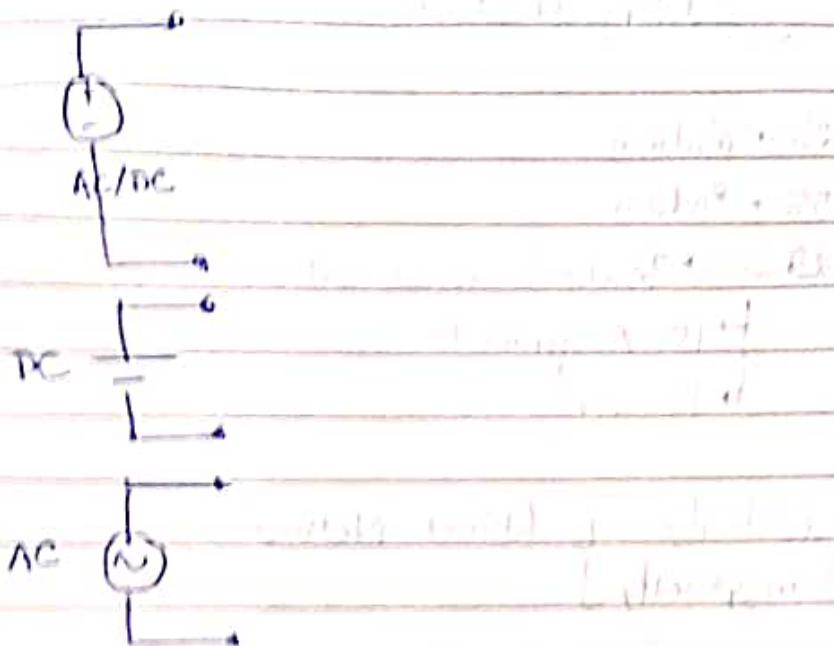→ not independent : An ideal independent source is an active element that provides a specified voltage/current that is completely independent other ckt. variables




Dependent Sources

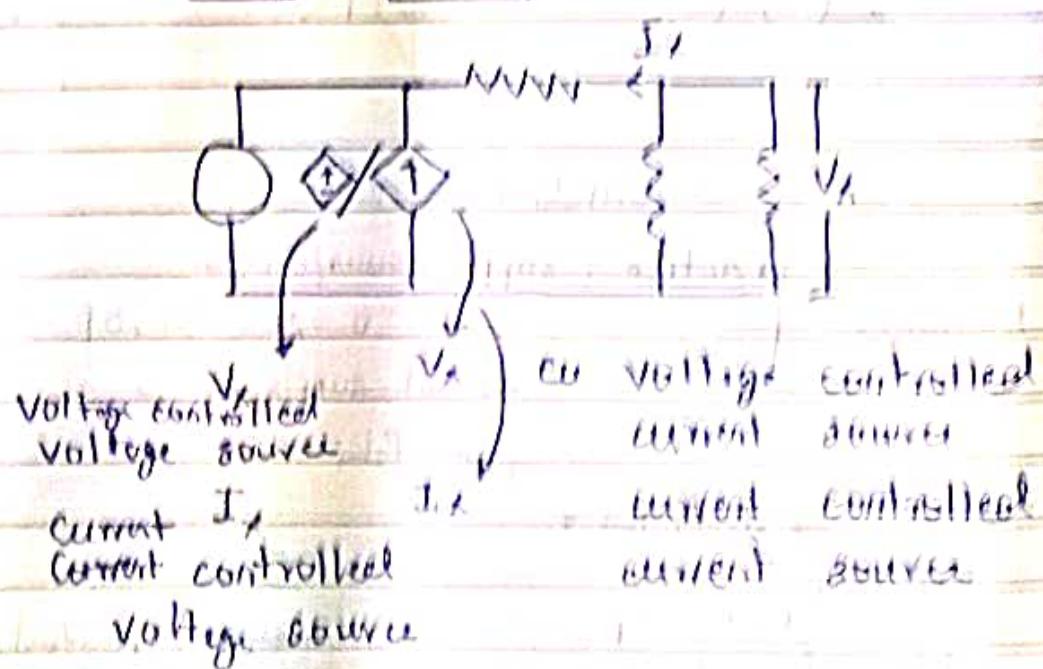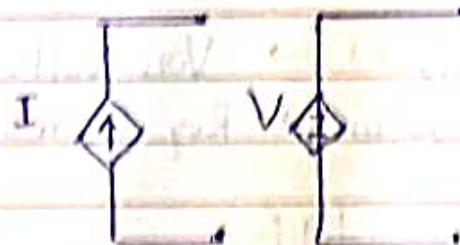An ideal dependent source is an active element in which the source quantity is controlled by another voltage or current.



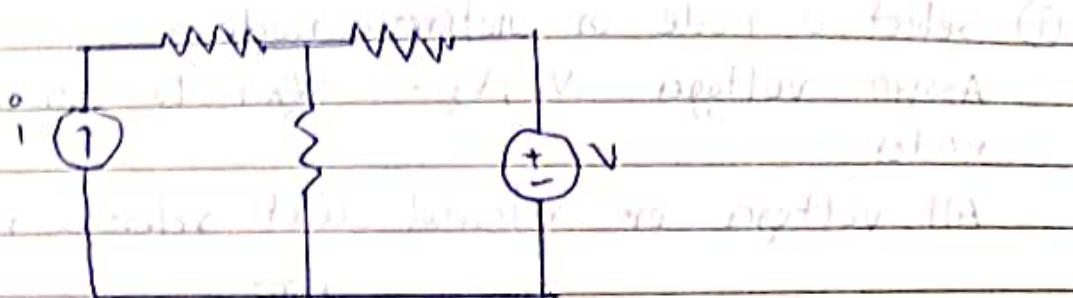Nodal Analysis - is a technique that uses systematic application of KCL.



Branch : Represents a single element in a circuit such as voltage source in an element.


Node : A point of connection b/w 2 or more branches

loop : A closed form of a circuit.

Note : A network with 'b' branches, 'n' no. of nodes and 'l' independent loops will satisfy fundamental theorem.

$$b = l + n - 1$$

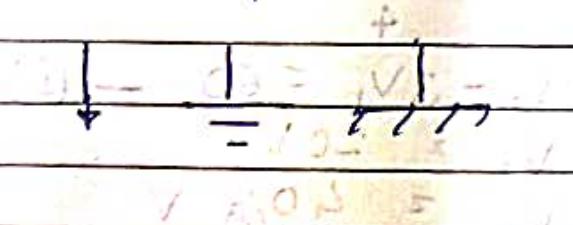Note 2 : Reference node is also called as Datum node or ground. It is assumed to have 0 potential.



Steps

① Select a node or reference node.


Assign voltages $V_1, V_2 \dots V_{n-1}$ to remaining ($n-1$) nodes.

All voltages are referred w.r.t reference node
non-

② Apply KCL to each ($n-1$) reference nodes.

Use Ohm's law to express branch current in terms of voltages.

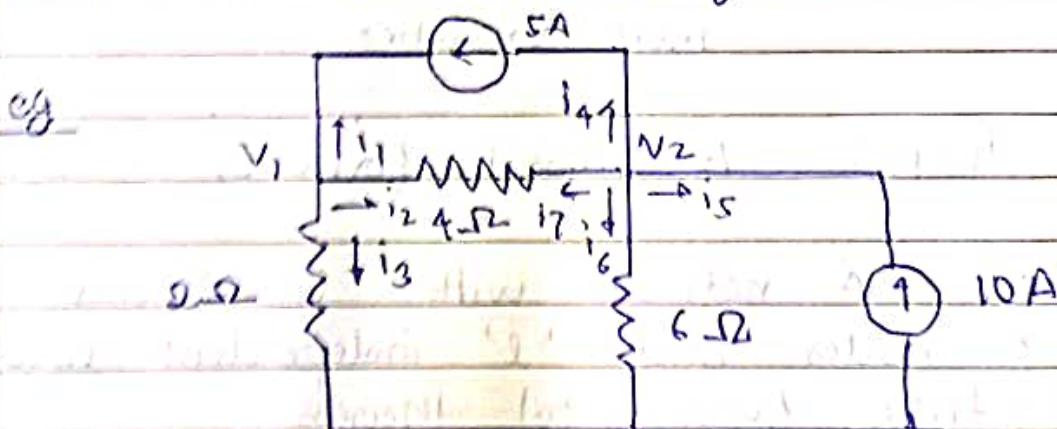③ Solve resulting simultaneous equation to obtain the unknown load voltage.



$$\frac{V_1}{2} + \frac{V_1}{4} - \frac{V_2}{4} - 5 = 0$$

$$3V_1 - V_2 = 20 \quad \text{--- (1)}$$

$$\frac{V_2}{6} + \frac{V_2 - V_1}{4} + 5 - 10 = 0$$

$$5V_2 - 3V_1 = 60 \quad \text{--- (2)}$$

$$V_1 = 20 \text{ V}$$

$$V_2 = 40/3 \text{ V}$$

Note : Cremer's rule


$$\begin{bmatrix} 8 & -1 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 60 \end{bmatrix}$$

$$\Delta = 12$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{[8 \ 20 \ -1]}{[60 \ 5]} / 12$$

$$\text{same for } V_2 = \frac{\Delta_2}{\Delta}$$

eg :

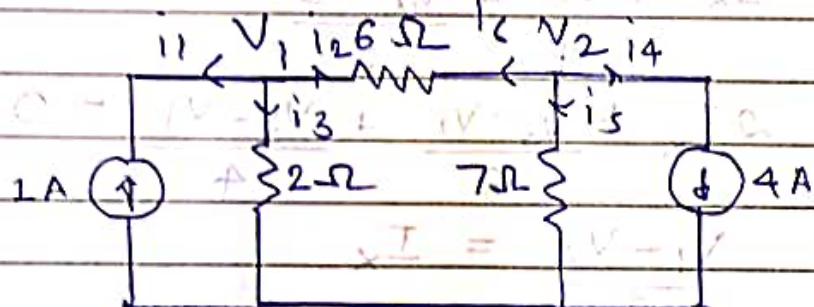

$$\frac{V_1}{2} + V_1 - V_2 - 1 = 0 \quad \text{--- (1)}$$

$$4V_1 - V_2 = 6 \quad \text{--- (1)}$$

$$0 = 2V_1 - 6V_2 + 168 + 4V_2 \quad \text{--- (2)}$$


$$\frac{V_2 - V_1}{6} + \frac{-V_2 + 4V_2}{7} = 0$$

$$0 = 13V_2 - 168 \quad \text{--- (2)}$$

$$V_1 = -2V$$

$$V_2 = -14V$$

(Q) Determine the voltages at the nodes.

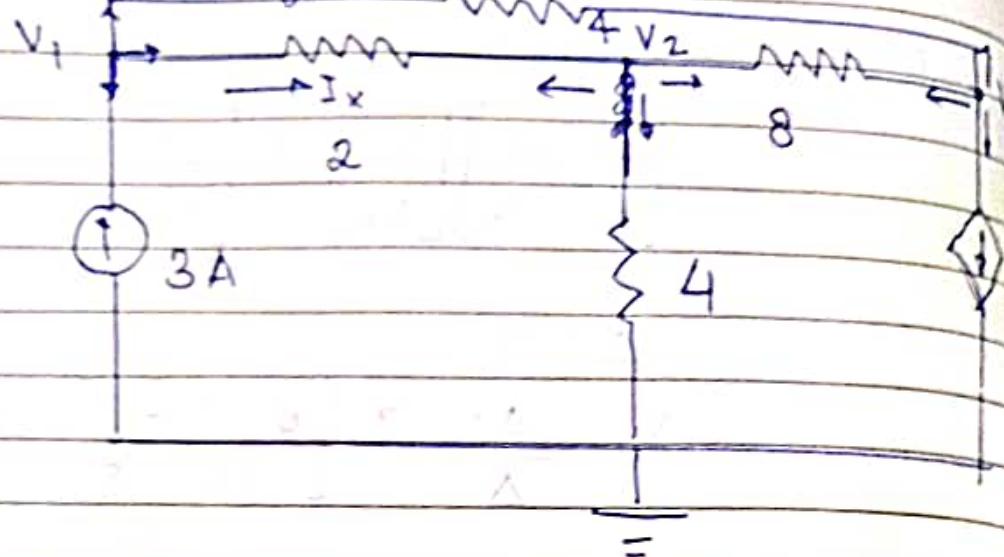

$$-3 + I_x + \frac{V_1 - V_3}{4} = 0$$

$$-I_x + \frac{V_2}{4} + \frac{V_2 - V_3}{8} = 0$$

$$2I_x + \frac{V_3 - V_2}{8} + \frac{V_3 - V_1}{4} = 0$$

$$\frac{V_1 - V_2}{2} = I_x$$

$$-12 + 4I_x + V_1 - V_3 = 0$$

$$V_1 - V_3 + 4I_x = -12 \quad \text{--- (1)}$$

$$-8I_x + 2V_2 + V_2 - V_3 = 0$$

$$3V_2 - V_3 - 8I_x = 0 \quad \text{--- (2)}$$

$$16I_x + V_3 - V_2 + 2V_3 - 2V_1 = 0$$


~~$$3V_3 - V_2 - 2V_1 - 8V_2 = -2V_1 + 16I_x = 0 \quad \text{--- (3)}$$~~

$$V_1 - V_2 - 2I_x = 0 \quad \text{--- (4)}$$

$$\boxed{\begin{aligned} V_1 &= -96/11 \approx -8.727 \\ V_2 &= -36/11 \approx -3.272 \\ V_3 &= -12/11 \approx -1.090 \\ I_x &= -1.09 \text{ A} \end{aligned}}$$

$$\boxed{\begin{aligned} V_1 &= 24/5 = 4.8 \text{ V} \\ V_2 &= 12/5 = 2.4 \text{ V} \\ V_3 &= -12/5 = -2.4 \text{ V} \\ I_x &= 6/5 = 1.2 \text{ A} \end{aligned}}$$

(Q) Determine voltages at nodes 1, 2, 3

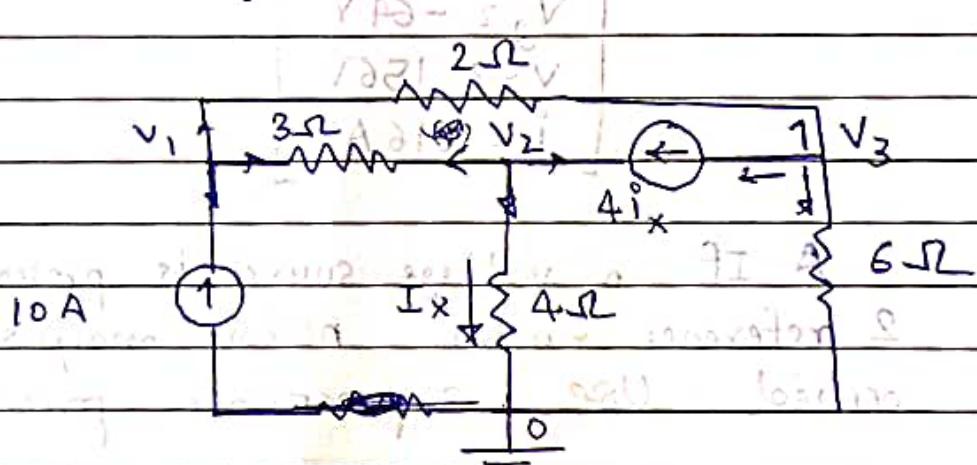

$$-10 + \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{3} = 0$$

$$-30 + 2V_1 - 2V_2 + 3V_1 - 3V_3 = 0$$

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{---(1)}$$

$$\frac{V_2 - V_1}{3} + I_x - \frac{4I_x}{4} = 0$$

$$V_2 - V_1 - 9I_x = 0 \quad \text{---(2)}$$

$$\frac{V_2 - 0}{4} = I_x$$

$$V_2 - 4I_x = 0 \quad \text{--- (3)}$$

$$\frac{V_3 - V_1}{2} + 4I_x + \frac{V_3}{6} = 0$$

$$V_3 - V_1 + 24I_x + V_3 = 0$$


$$4V_3 - 3V_1 + 24I_x = 0 \quad \text{--- (4)}$$

$$\begin{bmatrix} V_1 = 80V \\ V_2 = -64V \\ V_3 = 156V \\ i = 16A \end{bmatrix}$$


2. If a voltage source is present b/w 2 reference nodes nodal analysis is not applied. Use supernode principle.

3. If a voltage source is present b/w 2 reference nodes it forms a supernode. In such case apply both KCL and KVL to determine node voltages.

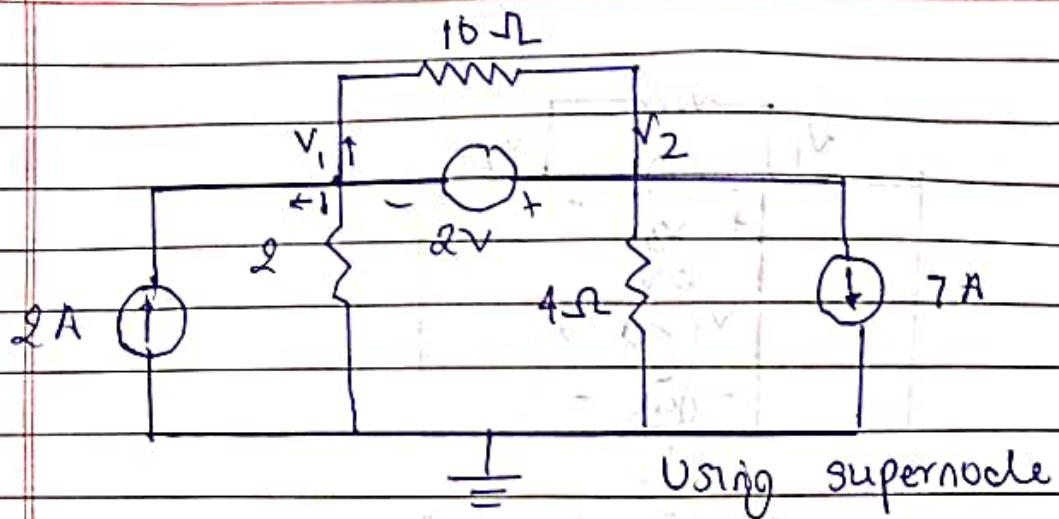4. A supernode is formed by enclosing dependent or independent voltage source connected between two non-reference nodes and any element connected in parallel with it.



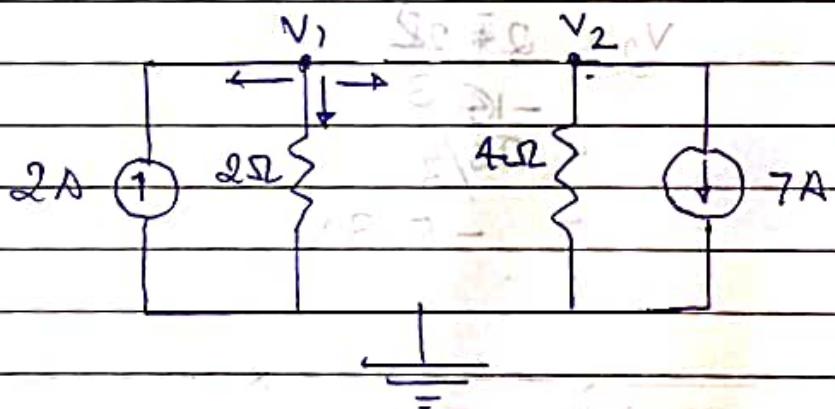- Remove voltage source & apply KCL
- V_1 & V_2 become supernode
- Redraw ckt by eliminating voltage source & any branch parallel with it.




$$-2 + \frac{V_1}{2} + \frac{V_2}{4} + 7 = 0$$

$$\boxed{V_1 = 4V}$$

$$2V_1 + V_2 + 8 = 0$$

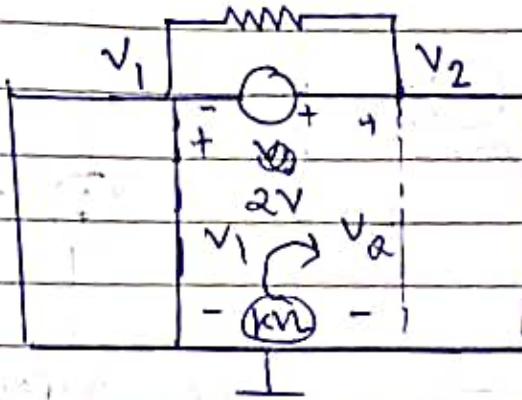- Restore voltage source & apply KVL & redraw the ckt.



$$2V_1 + -V_2 + 20 = 0$$

$$V_1 + 2V - V_2 = 0 \quad \text{--- (1)}$$

$$V_2 - V_1 = 2 \quad \text{--- (2)}$$

$$3V_1 = -20$$

$$V_1 = -\frac{20}{3} = -6.7V$$

$$V_2 = 2 + 2V_1$$


$$= -\frac{20}{3}$$

$$= -6.7V$$

$$= -5.3V$$

Youtube

1)

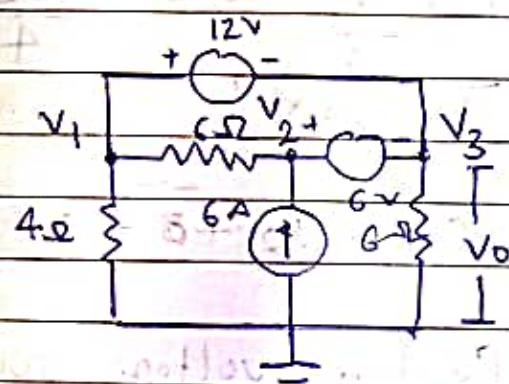



$$\frac{V_1 - V_2}{6} + \frac{V_1}{4} + \frac{V_3}{6} = 0$$

$$4V_1 - 4V_2 + 6V_1 + 4V_3 = 0$$


$$10V_1 - 4V_2 + 4V_3 = 0 \quad \text{--- (1)}$$

$$\frac{V_2 - V_1}{6} - \frac{V_1}{4} + \frac{V_3}{6} = 0$$

$$V_2 - V_1 - 3V_1 + V_3 = 0$$

$$V_2 + V_3 - V_1 = 3V_1 \quad \text{--- (2)}$$


Don't
so) ve

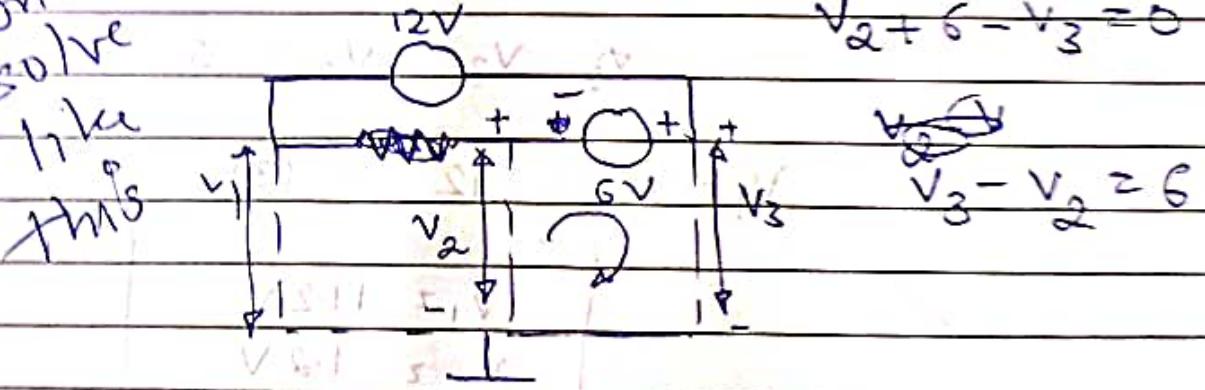

$$V_1 = -12/5 = -2.4V$$

$$V_2 = 6/5 = 1.2V$$

$$V_3 = 12/5 = 2.4V$$

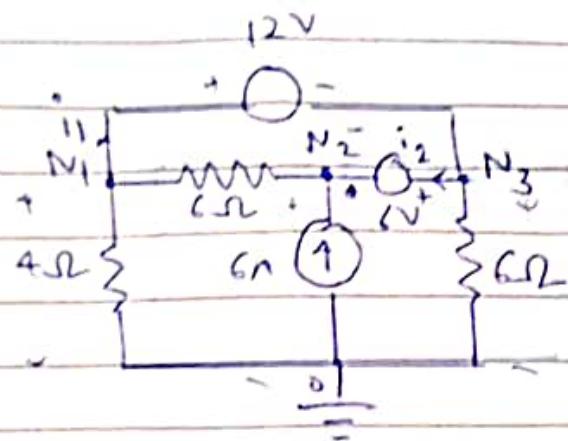

$$\underline{N_1} \quad \frac{V_1}{4} + \frac{V_1 - V_2}{6} + i_1 = 0$$

$$\underline{N_3} \quad -i_1 + \frac{V_2 - V_1}{6} + \frac{V_3}{6} = 0$$

$$\underline{N_2} \quad \frac{V_2 - V_1}{6} + -6 - \frac{i_2}{2} = 0$$

$$\frac{V_1}{4} + \frac{V_3}{6} = 6 \quad \text{(1)}$$

$$6V_1 + 4V_3 = 144 \quad \text{(1)}$$


$$V_2 + 6 - V_3 = 0$$

$$V_3 - V_2 = 6 \quad \text{(2)}$$

$$V_1 - V_3 = 12 \quad \text{(3)}$$

$$\boxed{\begin{aligned} V_1 &= 19.2V \\ V_2 &= 1.2V \\ V_3 &= 7.2V \end{aligned}}$$

2) Current in 2Ω = ?

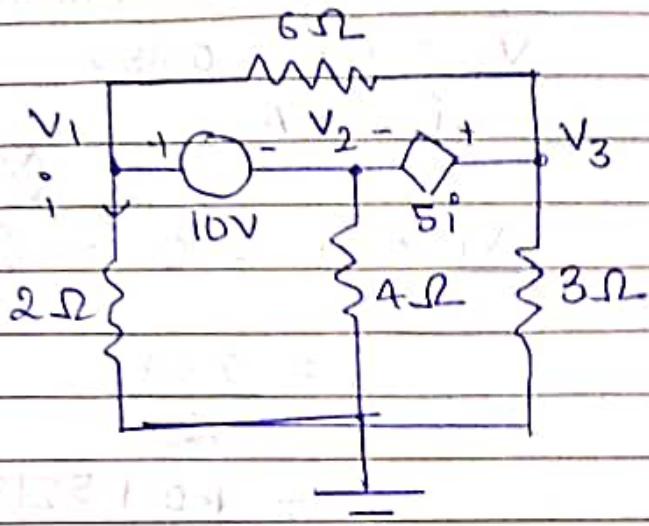

$$V_1 - V_2 = 10V \quad \text{--- (1)}$$

~~$V_2 - V_3 = 5i$~~

$$V_3 - V_2 + 5i = 0 \quad \text{--- (2)}$$

~~$\frac{V_1}{2} + \frac{i_2}{4} + \frac{V_2}{6} + \frac{V_3}{3} = 0 \quad \text{--- (3)}$~~

~~$i_2 + V_2 + V_3 = 0 \quad \text{--- (2)}$~~

~~$-\frac{i_2}{4} + \frac{V_2}{4} + -\frac{i_3}{3} = 0 \quad \text{--- (4)}$~~

~~$\frac{V_3 - V_1}{6} + \frac{i_3}{3} + \frac{V_3}{3} = 0 \quad \text{--- (5)}$~~

~~$\frac{6V_1}{4} + 3V_2 + 4V_3 = 0 \quad \text{--- (2)}$~~

~~$\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{3} = 0 \quad \text{--- (2)}$~~

~~$V_1 - V_3 + -5i + 10 = 0 \quad \text{--- (4)}$~~

$$6V_1 + 8V_2 + 4V_3 = 0 \quad \text{--- (3)}$$

$$V_1 = \frac{C}{L} = 0.85V$$

$$V_2 = -\frac{64}{7}V = -9.14V$$

$$V_3 = \frac{C}{L} = 0.85V$$

$$i = 2A$$

\otimes


$$\frac{V_1}{2} - i = 0 \quad \text{--- (4)}$$

$$i = \frac{3.643}{2}$$

$$= 1.5215A$$

\checkmark

(Q) Find 'v' and 'i' in the ckt.

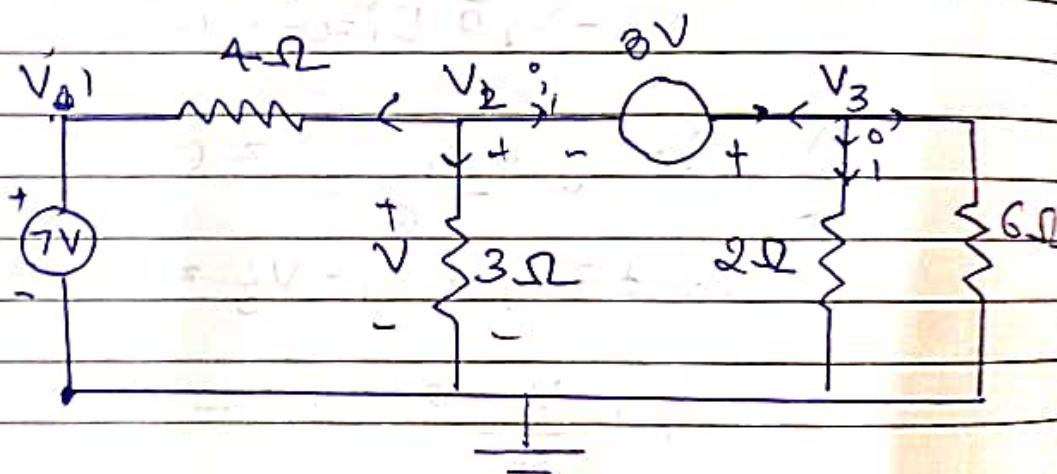

$$V_1 = 7V \quad \text{--- (1)}$$

~~$V_2 = V_3$~~ $V_3 - V_2 = 3 \quad \text{--- (2)}$

$$\frac{V_2 - V_1}{4} + \frac{V_2}{3} + i = 0$$

$$\frac{V_3}{2} - i + V_3 = 0$$

$$\frac{V_2 - V_1}{4} + \frac{V_2}{3} + \frac{V_3}{2} + \frac{V_3}{6} = 0$$

$$\frac{V_2}{4} - \frac{7}{4} + \frac{V_3}{2} + \frac{V_3}{6} = 0$$

$$3V_2 - 21 + 6V_3 + 2V_3 = 0 \quad 3V_3 + 8V_3 = 21$$

$$\begin{cases} 3V_2 + 8V_3 = 21 \\ 3V_2 - 3V_3 = 9 \end{cases}$$

$$\begin{cases} 11V_3 = 30 \\ V_3 = \frac{12}{11}V = 1.09V \end{cases}$$

$$\begin{cases} V_2 = \frac{4.5}{11}V = 0.409V \\ V_1 = 7V \end{cases}$$

$$\begin{cases} i = \frac{V_3}{R_2} = 0.545A \\ i = \frac{V_3}{1.4V} \end{cases}$$

~~$$3V_2 + 8V_3 = 21$$~~

~~$$3V_3 - 3V_2 = 9$$~~


$$11V_3 = 30$$

$$\begin{cases} V_3 = 2.72V \\ V_2 = -0.28V \end{cases}$$

$$\begin{cases} i = 1.4A \end{cases}$$

~~$$V_2 = 2V + 2V = 4V$$~~

~~$$V_3 = 4V + 1.4A \times 1V$$~~

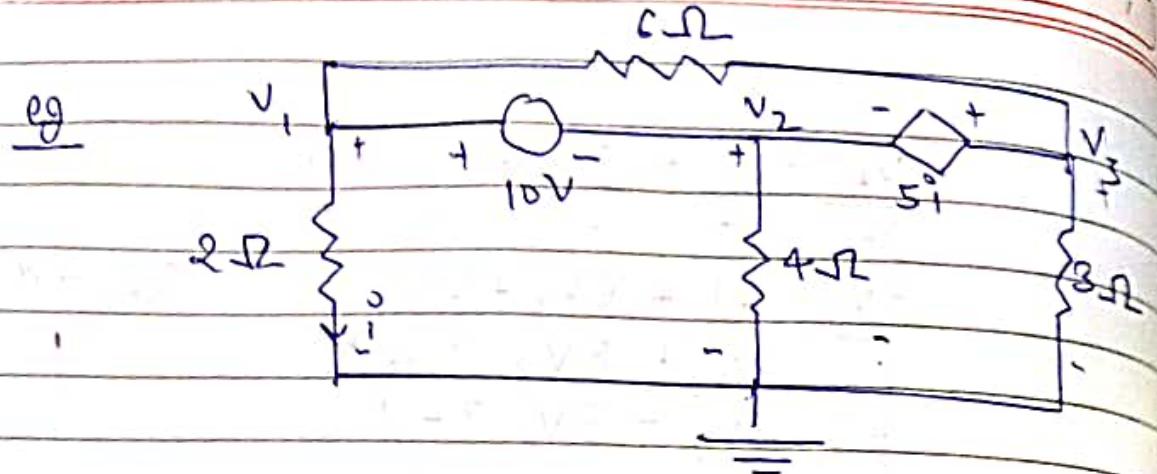

$$\textcircled{9} \quad V_1 - 10 - V_2 = 0$$

$$V_1 - V_2 = 10 \quad \text{--- } \textcircled{1}$$

$$V_2 + 5i - V_3 = 0$$

$$\textcircled{9} \quad V_3 - V_2 = 5i \quad \text{--- } \textcircled{2}$$

$$\frac{V_1}{2} = i$$

$$V_1 = 2i \quad \text{--- } \textcircled{3}$$

$$\textcircled{9} \quad V_3 - V_2 = \frac{5V_1}{2}$$

$$5V_1 + V_2 - V_3 = 0 \quad \text{--- } \textcircled{2}$$

$$2P = 5V_1 + V_2 - V_3$$

$$\frac{V_1}{2} + \frac{V_1 - V_3}{6} + i_1 = 0$$

$$-i_1 + \frac{V_2}{4} + i_2 = 0$$


$$-i_2 + \frac{V_3 - V_1}{6} + \frac{V_3}{3} = 0$$

$$\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{3} = 0$$

$$6V_1 + 3V_2 + 4V_3 = 0 \quad \text{--- } \textcircled{4}$$

$$\left. \begin{array}{l} V_1 = 3.043 \text{ V} \\ V_2 = -6.956 \text{ V} \\ V_3 = 0.6529 \text{ V} \end{array} \right\}$$

$$i = \frac{V_1}{2} = 1.5215 \text{ A}$$

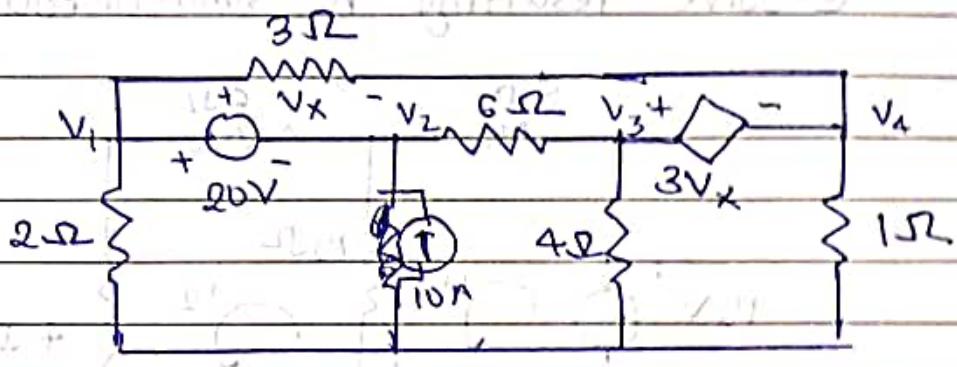HW :

$$\text{Ans: } \left. \begin{array}{l} V_1 = 26.67 \text{ V} \\ V_2 = 6.67 \text{ V} \end{array} \right\}$$

$$\left. \begin{array}{l} V_3 = 173.33 \text{ V} \\ V_4 = -46.66 \text{ V} \end{array} \right\}$$


Mesh - Analysis

A mesh is a loop that does not contain any other loop within it. Mesh analysis is applicable to planar ckt's only.

A planar ckt is one that can be drawn in a plane with not branches crossing one another.

Step 3:

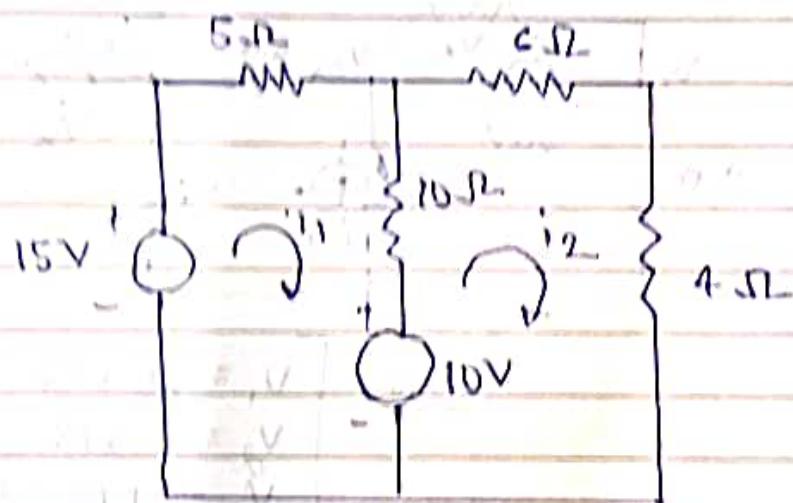- (1) Assign mesh currents i_1, i_2, i_3 to n meshes.
- (2) Apply KVL and use ohm's law to express the voltage in terms of mesh current.
- (3) Solve resulting n simultaneous equations.



$$15 - 5i_1 - 10(i_1 - i_2) - 10 = 0$$

$$15 - 5i_1 - 10i_1 + 10i_2 - 10 = 0$$

$$10i_2 - 15i_1 + 5 = 0 \quad | \cdot 10$$

$$3i_1 - 2i_2 = 1 \quad | \quad (1)$$

$$-6i_2 - 4i_2 + 10 = 10(i_2 - i_1) = 0$$


$$-10i_2 + 10 = 10i_2 + 10i_1 \quad | \cdot 10$$

$$10i_1 - 20i_2 + 10 = 0$$

$$2i_2 - i_1 = 1 \quad | \quad (2)$$

$$\begin{cases} i_1 = 2 \\ [i_1 = 1 \text{ A}] \end{cases}$$

$$[i_2 = 1 \text{ A}]$$

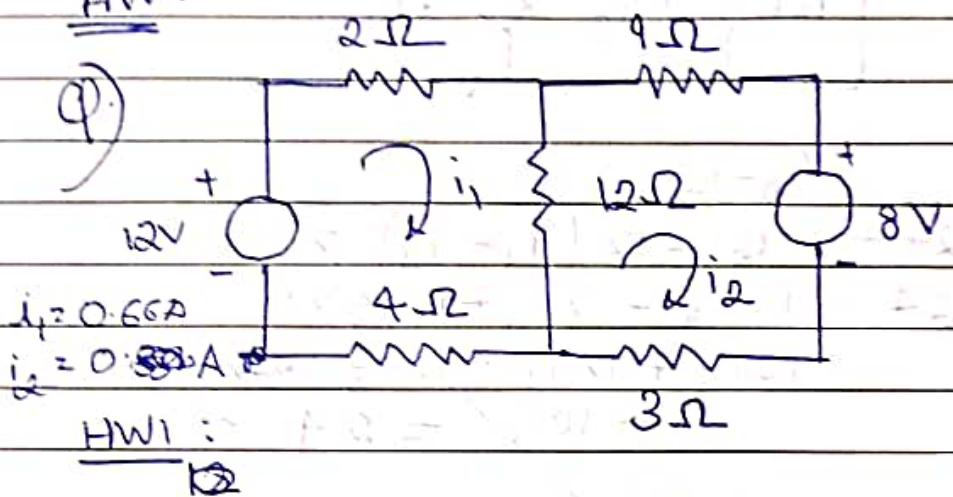HW:

$$V_1 + 20 - V_2 = 0$$

$$V_2 - V_1 = 20 \quad \text{--- (1)}$$

$$V_3 - V_2 = 3V_x \quad \text{--- (2)}$$

~~$$V_4 - V_1 = V_x \quad \text{--- (3)}$$~~

~~$$V_4 - V_1 = V_x \quad \text{--- (3)}$$~~

~~$$\frac{V_1}{2} + \frac{V_1 - V_4}{3} + i_1 = 0$$~~


~~$$\frac{V_2 - V_3}{6} - 10 - i_1 = 0$$~~

~~$$\frac{V_3 - V_2}{6} + \frac{V_3 + V_4}{4} + i_2 = 0$$~~

~~$$\frac{V_4 - V_1}{3} + \frac{V_4 + V_3}{4} - i_2 = 0$$~~

$$\frac{V_1}{2} - 10 + \frac{V_3 + V_4}{4} = 0 \quad \text{--- (4)}$$

Q) Find current i_0 in the ckt.

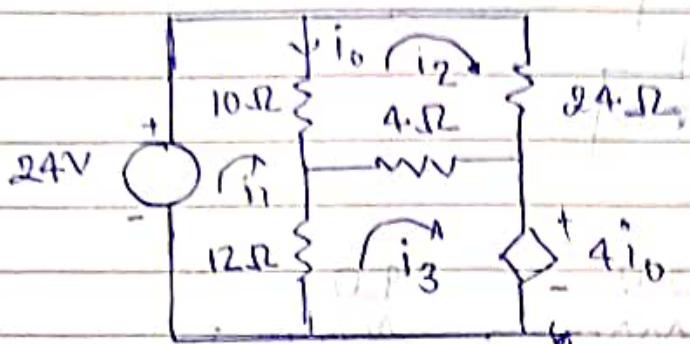

$$24 - 10i_0 - 12(i_1 - i_3) = 0$$

$$24 - 10i_0 - 12i_1 + 12i_3 = 0$$

$$10i_0 + 12i_1 - 12i_3 = 24 \quad \text{---} ①$$

$$10i_0 - 24i_2 - 4(i_2 - i_3) - 10(i_2 - i_0) = 0$$

$$-24i_2 - 4i_2 + 4i_3 - 10i_2 + 10i_0 = 0$$

$$10i_0 - 38i_2 + 4i_3 = 0 \quad \text{---} ②$$

$$12(i_3 - i_1) - 4(i_3 - i_2) - 4i_0 = 0$$

$$12i_3 - 12i_1 - 4i_3 + 4i_2 - 4i_0 = 0$$

$$-12i_1 + 8i_3 - 8i_2 - 4i_0 = 0$$

$$2i_3 - 2i_2 - i_0 = 0 \quad \text{---} ③$$

$$i_1 - i_0 - i_2 = 0 \quad \text{---} ④$$

$$i_1 = 2.603 \text{ A}$$

$$i_2 = 0.679 \text{ A}$$

$$i_3 = 1.641 \text{ A}$$

$$i_0 = 1.92 \text{ A}$$

$$24 - 10(i_0 - i_2)$$

$$24 - 10i_0 - 12(i_1 - i_3) = 0$$

$$24 - 10i_0 - 12i_1 + 12i_3 = 0$$


$$12i_1 - 12i_3 + 10i_0 = 24 \quad \text{---(1)}$$

7

$$\left\{ \begin{array}{l} i_1 = 2.029 \text{ A} \\ i_2 = 0.529 \text{ A} \\ i_3 = 1.279 \text{ A} \\ \text{or } i_0 = 1.5 \text{ A} \end{array} \right. \quad \left\{ \begin{array}{l} 2.25 \\ 0.75 \\ 1.5 \\ 1.5 \end{array} \right.$$

(Q)

Mesh Analysis with current Sources

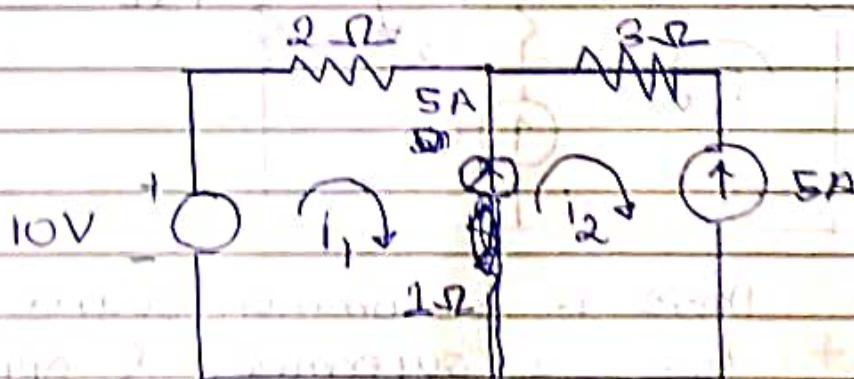

Super-mesh Analysis


$$i_1 = 10/(2+1) = 10/3 = 3.33$$

$$i_2 = 0.66 = 5/(3+1) = 5/4 = 1.25$$

$$i_1 - i_2 = 3.33 - 1.25 = 2.08$$

when current source

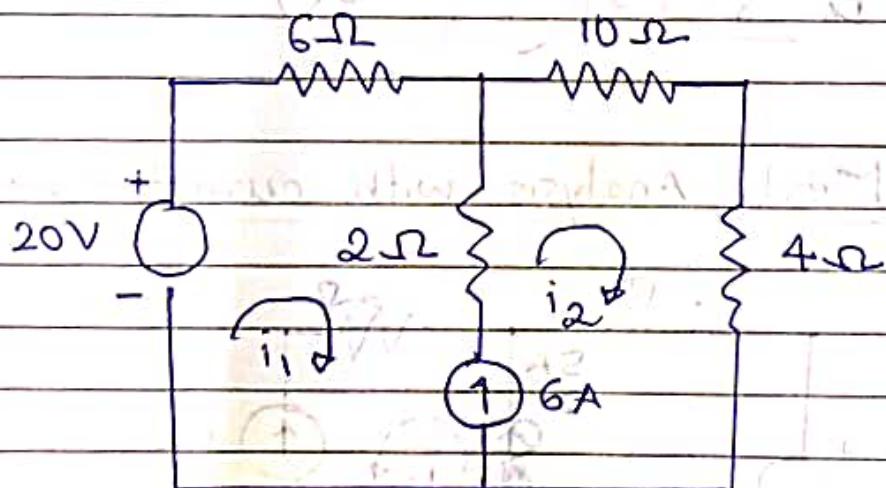- * If exists b/w 2 meshes, then we create a supermesh by excluding the current source and any elements connected in series with it.
- * Apply KVL for the supermesh - without changing the branch currents.
- * Restore the current source and apply KCL at the corresponding node.



Since there is a common source is present form a supermesh & apply KVL without changing current directions

$$20 - 6i_1 - 10i_2 - 4i_2 = 0$$


$$6i_1 + 14i_2 = 20 \quad \text{--- (1)}$$

~~$$i_1 + 6 = i_2$$~~

~~$$i_2 - i_1 = 6 \quad \text{--- (2)}$$~~

$$\begin{cases} i_1 = 3.2 \text{ A} \\ i_2 = 2.8 \text{ A} \end{cases}$$

Q) find the current

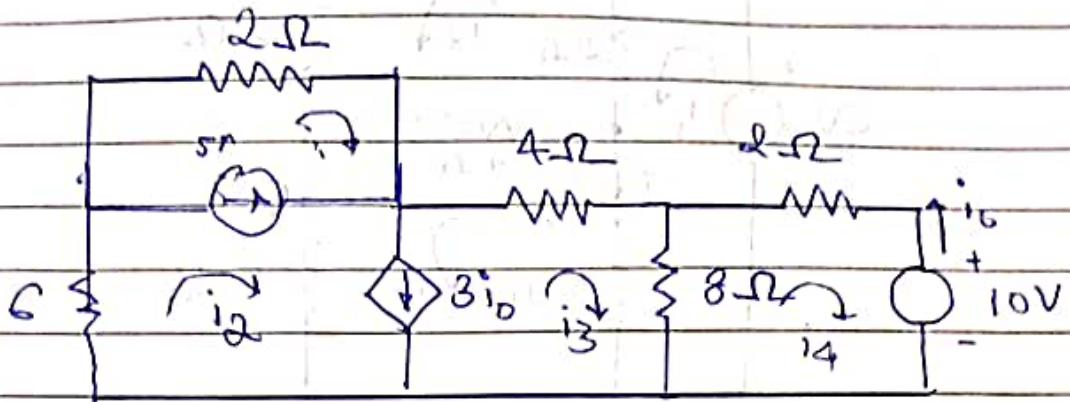

$$10 - 5 = -2i_1 + 3i_0 \quad (1) \quad (i_1 - i_3)A - (i_1 - i_2)2 = 5$$

~~$$10 - 0 = -2i_1 - 4i_3 - 2i_4 - 10 + 6i_2 = 0$$~~

~~$$i_1 + 3i_2 + 2i_3 + i_4 + 10 = 0 \quad (1)$$~~

~~$$i_2 = 2.5A$$~~

$$i_2 = -2.5A$$

~~$$i_3 = 3.42A$$~~

$$i_3 = -3.42A$$

~~$$i_4 = 2.14A$$~~

$$i_4 = -2.14A$$

~~$$i_1 = 12.5A$$~~

$$i_1 = -12.5A$$

~~$$i_2 = 7.5A$$~~

$$i_2 = -7.5A$$

~~$$i_3 = 9.6A$$~~

$$i_3 = -9.6A$$

~~$$i_4 = 5.77A$$~~

$$i_4 = -5.77A$$

~~$$-2i_1 - 4i_3 - 8(i_3 - i_4) - 6i_2 = 0 \quad (2)$$~~

~~$$-2i_1 - 4i_3 - 8i_2 + 8i_4 - 6i_2 = 0$$~~

~~$$-2i_1 - 6i_2 - 12i_3 + 8i_4 = 0$$~~

~~$$i_1 + 3i_2 + 6i_3 - 4i_4 = 0 \quad (1)$$~~


$$i_2 = 5 + i_1$$

$$i_2 - i_1 = 5 \quad (3)$$

$$5 + i_1 = 3i_0 + i_3$$

$$-i_1 + i_3 + 3i_0 = 5 \quad (4)$$

ANS:

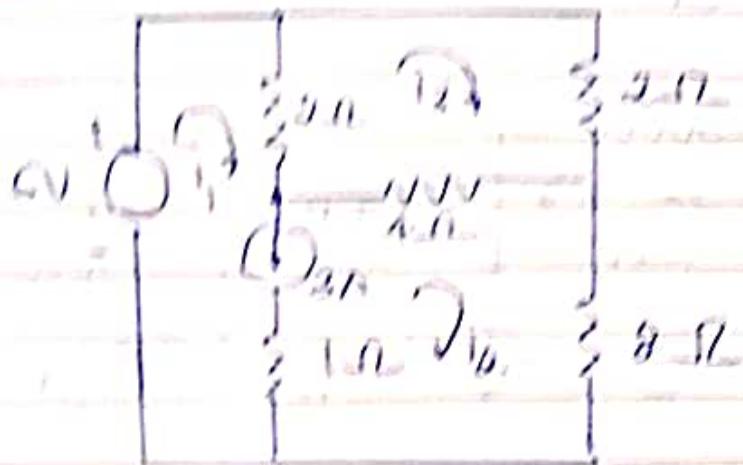

$$0 = 2(i_1 - i_2) - 4(i_2 - i_3) - 3i_3 = 0 \quad \text{--- (1)}$$

$$-2(i_2 - i_1) - 2(i_3) - 4(i_3 - i_2) = 0 \quad \text{--- (2)}$$

$$i_1 = i_2 + i_3 + 3$$

$$i_1 = i_0 = i_3 + 3 \quad \text{--- (3)}$$

$$-2i_3 + 2i_1 = 2i_3 - 4i_3 + 4i_2 = 0$$

$$2i_1 + 4i_0 = 8i_3 = 0$$

$$i_1 + 0.2i_0 = 4i_2 = 0 \quad \text{--- (4)}$$


$$-2i_3 + 2i_1 = 2i_3 \quad 0 = 2i_1 + 2i_3 - 4i_2 + 4i_3 - 8$$

$$2i_1 + 12i_0 - 6i_3 = 6$$

$$i_1 + 6i_0 - 3i_3 = 3 \quad \text{---}$$

$$\begin{bmatrix} i_1 = 4.8A \\ i_2 = 0.4A \\ i_3 = 1.4A \end{bmatrix}$$

Youtube

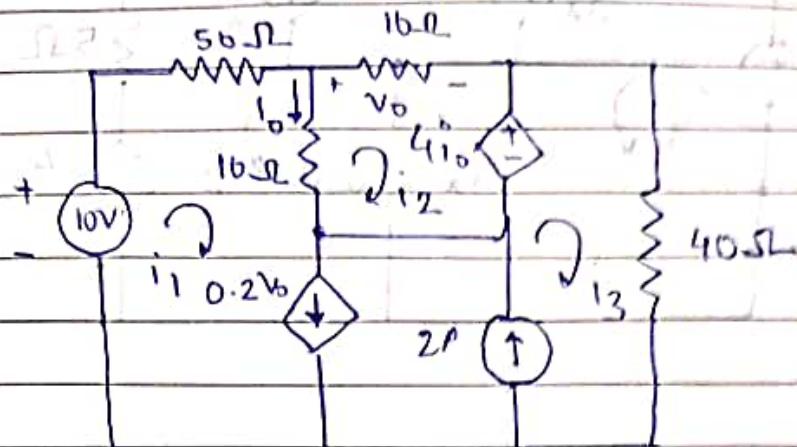

$$10 - 50i_1 - 10(i_1 - i_2) + 4i_0 - 40i_3 = 0$$

~~$$10 - 60i_1 + 10i_2 + 4i_0 - 40i_3 = 0$$~~

~~$$60i_1 - 10i_2 + 40i_3 - 4i_0 = 10 \quad \text{--- (1)}$$~~

~~$$10(i_2 - i_1) - 10i_2 - 4i_0 = 0$$~~

~~$$i_1 - 10i_2 - 4i_0 = 0$$~~

~~$$10i_1 + 4i_0 = 0 \quad \text{--- (2)}$$~~

~~$$10i_2 = V_o \quad \text{--- (3)}$$~~

$$i_1 = -0.923A$$

~~$$i_1 - i_2 + i_2 = 0.2V_o$$~~

$$i_2 = -0.457A$$

~~$$i_1 = 0.2V_o \quad i_0 = 2.32A$$~~

~~$$i_1 = 2i_2 \quad V_o = -4.94V$$~~

~~$$i_2 - i_3 + 2 = i_2$$~~


~~$$i_3 = 2A \quad \text{--- (5)}$$~~

~~$$60i_1 - 10i_2 + 40 \times 2 - 4(-10i_1) = 10$$~~

$$70i_1 = 54 \quad i_1 = 0.771A$$

~~$$70i_1 - 10i_2 + 70 = 0 \quad \text{--- (7)}$$~~

$$i_1 = -0.457A$$

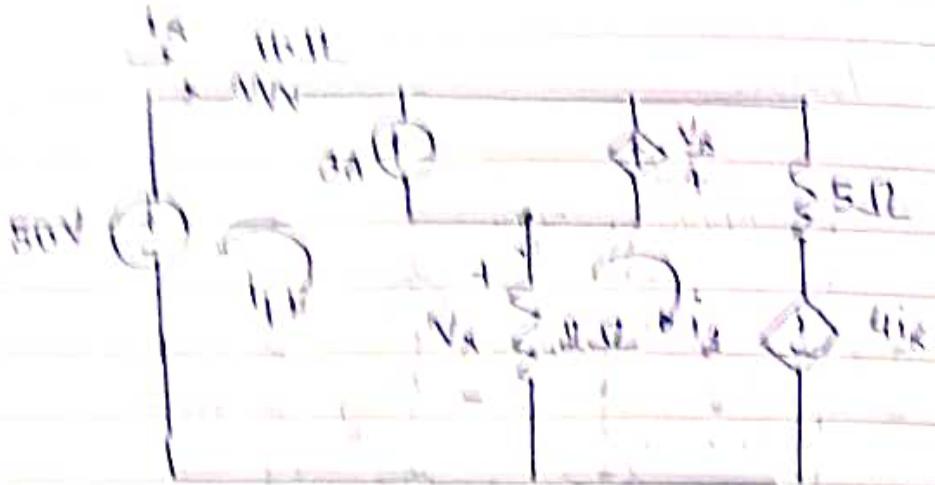

$$50 - 10i_1 - 5i_2 = 4i_3 = 0 \rightarrow \textcircled{1}$$

$$i_1 = i_2 \rightarrow \textcircled{2}$$

$$\omega(i_2 = i_1) = V_R \rightarrow \textcircled{3}$$

$$3 + \frac{V_R}{4} = i_2 - i_1 \rightarrow \textcircled{4}$$

$$3 + \frac{V_R(i_2 - i_1)}{4} = i_2 - i_1$$

$$3 + 2i_2 - 2i_1 = 0$$

$$i_2 - i_1 = 6 \rightarrow \textcircled{5}$$

$$10i_1 - 5i_2 = 4i_3 = 50$$

$$6i_1 - 5i_2 = 50 \rightarrow \textcircled{6}$$

$$\left\{ \begin{array}{l} i_1 = 80\text{A} \\ i_2 = 86\text{A} \end{array} \right.$$


$$\left\{ \begin{array}{l} i_3 = 80\text{A} \\ V_R = 12\text{V} \end{array} \right.$$

$$50 = 14i_1 - 5i_2 \rightarrow \textcircled{7}$$

$$i_1 = 2.165\text{A}$$

$$i_2 = 4.105\text{A}$$

$$V_R = 4\text{V}$$

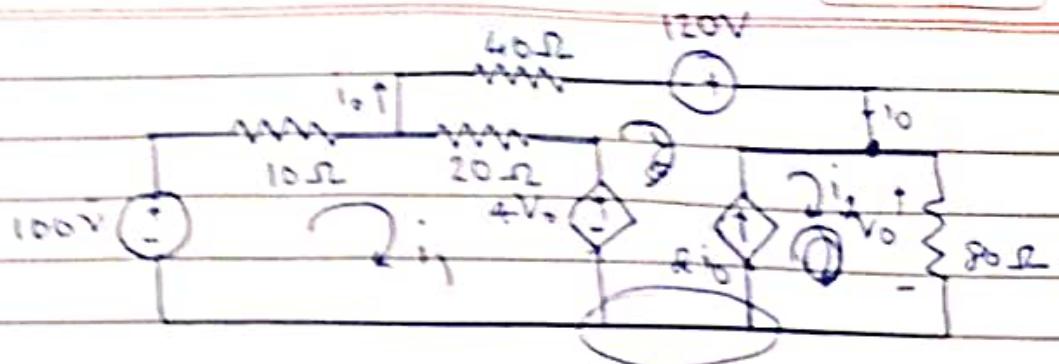

$$100 - 10i_1 - 20(i_1 - i_0) - 4V_0 = 0$$

$$100 = 10i_1 + 20i_1 - 20i_0 + 4V_0$$

~~$$5i_1 - 30i_0 + 4V_0 = 100 \quad \text{--- (1)}$$~~

~~$$15i_1 - 10i_0 + 2V_0 = 50 \quad \text{--- (2)}$$~~

$$100 - 10i_1 - 40i_0 + 120 - 80i_2 = 0$$

$$i_1 + 8i_2 + 4i_0 = 22 \quad \text{--- (3)}$$

~~$$80i_2 = V_0 = 0 \quad \text{--- (4)}$$~~

~~$$i_2 - 2i_0 + (i_1 - i_0) \quad 3i_0 = i_2 \quad \text{--- (5)}$$~~

$$i_2 + (i_1 - i_0) - 3i_0 - (i_1 - i_0) = 0$$

~~$$i_2 = 3i_0 \quad \text{--- (6)}$$~~


$$i_1 = 178.8 \text{ A}$$

$$i_2 = -5.6 \text{ A}$$

$$i_3 = -16.8 \text{ A}$$

$$\therefore V_0 = 1344 \text{ V}$$

(4)

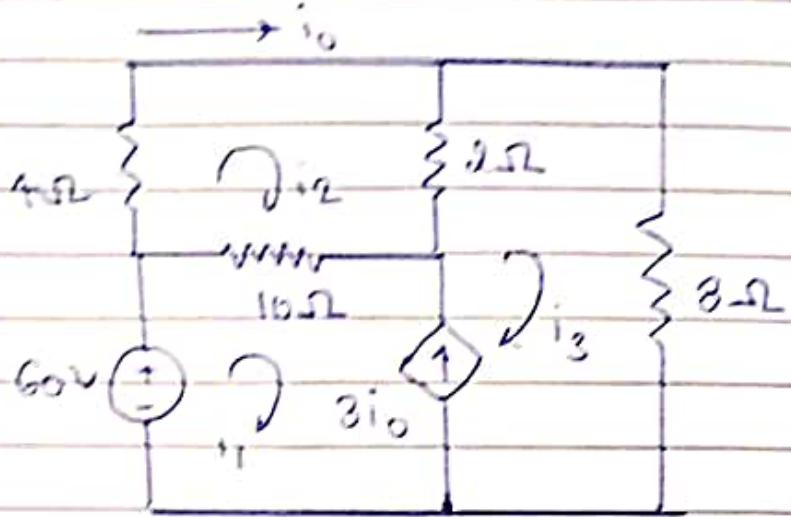

$$60 - 10(i_1 - i_2) - 2(i_2 + i_3 - i_1) - 8i_3 = 0$$

$$60 - 10i_1 + 10i_2 - 2i_2 + 2i_3 - 8i_3 = 0$$

$$60 - 10i_1 + 12i_2 - 10i_3 = 0$$

6

$$5i_1 - 6i_2 + 5i_3 = 0 \quad \text{--- (1)}$$

$$4 - 4i_2 - 2(i_2 - i_3) - 10(i_2 - i_1) = 0$$

$$-4i_2 - 2i_2 + 2i_3 - 10i_2 + 10i_1 = 0$$

$$10i_1 - 16i_2 + 2i_3 = 0$$

$$5i_1 - 8i_2 + i_3 = 0 \quad \text{--- (2)}$$

$$i_3 = 3i_0 + i_1 \leftarrow \text{--- (3)}$$

$$i_1 - i_3 + 3i_0 \geq 0 \quad \text{--- (3)}$$

$$i_2 - i_0 \geq 0 \quad \text{--- (4)}$$


$$i_1 = 1.442A$$

$$i_2 = 1.731A$$


$$i_3 = 6.63A$$

$$i_0 = 6.73A$$

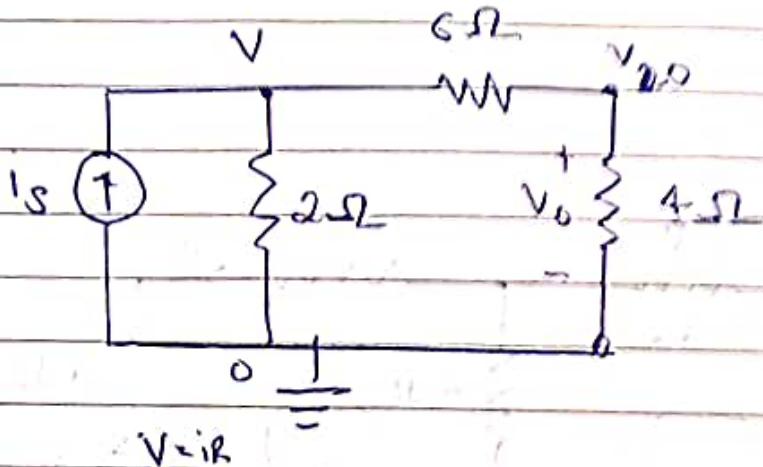(Q) Find V_o in the cut where $i_s = 15A \rightarrow 30A$



$$V = iR$$

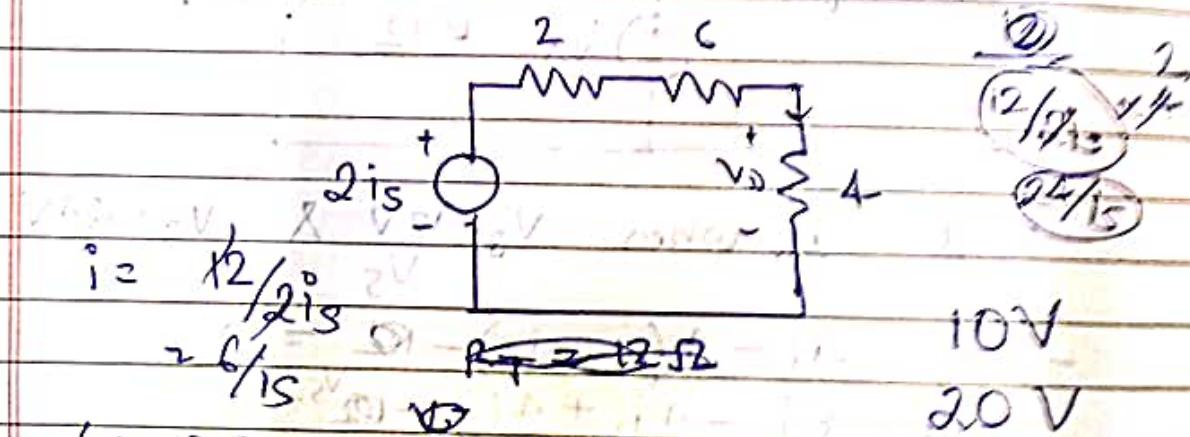

$$\frac{12}{i_s} 4 \quad V_o = \left(\frac{2}{i_s}\right) A$$

$$\frac{12}{i_s}$$

$$i_s \frac{V - V_o}{2} + \frac{V_o - V}{4} - i_s = 0$$


$$\frac{V_o}{4} + \frac{V_o - V}{6} = 0$$

$$(5) \quad 2V_o + 3V_o - 6V = 0$$

$$5V_o = 6V \Rightarrow V_o = 1.2V$$

$$5V_o = 6V \Rightarrow V_o = 1.2V$$

$$2V_o + 3V_o - 6V = 0$$

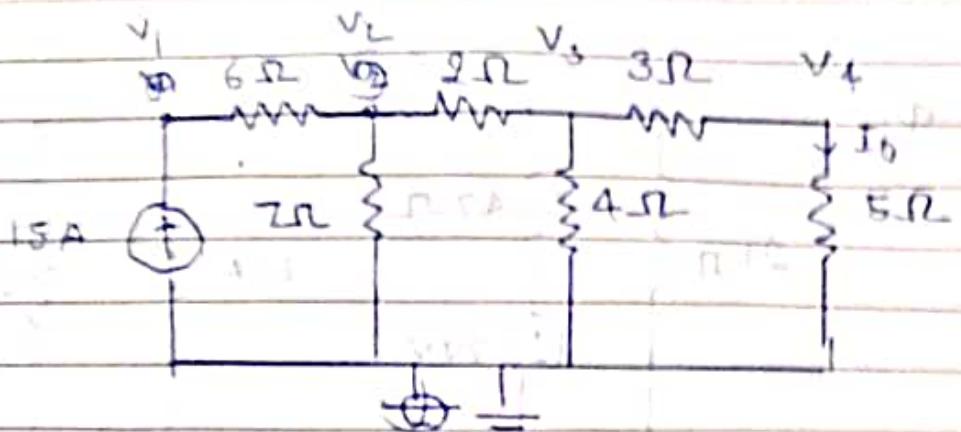

$$15 = \frac{V_1 - V_2}{6}$$

$$V_1 - V_2 = 90 \quad \text{--- (1)}$$

$$\frac{V_2 - V_1}{6} + \frac{V_2 - V_3}{2} + \frac{V_2}{7} = 0 \quad \text{--- (2)}$$

$$\frac{V_3 - V_2}{2} + \frac{V_3 - V_4}{3} + \frac{V_3}{4} = 0 \quad \text{--- (3)}$$


$$V_4 = \frac{V_4 - V_3}{5} \quad \text{--- (4)}$$

Superposition Theorem


It states that the response in a linear circuit having more than 1 independent source can be obtained by adding the responses caused by the sources each acting one at a time.

When a single source is considered the other independent voltage sources are short circuited and independent current sources are open circuited.

(P)

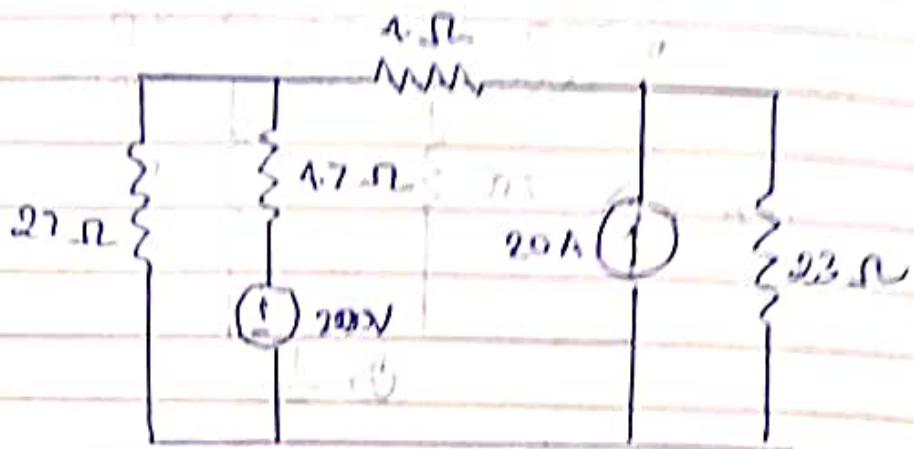


Find current in 23Ω resistor.

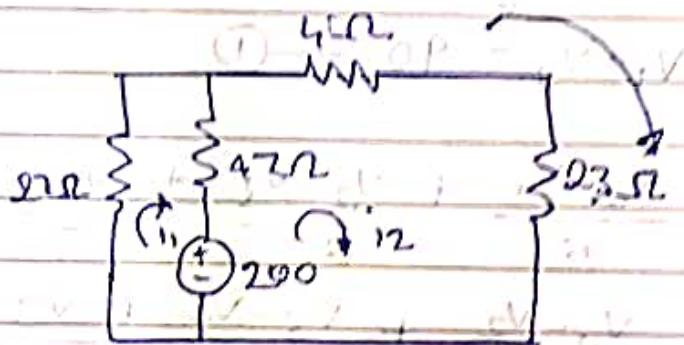



$$\begin{aligned} -27i_1 - 47(i_1 - i_2) - 200 &= 0 \\ -27i_1 - 47i_1 + 47i_2 &= 200 \\ 47i_2 - 74i_2 &= 200 \end{aligned}$$
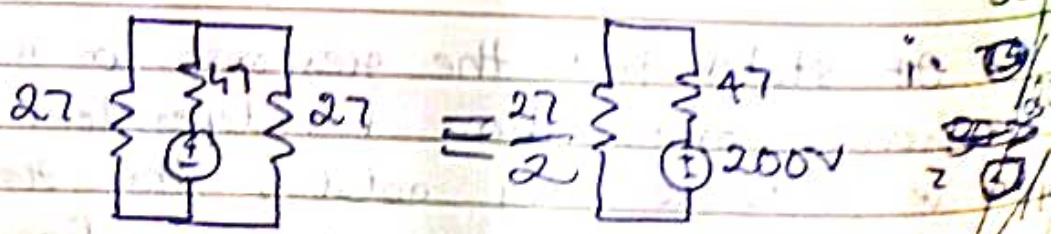
$$200 - 47(i_2 - i_1) + 4i_2 - 28i_2 = 0$$



$$i = \frac{200}{860.5} = 0.23 A$$

$$i_1 = \frac{3.3}{2} = 1.65 A$$

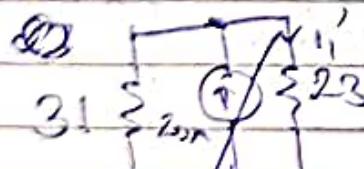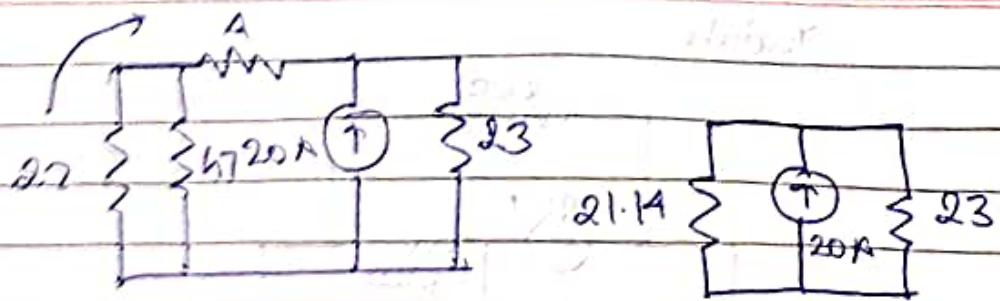

$$R_{eq} = 11.015$$

$$i_1 V = 220 \cdot 308$$

$$[i_1 = 9.58 \text{ A}]$$


$$V = 244.97 \text{ V}$$

$$i_T = i_1 + i_1'$$


$$= 1.65$$

$$+ 9.58$$

$$\underline{11.23 \text{ A}}$$

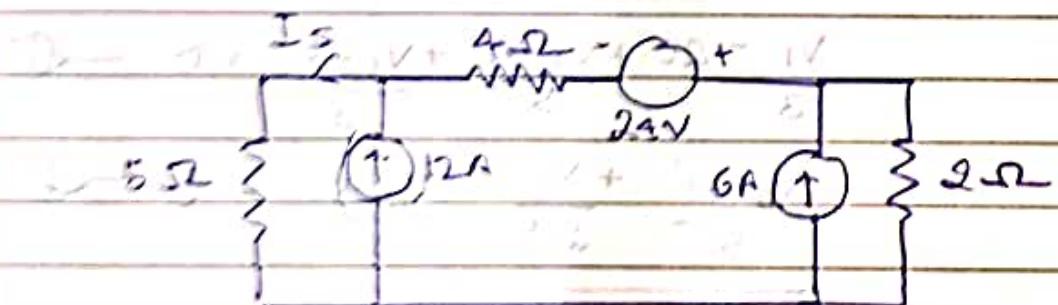



find I_3 in slot?

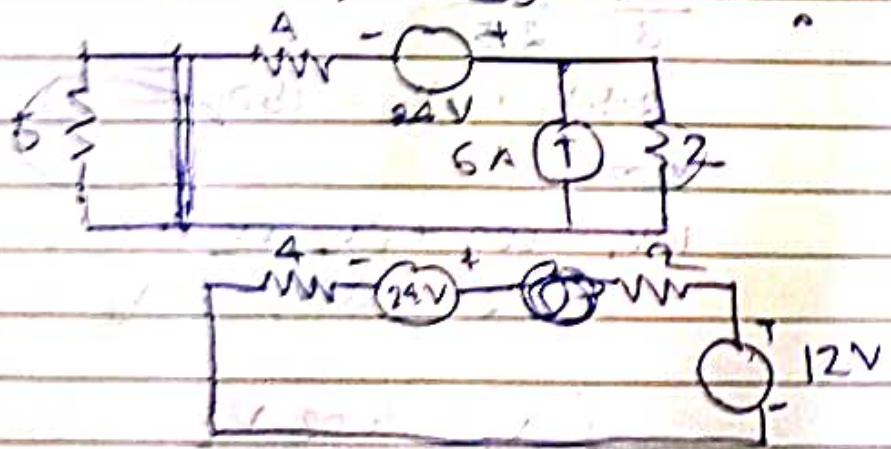

$$-4i + 24 - 2i - 12 = 0$$

$$12 = 6i$$

$$[i = 2 \text{ A}]$$

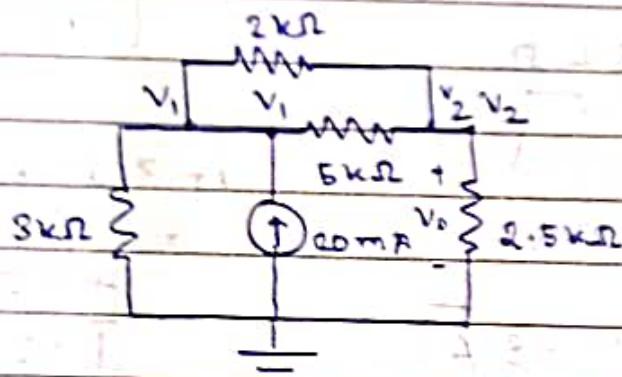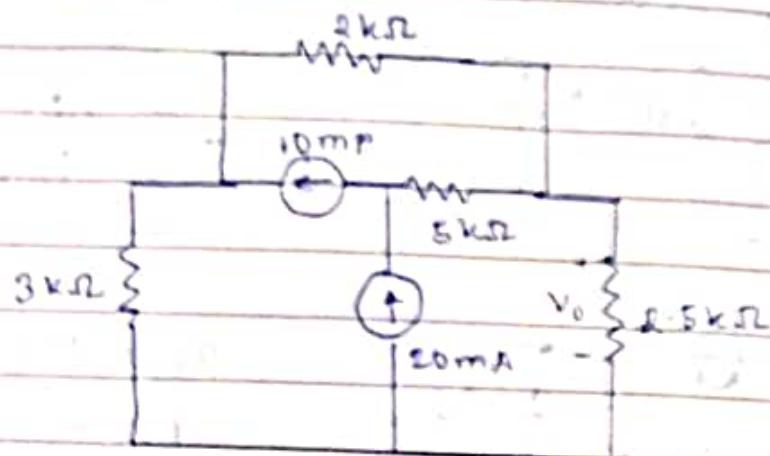Youtube

$$\frac{V_1}{3} - 20 + \frac{V_1 - V_2}{5} + \frac{V_1 - V_2}{2.5} = 0 \quad \textcircled{1}$$

$$\frac{V_2 - V_1}{5} + \frac{V_2}{2.5} + \frac{V_2 - V_1}{2.5} = 0 \quad \textcircled{2}$$

$$\frac{V_1 + V_2}{3} = 20$$


$$2.5V_1 + 3V_2 = 150 \quad \textcircled{3}$$

$$10V_1 - 600 + 5V_1 - 6V_2 + 15V_1 - 15V_2 = 0$$

$$31V_1 - 21V_2 = 600 \quad \textcircled{4}$$

$$\begin{cases} V_1 = 84.02 \text{ V} \\ V_2 = 21.64 \text{ V} \end{cases}$$
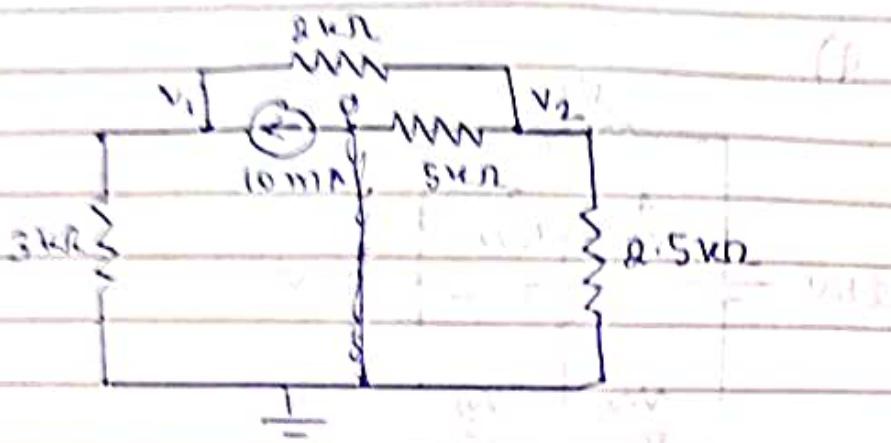
$$i_{o1} = \frac{V_2}{2.5} = 8.608 \text{ mA}$$



$$\frac{v_1}{3} + \frac{v_1 - v_2}{2} - 10 = 0$$

$$\frac{v_2 - v_1}{2} + \frac{v_2}{2.5} + 10 = 0$$

$$\frac{v_1}{3} + \frac{v_2}{2.5} = 0$$

$$2.5v_1 = -3v_2 \quad \textcircled{1}$$

$$5v_1 = -6v_2$$

$$\frac{v_2}{5} - 2v_1 + 3v_1 - 3v_2 - 60 = 0$$

$$5v_1 - 3v_2 = 60 \quad \textcircled{2}$$

$$-9v_2 = 60$$

$$v_2 = -20 = -6.67 \text{ V}$$



$$v_1 = 8 \text{ V}$$

$$i_{02} = \frac{v_2}{2.5} = -2.667 \text{ mA}$$

$$i = 10.94 \text{ mA}$$

$$V_o = i_0 R = \\ = 27.35 \text{ V}$$

(Q)

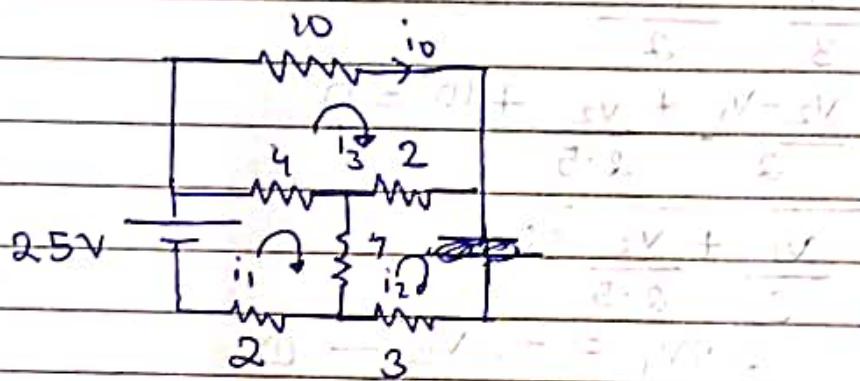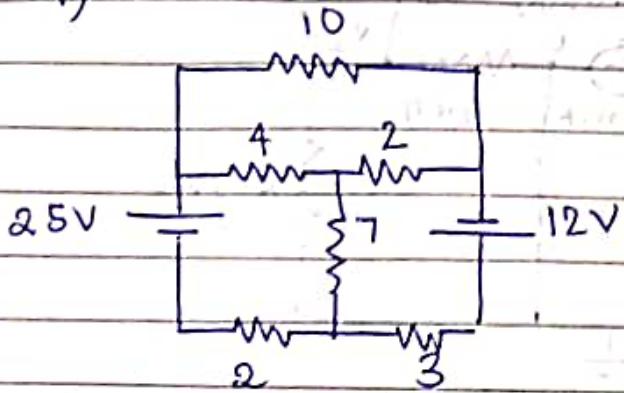

$$25 - 4(i_1 - i_3) - 7(i_1 - i_2) - 2i_1 = 0$$

$$25 - 4i_1 + 4i_3 - 7i_1 + 7i_2 - 2i_1 = 0$$

$$-13i_1 + 7i_2 + 4i_3 = -25 \quad \text{--- (1)}$$

$$-7(i_2 - i_1) - 2(i_2 - i_3) - 3i_2 = 0$$

$$-7i_2 + 7i_1 - 2i_2 + 2i_3 - 3i_2 = 0$$

$$7i_1 - 12i_2 + 2i_3 = 0 \quad \text{--- (2)}$$

$$-10i_3 - 2(i_3 - i_2) - 4(i_3 - i_1) = 0$$

$$-10i_3 - 2i_3 + 2i_2 - 4i_3 + 4i_1 = 0$$


$$4i_1 + 2i_2 - 16i_3 = 0 \quad \text{--- (3)}$$

$$i_1 = 3.466 \text{ A}$$

$$i_2 = 2.21 \text{ A}$$

$$i_3 = 1.14 \text{ A}$$



$$i_{01} = i_3 = 1.14 \text{ A}$$

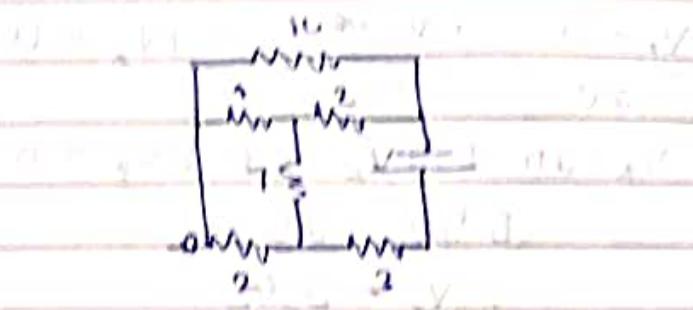

$$111) \quad i_{02} = 0.17A \rightarrow$$

$$x_0 = 1.861 \text{ A}$$

(Q)

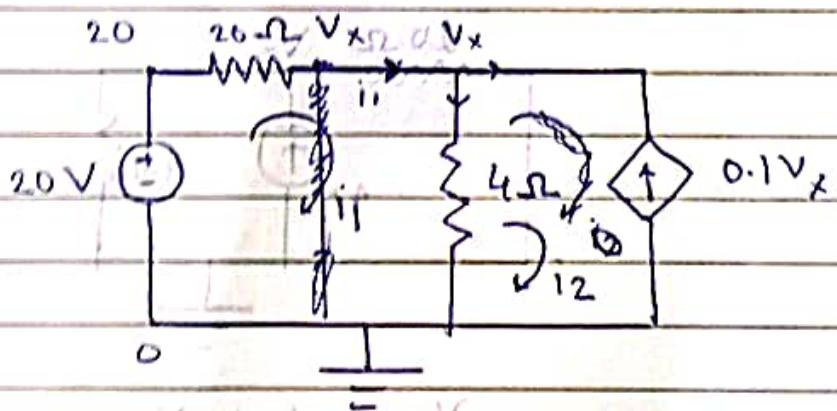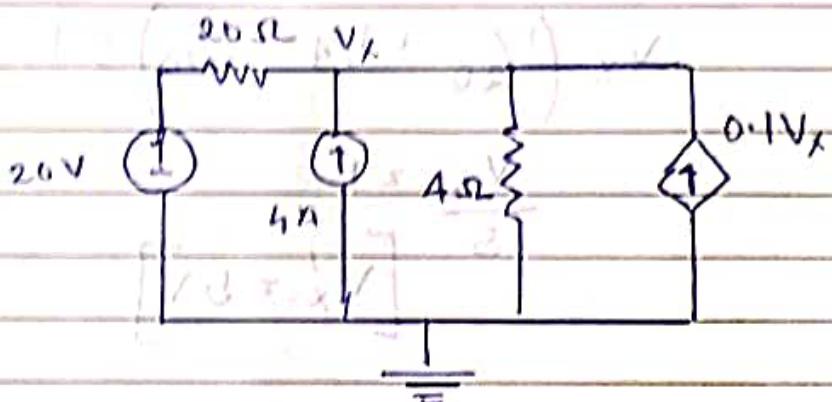

$$111) \quad 2.0 - 2.0i_1 - 4(i_1 - i_2) = 0$$

$$111) \quad 2.0 - 2.0i_1 - 4i_1 + 4i_2 = 0$$

$$111) \quad 24i_1 - 4i_2 = 2.0$$

$$111) \quad 1.6i_1 - i_2 = 5 \quad \text{--- (1)}$$

$$111) \quad i_1 = i_1 - i_2 - 0.1V_x \quad \text{--- (2)}$$

$$i_2 = -0.1V_x$$

$$\frac{V_x - 20}{20} + \frac{V_x - 4}{4} - 0.1V_x = 0$$

$$V_x - 20 + 5V_x - 0.8V_x = 0$$

$$5.5V_x = 20$$


$$V_x = 3.63$$

$$\frac{V_x - 1}{20} + \frac{V_x - 4}{4} - \frac{V_x}{10} = 0$$

$$V_x \left(\frac{1}{20} + \frac{1}{4} - \frac{1}{10} \right) = 1$$

$$\frac{V_x - 1}{5} = 1$$

$$V_x' = 5V$$

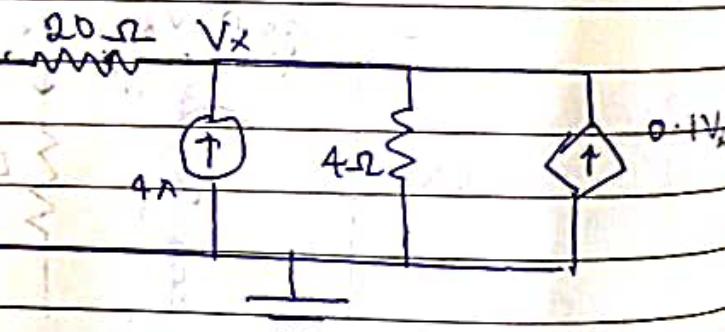

$$\frac{V_x - 4}{20} + \frac{V_x - 4}{4} - \frac{V_x}{10} = 0$$



$$\frac{5V_x - V_x}{20} = 4$$

$$\frac{4V_x}{20} = 4$$

$$V_x'' = 20V$$

$$V_x = 25V$$

(Q)

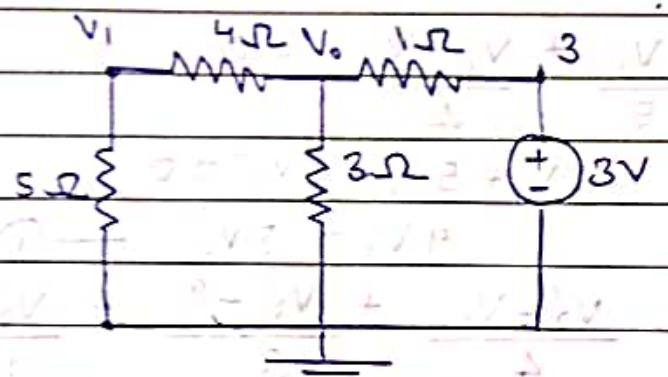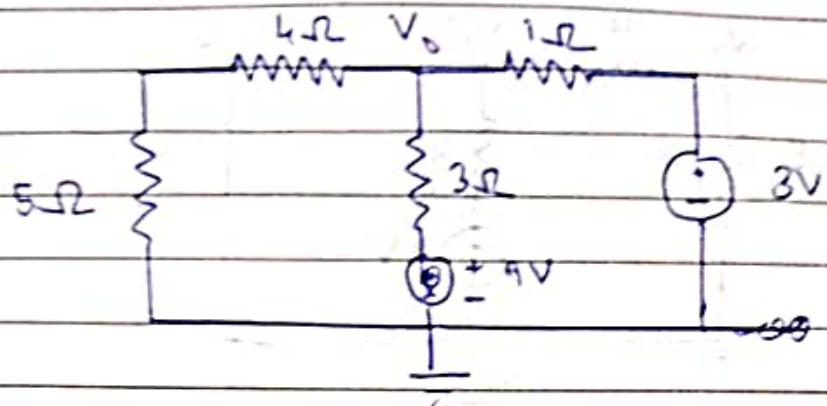

$$0 = 3 - V_o + \frac{V_o}{4} + \frac{V_o}{3} - \frac{V_1}{5}$$

$$V_o - 3 + V_o \cdot \frac{1}{4} + V_o \cdot \frac{1}{3} - V_1 \cdot \frac{1}{5} = 0$$

~~$$0 = 3 - V_1 + \frac{V_1}{4} + \frac{V_1}{3}$$~~

~~$$5V_1 - 15V_o - 36 + 4V_o + 3V_o - 3V_1 = 0$$~~

~~$$3V_1 - 12V_o - 18 - 19V_o - 3V_1 = 36 \quad \text{--- (1)}$$~~

$$\frac{V_1}{5} + \frac{V_1 - V_o}{4} = 0$$


~~$$\frac{9V_1}{20} - \frac{V_o}{4} = 0$$~~

~~$$20V_1 - 4V_o = 0$$~~

$$9V_1 - 5V_o = 0 \quad \text{--- (2)}$$

$$V_o = 2.07V$$

$$V_1 = 1.153V$$

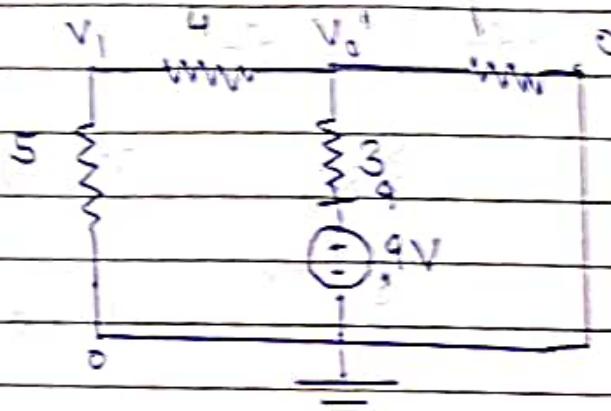

$$\frac{V_1}{5} + \frac{V_1 - V_o''}{4} = 0$$

~~$$4V_1 + 5V_1 - 5V_o'' = 0$$~~

$$9V_1 = 5V_o'' \quad \text{--- (1)}$$

$$\frac{V_o'' - V_1}{4} + \frac{V_o'' - 9}{3} + \frac{V_o''}{1} = 0$$

$$\frac{V_o''}{4} + \frac{V_o''}{3} + \frac{V_o''}{1} - \frac{V_1}{4} - 3 = 0$$


~~$$\frac{19V_o''}{12} - \frac{3V_1}{12} - \frac{36}{12} = 0$$~~


~~$$-19V_o'' - 3V_1 = 36 \quad \text{--- (2)}$$~~

$$V_o'' = 2.07V$$

$$V_o = 4.14V$$

(q)

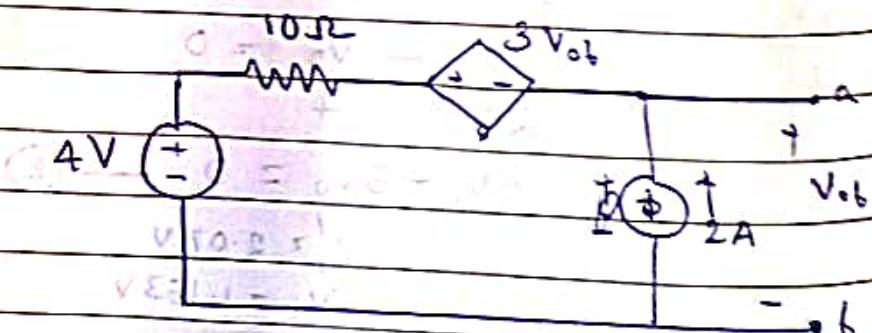

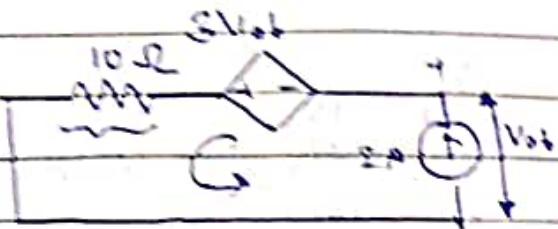

$$V_R = 10 \cdot I$$



$$= 20V$$

$$V_{ob} = V_R + V_{ob}$$

$$\therefore 3V_{ob} - V_R + V_{ob} = 0$$

$$4V_{ob} = 20$$

$$V_{ob} = 5V$$

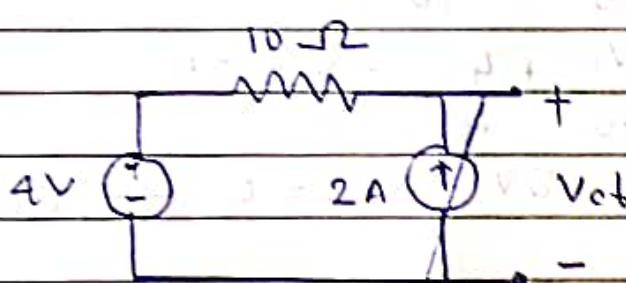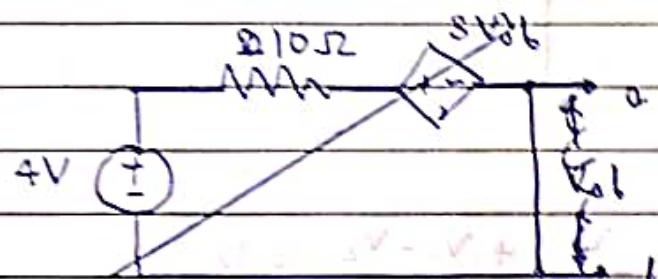


{ DO not remove
current/voltage
dependent
sources }

$$V_R = 20V$$

$$V_{ob} - V_R - 4 = 0$$

$$V_{ob} = 24V$$



$$12 + 24 + V_{ob} = 29V$$

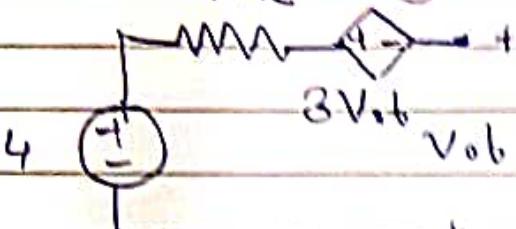

$$4 - 0 - 3V_{ob} - V_{ob} = 0$$

$$V_{ob} = 1V$$

$$[V_{ob} = 6V]$$

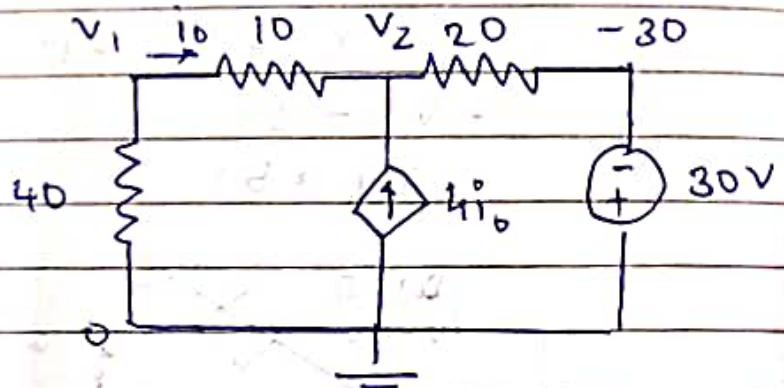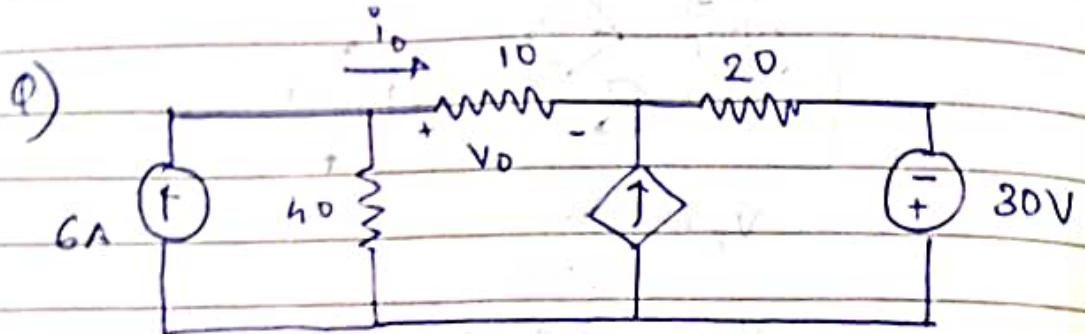

$$\frac{V_3}{40} + \frac{V_1 - V_2}{10} = 0$$

$$\frac{V_1}{40} + \frac{4V_1 - V_2}{40} - \frac{V_2}{10} = 0$$

$$5V_1 - 4V_2 = 0 \quad \leftarrow (1\right)$$

$$\frac{V_2 - V_1}{10} + \frac{V_2 + 30}{20} - 4\left(\frac{V_1 - V_2}{10}\right) = 0$$

$$\left(\frac{V_2 - V_1}{10}\right) + 4\left(\frac{V_2 - V_1}{10}\right) + \frac{V_2 + 30}{20} = 0$$

$$2\left(\frac{5V_2 - 5V_1}{20}\right) + \frac{V_2 + 30}{20} = 0$$

$$10V_2 - 10V_1 + V_2 + 30 = 0$$

$$11V_2 - 10V_1 = -30$$


$$V_1 = -8$$

$$V_2 = -10V$$

$$V_s = V_1 - V_2$$

$$= 8V$$

$$i_3 = 2/40 = 0.2A$$

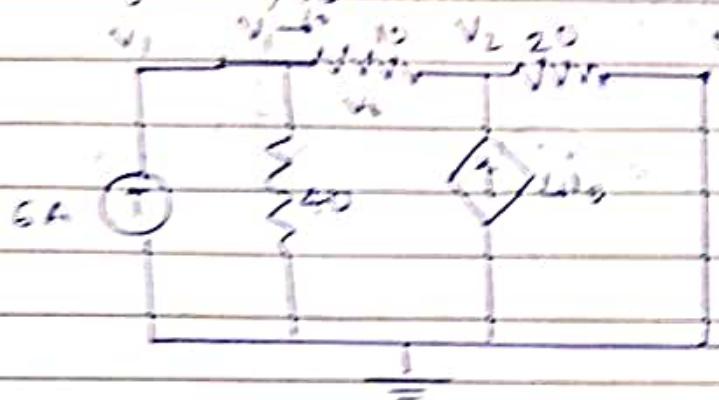

$$\frac{V_1 - V_2}{10} + \frac{V_1}{40} = 6 \quad \text{--- (1)}$$

$$\frac{4V_1 - V_2}{40} - \frac{4V_2}{20} = 6$$

$$3V_1 - 4V_2 = 240 \quad \text{--- (1)}$$

$$\frac{V_2 - V_1}{10} + \frac{V_2}{20} - 4\left(\frac{V_1 - V_2}{10}\right) = 0$$

$$5(V_2 - V_1) + \frac{V_2}{20} = 0$$

$$5 \frac{10V_2 - 10V_1 + V_2}{20} = 0$$

$$11V_2 = 10V_1 \quad \text{--- (2)}$$

$$V_1 = 110V$$

$$V_2 = 160V$$

~~$$V_2 = V_3 - V_1 = -16V$$~~



~~$$i_3 = -16/20 = -0.8A$$~~

~~$$V_1 - V_2 = 16V$$~~

~~$$i_3 = 16/20 = 0.8A$$~~

$$\begin{cases} V_2 = 16 + 2 \\ i_3 = 1.8A \end{cases}$$

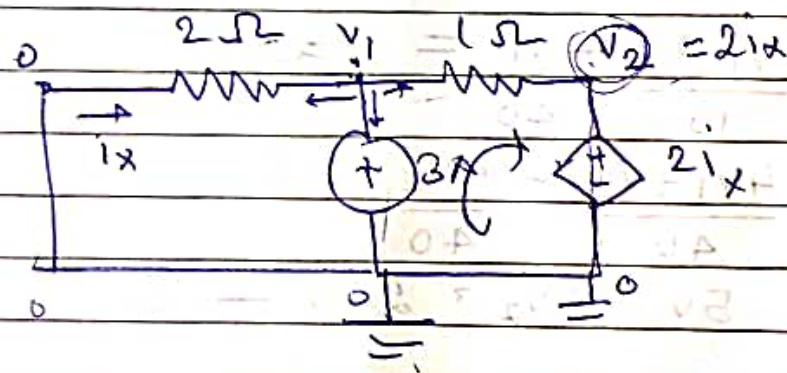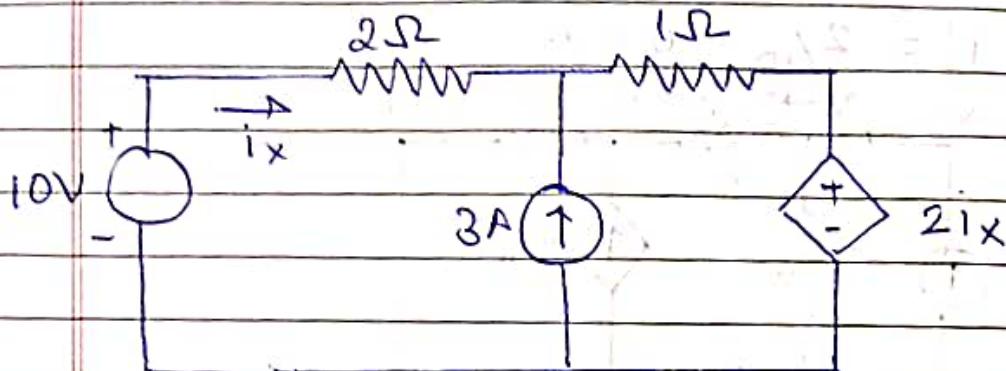Q) Find i_x in ckt using superposition theorem



$$\frac{V_1 - 3 + V_1 - V_2}{2} = 0 \quad | \cdot 2 \quad 3(-2i_x) = 6 \\ \frac{V_1 - 3 + V_1 - V_2}{2} = 0 \quad | \cdot 1 \quad 3(-2i_x) = 6 \\ \underline{V_1 - 6 + 2V_1 - 2V_2 = 0} \\ \underline{3V_1 - 2V_2 = 6} \quad \text{--- (1)}$$


$$V_2 = 2i_x \quad \text{--- (2)}$$

$$-\frac{V_1}{2} = i_x \quad \text{--- (3)}$$

~~$V_1 = -2i_x$~~

$$-6i_x - 2i_x = 6 \\ -8i_x = 6 \\ i_x = -\frac{3}{4} \quad \text{--- (4)}$$

$$V_1 = -2i_x \\ V_2 = 2i_x$$



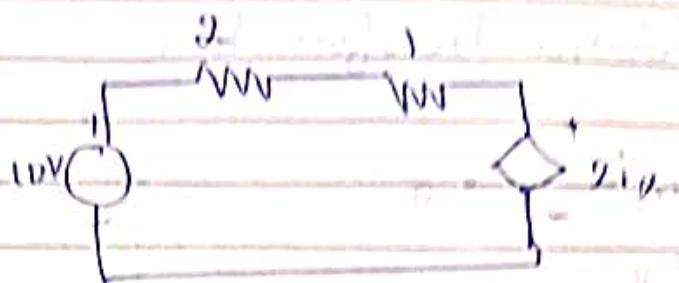


$$10 - 2i_x - i_x - 2i_x = 0$$


$$i_x = \frac{10}{5\Omega} = 2A$$

$$i_x = i_x + i_{x_2}$$

$$\therefore 2A = 1.25A$$

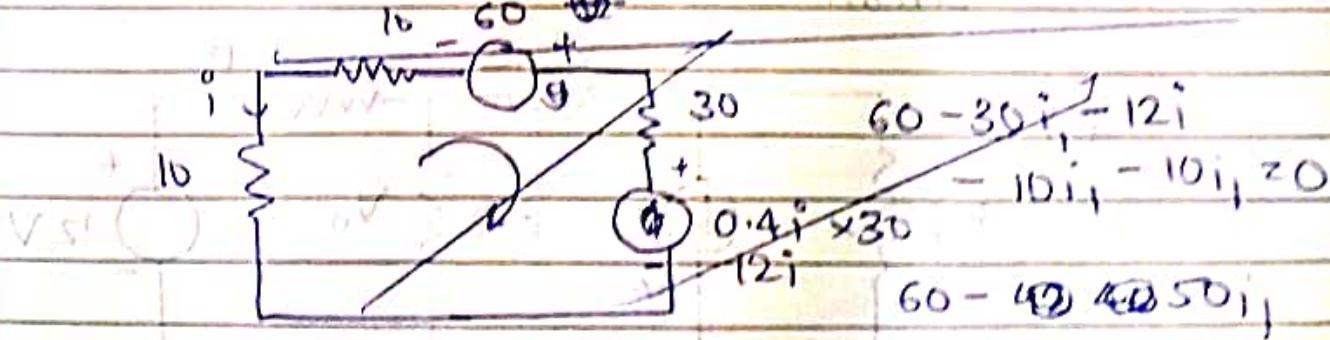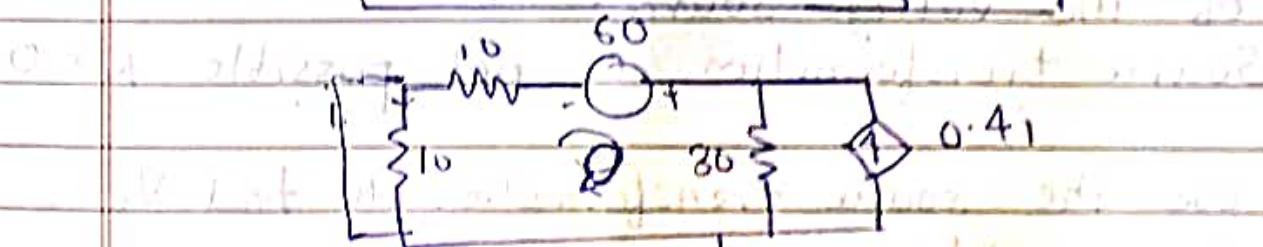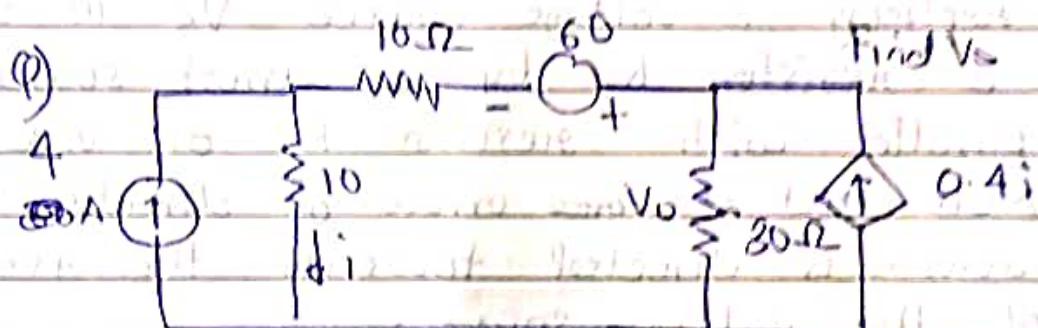


Source Transformation



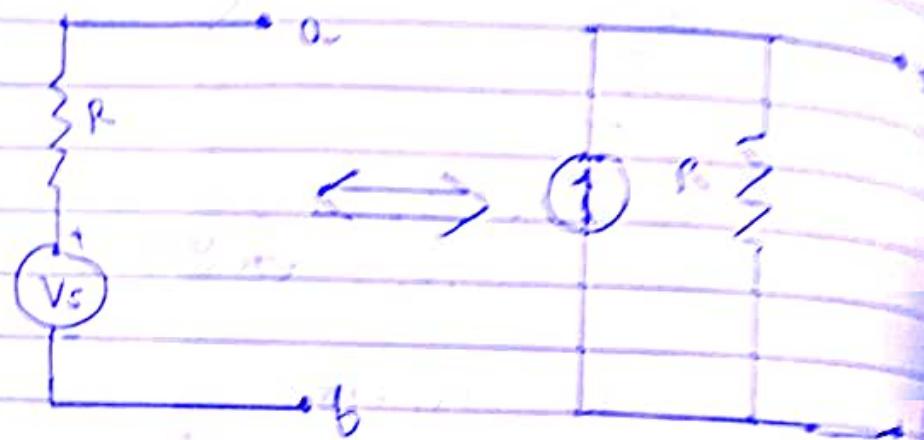


A source transformation is the process of replacing a voltage source V_s in series with a resistor R by a current source I_s in parallel with resistor R , or vice versa. Note that \rightarrow ~~one~~ arrows of direction of current source is directed towards the $-ve$ terminal of the voltage source.


Source transformation is not possible if $R=0$.

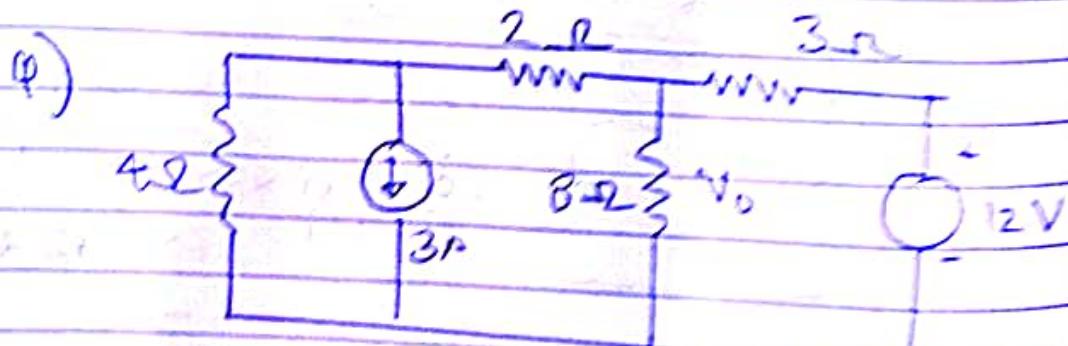Use the source transformation to find V_{ab} in the circuit.



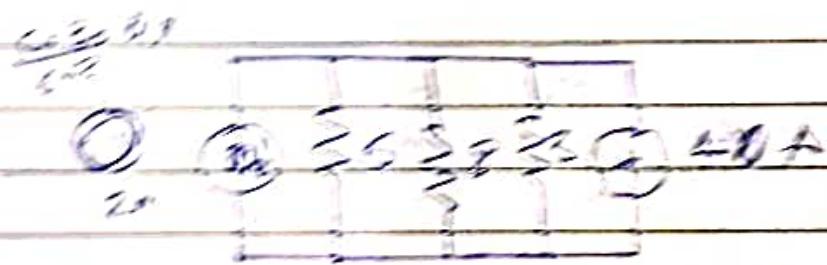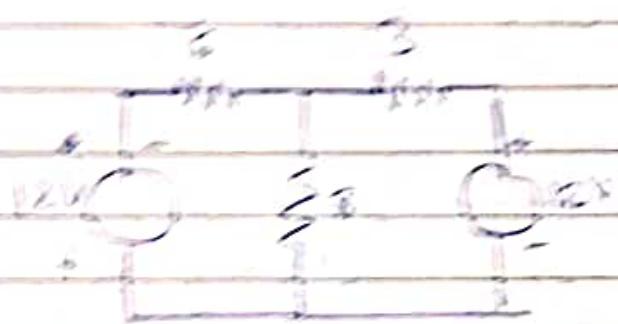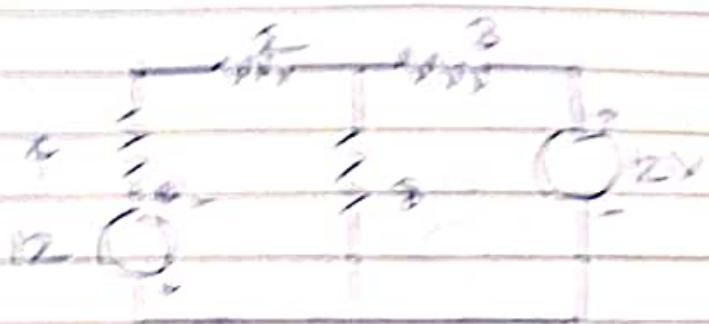

$20 \cdot 3 = 60$

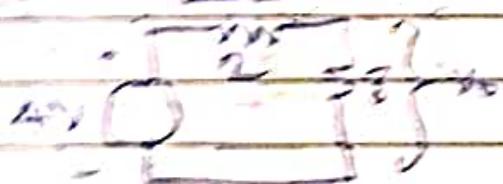

$12 \cdot 10^3$








$i = 0.4 A$

$\text{approx } 4.48$




$? 3.27$

~~11~~

(Q)

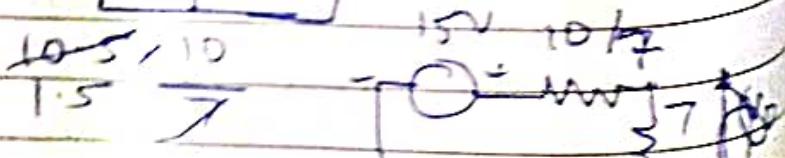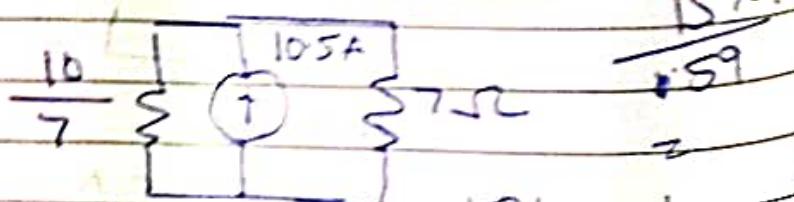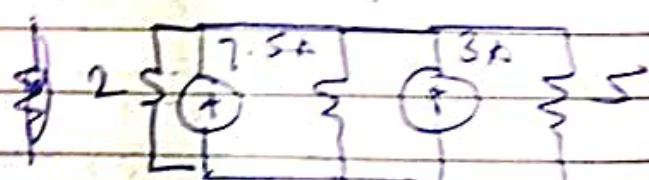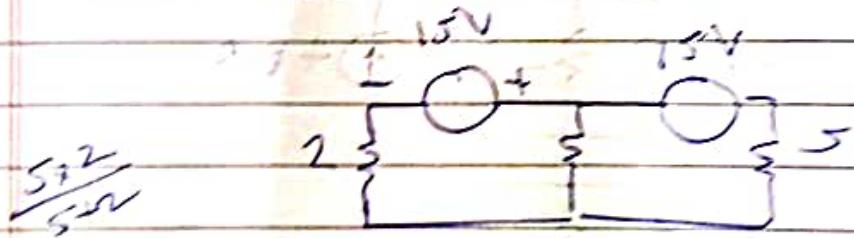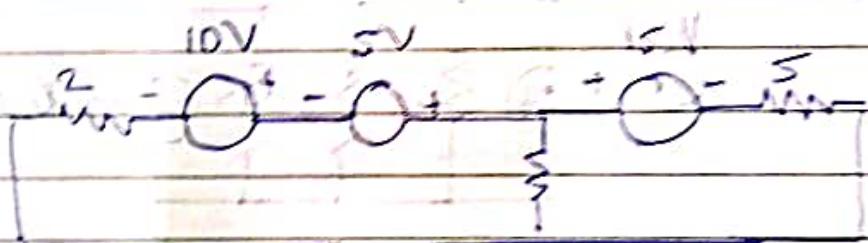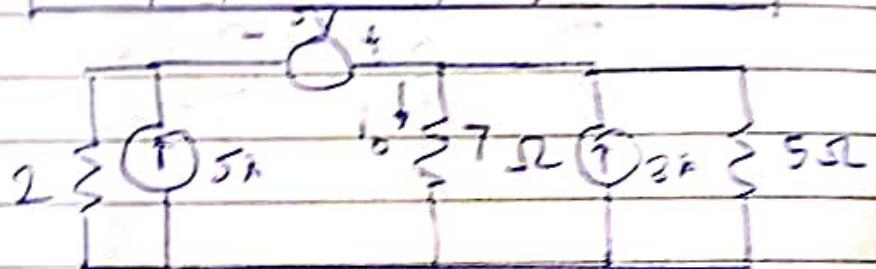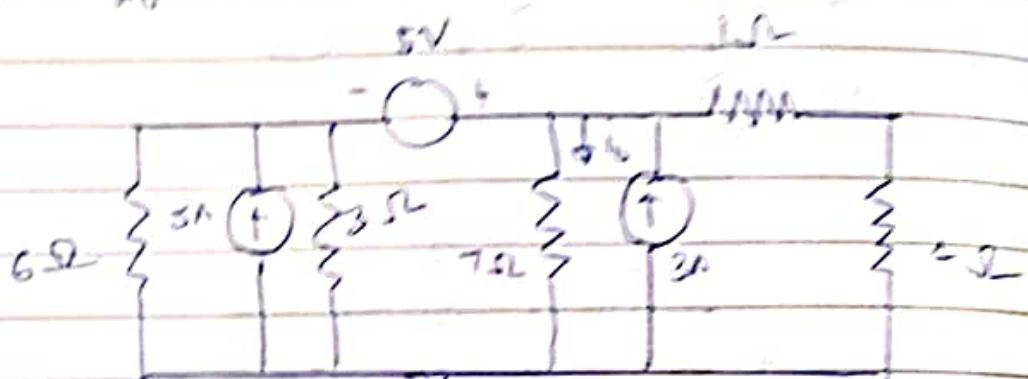Find i_1 , i_2 , i_3 

$$[i = 1.78 \text{ A}]$$

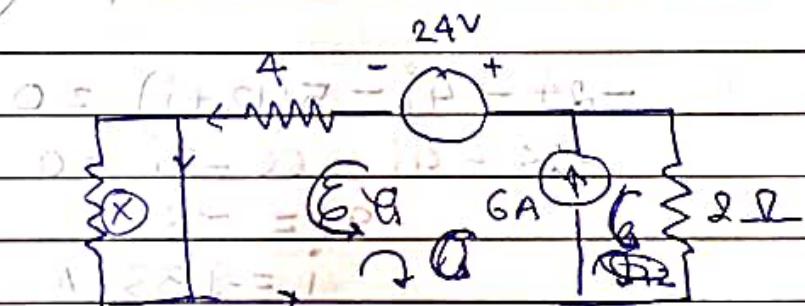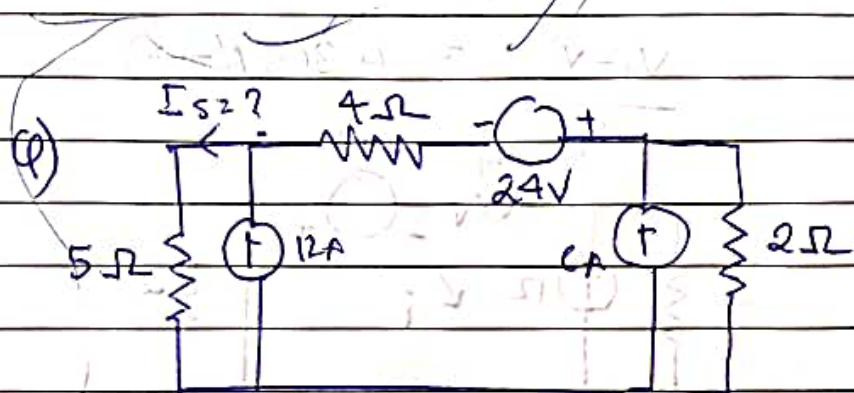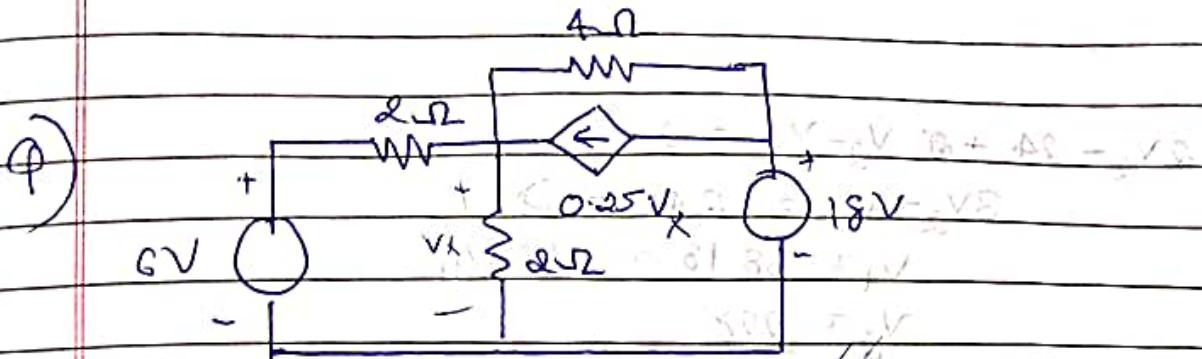


$$-24 - 4i + 2i = 0$$

$$-4i_1 + 24 - 2(6+i) = 0$$

$$-4i_1 + 24 - 12 - 2i = 0$$

$$12 = 6i$$

$$i = 2A \rightarrow$$

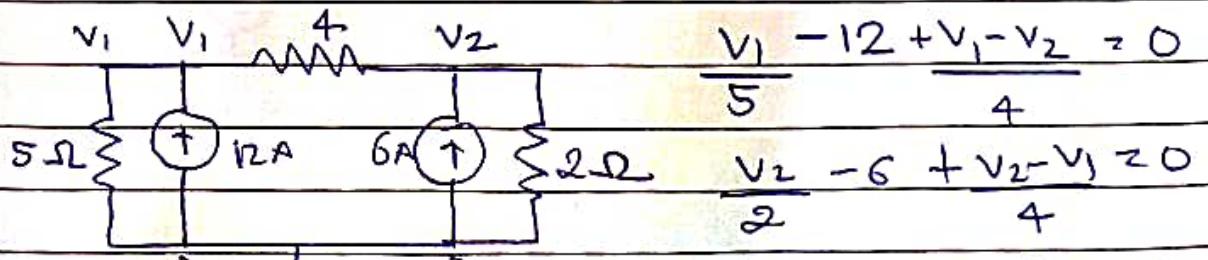

$$\frac{V_1}{5} - 12 + \frac{V_1 - V_2}{4} = 0$$

$$\frac{V_2}{2} - 6 + \frac{V_2 - V_1}{4} = 0$$

$$4V_1 - 240 + 5V_1 - 5V_2 = 0 \quad (1)$$

$$9V_1 - 5V_2 = 240 \quad (1)$$


$$2V_2 - 24 + V_2 - V_1 = 0$$

$$3V_2 - V_1 = 24 \quad \text{--- (2)}$$

$$V_1 = 38.18 \approx 420/\mu$$

$$V_2 = \frac{228}{\mu}$$
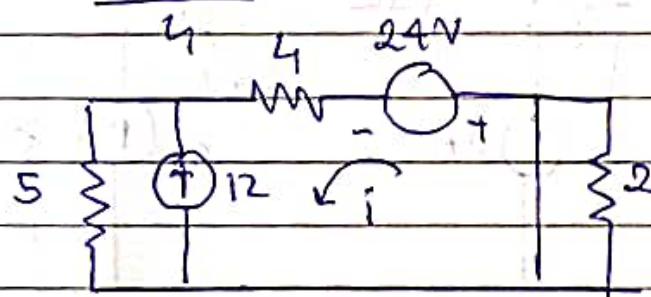
$$\frac{V_1 - V_2}{4} = 4.363 \text{ A} (\rightarrow)$$



$$-24 - 4i - 5(12+i) = 0$$



$$-24 - 4i - 60 - 5i = 0$$

$$-9i = -84$$

$$i = 9.33 \text{ A}$$

$$i = 9.33 \text{ A} (\rightarrow)$$

$$\{ i_s = 3.693 \text{ A} \}$$

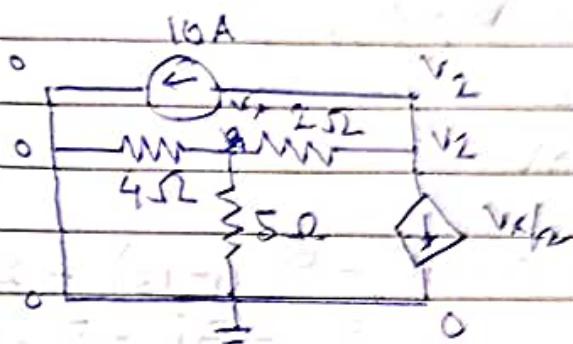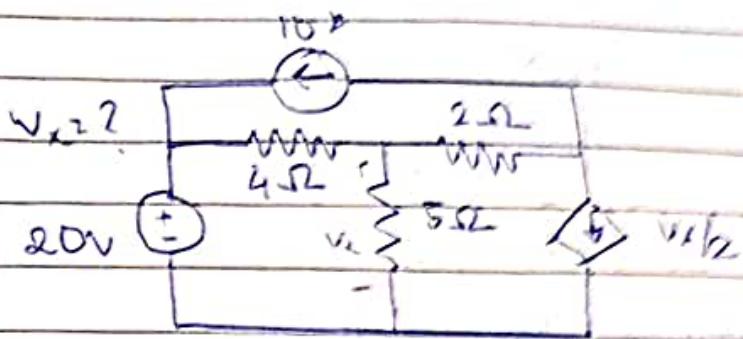

$$\frac{v_{x_1}}{4} + \frac{v_{x_1}}{5} + \frac{v_{x_1} - v_2}{2} = 0$$

$$5v_{x_1} + 4v_{x_1} + 10v_{x_1} - 10v_2 = 0$$

$$10v_2 = 19v_{x_1} \quad \text{--- (1)}$$


$$\frac{v_2 - v_{x_2}}{2} + \frac{v_{x_2} + 10}{2} = 0$$

$$v_2 - v_{x_2} + v_{x_2} + 20 = 0$$

$$v_2 = -20 \text{ V}$$

$$\left\{ \begin{array}{l} v_{x_1} = \frac{-200}{19} \text{ V} \\ v_{x_2} = -10.526 \text{ V} \end{array} \right.$$

$$v_x = -5.26 \text{ V}$$

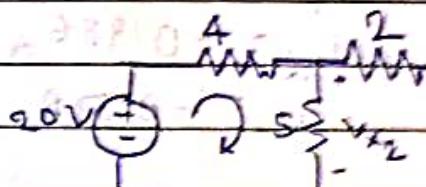


$$20 - 4i - 5(i - v_x) = 0$$

$$40 - 8i - 10i + 5v_x = 0$$

$$40 - 18i + 5v_x = 0 \quad \text{--- (1)}$$
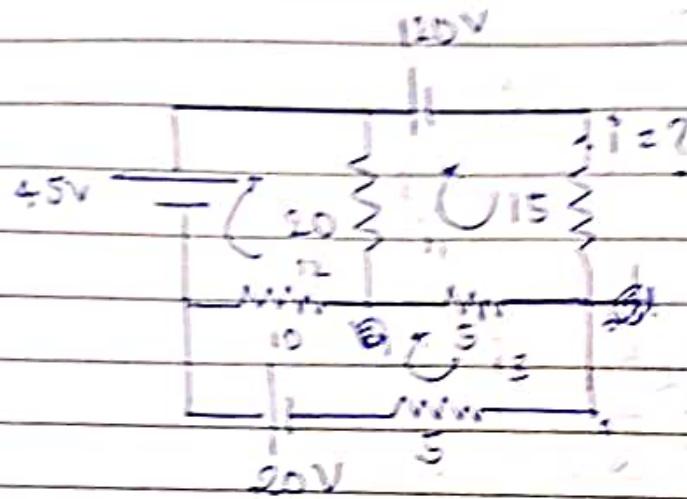
$$v_x = 5.26 \text{ V} \quad i = 2.68 \text{ A}$$



$$-120 - 15i_1 - 5(i_1 - i_3) - 20(i_1 - i_2) = 0$$

$$-120 - 15i_1 - 5i_1 + 5i_3 - 20i_1 + 20i_2 = 0$$

$$-40i_1 + 20i_2 + 5i_3 = 120 - 0$$

$$45 - 20(i_2 - i_1) - 10(i_2 - i_3) = 0$$

$$45 - 20i_2 + 20i_1 - 10i_2 + 10i_3 = 0$$

$$20i_1 - 30i_2 + 10i_3 = -45 - 0$$

$$20 - 10(i_3 - i_2) - 5(i_3 - i_1) - 5i_3 = 0$$



$$20 - 10i_3 + 10i_2 - 5i_3 + 5i_1 - 5i_3 = 0$$

$$5i_1 + 10i_2 - 20i_3 = -20 - 0$$

$$i_1 = 3.54 \text{ A}$$

$$i_2 = 0.985 \text{ A}$$

$$i_3 = 0.37 \text{ A}$$

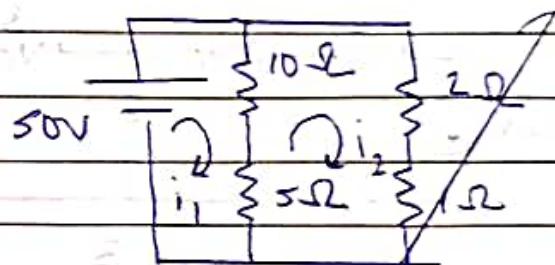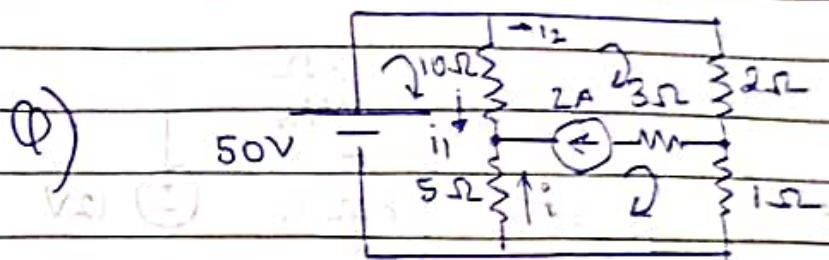

$$50 - 10(i_1 - i_2) - 5(i_1 - i_2) = 0$$

$$50 - 15i_1 + 15i_2 = 0$$

~~$$15i_1 - 3i_2 = 10 \quad \text{--- (1)}$$~~

$$50 - 10(i_1 - i_2) - 5(i_1 - i_3) = 0$$

~~$$50 - 10i_1 + 2i_2 - i_1 + i_3 = 0$$~~

~~$$-3i_1 + 2i_2 + i_3 = -10 \quad \text{--- (2)}$$~~

$$-10(i_2 - i_1) - 2i_2 - i_3 - 5(i_3 - i_1) = 0$$







~~$$-10i_2 + 10i_1 - 2i_2 - i_3 - 5i_3 + 5i_1 = 0$$~~







~~$$15i_1 - 12i_2 - 6i_3 = 0$$~~

$$i_2 = 2 + i_3$$

$$i_2 - i_3 = 2 \quad \text{--- (3)}$$

(4)

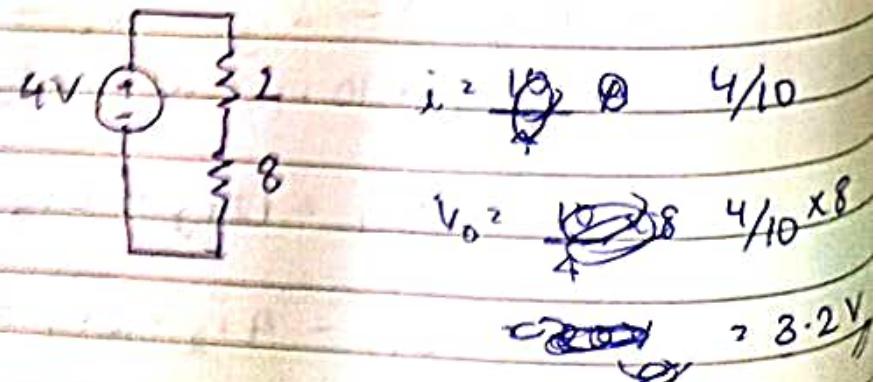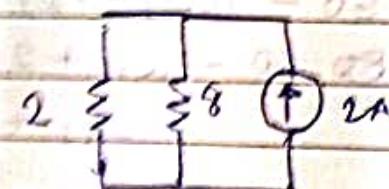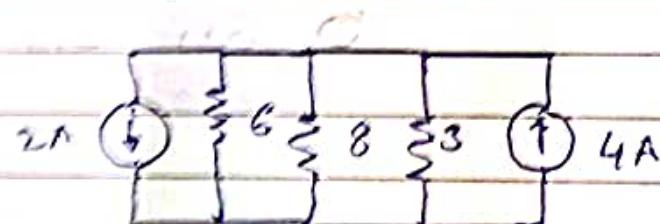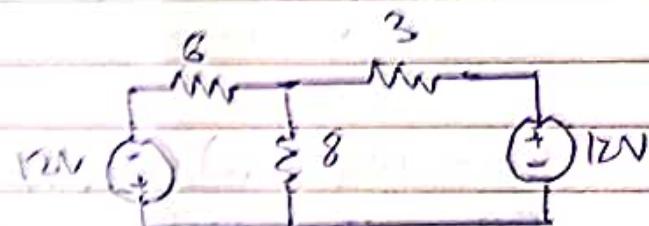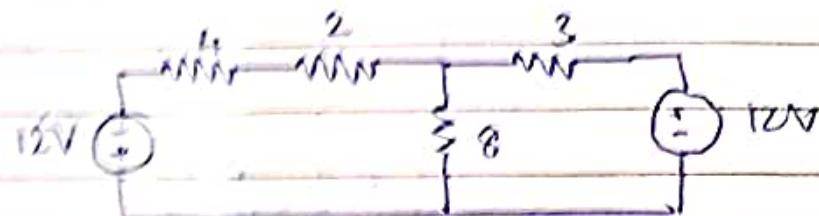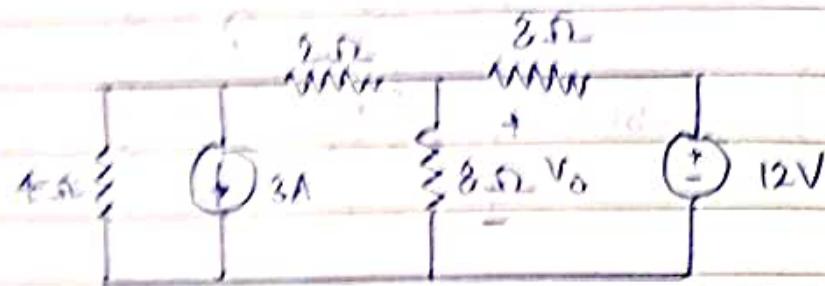


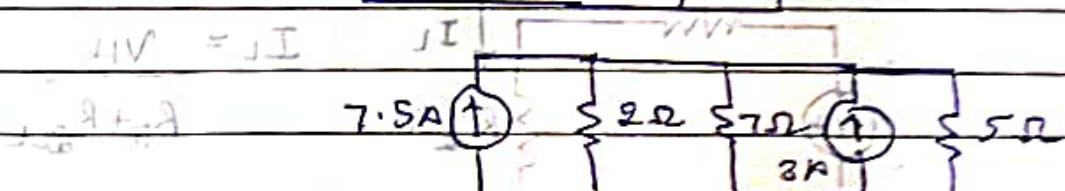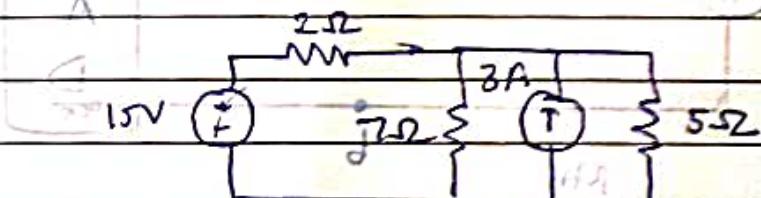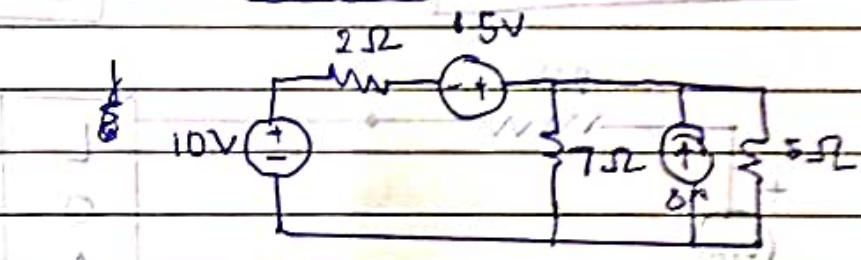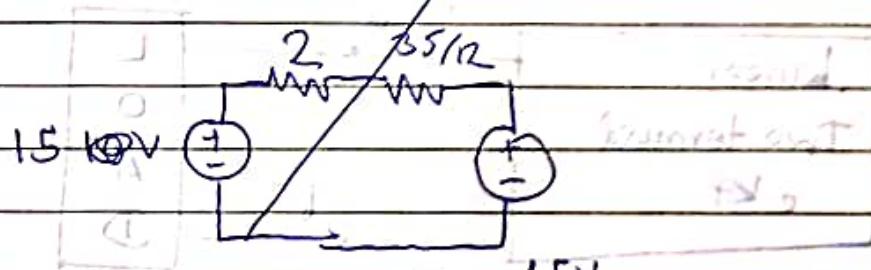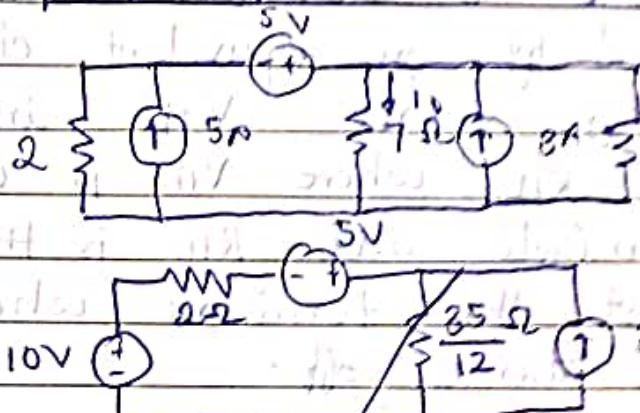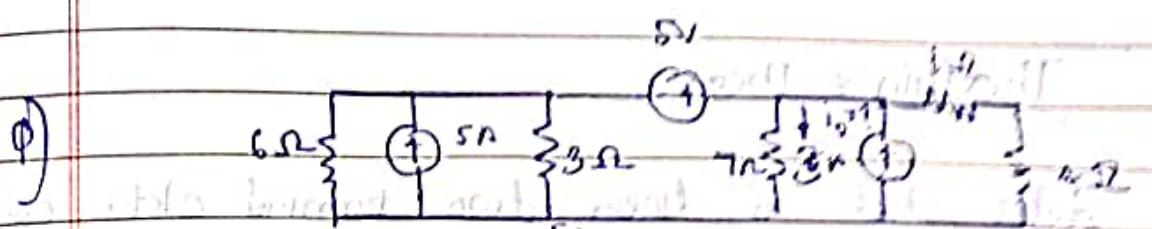

$$18.5 = 1V$$

$$19.5V = V_{10.5\Omega}$$

$$\frac{1.5}{R+10} = \frac{1}{10.5}$$

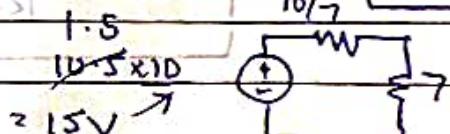




$$15 = (10/7 + 7)i$$

$$i = \frac{15 \times 10}{59}$$

$$= 1.77 A$$

Thevinin's Theorem

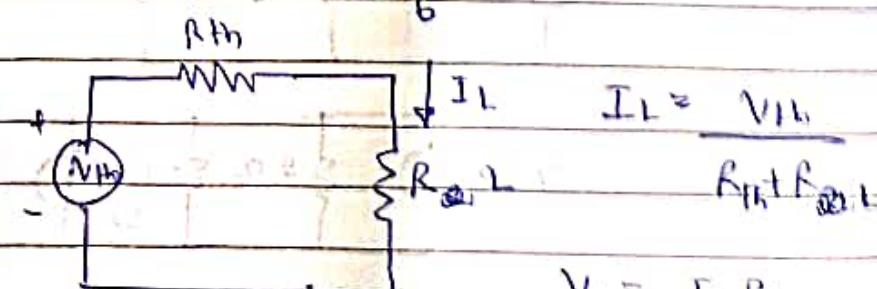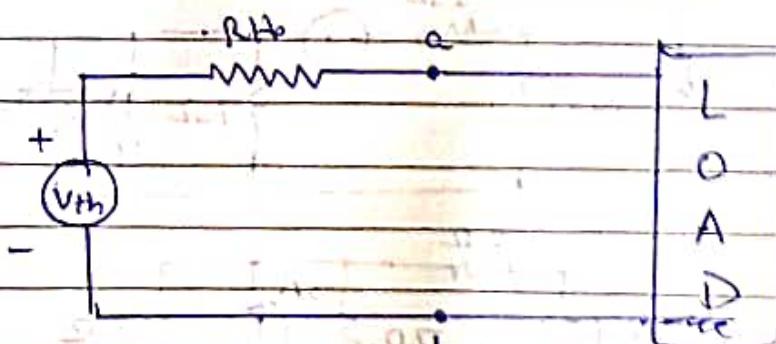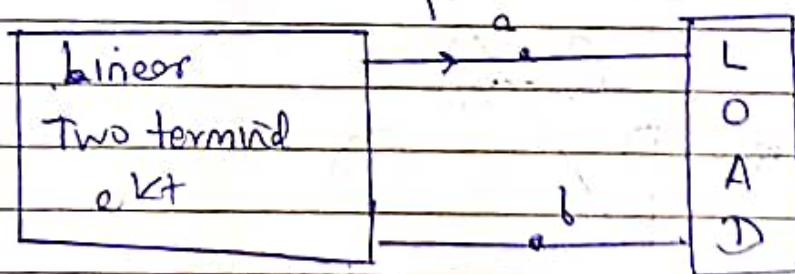
It states that a linear two terminal ckt. can be replaced by an equivalent circuit consisting of a voltage source V_{th} in series with a resistor R_{th} , where V_{th} is open ckt. voltage at the terminals and R_{th} is the equivalent resistance at the terminals when the independent sources are turned off.



$$V_L = I_L R_L$$


$$V_L = \frac{V_{th} R_L}{R_{th} + R_L}$$

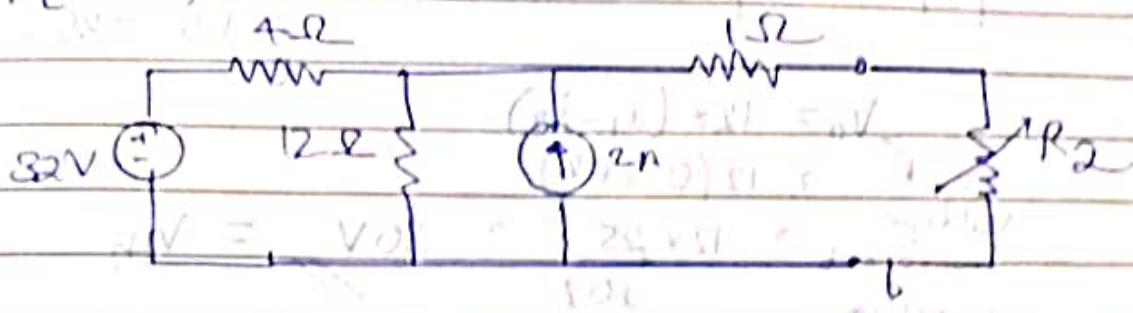- (Q1) Find the Thevenin's equivalent circuit to the left of the terminals a, b. Find current through R_L when $R_L = 6, 16 \text{ & } 36 \Omega$



Steps

- ① Calculate R_{Th}

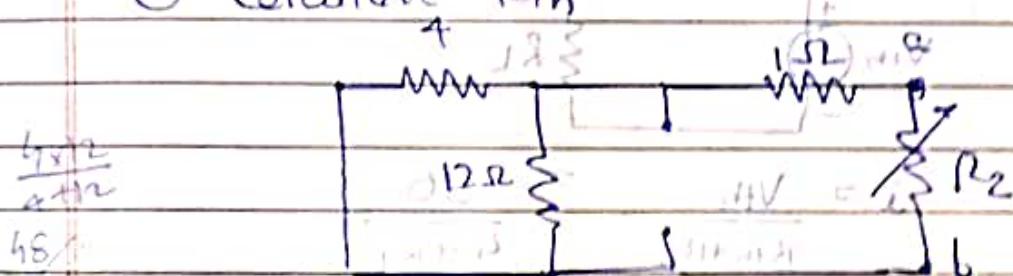


Turn off all sources & redraw circuit

$$R_{Th} = 4\Omega$$

From now to Step 2 Thévenin's Law (②)

- ② calculate V_{Th}

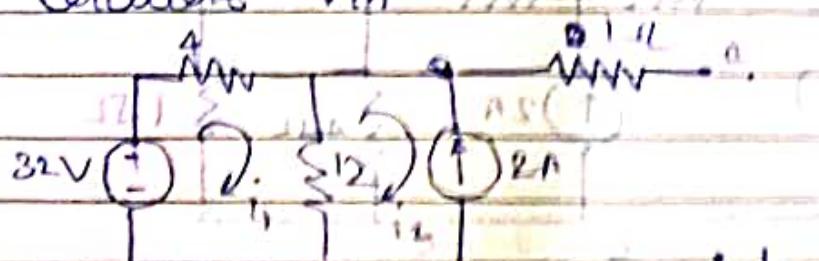

$$32 - 4i_1 - 12(i_1 - i_2) = 0$$

$$32 - 4i_1 - 12i_1 + 12i_2 = 0$$

$$\therefore 16i_1 - 12i_2 = 32$$

$$4i_1 - 3i_2 = 8 \quad \text{--- (1)}$$

$$i_2 = -2A$$

Alternatively use nodal analysis.

$$4i_1 + 6 = 8$$

$$[i_1 = 0.5A]$$


$$\frac{V_{Th} - 32}{4} + \frac{V_{Th} - 2}{12} = 0$$

$$\{ V_{Th} = 30V \}$$

$$V_o = 12 \times (i_1 - i_2)$$

$$\Rightarrow 12(0.5 + 2)$$


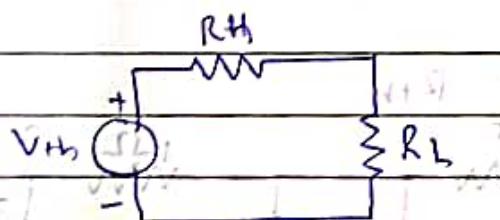
$$\begin{aligned} \text{Voltage across } a, b &= 12 \times \frac{25.5}{102} = 30V = V_{Th} \\ \text{is voltage across } 12\Omega. \end{aligned}$$



$$i = \frac{V_{Th}}{R_{Th} + R_L}$$


$$\left\{ \begin{array}{l} R_L = 6 \quad i = 10/3A \\ R_L = 16 \quad i = 3/2A \\ R_L = 36 \quad i = 3/4A \end{array} \right.$$

(Q) Find equivalent ckt and current?

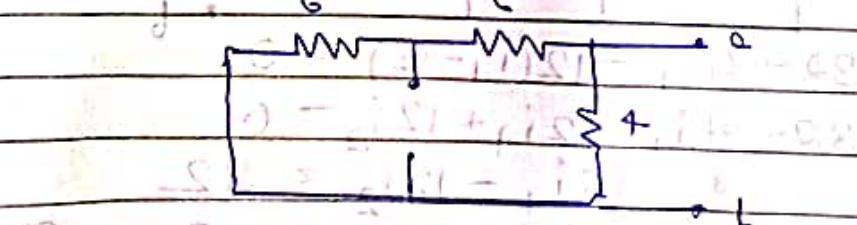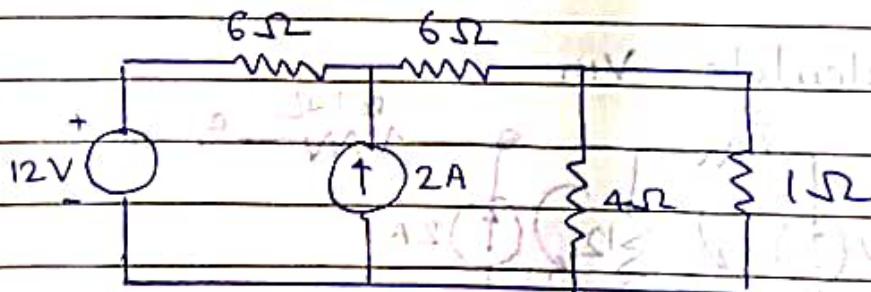


$$\textcircled{1} - 8 = 5i_8 - i_9$$

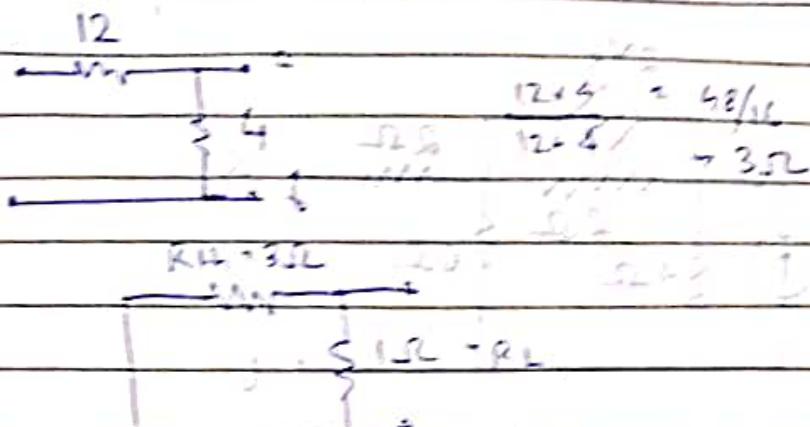→ 2nd diagram contains 3 parallel paths with voltage 0



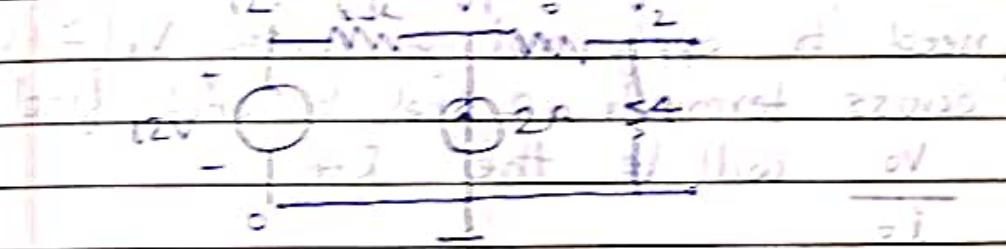→ 3rd diagram shows 2 parallel paths with voltage 0



→ 4th diagram contains 3 parallel paths with voltage 0

$$\frac{V_1 - 12}{2} + \frac{V_2}{2} = 0$$

$$2V_1 - 12 - V_2 + 12 = 0 \quad \Rightarrow \quad 2V_1 - V_2 = 0 \quad \text{--- (1)}$$

$$V_1 - V_1 + V_2 = 24 \quad \Rightarrow \quad V_2 = 24 \quad \text{--- (2)}$$

$$\frac{V_1 - V_2}{2} + \frac{V_2 - 24}{3} = 0$$

$$4V_2 - 4V_1 + 6V_2 = 0 \quad \Rightarrow \quad 10V_2 - 4V_1 = 0 \quad \text{--- (3)}$$

$$2V_2 - V_1 = 0 \quad \Rightarrow \quad V_1 = 2V_2 \quad \text{--- (4)}$$


$$0 = 5V_2 - V_2 - 24 - 12 - i \cdot 2 \quad \Rightarrow \quad i = \frac{36}{16} = 2.25 \text{ A}$$

$$V_2 = 6V \quad \Rightarrow \quad V_1 = 12V \quad \text{--- (5)}$$

$$V_2 = 6V \quad \Rightarrow \quad i = \frac{6}{3} = 2 \text{ A}$$

~~$$V_2 = 6V \quad \Rightarrow \quad i = \frac{6}{3} = 2 \text{ A}$$~~

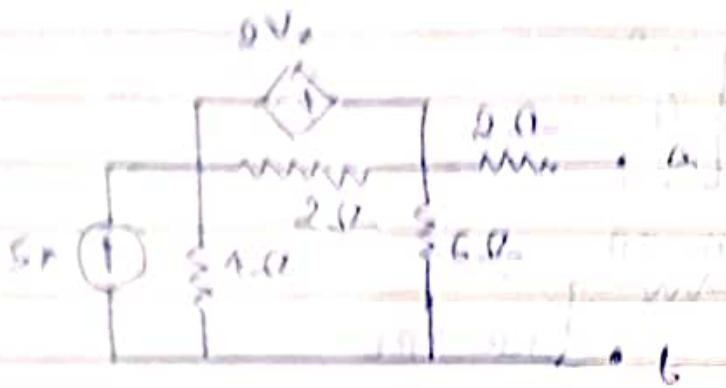Q) Find the Thevenin's theorem equivalent circuit.




In dependent sources to find R_{th} we need to apply voltage source v_o ($\approx 1V$) across terminals a and b and find v_o / i_o will be the R_{th} :

$$i_o$$

Assume current flowing b/w terminals a and b is i_o then $R_{th} = v_o / i_o = 1 / 2\Omega$

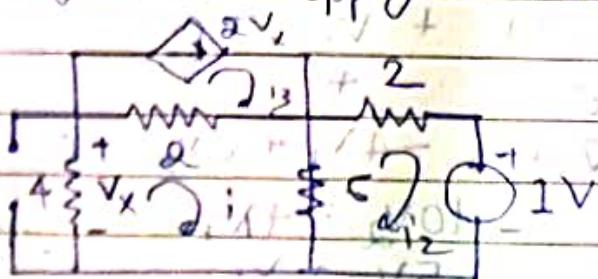Alternatively we will assume 1A current source to find the corresponding voltage v_o and apply $R_{th} = v_o / 1$.





$$-4i_1 - 2(i_3 - i_1) - 6(i_1 - i_2) = 0 \quad \text{--- (1)}$$

$$2v_x - 2(i_3 - i_1) = 0 \quad \text{--- (2)}$$


$$-2i_2 - 1 - 6(i_2 - i_1) = 0 \quad \text{--- (3)}$$

$$4i_1 - 2v_x = 0 \quad \text{--- (4)}$$

Youtube

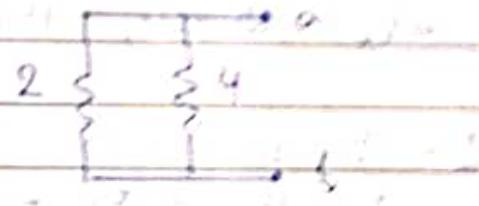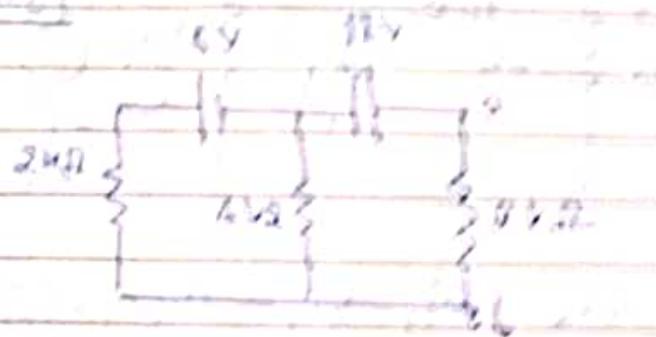

$$V_{12} = 12V - 2 \cdot 2\Omega = 8V$$

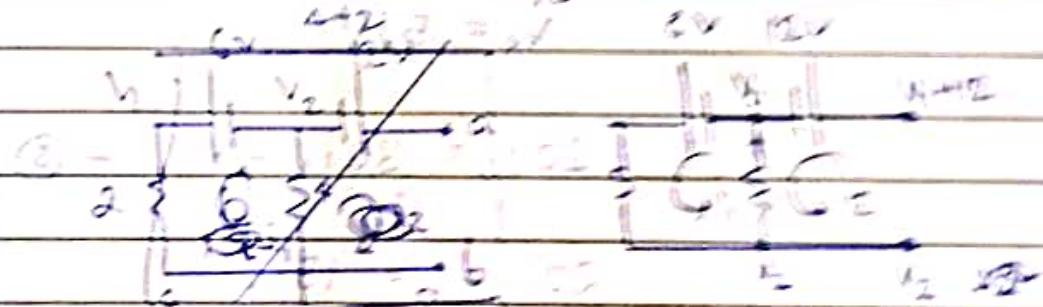

$$V_1 = 12V - 2 \cdot 2\Omega = 8V$$


$$\begin{aligned} V_1 &= 12V - 2 \cdot 2\Omega \\ &= 12V - 4V \\ &= 8V \end{aligned}$$

$$\begin{aligned} E &= 2 \cdot 12V - 4V \\ V_{AB} &= 8V \end{aligned}$$

$$\begin{aligned} i &= \frac{V_{AB}}{R_{AB}} \\ &= \frac{8V}{10\Omega + 3\Omega} \\ &= \frac{8V}{13\Omega} \end{aligned}$$

$$i = \frac{8V}{13\Omega} = \frac{8}{13}A = 0.615A$$
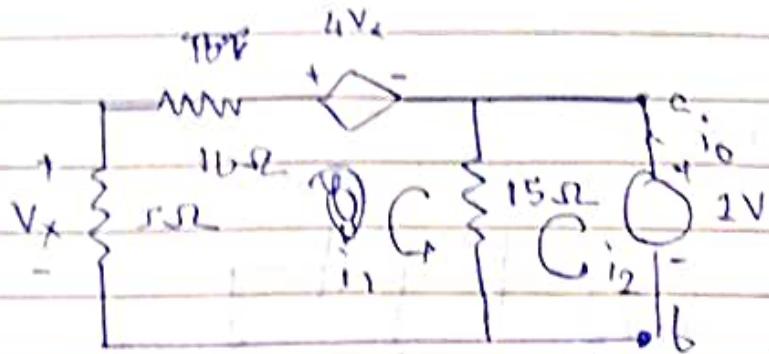
$$P = i^2 R = \left(\frac{8}{13}\right)^2 \cdot 10\Omega = \frac{64}{169} \cdot 10\Omega = 3.84W$$



$$4V_x - 10i_1 - 5i_1 - 15(i_1 - i_2) = 0$$

$$4V_x - 15i_1 - 15i_1 + 15i_2 = 0$$

$$4V_x = 30i_1 - 15i_2 \quad \text{--- (1)}$$

$$1 - 15(i_2 - i_1) = 0$$

$$1 = 15i_2 - 15i_1 \quad \text{--- (2)}$$

$$V_x = 5i_1$$

$$20i_1 = 30i_1 - 15i_2 \quad \text{--- (3)}$$

$$20i_1 + 1 = 15i_1$$

$$\frac{-1}{5} = i_1 = 2 - 0.2A$$

$$V_x = 1V$$

i(1)

$$1 = 15i_2 - (-3)$$

$$i_2 = \frac{1+3}{15} = \frac{-2}{15}A$$

$$i_0 = i_2 = -\frac{2}{15}A$$


$$R_{Th} = -\frac{15}{2}$$

$$= 7.5\Omega$$

Since no independent source

$$V_{Th} = 0$$

8

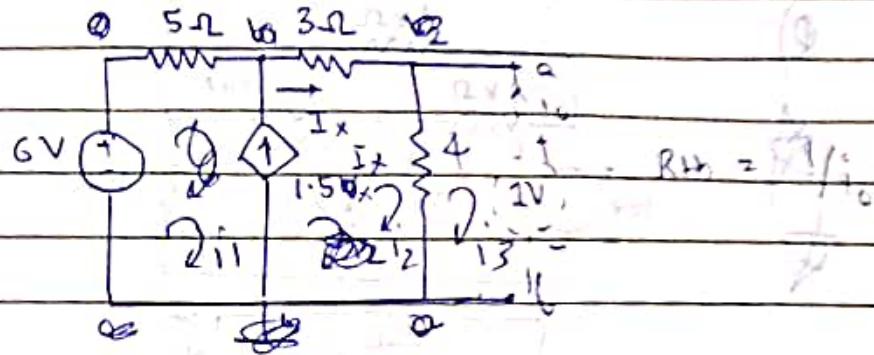

$$6 - 5i_1 - 3i_2 - 4(i_2 - i_3) = 0$$

$$6 - 5i_1 - 3i_2 - 4i_2 + 4i_3 = 0$$

$$5i_1 + 7i_2 - 4i_3 = 6 \quad \text{--- (1)}$$

$$-5 + 4 - 4i_3 = c \quad -1 - 4(i_3 - i_2) = 0$$

$$4i_2 - 4i_3 = 1 \quad \text{--- (2)}$$

$$-5 + 14 - 4x_3 \geq 15 \quad i_2 = i_1 - ③$$

$$-4i_3 = 9/11 - 14$$

$$13^2/314 A^5 \Rightarrow i_1 + 1.5 i_2 = i_3$$

$$2i_1 = -\cancel{2}i_2 - ④$$

$$R_{Th} = 4.3 \Omega$$

$$5i_1 + 7(-2i_1) - 4i_3 = 6$$

$$5i_1 - 14i_2 - 4i_3 \geq 6$$

12 4

$$\frac{1}{4} = i_1 - i_2 \quad \text{so} \quad -13i_1 - 4i_2 = 5$$

$$\frac{1}{4}z^2 - 2 + 13i - 4(-2i) = 5$$

$$-13i + 8i = 5$$




$$i_3 = 9/4 \text{ A}$$

$i_1 = -1 \mu$

$$i_{S2} = 2A$$

$$= 4 \cdot \underline{\downarrow} z = (-5 + 14) \cdot \underline{\downarrow} z$$

(1)

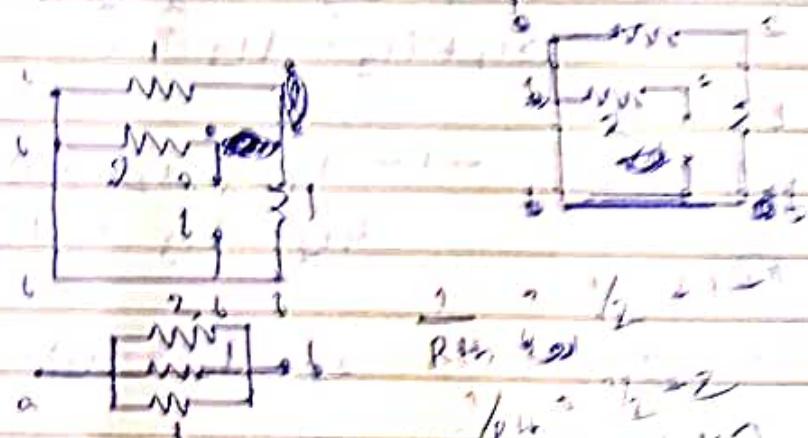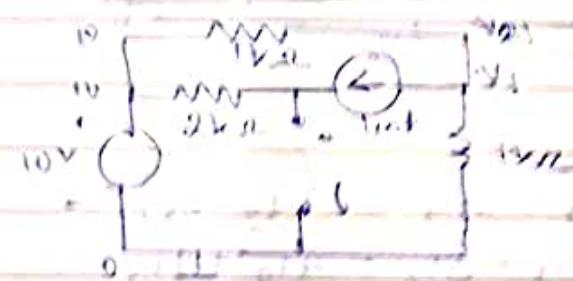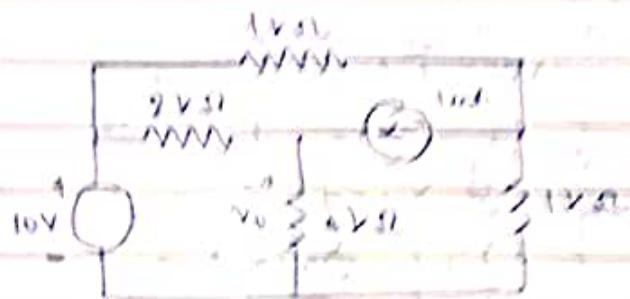

$$\text{Ans} 10 \rightarrow N_1 = (10^3) 2 \times 10^3$$

$\text{Ans} [V_1 = 8 \text{ V}]$



$$N_{ab} = 2 - 10 \cdot 0$$

$$V_{ab} = 12 \text{ V} - V_m$$

$$12 - i_1 - i_2 - 12 = 312 = 312$$

$$V_m = 4 \times \frac{2}{2+2}$$

$$= 2 \text{ V}$$

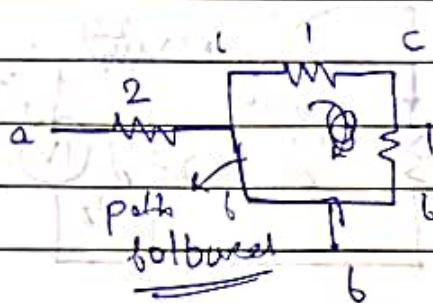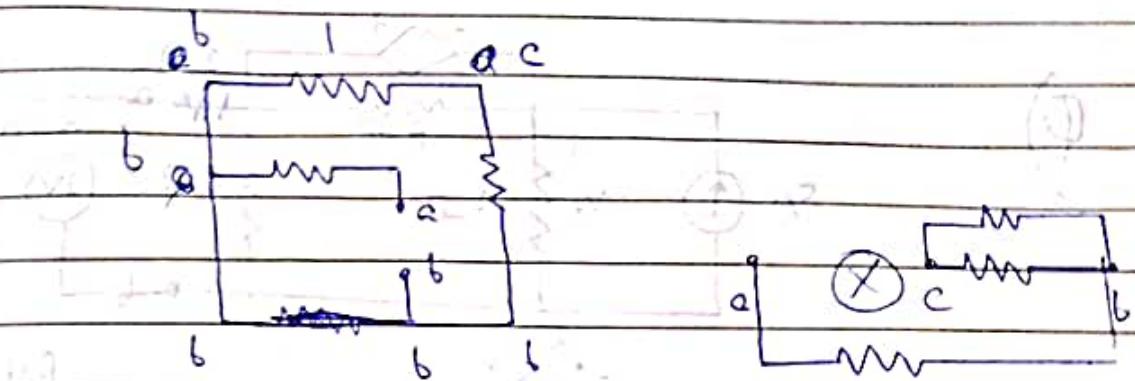


$$\textcircled{1} \rightarrow O = (i_1 - i_2) \rightarrow R_{Th} = 2\Omega$$

$$V_o = i_2 + i_3 - i_4 + i_5 - i_6 - i_7 -$$

IMP points

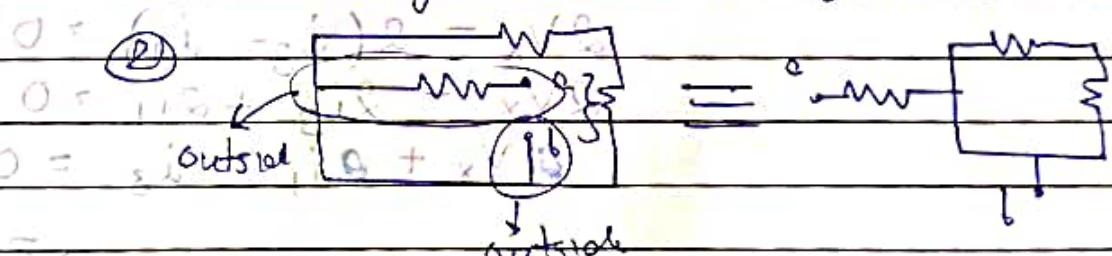(1) → O = i_1 (1) Current Sources are short open ckt
Voltage Sources are short ckt



$$\textcircled{2} \rightarrow O = (i_1 - i_2)$$

(3) Use short ckt path (if exists) in

$$(4) \rightarrow I = \frac{R_{Th}}{2} - i_2$$

$$(5) \rightarrow v_o = i_2 - \textcircled{2}$$


also, i

also, o = i

also, o = i

also, o = i

(P)

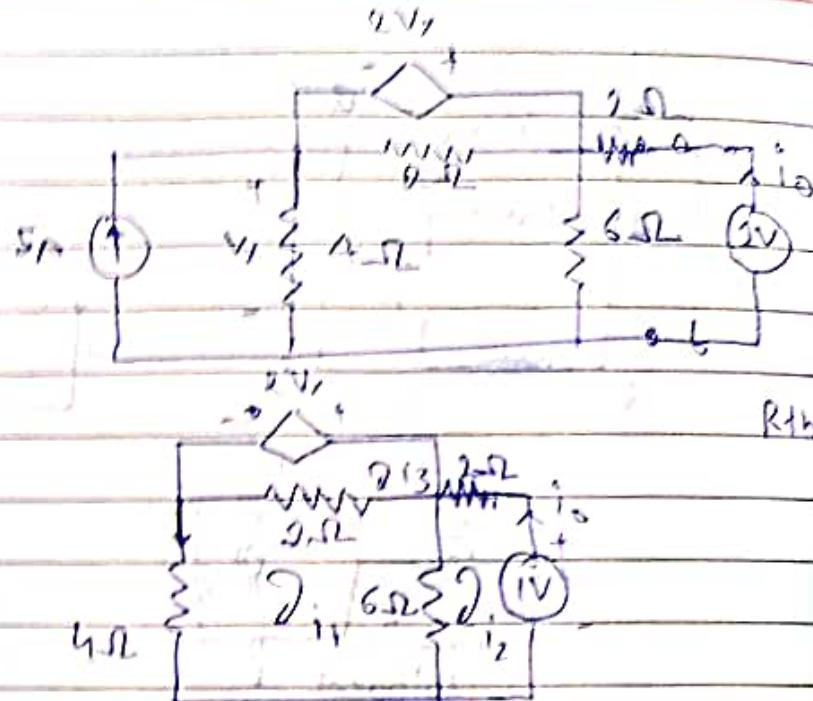

$$\begin{aligned}-4i_1 - 2(i_1 - i_3) - 6(i_2 - i_1) &= 0 \\ -4i_1 - 2i_1 + 2i_3 - 6i_1 + 6i_2 &= 0\end{aligned}$$

$$6i_2 - 12i_1 + 2i_3 = 0$$

$$3i_2 - 46i_1 + i_3 = 0 \quad \text{--- (1)}$$

$$2V_x - 2(i_3 - i_1) = 0$$

$$2V_x - 2i_3 + 2i_1 = 0$$

$$2V_x + 2i_1 - i_3 = 0 \quad \text{--- (2)}$$

$$-2i_2 - 1 - 6(i_2 - i_1) = 0 \quad \text{--- (3)}$$

$$-2i_2 - 1 - 6i_2 + 6i_1 = 0$$

$$6i_1 - 8i_2 = 1 \quad \text{--- (3)}$$

$$-4i_2 = V_x \quad \text{--- (4)}$$

$$i_1 = 0.02A$$

$$i_2 = -0.108A$$

$$i_3 = 0.45A$$

~~$$i_1 = 0.02A$$~~

$$V_x = 0.43V$$

$$i_1 = 0.02A$$


$$i_2 = -0.108A$$

$$i_3 = 0.45A$$

$$i_0 = -i_2 \quad \text{at node } A \quad (1)$$

$\rightarrow 10.67 \text{ A}$

$$R_{Th} = \frac{V_0}{i_0} = G \cdot R$$

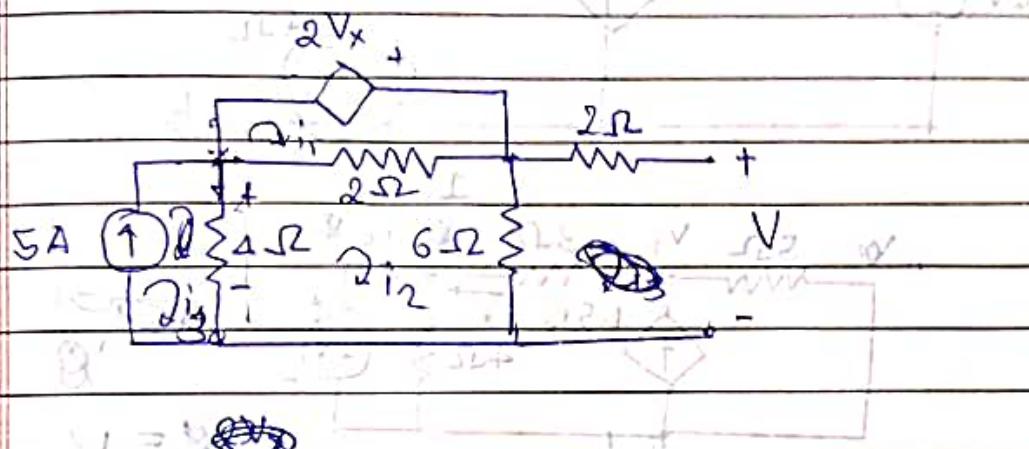

$$2V_x + i_2 - i_1 = 0 \quad (1)$$

~~$4(i_2 - i_3) = V_x$~~

~~$-2(i_2 - i_1) - 6i_2 - 4(i_2 - i_3) = 0$~~

~~$4i_1 - 2i_2 + 2i_1 - 6i_2 - 4i_2 + 4i_3 = 0$~~

~~$2i_1 - 12i_2 + 4i_3 = 0$~~

~~$i_1 - 6i_2 + 2i_3 = 0 \quad (2)$~~

~~$i_1 = i_2 - i_3, V = 0$~~

~~$5 = i_3 + (i_2 - i_1)$~~

~~$5 = i_3 - i_2 + i_2 - i_1 + i_1$~~

~~$V_x = 4 \text{ V}$~~

~~$V_x + (i_2 - i_3)4 = 0$~~

~~$V_x = (i_3 - i_2) +$~~

~~$V_x = 20 - 4i_2$~~

~~(5)~~

$$i_1 - 6i_2 + 10 = 0$$



$$6i_2 - i_1 = 10 \quad (4)$$

$$V_m = 6i_2 \cdot 2 = \frac{6 \times 10}{3} = 20 \text{ V}$$

$$\left\{ \begin{array}{l} i_1 = 10 \text{ A} \\ i_2 = 10/3 \text{ A} \\ (1) V_x = 20/3 \text{ V} \end{array} \right.$$

(q)

Find Thevenin's equivalent ckt

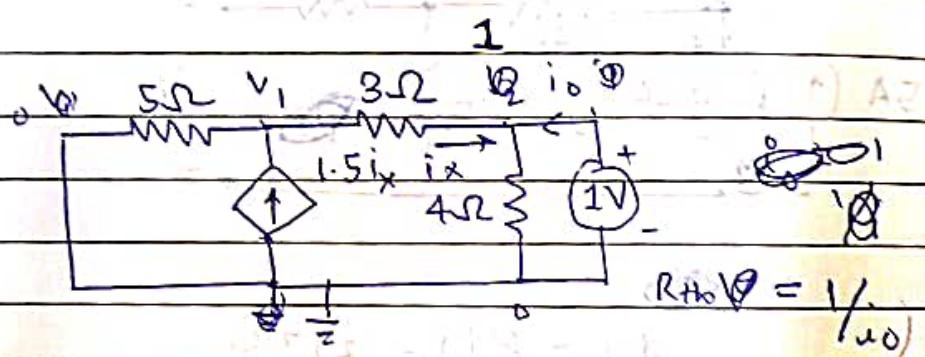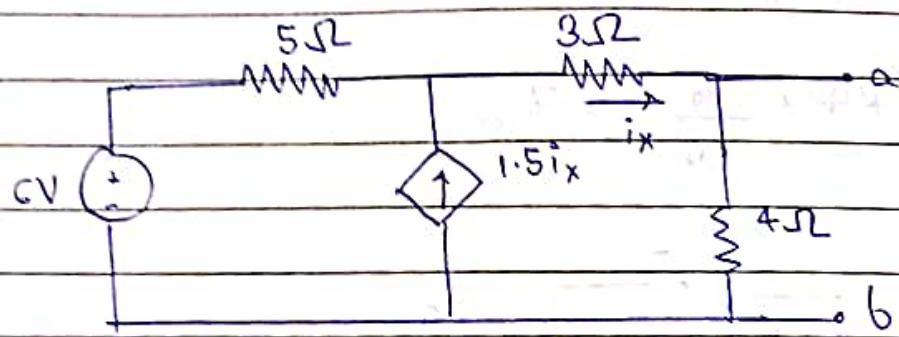

$$\frac{V_1}{5} - 1.5i_x + \frac{V_1 - V_2}{3} = 0$$

$$V_1 - 1.5i_x + \frac{V_1 - V_2}{3} = 0$$

$$V_2 = V_1 - 1.5i_x$$

$$3V_1 - 22.5i_x + 5V_1 - 5i_x = 0$$

$$0 - \frac{V_1 - 1}{3} = i_x$$

$$8V_1 - 22.5i_x = 0$$


$$V_1 - 1 = 3i_x$$

$$V_1 - 3i_x = 1$$

$$R_{Th} = 1$$

$$i_x = -2A$$

$$V_1 = 7V$$

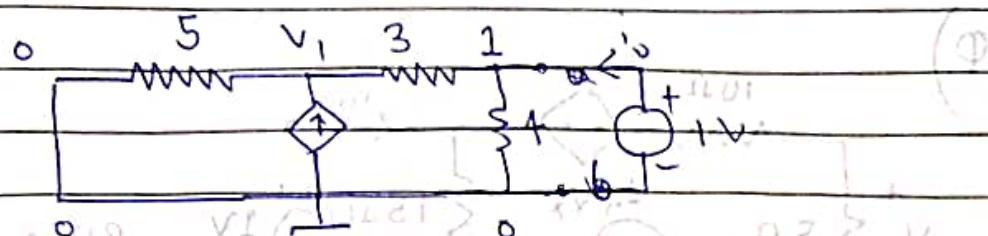

$$\frac{V_1}{5} + \frac{V_1 - 1}{3} + -\frac{10}{2} 3 i_x = 0$$

$$0 = (6V_1 + 10V_1 - 10 - 45i_x) = 0$$

$$0 = 12V_1 + 10V_1 - 10 - 45i_x = 0$$

$$16V_1 - 45i_x = 10 \quad \text{--- (1)}$$

$$(1) \rightarrow 0 = 12V_1 + 10V_1 - 45i_x = 0$$

$$\frac{V_1 - 1}{3} = i_x$$

$$0 = (i_1 - i_2)2 - 1$$

$$(2) \rightarrow V_1 = 12 - 3i_x - 12i_2$$

$$V_1 - 3i_x = 0 \quad \text{--- (2)}$$

$$(2) \rightarrow i_2 = V_1$$

$$V_1 = 5V$$

$$5 = 12 - 3i_x - 12i_2 \quad \left\{ \begin{array}{l} i_x = -2A \\ i_2 = 5A \end{array} \right.$$

$$5 = R_{TH} \cdot 5 \quad i_0 = -1 \times 1 - 2A$$

$$R_{TH} = \frac{V_1}{i_0} = \frac{5}{-1} = 5 \Omega$$

2000 वोल्ट में तब लोडमत ऑफ रेसिन A


0 वोल्ट बनाए रखा तब लोडमत ऑफ रेसिन B

तब लोडमत ऑफ रेसिन C बनाए रखा तब लोडमत ऑफ रेसिन D

तब लोडमत ऑफ रेसिन E बनाए रखा तब लोडमत ऑफ रेसिन F

तब लोडमत ऑफ रेसिन G बनाए रखा तब लोडमत ऑफ रेसिन H

(P)

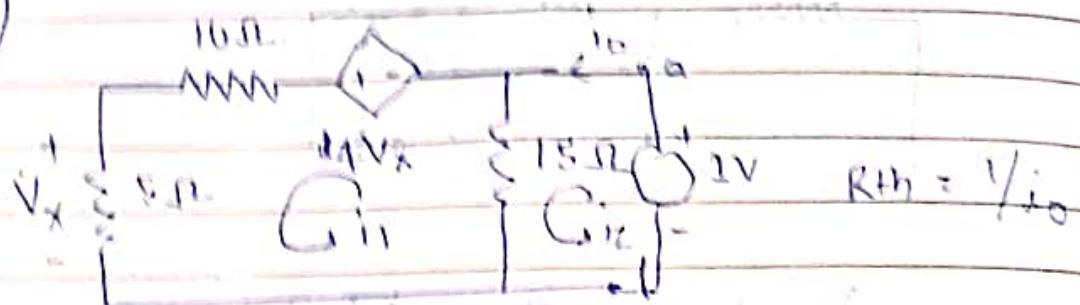

$$4V_x - 10i_1 - 5i_1 - 15(i_1 - i_2) = 0$$

$$4V_x - 15i_1 - 15i_1 + 15i_2 = 0$$

$$4V_x - 30i_1 + 15i_2 = 0 \quad \text{--- (1)}$$

$$1 - 15(i_2 - i_1) = 0$$

$$15i_{12} - 15i_2 + 1 = 0 \quad \text{--- (2)}$$

$$-5i_1 + V_x = 0$$


$$V_x = 5i_1 \quad \text{--- (3)}$$

$$\left\{ \begin{array}{l} i_1 = 0.2A \\ i_2 = 0.133A \\ V_x = 1V \end{array} \right\} \quad \left\{ \begin{array}{l} R_{TH} = 7.5 \Omega \\ V_{TH} = 0 \end{array} \right\}$$

Norton's Theorem

A linear two terminal ckt can be replaced by an equivalent ckt consisting of a current source I_{DN} in parallel with a resistor R_N . Where I_{DN} is the short ckt current through the terminals and R_N is the equivalent resistance.

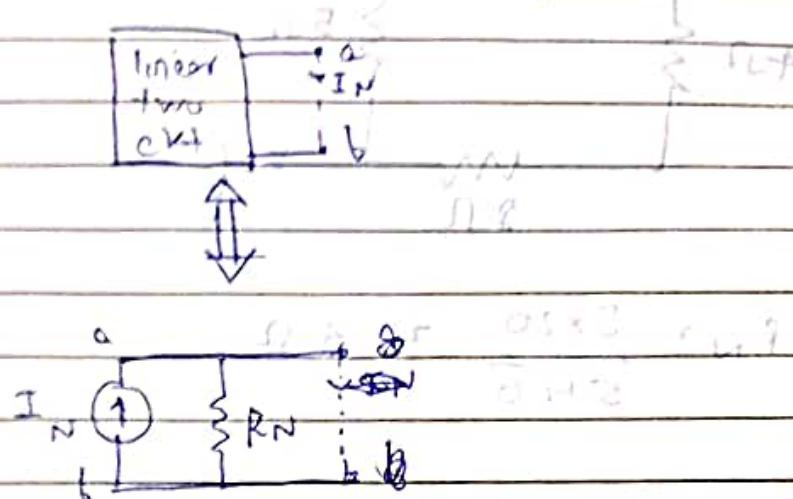at terminals when the independent sources are turned off:



Steps


(1) R_N is same as R_{Th} .


(2) I_N is calculated by short circuiting the terminals a and b.

Note (i) The short ckt current I_N is same as Norton's current.


(ii) We can apply source transformation b/w Norton & Thevenin ckt.

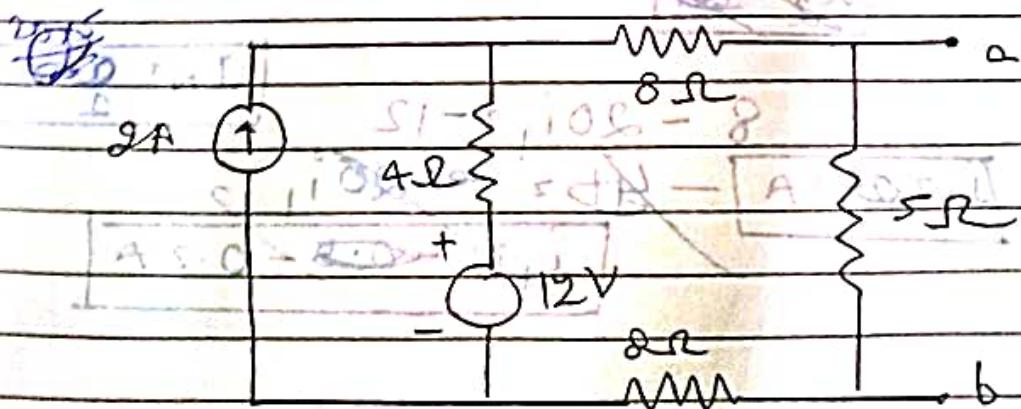(iii) Final Norton's equivalent ckt for -



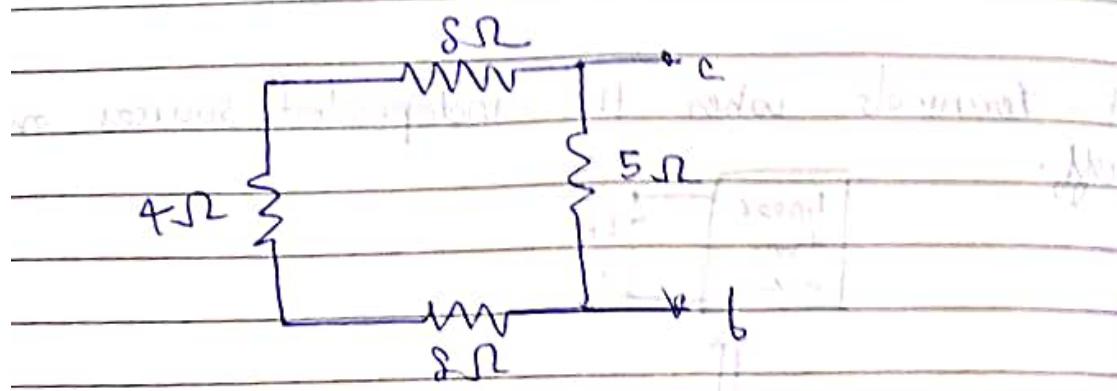
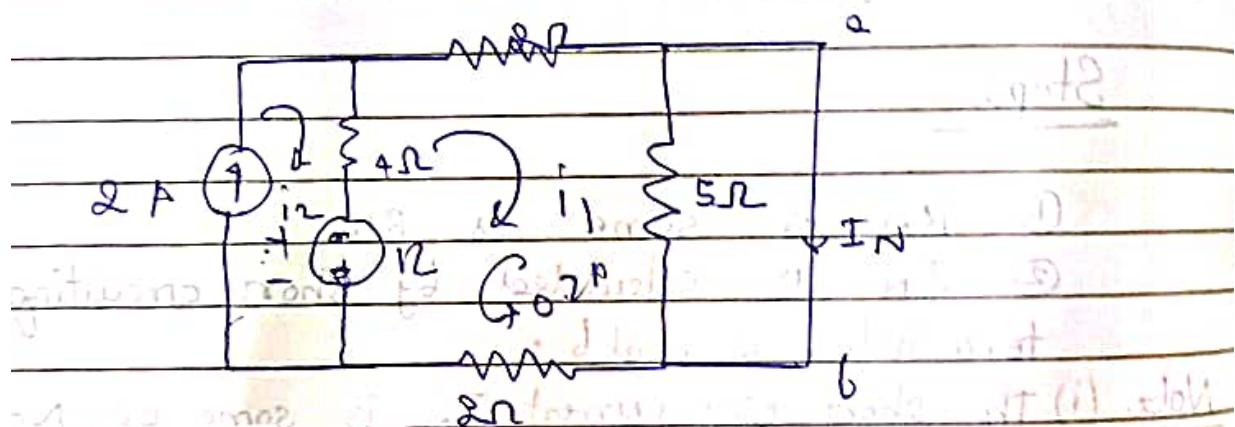
$$R_N = \frac{5 \times 2}{5 + 2} = 4\Omega$$



$$12 - 8i_1 - 8i_2 - 4(i_1 - i_2) = 0$$

$$-16i_1 - 4i_1 + 4i_2 = 12$$

$$4i_2 - 20i_1 = 12$$

~~i₂~~

$$IN = \frac{12}{2} A$$


$$8 - 20i_1 = 12$$

$$i_1 = 0.1 A$$

$$i_2 = 0.3 - 0.2 A$$

Alternative Method

using Thvenin's Voltage

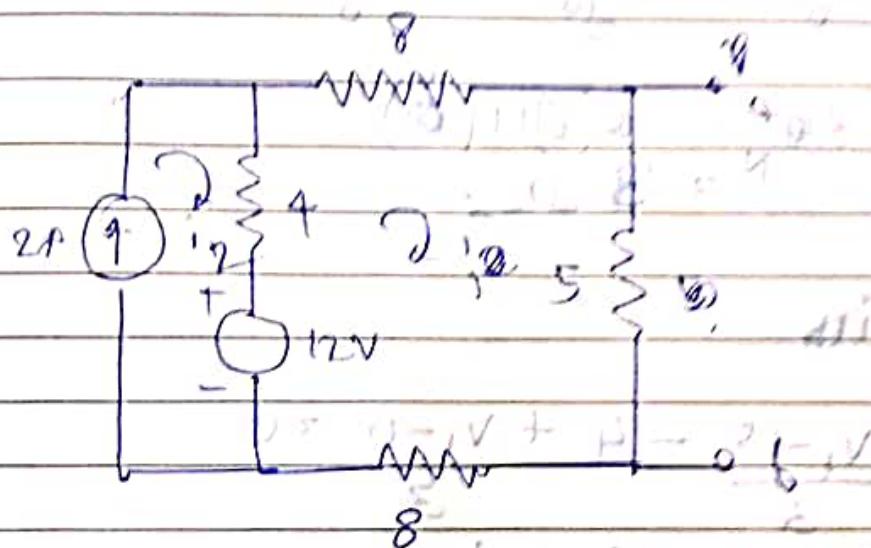

$$12 - 4(i_1 - i_2) - 8i_1 - 5i_1 - 8i_1 = 0$$

$$12 - 4i_1 + 4i_2 = 12i_1 / 20$$

$$12 = 25i_1 - 4i_2 \quad \text{--- (1)}$$

$$\{i_2 = 2A\} \Rightarrow i_2 = \frac{1}{2} A$$

$$12 = 25i_1 + 8$$

$$i_1 = \frac{20}{25} A$$


$$V_{Th} = \frac{20}{25} \times 5$$

$$= 4V$$

$$f_A = \frac{V_{Th}}{R_{load}} = \frac{4}{4} = 1A$$

$$f_A = 1A \quad 0 = 0 + 0 -$$

$$f_A = 1A \quad 0 = 0 + 0 -$$

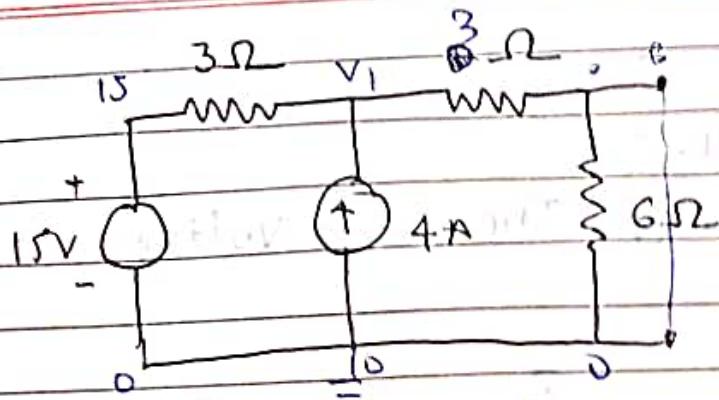

$$R_{TH} = 0(6) \parallel 10\Omega$$

$$N = 3\Omega$$

i1

$$\frac{V_1 - 15}{3} - 4 + \frac{V_1 - 0}{3} = 0$$


$$2V_1 - 15 = 4$$

$$2V_1 = 19$$

$$V_1 = 9.5$$

$$i_N = \frac{V_1}{3} = \frac{9.5}{3} = 4.5A$$

$$\{i_{10}, N = 84.5A\}$$

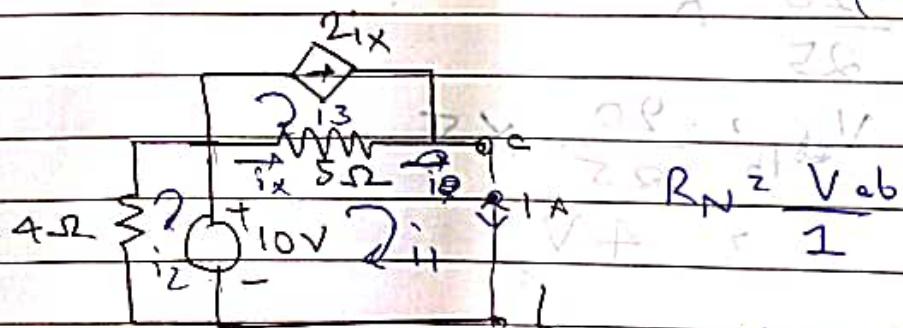

$$(1 - \frac{i_3}{i_2})^5$$

$$A = 0.5$$

$$Z_B = 2\Omega$$

$$Z_A = 1\Omega$$

$$R_N = V_{ab} = 1$$

$$\{i_x = 0.13A\}$$

$$10 - 5(i_1 - i_3) = 0$$



$$-10 - 4i_2 = 0$$

$$i_1 - i_2 = i_x$$


$$\{i_1 = 3i_x\}$$

$$i_3 = 2i_x$$

$$\{i_1 = 1A\}$$

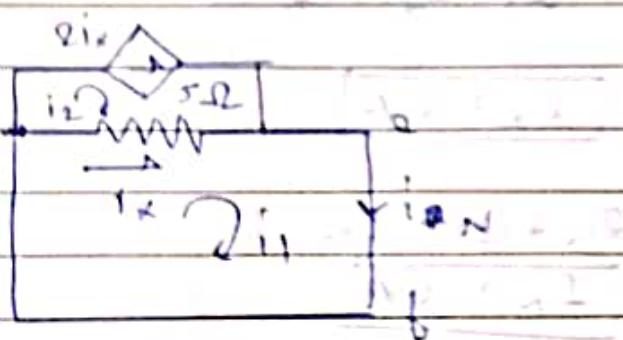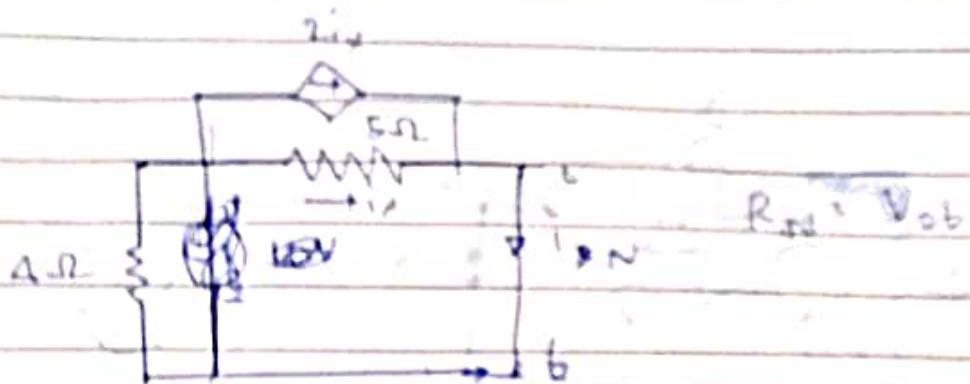

$$Q \rightarrow i_N = 3i_x$$

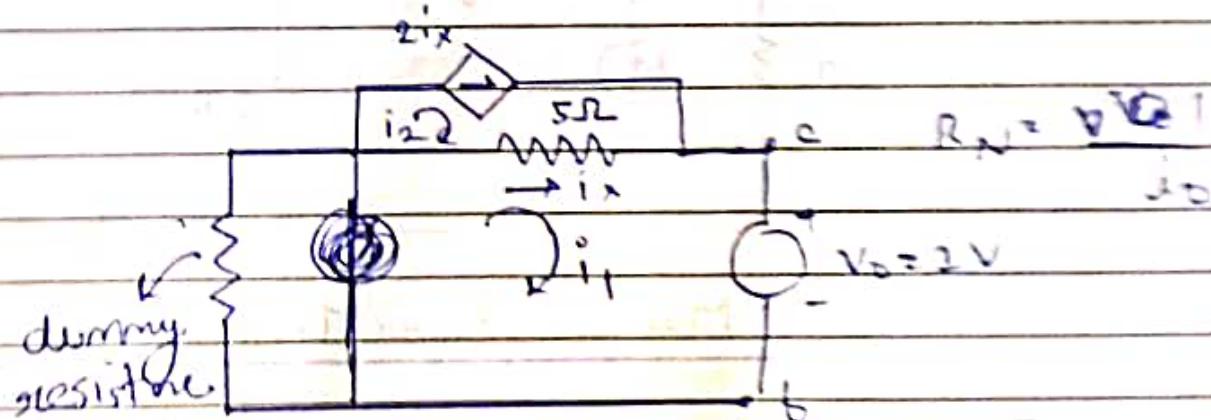

all at load point i_1 is zero

$$\text{loop } 1: i_1 - i_2 + 2i_x - 1 - 5(i_1 + i_2) = 0$$

$$\text{loop } 2: 2i_x - 5(i_2 - i_1) = 0$$

$$i_2 = 2i_x$$

$$i_1 - i_2 = i_x$$


$$i_1 = 3i_x$$

$$i_x = 3i_x = 0.5A$$

$$1 = 5i_x$$

$$\{ i_x = 0.2A \}$$

$$R_N = \frac{10}{83} = 1.6\Omega$$

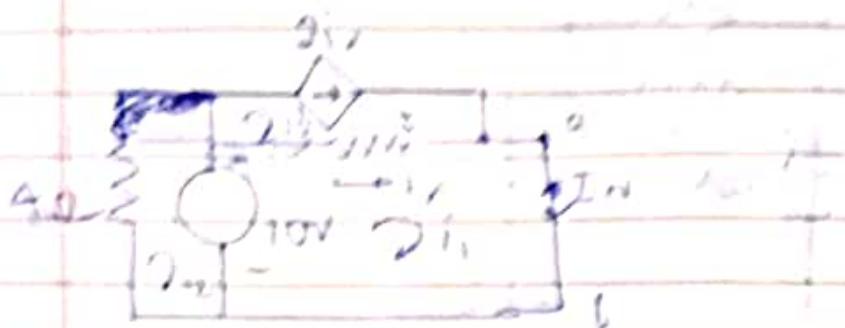


$$\therefore 10 - 5(i_1 - i_2) = 0$$

$$i_1 = i_2 + i_N$$

$$i_1 = 2A$$


$$2i_1 + i_N = i_N$$

$$i_N = 6A$$

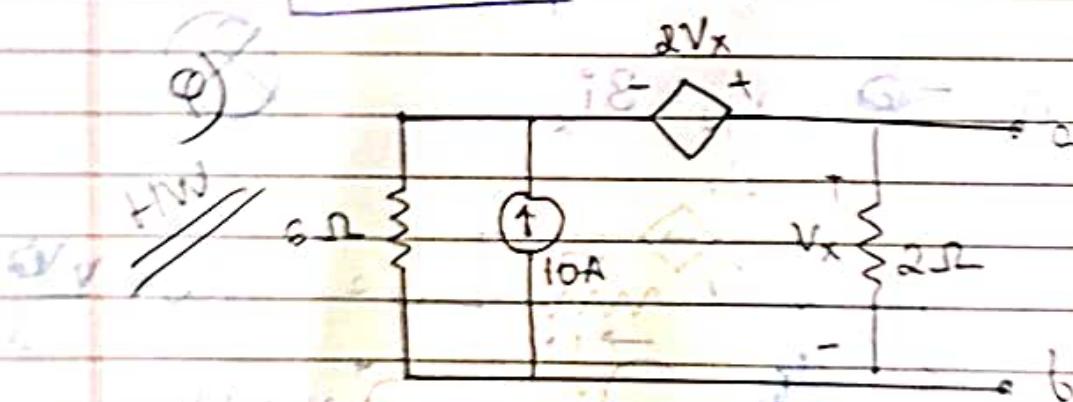

Maximum Power Transfer Theorem

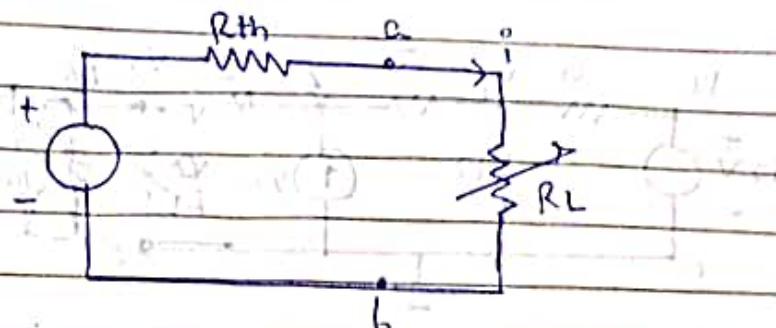The maximum power is transferred to the load when load resistance is equal to source resistance as seen from the load.



$$P = i^2 R$$

$$\left(\frac{V_{th}}{R_{th} + R_L} \right)^2 \cdot R_L \cdot \frac{\partial P}{\partial R} = V_{th} \left[(R_{th} + R_2)^2 - 2R_2(R_{th} + R_2) \right]$$

$$0 = V_{th}^2 - V_{th} \cdot V_{th} \cdot (R_{th} + R_2)^2$$

$$0 = V_{th}^2 - V_{th} \cdot V_{th}$$


$$V_{th} \left[R_{th} + R_2 - 2R_L \right] = 0$$

~~$$0 = V_{th}^2 - V_{th} \cdot R_{th} = R_L - V_{th}$$~~

~~$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$~~

~~$$0 = V_{th}^2 - V_{th} \cdot V_{th}$$~~

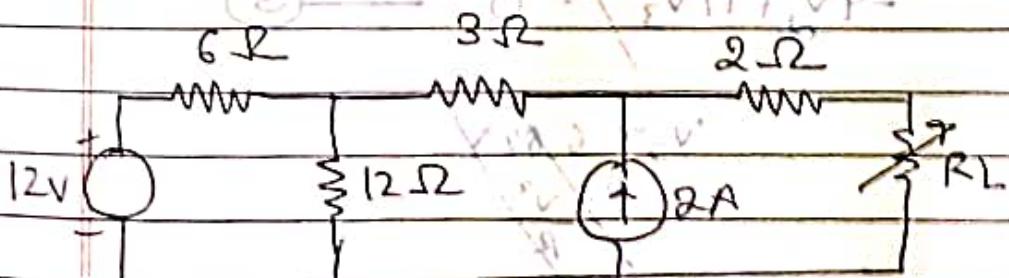
1) Find the R_2 for max power transfer in a circuit
Also calculate max. power.



$$R_{th} = \frac{6 \times 12}{6 + 12} + 5 = \frac{14V}{18} = \frac{7V}{9}$$

$$= \frac{2}{4+5} \cdot \frac{14V}{9} = \frac{14V}{45}$$

$$= 9\Omega = R_L$$

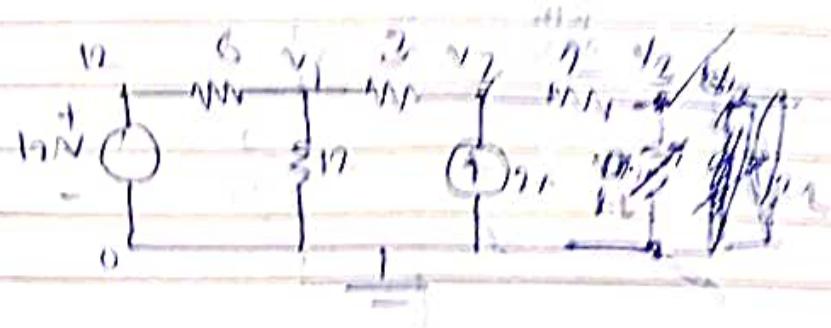

$$\frac{V_1 - 12}{6} + \frac{V_1}{12} + \frac{4V_1 - V_2}{3} + 0 = 0$$

$$2V_1 - 24 + V_1 + 4V_1 - V_2 + 0 = 0$$

$$7V_1 - V_2 = 24 \quad \textcircled{1}$$

$$\frac{V_2 - V_1}{3} + 0 + \frac{V_2 - V_3}{2} + 0 = 0$$

$$2V_2 - 2V_1 - 12 + 3V_2 - 3V_3 = 0$$

~~5V2 - 3V1~~

$$-2V_1 + 5V_2 + 3V_3 = 12 \quad \textcircled{2}$$

$$\frac{V_3 - V_2}{3} + \frac{V_2}{2} + 0 = 0$$

$$9V_3 - 9V_2 + 2V_3 = 0$$


$$-9V_2 + 11V_3 = 0 \quad \textcircled{3}$$

$$\begin{matrix} V_3 = 5.625 \\ \frac{V_2}{3} = 2.875 \\ -9V_2 + 11V_3 = 0 \end{matrix}$$

$$\frac{V_2 - V_1}{3} - 2 + 0 = 0 \quad \textcircled{4}$$

$$V_2 - V_1 = 6$$

$$V_2 = 6 + V_1$$

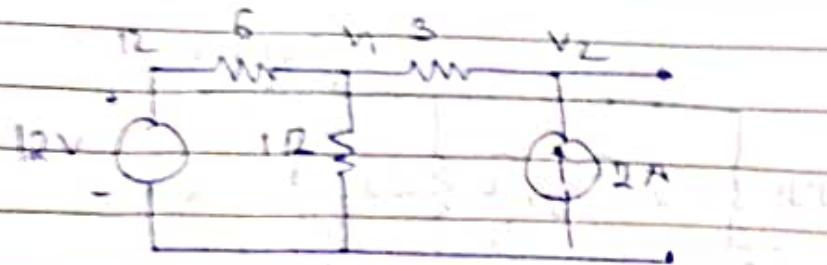

$$\frac{V_1 - 12}{6} + \frac{V_1}{12} + \frac{V_1 - V_2}{3} = 0$$

$$2V_1 - 24 + V_1 + 4V_1 - 4V_2 = 0$$


$$7V_1 - 4V_2 = 24 \quad \textcircled{1}$$

$$\frac{V_2 - V_1}{3} = 2 \Rightarrow 0$$

$$V_2 - V_1 = 6 \quad \textcircled{2}$$

$$V_1 = V_2 = 22 \text{ V}$$


Q) Find max power transfer in R_L

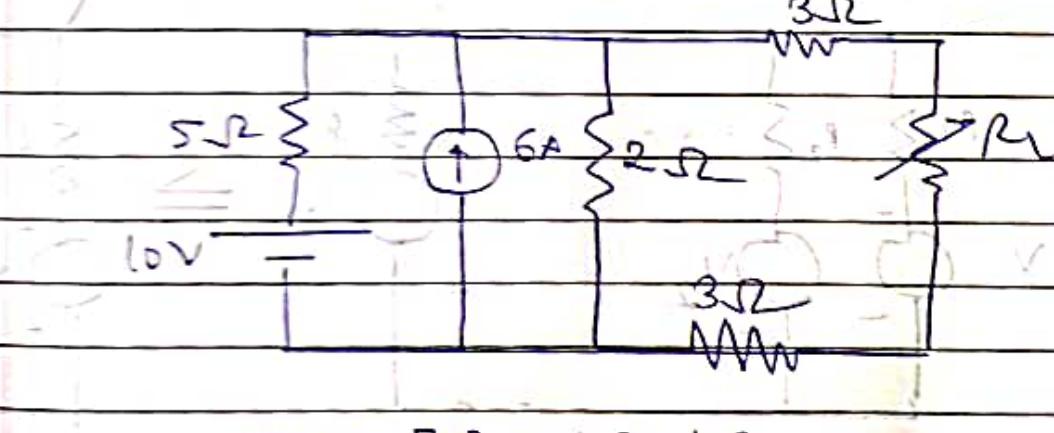

$$R_{th} = \frac{5 \times 2}{5+2} + 3 + 3$$

$$= 6 + 1.428$$

$$= 7.428 \Omega$$

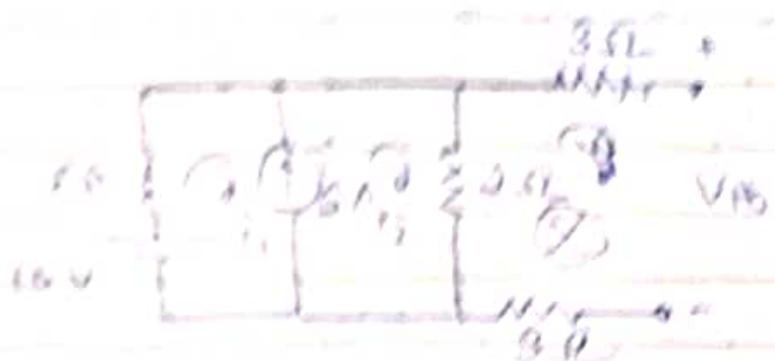

$$10 = 5I_1 + \text{dil}_2 > 0$$

$$\text{dil}_2 = 3I_2$$


$$I_1 = 0.73A$$

$$I_2 = 0.71A$$

$$V_{m,2} = 0.21 \times 30 = 6.3V$$

$$7.42 \cdot 0.73A = 5.4V$$

$$\left\{ P = 60.92W \right\}$$

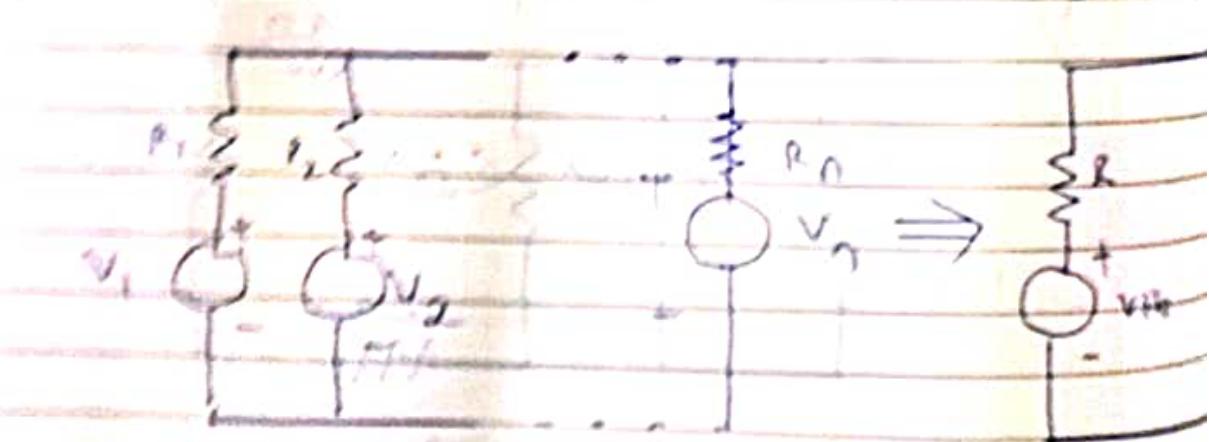

$$G_i = Y_R$$

Millman's theorem states that in any network if the voltage sources V_1, V_2, \dots, V_n and their internal resistances R_1, R_2, \dots, R_n are connected in parallel, they can be replaced by a single source V in series with a resistance R where

$$V = \frac{V_1 G_{in} + V_2 G_{in} + \dots + V_n G_{in}}{G_1 + G_2 + \dots + G_n}$$


$$\Delta R = \frac{1}{G_1 + G_2 + \dots + G_n}$$

Similarly if a number of current sources are connected as shown can be replaced by a single current source (i_1, i_2, \dots, i_n)

$$I = \frac{i_1 R_1 + i_2 R_2 + \dots + i_n R_n}{R_1 + R_2 + \dots + R_n}$$

$$G = \frac{1}{R_1 + R_2 + \dots + R_n}$$
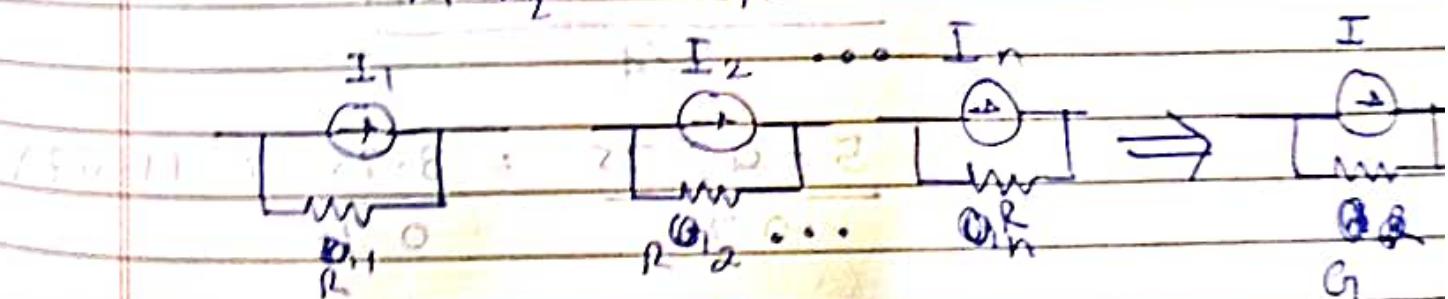
$$V = \frac{i_1 R_1 + i_2 R_2 + \dots + i_n R_n}{R_1 + R_2 + \dots + R_n} \times 0.1 = V$$





$$A.P.O.G = V = i$$

$$E +$$

(Q)

Find current through 3Ω resistor.

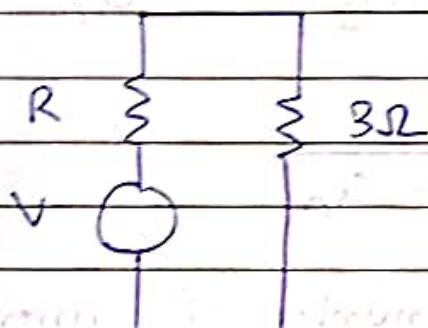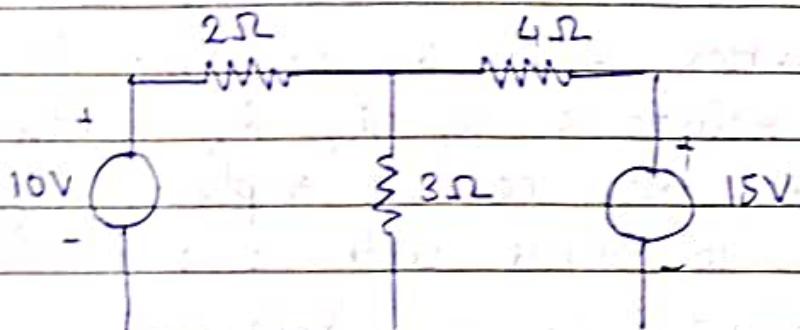

$$G_1 = \frac{1}{2}, G_2 = \frac{1}{4}$$

$$G_1 + G_2 = \frac{2}{4} + \frac{1}{4} = \frac{3}{4}$$



$$R = \frac{1}{G_1 + G_2} = \frac{1}{\frac{3}{4}} = \frac{4}{3} = 1.33\Omega$$

$$V = \frac{10 \times \frac{1}{2} + 15 \times \frac{1}{4}}{\frac{3}{4}}$$

$$\left(\frac{5}{0.75} + \frac{43.75}{0.75} \right) = \frac{5 + 43.75}{0.75} = \frac{48.75}{0.75} = 65$$

$$i = \frac{V}{R+3} = \frac{65}{1.33 + 3} = 13.33A$$

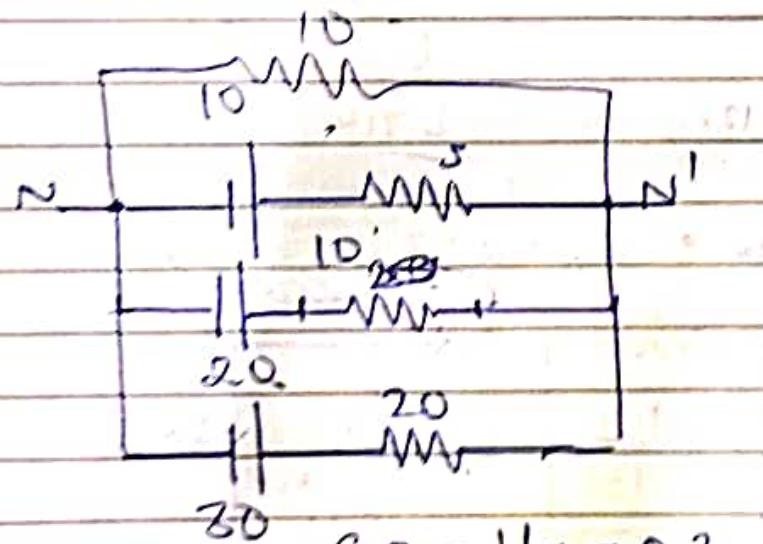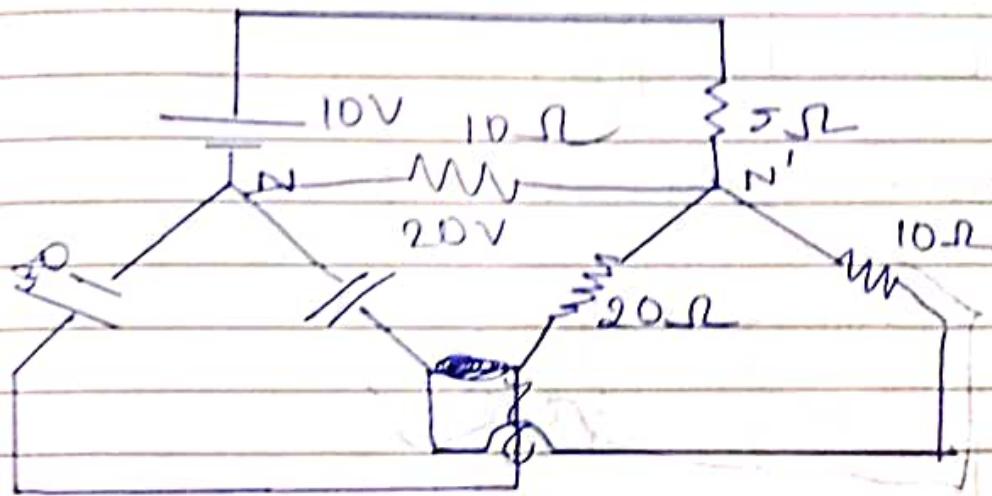(Q) Find the current through $10\text{ }\Omega$ connected between terminals $N-N'$



$$G_1 = \frac{1}{10} = 0.1$$

~~$G_2 = \frac{1}{20} = 0.05$~~

$$G_3 = \frac{1}{30} = 0.033$$

$$\frac{10 \times 0.1 + 30 \times 0.033}{0.28}$$

~~$R_1 = \frac{1}{0.1} = 10\text{ }\Omega$~~

$$\begin{aligned} & \frac{4(2+1.5)}{2.5} \\ & = 14 \end{aligned}$$



$$(14 - 4) - 10 = 10$$

$$I = \frac{10}{20} = 0.5$$

Bankbook

1	2	3	4	5	6	7	8
100	100	100	100	100	100	100	100
100	100	100	100	100	100	100	100
100	100	100	100	100	100	100	100
100	100	100	100	100	100	100	100

200000 Cr. 3000

1	2	3	4	5	6	7	8
100	100	100	100	100	100	100	100
100	100	100	100	100	100	100	100
100	100	100	100	100	100	100	100
100	100	100	100	100	100	100	100

Bank A/c = 3714.52

Bank

Bank = 200000.00

1	2	3	4	5	6	7	8
100	100	100	100	100	100	100	100
100	100	100	100	100	100	100	100
100	100	100	100	100	100	100	100
100	100	100	100	100	100	100	100

60 = 2(100) - 40 = 0

800 + 60 + 20 = 0


1000 + 200 + 90 = -40 = ① 0201

200 + 100 + 2(100) = 0

0 + 100 = -20 = ②

0 + 100 = 100

100 + 100 = 200

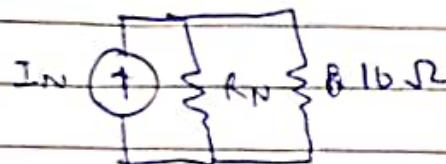


$$\text{Q} \quad i_{10\Omega} = \frac{R_N}{10 + R_N} \times i_N \\ = 1.699 \text{ A}$$


~~Q~~ Gotti - A 40V is b/w IN branch & C.R so
cannot neglect G.R } } }

2)

$$i = ? \text{ } 50\Omega$$

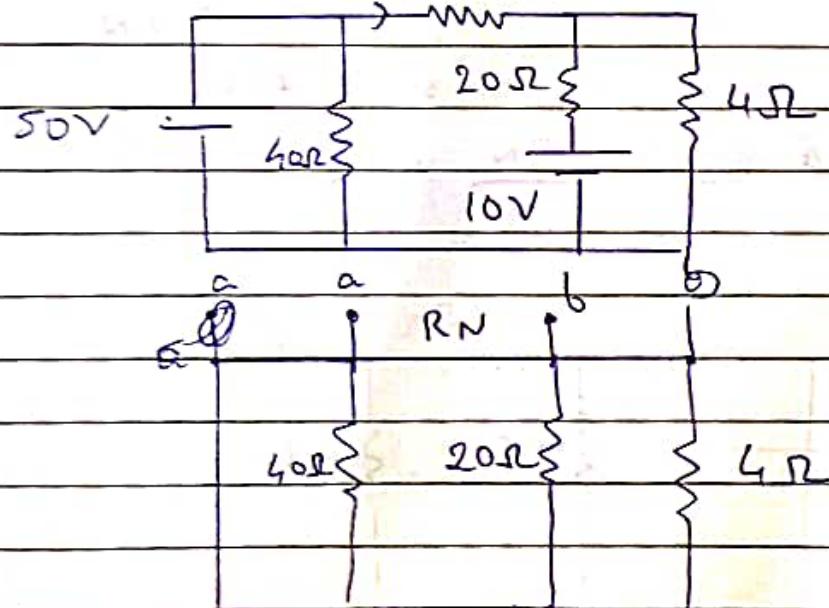

$$R_N = \frac{4}{20+4} = 3.33 \Omega$$

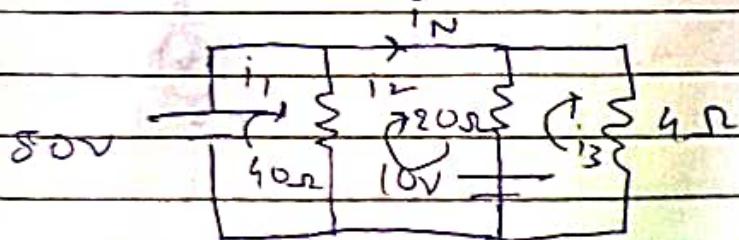

$$150 - 40(i_1 - i_2) = 0$$

$$\Rightarrow -40i_1 + 40i_2 = -150 \quad \textcircled{1}$$

$$-40(i_2 - i_3) - 20(i_3 - i_4) = 10 = 0$$

$$\Rightarrow 40i_1 = 60i_2 + 20i_3 + 10 = \textcircled{2}$$

$$10 = 20(i_3 - i_2) - 4i_3 = 0$$


$$\Rightarrow 20i_2 = 24i_3 = -10 = \textcircled{3}$$

$$i_1 = 15.75 \text{ A}$$

$$i_2 = 14.5 \text{ A} = i_N$$


$$i_3 = 12.5 \text{ A}$$
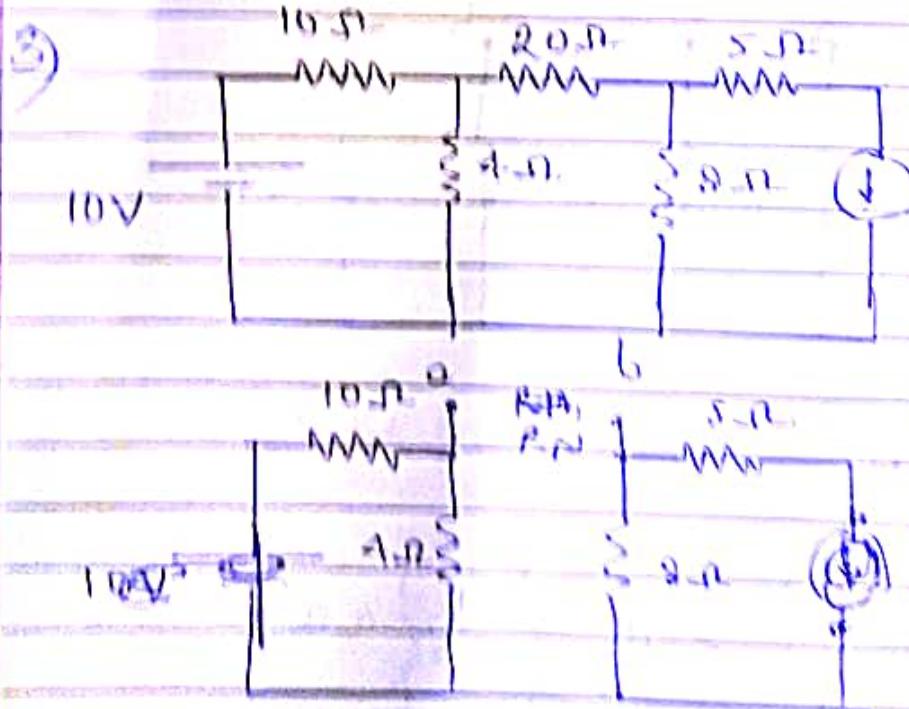
$$i_1 = \frac{R_N}{R_N + R_L} \times i_N = 0.905 \text{ A}$$



$$R_p = \frac{10 \times 4}{10 + 4} = 2.857 \Omega$$

$$R_N = 10.857 \Omega$$

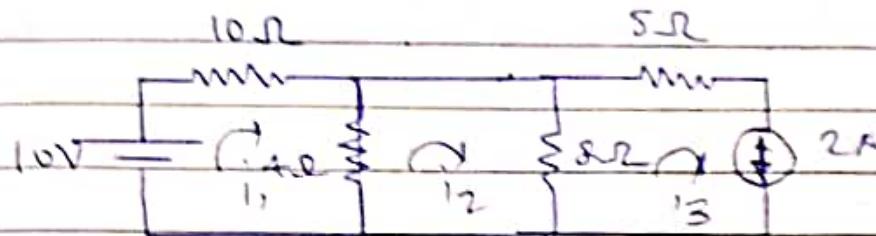

$$10 - 10i_1 - 4(i_1 - i_2) = 0$$

$$\Leftrightarrow -14i_1 + 4i_2 = -10 \quad \text{--- (1)}$$

$$-4(i_2 - i_1) - 8(i_2 - i_3) = 0$$

$$-4i_2 + 4i_1 - 8i_2 + 8i_3 = 0$$

$$4i_1 - 12i_2 + 8i_3 = 0 \quad \text{--- (2)}$$


$$i_3 = 2A \quad \text{--- (3)}$$

$$4i_1 - 12i_2 = -16 \quad \text{--- (4)}$$

$$i_1 = 1.21 A \quad i_2 = 1.736 A$$

$$i_N = i_2 = 1.736 A$$
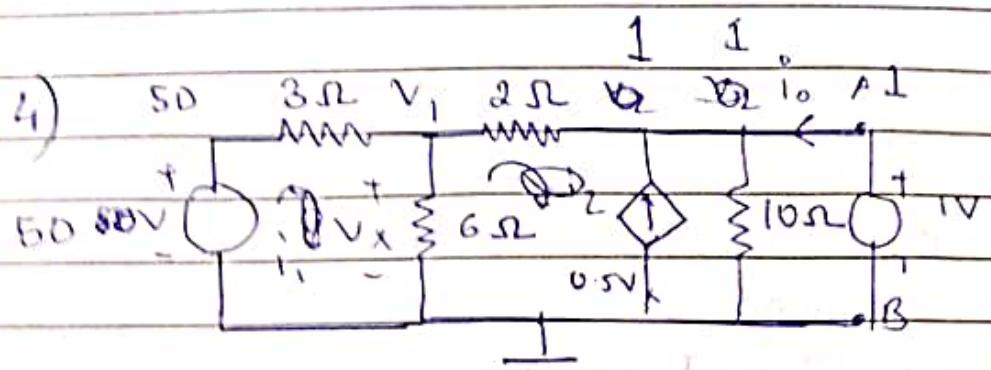
$$i_L = \frac{R_N}{R_N + R_L} \times i_N = 0.6 A$$



$$\frac{V_1 - 50}{3} + \frac{V_1}{6} + \frac{V_1 - 1}{2} = 0$$



$$2V_1 - 100 + V_1 + 3V_{01} - 3 = 0$$

$$\begin{cases} 6V_1 = 103 \\ V_1 = 17.167 \text{ V} \end{cases}$$

$$i = \frac{V_1 - 1}{2} = 8.08 \text{ A } (\rightarrow)$$

$$V_x = 0.5V_1 = 17.167 \text{ V}$$

$$i' = 8.835 \text{ A } (\uparrow)$$

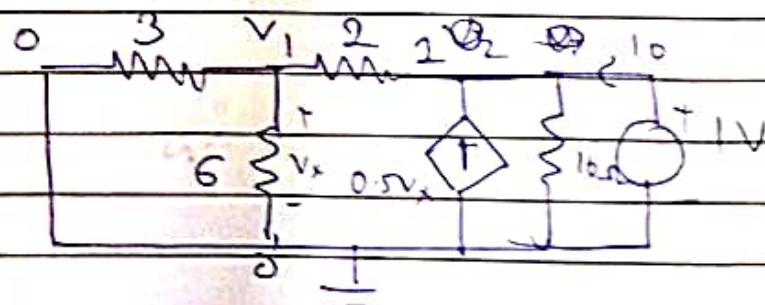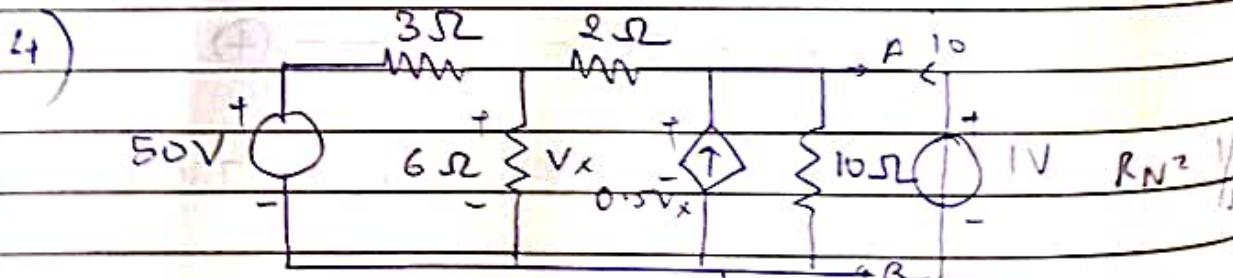

$$\text{Q} \quad \frac{V_1}{3} + \frac{V_1}{6} + \frac{V_1 - 1}{2} = 0$$

$$2V_1 + V_1 + 3V_1 - 3 = 0$$

$$V_1 = 3/6 = 0.5V$$

$$V_x = 0.5V$$

$$i = \frac{1.5}{6} A$$

$$\nabla i_1 = \frac{V_1 - 1}{2} = \frac{0.5 - 1}{2} = -0.25A$$

$$i_2 = \frac{1}{10} = 0.1A$$

$$-0.25 + 1.5 + i_3 + 0.1 = 0$$

$$i_3 = 1.25 - 1.33A$$

$$R_{AB} = 1/133$$

(5)


AC Circuits

The sinusoid is a signal that is the form of sine or cosine function.



Sinusoidal current is usually referred to as alternating current or AC.

Sinusoidal signal is easy to generate or transmit & it is easy to handle i.e. the derivative or integral of a sinusoidal is also a sinusoidal.
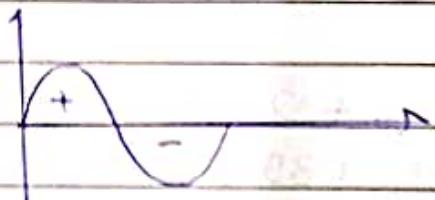
$$V(t) = V_m \sin(\omega t) \quad \text{where } V_m \text{ is amplitude}$$



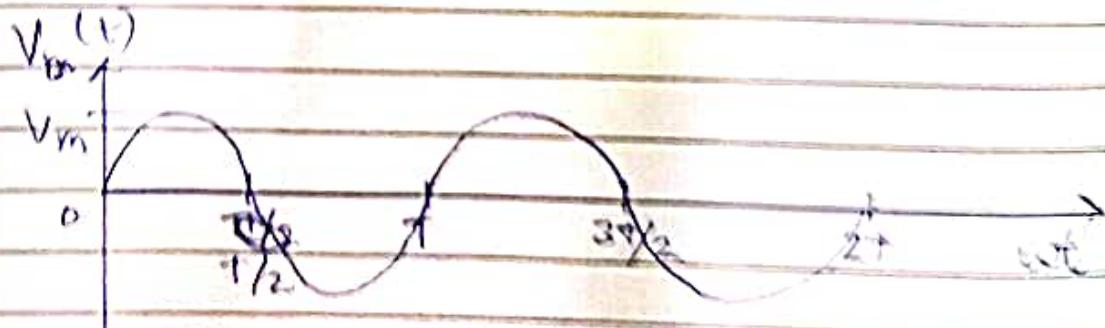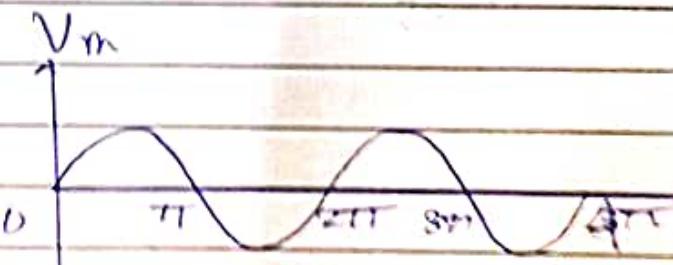ω is angular frequency
in radians second
 (ωt) is called phase
argument of sinusoid



The sinusoid repeats after every T seconds where T is called period

$$V_1 = 2\pi r$$

$$V_1 = \frac{2\pi r}{60} \text{ m/s}$$

$V(t) = \text{constant}$

$$V(t+T) = V_0 \sin(\omega t + \phi)$$

$$\Rightarrow V_0 \sin(\omega t + \phi)$$

$$\Rightarrow V_0 \sin(\omega t - \phi)$$

$$\Rightarrow V_0 \sin(\phi)$$

$$V(t+T) = V(t)$$

$\therefore V(t)$ is periodic function


$$\therefore \text{the period} = T$$

General expression of sinusoid

$$V(t) = V_0 \sin(\omega t - \phi)$$

$(\omega t - \phi) = \text{argument}$

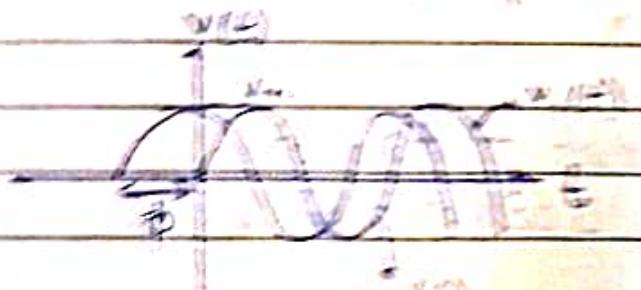$\phi \rightarrow$ phase angle / phase of sinusoid



$$V_2(t) = V_0 \sin(\omega t - \phi)$$

$$\therefore V_2(t) = V_0 \sin(\omega t - \phi)$$

say leads us by ϕ day
or we lag by ϕ

now for the simplicity the sinusoids make our life
easier if we are able to add or combine form with
different phase and amplitude.

$$y_1(t=3) = \sin A \cos \omega t + \sin B \cos \omega t$$

$$y_2(t=3) = \cos A \cos \omega t = \sin A \sin \omega t$$

$$\sin(\omega t = \pi) = -\sin \omega t$$

$$\cos(\omega t = \pi) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \sin \omega t$$

Adding two sinusoids

$$A \cos \omega t + B \cos \omega t = C \cos(\omega t - \theta)$$




$$C = \sqrt{A^2 + B^2}$$

$$\theta = \tan^{-1}(B/A)$$

$$3 \cos 30t + 5 \sin 30t$$

$$5 \cos 30t + (\theta \text{ E3})$$

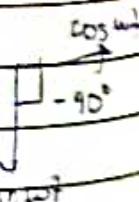

Q 8.3

$$V(t) = 12 \cos(50t + 10^\circ)$$

$$A = 12 \text{ V} \quad \text{and} \quad \omega = 50 \text{ rad/s}$$

$$\omega = 50 \text{ rad/s} \quad 0.125 \text{ rev/s}$$

$$\Phi = 10^\circ \quad f = 7.957 \text{ Hz}$$

Calculate $\sin \theta$ and $\cos \theta$

$$v_x = -12.5 \cos(30^\circ - 45^\circ)$$

$$v_y = 12.5 \sin(30^\circ - 45^\circ)$$

$$\vec{v} = 12.5 \cos(30^\circ - 45^\circ)$$

$$= 12.5 \cos(-45^\circ)$$

$$v_x = 12.5 \cos(-45^\circ)$$

$$v_x = 12.5 \cos(-45^\circ)$$

$$v_x = 12.5 \cos(-45^\circ) \text{ by } 30^\circ$$

$$v_x = 12.5 \cos(-45^\circ)$$

$$= 12.5 \cos(-45^\circ)$$

$$v_x = -12.5 \cos(30^\circ - 45^\circ)$$

$$v_x = 12.5 \cos(30^\circ - 45^\circ)$$

$$= 12.5 \cos(30^\circ + 45^\circ)$$

$$v_x = 12.5 \cos(75^\circ)$$

~~$v_x = 12.5 \cos(30^\circ - 45^\circ)$~~

~~RST~~
~~125~~
~~-~~

~~$v_x = 12.5 \cos(30^\circ - 45^\circ)$~~

~~$v_x = 12.5 \cos(30^\circ + 45^\circ)$~~

~~$v_x = 12.5 \cos(75^\circ)$~~

$$i_1 = 11 \sin(377t + 85^\circ)$$

$$i_2 = 5 \cos(377t + 46^\circ)$$

$$i_2 = 5 \cos(377t + 90 + 46^\circ)$$

$$i_2 = 5 \sin(377t + 136^\circ)$$

$$i_1 = 11 \sin(377t + 125^\circ)$$

$$= 11 \sin(377t + 180 - 180 + 125^\circ)$$

$$= 11 \sin(377t - 155^\circ)$$

$$\phi_1 - \phi_2 = 205 - 360$$

$$= -155^\circ$$

Euler's identity

$$e^{j\phi} = \cos\phi + j\sin\phi$$

Phasor is a complex number that represents the amplitude and phase of a sinusoid. Sinusoids are easily expressed in terms of phasors which are more convenient to work with than sine and cosine functions. A complex number z can be written in rectangular form when it is equal to:

$$z = x + jy \quad (\text{rectangular form})$$

$$(23) z = r\angle\phi \rightarrow \text{Polar form}$$

$$r^2 = \sqrt{x^2 + y^2} \quad \phi = \tan^{-1}(y/x)$$

The idea of phasor representation is based on Euler identity.

$$\{e^{j\phi} = \cos\phi + j\sin\phi\}$$

$$z = re^{j\phi} \rightarrow \text{exponential form}$$

$$\cos\phi = \operatorname{real}(e^{j\phi})$$

$$\text{At } V(t) = V_m \cos(\omega t + \phi)$$

$$= \operatorname{Re} [V_m e^{j(\omega t + \phi)}]$$

$$= \operatorname{Re} [V_m e^{j\phi} \cdot e^{j\omega t}]$$


$$= \operatorname{Re} [V e^{j\omega t}] \quad \text{--- (1)}$$

where

$$V = V_m e^{j\phi} = V_m \angle \phi \quad \text{--- (2)}$$

V is the phasor representation of sinusoidal $v(t)$.

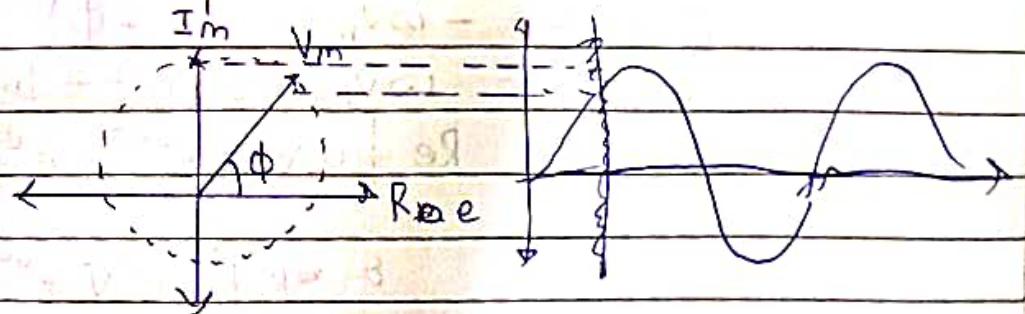A phasor is a complex representation of the magnitude and phase of the sinusoid.



If we project any point of $v(t)$ on real axis it will appear like in figure 10.6.

To get the phasor corresponding to a sinusoid express the sinusoid in cosine form so that sinusoid can be written as a real part of an a complex number. Then take out the time factor $e^{j\omega t}$ and whatever is left is a phasor corresponding to the sinusoid.

Time Domain

Phasor Domain

$$V_m \cos(\omega t + \phi)$$

$$V_m \angle \phi$$

$$V_m \sin(\omega t + \phi)$$

$$V_m \angle \phi - 90^\circ$$

$$I_m \cos(\omega t + \theta)$$

$$I_m \angle \theta$$

$$I_m \sin(\omega t + \theta)$$

$$I_m \angle \theta - 90^\circ$$

$$V(t) = V_m \sin(\omega t + \phi) \\ = \text{Re}(V e^{j\omega t})$$

$$\frac{\partial V(t)}{\partial t} = -\omega V_m \sin(\omega t + \phi)$$

$$= \omega V_m \cos(\omega t + \phi - 90^\circ)$$

$$\text{Re} [\omega V_m e^{j\omega t} \cdot e^{j\phi}, e^{j90^\circ}]$$

$$\delta = \text{Re} [j\omega V e^{j\omega t}]$$

This shows that derivative of $V(t)$ is transferred to the phasor domain is $j\omega V$.

$$\frac{dV(t)}{dt} \rightarrow j\omega V$$

i
→ mm

$$V = L di$$

$\frac{dt}{dt}$

$$= L \frac{d i}{dt}$$

$$= X_L I$$

$$V(t) = V_m \sin(\omega t) \quad |V_m e^{j\omega t}| \rightarrow I_m$$

$$\frac{d(V(t))}{dt} = V_m \cos(\omega t), \quad |V_m e^{j\omega t}|$$

$$= V_o(t) / (j\omega)$$

Re

C

 $V_m (\omega t + \phi_2 - 90^\circ - 90^\circ)$

$$V(t) = V_m \cos(\omega t + \phi_1) + V_m \sin(\omega t + \phi_2)$$

$$= V_m \angle \phi_1 + V_m \angle \phi_2 (\phi_2 - 90^\circ)$$

Time Domain

Phasor Time

$V(t)$ is instantaneous representation is instantaneous representation

Time dependent

Not time dependent

Always real

Phasor is always complex

Note Phasor analysis applies only when frequency is constant.

Evaluations

$$\begin{aligned}
 \textcircled{a}) & \quad (40 \angle 50^\circ + 20 \angle -30^\circ)^{1/2} \\
 &= \left[(25.71 + j 30.64) + (17.32 - j 10) \right]^{1/2} \\
 &= \left[43.03 + j 20.64 \right]^{1/2} \\
 &\approx 6.91 \angle 12.81^\circ
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{b}) & \quad \frac{10 \angle -30^\circ + (3 - j4)}{(2 + j4)(3 - j5)^*} \\
 &= \frac{(8.66 - 5j) + (8 - 4j)}{(2 + j4)(3 + j5)}
 \end{aligned}$$


$$\begin{aligned}
 &= \frac{(11.66 - 9j)}{(-14 + 22j)}
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{14.729 \angle -37.66^\circ}{-26.076 \angle 122.47^\circ}
 \end{aligned}$$

$$\begin{aligned}
 &= 0.5648 \angle -160.13^\circ //
 \end{aligned}$$

Transform the sinusoidal to phasor.

$$v_2 = 4 \sin(30t + 50^\circ)$$

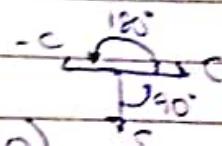

$$= -4 \sin(30t + 50 + 90 - 90)^\circ$$

$$= -4 \cos(30t - 40^\circ)$$

$$= -4 \cos(30t - 40 + 180 - 180)^\circ$$

$$= 4 \cos(30t - 220^\circ)$$

$$= 4 \cos(30t + 140^\circ)$$

$$= 4 \angle 140^\circ - 4 \angle 220^\circ$$

$$r \angle \phi = 4 \angle 140^\circ$$

$$\text{Q) } i_1 = 6 \cos(50t - 40^\circ)$$

$$6 \angle 220^\circ$$


$$\text{time } I = 6 \angle -40^\circ$$

$$\text{Ans. } I = -3 + j4$$

$$\text{For } r \angle \phi = 5 \angle 126.86$$

$$= 5 \cos(\omega t + 126.86^\circ)$$

Sinusoid.

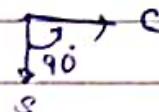

$$i_2 = 4 \cos(\omega t + 30^\circ)$$

$$i_2 = 5 \sin(\omega t - 20^\circ) = 5 \sin(\omega t - 20 + 90 - 90)^\circ$$

$$\text{Find the sum of sinusoids} = 5 \cos(\omega t - 110^\circ)$$

$$4 \angle 36^\circ + 5 \angle -110^\circ$$

$$= 3.46 + 2j + (-1.71) 4 - j4.698$$


$$1.75 - 2.498j$$

$$= 3.215 \angle -57.03^\circ$$

$$= 3.215 \cos(\omega t - 57.03^\circ)$$

$$v_1 = -10 \sin(\omega t + 30^\circ)$$

$$v_2 = 20 \cos(\omega t - 45^\circ)$$

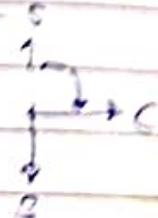

$$v_1 = -10 \sin(\omega t + 30^\circ - 90^\circ + 90^\circ)$$

$$v_1 = 10 \cos(\omega t + 120^\circ)$$

$$v_1 + v_2 = 20 \angle -45^\circ + 10 \angle 120^\circ$$

$$= 14.14 + -j14.14 + -5 + j8.66$$

$$= 9.14 - j5.48$$

$$= 10.65 \angle -30.94^\circ$$

$$= 10.65 \{ \cos(\omega t - 30.94^\circ) \}$$

(Q) Determine the current in ck_1 using phasor approach

$$4i + 8jdt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

$$\frac{4I + 8I}{2j00} - 3Ij\omega^2 = 50 \angle 75^\circ$$

$$4I - 10Ij\omega = 12.94 + 48.296j$$

$$4I - j \frac{1000}{70} I = 12.94 + 48.296j$$

$$I = \frac{12.94 + 48.296j}{4 - j10} = 0.50 \angle 75^\circ$$

$$10.71 \angle 69^\circ$$

$$4.64 \angle 143.19^\circ$$

$$= 4.64 \cos(2t + 143.19^\circ)$$

(q) Find $v(t)$ in the ckt

$$2 \frac{dv}{dt} + 5v + 10 \int v dt = 40 \cos(5t - 20^\circ)$$

$$2j\omega v + 5v + \frac{10V}{j\omega} = 20 \angle -20^\circ$$

$$10Vj + 5V + 2Vj = 20 \angle -30^\circ$$

$$jV = -20 \angle -30^\circ$$

$$5 \angle +20^\circ$$

$$2 \angle 20^\circ$$

$$9.43 \angle 57.99^\circ$$

$$= 2.121 \angle -87.99^\circ$$

$$= 2.121 \cos(5t - 87.99^\circ)$$

Phaser Relationship for circuit elements

Time Domain Phaser Domain

$$R \quad V = R I \quad V = RI$$

$$L \quad V = L \frac{di}{dt} \quad V = j\omega LI$$

$$C \quad V = \frac{1}{C} \int i dt \quad V = \frac{I}{j\omega L}$$

$$Z = \frac{V}{I} = \text{Impedance of the ckt.}$$


when $\omega = 0$ $Z_L = 0$ $\left\{ \begin{array}{l} \text{short ckt} \\ \text{parallel} \end{array} \right.$

$\omega \rightarrow \infty$ $Z_L \rightarrow \infty$ $\left\{ \begin{array}{l} \text{open ckt} \\ \text{parallel} \end{array} \right.$

when $\omega = 0$ $Z_L = \infty$ $\left\{ \begin{array}{l} \text{open ckt} \\ \text{series} \end{array} \right.$

$\omega \rightarrow \infty$ $Z_L = 0$ $\left\{ \begin{array}{l} \text{short ckt} \\ \text{series} \end{array} \right.$

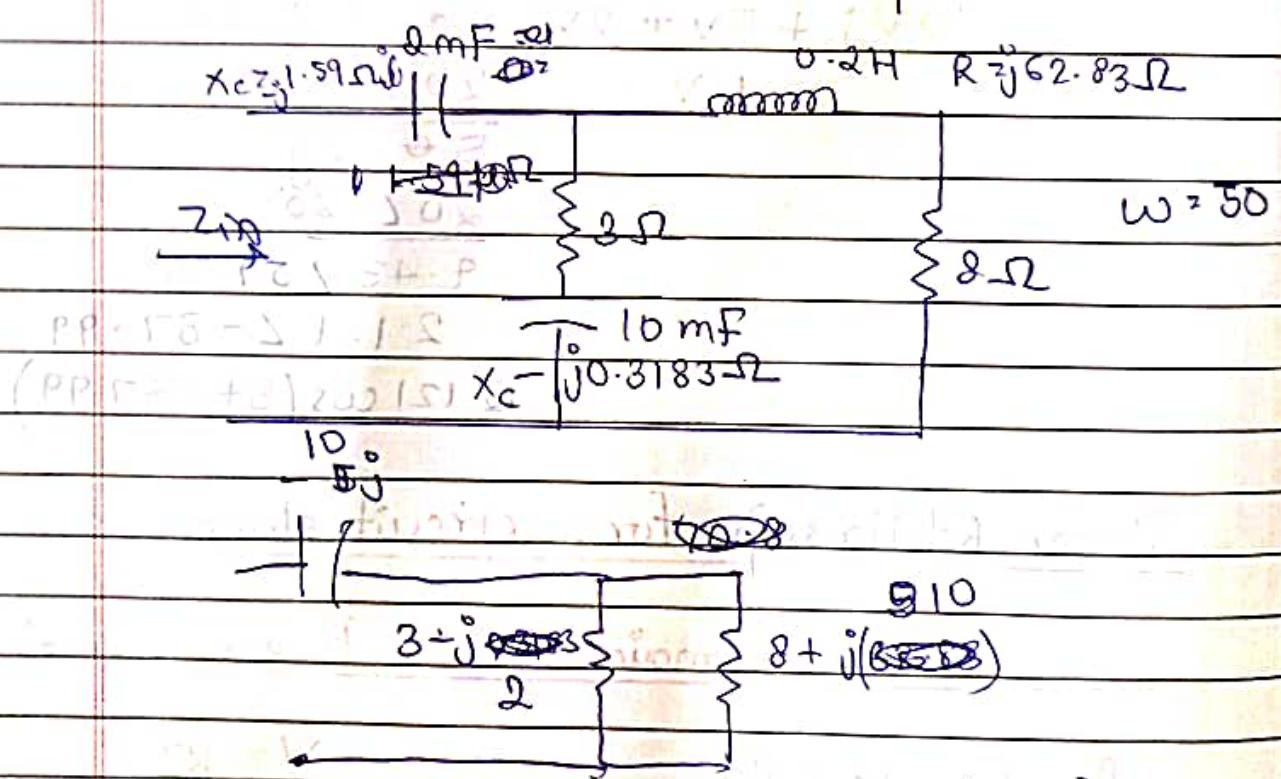- (q) Find the input impedance of the circuit assuming that ckt operates at $\omega = 50 \text{ rad/s}$



$$3.01 \angle -0.102^\circ \quad 63.33 \angle 1.44^\circ$$

$$R_{eq} = \frac{190.62 \angle 1.338^\circ}{11 - j62.517}$$

$$190.62 \angle 1.338^\circ$$

$$63.477 \angle -1.396^\circ$$

$$3 \angle 2.734^\circ$$

$$2.754 + j1.489$$


$$4.058$$

$$R_{eq} = \frac{(8+10j)(3-j)}{(8+10j+3-j)} = \frac{(12+10j)(3-j, L-0j)}{13+10j}$$

$$Z_{eq} = R_{eq} + 10j$$

$$= 32.2j \Omega (2.22 - j1.07) \Omega$$

(Q) Find $v_o(t)$

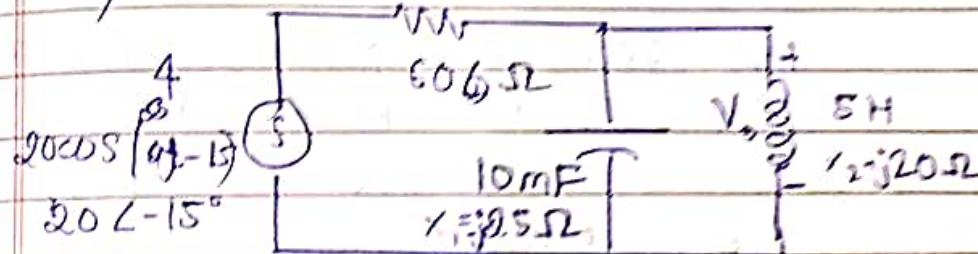

$$R_p = \frac{(-j2.5)(j20)}{-5j}$$

$$= \frac{25L-1.57}{20L+1.57}$$

$$R_p = 100L \angle 1.57^\circ \Omega$$

$$R_{net} = (j100 + 60) \Omega$$

$$i_1 = V/R$$

$$0.171 \angle -74.03^\circ$$

~~$$3V \text{ through } 20L-15^\circ \rightarrow 0.171 \angle -13.97^\circ$$~~

~~$$116.61 \angle -13.97^\circ$$~~


~~$$0.2 \angle -12.43^\circ$$~~

~~$$(0.129 - j0.152) A$$~~

$$0.171 \angle -74.03^\circ \quad 100$$

$$V_o = 0 \left(0.2 \angle -12.43^\circ \right) \left(0.171 \angle -74.03^\circ \right) \left(100 \angle 0^\circ \right)$$

~~$$= 17.1 \angle -96.43^\circ$$~~

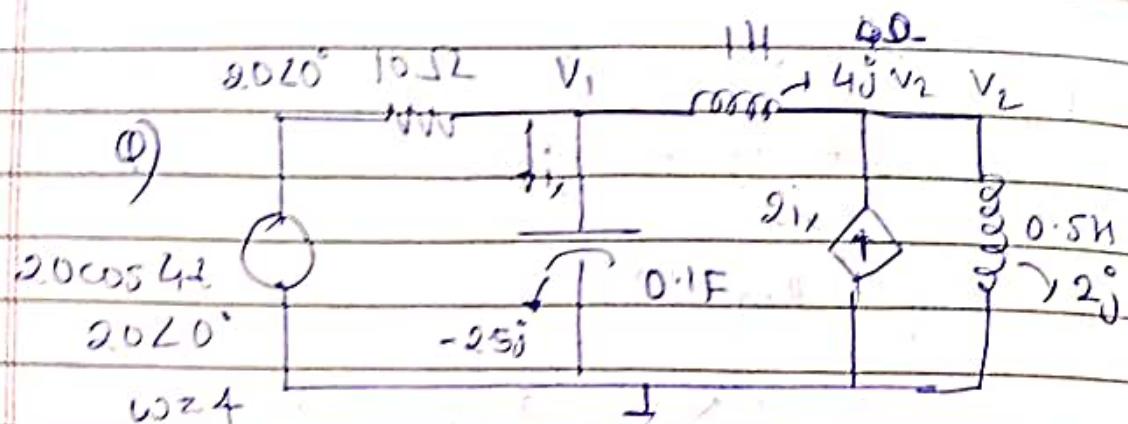

Steps 1) Transform the circuit to phasor or frequency domain

2) Solve the problem using any of the known techniques mesh, nodal, superposition etc.

3) Transform resulting phasor to the time domain

$$\frac{2 - V_1}{10} + \frac{V_1}{-0.5j} + \frac{V_2 - V_1}{4j} = 0$$

$$2 - 0.1V_1 + (0.4j)V_1 + j0.25(V_2 - V_1) = 0$$

$$2 + V_1(0.1 + 0.4j + 0.25j) + -0.25V_2 = 0$$

$$V_1(0.1 + 0.45j) - 0.25V_2 = 0$$

①

$$\frac{V_2 - V_1}{4j} + 2i_x + \frac{V_2}{2j} = 0$$

$$j(V_1 - V_2)(0.25) - 2i_x - 0.5jV_2 = 0$$

$$0.25jV_1 - j(0.75)V_2 = 2i_x = 0$$

②

$$0.25jV_1 - j(0.75)V_2 = 2i_x$$

$$0.4jV_1 + i_x = 0$$

③

$$jV_1 - j(0.75)V_2 - 2(0.4j)V_1 = 0$$

$$j(0.2V_1) = j(0.75V_2)$$

$$\{V_1 = 3.5V_2\}$$

i =

$$3.5V_2 \times (-0.1j + 0.63j) - j0.25V_2 = -2$$

~~X~~ ————— X —————

$$\frac{V_2 - 20}{10} + \frac{V_1 - V_2}{4j} + V_1 = 0$$

$$0.1V_1 - 2 + -0.25V_1j + 0.25V_2j + 0.4V_1j = 0$$

$$V_1(0.1 - 0.25j + 0.4j) + 0.25V_2j = 2$$

$$jV_1(0.1 + 1.5j) + 0.25V_2j = 2$$
—①

$$\frac{V_2 - V_1}{4j} - 2i_x + V_2 = 0$$

$$-0.25V_2j + 0.25V_1j - 2i_x + 0.5V_2j = 0$$

~~V₁ = 3.5V₂~~

$$0.25V_1j - V_2(0.25j + 0.50j) - 2i_x = 0$$

$$0.25V_1j - 0.75V_2j - 2i_x = 0$$
—②

~~$\frac{V_1}{V_2} = -2.5j$~~

$$\frac{V_1}{V_2} = -2.5j$$

$$-0.4V_1j = i_x \quad \text{---③}$$

0.75

$$0.25V_1j - 0.75V_2j - 0.8V_1j = 0$$

$$-0.55V_1j = 0.75V_2j \quad \underline{V_1 = 1.36V_2}$$

$$V_1 (-0.01 + 1.5j) + 0.25 V_2 j = 2$$

$$-1.36 V_2 (0.1 + 1.5j) + 0.25 V_2 j = 2$$

$$V_2 \left(-0.136 - 2.04j + 0.25j \right) = 2$$

$$V_2 = \frac{2}{-0.136 - 1.79j}$$

$$= -6.084 + 1.11j$$

$$V_1 = 0.114 - 1.509j$$


$$i_x = 0.4 V_1 j$$

$$= -0.603 + 0.045 i$$

$$\{ i_x = 7.59 \angle 108.4^\circ \}$$


$$i_x = 7.59 \cos(\omega t + 9.108.4^\circ)$$

Q) Find V_1, V_2 in the ckt. HW

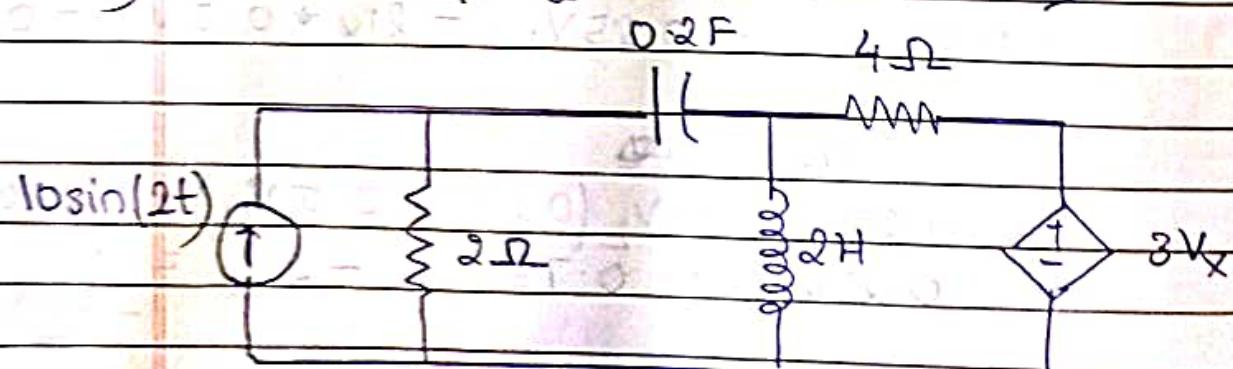

$$V_1 = 20.96 \sin(2t + 58^\circ) V$$

$$V_2 = 44.17 \sin(2t + 41^\circ) V$$

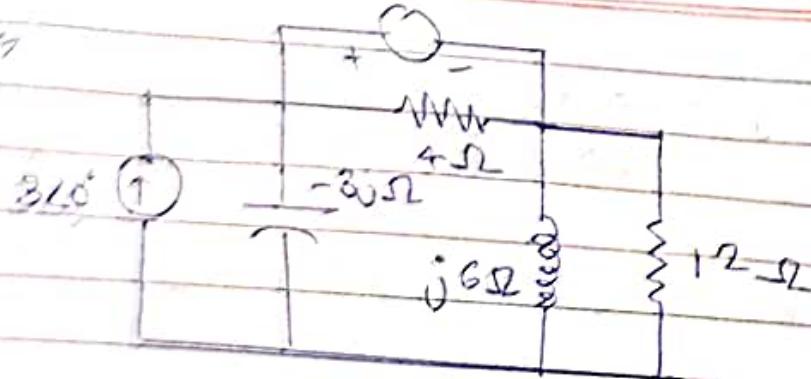
~~10 < 45°~~Find V_1 & V_2

$$V_1 = 25.78 \angle -70.48^\circ$$

$$V_2 = 31.41 \angle -87.18^\circ$$

{ Use supernode }

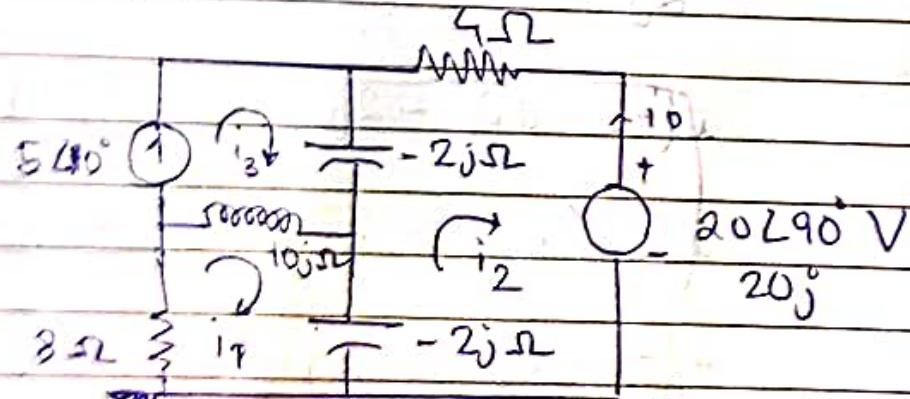- Q) Determine ~~no~~ is using mesh analysis



$$-3i_1 - j10i_2 + 2j = 0$$

$$-3i_1 - 10j(i_1 - i_3) + 2j(i_1 - i_2) = 0$$

$$-8i_1 - 10ji_1 + 10ji_3 + 2ji_1 - 2ji_2 = 0$$

$$i_1(-3 - 10j) + 2j = -2ji_2 + 10ji_3 = 0$$

$$i_1(-8 - 8j) - 2ji_2 + 10ji_3 = 0 \quad \text{--- (1)}$$

$$i_3 = 5 \angle 10^\circ A \\ = 5A \angle 10^\circ + 0.868j \quad - (2)$$

$$i_1 - 4i_2 - 20j + 2j(i_2 - i_1) + 2j(i_2 - i_3) = 0$$

$$-4i_2 - 20j + 2ji_2 - 2ji_1 + 2ji_2 - 2ji_3 = 0$$

$$i_2(-4 + 2j + 2j) - 2ji_1 - 2ji_3 = 20j$$

$$-2ji_1 + i_2(-4 + 4j) - 2ji_3 = 20j$$

$$-2ji_1 + i_2(-4 + 4j) - 10j = 20j \quad - (3)$$

$$-2ji_1 + i_2(-4 + 4j) = 30j \quad - (4)$$

$$i_1(-8 - 8j) - 2ji_2 + (10j)(5) = 0$$

$$i_1(-8 - 8j) - 2ji_2 = -50j \quad - (5)$$

$$i_1(-8 - 8j) - 2ji_2 = -50j \quad - (5)$$

$$-32j i_1 - i_2(-4 + 4j) = 400 \quad - (6)$$

$$i_1 = \frac{400}{-32j} = \frac{400 + 30j}{-0.88 + 11.76j}$$



$$i_2 = \frac{-23.52 + 28.24j}{(-4 + 4j)} = 6.47 - 0.5j$$

$$i_2 = 6.42 \angle -5.21^\circ$$

$$i_2 = i_2 = 6.42 \cos(\omega t - 5.21^\circ)$$

$$i_2 = i_2 = 6.42 \cos(\omega t - 144.78^\circ)$$

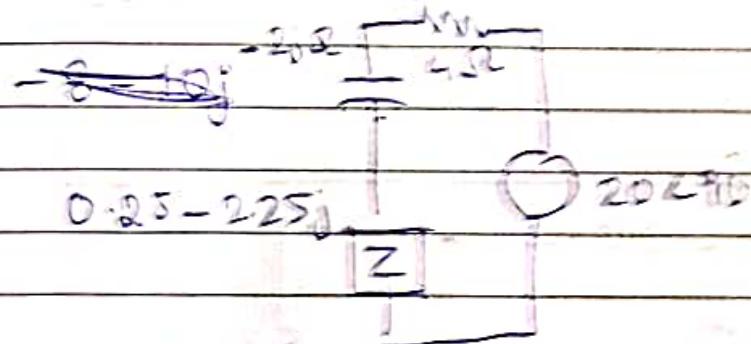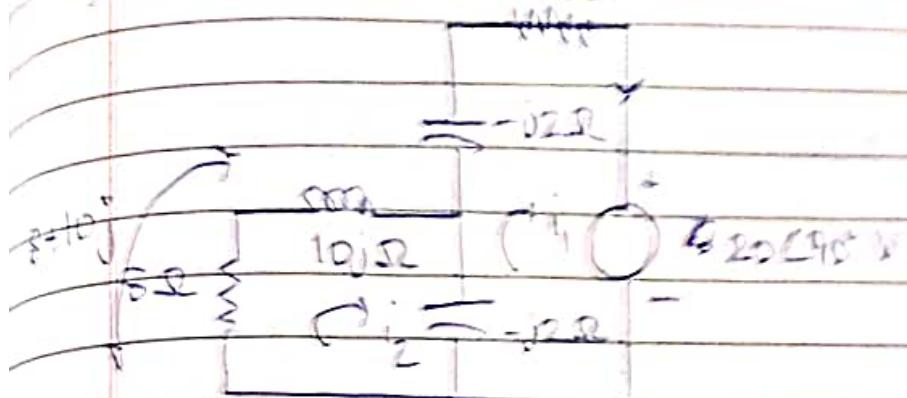Q) Solve some question using superposition method.




$$Z_{eq} = 4 \cdot 25 - 4 \cdot 25 j$$

$$V = 20j$$

$$i_1' = -2.353 + 2.353 j$$

$$\theta = 33.3^\circ \angle 180^\circ$$

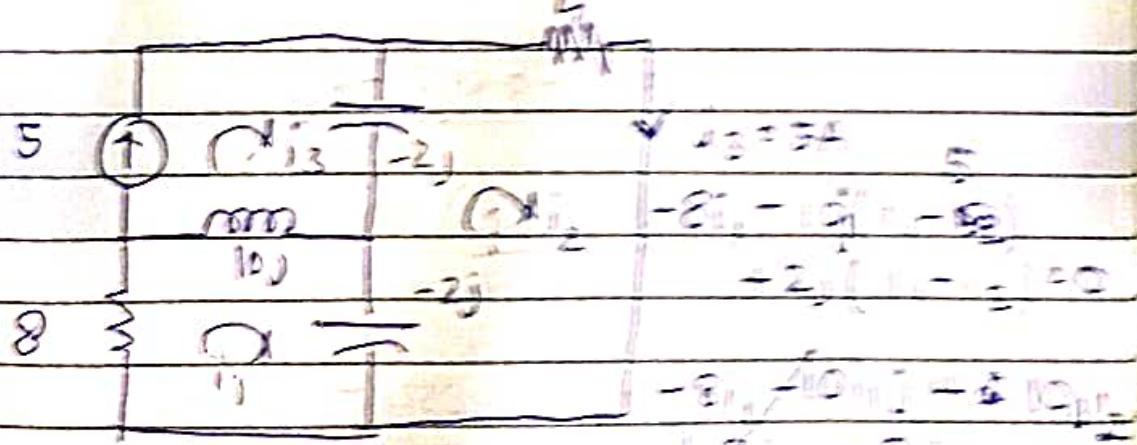



$$i_1(-8 - 10j + 2j) = i_2(1 - 2j - 5j) = 0$$

$$i_1(-8 - 8j) = i_2(5j) = 0$$

$$3.21(1+j) = i_2$$

$$-20(i_2 - i_1) - 2jV_1$$

(Q)

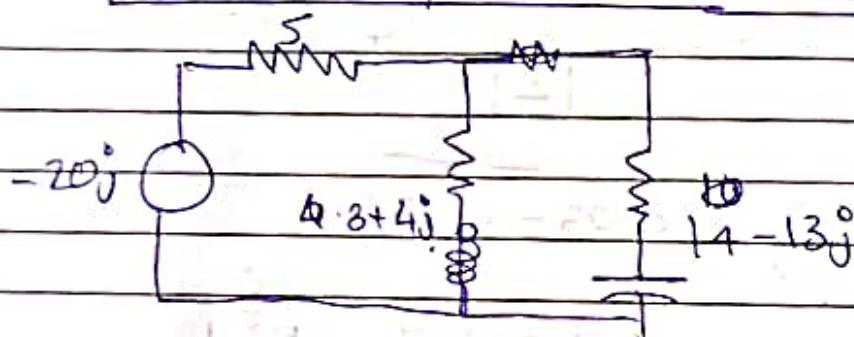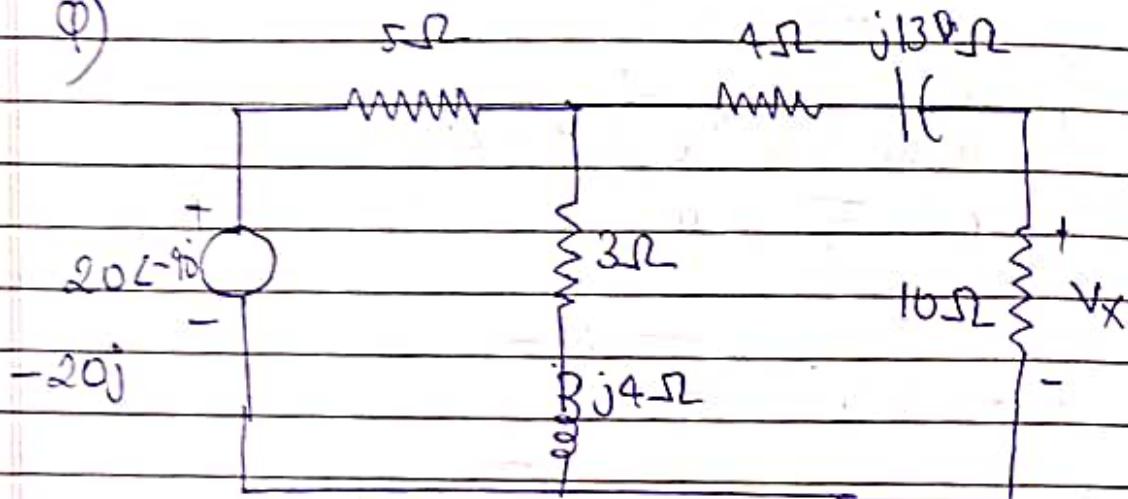

$$Z_{eq} = 8.905 + 3.067j$$

$$i = -0.6915 - 2j$$

$$i_2 = \left(\frac{R_1}{R_1 + R_2} \right) x i$$

$$i_2 = 0.4854 \angle 0.2586$$

$$= 0.5499 \angle -28.04^\circ$$

$$V_2 = i_2 \times R_2$$


$$= 5.499 \angle -28.04^\circ$$

$$V = 5.499 \cos(\omega t - 28.04^\circ)$$


(q)

Find Thvenin
eq. cktacross Δab

$$30 \angle 20^\circ$$

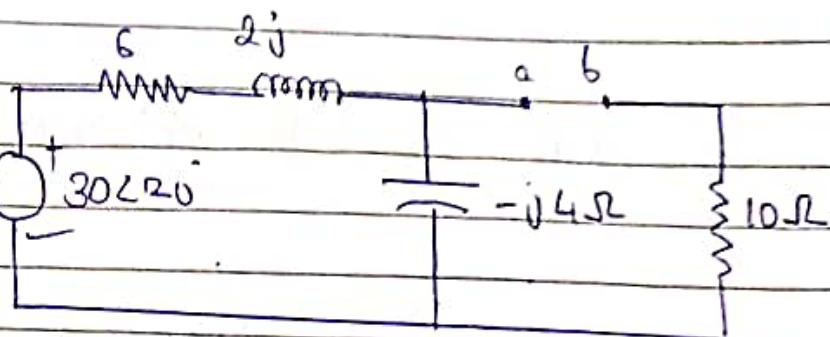

$$Z_{Th} = 12.4 - 3.2j$$

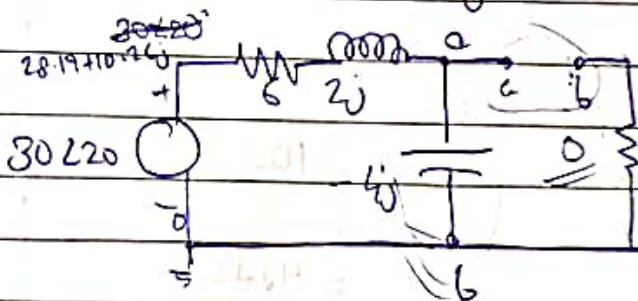

$$V = 28.19 + j0.26j$$

$$i = V \rightarrow 3.0715 + 2.948j$$

$$Z = 911.794 + 35.352j$$

$$\Delta V = 16.394 + 82.118j$$

$$V_{Th} = V_{ab} = 11.796 - 24.092j$$

$$\Delta V = 148.62 + 17.94j$$

$$V_a =$$



$$\Delta V = 89.975 + 13.326j$$

$$\Delta W = 11.78 + 35.58j$$


$$14.86j$$

$$V_{Th} \left\{ \alpha \angle \theta = 18.97 \angle -51.56^\circ \right\}$$

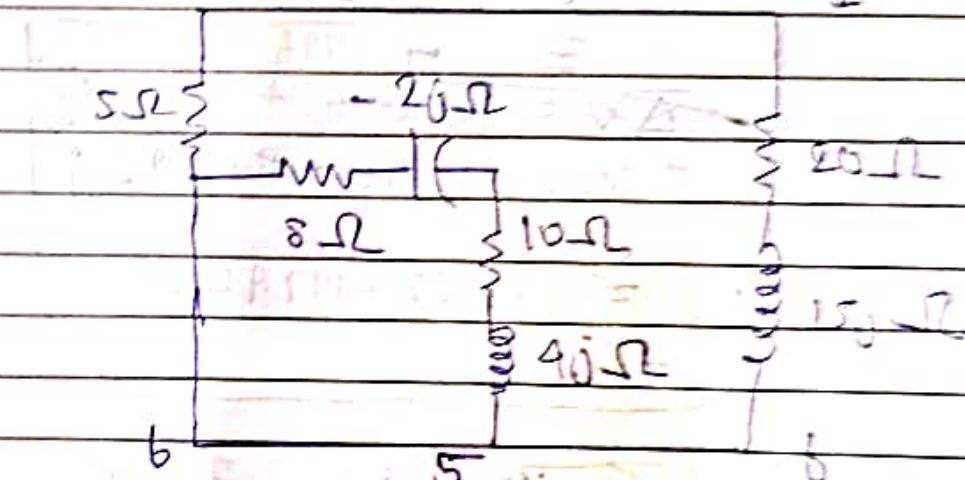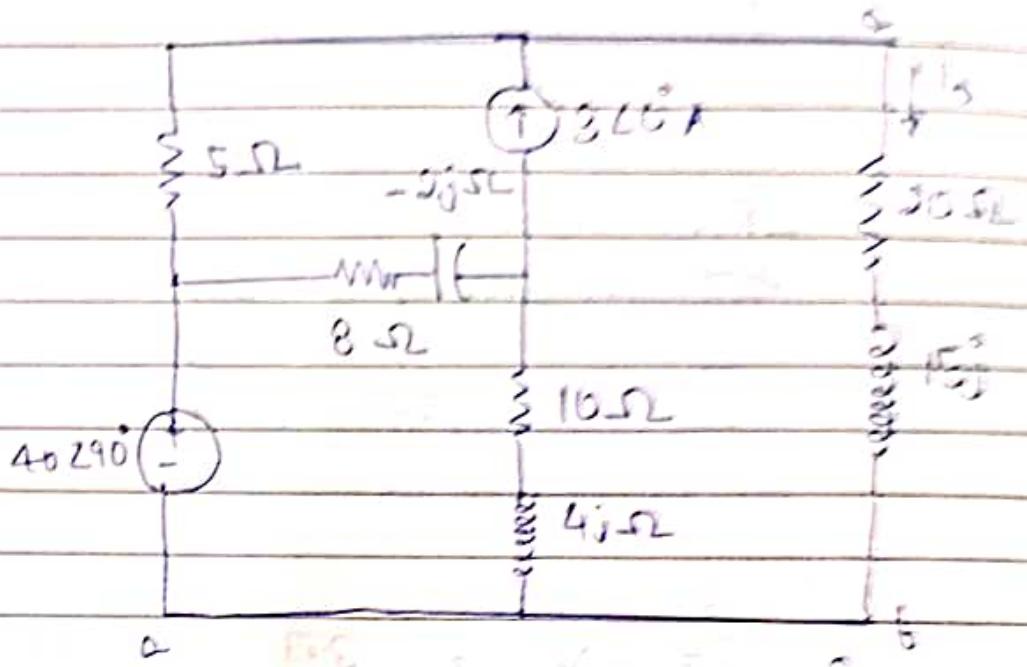(P) Calculate i_o in the circuit using Norton's Theorem.


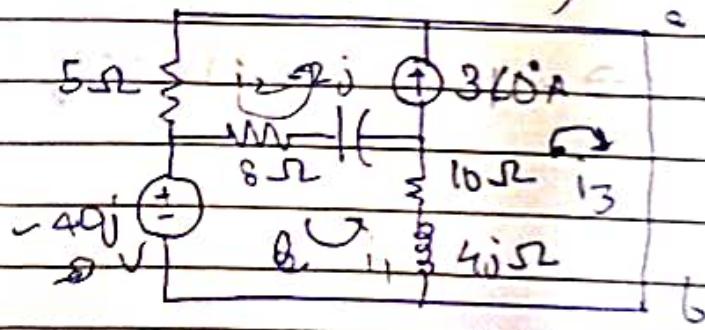
$$R_N = \left(\cancel{3i_o} \parallel \cancel{4j} \right) \Omega$$



$$-(-40j) - (4j+10)i_1 + 2j(i_1-i_2) - 8(i_1-i_2) = 0$$

$$i_2 = 3A$$

$$40j - (4j+10)i_1 + 2ji_1 - 6j - 8i_1 + 24 = 0$$

~~$$40j - (4j+10+2j-8)i_1 = -34j - 24$$~~

$$i_1 = \frac{34j + 24}{2j + 18}$$

$$= 1.52j + 1.719j$$

$$\begin{aligned} & -(-40j) - 4j(i_1 - i_3) - 10(i_1 - i_3) + 2j(i_1 - i_2) \\ & - 8(i_1 - i_2) = 0 \end{aligned}$$

$$\begin{aligned} & 40j - 4ji_1 + 4ji_3 - 10i_1 + 10i_3 + 2ji_1 - 2ji_2 \\ & - 8i_1 + 8i_2 = 0 \end{aligned}$$

$$\begin{aligned} & i_1(-4j - 10 + 2j - 8) + i_2(-2j + 8) + i_3(4j + 10) + 40j = 0 \\ & i_3(-4j + 10) = 0 + 40j = 0 \end{aligned}$$

$$i_1(-18 - 2j) + i_2(8 - 2j) + i_3(4j + 10) + 40j = 0$$

$$-5i_2 - 8(i_2 - i_1) + 2j(i_2 - i_1) - 10(i_3 - i_1) - 4j(i_3 - i_1)$$


$$i_1(8 - 2j + 10 + 4j) + i_2(-5 - 8 + 2j) + i_3(-10 - 4j) = 0 - ②$$

$$i_2 + 3^2 i_3 - \textcircled{3} = 0$$

$$[i_2 - j8] A$$

$$[i_3 - 3 + j8] A$$

(Q)

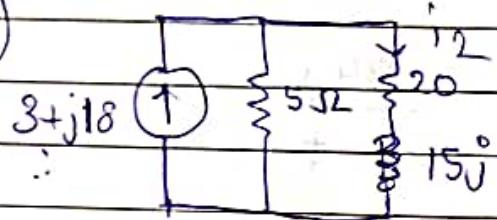


$$1.147 \angle 0.911^\circ$$

$$1.465 \angle 28.45^\circ$$

$$\left\{ \begin{array}{l} i_2 = 0.465 \angle 6.11^\circ \\ i_2 = 0.465 \angle 6.11^\circ \end{array} \right.$$

HW

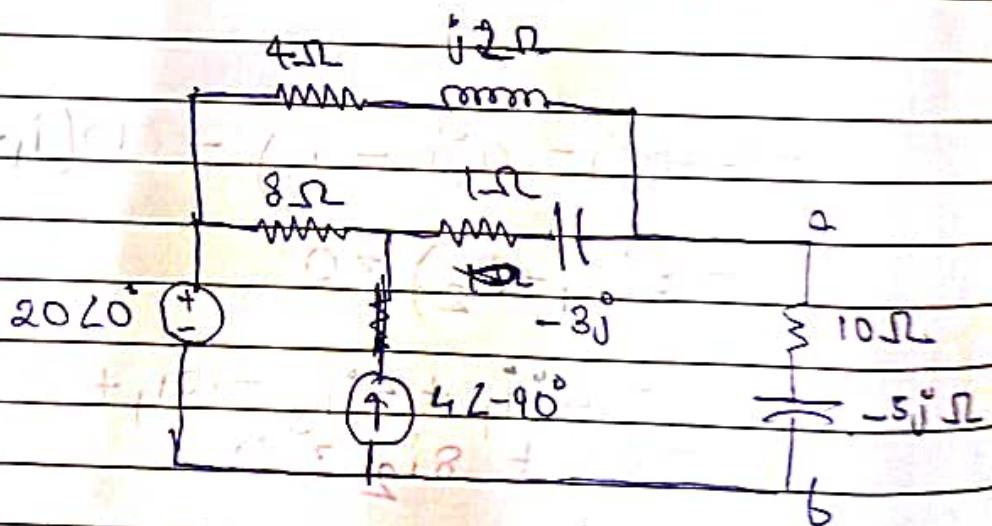

$$Z_N = 3.14 + j0.7\Omega$$

$$I_N = 8.39 \angle -32.68^\circ A$$

$$i_o = 1.97^\circ \angle -2.1 A$$


Instantaneous Power $P = VI$

Average or Real Power in Watts is the average of instantaneous power, $P = \frac{1}{T} \int_0^T P \cdot dt$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

Max Avg Power Transfer

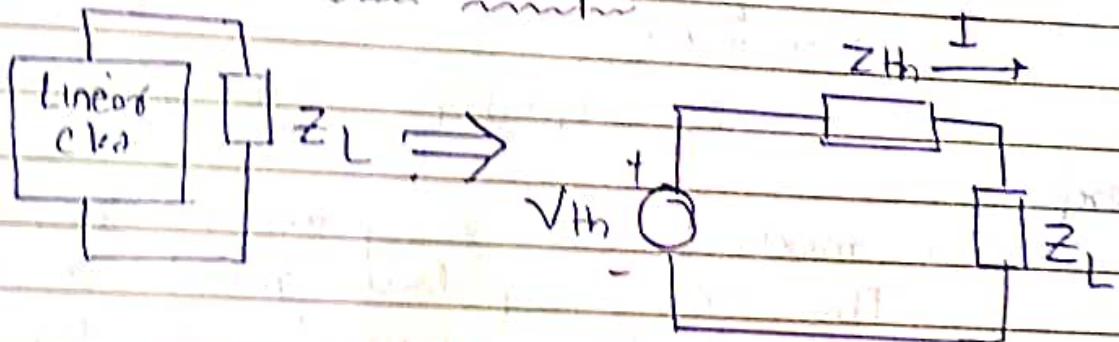

For the above circuit let $Z_{th} = R_{th} + jX_{th}$
 $Z_L = R_L + jX_L$

The current through the load is $I = \frac{V_{th}}{Z_{th} + Z_L}$

$$\left[I = \frac{V_{th}}{(R_{th} + R_L) + j(X_{th} + X_L)} \right] = \frac{V_{th}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}} = |I|$$

The average power delivered to the load is

$$P = \frac{1}{2} |I|^2 R_L$$

$$\left\{ P = \frac{V_{th}^2 R_L}{2[(R_{th} + R_L)^2 + (X_{th} + X_L)^2]} \right\}$$

$$\frac{dP}{dX_L} = -\frac{V_{th}^2 R_1 \cdot 2(X_{th} + X_L)}{\left[(R_{th} + R_L)^2 + (X_{th} + X_L)^2\right]^2} = 0 \Rightarrow X_{th} + X_L = 0$$

$$\{ X_{th} = -X_L \}$$

$$\frac{\partial P}{\partial R_L} = 0 \Rightarrow R_L = \sqrt{R_{th}^2 + (X_L + X_{th})^2} \quad (A)$$

\therefore To meet requirements of avg. power results in

$$\{ \text{put this in } (A) \} \quad X_L = -X_{th} \quad \text{and} \quad R_L = R_{th}, \text{ i.e.}$$

$$Z_L = R_L + jX_L = R_{th} - jX_{th} = \overline{Z}_{th} \text{ or } Z_{th}^+$$

Therefore,

For maximum average power transfer,


The load impedance must be equal to the complex conjugate of the thevenin's impedance Z_{th} .

$\therefore \boxed{P_{max}}$

$$P_{max} = \frac{(V_{th})^2}{8R_{th}}$$


No capacitor/inductor consumes power.

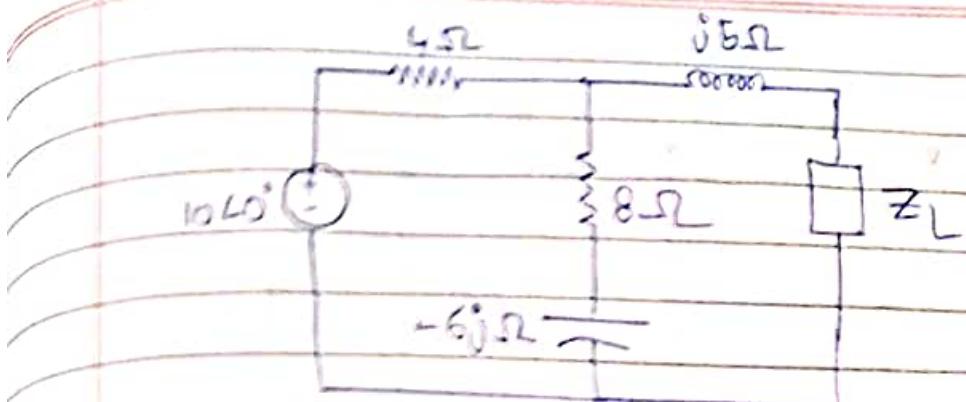- (Q) Determine the load impedance Z_L that maximized the average power from the circuit. Also calculate the maximum average power.



(Q2)

$$Z_{eq} = 2.933 + 4.467j$$

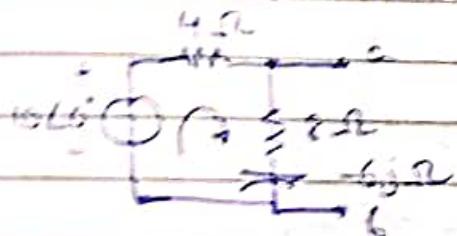

$$V_{th} = ?$$

$$10 - 4i - (8 - 6j)i = 0$$

$$\frac{10}{4} = 2.5$$

$$4j \quad 12 - 6j$$

$$i = 0.667 + 0.333j$$


$$V_{th} = V_{ab} = i \times Z(8 + 5j)$$

$$\left\{ Z_L = Z_{th} = 2.933 - 1.33j \right\} \rightarrow 7.449 \angle -10.28^\circ V$$


$$Z_{th} = R_{th} \quad P = \frac{(V_{th})^2}{R_{th}}$$

$$= \frac{9 \times 10^{-6}}{(7.449)^2}$$

$$\left\{ P_{th} = 2.317 W \right\}$$

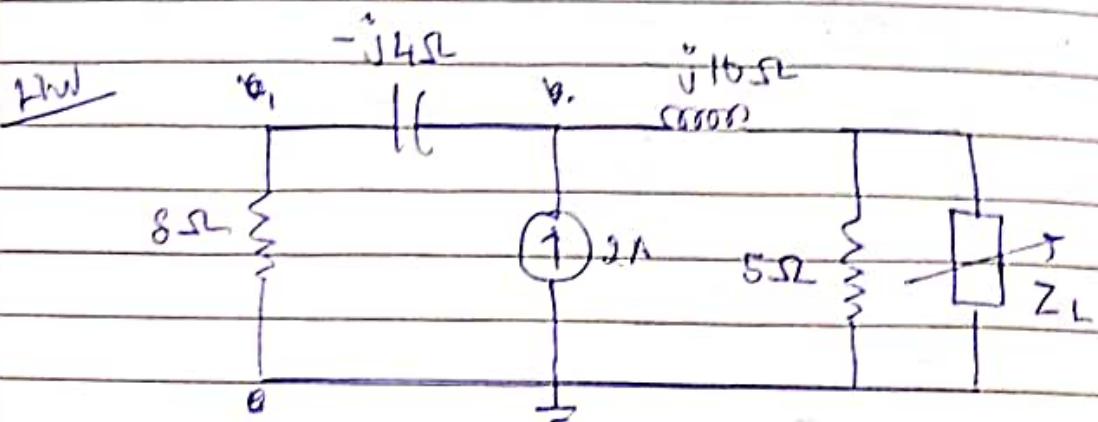




$$Z_{th} = (3.415 + 0.732j) \Omega$$

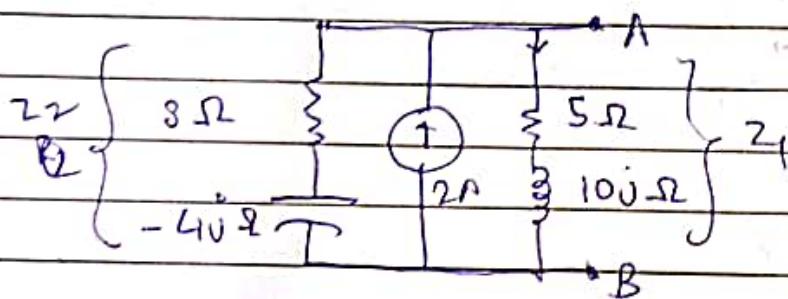

$$\begin{aligned} V_{th} &= V_{AB} = i_{AB} \times (5 + 10j) \\ &= \left(\frac{B \cdot Z_2}{Z_1 + Z_2} \right) \times i_T \times (5 + 10j) \end{aligned}$$

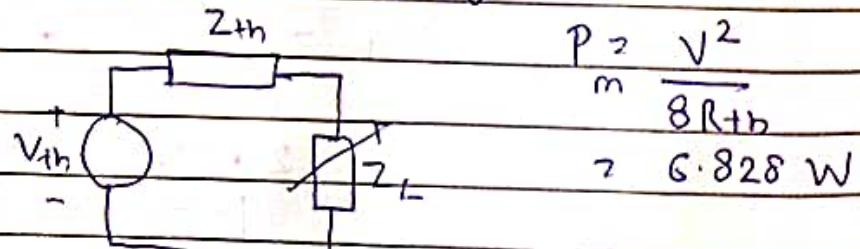
$$V_{th} = 13.658 + 2.926j \approx 13.967 \angle 12.091^\circ$$



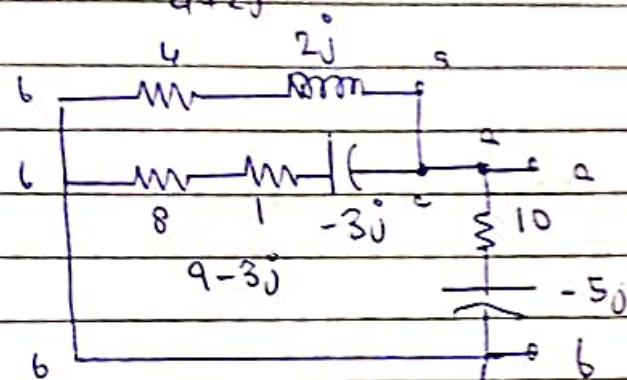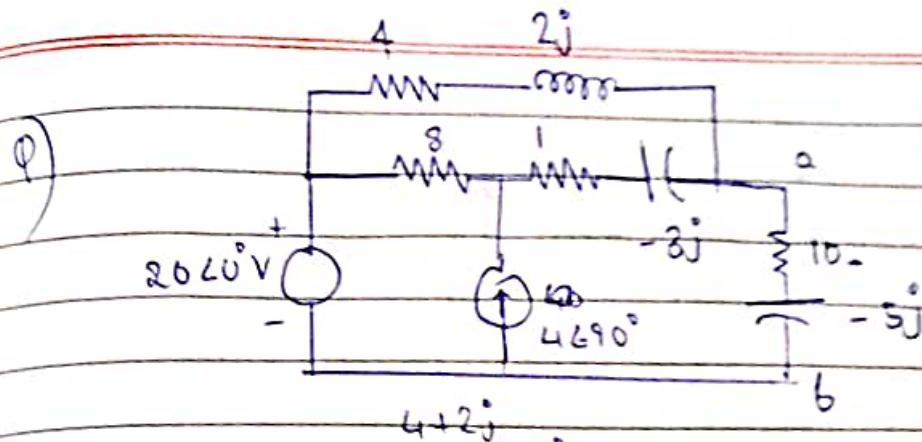

$$Z_{ab} = Z_N = (4+2j)(1)(9-3j)(1)(10-5j)$$

~~$$Z_N = 2.618 + 0.184j$$~~

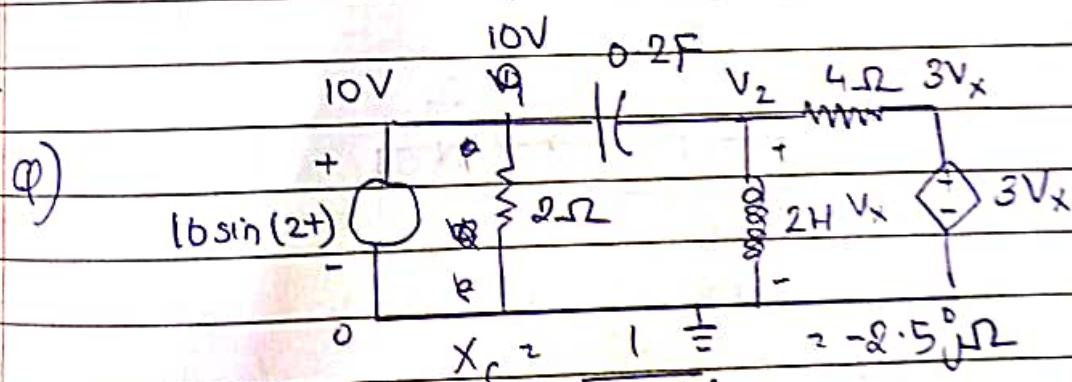

$$X_L = 2 \times 2 = 4j\Omega$$

$$\{ V_1 = 10V \}$$



$$\frac{V_1}{2} (-0.5 + 0.15j) = 4j \quad \frac{10}{2} = 5 \quad \frac{V_2 - 10}{2} + \frac{V_2 - 0}{4j} + \frac{V_2 - 3V_x}{4} = 0$$

$$\frac{V_2}{2} j - 4j + \frac{V_2}{4j} - \frac{V_2}{2} = 0 \quad V_2 = V_x$$

$$V_2 = 2.201 - 7.33j \quad \frac{V_2}{4} + \frac{V_x}{4} - \frac{V_2}{2} = 0$$


$$0.15V_2 = 4 \quad \{ V_2 = 26.67V \}$$

(q)

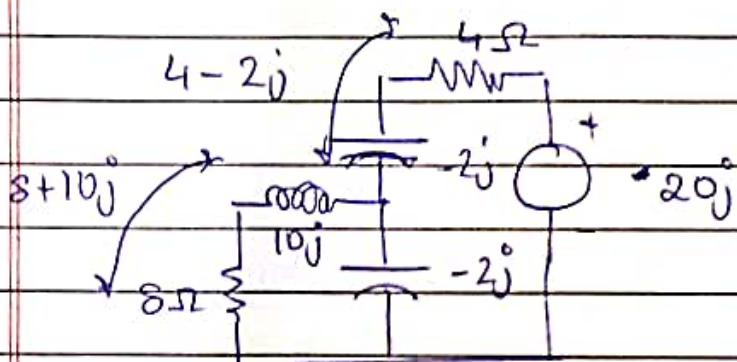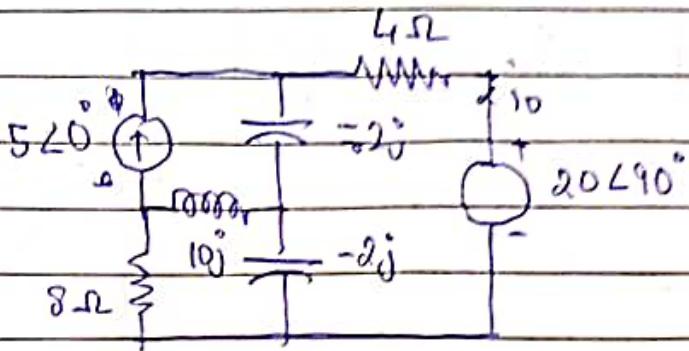

$$Z_{Req} = 4 \cdot 2.5 - 4 \cdot 2.5j$$
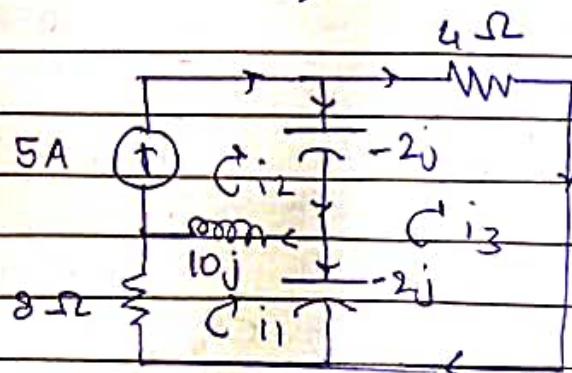
$$i_0' = \frac{20j}{Z_{Req}} = -2.35 + 2.35j$$



$$-8i_1 - 10j(i_1 - i_2) + 2j(i_1 - i_3) = 0$$

$$-8i_1 - 10j i_1 + 10j i_2 + 2j i_1 - 2j i_3 = 0$$

$$(-8 - 8j)i_1 + 10j i_2 - 2j i_3 = 0 \quad \text{--- (1)}$$

$$i_2 = 5A \quad \text{--- (2)}$$

$$(8 - 8j)i_1 - 2j i_3 = -50j \quad \text{--- (3)}$$

$$-4i_3 + 2j(i_3 - i_1) + 2j(i_3 - 5) = 0$$

$$-4i_3 + 2j i_3 - 2j i_1 + 2j i_3 - 10j = 0$$

$$i_3(-4+8j) = 2ji_1 + 10j \rightarrow \textcircled{4}$$

$$\begin{array}{c} -(8+8j) \\ - (4+4j) \end{array} \begin{array}{c} -2j \\ -2j \end{array}$$

$$\begin{bmatrix} -(8+8j) & -2j \\ -2j & -(4+4j) \end{bmatrix} \begin{bmatrix} i_1 \\ i_3 \end{bmatrix} = \begin{bmatrix} -50j \\ 10j \end{bmatrix}$$


$$\begin{aligned} \Delta_0 &= 8(1+j) \cdot 4(1+j) - (-2j)(-2j) \\ &= 32(1+j)^2 - (4j^2) \\ &= 32(1+2j-j^2) - 4 \\ &= 32(1+2j+1) - 4 \\ &= 32(2+2j) - 4 \\ &= 64 + 64j - 4 \\ &= 60 + 64j \end{aligned}$$

$$\Delta_2 = \left| \begin{array}{cc} \Delta_0 & \\ \hline -(8+8j) & -50j \\ -2j & 10j \end{array} \right| = 180 - 80j$$

$$\Delta_1 = \left| \begin{array}{cc} -50j & -2j \\ 10j & -(4+4j) \end{array} \right| = -220 + 200j$$

$$i_3 = \frac{i_1}{\Delta_0} = \frac{i_3}{\Delta_2} = \frac{\Delta_2}{\Delta_0} = -1.085 - 2.88j$$
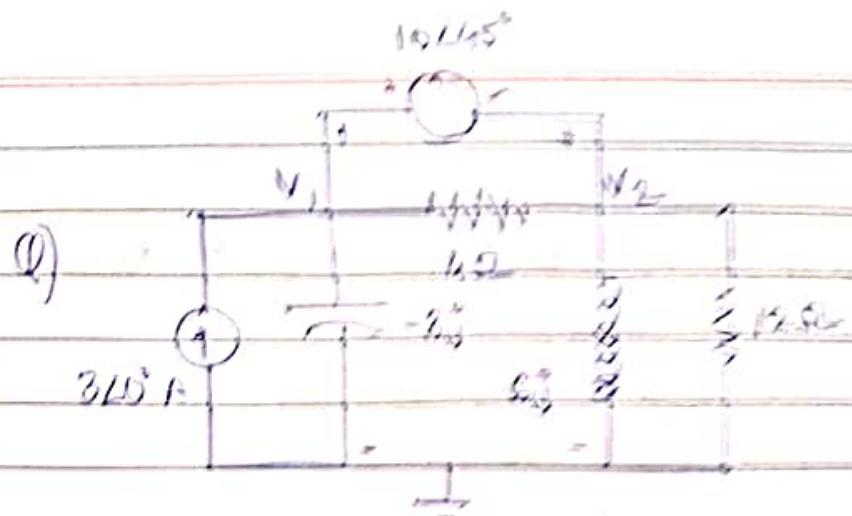
$$\begin{aligned} i_0 &= i_0 + i_0 \\ &= -3.39 - 0.53j \\ &= 3.43 \angle 171^\circ \end{aligned}$$



$$-3 + \frac{V_1}{2j} + \frac{V_1 - V_2}{4} + \frac{V_1}{12} = 0$$

$$\cancel{\frac{V_2 - V_1}{4}} + \frac{V_2}{6j} + \frac{V_2}{12} - \cancel{\frac{V_1}{12}} = 0$$

$$-3 + \frac{V_1}{2j} + \frac{V_2}{6j} + \frac{V_2}{12} = 0$$

$$-3 + \frac{V_{1j}}{2} - \frac{V_{2j}}{6} + \frac{V_2}{12} = 0$$

$$-36 + 4V_{1j} - 2V_{2j} + 8V_2 = 0$$

$$V_2(1-2j) + V_1(-j) = 36 \quad \textcircled{1}$$

$$V_1 - (7.07 + 7.07j) - V_2 = 0$$

$$V_1 - V_2 = 7.07 + 7.07j \quad \textcircled{2}$$

$$(1-2j)V_1 - (1-2j)V_2 = 21.21 - 7.07j \quad \textcircled{3}$$

$$(1-2j+4j)V_1 = 57.21 - 7.07j$$

$$V_1 = 8.614 - 24.298j$$

$$= 25.78 \angle -70.4^\circ$$

Exam Pattern

(1) Nodal/Mesh Analysis — [supermesh
supernode]


9 10

(2) Superposition/Thevenin/Max. Power

10

AC extre

+ Phasor Analysis (Add, multiply)

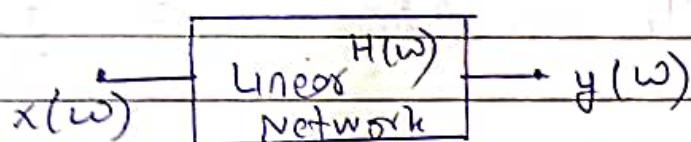Frequency Response Analysis

* The frequency response of this circuit is the variation in its behaviour with the change in input signal frequency.

* The frequency response analysis is very significant in communication systems and control systems.

* Filters Applications are in filters, TV, radio etc.

The transfer function $H(\omega)$ also called network function is a useful tool for finding frequency response of ckt. It can be expressed as

$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

Since the input and output variable be voltage or current, therefore the possible transfer function

$$H(s) = \text{Voltage gain} = \frac{V_o(s)}{V_i(s)}$$

$$H(s) = \text{Current gain} = \frac{I_o(s)}{I_i(s)}$$

$$H(s) = \text{Transfer impedance} = \frac{V_o}{I_i(s)}$$

$$H(s) = \text{Transfer Admittance} = \frac{I_o}{V_i(s)}$$

Transfer function $H(s)$ can be expressed in terms of its numerator polynomial $N(s)$ and denominator polynomial $D(s)$

$$\left\{ H(s) = \frac{N(s)}{D(s)} \right\}$$

The roots of $N(s) = 0$ are called zeros of the system.

The roots of $D(s) = 0$ are called poles of the system.


Frequency at which overall frequency of system becomes zero is called zero of system.

Frequency at which overall frequency of system becomes ∞ is called pole of system.

A Zero is a value that results in zero value of the function.

A pole is a value of that results in the function as ∞ .

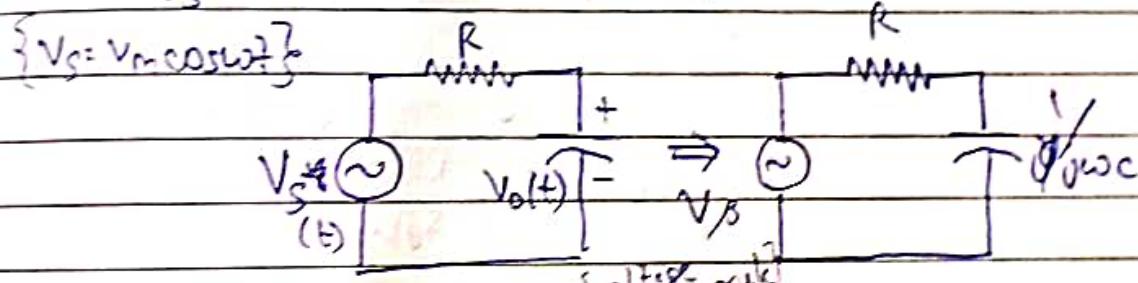Q2: For the R-C circuit, obtain a transfer function $\frac{V_o}{V_s}$ and its frequency response.





$$H(\omega) = \frac{V_o}{V_s} = \frac{1}{R + j\omega C}$$

where $\omega_0 = \frac{1}{RC} = \frac{1}{1 + j\omega_0 C}$

$$H = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}} \angle -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

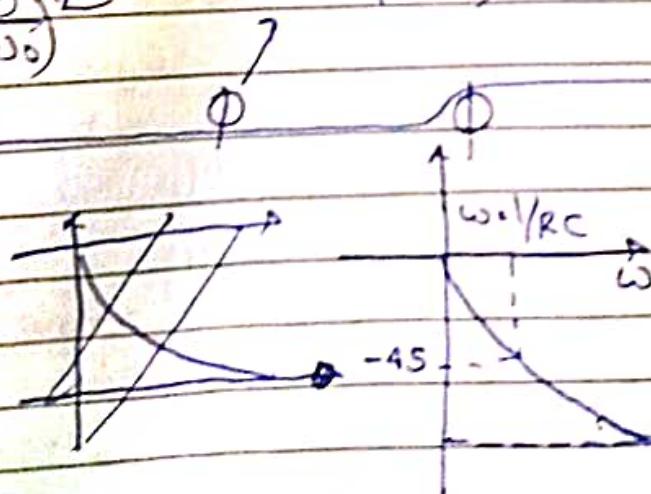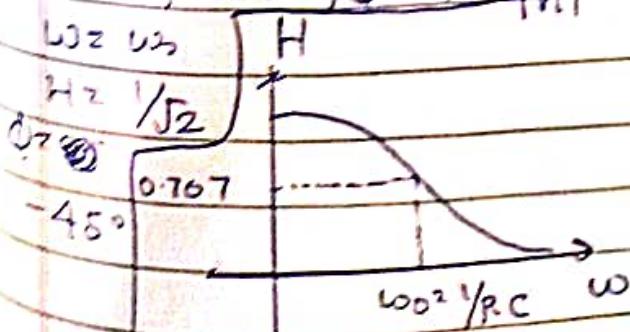
$\omega=0, H=1, \phi=0$
 $\omega=\infty, H=0, \phi=-90^\circ$



{cutoff frequency}

Ans.

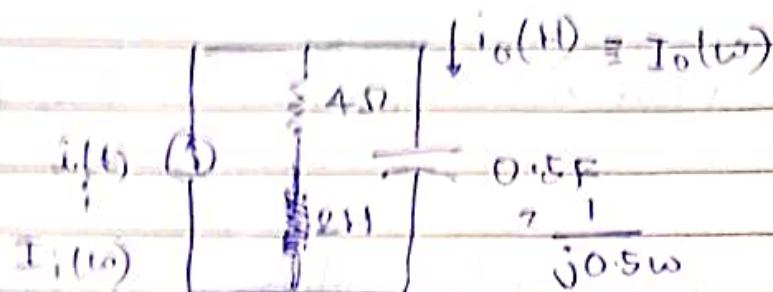For the C(s), $I_0(s)$ and its poles and zeroes
 $I_0(s)$



$$I_0(s) \propto \frac{V_0}{j0.5s}$$

$$I_i(s)$$

$$\frac{4 + j2s}{4 + 0.5js + 1} \times I_i(s)$$

$$I_i(s)$$

$$(4 + 2js)(0.5js)$$

$$2js + \omega^2(j)^2 + 1$$

$$\text{Transfer function} \quad \frac{2js - \omega^2}{2js - \omega^2 + 1} = \frac{2js - \omega^2}{2js - s^2 + 1}$$

$$N(s) = 0$$

$$2js - \omega^2 = 0$$

$$\omega = 0 \text{ or } \omega = 2j$$

$$D(s) = 0$$

$$2js - \omega^2 + 1 = 0$$

$$\omega^2 - 2js + 1 = 0$$

$$(\omega - 1)^2 = 0$$

$$\omega^2 - j\omega - i\omega - 1 = 0$$

$$\omega = \pm 1$$


$$j\omega = s$$

$$(s + j5)(s - 3j5) \rightarrow \frac{2s + 3^2}{2s + 3^2 + 1}$$

$$2s + 3^2 = 0 \quad (20+0j)$$

$$s^2 + 2s + 1 = 0$$

$$s = -1, -1 \quad (\text{poles})$$

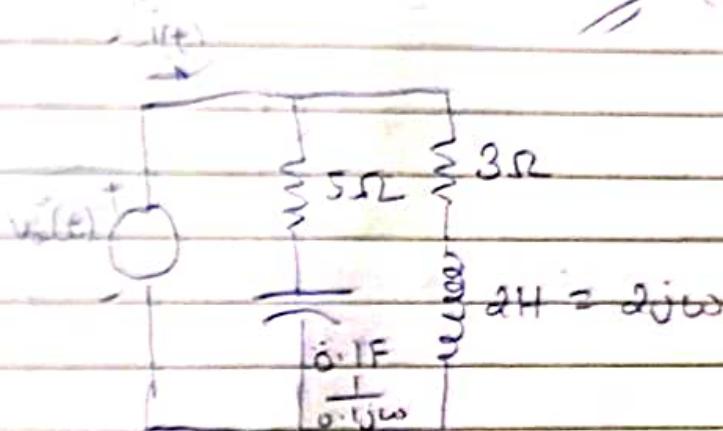

$$\text{TF} = \frac{V_o(t)}{i(t)} = \frac{(3 + 2j\omega)(s + \frac{1}{0.1\omega})}{3 + 2j\omega + 5 + \frac{1}{0.1\omega}} \times I(t)$$

$$j\omega = s$$

$$= (3 + 2s)(s + \frac{10}{s})$$

$$3 + 2s + s + \frac{10}{s}$$

$$s^2 + 10s + 35s + 10 = 0$$

$$= 15 + \frac{30}{s} + 10s + 20 \quad s^2 - 7 \pm \frac{\sqrt{33}}{4}$$

$$3 + 2s + s + \frac{10}{s}$$

$$s^2 + 2s + 8s + 10 = 0$$

$$0 \quad 35s + 30 + 10s^2$$


$$s = -2 \pm j$$

Date: 17/10/2022

Filters

→ Passive Filters

→ Active Filters

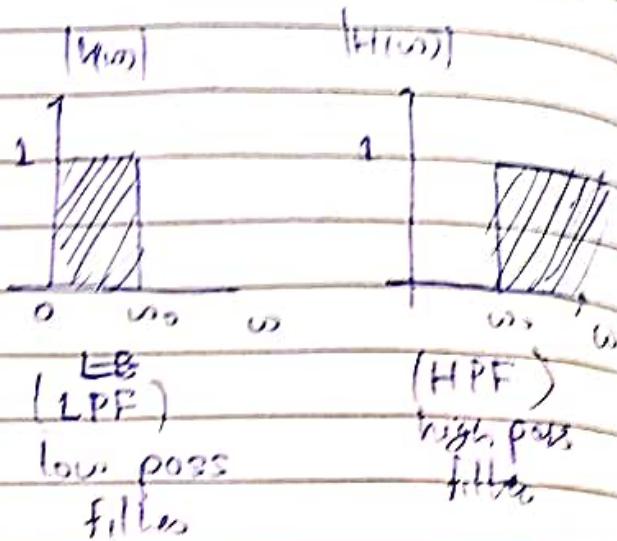

(BPF) Band pass filter

(BSF) $\omega_1 \omega_2$
Band stop filter

Passive Filters

A filter is a circuit that is designed to pass the signals of ^{with} desired frequencies and attenuate other frequencies.

A filter is a passive filter which consists of only RLC elements.

Active filter consists of active elements such as operational amplifiers, transistors, etc.


Design of Low Pass filter

A low pass filter is formed when output of RC circuit is taken of the capacitor.


Transfer function

$$H(\omega) = \frac{V_o(\omega)}{V_i(\omega)}$$

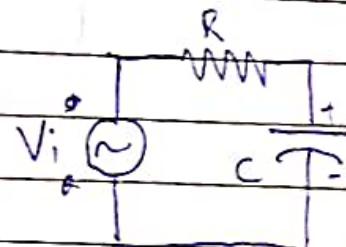
$$= \frac{1/j\omega C}{R + 1/j\omega C}$$



$$H(0) = 1, \quad H(\infty) = 0$$

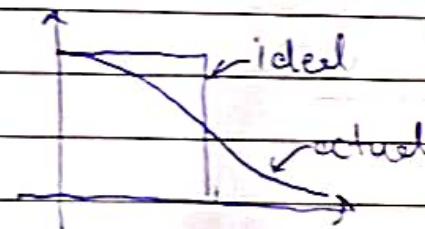

L.P.F

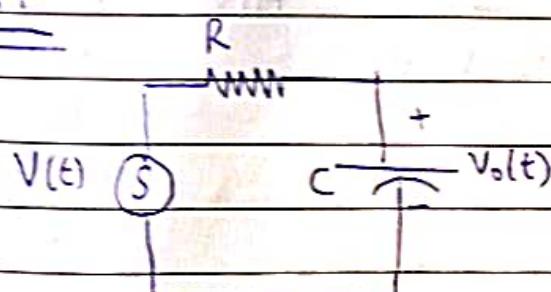

$$H(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{1/j\omega C}{R + 1/j\omega C}$$


$$H(\omega) = \frac{1}{1 + \omega^2 CR^2}$$

$$|H(\omega)| = 1$$

$$|H(\infty)| = 0$$

$$H(\omega_2) = \frac{1}{\sqrt{1 + 8R^2C^2}}$$
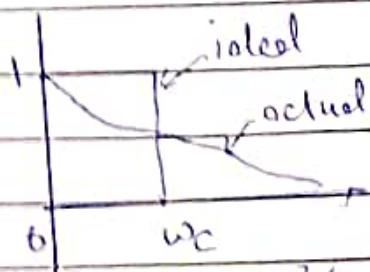
$$\omega_2 = \frac{1}{RC} \sqrt{\frac{1}{2}}$$



$$P = V^2/R \quad (\text{crossed out})$$

when $\omega = \omega_c$

$$P = \frac{0 \cdot \left(\frac{1}{\sqrt{2}}V\right)^2}{R} = \frac{1}{2} \frac{V^2}{R}$$


$$= 0.5P$$

$\omega_c \rightarrow$ half power frequency
OR

- cut-off frequency

This is Low Pass Filter.

HPF:

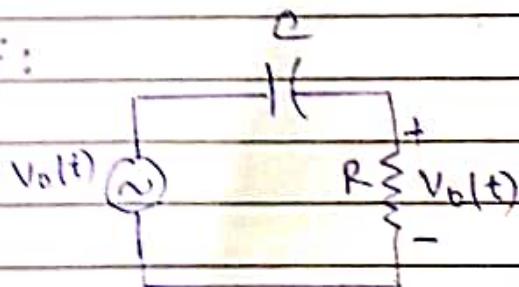


$$\begin{aligned} H(\omega) &= \frac{V_o(\omega)}{V_i(\omega)} \\ &= \frac{R}{R + \frac{1}{j\omega C}} \end{aligned}$$

$$A(\omega) = \frac{R j \omega C}{R j \omega C + 1}$$

$$\begin{aligned} H(0) &= 0 \\ H(\infty) &= 1 \end{aligned}$$


$$\omega_c = \frac{1}{RC}$$

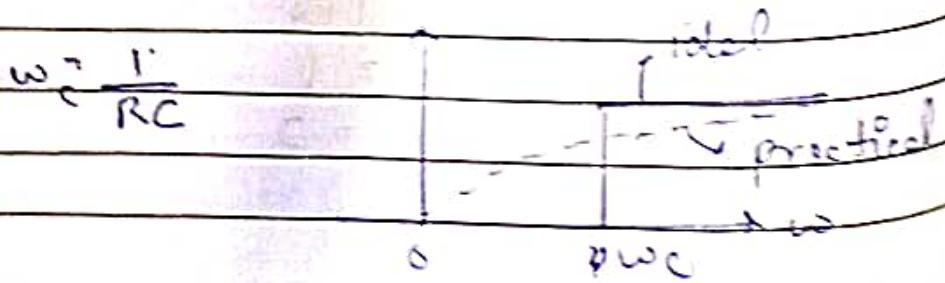

★


A low pass filter can also be formed of an R-L ckt by taking output across resistor.

A high pass filter can also be formed by taking output across the inductor.

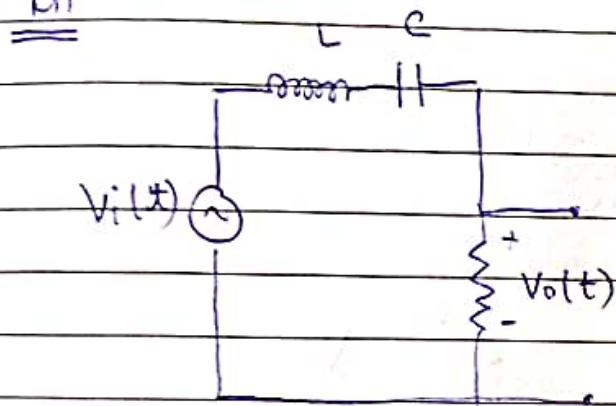BPF

$$\begin{aligned} H(\omega) &= \frac{V_o(\omega)}{V_i(\omega)} \\ &= \frac{R}{R + j(\omega L - \frac{1}{\omega C})} \end{aligned}$$

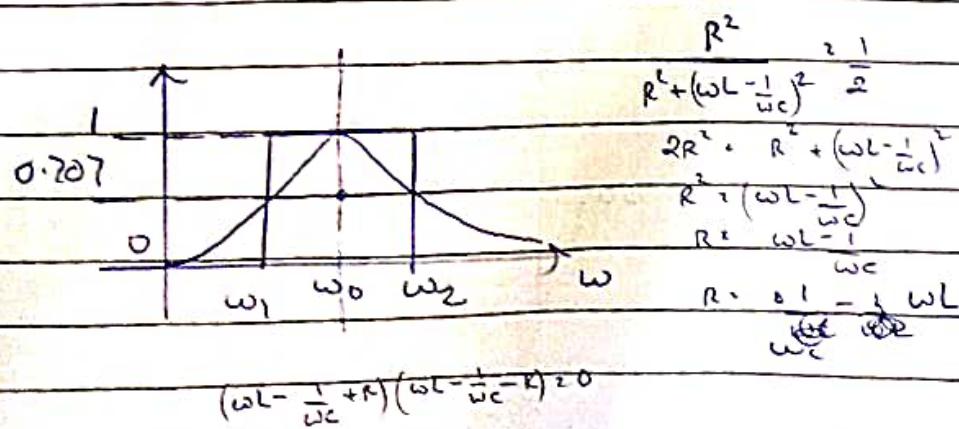BPF passes a band of freq. ($\omega_1 < \omega < \omega_2$) centered on ω_0 , when ω_0 is a resonant frequency




$$\omega_1 = \frac{-R + \sqrt{(R)^2 + \frac{1}{LC}}}{2L} \quad \text{This is}$$

Band pass
Filter

$$\omega_2 = \frac{R + \sqrt{(R)^2 + \frac{1}{LC}}}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

BPF / Notch Filter

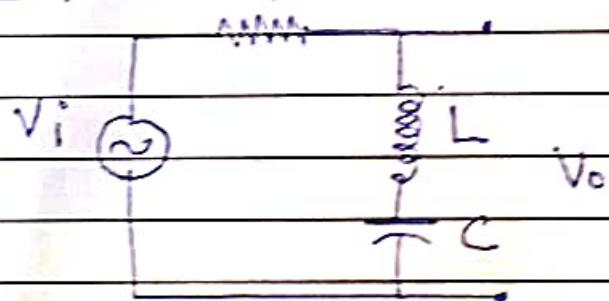


$$H(j\omega) = \frac{V_o}{V_i} = j \left(\frac{\omega L - 1}{\omega C} \right)$$

$$= \frac{R + j(\omega L - 1)}{j(\omega L - 1 + \frac{1}{\omega C})}$$

$$\Rightarrow H(0) = 1$$

$$H(\infty) = 1$$

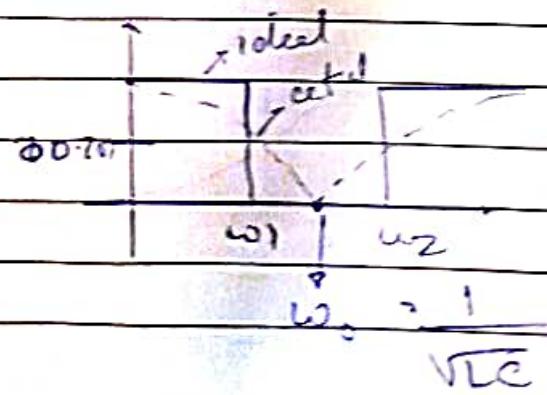


At corner frequency $|H(\omega)| = \frac{1}{\sqrt{2}} H(\omega_c)$

PAGE NO.:

DATE: / /

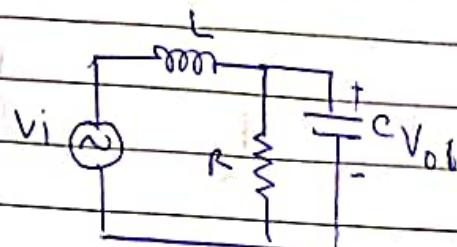(Q) Determine the type of filter shown in the figure. Also calculate the cutoff frequencies.



$$L = 2\pi$$

$$R = 2k\Omega$$

$$C = 2\mu F$$

$$s = j\omega$$

$$H(\omega) = \frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{R}{j\omega C} \right)^2 + \left(\frac{j\omega L}{R} - \frac{1}{j\omega C} \right)^2}}$$

$$\left. \begin{aligned} H(\omega) &= 1/\sqrt{2} \\ \text{To find } \omega_c &\text{ corner frequency} \end{aligned} \right\}$$

$$\frac{R \times 1}{s + \frac{1}{RC}} = \frac{R}{s + \frac{1}{RC} + \frac{1}{sL}}$$

$$s + \frac{1}{RC}$$

$$sL + \frac{1}{sC}$$

$$sL + \frac{1}{sC}$$

$$sL + \frac{1}{sC}$$

$$\frac{RSC + 1}{sC}$$

It is a
low pass

filter

$$\frac{(RSC + 1)^2}{s^2 RLC + sL + R}$$

$$(RSC + 1)sL + R$$

$$(RSC + 1)$$

$$H(\omega) = \frac{H(0)}{1 + \frac{1}{s^2 RLC + sL + R}} \Big|_{\omega = \omega_c}$$

$$H(\infty) = 0$$

(P) Final type of filter and corner frequency.




$$\frac{H(\omega)}{V_i} = \frac{V_1}{V_i} = \begin{bmatrix} \frac{(j\omega L)R_2}{j\omega L + R_2} \\ \frac{R_1 + (j\omega L)R_2}{j\omega L + R_2} \end{bmatrix} V_1 \quad \omega j = s$$

$$\frac{V_1}{V_i} = \frac{\frac{sR_2L}{sL + R_2}}{\frac{R_1sL + R_1R_2 + sLR_2}{sL + R_2}} = \frac{sR_2L}{R_1sL + R_1R_2 + sLR_2}$$

$$H(\omega) = \frac{sR_2L}{R_1sL + R_1R_2 + sLR_2} = \frac{sR_2L}{s(L + R_1 + R_2)} = \frac{sR_2}{s(L + R_1 + R_2) + R_2}$$

$$H(0) = 0$$

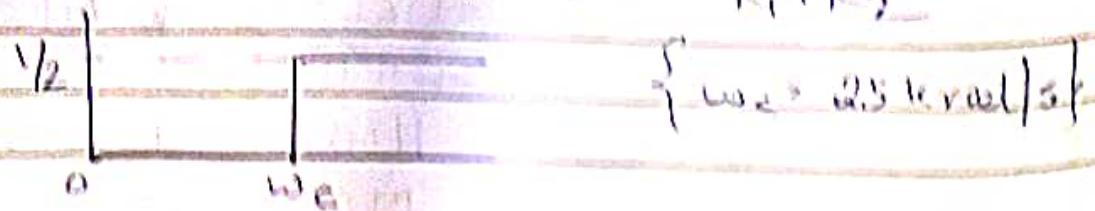
$$H(\infty) = \frac{R_2L}{R_1L + R_2L} = \frac{R_2}{R_1 + R_2} = \frac{1}{2}$$



Two - Port Network


A pair of terminals through which current can enter or leave is called as a port.

Pair of terminals

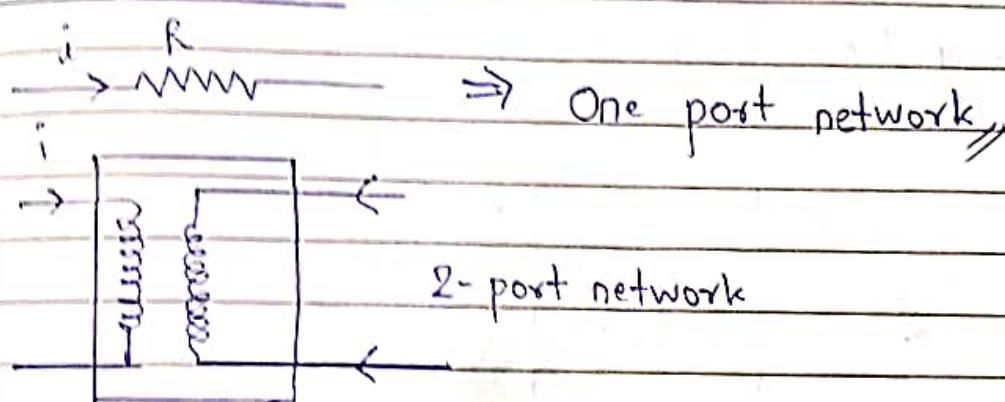

Two terminal devices ($R-L-C$) results in one port network.

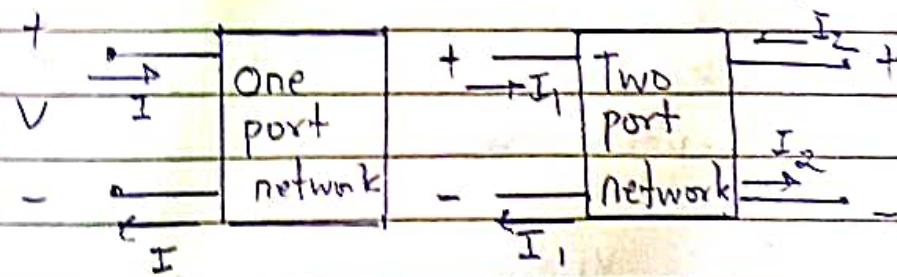
Two port network is a electric network having 2 separate ports for input and output.



Applications are : communication systems
control systems
Power system networks
etc..

The various terms that define voltage and current of a network are called parameters.
 e.g., $\frac{V_1}{I_1}$ = Resistance
 Z parameter

Impedance Parameters:

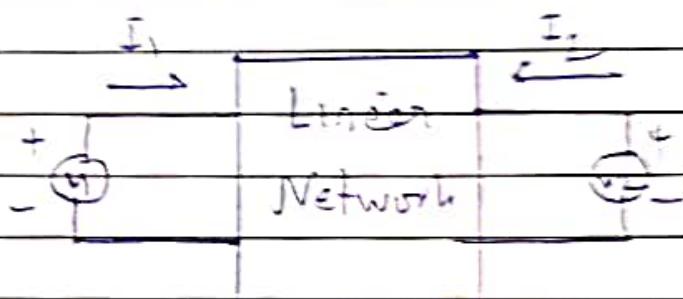

$$\begin{aligned} V_1 &= Z_{11} i_1 + Z_{12} i_2 \\ V_2 &= Z_{21} i_1 + Z_{22} i_2 \end{aligned}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = [Z] \begin{bmatrix} i \end{bmatrix}$$

When Z terms are called impedance parameters or Z -parameters.

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

open circuit input impedance

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$


o.c transfer impedance from port 1 to port 2

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{E_2=0}$$

o.c transfer impedance from port 2 to port 1


$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

o.c o/p impedance

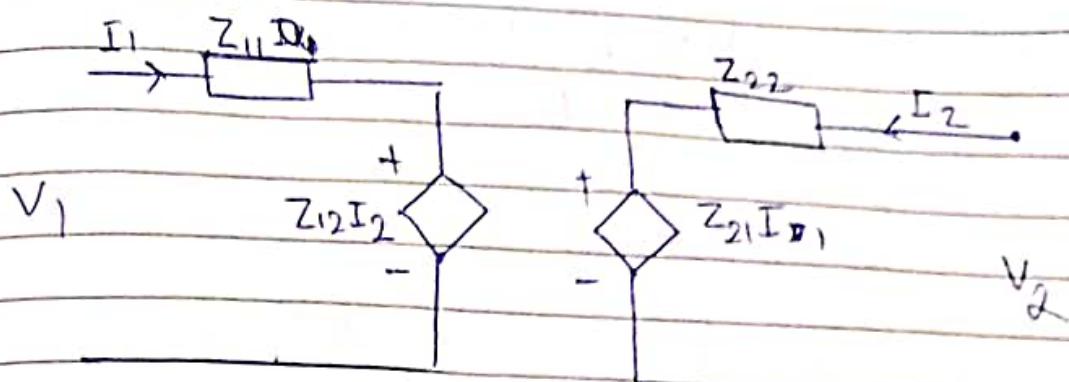

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

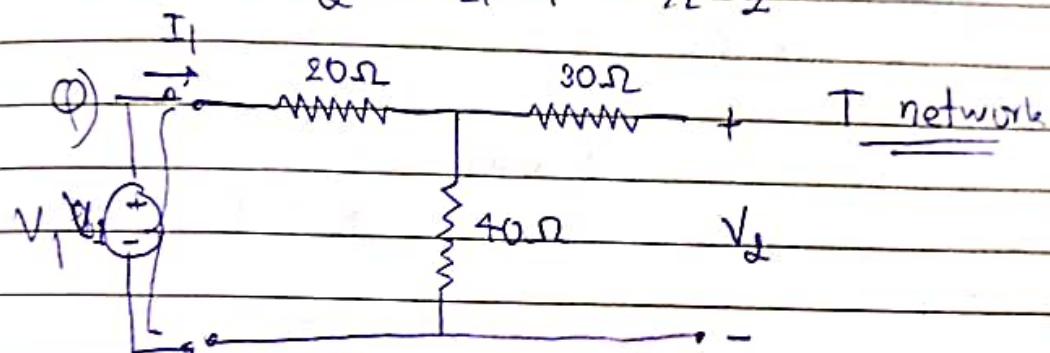

① To determine Z_{11} & Z_{21} apply a voltage source V_1 to the input nodes and keep the output load open circuited.

$$Z_{11} = \frac{V_1}{I_1} = \frac{(20+40)I_1}{I_1} = 60 \Omega$$

$$Z_{21}, \frac{V_2}{I_1} = \frac{40I_1}{I_1} = 40 \Omega$$


② To find Z_{12} & Z_{22} apply a voltage source V_2 to the output port and keep the input port open circuited

$$Z_{22} = \frac{4V_2/I_2}{I_2} = 40\Omega // 40\Omega$$

$$Z_{22} = \frac{(40+30)\Omega}{16}$$

$$= 70\Omega //$$
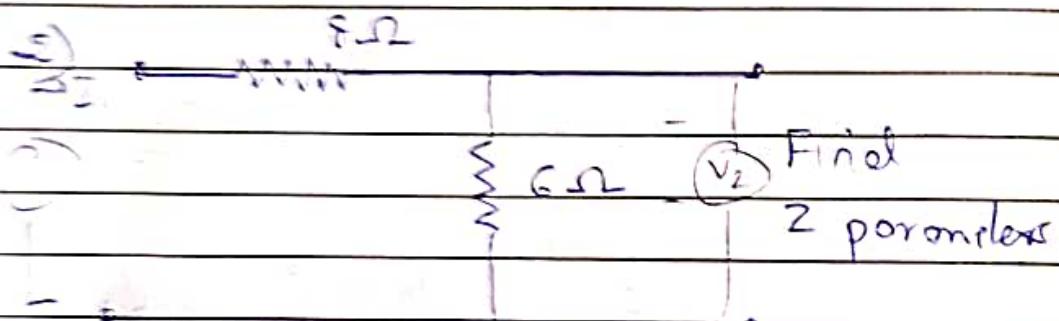
$$\boxed{Z = \begin{bmatrix} 60\Omega & 40\Omega \\ 40\Omega & 70\Omega \end{bmatrix}}$$



$$Z_{11} = \frac{V_1}{I_1} = 14\Omega$$


$$Z_{22} = \frac{V_2}{I_2} = \frac{6I_1}{I_2} = 6\Omega //$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{6I_2}{I_2} = 6\Omega //$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{6I_1}{I_1} = 6\Omega //$$

14	6
6	6

9)

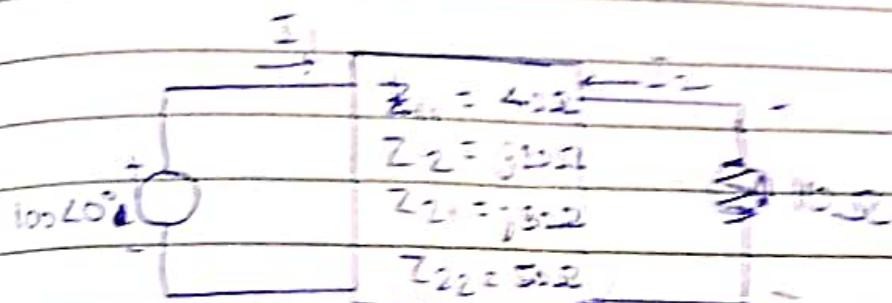Find i_1, i_2 & V_{ab} 

$$100 = 100 + 40 + 30 + 100$$

$$\frac{1}{100} = \frac{1}{40} + \frac{1}{30} + \frac{1}{100}$$

$$V_1 = Z_{11}i_1 + Z_{12}i_2$$

$$100 = 40i_1 + j20i_2 + 0j$$

$$V_2 = j30i_1 + 50i_2 = -10i_2$$

~~$500 = 200i_1 + 100i_2$~~

$$300 = 120i_1 + 60i_2 - ①$$

$$0 = 30j i_1 + 60i_2$$

$$0 = -30i_1 + 60i_2 - ②$$

 $\textcircled{1} \quad \textcircled{2}$

$$300 = 150i_1 + 0$$

$$i_1 = 2A \angle 0^\circ A$$



$$i_2 = \frac{30i_1}{60j} = \frac{1}{2} \angle -90^\circ A$$

$$= 1.5 \angle -90^\circ A$$

$$(I_1, I_2) \equiv (V_1, V_2)$$

$$\begin{cases} I_1 = Y_{11}V_1 + Y_{12}V_2 \\ I_2 = Y_{21}V_1 + Y_{22}V_2 \end{cases}$$

Admittance Parameters / Y parameters

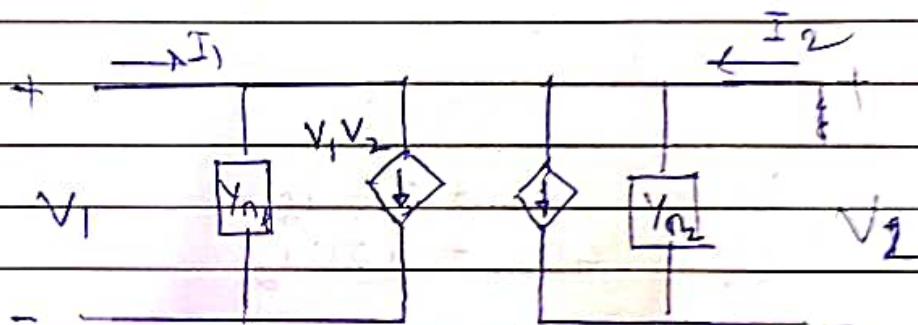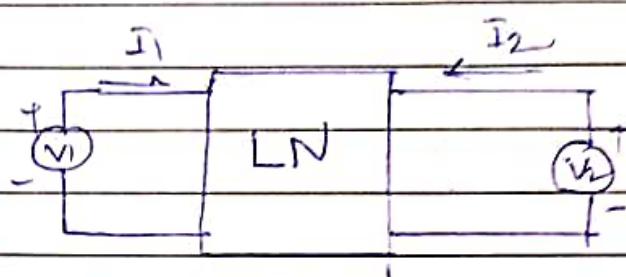

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \quad | \quad V_2 = 0$$

short ckt input
~~temp~~ admittance

$$Y_{12} = \frac{I_1}{V_2} \quad | \quad V_1 = 0$$


short ckt
~~short ckt~~ transfer
admittance from
port 1 to port 2

$$Y_{21} = \frac{I_2}{V_1} \quad | \quad V_2 = 0$$

short ckt transfer admittance
from port 2 to port 1

$$Y_{22} = \left| \begin{array}{c|c} I_2 & \\ \hline V_2 & V_1=0 \end{array} \right| \quad \text{Short circuit output admittance.}$$

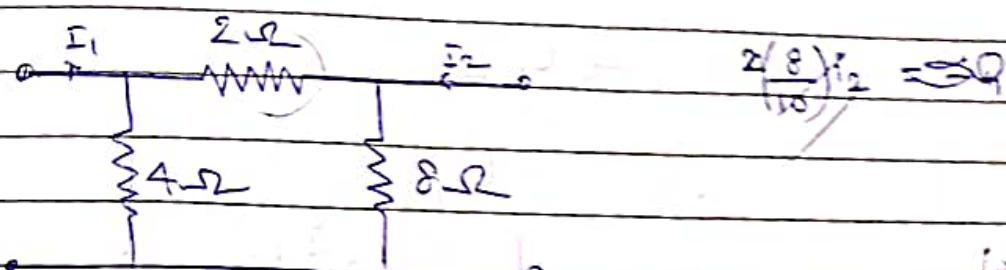(e) Obtain γ -parameters of the Π network



$$\frac{2(8)}{16} i_2 = 5\Omega$$

$$Z_{in} = Y_{11} = \frac{I_1}{V_1} = \frac{2}{1} = 2 \Omega$$

$$Z_{in} = ?$$

① To find Y_{11} & Y_{21} apply a current source I_1 to the input port and make the output port short circuited.

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{11} = I_1/V_1 = \frac{I_1}{(8/6)I_1} = 6/8 = 3/4 \Omega$$

$= 0.75 \text{ mho}$

$$Y_{12} = I_1/V_2 = \frac{I_1}{16 I_2} = \frac{10}{16} \Omega$$

$$Y_{21} = I_2/V_1 = I_2/V_1$$

$$I_2 = -4/6 I_1$$

$$= -4/6 \times 1/48/5 I_1 = -0.5 S$$

To get Y_{12} & Y_{22} short ckt the input port and apply a current source I_2 at the output.

$$Y_{12} = I_1/V_2$$

$$I_1 = -\frac{0.8}{10} I_2$$


$$\therefore Y_{12} = \frac{-0.8/10}{16/10} I_2$$

$$= -\frac{0.1}{2} S = 0.5 S$$

$$Y_{22} = I_2/V_2$$

$$= \frac{I_2/16}{10/I_2} = \frac{16}{10}$$

$$= 0.625 S$$

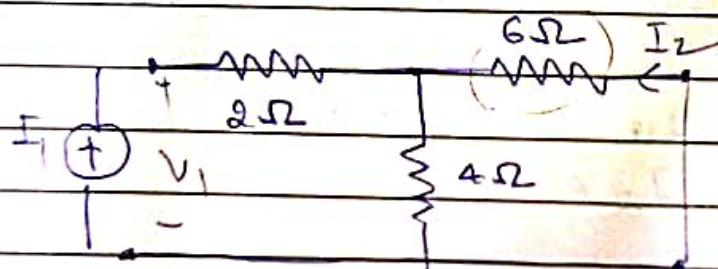

$$\frac{6 \times 4}{6+4} = \frac{24}{10} + 2 \\ = 4.4/10$$

$$Y_{11} = \frac{V_1}{I_1} = \frac{4.4 I_1}{10} = \frac{10}{44}$$

$$= 0.227 S$$

$$Y_{21} = \frac{I_2}{V_1}$$

$$= \frac{4}{10}$$

$$I_2 = -\frac{2}{5} I_1$$


$$Y_{21} = -\frac{2/5}{22.44/10} I_1 = -\frac{1}{11} S = -0.091 S$$

QUESTION
ANSWER


$$\log \frac{3}{2} = \frac{0.4771}{0.0109}$$

$$2 - 4 \times 10^{-4} = 1 - 10^{-4}$$
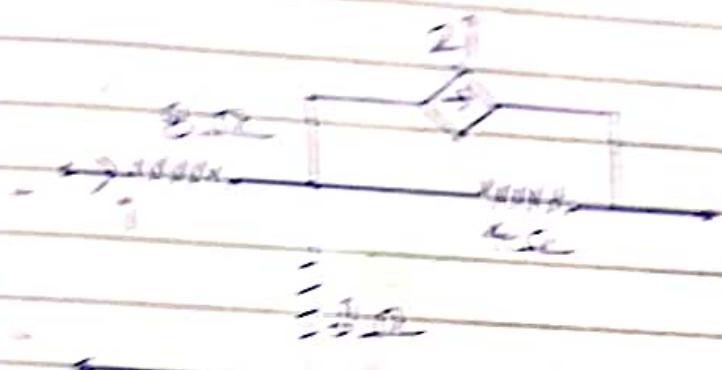
$$\log \frac{2}{3} = \frac{0.3010}{0.0109}$$



Q) Obtain S.C. parameters

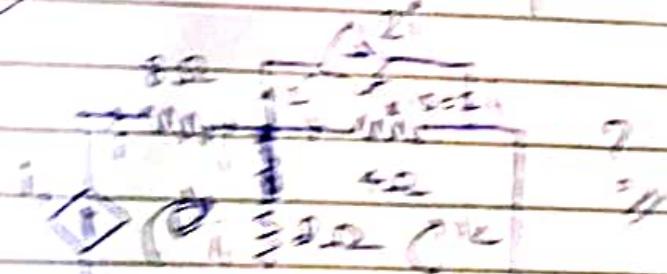

$$i_1 - 8i_3 - 2i_4 + i_2 = 0$$

$$i_2 - 7i_3 - 2i_4 + 5i_2 = 0$$

$$i_{12} = 3i_1 \quad \text{X}$$

$$-2(i_2 - i_1) - 4(i_2 - 2i_1) = 0$$

$$-2i_2 + 2i_1 - 4i_2 + 8i_1 = 0$$

~~$$6i_1 = 6i_2$$~~
$$\frac{i_1}{i_2} = 1$$

Hybrid Parameters

$$(V_1, I_2) = f(V_2, I_1)$$


$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \Rightarrow S.C \text{ I/p Impedance}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \Rightarrow O.C \text{ & reverse voltage gain}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \Rightarrow S.C \text{ forward current gain}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \Rightarrow O.C \text{ output admittance}$$

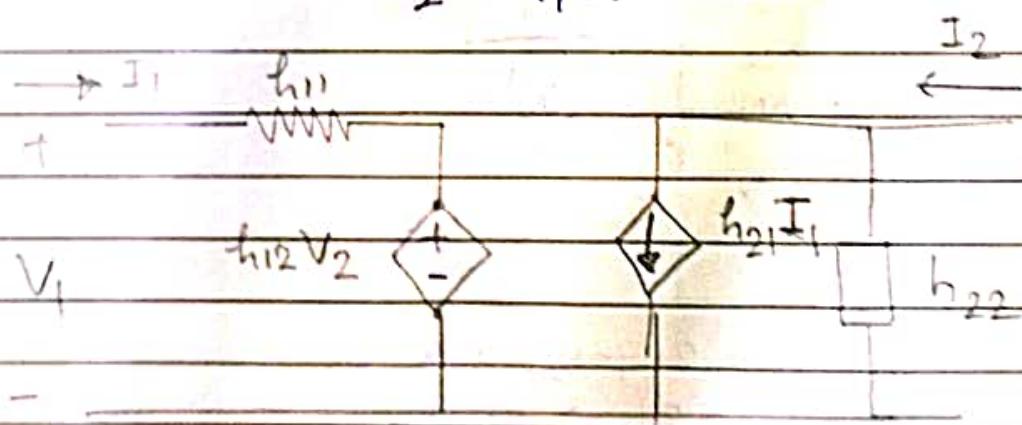

g-parameters

$$(I_1, V_2) = f(V_1, I_2)$$

$$I_1 = g_{11}V_1 + g_{12}I_2$$


$$V_2 = g_{21}V_1 + g_{22}I_2$$

$g_{11} \Rightarrow$ O.C i/p Admittance

$g_{12} \Rightarrow$ S.C Reverse current gain

$g_{21} \Rightarrow$ O.C forward volt gain

$g_{22} \Rightarrow$ S.C o/p impedance

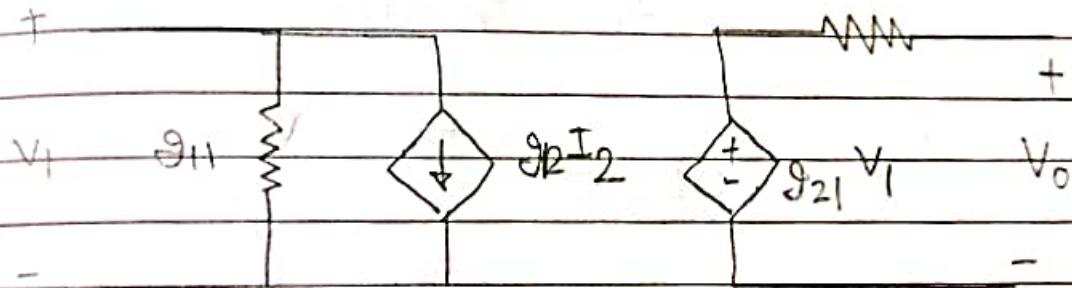

Q) Find the hybrid parameters



$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \frac{V_1}{I_1} = \frac{8 \times 2}{I_1} = 8 g_{11}$$

$$\frac{G_1 Z + 2}{S+3}$$

$$h_{11} = \left| \begin{array}{c} V_1 \\ I_1 \end{array} \right| = \frac{4I_1}{I_1} = 4 \Omega$$

$V_2 = 0$

$$h_{12} = \left| \begin{array}{c} V_1 \\ V_2 \end{array} \right| = \frac{4I_1}{9I_2}$$

$I_2 = 0$

$$\left\{ \begin{array}{l} C I_1 = -I_2 \\ 3+6 \\ I_2 = -2/3 I_1 \end{array} \right.$$

2

$$h_{12} = \frac{4I_1}{39(-2/3)I_1} = \frac{2}{3} \Omega$$


$$h_{21} = \left| \begin{array}{c} V_2 \\ I_1 \end{array} \right| = \frac{-2/3 I_1}{I_1} = -2/3 \Omega$$

$V_2 = 0$

$$h_{22} = \left| \begin{array}{c} I_2 \\ V_2 \end{array} \right| = \frac{I_2}{9I_2} = 1/9 \text{ mho/s}$$

$I_1 = 0$

① Find the g-parameter as a function of

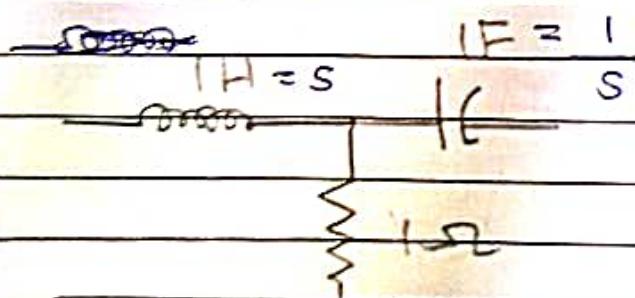

~~$$V_1 = g_{11}V_1 + g_{12}I_2$$~~

$$V_2 = g_{21}V_1 + g_{22}I_2$$

$$\begin{aligned} g_{11} &= \frac{I_1}{V_1} \Big|_{I_2=0} \\ &= \frac{I_1}{(s+1)I_1} = \frac{1}{s+1} \text{ into } S. \end{aligned}$$

$$g_{12} = \left. \frac{V_1}{I_2} \right|_{V_1=0} = \frac{I_1}{I_2} \Big|_{V_1=0}$$

$$I_2 = -\left(\frac{1}{1+s}\right) I_1$$

$$g_{12}^2 = \frac{-\frac{1}{1+s}}{\frac{1}{1+s}} = -\left(\frac{1}{1+s}\right)$$

$$\therefore I_1 = -\frac{1}{1+s} I_2$$

$$g_{21}^2 = \frac{I_1}{I_2} \Big|_{V_1=0} = \frac{1}{1+s}$$


$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} = \left(\frac{1}{1+s} \right) \cancel{I_2}$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} = \left(\frac{s+1}{1+s} \right) \cancel{I_2}$$

$$= \frac{s^2+s+1}{s^2+s} \text{ into } \Sigma_{11}$$

Transmission Parameters

$$(V_1, I_1) = f(V_2, -I_2)$$

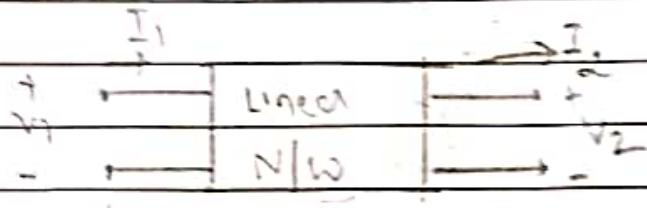

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \left| \begin{array}{c} V_1 \\ V_2 \end{array} \right| \quad \text{O.C. volt ratio}$$

$I_2 = 0$

$$B^2 = \left| \begin{array}{c} -V_1 \\ I_2 \end{array} \right| \quad \text{Negative S.C. impedance}$$

$V_2 = 0$


$$C = \left| \begin{array}{c} I_1 \\ V_2 \end{array} \right| \quad \text{O.C. Transfer admittance}$$

$I_2 = 0$

$$D = \left| \begin{array}{c} -I_1 \\ I_2 \end{array} \right| \quad \text{Negative S.C. current ratio}$$

$V_2 = 0$

H.W.

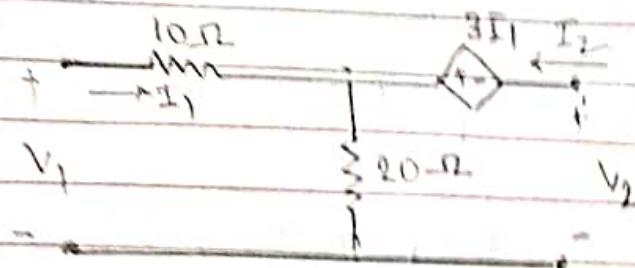

$$A = \left(\frac{20}{30} \right) V_2 + \frac{2}{3}$$

$$B = C = \frac{I_1}{V_2} = \frac{I_1}{\frac{30}{17} V_1} = \frac{I_1}{\frac{30}{17} \times 30 I_1} = \frac{1}{45}$$


~~B~~ $V_1 = 30 I_1$

~~V~~
~~V₁~~

$$V_2 = 20 I_1 - 3 I_1$$

$$V_2 = 17 I_1$$
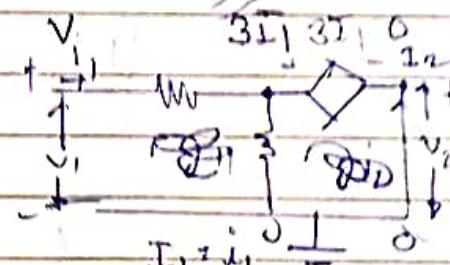
$$A = \frac{V_1}{V_2} = \frac{30}{17} = 1.76$$



$$C = \frac{I_1}{V_2} = \frac{I_1}{17 I_1} = \frac{1}{17}$$

To get B & D short ckt o/p and apply voltage source at i/p

$$B = -\frac{V_1}{I_2} = -\frac{13 I_1}{-17 I_1 / 20}$$

$$\cancel{B} = \frac{V_1 - 3 I_1}{10} = I_1 = \frac{20 \times 13}{17} \text{ mV}$$

$$V_1 = 13 I_1$$

$$\cancel{B} = \frac{3 I_1}{20} = i' \quad \text{and } I_2 + I_1 = i'$$

$$I_2 = \frac{3 I_1}{20} - I_1 = -\frac{17 I_1}{20}$$

Relationship between Parameters

Given the Z -parameters, let us obtain the Y parameters.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [Z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [Z]^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{--- (1)}$$

We know that,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [Y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{--- (2)}$$

$$\therefore \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [Y]^{-1} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[Y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [Z]^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\therefore [Y] = [Z]^{-1}$$

$$[Z]^{-1} = \frac{1}{Z_{11}Z_{22} - Z_{12}Z_{21}} \begin{bmatrix} Z_{22} - Z_{12}Z_{21} \\ -Z_{21} & Z_{11} \end{bmatrix}$$

$$\Delta_2 = Z_{11}Z_{22} - Z_{21}Z_{12}$$

$$\left\{ \begin{array}{l} Y_{11} = \frac{Z_{22}}{\Delta_2} \quad Y_{12} = -\frac{Z_{12}}{\Delta_2} \\ Y_{21} = -\frac{Z_{21}}{\Delta_2} \quad Y_{22} = \frac{Z_{11}}{\Delta_2} \end{array} \right.$$

~~Y₁₁~~

Given Z parameters, let us obtain L parameters:

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (4)}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$I_1 = \frac{-Z_{21}}{Z_{22}} I_2 + \frac{1}{Z_{22}} V_2 \quad \text{--- (5)}$$

Put (4) in (5)

$$V_1 = Z_{11}I_1 + Z_{12} \left(-\frac{V_2 - Z_{21}I_1}{Z_{22}} \right)$$

$$= \frac{(Z_{11}Z_{22} - Z_{21}Z_{12})I_1 + Z_{12}V_2}{Z_{22}} \quad \text{--- (5)}$$

eqn (4) & (5) can be written as

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{\Delta Z_{22}}{Z_{22}} & \frac{Z_{12}}{Z_{22}} \\ \frac{-Z_{21}}{Z_{22}} & \frac{1}{Z_{22}} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \quad \text{--- (6)}$$

the h-parameter are

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \quad \text{--- (7)}$$

$$\left\{ \begin{array}{l} h_{11} = \frac{\Delta Z}{Z_{22}} \quad h_{12} = \frac{Z_{12}}{Z_{22}} \quad h_{21} = \frac{-Z_{21}}{Z_{22}} \\ h_{22} = \frac{1}{Z_{22}} \end{array} \right.$$

Q) Find $[Z]$ and $[g]$ of a two port network

$$[T] = \begin{bmatrix} 10 & 1.5 \Omega \\ 28 & 4 \end{bmatrix}$$

$$\left. \begin{array}{l} V_{21} = AV_2 - BI_2 \\ I_{21} = CV_2 - DI_2 \end{array} \right\} T$$

$$\left. \begin{array}{l} V_1 = Z_{11}I_1 + Z_{12}I_2 \\ V_2 = Z_{21}I_1 + Z_{22}I_2 \end{array} \right\} Z$$

$$V_2 = \frac{I_1 + DI_2}{C} = \frac{1}{C}I_1 + \frac{D}{C}I_2$$

$$\left. \begin{array}{l} V_{21} = AV_2 - BI_2 \\ A - BI_2 + \frac{A}{C}(I_1 + DI_2) \end{array} \right\}$$

$$V_2 = \frac{I_1}{C} + \frac{D}{C}I_2$$


$$V_{21} = \frac{I_1(-B + AD)}{C} + \frac{A}{C}I_1$$

$$Z_{11} = -B + \frac{AD}{C} = -1.5 + \frac{10 \times 4}{2} = 18.5 \Omega$$

$$\left. \begin{array}{l} Z_{11} = A/C \\ Z_{12} = \frac{AD - BC}{C} = \frac{\Delta T}{C} \\ Z_{21} = 1/C \\ Z_{22} = D/C \end{array} \right\}$$

③ Interconnection of Networks

Series Connection

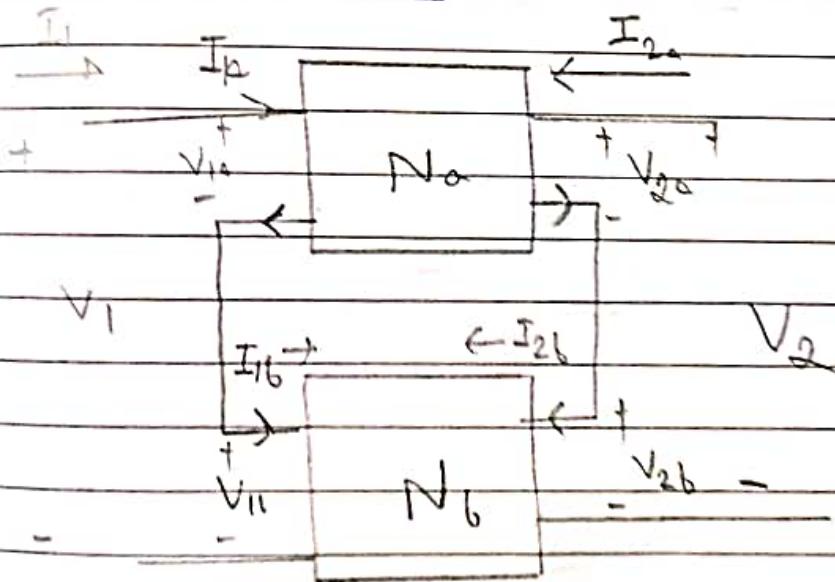

For n/w 'a'

$$V_{1a} = Z_{11a} I_{1a} + Z_{12a} I_{2a}$$

$$V_{2a} = Z_{21a} I_{1a} + Z_{22a} I_{2a}$$

For n/w 'b'

$$V_{1b} = Z_{11b} I_{1b} + Z_{12b} I_{2b}$$

$$V_{2b} = Z_{21b} I_{1b} + Z_{22b} I_{2b}$$

$$[I_1 = I_{10} + I_{1b} \quad \& \quad I_{20} = I_{2b}]$$

$$V_1 = V_{10} + V_{1b} = (Z_{110} + Z_{11b}) I_1 + (Z_{120} + Z_{12b}) I_2$$


$$V_2 = V_{20} + V_{2b} = (Z_{210} + Z_{21b}) I_1 + (Z_{220} + Z_{22b}) I_2$$

the Z parameters overall are :-

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{110} + Z_{11b} & Z_{120} + Z_{12b} \\ Z_{210} + Z_{21b} & Z_{220} + Z_{22b} \end{bmatrix}$$

$$[Z] = [Z_0] + [Z_b]$$

Parallel Connections

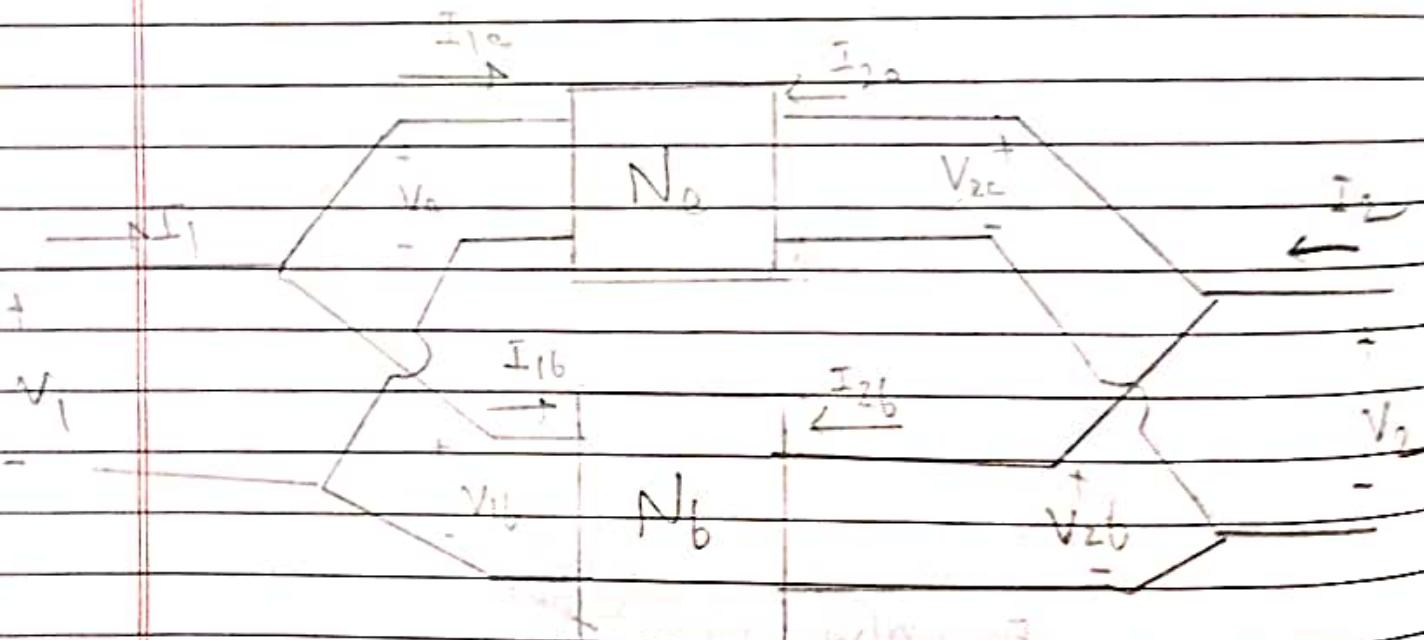

For $N|W+A$:

$$I_{10} = Y_{110} V_{10} + Y_{120} V_{20}$$

$$I_{20} = Y_{210} V_{10} + Y_{220} V_{20}$$

For N/W - 6 :

$$I_{1b} = Y_{11b} V_{1b} + Y_{12b} V_{2b}$$

$$I_{2b} = Y_{21b} V_{1b} + Y_{22b} V_{2b}$$

$$\underline{V_1 = V_{1a} = V_{1b}} \quad \underline{V_2 = V_{2a} = V_{2b}}$$

$$I_1 = I_{1a} + I_{1b}$$

$$I_2 = I_{2a} + I_{2b}$$


$$I_1 = (Y_{11a} + Y_{11b}) V_1 + (Y_{12a} + Y_{12b}) V_2$$

$$I_2 = (Y_{21a} + Y_{21b}) V_1 + (Y_{22a} + Y_{22b}) V_2$$

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} Y_{11a} + Y_{11b} & Y_{12a} + Y_{12b} \\ Y_{21a} + Y_{21b} & Y_{22a} + Y_{22b} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Cascade Connections

$$Y = [Y_a] + [Y_b]$$

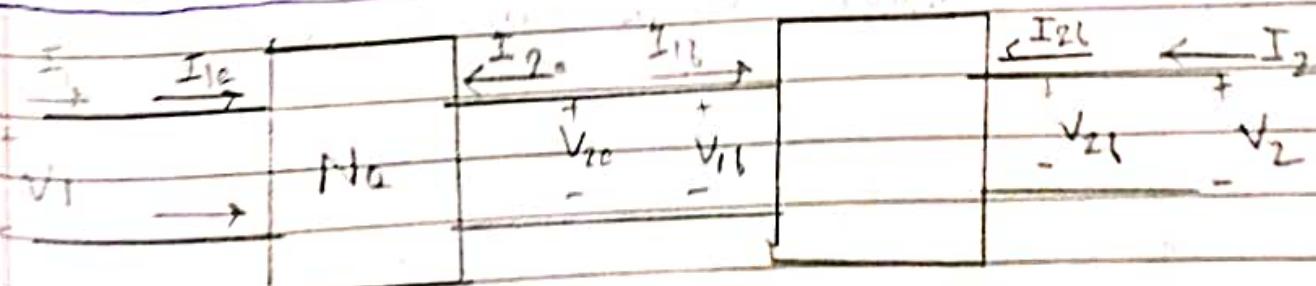

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \textcircled{1}$$

$$\begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2L} \\ -I_{2L} \end{bmatrix} \quad \textcircled{2}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} \quad \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} = \begin{bmatrix} V_{1L} \\ I_{1L} \end{bmatrix} \quad \begin{bmatrix} V_{2L} \\ -I_{2L} \end{bmatrix}$$


substitute \textcircled{2} in \textcircled{1}

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

Transmission parameters of overall network is product of individual transmission parameters of networks in cascade connections.

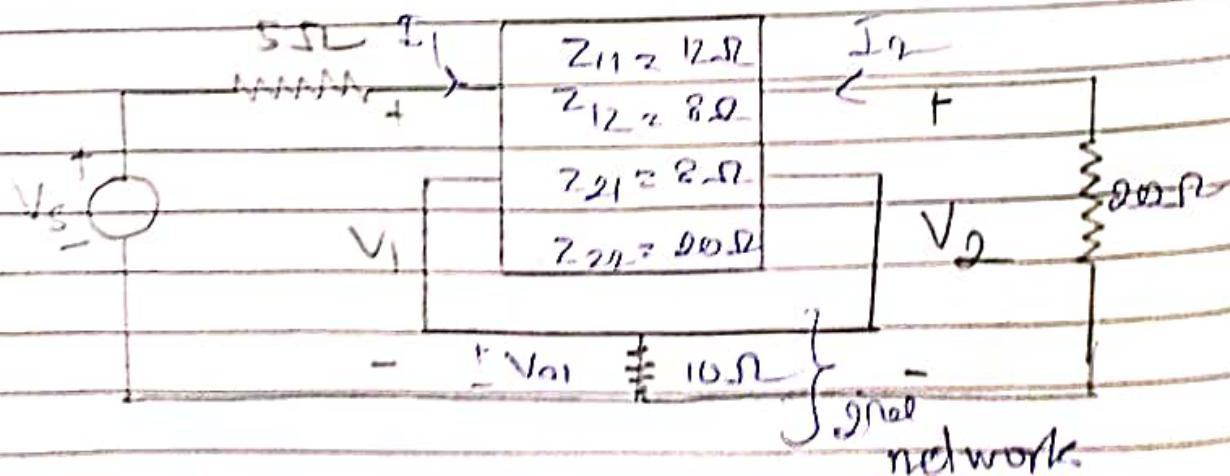\textcircled{1}) Evaluate V_2/V_s in the ckt



$$Z'_{11} = \frac{V_{P1}}{I_1} = \frac{10V_{D1}}{I_1} = 10,$$

$$Z'_{12} = \frac{V_{P1}}{I_2} = \frac{10I_1}{I_2} = 10$$

$$\{ I_1 = -I_2 \}$$

$$Z'_{21} = \frac{V_{P2}}{I_1} = 10$$

$$V_{P2} = V_{D2}/I_2 = 10$$

$$[Z]' = \begin{bmatrix} Z'_{11} & Z'_{12} \\ Z'_{21} & Z'_{22} \end{bmatrix} = \begin{bmatrix} 10 & 10 \\ 10 & 10 \end{bmatrix}$$

$$[Z]_{\text{net}} \rightarrow [Z] + [z]' \quad V_S - 5I_1 = V_1$$

$$= \begin{bmatrix} 22 & 18 \\ 18 & 30 \end{bmatrix}$$

$$\begin{aligned} V_1 &= 22I_1 + 18I_2 - ① \\ V_2 &= 18I_1 + 30I_2 - ② \end{aligned}$$

$$V_1 = V_S - 5I_1 - ③ \quad \text{put } ③ \& ④ \text{ in } ①$$

$$\begin{aligned} V_S &= 27I_1 + 18I_2 \\ -20I_2 &= V_2 = 18I_1 + 30I_2 \end{aligned}$$

~~+8I₂~~

$$I_2 = -V_2/20 - ④$$

$$\begin{aligned} V_S - 5I_1 &= 22I_1 + 18I_2 \\ &\quad - 20I_2 \\ &\quad \hline 20 \end{aligned}$$

$$V_S = 27I_1 - 0.9V_2 - ⑤$$

$$V_2 = 18I_1 + 3\phi \left(\frac{-V_{02}}{2\phi} \right)$$

$$V_2 = 18I_1 - 1.5 V_{02}$$

$$2.5V_2 = 18I_1$$

$$V_S = \frac{27}{18.2} (2.5V_2) - 0.9V_{02}$$


~~$V_S = 8.25(V_2)$~~

$$\frac{V_2}{V_S} = \frac{1.9}{2.85}$$

$$\approx 0.35$$

 20°

(d)

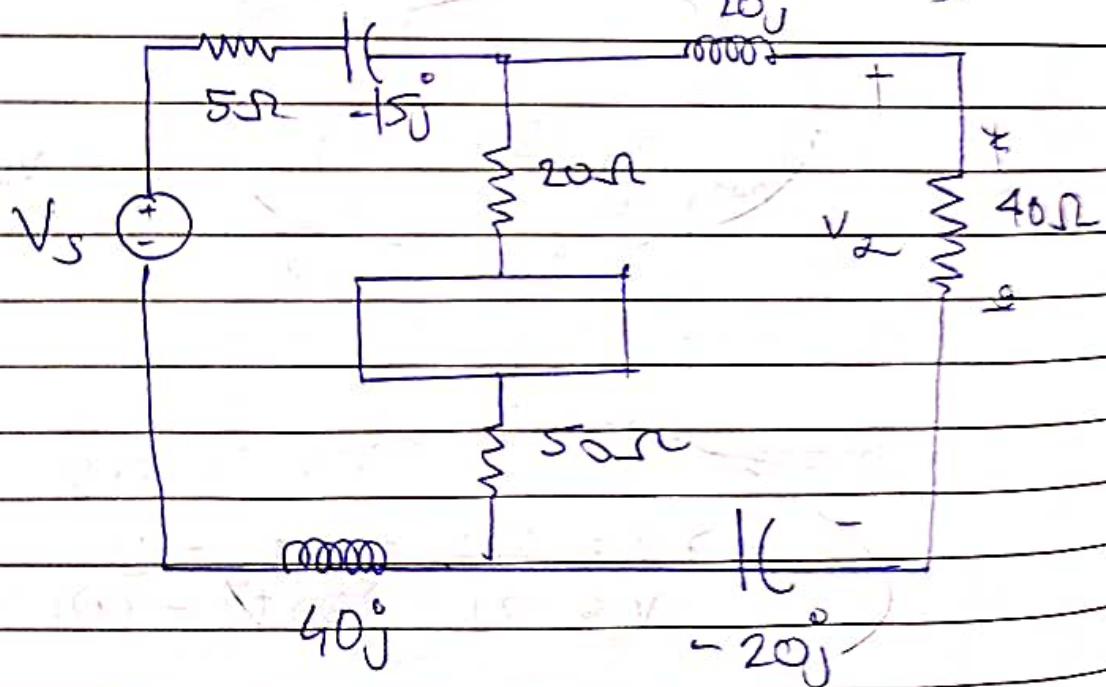

Ans $0.58 L - 40^\circ$

$$f(t) = a_0 + a_1 \cos \omega_0 t + a_2 \cos 2\omega_0 t + \dots \\ + b_0 + b_1 \sin \omega_0 t + b_2 \sin 2\omega_0 t + \dots$$

$$f(t) = a_0 + \sum_{k=-\infty}^{\infty} a_k \cos(k\omega_0 t) + b_k \sin(k\omega_0 t)$$

{ Fourier Analysis }

~~Plot~~ where $\omega_0 = \frac{2\pi}{T}$

Useful trigonometry identities

$$1) \int (\sin n\omega_0 t) dt = 0$$

$$2) \int_0^T \cos n\omega_0 t dt = 0$$

$$3) \int_0^T \sin n\omega_0 t \cos n\omega_0 t dt = 0$$

$$4) \int_0^T \sin n\omega_0 t \sin m\omega_0 t dt = 0 \quad m \neq n$$

$$5) \int_0^T \cos n\omega_0 t \cos m\omega_0 t dt = 0 \quad m \neq n$$

$$6) \int_0^T \sin^2 n\omega_0 t dt = T/2 = \int_0^T \cos^2 n\omega_0 t dt$$

$$7) \int_0^t \sin at dt = -\frac{1}{a} \cos at$$

$$8) \int t \cdot \cos at dt = \frac{1}{a^2} \cos at + \frac{1}{a} t \sin at$$

$$9) \int t \cdot \sin at dt = \frac{1}{a^2} \sin at - \frac{1}{a} \cdot t \cdot \cos at$$

$$\cos 2n\pi = 1 \quad \cos n\pi = (-1)^n$$

$$\sin 2n\pi = 0 \quad \sin n\pi = 0$$

$$e^{j2\pi n} = 1 \quad e^{j\pi} = (-1)^n$$

$$e^{jn\pi/2} = (-1)^{n/2} \quad n - \text{even}$$

$$= j(-1)^{\frac{n-1}{2}} \quad n - \text{odd}$$

$$\cos \frac{n\pi}{2} = (-1)^{n/2} \quad n - \text{even}$$

$$= 0 \quad n - \text{odd}$$

$$\sin \frac{n\pi}{2} = (-1)^{(n-1)/2} \quad n - \text{odd}$$

$$= 0 \quad n - \text{even}$$

$$a_0 = \frac{1}{T} \int_0^T f(t) dt$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega t dt$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega t dt$$

Amplitude form:- we know that,


$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \phi)$$

$$C = \sqrt{A^2 + B^2} \quad \phi = \tan^{-1}(B/A)$$

① can be written as

$$f(t) = a_0 + \sum_{n \geq 1} A_n \cos(n\omega t + \phi_n)$$

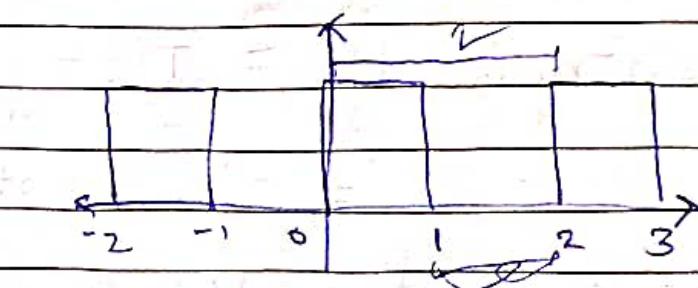② Determine the fourier series of waveform and obtain the amplitude & phase spectrum.



$$f(t) = \begin{cases} 1 & 0 < t < 1 \\ 2 < t < 3 \\ -2 < t < -1 \\ 0 & \text{otherwise} \end{cases}$$

of $\sum R_{nk} e^{j\omega_n t}$

$$\Rightarrow x(t) = \sum_{k=-\infty}^{\infty} c_k e^{j\omega_k t}$$

$$\sum_{k=-\infty}^{\infty} c_k = \frac{1}{T} \int_{-T/2}^{T/2} x(t) e^{-j\omega_k t} dt$$

$$= \frac{1}{2} \int_0^T e^{-j\omega_k t} dt = \frac{e^{-j\omega_k T}}{2j\omega_k} \Big|_0^T = \frac{1 - e^{-j\omega_k T}}{2j\omega_k}$$

written

$$\frac{1}{2} = \frac{2\pi}{2\pi} \quad k=0$$

$$c_0 = \frac{1}{2} \quad \text{for } k=0$$

$$c_1 = \frac{1 - e^{-j\omega_1 T}}{2j\omega_1} = \frac{1 - e^{-j\pi}}{2j \frac{2\pi}{T}} = \frac{1 - e^{-j\pi}}{4j\pi} = \frac{1 + 1}{4j\pi} = \frac{2}{4j\pi} = \frac{1}{2j\pi} = \frac{1}{2} e^{j\omega_1 t} - \frac{1}{2} e^{-j\omega_1 t}$$

$$\sin$$

$$x(t) = \frac{1}{2} + \frac{2}{\pi} \sin \pi t + \frac{2}{3\pi} \sin 3\pi t$$

$\pi, 3\pi, 5\pi, 7\pi$

$$c_k = \frac{1}{2} \left(\cos(\pi k) - \sin(\pi k) \right) \quad k \neq 0$$

$$1 - \cos \pi k \quad k = \text{odd}$$

$$2\pi k \quad k = \text{even}$$

$$= \frac{1}{2\pi k} = \frac{1}{\pi k}$$

$$x. \text{ or } \int_0^1 x(t) dt \text{ is not}$$

$$\begin{aligned} x(t) &= a_0 + a_1 e^{j\omega_0 t} + a_2 e^{j2\omega_0 t} + a_3 e^{j3\omega_0 t} \\ &\Rightarrow \frac{1}{2} + \frac{1}{j\omega_0} (\cos \omega_0 t + j \sin \omega_0 t) \\ &\quad + \left(\frac{1}{2j\omega_0} \right) (\cos 2\omega_0 t + j \sin 2\omega_0 t) \end{aligned}$$

$$\begin{aligned} \frac{1}{2} &\times 0 \int_0^1 e^{-j\omega_0 t} dt = -\frac{1}{2} \frac{e^{-j\omega_0 t}}{j\omega_0} \Big|_0^1 \\ &\Rightarrow 1 - e^{-j\omega_0 k} \\ &\approx \frac{2j\omega_0 k}{\pi} \left(1 - e^{-j\omega_0 k} \right) \\ &\approx \frac{\pi j 2\omega_0 k}{\pi} \left(1 - e^{-j\omega_0 k} \right) \end{aligned}$$


$$\begin{aligned} a_0 &= \frac{1}{T} \int_0^T f(t) dt = \frac{1}{T} \int_0^T dt + \int_0^T 0 dt \\ &\approx 1/2 \end{aligned}$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos(n\omega_0 t) dt$$

$$= \frac{2}{T} \int_0^T \cos(n\omega_0 t) dt = 0$$


$$b_n = \frac{2}{T} \int_0^T \sin(n\omega_0 t) dt = -\frac{\cos(n\omega_0 T)}{n\omega_0} = \frac{1 - \cos n\pi}{n\pi} = 2/n\pi$$

$$f(t) = \frac{1}{2} + \frac{2}{\pi} \sin(\pi t) + \frac{2}{3\pi} \sin(3\pi t) + \dots$$

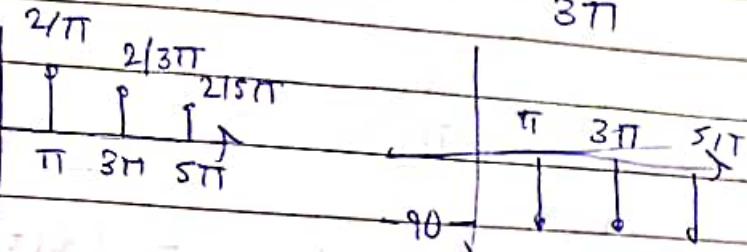H.W

$$\phi = \tan^{-1} \left(\frac{b_n}{a_n} \right)$$

$$= \text{q.} -90$$

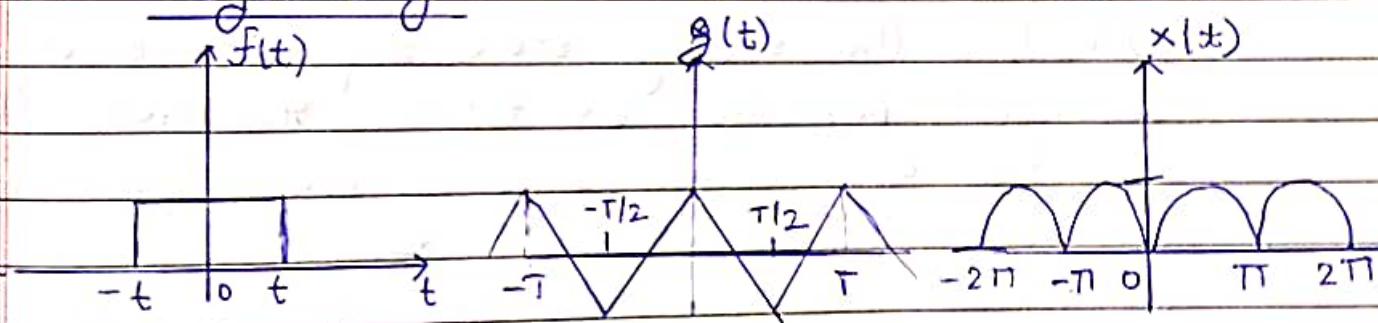Symmetry

The property of an even function $f_e(t)$ is

$$\int_{-T/2}^{T/2} f_e(t) dt = 2 \int_0^{T/2} f_e(t) dt$$


\therefore Fourier coefficients of even function

$$a_0 = \frac{2}{T} \int_0^{T/2} f(t) dt \quad a_n = \frac{4}{T} \int_0^{T/2} f(t) \cos(\omega_0 n t) dt$$

$$b_n = 0$$

A function $f(t)$ is even if its plot is symmetrical about vertical axis. e.g.: $t^2, t^4, \cos t$

Symmetry

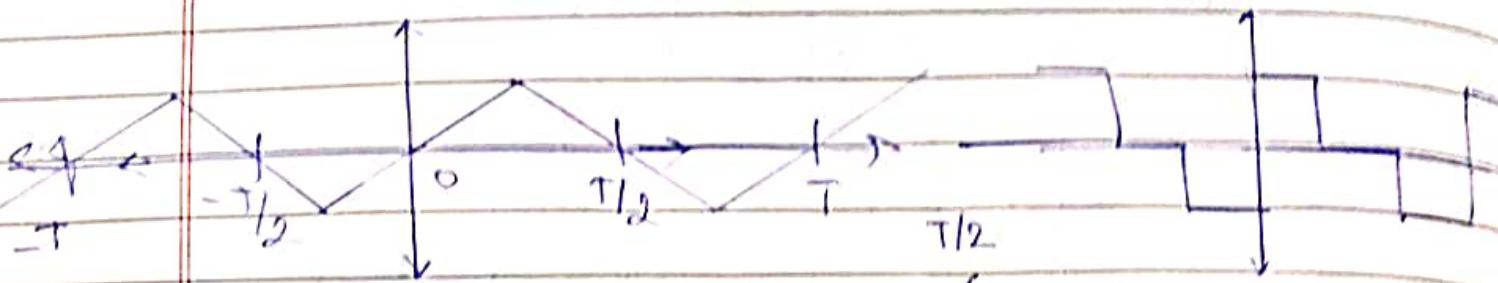

$$a_0 = 0 \quad b_n = \frac{4}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} f(t) \sin n\omega_0 t \, dt$$

$$a_n = 0$$

A function $f(t)$ is said to be odd if it's plot is antisymmetrical about the vertical axis.
 $f(t) = -f(-t)$. $f(t) = t, t^3, \sin t$.

Steps for Fourier Series Application to Circuit


① To find the steady state response to a non-sinusoidal periodic excitation requires the application of fourier series, AC phaser analysis and superposition principle.

② Express the given excitation function in a Fourier series.

③ Find the response for every term in the Fourier series.

④ Add the individual responses using superposition principle.
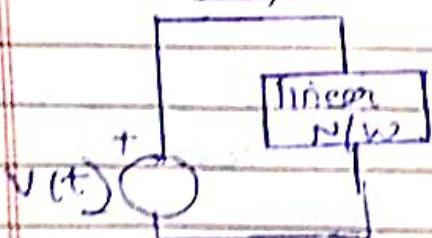
$$V(t) = V_0 + \sum_{n=1}^{\infty} V_n \cos(n\omega_0 t + \phi_n) \quad ①$$




dc components = V_0

ac components = $V_n = V_n L C$




with several harmonics

Fourier Analysis

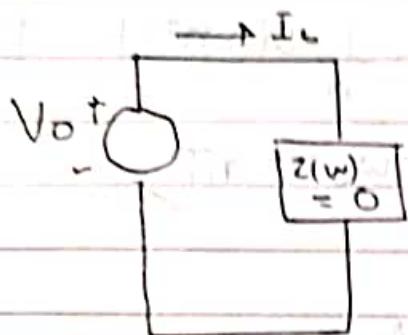

$$\text{Final Resp} = i(t) = i_0(t) + i_1(t) + i_2(t) + \dots + i_n(t)$$
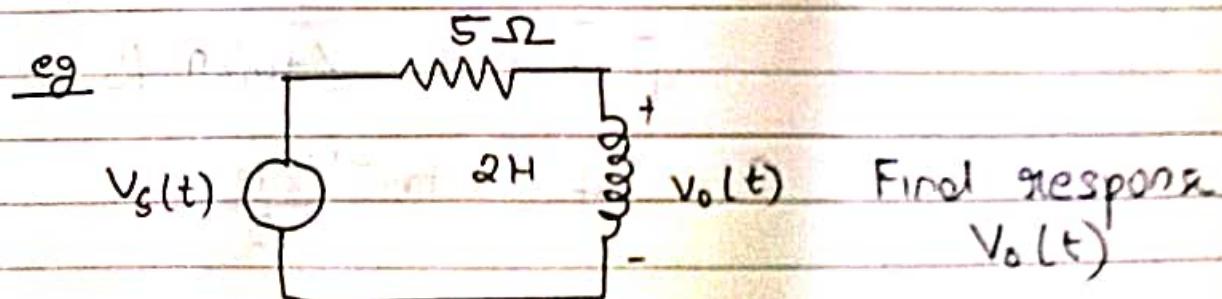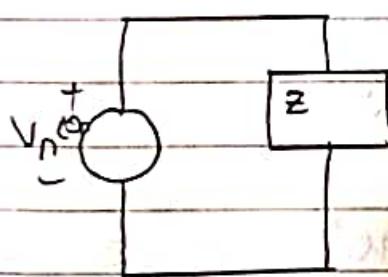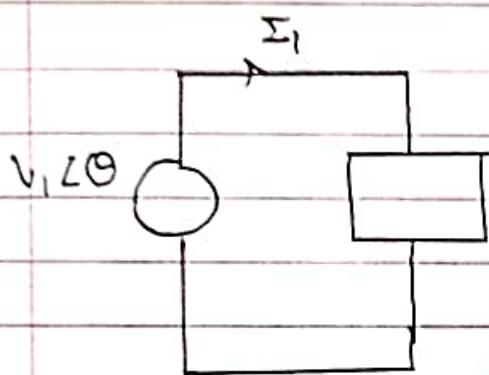
$$I_o + \sum_{n=1}^{\infty} [I_n] \cos(n\omega t + \phi)$$




$V_s(t)$

5Ω

$2H$

$v_o(t)$

First response
 $v_o(t)$

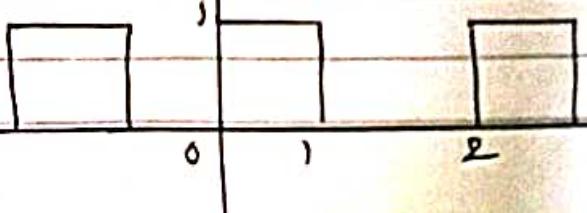

t

$$V_o(t) = \frac{1}{2} + \frac{2}{\pi} \sum_{k=1}^{\infty} \frac{1}{n} \sin n\pi t \quad \{n=2k-1\}$$

$$\omega_n = n\omega_0 = n\pi$$

$$V_o(t) = \frac{j\omega_0 n L}{R + j\omega_n L} \cdot V_s$$

For d.c components

$$V_s = 1/2$$

$$\omega_0 = 0$$

$$\therefore V_o = 0$$

For n^{th} harmonic,

$$V_s = \frac{2}{n\pi} L - 90^\circ$$

$$V_o = j \frac{2\pi L \cdot 90^\circ}{R + j\omega_n L} = \frac{2}{n\pi} L - 90^\circ$$

$$\sqrt{25 + 4\pi^2 n^2} \angle \tan^{-1} 2\pi L / 5$$

$$4 L - \tan^{-1} \left(\frac{2\pi L}{5} \right)$$

$$\sqrt{25 + 4\pi^2 n^2}$$


In time domain,

$$v_o(t) = \sum_{k=1}^{\infty} \frac{4}{\sqrt{25 + 4k^2\pi^2}} \cos\left(n\pi t - \frac{2n\pi}{5}\right)$$


$$n = 2k-1$$

$$k = 1, 2, 3, \dots$$
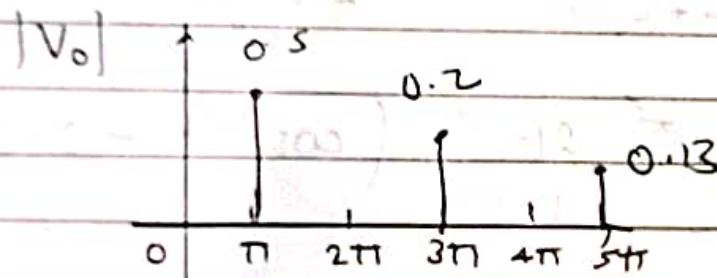
$$v_o(t) = 0.49 \cos(\pi t - 51.4^\circ) + 0.2 \cos(3\pi t - 75.1^\circ) \\ + 0.12 \cos(5\pi t - 80.9^\circ) + \dots$$



Q)

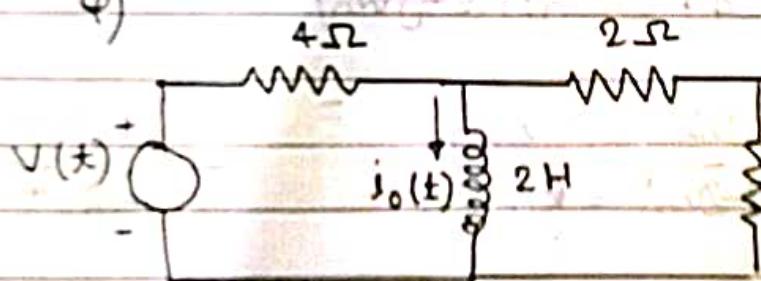

Find the response

$$i_o(t) \text{ in the ckt if } V(t) = 1 + \sum_{n=1}^{\infty} 2(-1)^n$$

$$\cdot (\cos(nt) - n \sin(nt))$$

$\omega_n = \frac{1}{2} n(1) = n$

$V_o(t) = 1$

$\omega_0 = 0$

$i_o(t) = 0$

$$Z_{eq} = 4 + \frac{4 \times 2j\omega_n}{4 + 2j\omega_n}$$

$$\frac{V_1}{I_1} = \left[4 + \frac{8j\omega_n}{4 + 2j\omega_n} \right] I_1 = \left[\frac{16 + 8j\omega_n + 8j\omega_n}{4 + 2j\omega_n} \right] I_1 = \left[\frac{16 + 16j\omega_n}{4 + 2j\omega_n} \right] I_1$$

$$I_0 = \left(\frac{-4}{4 + 2j\omega_n} \right) I_1$$

$$I_0 = \left(\frac{4}{4 + 2j\omega_n} \right) \left(4 + \frac{8j\omega_n}{4 + 2j\omega_n} \right) V_1$$

$$V_1 = \frac{2(-1)^n}{1+n^2} (\cos nt - \sin nt)$$

$$I_0 V_1 = \frac{32 + 32j\omega_n}{(4 + 2j\omega_n)(2 + j\omega_n)} V_1$$

$$\frac{32 + 32\omega_n j}{8 - 2\omega_n^2 + 8j\omega_n} = \frac{16 + 16\omega_n j}{4 - \omega_n^2 + 4\omega_n j} V_1$$

$$V_1 = \frac{2(-1)^n}{1+n^2} (+ \text{cosec}^{-1}(n))$$

$$I_0 =$$

Laplace Transform

$$L[f(t)] = F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

where $s \neq 0$ is a complex variable given by
 $s = \sigma + j\omega$

$$1) L[u(t)] = \int_0^{\infty} e^{-st} dt$$

$$= \frac{e^{-st}}{s} \Big|_0^{\infty} = \frac{1 - e^{0s}}{s} = \frac{1 - 1}{s} = 0$$

$$2) L[e^{-at}] = \int_{-\infty}^{\infty} e^{-at} \cdot e^{-st} dt$$

$$= \int_0^{\infty} e^{-(a+s)t} dt = \frac{e^{-(a+s)t}}{a+s} \Big|_0^{\infty}$$

$$= \frac{1 - e^{-(a+s)\infty}}{a+s} = \frac{1 - 0}{a+s} = \frac{1}{a+s}$$

$$3) L[e^{at}] = \frac{1}{s-a}$$

$$4) L[\sin(\omega t)] = \frac{\omega}{s^2 + \omega^2}$$

$$5) L[\cos(\omega t)] = \frac{s}{s^2 + \omega^2}$$

$$9) L[t] = \frac{1}{s^2}$$

$$7) L[\int f(at) dt] = \frac{1}{a} F\left[\frac{s}{a}\right] = L\left[\int f(t) dt\right] = \frac{1}{s} F(s)$$

$$8) L[e^{-at} \cdot f(t)] = F(s+a) \quad L\left[\frac{f(t)}{t}\right] = \int f(u) du$$

$$9) L\left[\frac{d f(t)}{dt}\right] = s \cdot F(s) - f(0)$$

$$10) L[t \cdot f(t)] = \frac{d}{ds} F(s)$$

$$11) \text{Initial value theorem } f(0) = \lim_{s \rightarrow \infty} s \cdot F(s)$$

$$\text{Final value theorem } f(\infty) = \lim_{s \rightarrow 0} s \cdot F(s)$$

$$\text{Convolution : } f_1(t) * f_2(t) = F_1(s) \cdot F_2(s)$$

$$L[a_1 f_1(t) + a_2 f_2(t)] = a_1 F_1(s) + a_2 F_2(s)$$

$$L[\delta(t)] = 1$$

Date _____
Page _____

Q) Apply Laplace transform of $f(t) = 3(s) + 2e^{-t} - 3e^{-3t}$, $t \geq 0$

$$L(f(t)) = F(s) = 1 + \frac{2}{s} - \frac{3}{s+2}, \quad s > 0$$

$$\begin{array}{r} 2 \\ \hline s^2 + s + 4 \\ \hline s(s+2) \end{array} \quad \begin{array}{r} 3 \\ \hline -2 \end{array}$$

Q) Find Laplace of $\cos 2t + e^{-3t}$, $t \geq 0$

$$F(s) = \frac{2s}{4+s^2} + \frac{1}{s+3}, \quad s > -3$$

$$\begin{array}{r} 2s + 3s + 4 + s^2 \\ \hline (4+s^2)(3+s) \end{array}$$

$$\begin{array}{r} 2s^2 + 3s + 4 \\ \hline (4+s^2)(3+s) \end{array}$$

Q) $F(s) = \frac{N(s)}{(s+p_1)(s+p_2) \dots (s+p_n)} = k_1 + k_2 + \dots + k_n$

where k_1, k_2, \dots, k_n are called Residues of $F(s)$

$$k_1 = (s+p_1) F(s) \Big|_{s=-p_1}$$

$$k_i = (s+p_i) F(s) \Big|_{s=-p_i}$$

$$F_s = \frac{k_n}{(s+p)^n} + \frac{k_{n-1}}{(s+p)^{n-1}} + \dots + \frac{k_1}{(s+p)} + F_1$$

$$k_n = (s+p)^n F_s \Big|_{s=-p}$$

$$k_{n-1} = s \frac{d}{ds} \left[(s+p)^n \cdot F(s) \right] \Big|_{s=-p}$$

$$k_{n-2} = \frac{d^2}{ds^2} \left[(s+p)^n \cdot F(s) \right] \Big|_{s=-p}$$

i) Find I.L.T of $F(s) = \frac{3}{s} - \frac{5}{s+1} + \frac{6}{s^2+4}$

$$L^{-1}[F(s)] = f(t) = 3u(t) - 5e^{-t} + 3\sin(2t)$$

ii) Find the inverse laplace transform of

$$F(s) = 1 + \frac{4}{s+3} - \frac{5s}{s^2+16}$$

$$L^{-1}[F(s)] = f(t) = s(t) + 4e^{-3t} - \frac{5}{16} \cos(4t)$$

iii) Find $f(t)$ if $F(s) = \frac{s^2+12}{s(s+2)(s+3)}$

$$F(s) = \frac{s}{(s+2)(s+3)} + \frac{12}{s(s+2)(s+3)}$$

$$\begin{aligned}
 F(s) &= \frac{3}{s+2} - \frac{s}{s+3} + \frac{12}{s(s+2)(s+3)} \\
 &= \cancel{\frac{3}{s+2}} - \cancel{\frac{s}{s+3}} - \left[1 - \frac{\cancel{12}}{\cancel{s+3}} \right] + \frac{12}{s(s+2)(s+3)} \\
 &= \frac{3}{s+2} - \frac{2}{s+2} + \frac{12}{s} \left[\frac{A}{s+2} + \frac{B}{s+3} + \frac{C}{s+3} \right]
 \end{aligned}$$

$$\begin{aligned}
 12 \left[\frac{A}{s+2} + \frac{B}{s+3} + \frac{C}{s+3} \right] &\stackrel{?}{=} \frac{A(s+2)(s+3) + B(s)(s+3) + C(s)(s+2)}{(s+2)(s)(s+3)} \\
 &\stackrel{?}{=}
 \end{aligned}$$

$$\frac{s^2+12}{s(s+2)(s+3)} = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+3}$$

$$A = s \cdot F(s) \Big|_{s=0} = \frac{12}{6} = 2$$

$$B = (s+2) F(s) \Big|_{s=-2} = \frac{s^2+12}{s(s+3)} = \frac{16}{-2} = -8$$

$$C = (s+3) F(s) \Big|_{s=-3} = \frac{s^2+12}{s(s+2)} = \frac{21}{3} = 7$$

$$F(s) = \frac{2}{s} + 8\cancel{\frac{1}{s+2}} - 8\frac{1}{s+2} + 7\frac{1}{s+3}$$

$$= 2u(t) - 8e^{-2t} + 7e^{-3t}$$

Q) Find I.L.T of $\frac{10s^2+4}{s(s+1)(s+2)^2}$

$$\frac{10s^2+4}{s(s+1)(s+2)^2} = \frac{A}{s} + \frac{B}{s+1} + \frac{Ck_1 + k_2}{(s+2)^2}$$

$$A = s \cdot F(s) \Big|_{s=0} = \frac{4}{0+4} = 1$$

$$B = (s+1)F(s) \Big|_{s=-1} = \frac{10+4}{(-1)(1)^2} = -14$$

$$k_1 = (s+2)^2 F(s) \Big|_{s=-2} = \frac{10(4)+4}{-2(-1)} = \frac{44}{2} = 22$$

$$k_2 = \frac{d}{ds} \left(\frac{10s^2+4}{(s+1)(s+2)} \right)$$

$$k_2 = \frac{(s^2+s)(20s) - (2s+1)(10s^2+4)}{(s^2+s)^2} \Big|_{s=-2}$$

$$= (4-2)(-40) - (-4+1)(\cancel{-20} + 4)$$

$$= \frac{(4-2)^2}{-36 - (-3)(\cancel{-20})} = \frac{4}{45}$$

$$= \frac{4}{-20 + 33} = \frac{4}{13}$$

~~1/s~~

$$F(s) = \frac{14}{s+1} + \frac{22}{(s+2)^2} + \frac{13}{(s+2)}$$

$$= u(t) - 14e^{-t} + 22te^{-2t} + 13e^{-2t}$$

Q) Find ILT $F(s) = \frac{20}{(s+3)(s^2+8s+25)}$

$$F(s) = \frac{A}{(s+3)} + \frac{Bs+C}{(s^2+8s+25)}$$

$$A = [s+3] F(s) \Big|_{s=-3}$$

$$= \frac{20}{9-24+25} = \frac{20}{10} = 2$$

$$B = (s^2+8s+25) F(s)$$

$$F(s) = A(s^2+8s+25) + Bs(s+3) + C(s+3)$$

$$s=0$$

$$As^2 + Bs^2 + Cs = 0$$

$$\underline{20} = 25A + 3C$$

$$A = 8$$

$$B = -2$$

~~$$20 = 20 + 3C$$~~

~~$$20 = 50 + 3C$$~~

$$C = -10$$

$$F(s) = \frac{2}{s+3} - \frac{2s+10}{s^2+8s+25}$$

$$= \frac{2}{s+3} - \frac{2s+10}{s^2+8s+16+9}$$

$$= \frac{2}{s+3} - \frac{2s+10}{(s+4)^2+3^2}$$

$$= \frac{2}{s+3} - 2 \left[\frac{s+4}{(s+4)^2+3^2} \right]$$

$$= \frac{2}{s+3} - 2 \left[\frac{s+4}{(s+4)^2+3^2} \right] - \frac{2 \times 3}{(s+4)^2+3^2}$$

$$f(t) = \left[2e^{-3t} - 2 \sin \cancel{c} \cos (\cancel{s+4} 3t) \right]$$

$$- \frac{2}{3} e^{-4t} \sin(3t) \right] \cancel{\text{Ans}}$$

Q) $F(s) = \frac{10}{(s+1)(s^2+4s+13)}$

$$F(s) = \frac{A}{s+1} + \frac{Bs+C}{s^2+4s+13}$$

$$A = (s+1) F_s \Big|_{s=-1} = \frac{10}{1-4+13} = \frac{10}{10} = 1$$

date
page

$$10 = A(s^2 + 4s + 13) + B_3(s+1) + C(s+1)$$

$$s=0$$

$$10 = A(13) + 0 + C$$

$$10 = 13 + C$$

$$\boxed{C = -3}$$

$$A s^2 + B s^2 = 0$$

$$\cancel{A} s^2 + \cancel{B} s^2 = 0$$

$$P(s) = \frac{1}{s+1} + \frac{s+3}{s^2 + 4s + 13}$$

$$\frac{1}{s+1} = \frac{s+3}{s^2 + 4s + 4 + 9}$$

$$\frac{1}{s+1} = \frac{s+3}{(s+2)^2 + 3^2}$$

$$P(t) = e^{-t} / - e^{3t} \cos(3t)$$

$$\frac{1}{s+1} = \frac{s+2}{(s+2)^2 + 3^2} = \frac{1}{3} \frac{3}{(s+2)^2 + 3^2}$$

$$f(t) = e^{-t} - e^{-2t} \cos(3t) + \frac{1}{3} e^{-2t} \sin(3t)$$


Application of Laplace Transform to circuits

- 1) Transform the given circuit from time domain to s-domain.
- 2) Solve the circuit with any of the 1 node technique.
- 3) Take inverse laplace transform of the solution to apply the solution in time domain.

Resistor - $V_R(t) = i(t) \cdot R$
 $V_R(s) = R \cdot I(s)$

Inductance - $V_L(t) = L \cdot \frac{di(t)}{dt}$
 $V_L(s) = L [s(I(s)) - I(0^-)]$
 $\therefore SLI(s) - \cancel{L}I(0^-)$
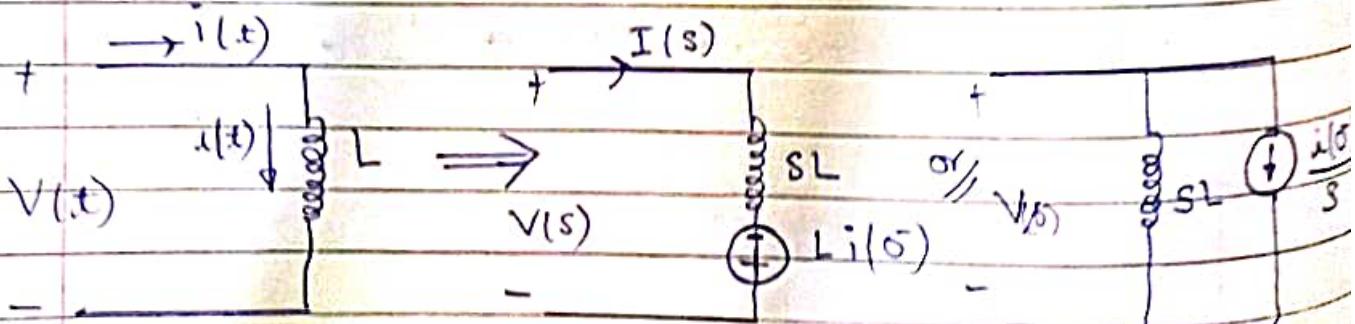
$$I(s) = \frac{1}{SL} V_L(s) + \frac{i(0^-)}{s}$$





Part - Operations

$$I(s) = C \cdot \frac{dv(s)}{ds}$$


V(s) \equiv v

$$I(s) = C [s \cdot v(s) - v(0)]$$


$$= sCv(s) - Cv(0)$$

$$V_c(s) = \frac{1}{sC} [I(s) + V(0)] = \frac{1}{s} \cdot \frac{1}{C} \cdot \frac{v(0)}{s} + \frac{1}{s} v(s)$$

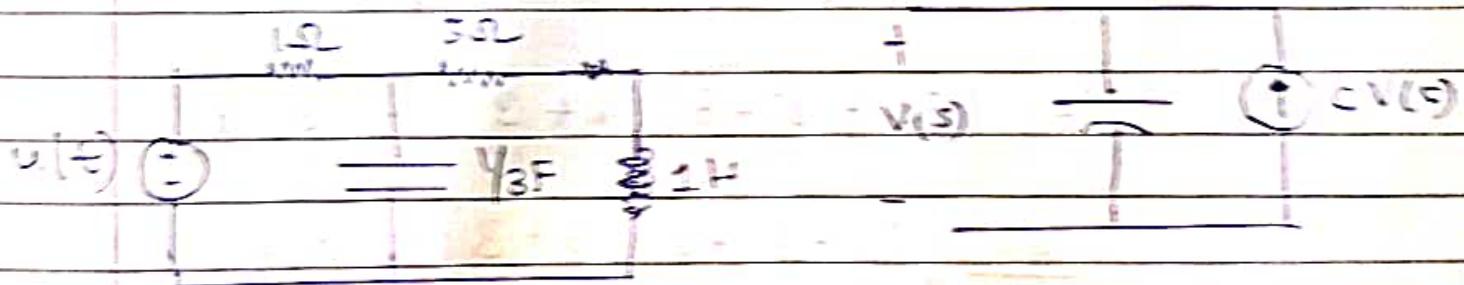- c) Find $v_c(t)$ in the circuit assuming given input condition



Transform every element to s domain

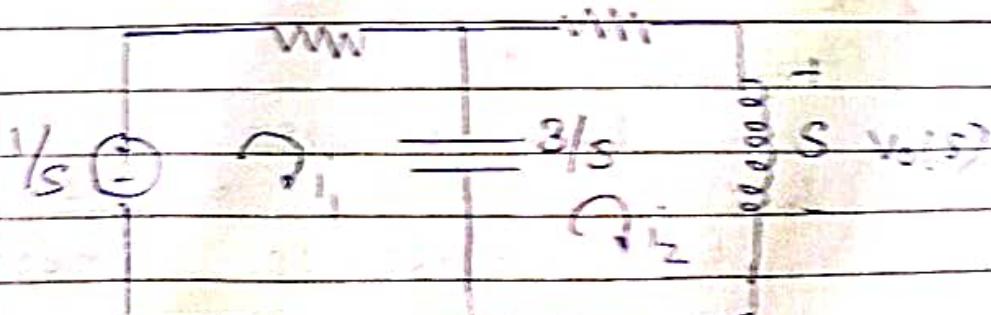

$$\frac{1}{s} - i_1 - \frac{3}{s}(i_1 - i_2) = 0$$

$$\frac{1}{s} - i_1 - \frac{3}{s}i_1 + \frac{3}{s}i_2 = 0$$

$$\frac{3}{s}i_2 - i_1\left(1 + \frac{3}{s}\right) = -\frac{1}{s}$$

$$i_1\left(1 + \frac{3}{s}\right) - \frac{3}{s}i_2 = \frac{1}{s} \quad \text{--- (1)}$$

$$-5i_2 - si_2 - \frac{3}{s}(i_2 - i_1) = 0$$

$$-5i_2 - si_2 - \frac{3}{s}i_2 + \frac{3}{s}i_1 = 0$$

$$i_2\left(5 + s + \frac{3}{s}\right) = \frac{3}{s}i_1$$

$$i_2\left(5s + s^2 + 3\right) = 3i_1 \quad \text{--- (2)}$$

$$\frac{i_2}{3}\left(5s + s^2 + 3\right)\left(1 + \frac{3}{s}\right) - \frac{3}{s}i_2 = \frac{1}{s}$$




$$\frac{i_2}{3}\left(5s + s^2 + 3\right)(s + 3) - 3i_2 = 1$$

$$\frac{i_2}{3}\left(5s^2 + 15s + s^3 + 3s^2 + 3s + 9\right) - 3i_2 = 1$$

$$i_2(s) = \frac{3}{s^3 + 8s^2 + 18s}$$

$$V_b(s) = s \times \frac{3}{s^3 + 8s^2 + 18s} = \frac{3}{s^2 + 8s + 18}$$

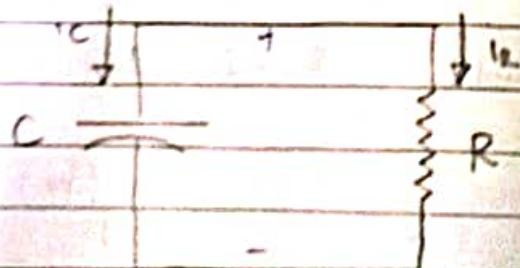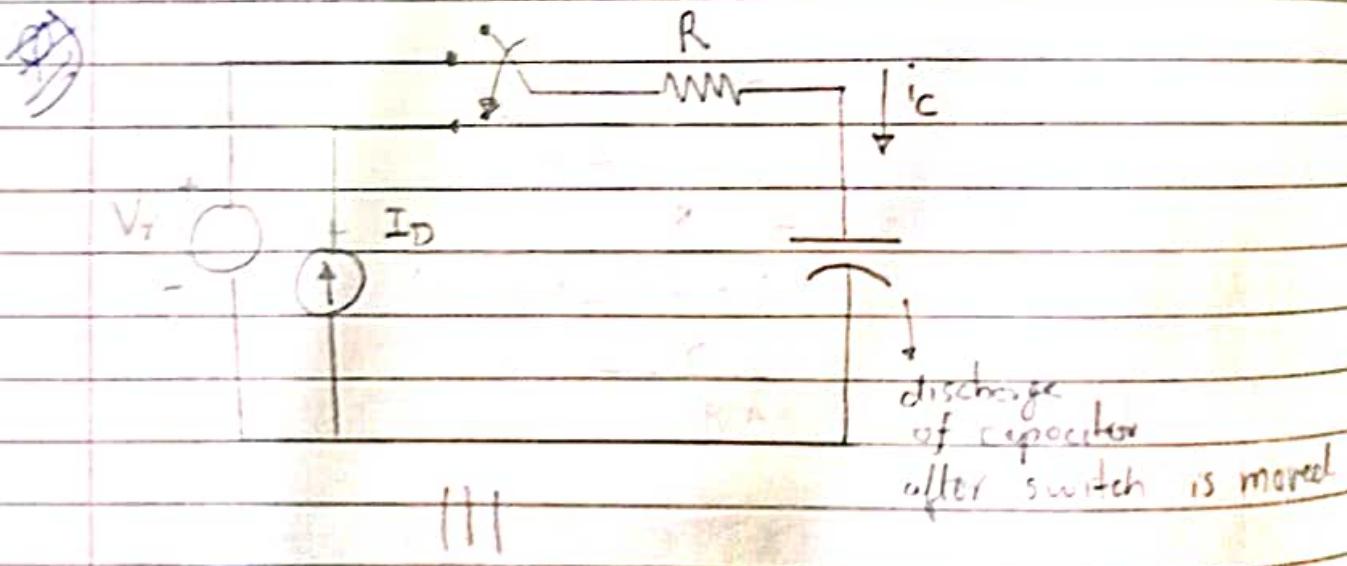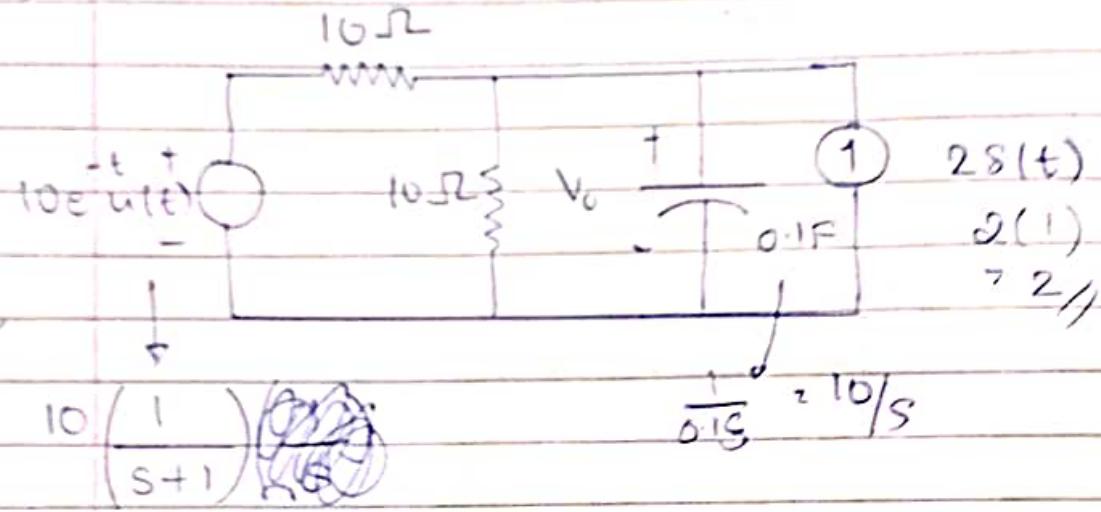(Q) Find $v_o(t)$ in the ckt assuming the initial condition $v_o(0^-) = 5V$



Consider a series combination of resistor and initially charged capacitor. The initial voltage of capacitor at $t=0$, $V(0) = V_0$. So energy stored $W(0)/E = \frac{1}{2} CV_0^2$. On applying KCL in the loop

$$i_C + i_R = 0$$

$$C \frac{dV}{dt} + \frac{V}{R} = 0$$

$$\frac{dV}{dt} + \frac{V}{RC} = 0$$

$$\int_{V_0}^V \frac{dV}{V} = \int_0^t -\frac{1}{RC} dt$$

~~OR~~

$$\ln(V) = -\frac{t}{RC} + \ln A_0$$

$$\ln\left(\frac{V}{V_0}\right) = -\frac{1}{RC} t \quad \text{constant}$$

$$V = V_0 e^{-t/RC}$$


$$\ln V = -t/RC$$

$$V = A e^{-t/RC}$$

using initial conditions

$$V(0) = A = V_0$$

$$V(t) = V_0 e^{-t/RC}$$

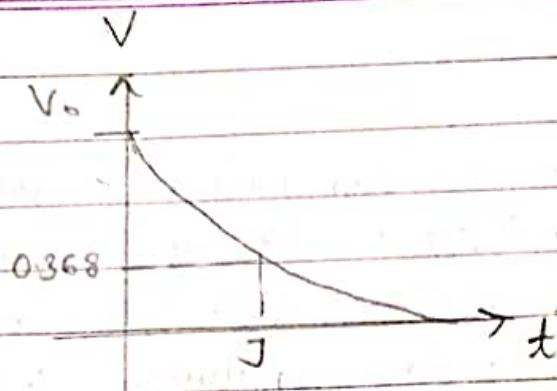

when $t = RC$, $V(t) = V_0 e^{-t/RC} = 0.368 V_0$

t	$V(t)/V_0$	$\{t=RC\}$
$1Z$	0.367	{ Time req. to reach
$2Z$	0.13	36% of initial value
$3Z$	0.04	is called time const.
$4Z$	0.018	
$5Z$	0.0067	

The voltage $V(t)$ is less than 1% of V_0 after $5Z$. Thus it is customary to assume the capacitor is fully discharged after 5 time constant.

$$P_R(t) = \frac{V(t)}{R} = \frac{V_0 e^{-t/Z}}{R}$$

Power dissipated in Resistor

$$P(t) = V \cdot i_R = \frac{V_0^2 e^{-2t/Z}}{R}$$

Energy absorbed upto 't' is -


$$W_R(t) = \int P \cdot dt = \int \frac{V_0^2}{R} e^{-2t/Z} dt$$

$$\frac{1}{2} CV_0^2 (1 - e^{-\omega t/2})$$

As $t \rightarrow \infty$

$$\omega_R = \frac{1}{2} CV_0^2$$

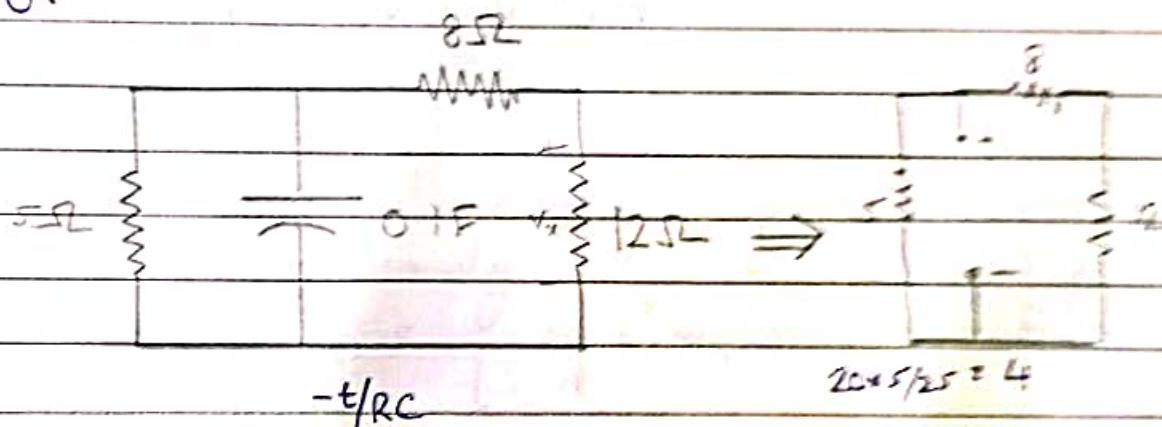(Q) Let $V_C(0) = 15V$. Find V_C , V_x and i_x at $t > 0$.



$$V_C = V_0 e^{-t/RC}$$

$$Req = 4\Omega$$

$$\left\{ V_C = 15e^{-t/0.4} \right.$$


$$V_x = \frac{12}{20} \times V_0 e^{-t/0.4}$$

$$= 3 \times 15 e^{-t/0.4}$$

$$\left\{ V_x = 9e^{-t/0.4} V \right\}$$

$$\left\{ i_x = \frac{V_x}{R} = 0.75e^{-t/0.4} A \right\}$$


Q9

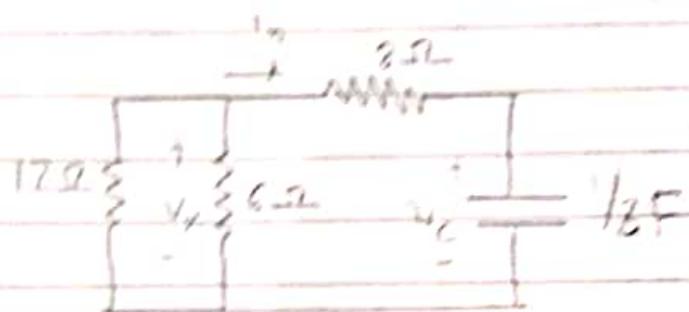

$$V_C(0) = 30V$$

Find V_C , V_L , i_R for $t > 0$

Q9

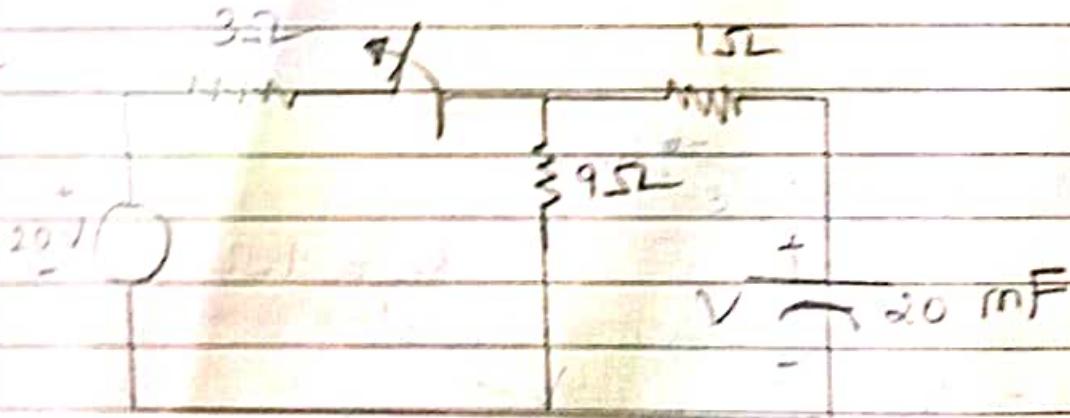

The switch in the ckt has been closed for a long time and it has been opened at $t=0$. Find $V(t)$ at $t=0$ also calculate the initial energy stored in the capacitor.

For $t < 0$ switch is closed
 cap \rightarrow open ckt.

$$i = \frac{20}{12}$$

$$= \frac{5}{3}$$

$$V_C = \frac{5}{3} \times 9$$

$$= 15 \text{ V}$$

\therefore Voltage across cap = 15 V

Since the voltage across capacitor cannot change instantaneously \therefore The voltage at $t = 0$ is same as voltage $t = 0^+$.

$$V_C(0) = 15 \text{ V}$$

$$V = V_0 e^{-t/RC}$$

$$= 15 e^{-t/10 \times 20 \times 10^{-3}}$$

$$= 15 e^{-5t} \text{ V}$$

$$\text{Energy} = W_C(0)$$


$$= \frac{1}{2} \times C \times V_0^2$$

$$= \frac{1}{2} \times 20 \times 10^{-3}$$

$$= \frac{1}{2} \times 20 \times 225$$

$$= 2.25 \text{ J}$$

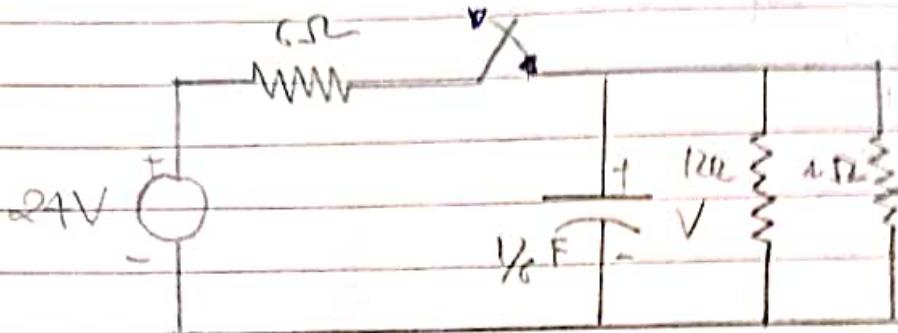Eg: Find $V(t)$ for $t > 0$; $W_c(0) = ?$



$$\frac{12 \times 4}{164} = 3\Omega$$

$$V_c = \frac{8 \times 24}{93}$$


$$= 8V$$

$$J = \frac{R_{eq} \cdot C}{L}$$

$$= \frac{1}{6} \times 3 = 0.5$$

$$V = 8e^{-2t} V$$
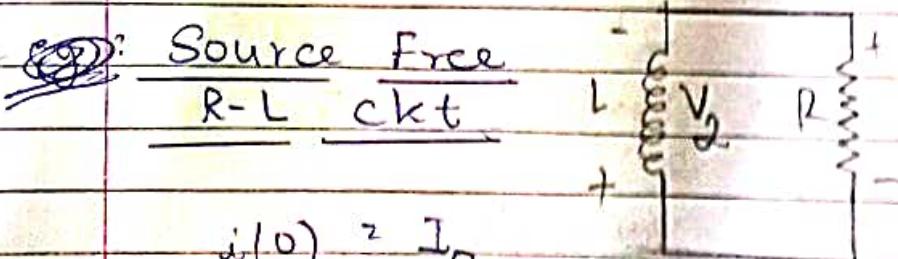
$$E(0) = \frac{1}{2} \times \frac{1}{6} \times 64 = \frac{16}{3} J$$



$$i(0) = I_0$$

$$\omega(0) = \frac{1}{2} L I_0$$

Applying KVL in the loop,

$$V_L + V_R = 0$$

$$\frac{d}{dt} L \frac{di}{dt} + i \cdot R = 0$$

$$\frac{di}{dt} + \frac{Ri}{L} = 0$$

$$\int_{I_0}^i \frac{di}{i} = - \int_0^t \frac{R}{L} dt$$


$$\ln\left(\frac{i}{I_0}\right) = -\frac{Rt}{L}$$

$$\frac{i}{I_0} = e^{-\frac{Rt}{L}}$$


$$\therefore i = I_0 e^{-\frac{Rt}{L}}$$

$$\left\{ \tau = L/R \right\}$$

$$\therefore i = I_0 e^{-t/\tau}$$

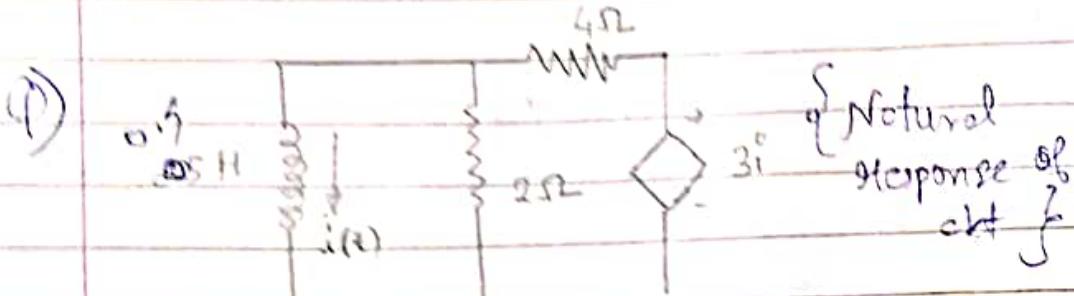

②

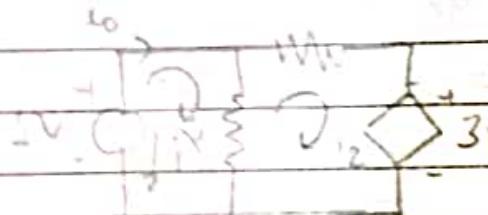

$$i_1 = -i_2 - i$$

$$-3i - 2(i_2 - i_1) - 4(i_2) = 0$$

~~$-3i - 2i_2$~~

$$-3i - 2i_2 + 2(-i) - 4i_2 = 0$$

$$6i_2 = -5i$$

$$i_2 = -\frac{5i}{6}$$

$$1 - (i_1 - i_2) \cancel{2} = 0$$

$$i_1 = -i$$

$$= 6/7 \mu A$$

$$1 - 2(-i) + 2i_2 \cancel{2} = 0$$

~~$1 + 2i_2 - 5i = 0$~~

~~$1 + 0 \cancel{7/6} = 0$~~

$$R = 1/(6/7)$$

$$= 7/6 \Omega$$

$$i = -6/7 \mu A$$

$$\frac{1}{2} + j_1 - j_2$$

$$\frac{1}{2} + j_1 - \frac{5}{6} j_2$$

$$j_1 = 3A$$

$$j_2 = \frac{5}{6} A$$

$$j_2 = 0.5A$$

$$R_{eq} = \frac{1}{2} \Omega$$

$$Z = L/R_{eq} = 3/2 \Omega$$

$$i(t) = 10 e^{-2t/3}$$


$$v(t) = L \frac{di(t)}{dt}$$

~~$$= -\frac{10}{3} e^{-2t/3}$$~~

$$\left(\frac{1}{2}\right) 10 \left(-\frac{2}{3}\right) e^{-2t/3}$$

$$v(t) = -10/3 e^{-2t/3} V$$
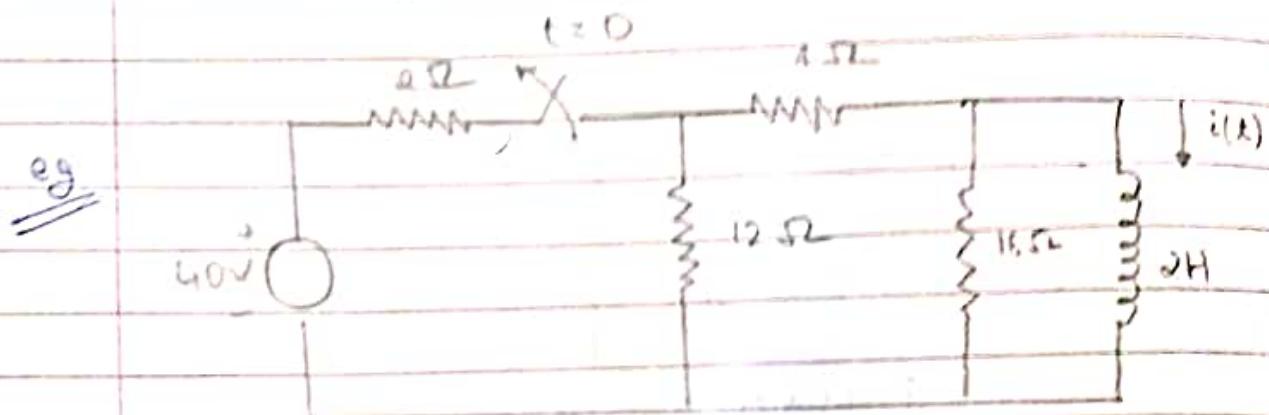
$$i(t) = \frac{v(t)}{Z} = -1677 e^{2t/3} A$$



$$i(t) = ?$$

for $t < 0$ switch is closed

~~$i_{eq} = \frac{40}{5} = 8A$~~

$$i_0 = \frac{40}{5} = 8A$$


~~$i_0 = \frac{80}{16.2}$~~

$$i(t) = \frac{12 \times 8}{16.2} = 6A$$




$$i = 6e^{-t/2}$$

$$Z = \frac{R + \cancel{L}}{2} = \frac{2 + 0.25}{84}$$

~~$i = 6e^{-4t}$~~

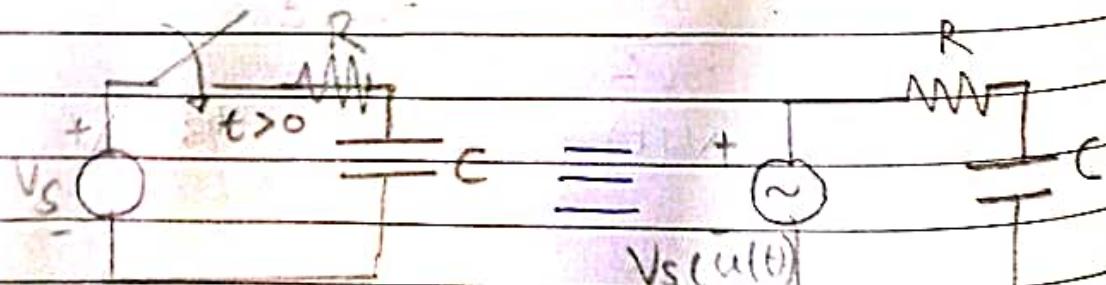

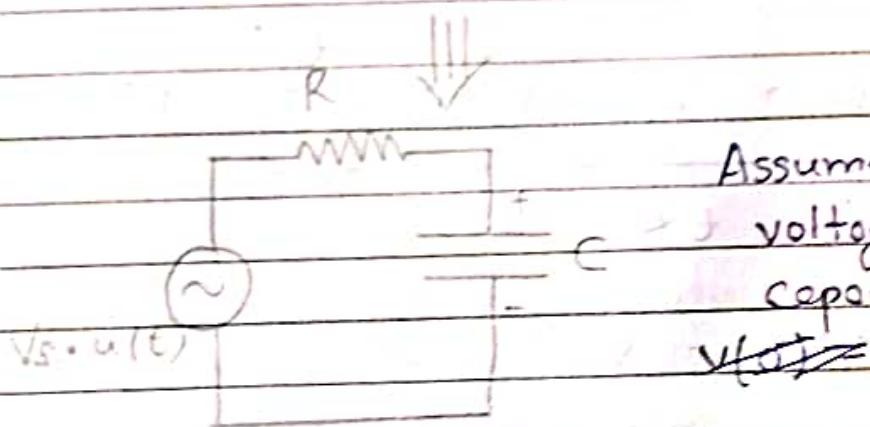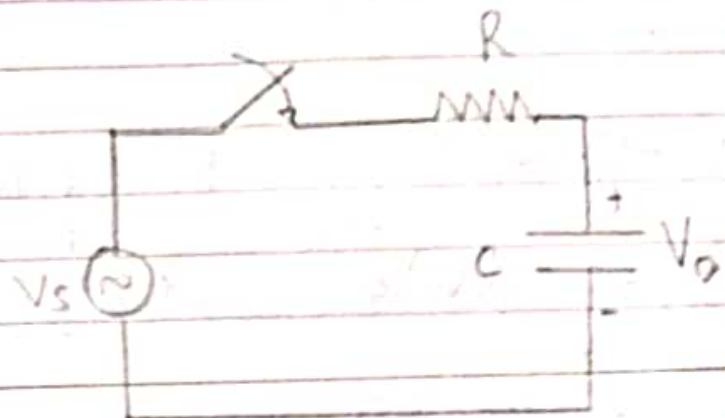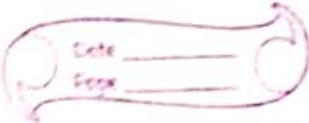switching action is replaced
by unit step.



Assume that initial voltage across capacitor.

$V(0^-)$ = voltage across capacitor just before switching

$V(0^+)$ = voltage across cap. just after switching

$$\frac{dV}{dt} + \frac{V}{RC} = \frac{Vs - u(t)}{R \cdot C} \quad (1)$$

For $t > 0$

$$v(t) \frac{dV}{dt} = - \left\{ \frac{-V + Vs(u(t))}{R \cdot C} \right\} \frac{1}{R \cdot C}$$

$$\int \frac{dV}{Vs - V} = - \frac{1}{RC} \int du$$

$$\ln(V - Vs) = -t/RC$$

$$\ln \left(\frac{V_t - Vs}{V_0 - Vs} \right) = -\frac{t}{RC}$$

$$V_t - V_s = (V_0 - V_s) e^{-t/RC}$$

$$V(t) = V_s + (V_0 - V_s) e^{-t/RC}; \quad t \geq 0$$

let $RC = J$

$$V(t) = V_s + (V_0 - V_s) e^{-t/J} \quad t \geq 0$$

for $t < 0$

$$V(t) \rightarrow V_0 \quad , t < 0$$

$$\rightarrow V_s + (V_0 - V_s) e^{t/J}, \quad t < 0$$


\downarrow
Forced
response

\downarrow
Natural
response

$$V(\infty) = V_s$$

$$\therefore V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/J} \quad t > 0$$

Step Response of R-L circuit

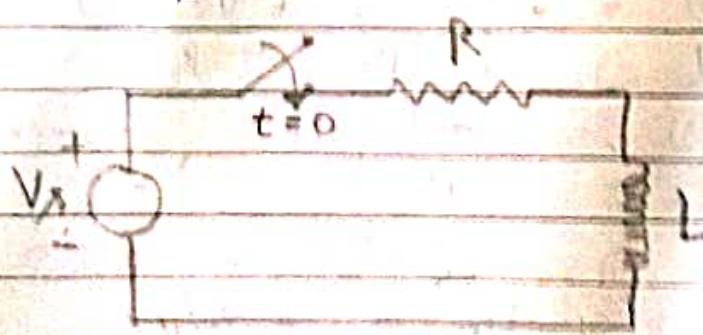

~~$i(t) = i_n + i_f$~~ — ①

②

Natural response,

$$i_n = A \cdot e^{-t/\tau} \quad \tau = L/R \quad \text{--- ②}$$

$$i_f = \frac{V_0}{R} \quad \text{--- ③}$$

$$i(t) = A \cdot e^{-t/\tau} + \frac{V_0}{R} \quad \text{--- ④}$$

let I_0 be the initial condition current through inductor.

$$i(0^-) = i(0^+) = i(0) = I_0$$



at $t=0$

$$I_0 = A + \frac{V_0 s}{R}$$


$$A = I_0 - \frac{V_0 s}{R} \quad \text{--- ⑤}$$

$$i(t) = \frac{V_0}{R} + \left(I_0 - \frac{V_0 s}{R} \right) e^{-t/\tau}$$
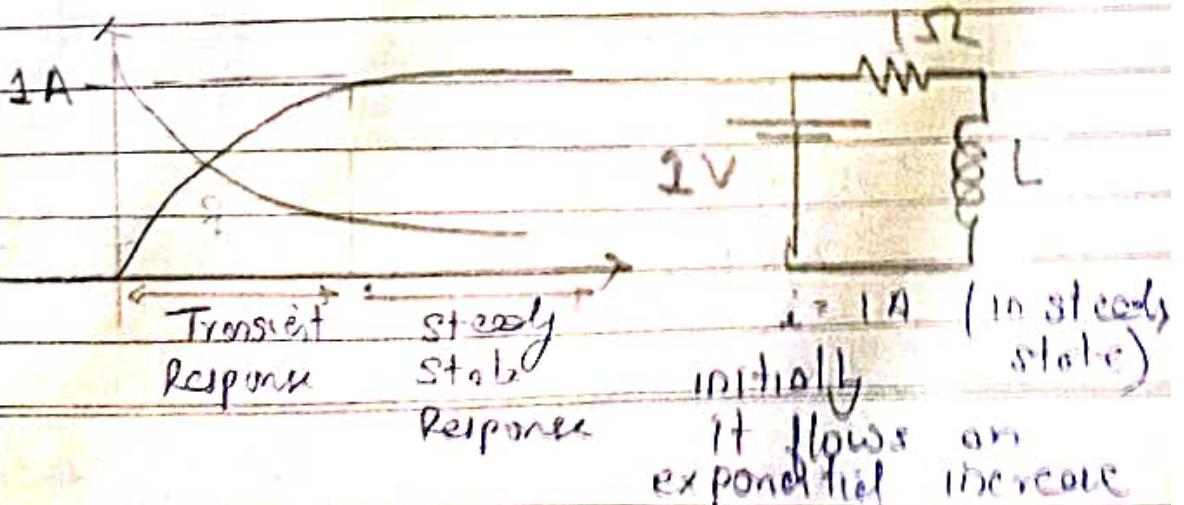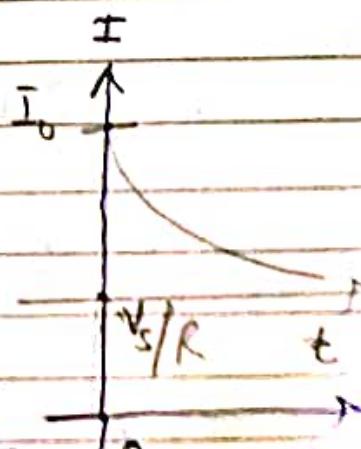
$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$



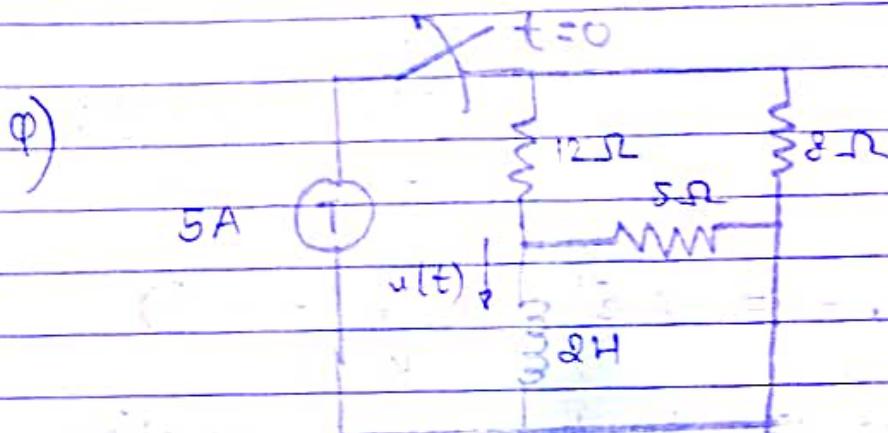only after 5 time constants, i reaches steady state at 2 A and remains constant.



Find $i(t)$ for $t > 0$

~~For $t < 0$~~


$$i_1 \leftarrow \frac{8}{20} \times 5 = 2A$$

$$\boxed{i(t) = 2A} \quad \text{for } t < 0$$

For $t > 0$,

$$E_L = 1/L_i^2$$

$$2 \times 2 \times 4$$

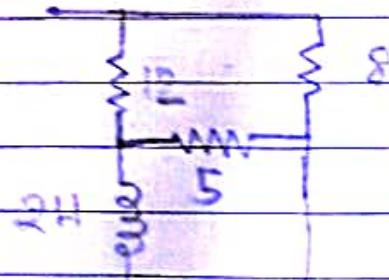


$$R = \frac{20 \times 5}{25} = 4\Omega$$

$$i = i_{0e}$$

$$\frac{J^2}{R} L = 2 = 0.5$$


$$i = 2e^{-t/0.5}$$

$$j = 2e^{-2t} \text{ A}$$

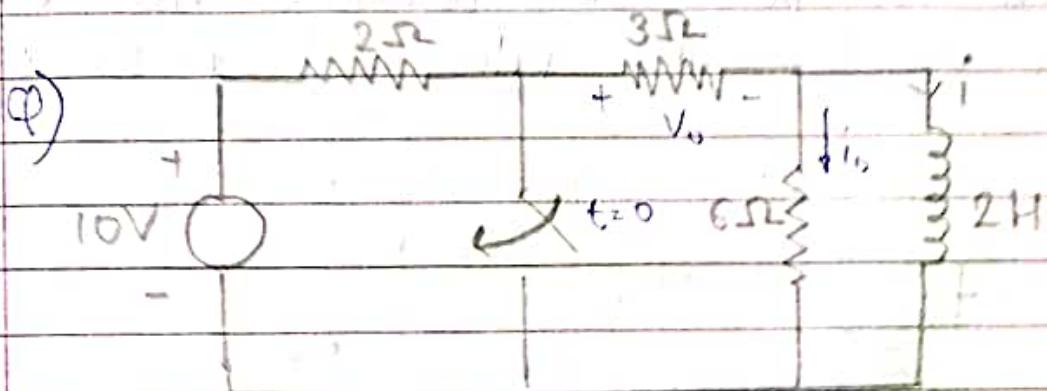

Find $i_0(t)$, $v_0(t)$ for $t < 0$, $t > 0$

For $t < 0$ For $t > 0$

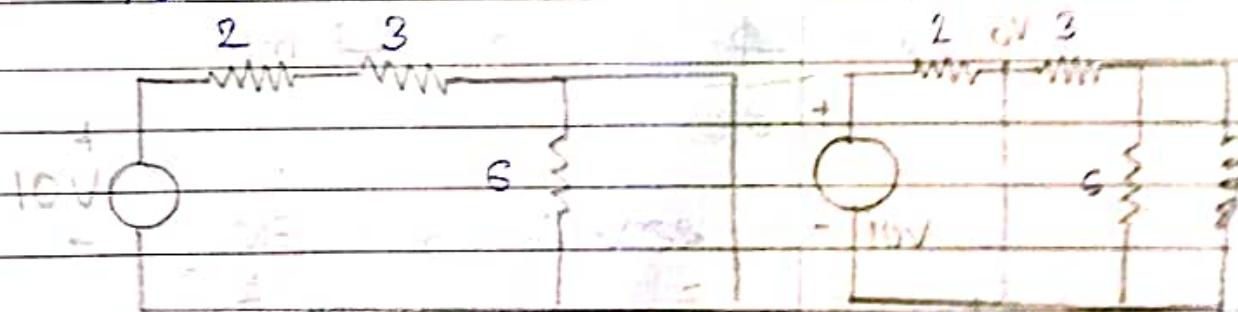

$$j = \frac{10}{5} = 2 \text{ A} = i_{01}$$

$$v_0 = 2 \times 3 = 6 \text{ V}$$

$t > 0$

$$j = i_0 e^{-t/4}$$

$$R = 18/9 = 2 \Omega$$

$$J = L/R$$

$$\left\{ J = 2/2 = 1 \text{ A} \right\}$$

$$j = 2e^{-t}$$


$$\frac{B^2}{R} \times 2e^{-t} / \%$$

$$[V_0 = -V_L] \quad \text{for } t > 0$$

$$i_0(t) = -\frac{2}{3} e^{-t}$$

$$i_0(t) = V_L / R$$

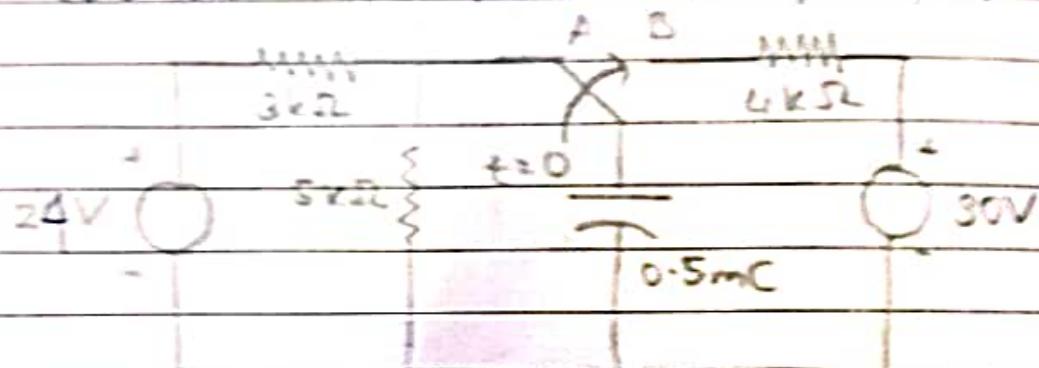C) The given circuit, the switch has been in position A for a long time. At $t=0$, the switch moves to position B. Determine $V(t)$ for $t \geq 0$ and calculate its value at $t=2\pi/3$



~~At $t < 0$,~~

At $t < 0$, 3

$$i = \frac{24}{5} \text{ mA} = 4.8 \text{ mA}$$

$V_C =$ ~~5~~ V across $5\text{k}\Omega$

$$= \frac{5}{80} \times 24 = 3$$

$$V(0) = 15 \text{ V}$$

for $t > 0$,

$$V(t) = V(\infty) + (V_0 - V_\infty) e^{-\frac{t}{RC}}$$

$$\Rightarrow J = RC = 4 \times 0.5 \times 10^3 \text{ s} = 2 \times 10^3 \text{ s}$$

$$V(\infty) = 30 \text{ V}$$



$$V(t) = 30 + -15e^{-\frac{t}{2}} = 30 - 15e^{-\frac{t}{2}}$$

$$t = 1 \text{ s} \quad \text{Initial value}$$

$$V(t) = 30 - 15e^{-\frac{t}{0.5}} \text{ V} = 20.9 \text{ V}$$

$$t = 4.8 \text{ s} \quad \text{Final value}$$
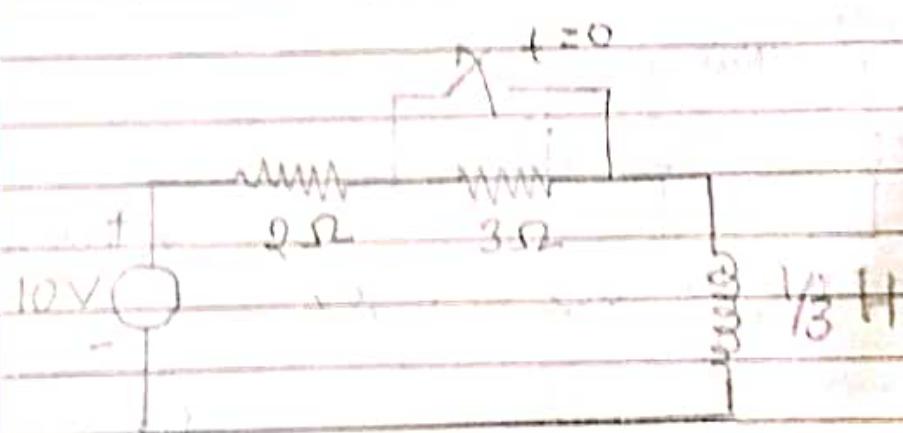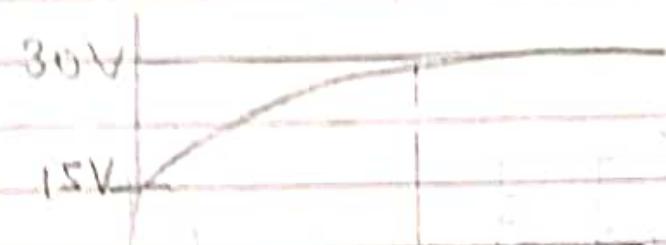
$$V(t) = 30 - 15e^{-\frac{4.8}{0.5}} \text{ V} = 27.97 \text{ V}$$



Find $i(t)$ for $t > 0$, assume that switch has been closed for a long time.

For $t < 0$,


$$i = \frac{10}{2} = 5 \text{ A}$$

$$\therefore i(0) = 5 \text{ A}$$

for $t > 0$


$$i_{\infty} = 2 \text{ A}, \quad i_2 = L/R^2 = 1/5 \text{ A}$$
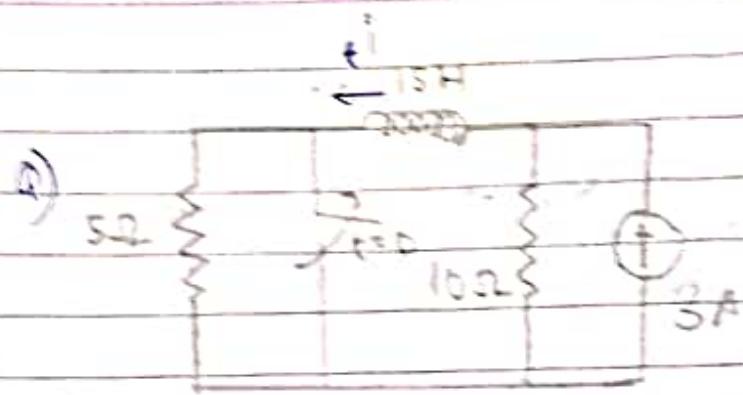
$$i(t) = i_{\infty} + (i_0 - i_{\infty}) e^{-t/1/5} = 2 + 3e^{-t/1/5}, \quad 5 + 3e^{-t/1/5} \text{ A}, \quad t > 0$$




Find $i_0(t)$ for $t > 0$

$t < 0$

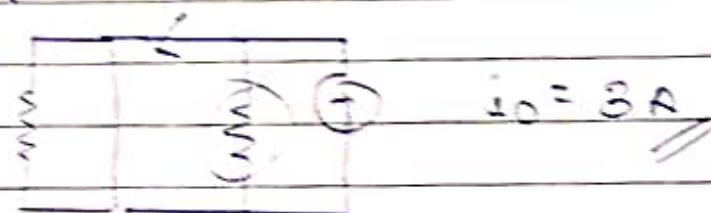

$t > 0$

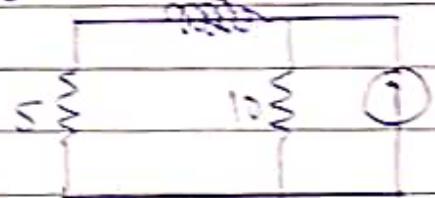

$$i_{00} = 0 \quad \frac{10}{15} \times 3 = 2A \quad \left. \begin{matrix} 5 \\ 5 \end{matrix} \right\} \quad \left. \begin{matrix} 5 \\ 10 \end{matrix} \right\}$$

$$i(t) = i_{00} + (i_0 - i_{00}) e^{-t/5}$$

$$= 2 + e^{-t/5}$$

$$J = \frac{L}{R} = \frac{1.5}{15} = 0.1 \text{ sec}$$

$$i(t) = 2 + e^{-\frac{t}{0.1}} A$$