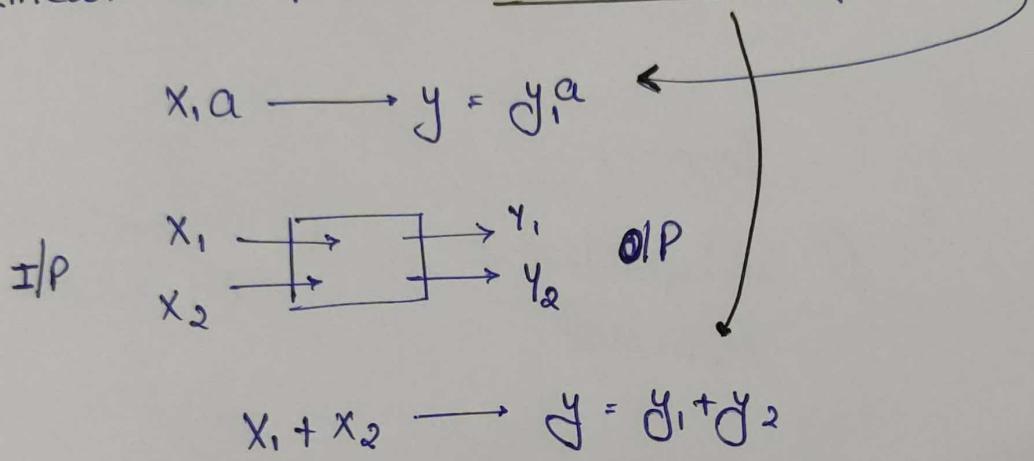


Linear ckt follows additive property. & Homogeneity prop.



→ R,L,C Circuit \Rightarrow Linear ckt

if. $i_1 = e^{v_1}$
 $i_2 = e^{v_2}$

$i = i_1 + i_2 = e^{v_1} + e^{v_2}$

$\frac{i}{i} = \frac{e^{v_1} + e^{v_2}}{e^{v_1 + v_2}}$

} Non Linear


$$\begin{aligned} i_1 &= e^{v_1} \\ i_2 &= e^{(v_1 + v_2)} \end{aligned}$$

→ Active Element ⇒ Any thing capable of generating energy.
 ↳ Generator, Battery

→ Passive Element ⇒
 ↳ R, L, C


Sources

① Ac or Dc


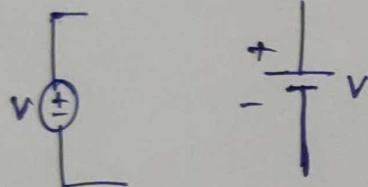


② Independent & dependent

③ Voltage Source
or Current -

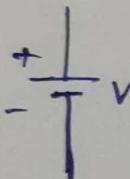

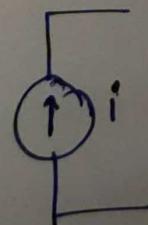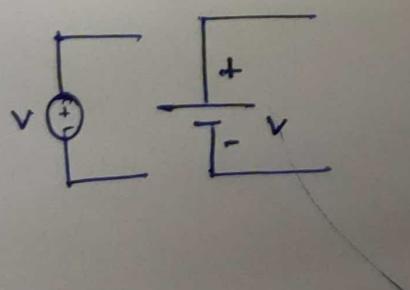- In ideal independent source, is an active element that provides specified voltage, current that is completely independent of other circuit variables.





$$f = l + n - 1$$

31/July/24

→ Dependent Source \Rightarrow (Controlled) is an active element in which the source quantity is controlled by another voltage or current.

Representation \Rightarrow

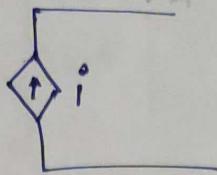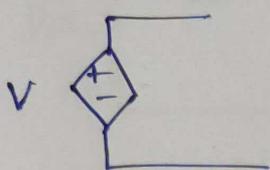


i) Voltage Controlled Current Source

ii) Current Controlled

i) Voltage controlled voltage source
ii) Current controlled

→ Branch \Rightarrow If represent single element such as voltage source or current

or any other element.

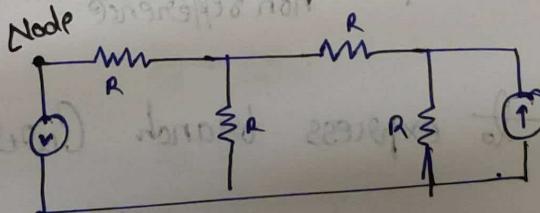


6 Branches

→ Node \Rightarrow Point of Connection b/w two or more branches.

→ Loop \Rightarrow Closed Path in Ckt.

A network with 'b' branches, 'n' independent loop & 'n' nodes will satisfies fundamental theorem.


Nodal Analysis

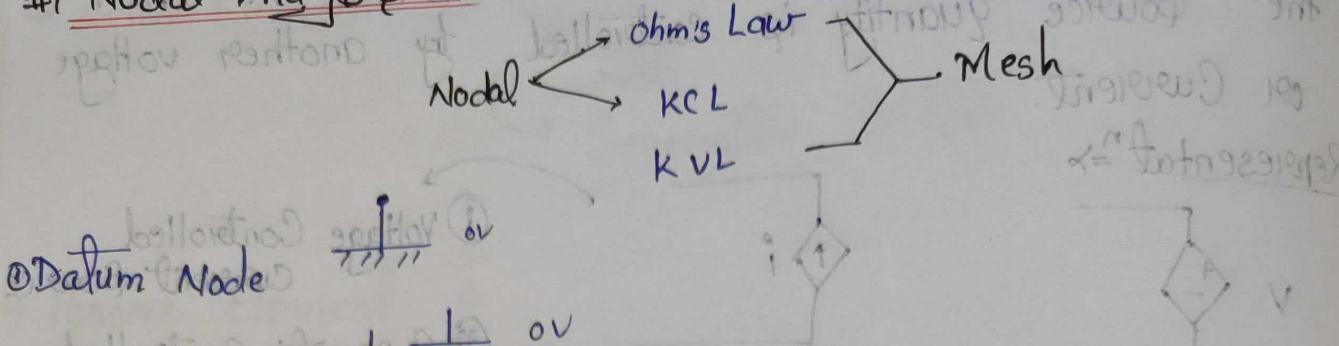

→ Steps to solve nodal analysis →

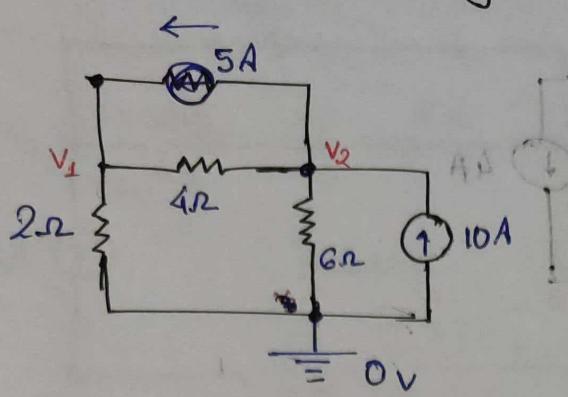- i) Select a node as reference node.
- ii) Assign voltages $(V_1, V_2, \dots, V_{n-1})$ to the remaining $n-1$ nodes.
- iii) Apply KCL to each of $(n-1)$ nodes (non-reference nodes).
- iv) Use ohm's law to express branch currents in terms of node voltages.
- v) Solve the resulting simultaneous equations to obtain unknown node voltages.

Que. 1) Calc. the node-voltages in the ckt. 02/Aug/24



At Node -1

$$\frac{V_1 - V_2}{4\Omega} + \frac{V_1 - 0}{2} + (-5) = 0$$

$$0 = \frac{V_1 - V_2}{4\Omega} + \frac{V_1 - 0}{2} - 10 = 0$$

$$V_1 - V_2 + 2V_1 - 20 = 0$$

$$3V_1 - V_2 = 20 \quad \text{--- (1)}$$

At Node -2

$$\frac{V_2 - V_1}{4} + \frac{V_2 - 0}{6} - 10 = 0$$

$$+5$$

$$3V_2 - 3V_1 + 2V_2 - \frac{60}{6} = 0$$

$$5V_2 - 3V_1 = \frac{120}{6} \quad \text{--- (2)}$$

$$15V_1 - 5V_2 = 100$$

$$-3V_1$$

$$4V_2 = 40 \quad 80$$

$$V_2 = 35 \text{ v}$$

$$V_1 =$$

$$\boxed{V_2 = 20 \text{ v}}$$

$$V_1 = \frac{20 + V_2}{3} = \frac{55}{3}$$

$$\boxed{V_1 = \frac{40}{3} \text{ v}}$$


Cramer's Rule

$$\begin{bmatrix} 3 & -1 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 60 \end{bmatrix}, \Delta = 12$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{bmatrix} 20 & -1 \\ 60 & 5 \end{bmatrix}}{12} = \frac{40}{3} \text{ v}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{bmatrix} 3 & 20 \\ -3 & 60 \end{bmatrix}}{12} = 20 \text{ v}$$

Que.) Obtain the node volt. in ckt

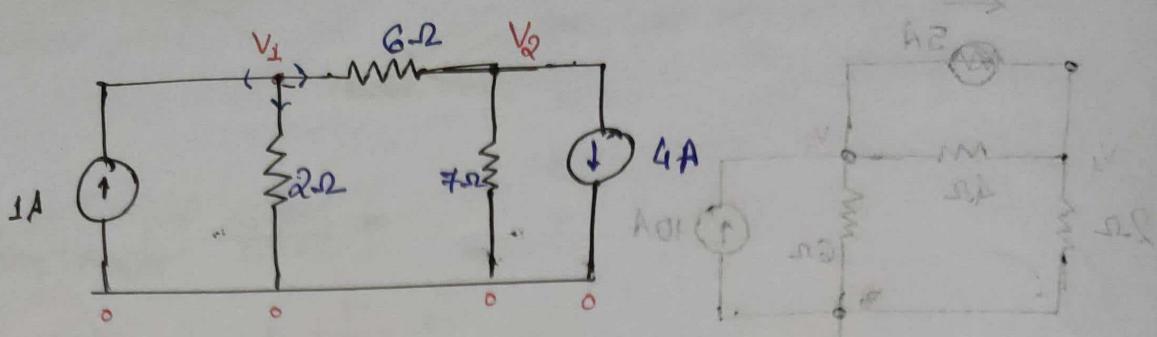

At Node - 1

By Applying KCL

$$-1 + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{6} = 0$$

→ 3 +

$$-6 + 3V_1 + V_1 - V_2 = 0$$

$$4V_1 - V_2 = 6 \quad \text{---(1)}$$

At Node - 2

$$\frac{V_2 - V_1}{6} + \frac{V_2 - 0}{7} + 4 = 0$$

$$7V_2 - 7V_1 + 6V_2 + 168 = 0$$

$$-7V_1 + 13V_2 = -168 \quad \text{---(2)}$$

$$\boxed{V_1 = -2 \text{ V}}$$

$$\boxed{V_2 = -14 \text{ V}}$$

$$0.8 \text{ ohm} = 2\text{V}$$

$$50\Omega = 2\text{V} - 1\text{V}$$

$$V_{CE} = 2\text{V}$$

$$= 1\text{V}$$

$$\boxed{V_{DS} = 2\text{V}}$$

$$\begin{bmatrix} 0 & 1 \\ 0 & 0 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 2 & 3 \\ 3 & 2 \end{bmatrix}$$


$$\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

Ques.) Determine Volt. at Node

02/Aug/24

efficiency short cut both

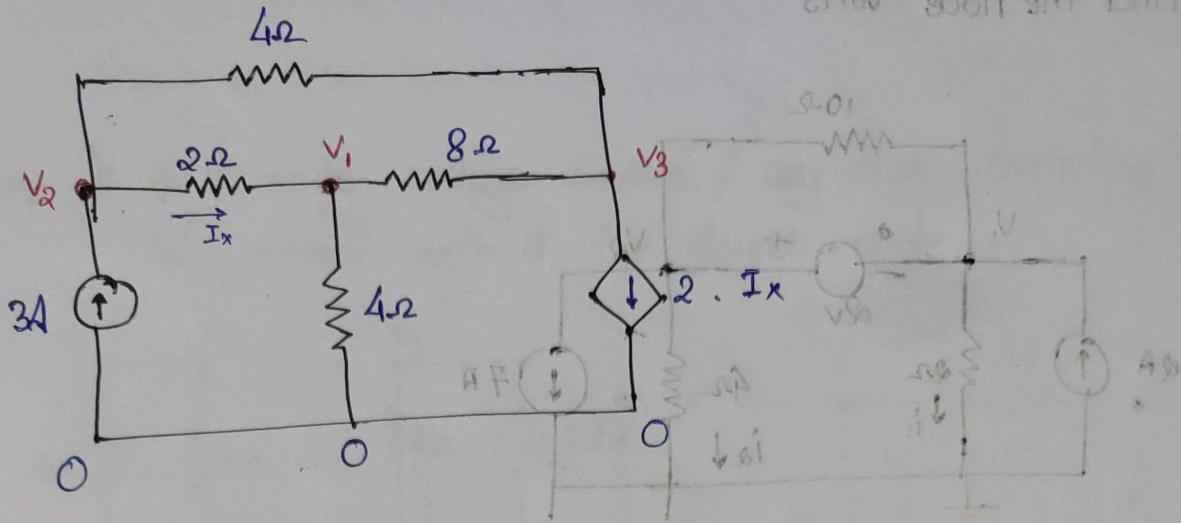

$$\frac{V_1 - V_2}{2} + \frac{V_1 - 0}{4} + \frac{V_1 - V_3}{8} = 0$$

$$4V_1 - 4V_2 + 2V_1 + V_1 - V_3 = 0$$

$$7V_1 - 4V_2 - V_3 = 0 \quad \text{--- (1)}$$

$$\frac{V_2 - V_3}{4} + \frac{V_2 - V_1}{2} + 3 = 0$$

$$V_2 - V_3 + 2V_2 - 2V_1 + 12 = 0$$

$$-2V_1 + 3V_2 - V_3 = -12 \quad \text{--- (2)}$$

$$\frac{V_3 - V_2}{4} + \frac{V_3 - V_1}{8} + 2I_x = 0$$

$$2V_3 - 2V_2 + V_3 - V_1 + 16 = 0$$

$$-V_1 - 2V_2 + 3V_3 = -16 = 0 \quad \text{--- (3)}$$

$$I_x = \frac{V_2 - V_{0.1}}{2}$$

$$\frac{V_3 - V_2}{4} + \frac{V_3 - V_1}{8} + V_2 - V_{0.1} = 0$$

$$2V_3 - 2V_2 + V_3 - V_1 + 8V_2 - 8V_{0.1} = 0$$

$$7V_1 - 10V_2 + 3V_3 = 0$$


$$-9V_1 + 6V_2 + 3V_3 = 0$$

$$V_1 = -2.4V$$


$$V_2 = -4.8V$$

$$V_3 = 2.4V$$

Q.) Find the node voltages

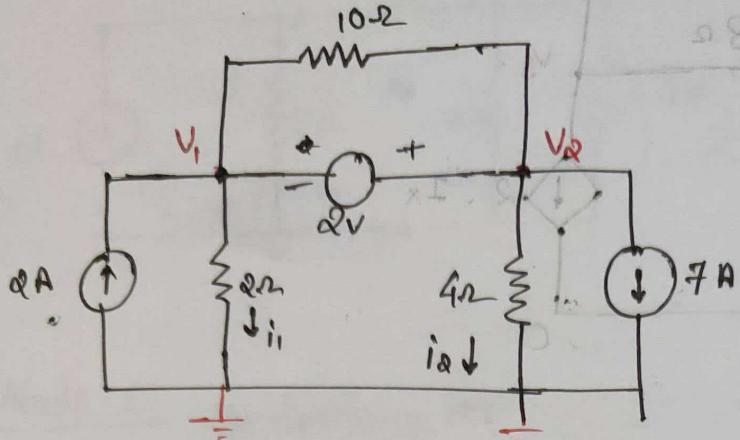

shown to have $V_1 = 8$

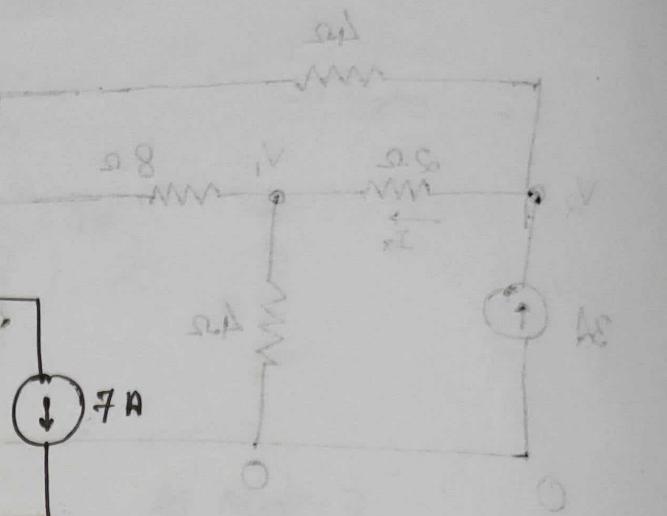

$$0 = \frac{V_1 - V_2}{10} + \frac{V_1}{2} - 2 = 0$$

$$0 = \frac{V_1 - V_2}{8} + \frac{0 - V_2}{4} + \frac{8V - V_2}{2}$$

$$0 = 8V - 1V + 1V - 8V + 8V - 8V$$

$$0 = 8V - 1V + 1V - 8V + 8V - 8V$$


Supernode Analysis

- For the above Circuit voltage source is present b/w two non reference source. which forms a Super node. In such cases we apply both KCL & KVL to determine node voltages.
- A Super node is formed by enclosing dependent or independent source connected with the two non-reference source connected node & any element connected in parallel with it.

06/ Aug/24

* The super node contains 2 volt source

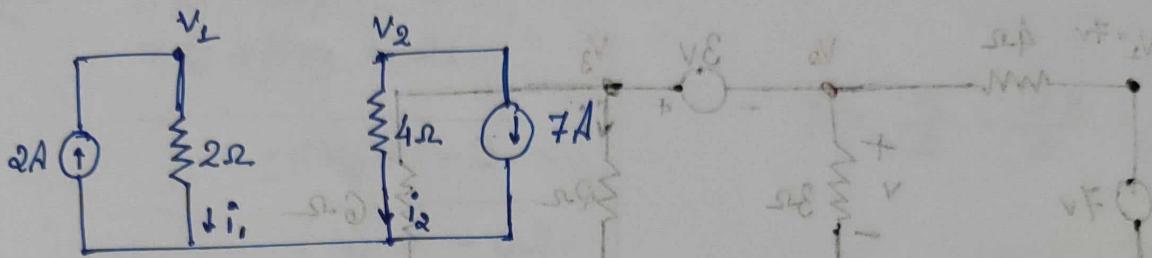* Step-1 \Rightarrow Remove voltage source & any other branches in parallel with the super node.




① Apply KCL at super node \rightarrow

$$-2 + \frac{V_1}{2} + \frac{V_2}{4} + 7 = 0$$

$$2V_1 + V_2 = -20 \quad \text{--- (1)}$$

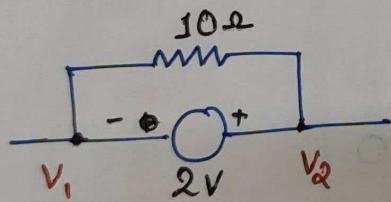② Restore super node & apply KVL \rightarrow



Apply KVL,

$$V_1 + 2 - V_2 = 0 \quad \text{--- (2)}$$

$$V_1 - V_2 = -2$$

from eqn 1 & 2

$$3V_1 = -22$$


$$V_1 = -7.33$$

$$V_2 = -5.33$$


Note →

10Ω Resistor does not make any diff.
because it is connected across super node.

Q. 2)

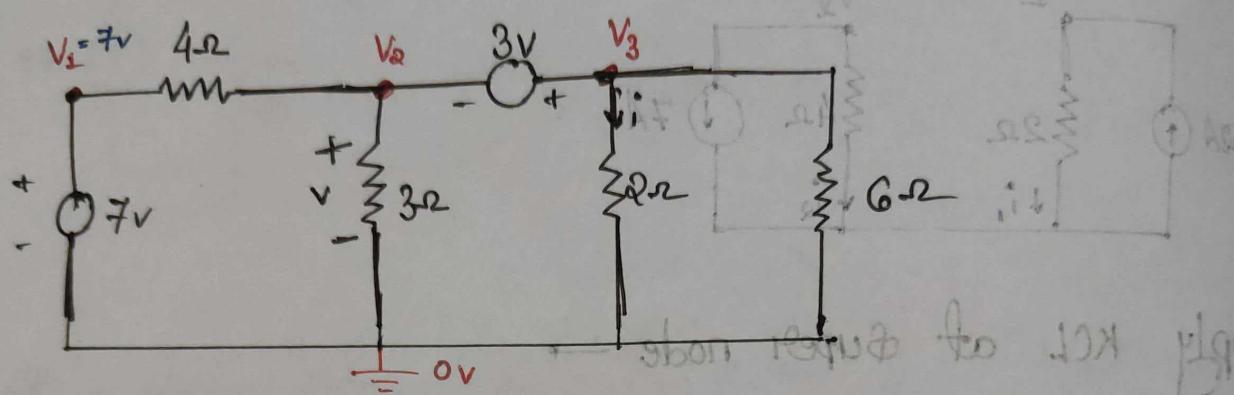

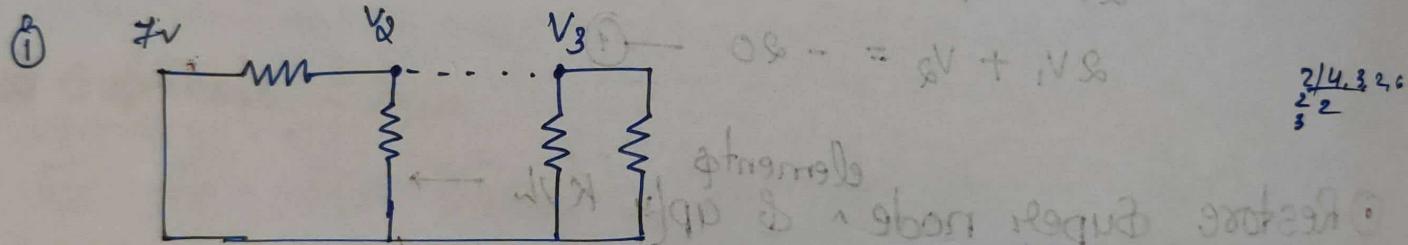
$$0 = 7 + \frac{8V}{4} + \frac{2V}{3} + 3 -$$



2/4.3/2


KCL →
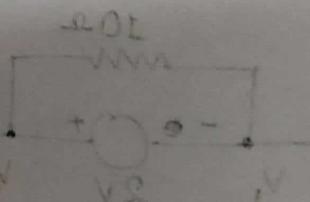
$$\frac{V_0 - 7}{4} + \frac{V_2}{3} + \frac{V_3}{2} + \frac{V_3}{6} = 0$$



$$3V_2 - 21 + 4V_0 + 6V_3 + 2V_3 = 0$$
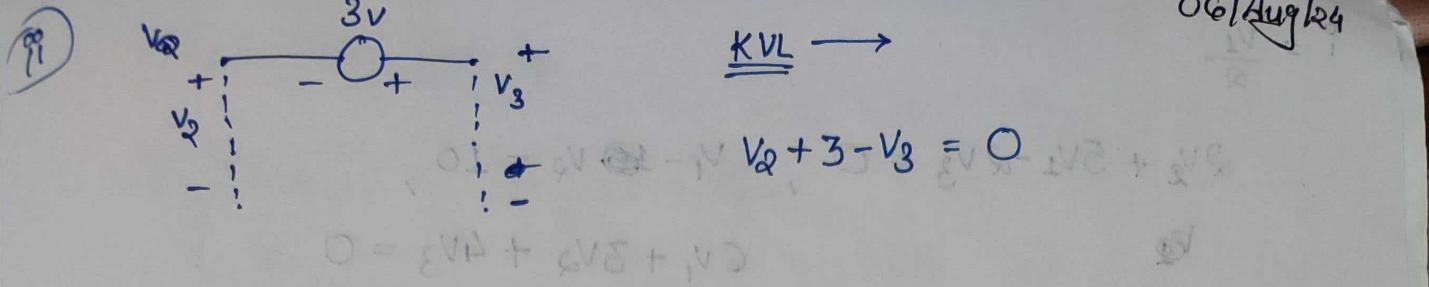
$$7V_2 + 8V_3 = 21 \quad \text{--- (1)}$$




$$\begin{array}{l} 7V_2 \quad 8V_2 - 8V_3 = -24 \\ 7V_2 + 8V_3 = 21 \\ \hline 15V_2 = -3 \end{array}$$

$$V_2 = -0.2V$$

$$V_3 = 2.8V$$

Ans

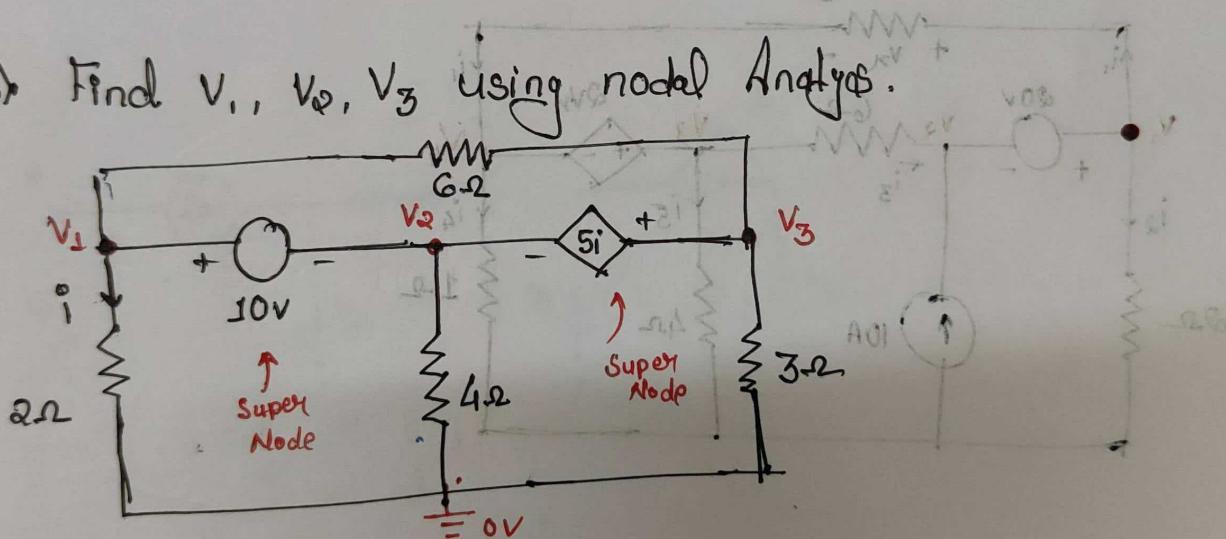Ques) Find V_1 , V_2 , V_3 using nodal Analysis.



①

KCL \rightarrow

$$\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{3} = 0$$

$$6V_1 + 3V_2 + 4V_3 = 0 \quad \text{--- (1)}$$

②

KVL \rightarrow

$$V_1 - 10 - V_2 = 0 \quad \text{--- (2)}$$

$$V_2 + 5i - V_3 = 0 \quad \text{--- (3)}$$

$$i = \frac{V_1}{\alpha}$$

$$2V_2 + 5V_1 - 2V_3 = 0, \quad V_1 - 10V_2 = 10,$$

$$6V_1 + 3V_2 + 4V_3 = 0$$

$$\boxed{V_1 = 3.04 \text{ V}}$$

$$\boxed{V_3 = 0.65 \text{ V}}$$

$$\boxed{V_2 = -6.95 \text{ V}}$$



$$PS = 2V_8 - 5V_8$$

$$LS = 8V_8 + 5V_8$$

$$E = 8V_8$$

$$V_{8.0} = 8V$$

Que.) Find the node-voltage.

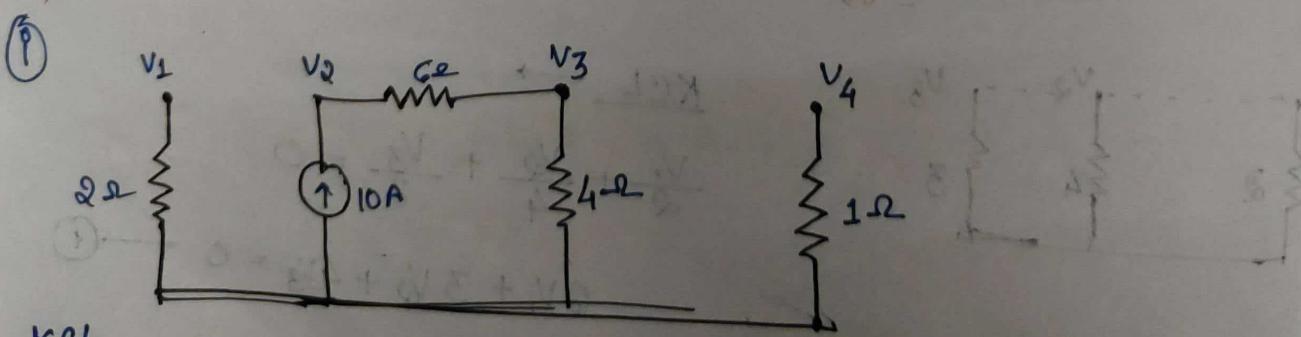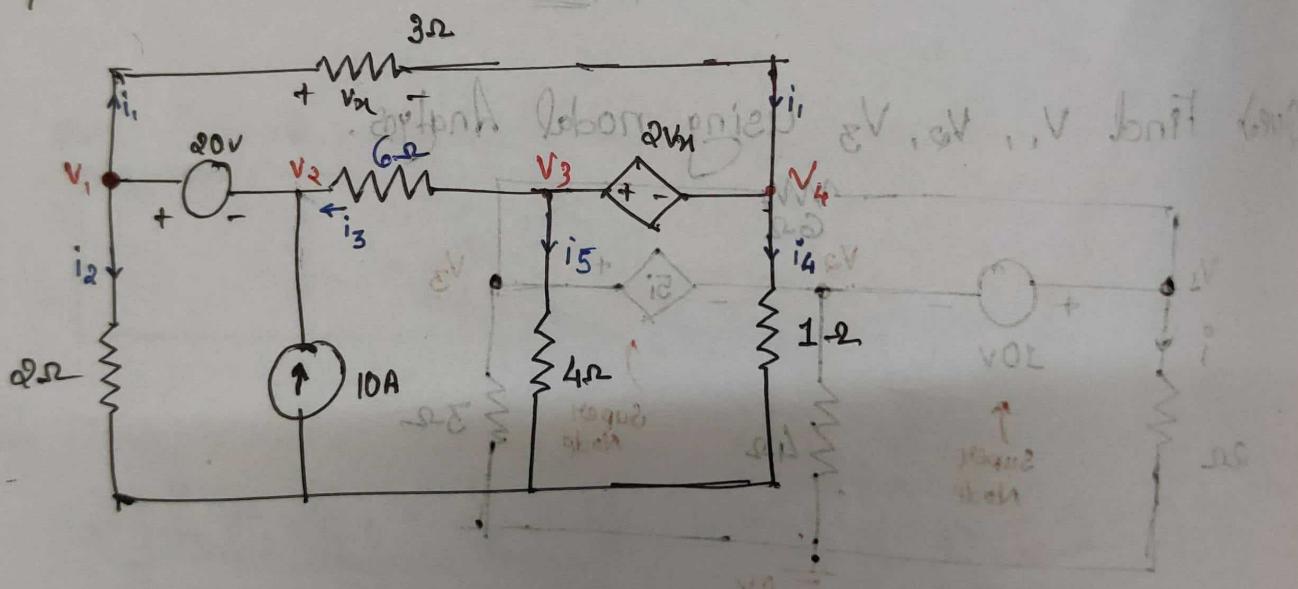

KCL

$$\frac{V_1}{2} - 10 = 0$$

$$0 = 8V - 10 + j$$

$$i_3 + i_0 = i_1 + i_2$$

$$\frac{V_3 - V_2}{6} + 10 = \frac{V_{41} - V_4}{3} + \frac{V_1}{2}$$



$$5V_1 + V_2 - V_3 - 2V_4 = 60 \quad \rightarrow ①$$

$$i_1 = i_4 + i_3 + i_5$$

$$\frac{V_1 - V_4}{3} = \frac{V_4}{1} + \frac{V_3 - V_2}{6} + \frac{V_3}{4}$$

\swarrow_{10}
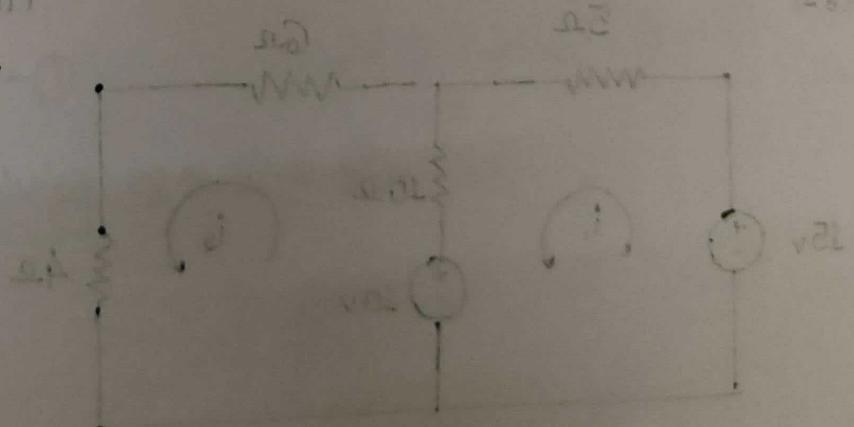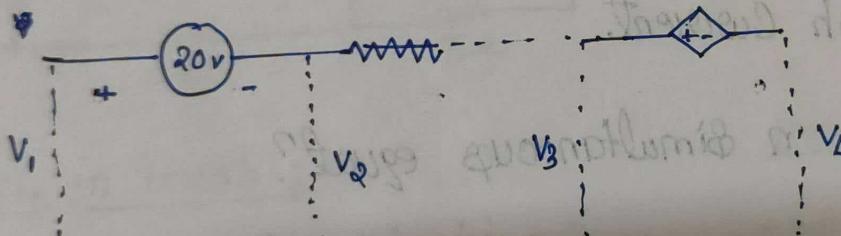
$$4V_1 + 2V_2 - 5V_3 - 16V_4 = 0 \quad \rightarrow ②$$



Mesh Analysis

It is a loop that does not contain any other loop inside.


A Mesh is a loop that

- Mesh analysis is applicable to planar of ckt only.
- A planar ckt is one that can be drawn in plane with no branches crossing one another.

* Steps to solve ⇒

- Identify no. of meshes and assign a mesh Current i_1, i_2, \dots, i_n .
- Apply KVL and use the Ohm's Law to express the voltages in terms of mesh Current.
- Solve the resulting simultaneous equations.

Ques. 1)

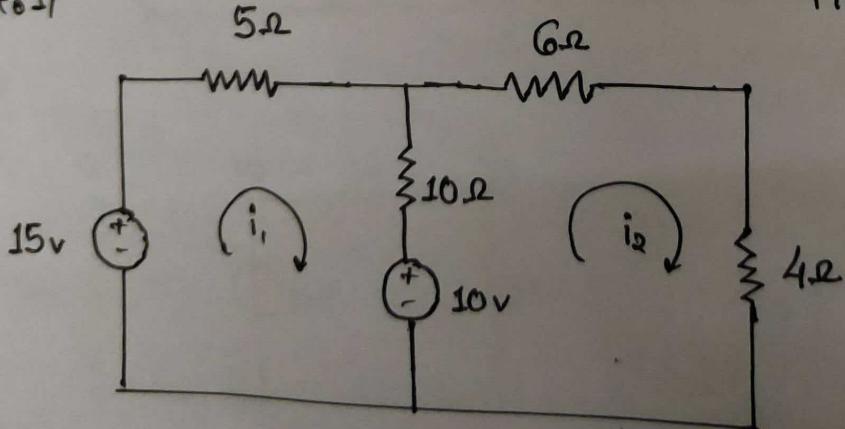

Find the mesh Current in ckt?

07/08/2024

KVL in mesh-1 \Rightarrow


$$15 - 5i_1 - 10(i_1 - i_2) - 10 = 0$$

$$-15i_1 + 10i_2 = -5 \quad \textcircled{1}$$


KVL in mesh-2 \Rightarrow

$$10 - 10(i_2 - i_1) - 6i_2 - 4i_2 = 0$$
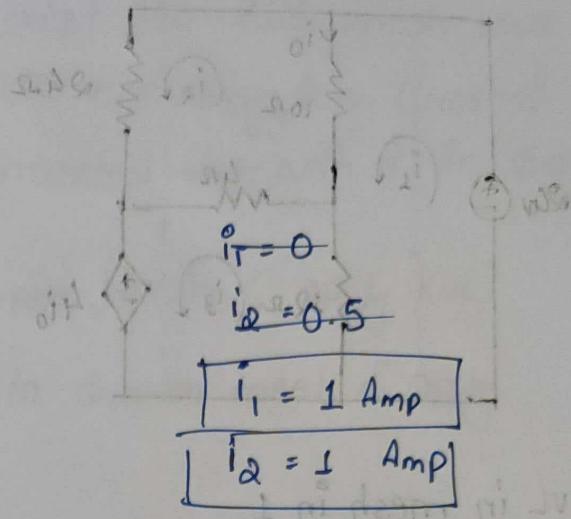
$$10i_1 - 20i_2 = -10 \quad \textcircled{2}$$



Q.2)

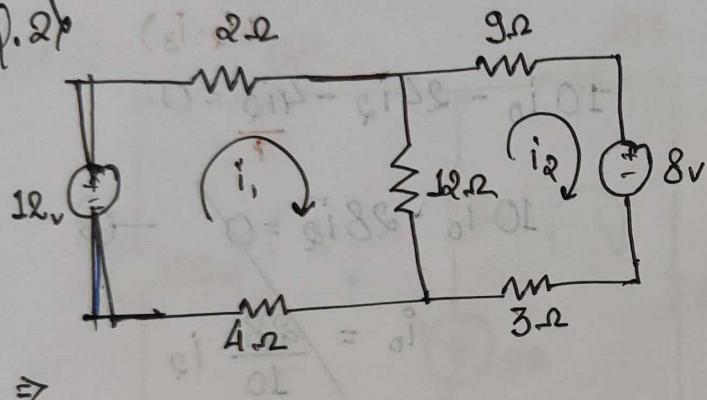

KVL in mesh-1

$$12 - 2i_1 - 12(i_1 - i_2) - 4i_1 = 0$$

$$-18i_1 + 12i_2 = -12 \quad \textcircled{1}$$

$$-12(i_2 - i_1) - 9i_2 - 8 - 3i_2 = 0$$

$$12i_1 - 24i_2 = 8 \quad \textcircled{2}$$

By solving eqn $\textcircled{1}$ & $\textcircled{2}$

$$i_1 = 0.66$$


$$i_2 = 0 \text{ Amp}$$

Super Mesh Analysis


07/ Aug/ 24

- i) When a Current Source exist b/w two mesh, we create a Super mesh by exp excluding the Current Source and any element connected therewith in series.
- ii) Remove the Current source in Super mesh & apply KVL.
- iii) Restore the Current source in Super mesh & apply KCL at corresponding node.

Ques. 1)

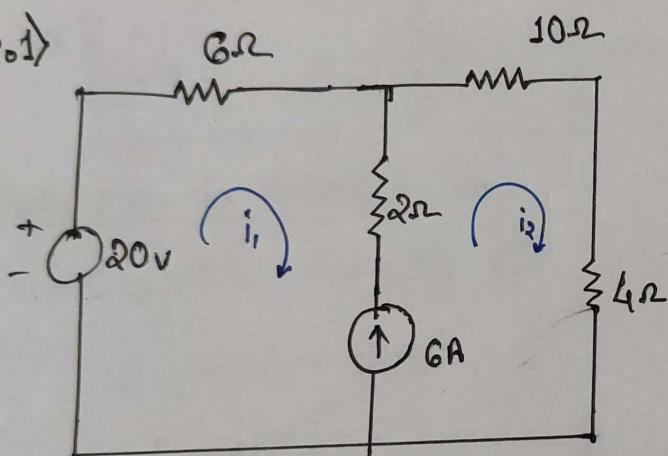


Ex

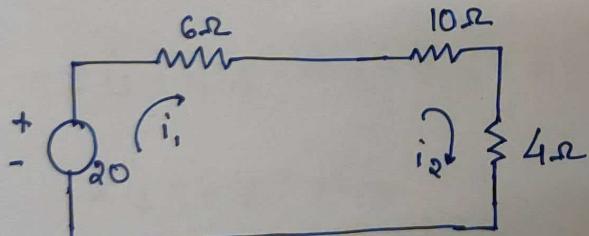

Applying KVL to Super mesh

$$20 - 6i_1 - 10i_2 - 4i_2 = 0$$
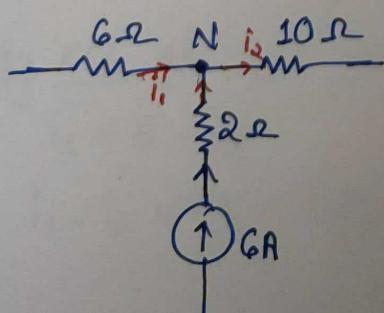
$$6i_1 + 14i_2 = 20 \quad \text{--- (1)}$$



Applying KCL at node N



$$-i_1 - 6 + i_2 = 0$$

$$i_1 - i_2 = -6 \quad \text{--- (2)}$$



$$\begin{aligned} i_1 &= 5.2 \text{ Amp} & i_1 &= -3.2 \text{ Amp} \\ i_2 &= -0.8 \text{ Amp} & i_2 &= 2.8 \text{ Amp} \end{aligned}$$

09/Aug/24

Q.)

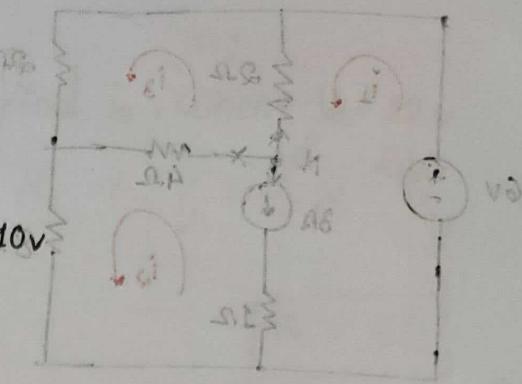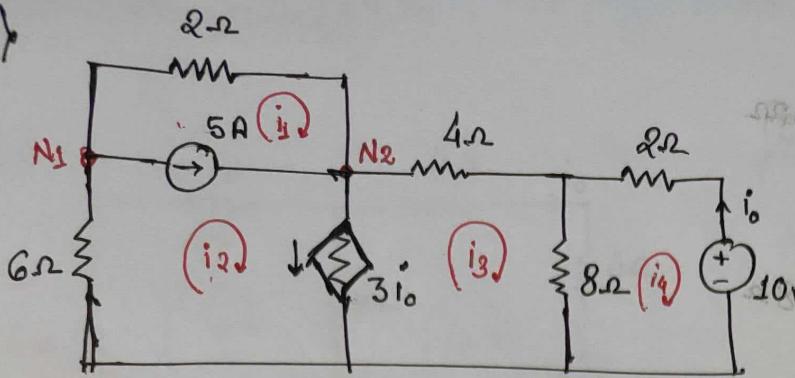

draw in mesh

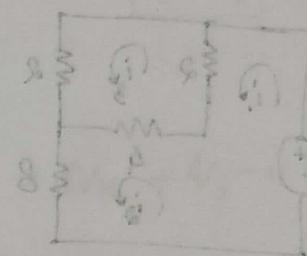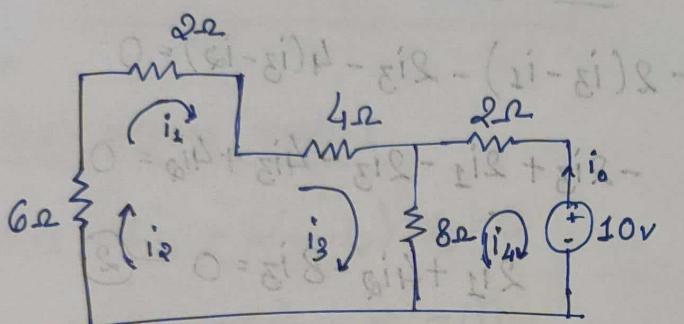

Apply KVL in Super mesh.

$$-6i_2 - 2i_1 - 4i_3 - 8(i_3 - \frac{i_4}{8}) = 0$$

~~$$2i_1 + 6i_2 + 12i_3 = 0$$~~

~~$$i_1 + 3i_2 + 6i_3 = 0 \quad \text{--- (1)}$$~~

~~$$-2i_1 - 6i_2 - 4i_3 - 8i_3 + 8i_4 = 0$$~~

~~$$2i_1 + 6i_2 + 12i_3 - 8i_4 = 0$$~~

~~$$i_1 + 3i_2 + 6i_3 - 4i_4 = 0 \quad \text{--- (2)}$$~~

$$0 = 8i_2 - (i_1 - i_4) - 2i_4 - 10 = 0$$

$$0 = 8i_2 - i_1 + i_4 - i_1 + i_2 - 10i_4 + 8i_3 = 10$$

$$\textcircled{1} - \textcircled{2} : 8i_3 - 10i_4 = 10 \quad \textcircled{3}$$

Since we get

Subtract

Apply KCL at N_1 & N_2 .

$$i_1 + 5 = i_2$$

$$i_1 - i_2 = -5 \quad \text{--- (3)}$$

$\underline{N_2}$


$$5 + i_1 - 3i_0 - i_3 = 0$$

$$i_1 - i_3 + 3i_4 = -5 \quad \text{--- (4)}$$


$$i_1 = -7.5 \text{ Amp} \quad i_3 = 3.9 \text{ Amp}$$

$$i_2 = -2.5 \text{ Amp} \quad i_4 = 2.14 \text{ Amp}$$

(Q.2)

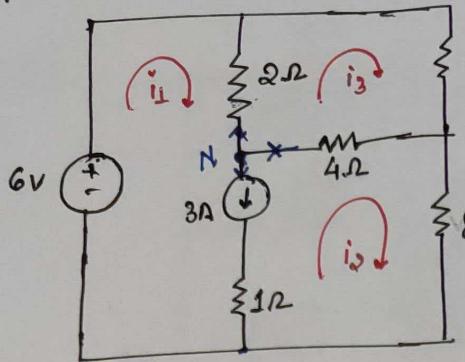

Ciri

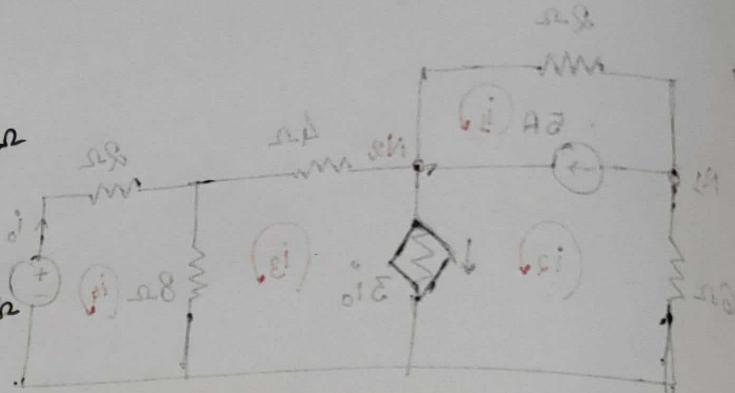


KVL in mesh

$$-2(i_3 - i_1) - 2i_3 - 4(i_3 - i_2) = 0$$

$$-2i_3 + 2i_1 - 2i_3 - 4i_3 + 4i_2 = 0$$

$$2i_1 + 4i_2 - 8i_3 = 0 \quad \text{--- (2)}$$

⇒

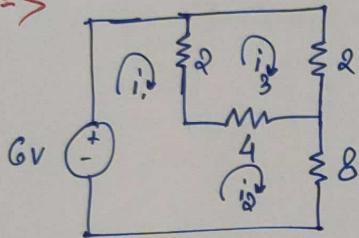

$$6 - 2(i_1 - i_3) - 4(i_2 - i_3) - 8i_2 = 0$$

$$6 - 2i_1 + 2i_3 - 4i_2 + 4i_3 - 8i_2 = 0$$

$$-2i_1 - 12i_2 + 6i_3 = 8 - 6 \quad \text{--- (1)}$$

KCL at Node

$$i_1 + i_3 = 3 \quad \text{--- (3)}$$

~~$$(i_3 - i_1) + (i_3 - i_2) = 3$$~~

~~$$-i_1 - i_2 + 2i_3 = 3 \quad \text{--- (4)}$$~~

~~$$(i_3 - i_1) + (i_2 - i_3) + 3 = 0$$~~

~~$$-i_1 + i_2 = -3 \quad \text{--- (5)}$$~~

~~$$i_1 = 2.18 \text{ Amp}$$~~

~~$$i_2 = 0.545 \text{ Amp}$$~~

~~$$i_3 = 0.818 \text{ Amp}$$~~

At Node
take all current
outward

$$i_1 = 3.4 \text{ Amp}$$

$$i_2 = 0.47 \text{ Amp}$$

$$i_3 = 1.1 \text{ Amp}$$

App


-6i

6

✓ V_E

✓ V_G

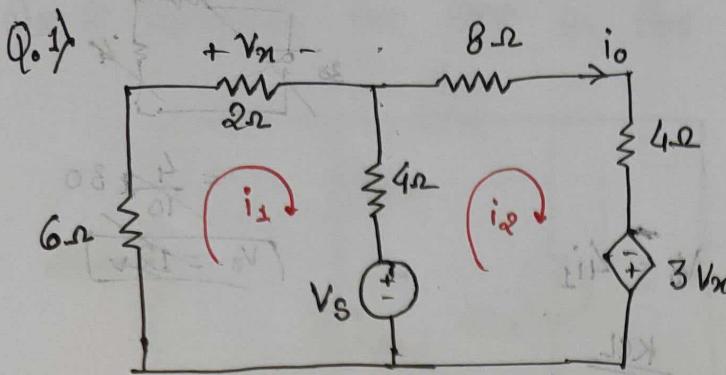Circuit Theorem \Rightarrow $V_{21} = i_1 \cdot R_1 + V_s$ brief 31.8.24




$$0 = 12 - (i_1 - i_2) + i_1$$

Apply KVL in mesh-1

$$-6i_1 - 2i_1 - 4(i_1 - i_2) - V_s = 0$$

$$-12i_1 + 4i_2 = V_s \quad (1)$$

find i_0 when $V_s = 12\text{V}$ & 24V .

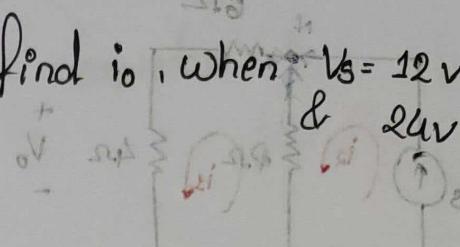

$$\boxed{V_x = 2i_1}$$

$$\boxed{i_0 = i_2}$$

$$0 = 12 - i_1 - (i_1 - i_2) + i_1$$

mesh-2

$$-8i_2 - 4i_2 + 3V_x + 4V_s - 4(i_2 - i_1) = 0$$

$$4i_1 - 16i_2 + 3V_x = -V_s \quad (2)$$

$$10i_1 - 16i_2 = -V_s$$

Add (1) & (2)

$$-2i_1 - 12i_2 = 0$$

$$\boxed{i_1 = -6i_2} \quad (3)$$

Substitute (3) in (1)

Sub

$$76i_2 = V_s$$

$$\text{Put } i_2 = \frac{V_s}{76} \rightarrow i_1 = -\frac{V_s}{12 \cdot 66}$$

$$\checkmark V_s = 12\text{V} \Rightarrow i_2 = 0.157 \text{ Amp}$$


$$\checkmark V_s = 24\text{V} \Rightarrow i_2 = 0.315 \text{ Amp}$$

{ Neglect ai moment Anfangsl. }
• i negative hoch

Q.) For the ckt find 'V_o' when i_s = 15A & i_o = 30A

$$V = IR$$

\Rightarrow

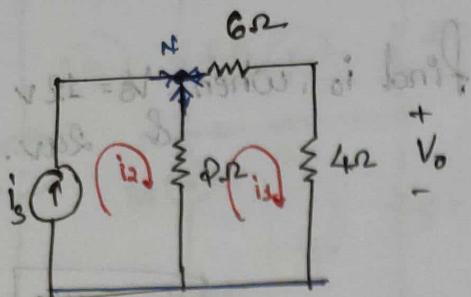


KVL

$$-2(i_1 - i_2) - 6i_1 - 4i_1 = 0$$

S - diagram

$$i_2 = 6i_1$$

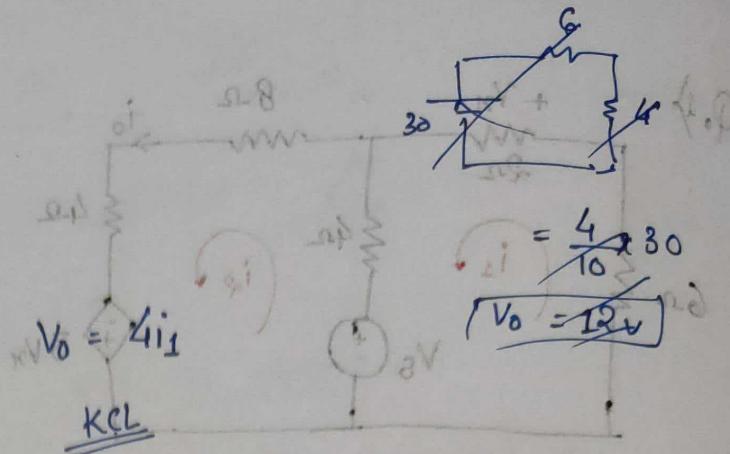

KCL

$$i_s + (i_1 - i_2) - i_1 = 0$$

$$i_s = i_2 \Rightarrow i_1 = \frac{i_s}{6}$$

$$V_o = \frac{4i_s}{6}$$

Superposition Theorem \Rightarrow

It states that the response in linear ckt having more than one independent source can be obtained by adding the responses caused by the sources, each acting one at a time.

When a single source is considered the other independent sources are de energised.

Volt \rightarrow short ckt

Current \rightarrow open ckt


} only for independent sources

{ if dependent source is present
don't remove it. }


13/Aug/24

Circuit Theorem

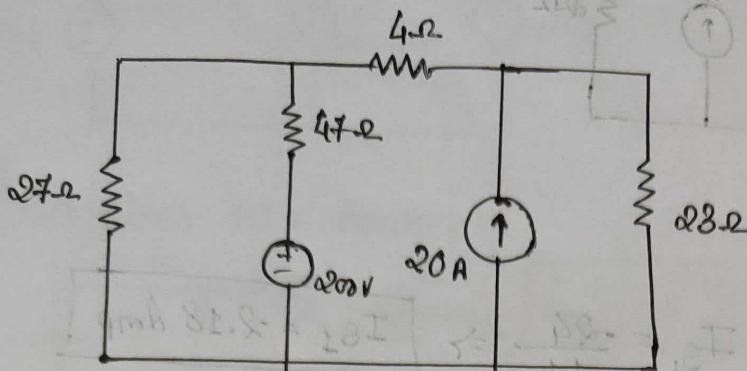Ques.) Compute the current in the 23Ω resistor.



i) Consider 200V Source.

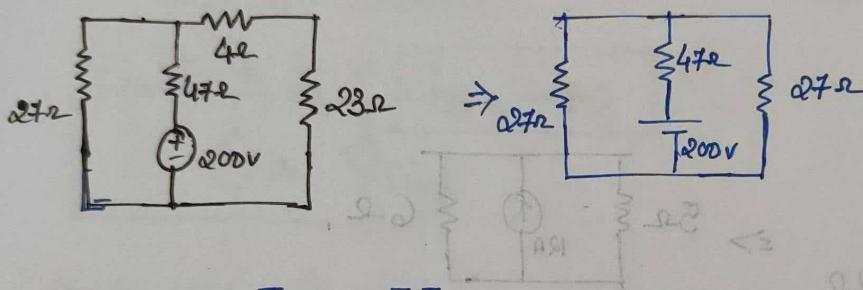


$$R_{eq} = 47 + \frac{27}{2}$$

$$R_{eq} = 60.5\Omega$$

$$I = \frac{200}{60.5} = 3.3 \text{ Amp}$$

ii) Consider 20A Current Source,

$$I_1 = 1.65 \text{ Amp}$$

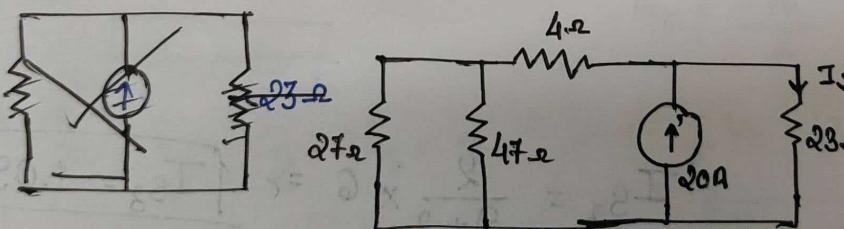

$$R_{eq} = 4 + \frac{27 \times 47}{27 + 47} = 21.15\Omega$$


$$V = IR$$

$$I_2 = \frac{21.15}{21.15 + 23} \times 20 \Rightarrow I_2 = 9.58 \text{ Amp}$$


$$\text{Total Current} = I_1 + I_2$$

$$= 11.23 \text{ Amp}$$

Q. 3


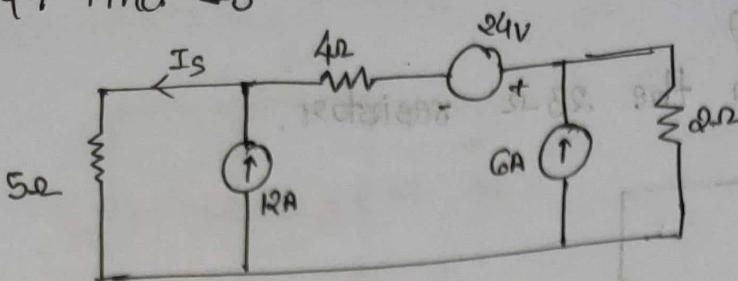
Q.) Find I_S in Ckt.

Consider 24V source,

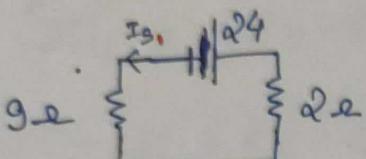


$$I_{S_1} = \frac{-24}{11} \Rightarrow I_{S_1} = -2.18 \text{ Amp}$$

Consider 12A source,

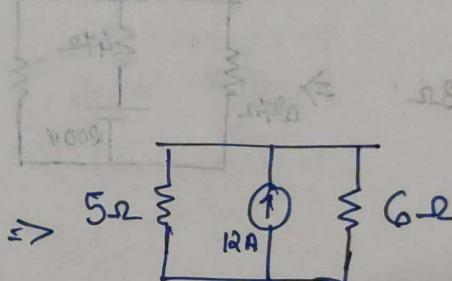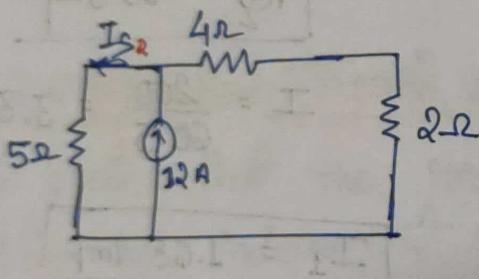

$$I_{S_2} = \frac{6}{5+6} \times 12 \Rightarrow I_{S_2} = 6.54 \text{ A}$$

Consider 6A source,

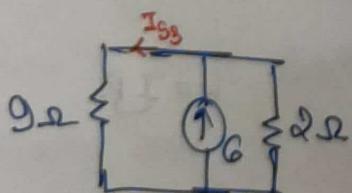


$$I_{S_3} = \frac{2}{9+2} \times 6 \Rightarrow I_{S_3} = 1.09 \text{ A}$$

$$I_{\text{Total}} = I_S = I_{S_1} + I_{S_2} + I_{S_3}$$

$$I_S = 5.45 \text{ Amp}$$



Q.3) Find i_x using Super-Pos. Theorem

13/Aug/24

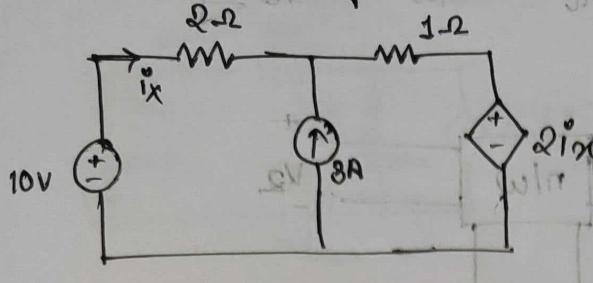


I	sV	V
H1	0	A
H2	2	0
H3	2	0

(i) Consider 10V Source.

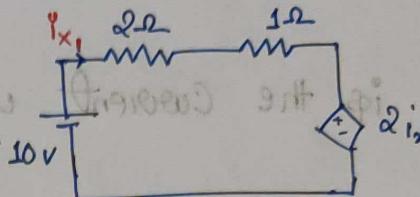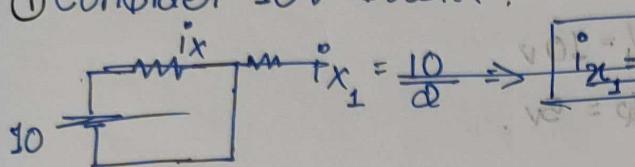

$$KVL: 10 - 2i_{x_1} - i_{x_1} = -2i_{x_1} = 0$$

(ii) Consider 3A Source.

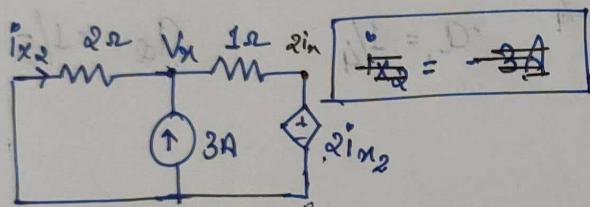

$$i_{x_1} = 2 \text{ A}$$

Apply KCL at V_N .

$$i_{x_2} = -1 \text{ Amp}$$

$$i_{x_2} = -0.6 \text{ A}$$

$$\frac{V_N}{2} + (-3) + \frac{V_N - 2i_{x_2}}{1} = 0$$


$$i_{x_2} = \frac{-V_N}{2}$$

$$V_N = 2V$$

$$-i_{x_2} - 3 + V_N - 2i_{x_2} = 0$$

$$\frac{5}{2} V_N = 3$$

$$V_N = 1.2V$$

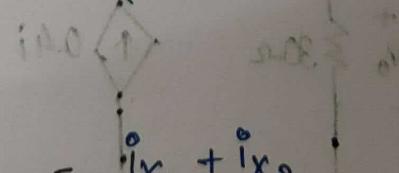


$$\text{Total } i_x = i_{x_1} + i_{x_2}$$

$$i_x = 1.4 \text{ Amp}$$

Q.) Measurement obtained for the n/w is given as.

V_1	V_2	I
4	0	1A
0	5	-1A

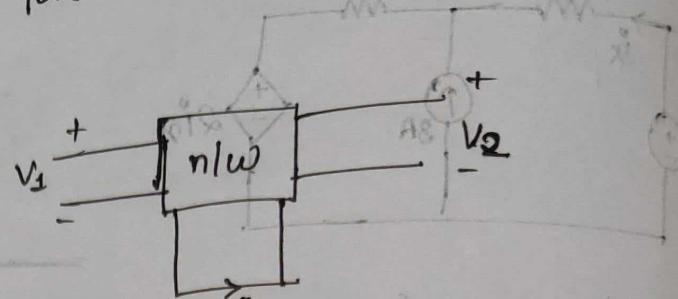

What is the current when $V_1 = 10V$, $V_2 = 5V$.

$$I = f(V_1, V_2)$$

$$\frac{I}{V_1} = \frac{1}{4}, \frac{I}{V_2} = \frac{1}{5}$$

$$I = \frac{V_1}{4} - \frac{V_2}{5}$$


$$= \frac{10}{4} - \frac{5}{5}$$

$$4V_1 = 1 \quad 4a_1 = 1, \quad a_2 = -1/5$$

$$4V_2 = 5 \quad a_1 = 1/4, \quad a_2 = -1/5$$

$$\Rightarrow I = 1.5A$$

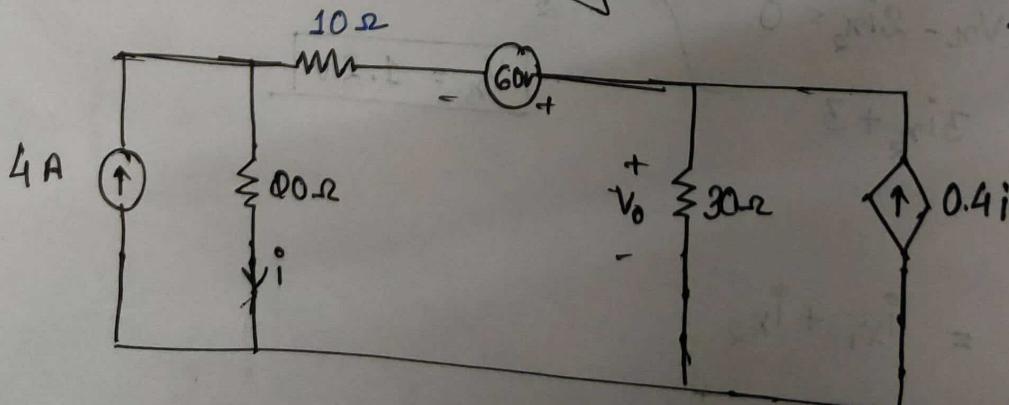
Q.) Find V_o in the ckt Using Superpositn.



$$V_o = 82.56V$$

14 Aug 24

Source Transformation \Rightarrow

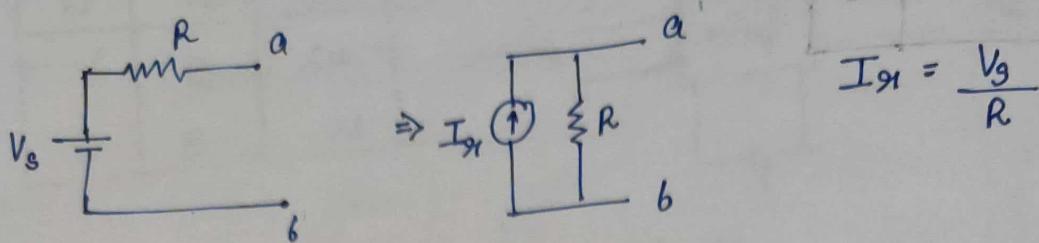

V_s \rightarrow I_s \rightarrow R




$$I_{Ra} = \frac{V_s}{R}$$

- Source trans. is another tool for simplifying the Ckt
This tool works on concept of Equivalence.
- Equivalent whose VI characteristic ~~are~~ is identical with original Ckt.
- Source transformation is process of replacing the voltage source ~~in~~ in series with Resistor 'R' with Current source ~~with~~ in parallel with R.
- Above two ckt's are equivalent, provided they have same Voltage Current relation at terminals a&b.
- If the sources are turned off the equivalent resistance of both the Ckt's is R.
- When terminal a,b are short circuited, the short circuited current going from a to b is $I_{Sc} = \frac{V_s}{R}$



$$\& I_s = I_{Sc}$$

• Thus $\frac{V_s}{R} \approx I_s$ in order for ckt to be equivalent.




14/Aug/24

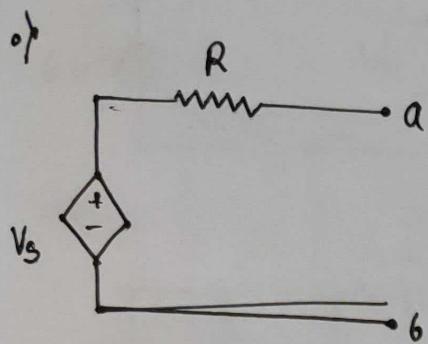

$$V_s = I_s R$$

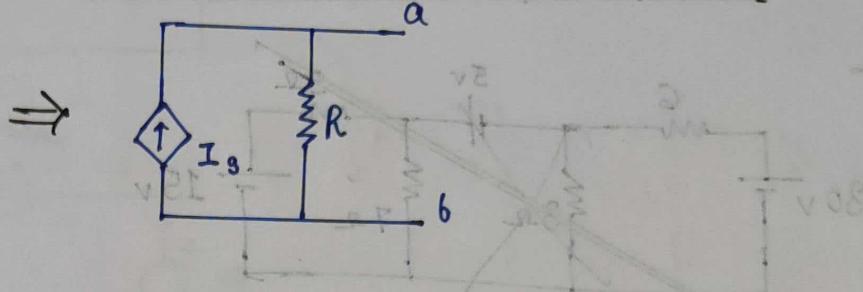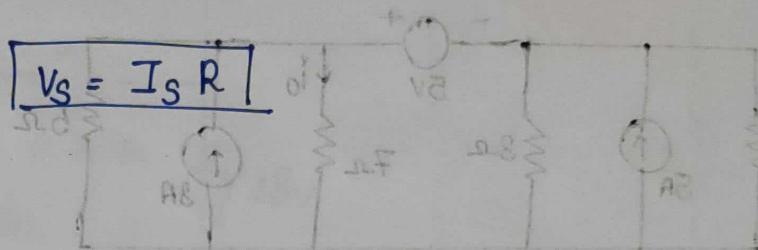

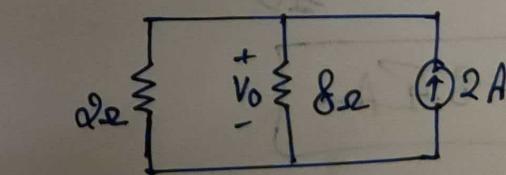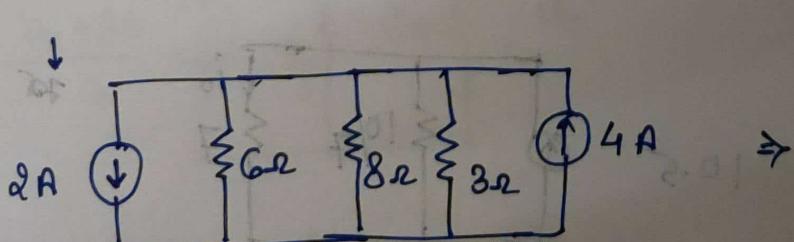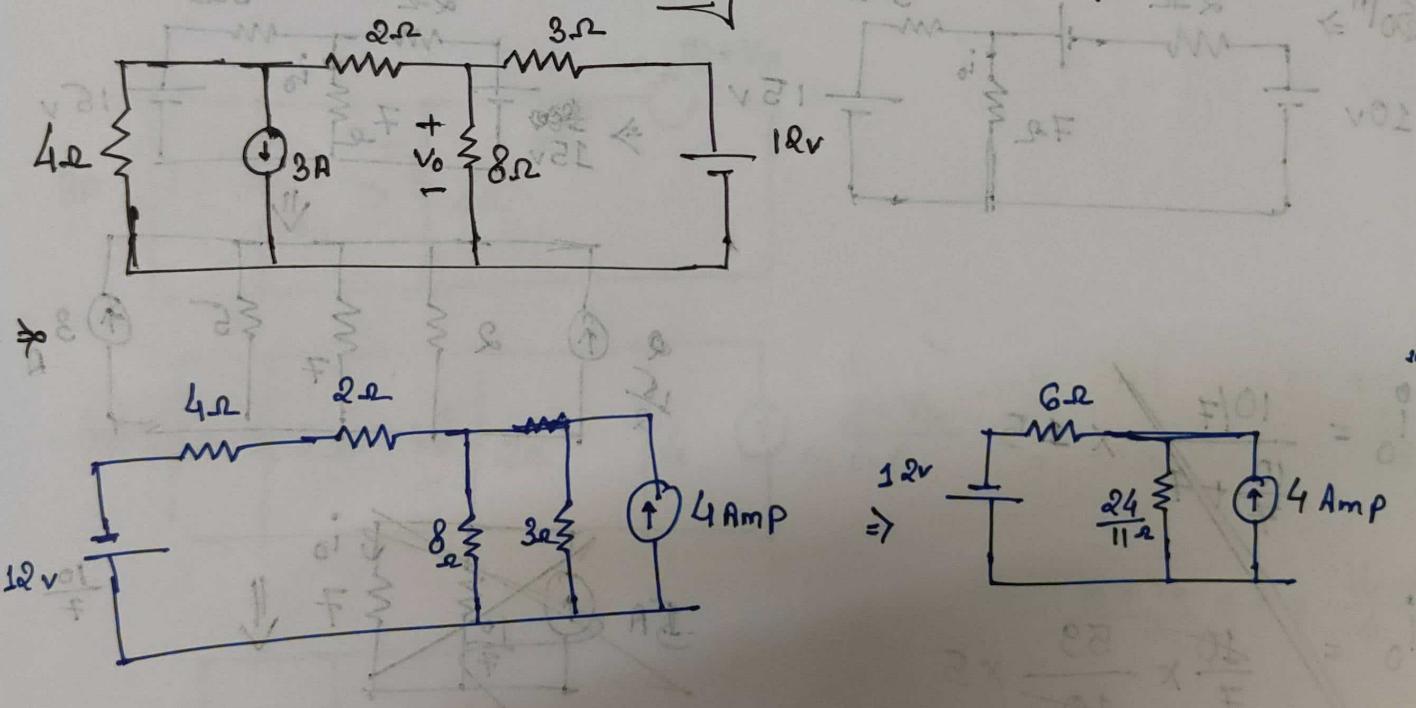Ques.1) Find V_o in the ckt, using source transformation.






$$I_{8\Omega} = \frac{2}{8+2} \times 2 = 0.4 \text{ A}$$

$$V_o = 0.4 \times 8$$

$$\boxed{V_o = 3.2 \text{ V}}$$

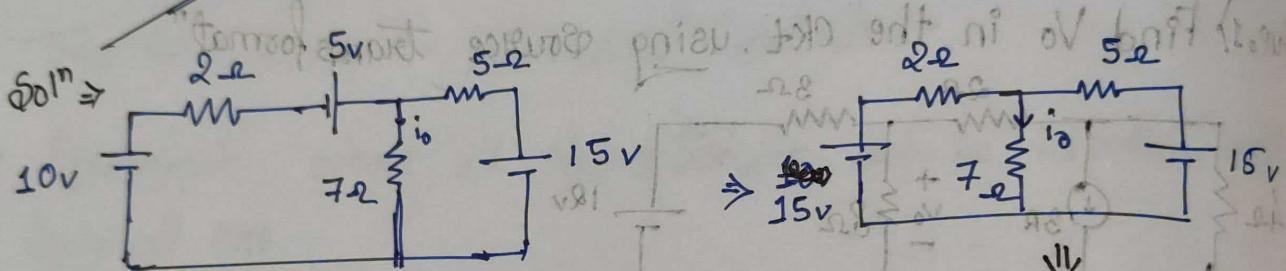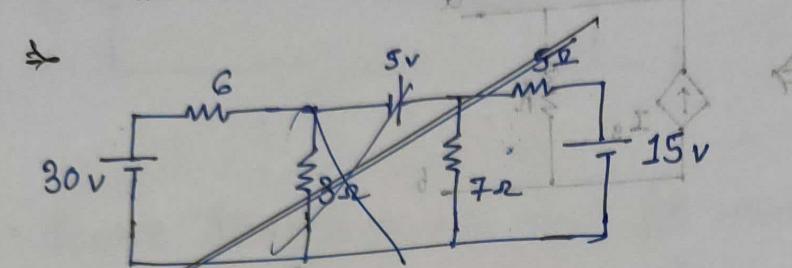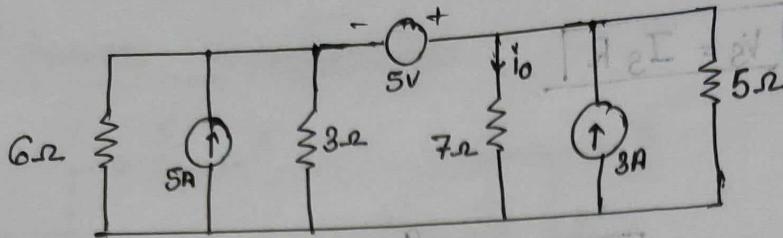Que. 2) Find i_o in the ckt using source Trans Σ meth



$$i_o = \frac{10/7}{\frac{10}{7} + 7} \times 15$$


$$i_o = \frac{10}{7} \times \frac{59}{10} \times 5$$

$$i_o = 8.4 \text{ A}$$

$$i_o =$$

$$i_o = \frac{10/7}{\frac{10}{7} + 7} \times 10.5 = \frac{10}{7} \times \frac{7}{59} \times 10.5$$

$$\boxed{i_o = 1.78 \text{ A}}$$

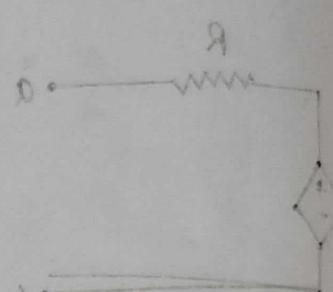

Q.3)

6V

= 7

3A


3A

3





V_x

I


Q.3) Find V_x ?

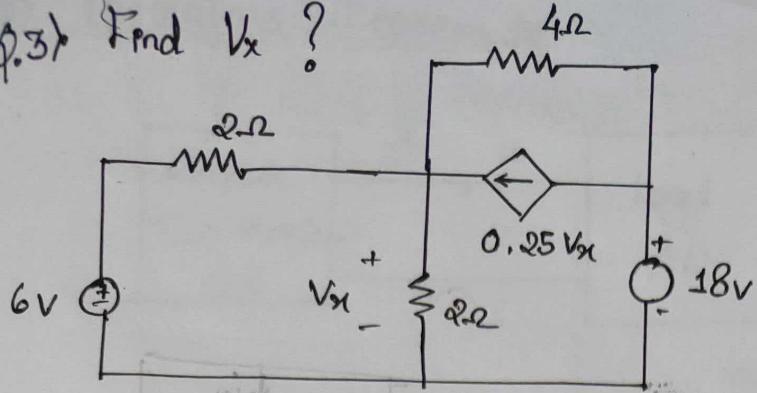

T.E. p.nieu 14/Aug/24

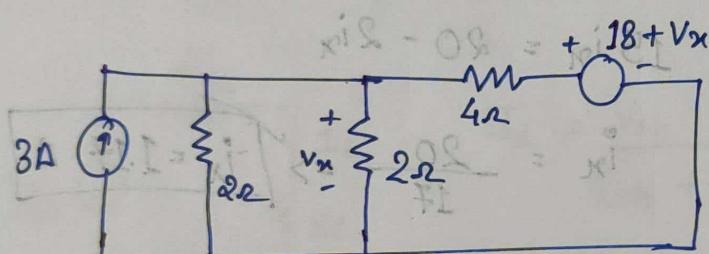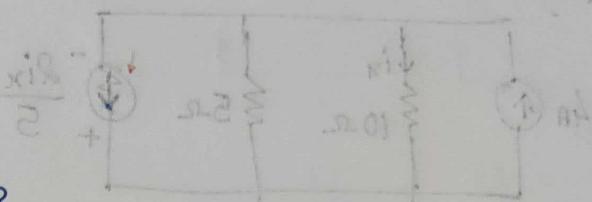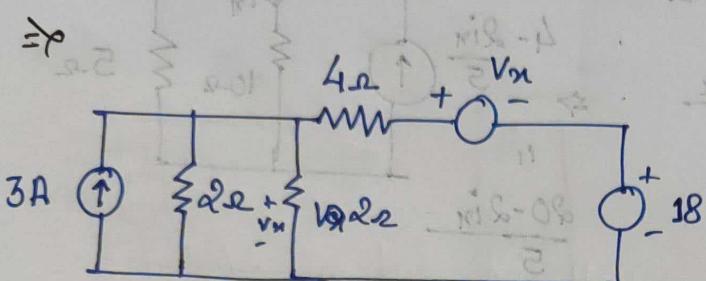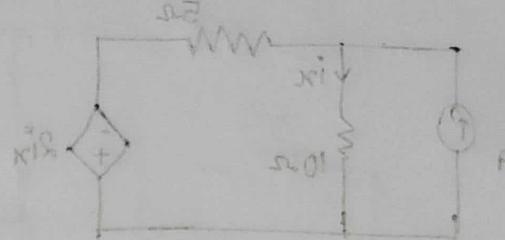

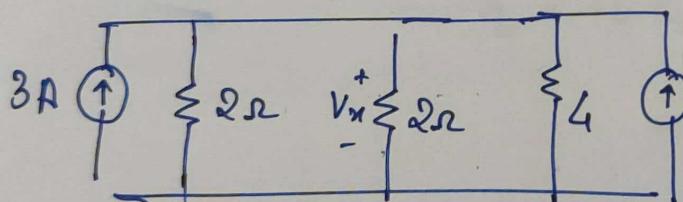
$$\frac{V_x - 0.9}{2} \times \frac{2}{2} = V_x$$



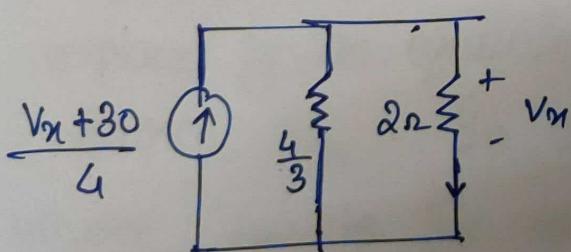3. Brachungs 4. Brachungs
3. 4. Brachungs

12
18

$$\frac{18 + V_x}{4} + 3 = \frac{V_x + 30}{4}$$







$$2 \times I_{2e} = V_x$$

$$I_{2e} = \frac{\frac{1}{1/3}}{\frac{4}{3} + 2} \times \frac{V_x + 30}{4} = \frac{V_x + 30}{10}$$

$$\left(\frac{V_x + 30}{10} \right) = V_x \Rightarrow 4V_x = 30$$

$$V_x = 7.5 \text{ V}$$



Q) Find i_x using S.T.

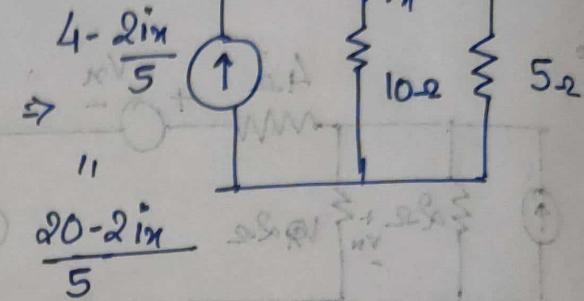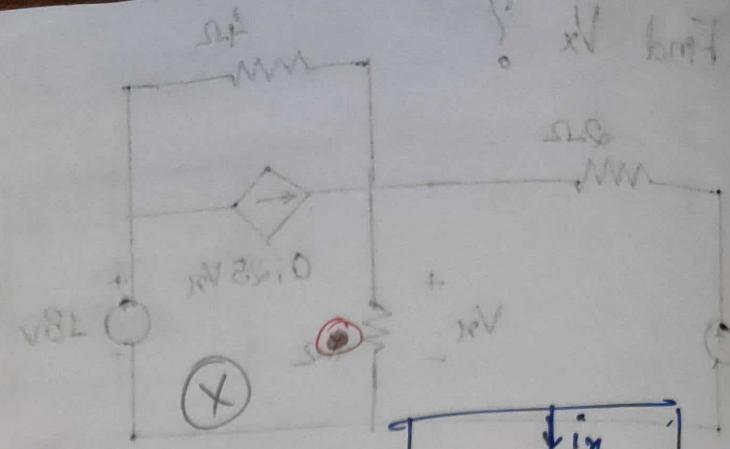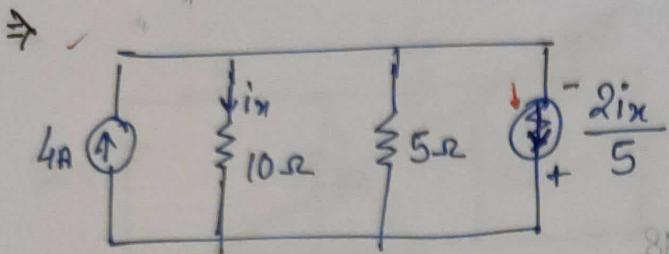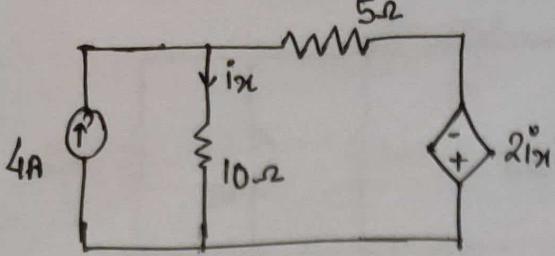




$$i_x = \frac{5}{15} \times \frac{20 - 2i_x}{5} \Rightarrow 15i_x = 20 - 2i_x$$

$$i_x = \frac{20}{17} \Rightarrow i_x = 1.17 \text{ A}$$

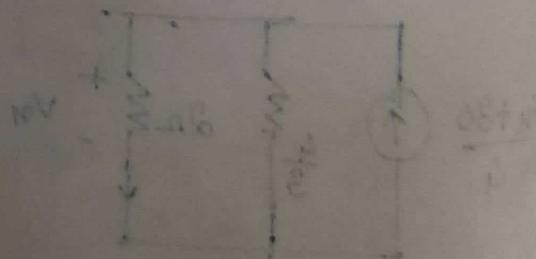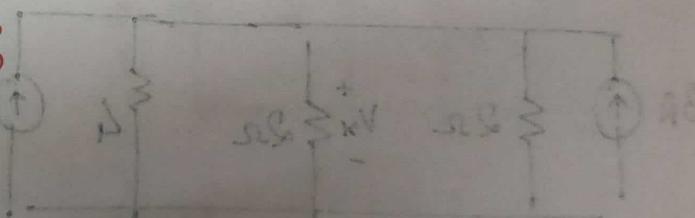Don't club dependent & independent source.



#) Thevinin's Theorem

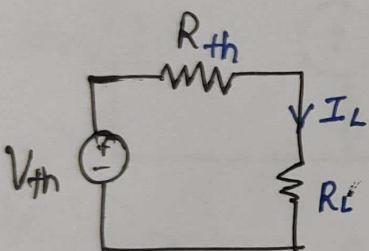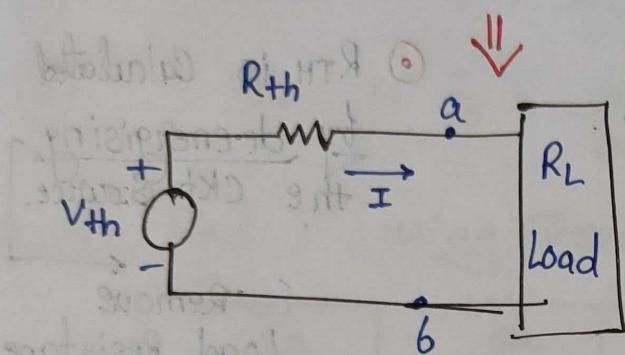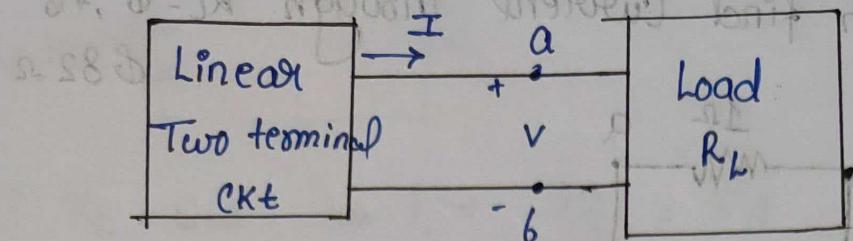


$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$V_L = I_L \cdot R_L = \frac{R_L}{R_L + R_{th}} V_{th}$$


It states that a linear two terminal circuit can be replaced by an equivalent circuit consisting of Voltage Source V_{th} . In series with Resistor ' R_{th} '.

where V_{th} is the open ckt voltage under terminals & R_{th} is the equivalent resistance at the terminals when all independent sources are turned off.

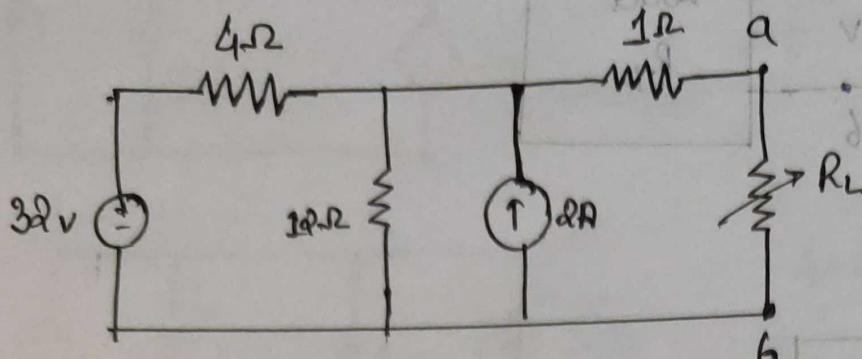Q) Find the thevinin's equivalent ckt, to the left of terminals a,b. Then find current through $R_L = 6 \Omega$.




\Rightarrow

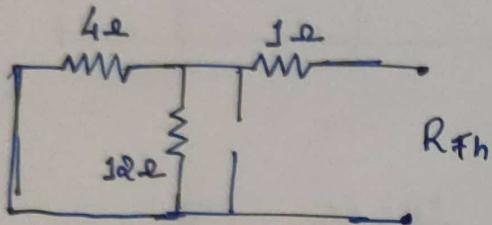

① R_{TH} is calculated by de-energising the ckt source.

Remove Load Resistor
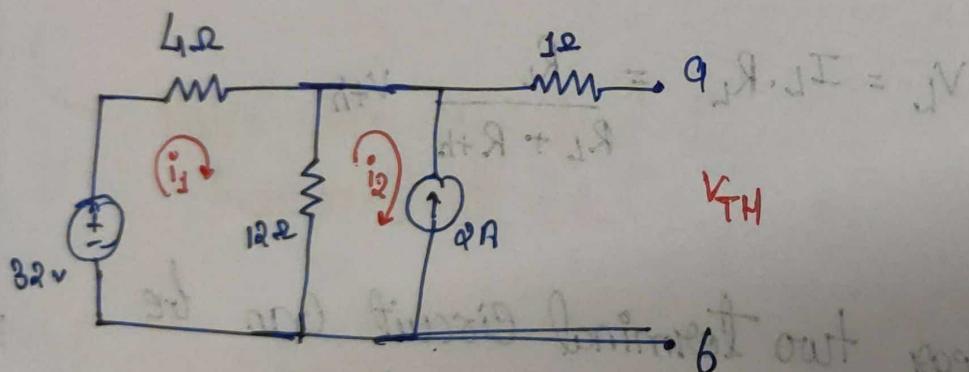
$$R_{TH} = \frac{4 \times 12}{16} + 1 = 4 \Omega$$



KVL in mesh-1

$$32 - 4i_1 - 12(i_1 - i_2) = 0$$

$$-16i_1 + 12i_2 + 32 = 0$$

KVL in mesh-2


$$12(i_2 - i_1) = 0$$

$$i_2 = -2$$

$$i_1 = 0.5 A$$

$$V_{TH} = 12(i_1 - i_2) \Rightarrow V_{TH} = 30 V$$

14/Jan/24

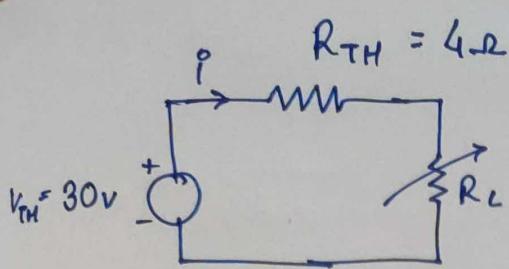


$$\textcircled{i} \quad R_L = 6\Omega \Rightarrow i_1 = \frac{30}{10} = 3A$$

$$\textcircled{ii} \quad = 16\Omega \Rightarrow i_2 = \frac{30}{20} = 1.5A$$




$$\textcircled{iii} \quad = 32\Omega \Rightarrow i_3 = \frac{30}{36} = 0.83A$$

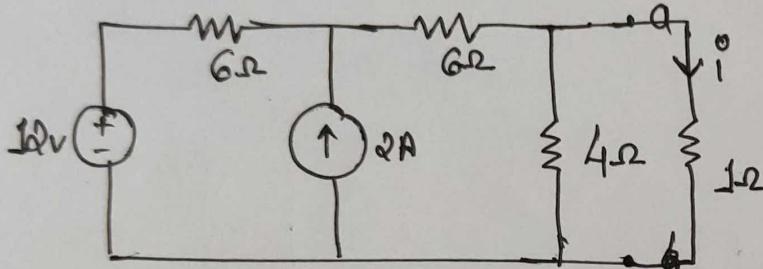Q02) Find 'i' using Thevenin's Theo.


{where we want to calc. Current that Resistor will be load Resistance}



\Rightarrow

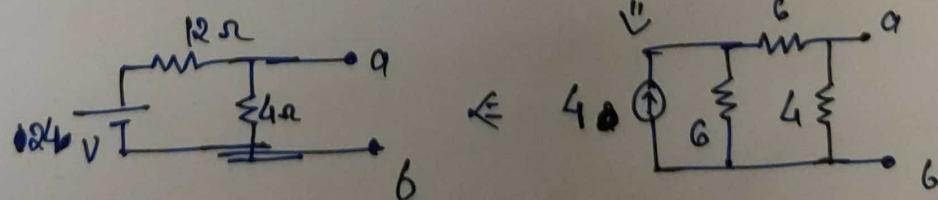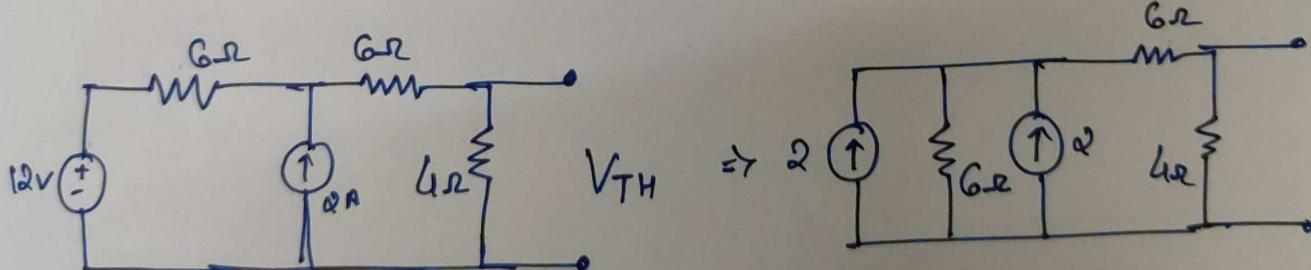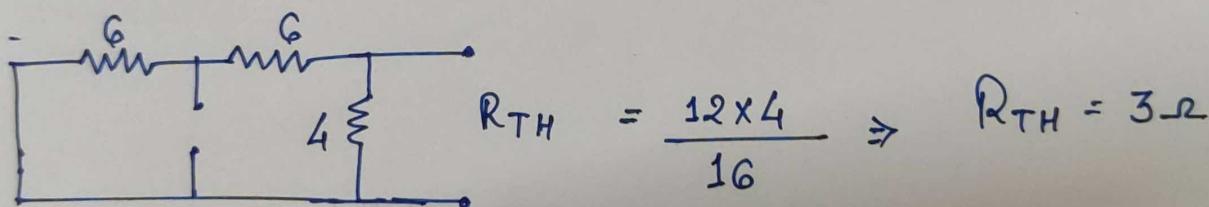


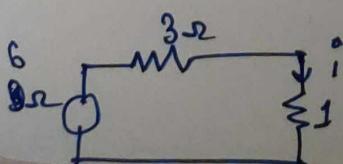
$$V_{TH} = \frac{4}{4+12} \times 12V = 3V$$



$$i = \frac{3V}{4} = 0.75A \quad 1.5A$$

20 Aug 24

Q.) Find Thevenin's equivalent ckt.

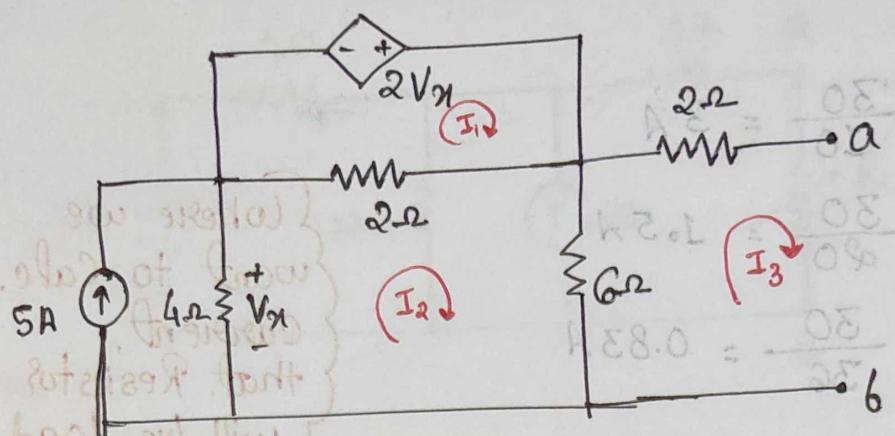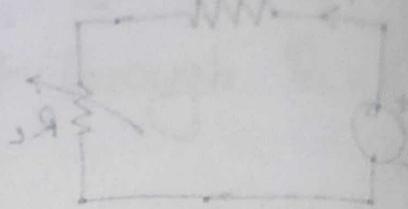


\Rightarrow Circuit contains dependent source & resistance of source is unknown.

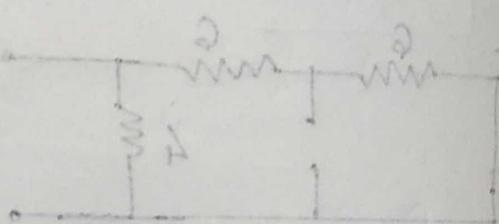ii) To calculate R_{TH} set $V_0 = 1V$ b/w terminals a & b. and assume that Current flowing b/w terminal a & b is i_0 .

Then,

$$R_{TH} = \frac{V_0}{i_0} = \frac{\Delta V_{SE}}{\Delta I} = R_{TH}$$



iii) Alternatively we may apply 1 Amp Current source & find the corresponding voltage V_0 to obtain the

$$R_{TH} = \frac{V_0}{1}$$


Applying KVL in mesh-1

$$2V_x - 2(i_1 - i_2) = 0$$

$$i_1 - i_2 = V_x - 1 \quad (1)$$

$$\rightarrow (-4i_2)$$

$$i_1 + 3i_2 = 0$$

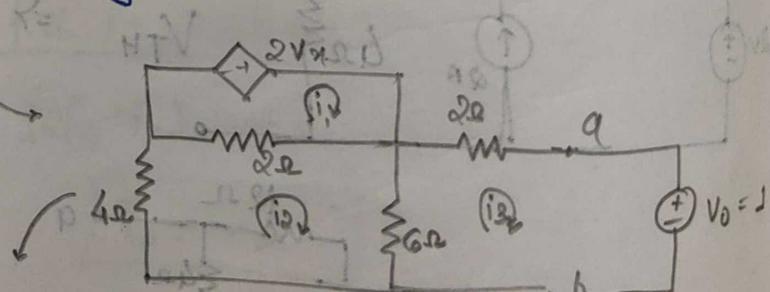

$$-2(i_2 - i_1) - \frac{3}{6}(i_2 - i_3) + V_x = 0$$

$$i_1 - 2i_2 + 3i_3 = 0 \quad (2)$$

mesh-3

$$-6(i_3 - i_2) - 2i_3 - 1 = 0$$

$$6i_2 - 8i_3 = 1 \quad \text{--- (3)}$$

$$i_1 = 0.166 \text{ Amp}$$


$$i_2 = -0.05 \text{ Amp}$$

$$i_3 = -0.166 \text{ Amp}$$

$$R_{TH} = \frac{V_o}{i_o} = \frac{1}{0.166}$$

$$\boxed{R_{TH} = 6 \Omega}$$

Now. for V_{TH} →

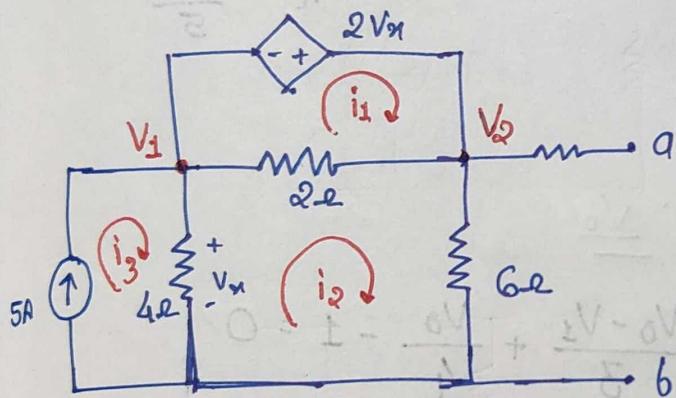

mesh-2

$$-2(i_2 - i_1) - 6(i_2) - 4(i_2 - i_3) = 0$$



$$-i_2 + i_1 - 3i_2 - 2i_2 + 10 = 0$$

$$-i_1 - 4i_2 = -10$$

$$i_1 - 6i_2 = -10$$

$$\therefore V_{TH} = 6i_2 \Rightarrow \boxed{V_{TH} = 20V}$$

Thevenin's eqn ckt →

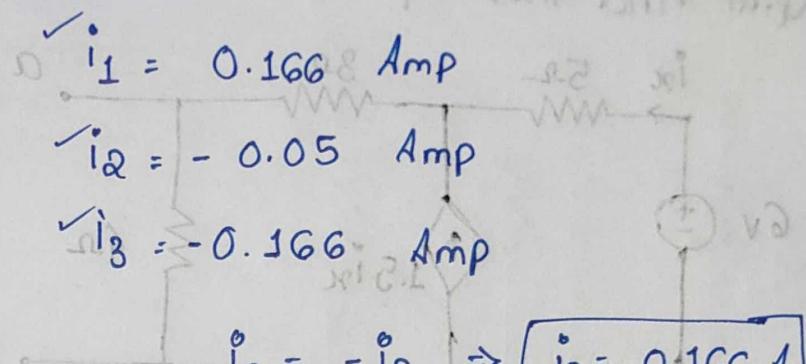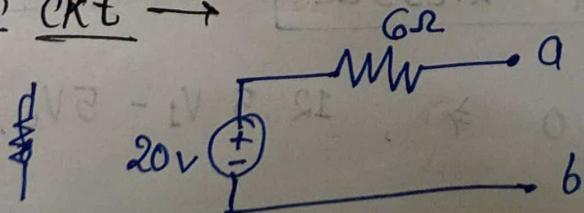

$$i_0 = -i_3 \Rightarrow \boxed{i_0 = 0.166 A}$$

Nodal Analysis at V_x

$$i_3 = 5 \text{ A}$$

mesh-1

$$2Vx - 2(i_1 - i_2) = 0$$

$$i_1 - i_2 = Vx$$


$$i_1 - i_2 = +4(i_2 - 5)$$

$$i_1 + 3i_2 = 20$$

$$5i_2 = -20$$

$$\boxed{i_2 = 10/3 \text{ A}} \\ \boxed{i_1 = 10 \text{ A}}$$

Q.2 Find thev. Eq. Ckt

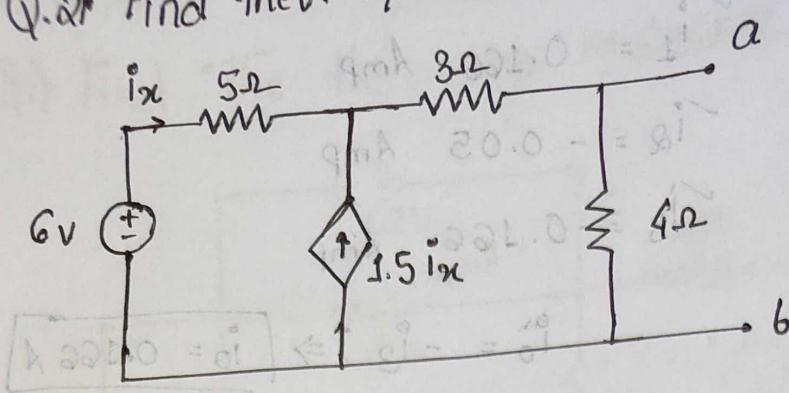


$$0 = 1 - 8i_x - (s_1 - s_1) \quad (1)$$

$$(2) \rightarrow L = 8i_x - s_1 \quad (2)$$

$$\frac{1}{20L} = \frac{1}{s_1} \Rightarrow HTA$$

For R_{TH} →

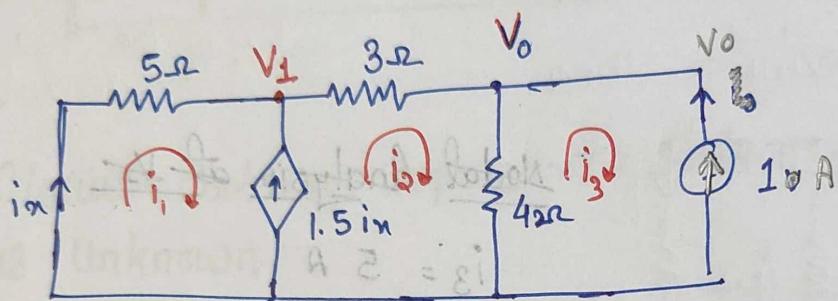

$$[R_{TH} = HTA]$$

$$HTV \text{ soft . work}$$

$$i_x = -\frac{V_1}{5}$$

$V_1 - i_x$ Nodal Analysis at V_1 & V_0 ,

$$-\dot{i}_x - 1.5\dot{i}_x + \frac{V_1 - V_0}{3} = 0$$

$$\frac{V_0 - V_1}{3} + \frac{V_0}{4} - 1 = 0$$

$$2.5(3 - s_1)A = s_1 - 1$$

$$-2\dot{i}_x + \frac{V_1 - V_0}{3} = 0$$

$$+ 2\frac{V_1}{5} + \frac{V_1 - V_0}{3} = 0$$

$$+ 6V_1 + 5V_1 - 5V_0 = 0$$

$$-5V_0 + 11V_1 = 0$$

$$4V_0 - 4V_1 + 3V_0 - 12 = 0$$

$$0 = 7V_0 - 4V_1 - 12 \quad (2)$$

$$0 = 0L + s_1L - s_1E - 1i + s_1$$

$$V_0 = 2.315V$$

$$V_1 = 1.052V$$

$$V_0 = 2.22V$$

$$V_1 = 0.88V$$


$$R_{TH} = \frac{V_0}{1} \Rightarrow R_{TH} = 2.315 \Omega$$

$$\rightarrow \frac{2.5}{5}V_1 + \frac{V_1 - V_0}{3} = 0 \Rightarrow 12.5V_1 - 5V_0 = 0 \quad (1)$$



Now for V_{TH} →

$$R_{TH} = \frac{V_0}{I} \Rightarrow R_{TH} = 2.22\Omega$$

Now for V_{TH} →

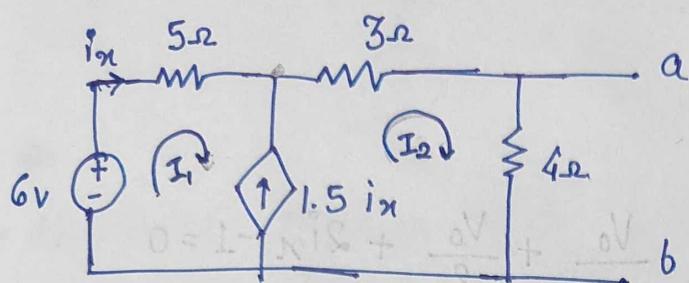


Super mesh analysis

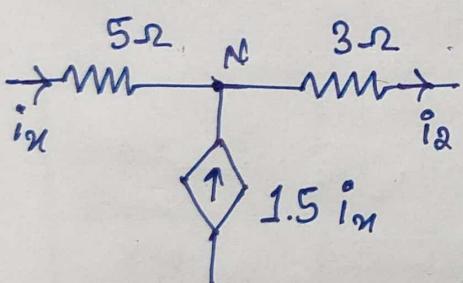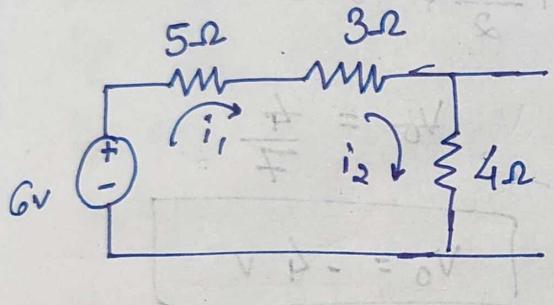

$$V_{TH} = 4 \times 2.5i_x$$

$$\boxed{V_{TH} = 2.66V}$$

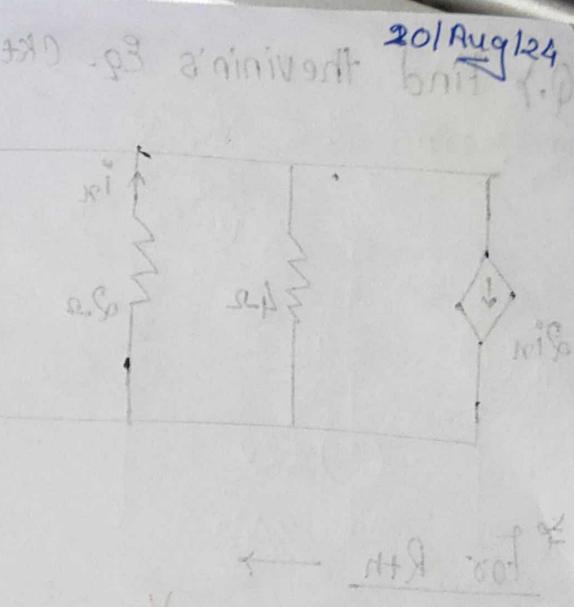

Applying KVL,

$$6 - 5i_1 - 7i_2 = 0$$

$$5i_x + 7i_2 = 6 \quad \text{--- (1)}$$

Applying KCL at N


$$i_x + 1.5i_x = i_2$$

$$i_2 = 2.5i_x \quad \text{--- (2)}$$

from (1) & (2)

$$\boxed{i_x = 0.266 A}$$


Egn ckt

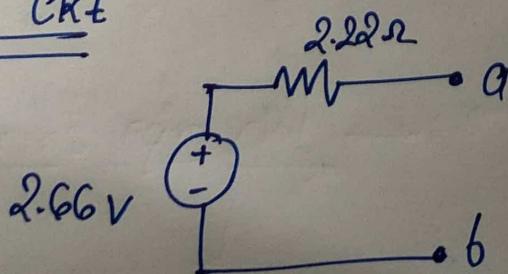

Norton's Theorem :-



21/Aug/24

Ques.

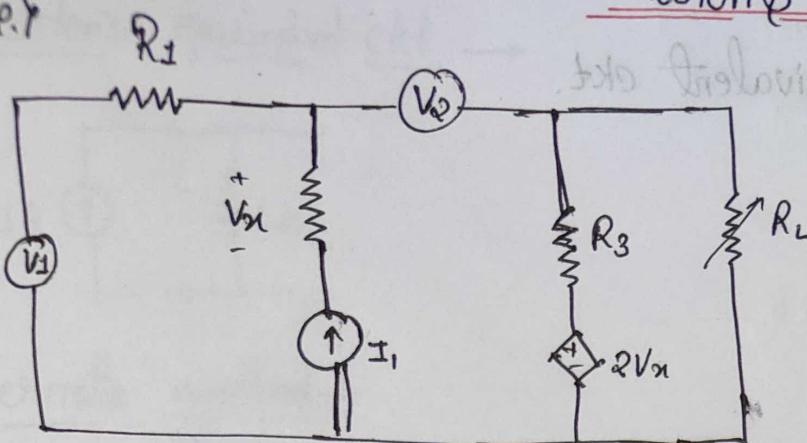

Source transformation
of Thvenin's
ckt.

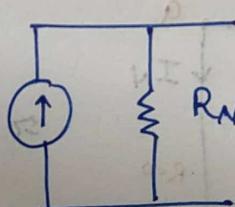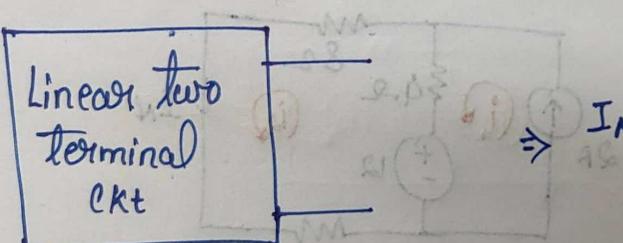- Norton's theorem state that linear two terminal ckt can be replaced by an equivalent ckt consisting of current source I_N in parallel with a resistor R_N , where I_N is the short ckt current to the terminal and R_N is the equivalent resistance at terminal when the independent source are turned off.
- $R_N = R_{TH}$



→ uI p. 260

- Norton's eq. ckt can be obtained by doing source transformation of thvenin's equivalent ckt.



$$qmA \perp = qI$$

$$qmA \perp = q^I = u^I$$


$$0 = q101 - 8 + q11 - q1$$

21 Aug 124

-: norton's equivalent ckt.

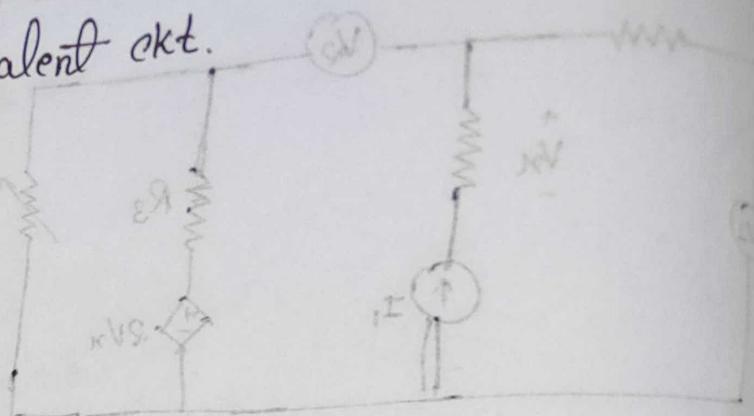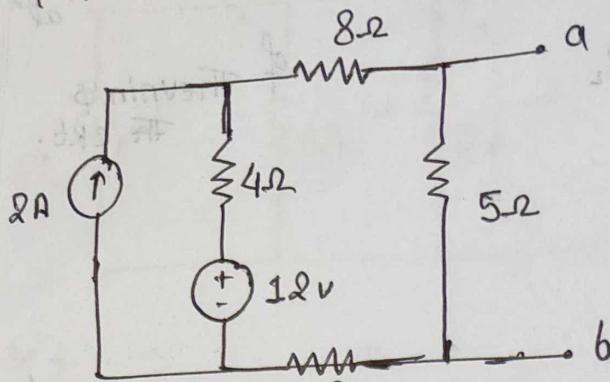


Calc. R_N →

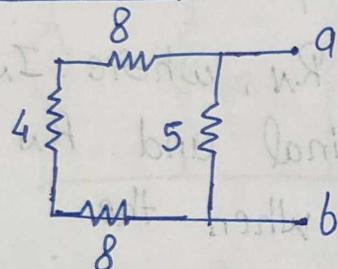


$$R_N = \frac{12 \times 5}{4+5} = \frac{20 \times 5}{25}$$

$$\boxed{R_N = 4\Omega}$$

Calc. of I_N →

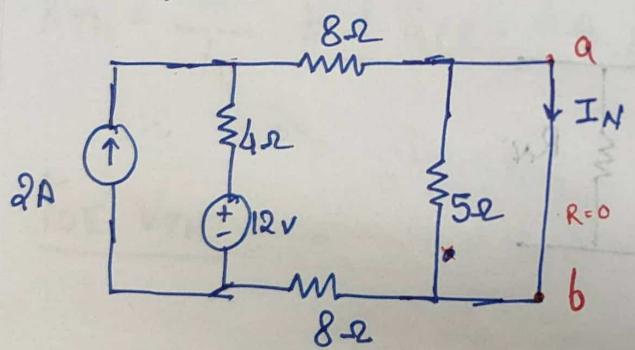

there is no effect of 5Ω Resistor

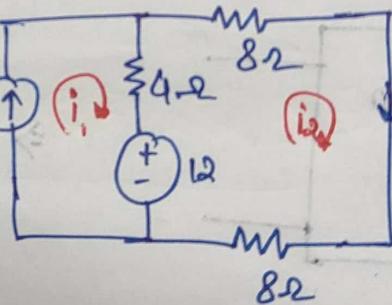

mesh - 1

$$\boxed{i_1 = 2}$$

Applying mesh
Analysis

mesh - 2

$$12 - 4(i_2 - i_1) - 8i_2 - 8i_2 = 0$$



$$12 - 4i_2 + 8 - 16i_2 = 0$$

$$\boxed{i_2 = 1 \text{ Amp}}$$


$$\boxed{i_N = i_2 = 1 \text{ Amp}}$$

Norton's equivalent ckt →

21/Aug/24

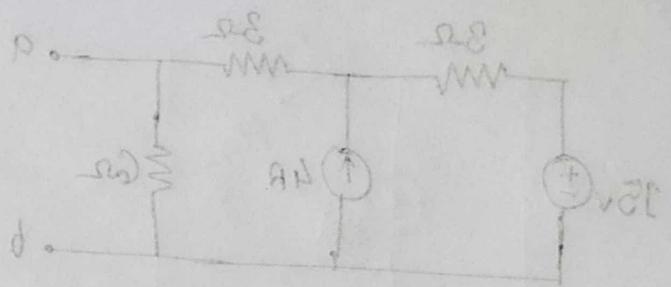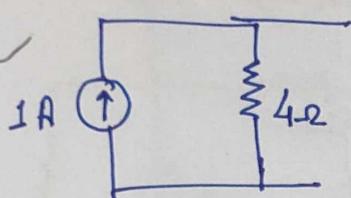

Alternate method →

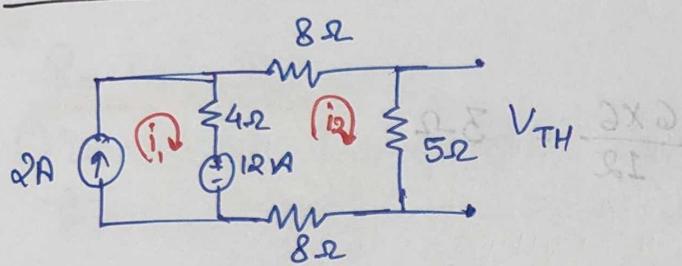

mesh-1

$$i_1 = 2 \text{ A}$$

mesh-2




$$12 - 4(i_2 - i_1) - 21i_2 = 0$$

$$12 - 4i_2 + 8 - 21i_2 = 0$$

$$i_2 = \frac{20}{25}$$

$$\therefore i_2 = 0.8 \text{ A}$$
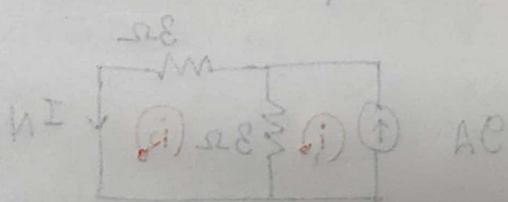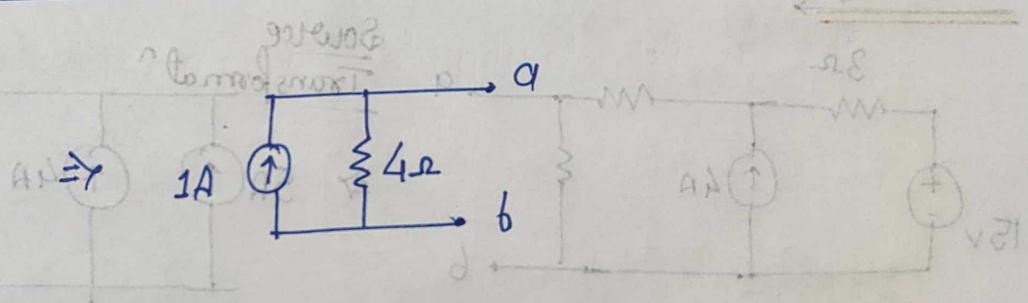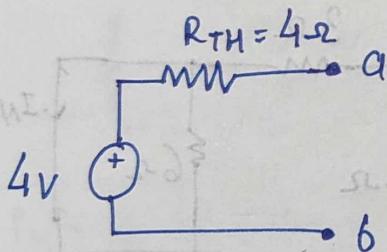
$$V_{TH} = 5 \times 0.8 \Rightarrow V_{TH} = 4 \text{ V}$$



$$0 = s18 - (i_1 - s1)3$$

$$0 = s18 - 3s - s15$$


$$A.B.A = uI$$

$$A.B.A = s1 \quad \therefore \frac{Fg}{s} = s1$$



1-dasm

2-dasm


$$A^2 = s1$$

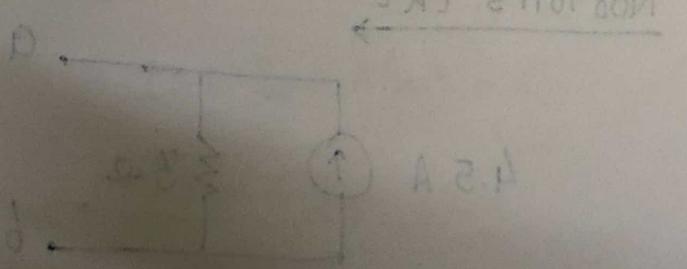

Que. & Find the Norton's Equi. ckt.

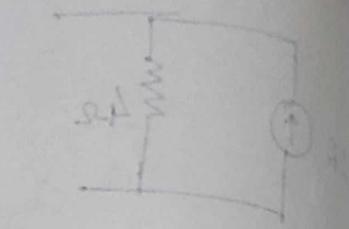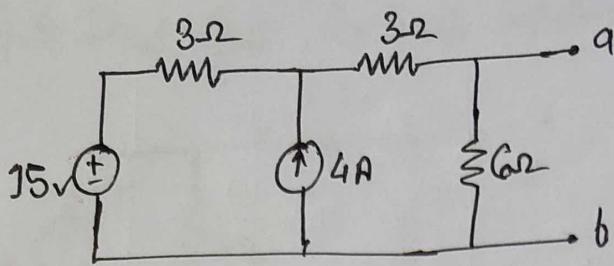


Cal. R_N

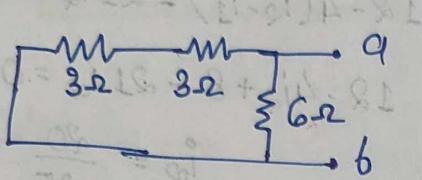


I-darm

$$R_N = \frac{6 \times 6}{12} = 3\Omega$$



bartam

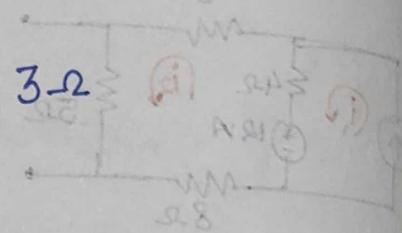

Cal. I_N

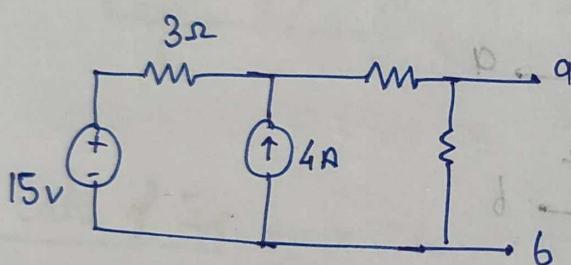

Source Transformation

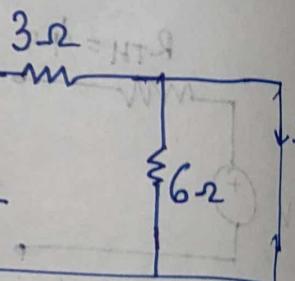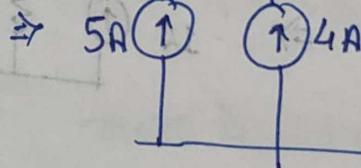


mesh-1

$$i_1 = 9A$$

mesh-2

$$3(i_2 - i_1) - 3i_2 = 0$$


$$3i_2 - 27 - 3i_2 = 0$$

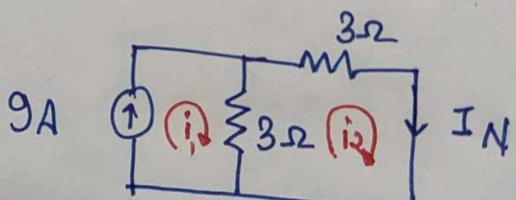



$$i_2 = \frac{27}{6} \Rightarrow i_2 = 4.5A$$

$$I_N = 4.5A$$

Norton's ckt


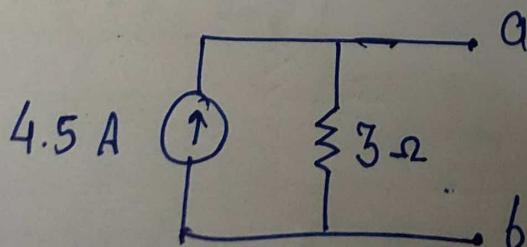


Que. 3) Find Norton's equ. ckt.

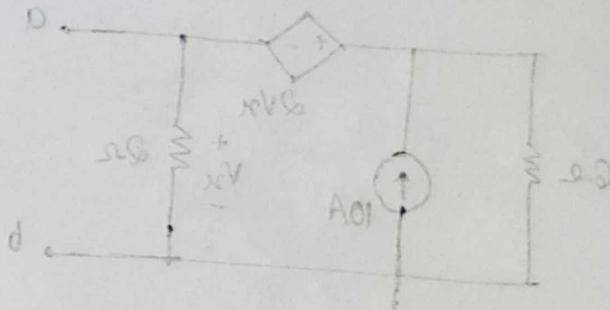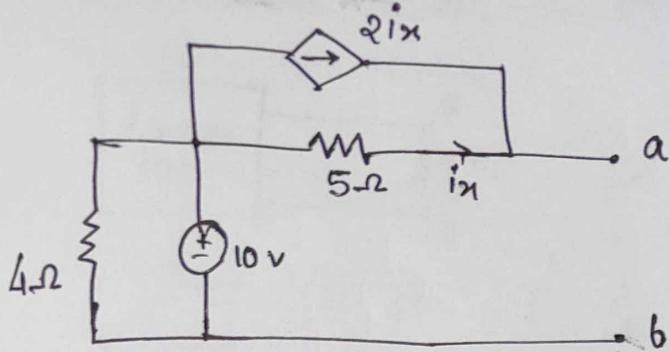

R_N Calculation \Rightarrow

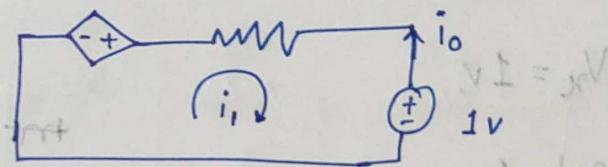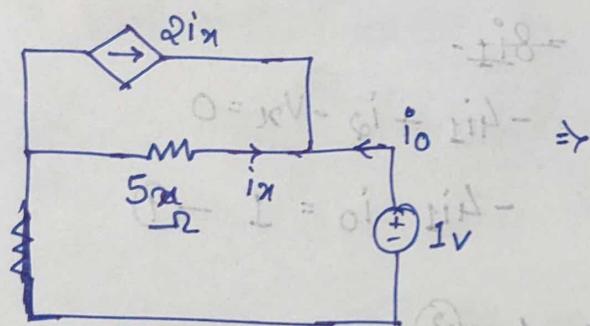① De-energize independent sources & apply 1V source across terminals a & b.



$$i_n = \frac{-1}{5} = -\frac{1}{5} A$$

$$10i_n - 5i_0 - 1 = 0$$

$$i_0 = \frac{10i_n - 1}{5}$$

~~$i_0 = -0.5 A$~~

$$i_0 = \frac{1 - 10i_n}{5}$$



$$i_0 = 3/5 A$$

$$R_N = \frac{V_0}{i_0} = 2 \Omega$$

~~$R_N = 2 \Omega$~~

$$\checkmark R_N = 1.67 \Omega$$

I_N Calculation \Rightarrow

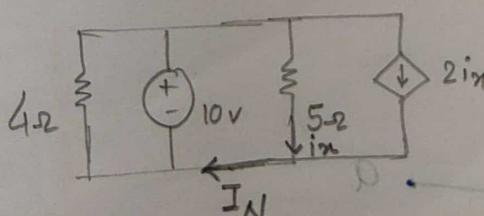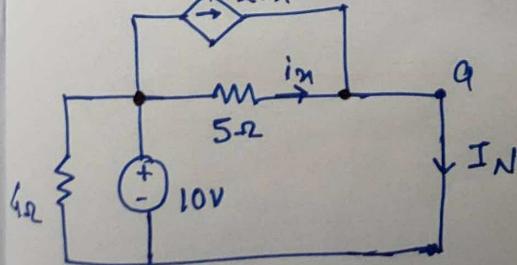

$$i_n = \frac{10}{5} = 2 A$$


$$I_N = i_n + 2i_n = 6 A$$

$$\checkmark I_N = 6 A$$


Que.4) Find Norton's equ. ckt.

$$R_N = 1\Omega$$

$$I_N = 10A$$

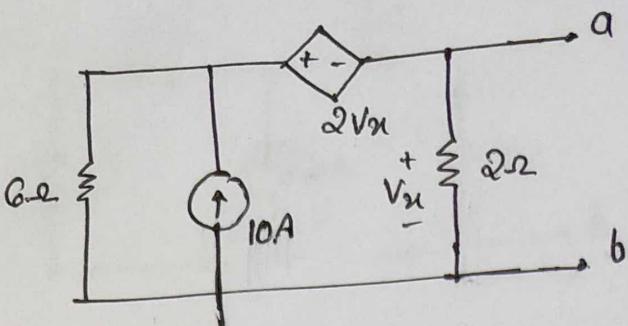

For $R_N \Rightarrow$

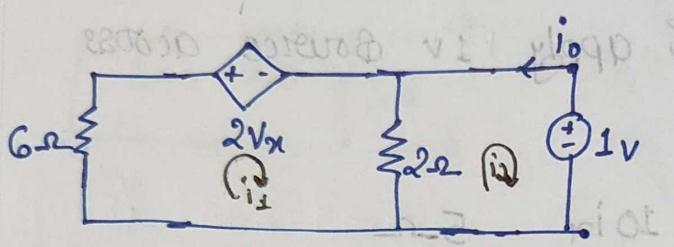

$$V_x = 1V$$

mesh-1

$$-1 - 2(i_2 - i_1) = 0 \Rightarrow -2i_1 - 2i_0 = -1 \quad \text{---(1)}$$

from (1) & (2) $i_0 = 1Amp$

$$i_2 = -i_0$$

$$-3i_1 - 2V_x - 2(i_1 - i_2) = 0$$


$$= 8i_1 -$$

$$-4i_1 + i_2 - V_x = 0$$

$$-4i_1 - i_0 = 1 \quad \text{---(2)}$$


$$R_N = \frac{V_0}{i_0} \Rightarrow R_N = 1\Omega$$

For $I_N \Rightarrow$

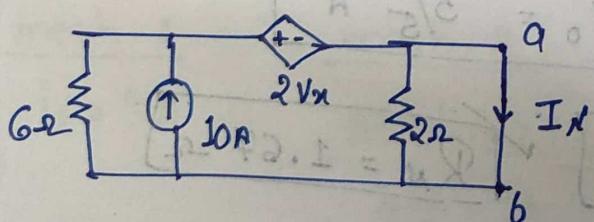



$$\Rightarrow I_N = 10A$$

Norton's Ckt \Rightarrow

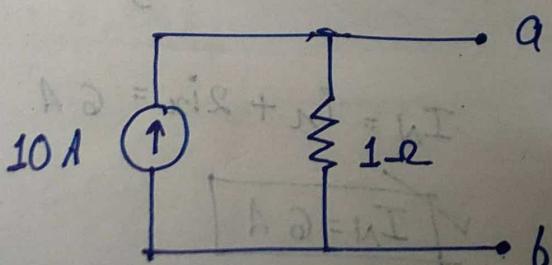


Maximum Power Transfer Theorem

23/Aug/24

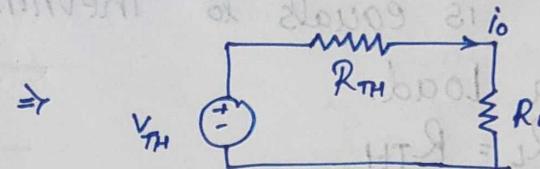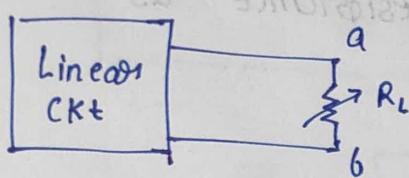

$$P = i_o^2 R_L$$
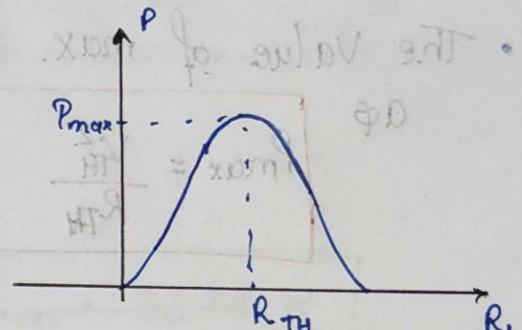
$$= \left[\frac{V_{TH}}{R_{TH} + R_L} \right]^2 R_L \quad \text{--- (1)}$$



To find max 'P' w.r.t. R_L

$$\frac{\partial P}{\partial R_L} = V_{TH}^2 \left[\frac{(R_{TH} + R_L)^2 - 2R_L \cdot (R_{TH} + R_L)}{(R_{TH} + R_L)^4} \right]$$




$$= V_{TH}^2 \left[\frac{(R_{TH} + R_L) - 2R_L}{(R_{TH} + R_L)^3} \right] = 0$$

$$R_{TH} + R_L - 2R_L = 0$$

$$R_L = R_{TH}$$

$$\therefore P_{max} = \left(\frac{V_{TH}}{R_{TH} + R_{TH}} \right)^2 \times R_{TH}$$

$$P_{max} = \frac{V_{TH}^2}{R_{TH}}$$

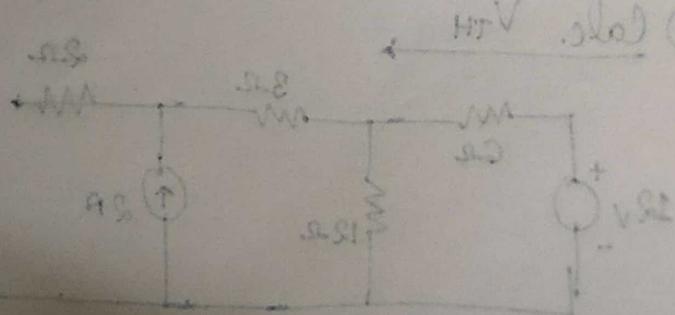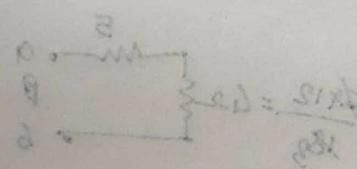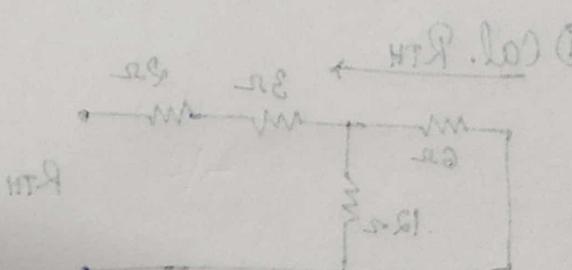

- It state that max. power can be transferred to load when load is equals to Thevenin's Resistance as seen from load.

$$R_L = R_{TH}$$

- The value of max. power when $R_L = R_{TH}$ is calculated


a.s

$$P_{max} = \frac{V_{TH}^2}{R_{TH}}$$


$$\left[\frac{V_{TH}}{R_{TH} + R_L} \right]^2$$

Ques. 1) Find P_{max} .

\Rightarrow

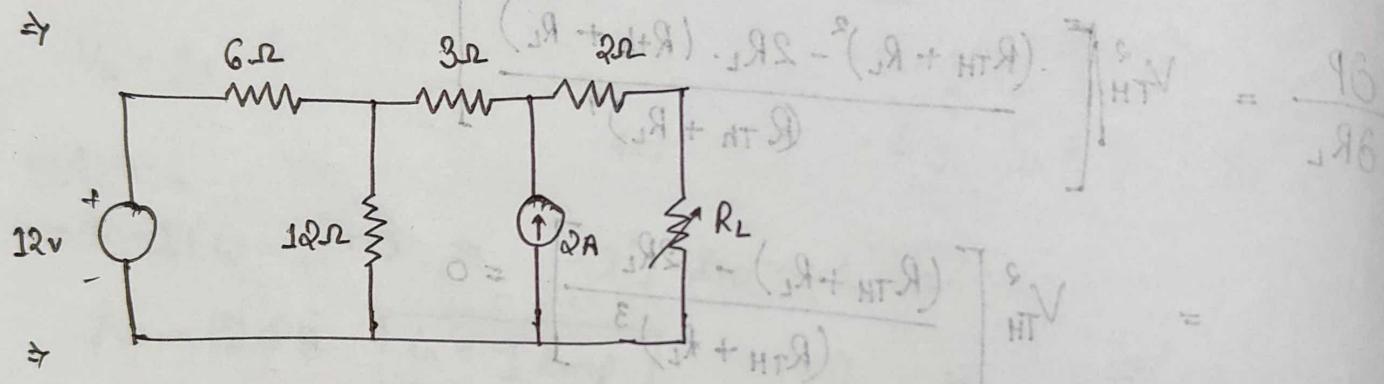


① Calc. R_{TH}

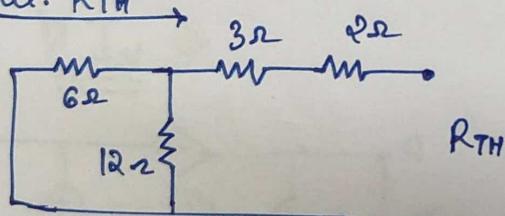



$$R_{TH} = 9\Omega$$


$$R_{TH} = 9\Omega$$

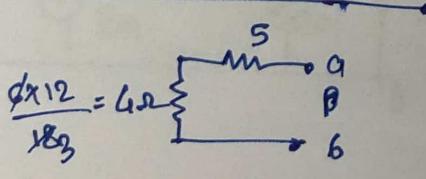

$$V_{TH} = 9V$$

② Calc. V_{TH}

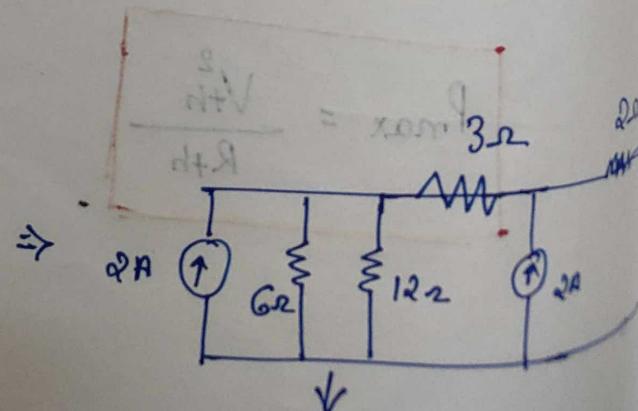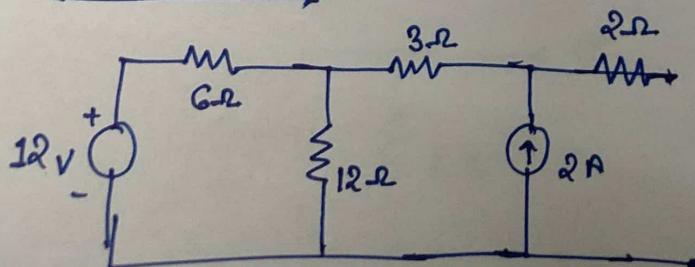

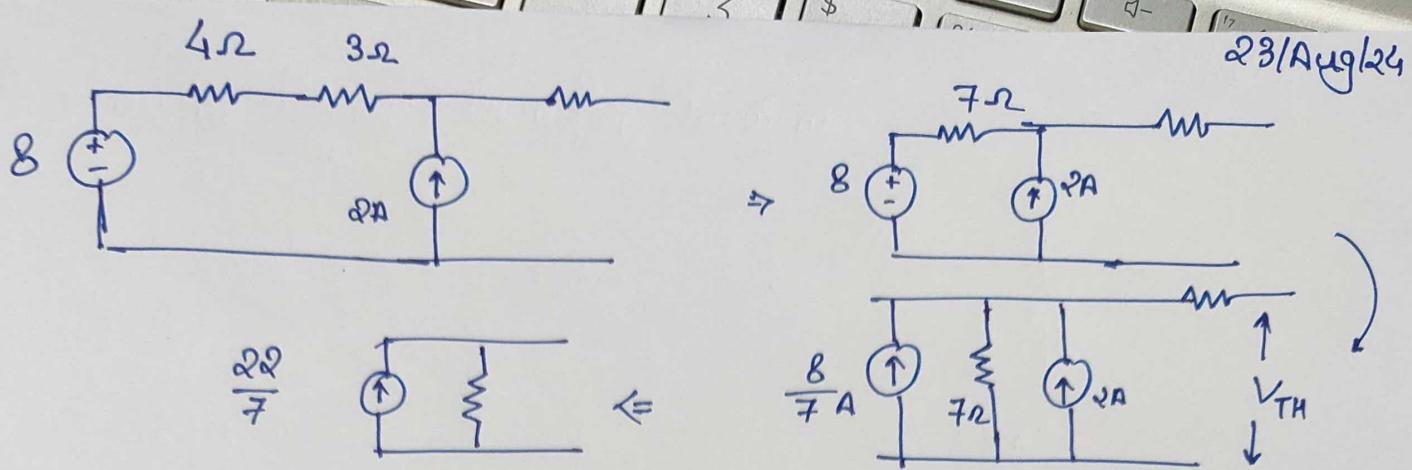

$$V_{TH} = \frac{22}{7} \times 7 \Rightarrow \boxed{V_{TH} = 22 \text{ V}}$$

$$\therefore P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(22)^2}{9 \times 4} \Rightarrow \boxed{P_{max} = 53.78 \text{ W}}$$

$$\checkmark \boxed{P_{max} = 18.44 \text{ W}}$$

27/Aug/24

AC Circuits

• Sinusoid \Rightarrow It represents mathematical function either in sine or cosine form.

$$V(t) = V_m \sin(\omega t)$$



$V_m \rightarrow$ Amplitude

$\omega t \rightarrow$ Argument

$\omega \rightarrow$ Angular freq.


$t \rightarrow$ Second

$$V(t) = V_m \sin(\omega t)$$

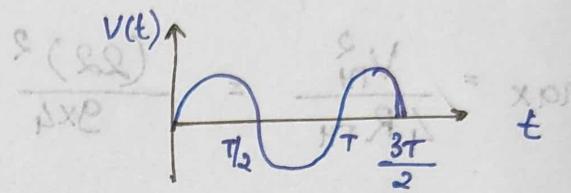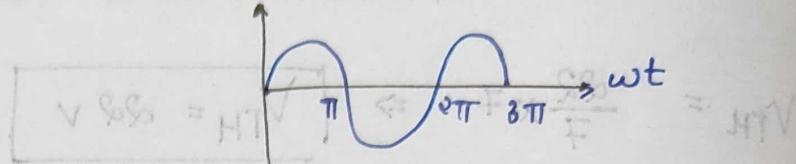


• A functn $f(t)$ is called periodic $\xrightarrow{\text{when}} f(t + T) = f(t)$.
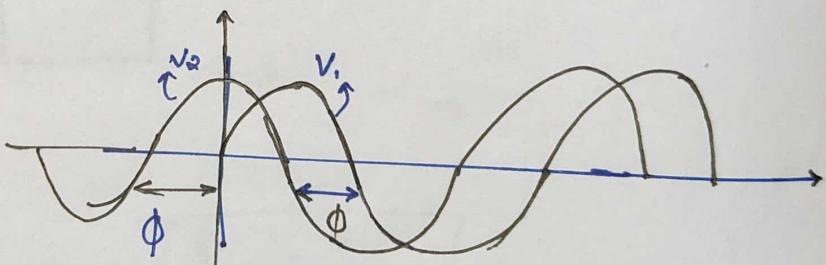
$$\left\{ \begin{array}{l} V_1 = V_m \sin(\omega t) \\ V_2 = V_m \sin(\omega t + \phi) \end{array} \right.$$



$$V_1 = V_m \sin(\omega t)$$


$$V_2 = V_m \cos(\omega t)$$

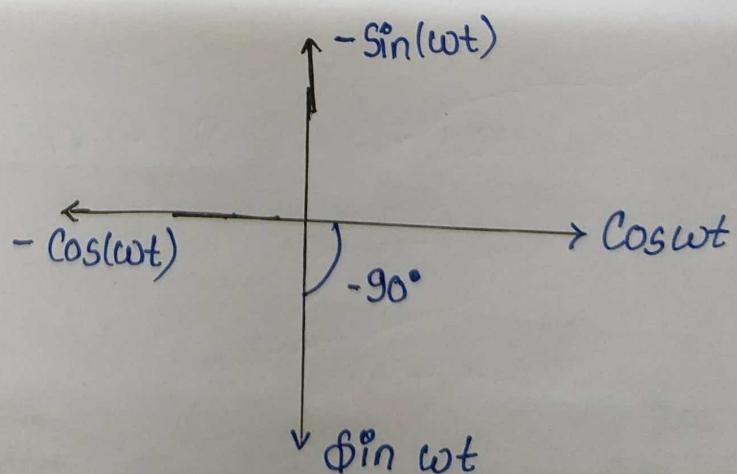

$$\cos(\omega t - 90^\circ) = \sin(\omega t)$$

$$\cos(\omega t + 90^\circ) = -\sin(\omega t)$$
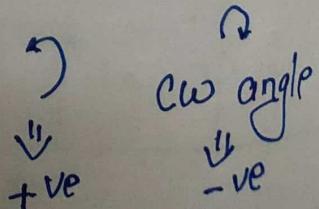
$$\cos(\omega t \pm 180^\circ) = -\cos(\omega t)$$










27/Aug/24

To compare two sinusoids express both of them either in Sine or Cosine with +ve amplitudes.

When two sinusoids are added, the result will be in Sinusoid provided both of them have same frequency.

$$A \cos(\omega t) + B \sin(\omega t) = C \cos(\omega t - \theta)$$

Same frequency

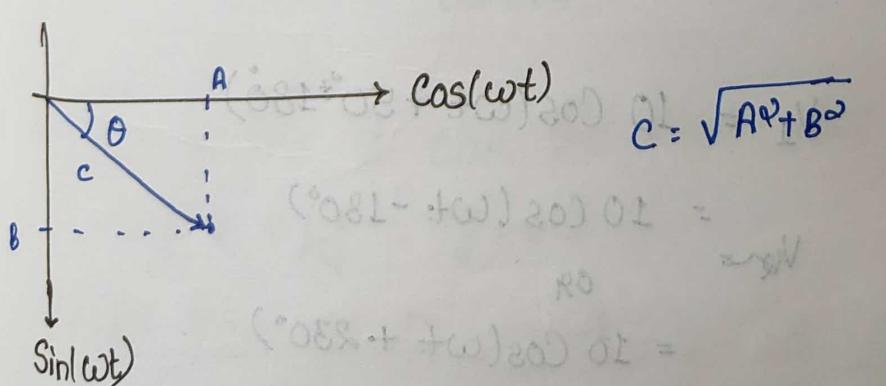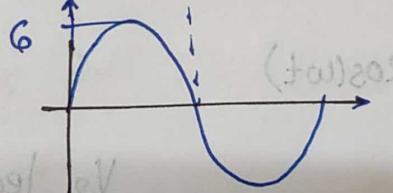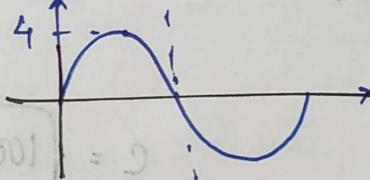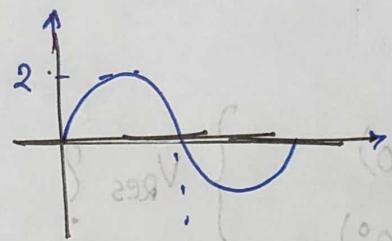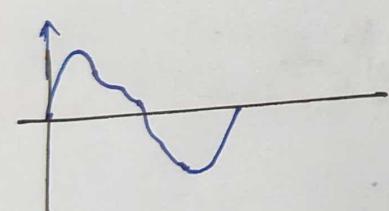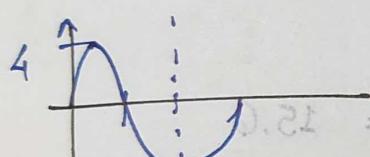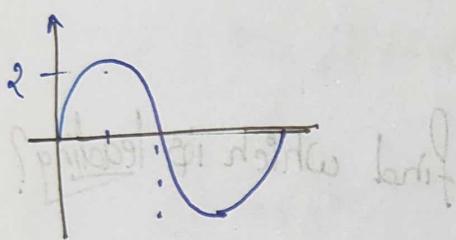

$$(\theta = \tan^{-1}(B/A)) \text{ rad} = \frac{\pi}{4}$$

$$(\theta = 45^\circ) \text{ rad} = \frac{\pi}{4}$$


$$(\theta = 45^\circ) \text{ rad} = \frac{\pi}{4}$$

$$(\theta = 45^\circ) \text{ rad} = \frac{\pi}{4}$$

$$\theta = \phi$$

Eg) $3 \cos \omega t - 4 \sin \omega t = 5 C \cos(\omega t - \theta)$

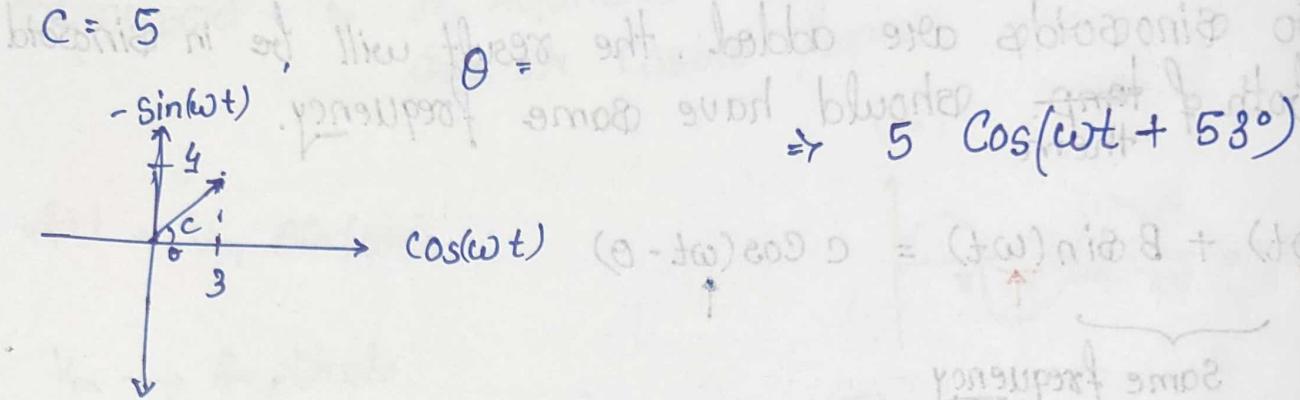A) B) $\theta = \tan^{-1}\left(\frac{B}{A}\right) = \tan^{-1}\left(-\frac{4}{3}\right)$




Q) $V_1 = -10 \cos(\omega t + 50^\circ)$ } $V_{\text{Res}} ?$ find which is leading?

$V_2 = 12 \sin(\omega t - 10^\circ)$

\Rightarrow

$$C = \sqrt{100 + 144} = 15.6$$

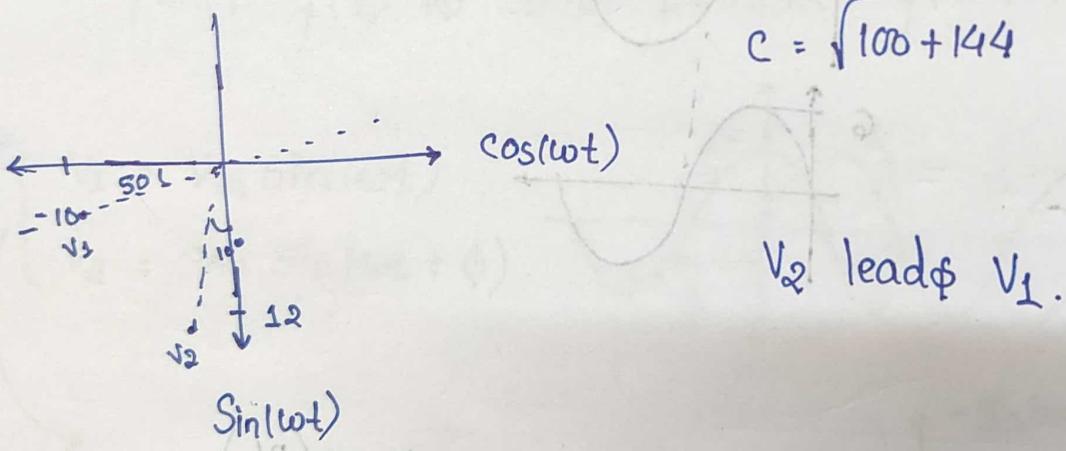

$V_2 = 12 \cos(\omega t - 10 - 90^\circ)$

$V_2 = 12 \cos(\omega t - 100^\circ)$

$\phi = 30^\circ$

$V_1 = 10 \cos(\omega t + 50^\circ \pm 180^\circ)$

$V_1 = 10 \cos(\omega t - 130^\circ)$

or

$= 10 \cos(\omega t + 230^\circ)$

28/Aug/24

$$V_1 = -10 \cos(\omega t + 50^\circ) = 10 \sin(\omega t + 50^\circ - 90^\circ) = 10 \sin(\omega t - 40^\circ)$$


$$V_2 = 12 \sin(\omega t - 10^\circ)$$

$$(V_1 + V_2) R =$$

Q.1) Find phase diff ϕ/ω

$$i_1 = -4 \sin(377t + 25^\circ)$$

$$i_2 = 5 \cos(377t - 40^\circ)$$

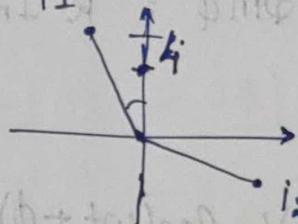

$$\begin{aligned} i_1 &= 4 \cos(377t + 25^\circ + 90^\circ) \\ &= 4 \cos(377t + 115^\circ) \end{aligned}$$

i_1 leads i_2 by 155°


$$\phi = 115^\circ + 40^\circ$$

$$\boxed{\phi = 155^\circ}$$

#) Phasor Analysis \Rightarrow relating to current $\phi_i \leftarrow V$

$$e^{j\phi} = \cos\phi + j \sin\phi$$

Euler's

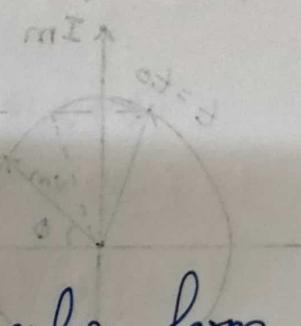


A Complex no. z can be expressed in rectangular form.

$$Z = x + jy, \quad j = \sqrt{-1}$$

$$\text{polar form } \Rightarrow Z = r \angle \phi$$
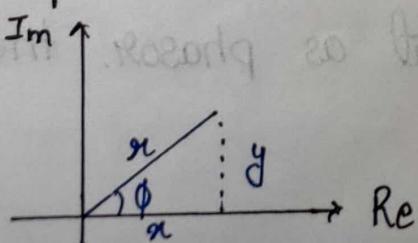
$$\text{Exponential form } \Rightarrow Z = r e^{j\phi}$$



$$\rightarrow Z = x + iy = r \angle \phi$$

$$= r(\cos\phi + j\sin\phi)$$

which shows that, $\cos\phi$ & $\sin\phi$ as real & Imaginary part of eqn

$$\therefore \cos\phi = \operatorname{Re}[e^{j\phi}]$$

$$\sin\phi = \operatorname{Im}[e^{j\phi}]$$

\rightarrow Que.

$$V(t) = V_m \cos(\omega t + \phi) = \operatorname{Re}[V_m e^{j(\omega t + \phi)}]$$


$$= \operatorname{Re}[V_m e^{j\omega t} e^{j\phi}]$$

$$= \operatorname{Re}[V e^{j\omega t}] \quad \text{--- ①}$$

where,

$$V = V_m e^{j\phi} = V_m \angle \phi \quad \text{--- ②}$$

$V \rightarrow$ is known as phasor represent of sinusoidal $v(t)$.

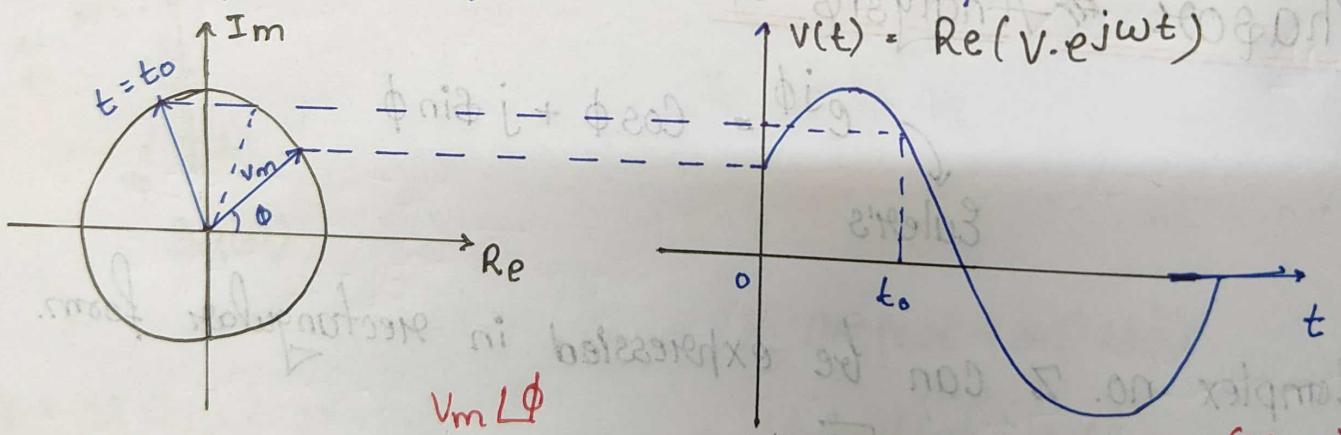

(Fig. 6)

- If we project every point on $V e^{j\omega t}$ on real axis it will appear like a sinusoid (fig 6)
- Whenever a sinusoid is represented as phasor, the term $e^{j\omega t}$ implicitly present.

from a given phasor V to obtain a corresponding sinusoid multiply the phasor V by the time factor $e^{j\omega t}$ & take the real part.

To get the phasor corresponding to sinusoid, we first express sinusoid in Cosine form. so that sinusoid can be written as real part of Complex No.

Phasor Domain \Rightarrow

Time Domain Representation

$$V_m \cos(\omega t + \phi)$$

$$V_m \sin(\omega t + \phi) \\ \hookrightarrow \cos(\omega t + \phi - 90^\circ)$$

Phasor Domain

$$V_m \angle \phi$$

$$V_m \angle \phi - 90^\circ$$

$$\overset{i}{\rightarrow} \text{mm} \text{---}$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I = I_m \cos(\phi) \omega t + \phi$$

$$I = I_m \angle \phi$$

$$\frac{di}{dt} = -I_m \sin(\omega t + \phi) \cdot \omega$$

$$= -I_m \omega \cos(\omega t + \phi + 90^\circ)$$

$$= \operatorname{Re} [I_m \cdot \omega \cdot e^{j(\omega t + \phi + 90^\circ)}]$$

$$= \operatorname{Re} [I_m \cdot \omega \cdot e^{j\omega t} \cdot e^{j\phi} \cdot e^{j90^\circ}] \xrightarrow{\text{Cos}(90^\circ) + j \sin(90^\circ)}$$

$$= \operatorname{Re} [I \cdot \omega \cdot e^{j\omega t} \cdot \cancel{e^{j\phi}}] = \operatorname{Re} [I \cdot j\omega \cdot e^{j\omega t}] \xrightarrow{\text{Cos}(\omega t) + j \sin(\omega t)}$$

$$\frac{di(t)}{dt} = I \cdot j\omega$$

$$I \cdot (j\omega \cos(\omega t) - \omega \sin(\omega t)) \\ I \omega ($$

$$\text{80/Aug/24}$$

Time Domain Phasor Domain

$$\frac{dV(t)}{dt} \rightarrow j\omega \cdot V$$

$$\int V(t) dt \rightarrow \frac{V}{j\omega}$$

Que. No. $[40 \angle 50^\circ + 20 \angle -30^\circ]^{1/2}$

★ ★

$$\sqrt{41}\angle\phi$$

↓

$$\sqrt{41} \angle \phi/2$$

~~$$(38.59 - 10.49j) + (3.08 + 19.76j)^{1/2}$$~~

~~$$= (41.67 + 9.27j)^{1/2}$$~~

~~$$= (42.68 \angle 0.21^\circ)^{1/2}$$~~

~~$$= 6.53 \angle 0.21^\circ$$~~

~~$$= 6.9 \angle 12^\circ \quad \underline{\text{Ans}} \quad \checkmark$$~~

Soln $\Rightarrow (47.72 \angle 25.62^\circ)^{1/2}$

$$(\phi + j\omega)^{1/2} \text{ mV}$$

$$= \sqrt{47.72} \angle \frac{25.62}{2}^\circ$$

$$(\phi + j\omega)^{1/2} \text{ mV}$$

$$= 6.9 \angle 12.8^\circ \quad \underline{\text{Ans}}$$

Ans

②

$$10 \angle -30^\circ + (3 - j4)$$

$$(2+j4)(3-j5)^* \rightarrow \text{conjugate}$$

$$(3+j5)$$

$$= 3.66 - 5j + 3 - j4$$

$$= 4.67 \angle 163.42^\circ + 5.83 \angle -59.03^\circ \quad 26.06 \angle 4.4^\circ$$

$$= 0.56 \angle -160^\circ \quad \underline{\text{Ans}}$$

$$\Rightarrow [a_1, b_1, c_1]$$

$$[a_2, b_2, c_2] = [j, 1, 0]$$

$$[a_3, b_3, c_3] = [j^2, 0, 1]$$

30/Aug/24

Q) Transform the sinusoids to phasors

$$\text{i) } V(t) = -4 \sin(30t + 50^\circ)$$

$$\Rightarrow = 4 \cos(30t + 140^\circ)$$

$$= 4 \angle 140^\circ \quad \checkmark$$

$$\text{ii) } i(t) = 6 \cos(50t - 40^\circ)$$

$$= 6 \angle -40^\circ \quad \checkmark$$

Q.2) Find the sinusoids for the given phasor.

$$\text{i) } I = -3 + j4$$

$$|I| = \sqrt{x^2 + y^2} \Rightarrow |I| = 5$$

$$= 5 \angle 126.86^\circ$$

$$\theta = \tan^{-1}\left(\frac{4}{3}\right) =$$

$$= 5 \cos(\omega t + 126.86^\circ)$$

$$\text{ii) } V = j \cdot 8 \cdot e^{-j20^\circ} \Rightarrow 8 \cos(\omega t + 70^\circ) \text{ Ans } I = 8 \left| \frac{j}{\omega j} \right| = 1 \angle 90^\circ$$

$$= 1 \angle 90^\circ \times 8 \angle -20^\circ$$

$$= 8 \angle 70^\circ$$

$$= 8 \cos(\omega t + 70^\circ)$$

$$\text{iii) } i_1(t) = 4 \cos(\omega t + 30^\circ)$$

$$\Rightarrow I_1 = 4 \angle 30^\circ$$

$$i_2(t) = 5 \sin(\omega t - 20^\circ)$$

$$\Rightarrow I_2 = 5 \angle -110^\circ$$

$$\hookrightarrow \cos(\omega t - 56.9^\circ)$$

$$i_1 + i_2 = 3.21 \angle -56.9^\circ$$

$$= 3.21 \cos(\omega t - 56.9^\circ)$$

Steps →

i) Convert to polar form.

ii) Add.

iii) Convert to time domain form.

$$\textcircled{IV} \quad V_1 = -10 \sin(\omega t + 30^\circ) \quad \left. \begin{array}{l} \text{Ans should be in} \\ \downarrow 10 \cos(\omega t + 120^\circ) \end{array} \right\} V_1 + V_2 \quad \begin{array}{l} \text{at steady state} \\ \text{Time domain form} \end{array}$$

$$V_2 = 20 \cos(\omega t - 45^\circ)$$

\Rightarrow

$$V_1 + V_2 = 10 \angle 120^\circ + 20 \angle -45^\circ$$

$$= 10.66 \angle -30.9^\circ$$

$$= 10.66 \cos(\omega t - 30.9^\circ)$$

Ans

$$\textcircled{V} \quad 4i(t) + 8 \int i(t) dt - 3 \frac{di(t)}{dt} = 50 \cos(\omega t + 75^\circ)$$

using the phasor approach, determine i .

\Rightarrow

i) Time domain to phasor domain

$$4I + 8 \frac{I}{j\omega} - 3I(j\omega) = 50 \angle 75^\circ$$

$$\cancel{4I} + \cancel{48I}$$

$$4I - 8Ij - 3Ij = 50 \angle 75^\circ$$

$$4I - 8Ij = 50 \angle 75^\circ$$

$$I = \frac{50 \angle 75^\circ}{4 - 10j}$$

$I =$

$$\frac{50 \angle 75^\circ}{10.64 - 68.19}$$

$$I = 4.64 \angle 143.19^\circ$$

$$\checkmark I = 4.64 \cos(2t + 143.2^\circ)$$

03/Sep/24

Phasor-Relationship for Circuit Elements

Time-domain

$$R \quad V(t) = R \cdot i(t)$$

$$L \quad V(t) = L \cdot \frac{di(t)}{dt}$$


$$C \quad V(t) = \frac{1}{C} \int i(t) dt$$

Phasor-domain

$$\bar{V} = RI$$

$$\bar{V} = j\omega L \cdot I$$

$$V = \frac{I}{j\omega C}$$

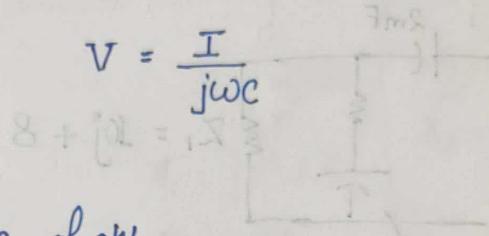

$Z = \frac{V}{I}$ is called Impedance of ckt.

in, when $\omega = 0$, $Z_L = 0 \Rightarrow DC$

out, $\omega = \infty, Z_L = \infty$

$\omega = 0, Z_C = \infty \Rightarrow DC$

$\omega = \infty, Z_C = 0$

e.g)

$$2 \frac{dv}{dt} + 5v(t) + 10 \int v(t) dt = 20 \cos(5t - 30^\circ)$$

$$\omega = 5$$

∴

$$2j\omega V + 5V + 10 \frac{V}{j\omega} = 20 \angle -30^\circ$$

$$10jV + 5V + \frac{2V}{j} = 20 \angle -30^\circ$$


$$5V + 8jV = 20 \angle -30^\circ$$

$$V = \frac{20 \angle -30^\circ}{5 + 8j} = 2.119 \angle -27.99^\circ$$

$$\checkmark V(t) = 2.119 \cos(5t + 27.99^\circ)$$

Ans

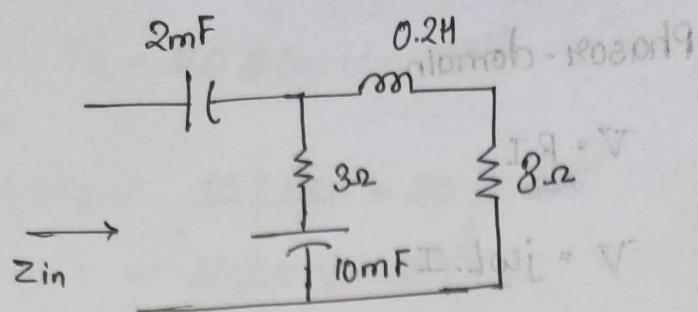
Q.1) Find the i/p impedance of ckt, assuming the $\omega = 50$ rad/s



diode - 9 mV

$$(\pm)i \cdot R = (\pm)V$$
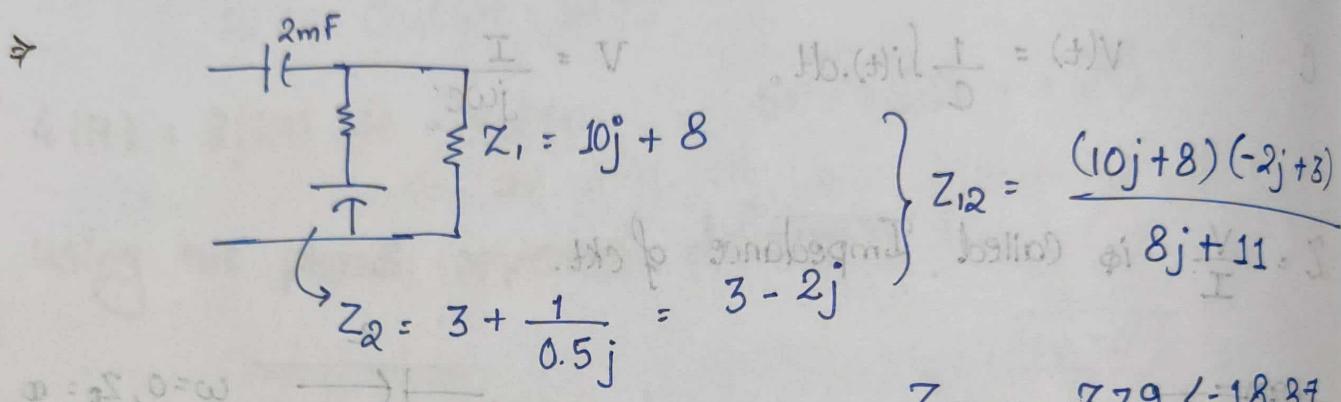
$$\frac{(\pm)i b \cdot L}{\pm b} = (\pm)V$$



$$Z_{12} = \frac{(10j+8)(-2j+3)}{8j+11}$$

$$Z_{12} = 3.39 \angle -18.87^\circ$$

$$Z_{12} = 3.217 - 1.06j$$

$$Z_{in} = \frac{1}{2 \times 50j} + 3.217 - 1.06j$$

$$= -10j + 3.217 - 1.06j$$


$$Z_{in} = 3.217 - 2.06j$$

$$Z_{in} = 3.217 - 11.06j$$

03/Sep/24

Q.2) Determine the V_o in the ckt


$$X_C = \frac{1}{j\omega C}$$

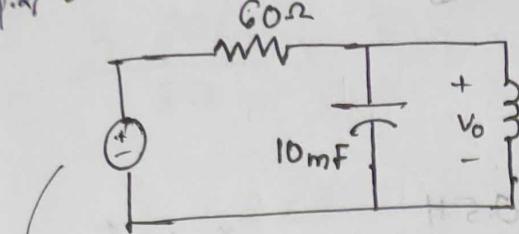

$$X_L = j\omega L$$

$$20 \cos(4t - 15^\circ)$$

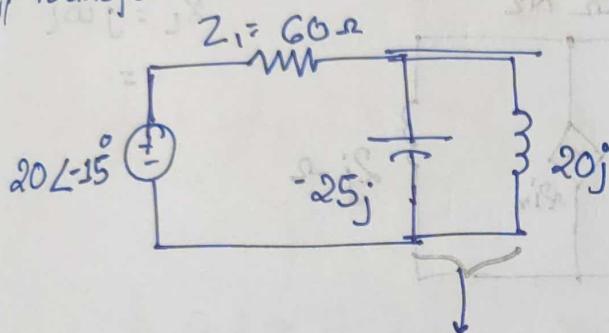Transform all the elements present in ckt in phasor domain.



$$X_L = j\omega L$$

$$\begin{aligned} X_L &= j \times 4 \times 5 \\ X_L &= 20j \end{aligned}$$

$$\omega = 4$$

$$X_C = \frac{1}{j \times 4 \times 10} = \frac{1}{1000}$$

$$X_C = -20j$$

$$X_C = -25j$$

$$Z_2 = \frac{X_L X_C}{X_L + X_C}$$

$$Z_2 = 100j$$

~~$$Z_{\text{Res}} = 60 + 100j$$~~

~~$$V_o = \frac{20 \angle -15^\circ}{60 + 100j} = 0.047 - 0.165j$$~~

$$V_o = V \times \frac{Z_2}{Z_1 + Z_2}$$


~~$$V_o = 0.175 \angle -74.0^\circ$$~~

$$V_o = \frac{100j \times 20 \angle -15^\circ}{60 + 100j}$$

$$V_o = 17.15 \angle 15.96^\circ$$


$$V_o = 17.15 \cos(4t + 15.96^\circ)$$

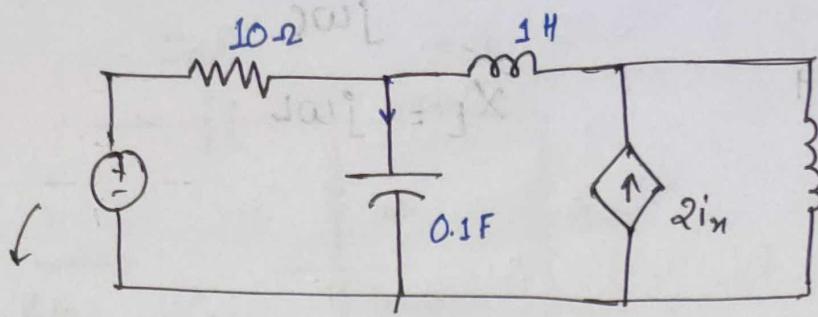Q.3) Find i_x in the ckt using Nodal Analysis



$$x_c = \frac{1}{j\omega C} = \frac{1}{j \times 4 \times 0.1} = -2.5j$$

$\omega = 4$

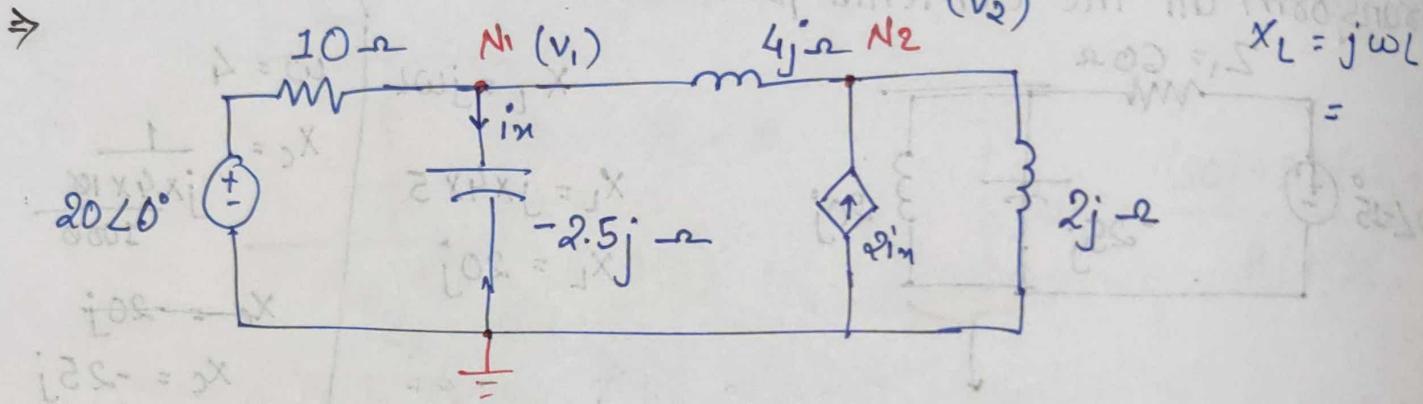

Nodal Analysis at N1

KCL at $N_1 \Rightarrow$

$$\frac{V_1 - 20\angle 0^\circ}{10} + \frac{V_1 - V_2}{4j} + \frac{V_1}{-2.5j} = 0 \quad \text{--- (1)}$$

$$\frac{V_1 - 20\angle 0^\circ}{10} + \frac{V_2 - V_1}{4j} + \frac{V_1}{-2.5j} = 0$$

KCL at $N_2 \Rightarrow$

$$\frac{V_2 - V_1}{4j} + 2i_x + \frac{V_2}{2j} = 0 \quad \text{--- (2)}$$

$$i_x = \frac{V_1 - V_2}{-2.5j}$$

$$\frac{V_1 - V_2}{4} - \frac{V_1}{2.5j} - \frac{V_2 j}{2} = 0$$

$$\frac{V_1 - 20 \angle 0^\circ}{10} - \frac{V_2 j}{2} = 0$$

$$\frac{V_1}{10} - 2 \angle 0^\circ - \frac{V_2}{2} j = 0$$

$$v_i \left(\frac{1}{10} - \frac{j}{4} + \frac{j}{2.5} \right) v_i + \left(\frac{j}{4} \right) v_2 = -2 \angle 0^\circ$$

$$\left(\frac{j}{4} - \frac{j}{2.5} \right) v_i + \left(-\frac{j}{4} - \frac{j}{2} \right) v_2 = 0$$

$$0 = (s_i - s_i)(s_i) - (s_i - s_i)s_i - i8 -$$

$$\left(\frac{1}{10} 0.1 + 0.15j \right) v_i + (0.25j) v_2 = 2 \angle 0^\circ + i8 +$$

$$\rightarrow (-0.15j) v_i + (0.15j) v_2 = 2 \angle 0^\circ + s_i(i8) - i(i8)$$

$$\begin{bmatrix} (A) & (B) & (F) \\ \begin{bmatrix} 0.1 + 0.15j & 0.25j \\ -0.15j & 0.1 + 0.15j \end{bmatrix} & \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} & = \begin{bmatrix} 2 \angle 0^\circ \\ (1 - 0) \end{bmatrix} \\ (C) & (D) & (E) \end{bmatrix} - (s_i - s_i)(i8) -$$

$$V_1 = \frac{\Delta}{\Delta_1} = \frac{0AD - BC}{ED - FB} = \frac{s_i A - 0.168 \angle 153.43^\circ}{1.5 \angle 90^\circ} = 0.112 \angle 63.43^\circ$$

$$V_1 = 0.054 + 0.109j$$


$$V_2 = \frac{\Delta_2}{\Delta_0} = \frac{AF - CE}{AD - BC} = \frac{0.3i}{-0.15 + 0.075i} = \frac{0.8 - 1.6i}{(1 - s_i)(i8)} =$$

$$0 = (s_i - 0.112)(i8) - (s_i - 0.112)(i8) -$$

$$0 = i(i8) + 0.112 \cdot i8 - i(i8) + 0.112 \cdot i8$$

04/Sep/24

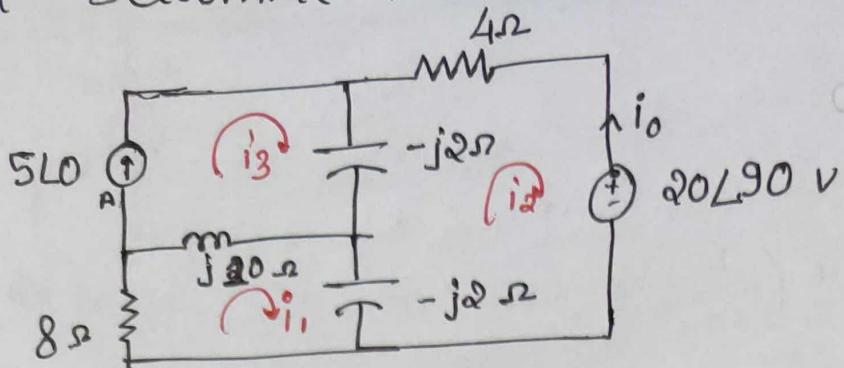Q. If determine the current i_0 in the ckt using mesh analysis



$$0 = i \frac{dV}{ds} - 0.5 \angle 2 - \frac{1V}{dt}$$

\Rightarrow

KVL

Mesh-1

$$-8i_1 - 10j(i_1 - i_3) - (-j2)(i_1 - i_2) = 0$$

$$-8i_1 - 10j i_1 + 10j i_3 + 2j i_1 - 2j i_2 = 0$$

$$(-8 - 8j)i_1 + (-2j)i_2 + (10j)i_3 = 0 \quad \text{--- (1)}$$

mesh-2

$$-(2j)(i_2 - i_3) - (2j)(i_2 - i_1) - 4i_2 - 20\angle 90 = 0$$

$$(2j)i_2 - (2j)i_3 + (2j)i_2 - (2j)i_1 - 4i_2 = 20\angle 90$$

$$(-2j)i_1 + (-4 + 4j)i_2 + (-2j)i_3 = 20\angle 90 \quad \text{--- (2)}$$

Mesh-3

$$-(10j)(i_3 - i_1) - (-2j)(i_3 - i_2) + 5\angle 0 = 0 \quad i_3 = 5\angle 0$$

$$(-10j)i_3 + (10j)i_1 + (2j)i_3 + (-2j)i_2 = -5\angle 0$$

$$-(-2j)(5\angle 0 - i_2) - (10j)(5\angle 0 - i_1) = 0$$

$$2j \cdot 5\angle 0 + (-2j)i_2 - 10j \cdot 5\angle 0 + (10j)i_1 = 0$$

04/Sep/24

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} E \\ F \end{bmatrix}$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{EB - BF}{AD - BC} = \frac{140 + 200j}{68} = 140 + 2.94j$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{AF - CE}{AD - BC} = \frac{340 - 240j}{68} = 5 - 3.529j$$

$$i_1 = 140 \angle 1.2^\circ$$

$$i_2 = 6.12 \angle -35.2^\circ$$

$$i_1 = 118 - (6.12)(j) - j(118) -$$

$$i_1 = -6.12 \angle -35.2^\circ$$

$$i_2 = 6.12 \angle 87^\circ$$

$$i_1 = 6.12 \angle 87^\circ + j(6.12)$$


$$\begin{bmatrix} 6.12 & 0 \\ 0 & 118 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 6.12 \\ 118 \end{bmatrix}$$

$$i_1 = \frac{6.12 \angle 87^\circ}{118} = \frac{6.12 \angle 87^\circ}{118} = \frac{6.12 \angle 87^\circ}{118} = 0.052 \angle 87^\circ$$

$$\frac{6.12 \angle 87^\circ}{118} = \frac{6.12 \angle 87^\circ}{118} = 0.052 \angle 87^\circ$$

Ques.2

$$i_o = ?$$

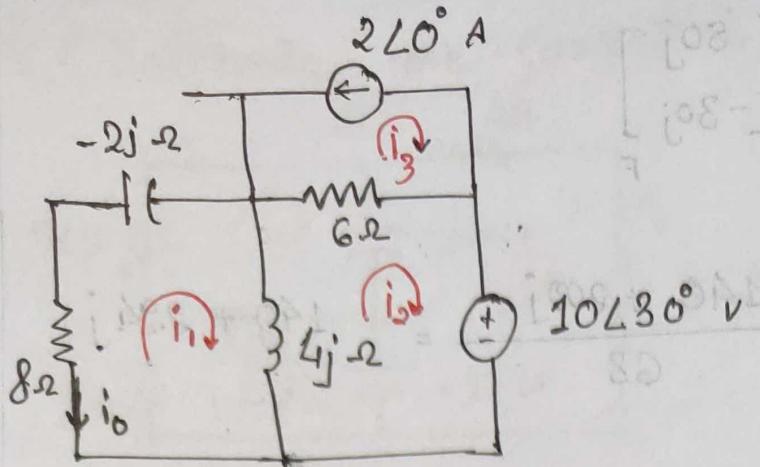

KVL

Mesh-1

$$-(-2j)i_1 - (4j)(i_1 - i_2) - 8i_1 = 0$$

$$2j i_1 - 4j i_1 + 4j i_2 - 8i_1 = 0$$

$$(8 - 2j) i_1 + (4j) i_2 = 0 \quad \text{---(1)}$$

Mesh-3

$$i_3 = -2∠0°$$

Mesh-2

$$-(4j)(i_2 - i_1) - 6(i_2 + i_3) = 10∠30°$$

$$-4j i_2 + 4j i_1 - 6i_2 = 12∠0°$$

$$= 10∠30°$$

$$(4j) i_1 + (-6 - 4j) i_2 = -2$$

$$\begin{bmatrix} (a) & & (b) & & (c) & \\ -8 - 2j & 4j & & & & \\ 4j & -6 - 4j & & & & \\ (d) & & i_1 & & 0 & \\ & & & i_2 & -3.34 + 5j & \\ & & & & & (f) \end{bmatrix} = \begin{bmatrix} (e) \\ & & & & & \end{bmatrix}$$

$$f = \frac{21.256}{-13.6^\circ}$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{ED - FB}{AD - BC} = \frac{0.336 - 0.026j}{1.19} = 0.274 \angle -4.41^\circ$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{AF - CE}{AD - BC} = 0.696 \angle -80.37^\circ$$

$$i_o = -i_1 = -1.19 \angle -114.5^\circ$$




Ans

Find the node Voltages?

Ques. 3)

0.2F

4Ω

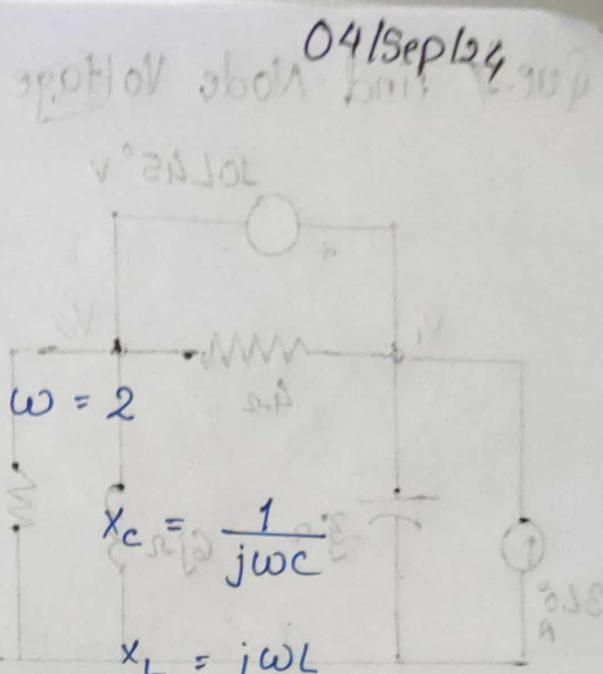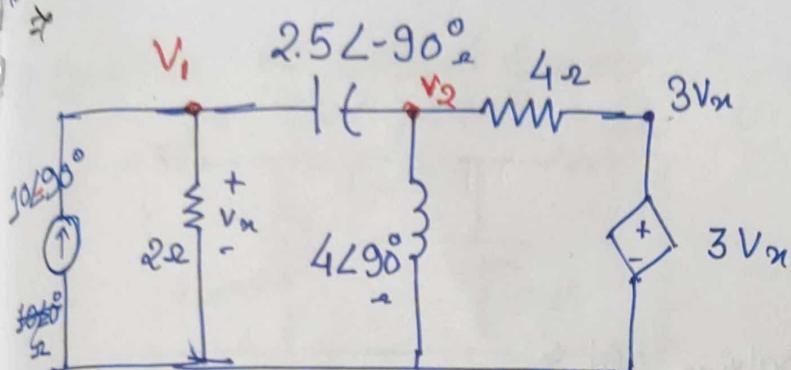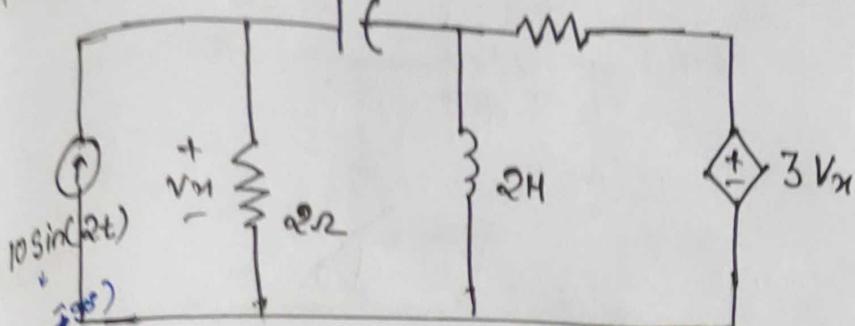

$$V_{RN} = \frac{V_1 - V_2}{2}$$

$$V_1 = V_{RN}$$

$$\underline{\text{At } V_2}$$

$$-10\angle 90^\circ + \frac{V_1}{2} + \frac{V_1 - V_2}{2.5\angle -90^\circ} = 0, \quad \frac{V_2 - V_1}{2.5\angle 90^\circ} + \frac{V_2}{4\angle 90^\circ} + \frac{V_2 - 3V_x}{4} = 0$$



$$\left. \frac{V_1}{2} + \frac{V_1}{2.5\angle -90^\circ} - \frac{V_2}{2.5\angle -90^\circ} = 10\angle -90^\circ \quad (1) \right)$$

$$\frac{V_2}{2.5\angle 90^\circ} - \frac{V_1}{2.5\angle 90^\circ} + \frac{V_2}{4\angle 90^\circ} + \frac{V_2}{4} - \frac{3V_1}{4} = 0$$


$$\left(-\frac{1}{2.5\angle 90^\circ} - \frac{3}{4} \right) V_1 + \left(\frac{1}{4} + \frac{1}{2.5\angle 90^\circ} + \frac{1}{4\angle 90^\circ} \right) V_2 = 0$$

$$V_1 = 54.63 \angle 99.72^\circ$$

Que. Find Node Voltage

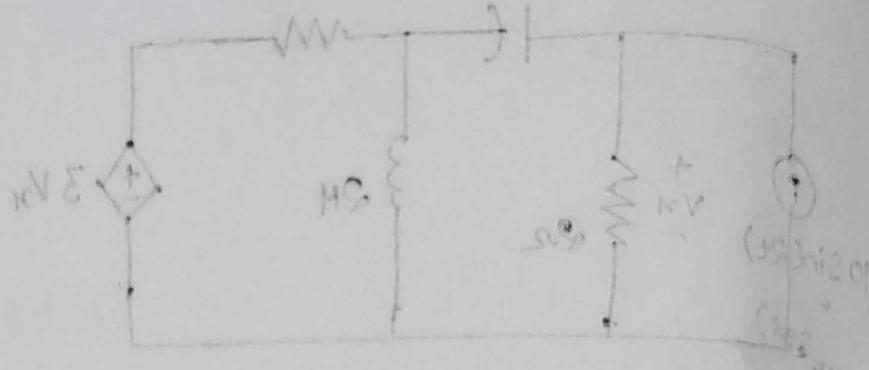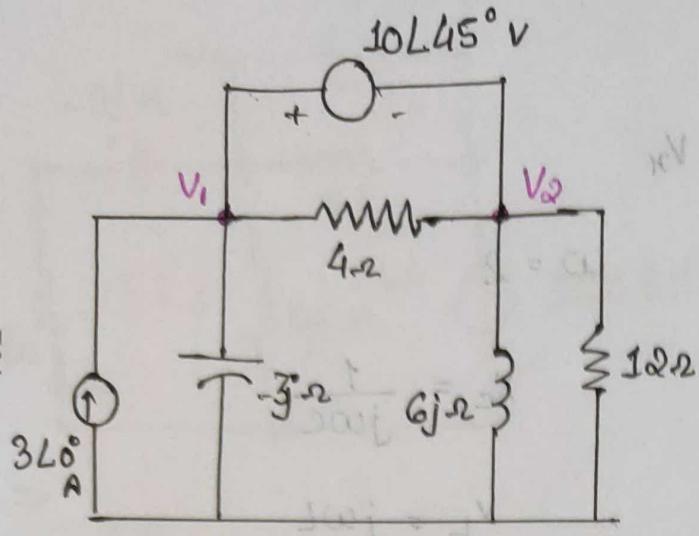


Applying Super Node Analysis →

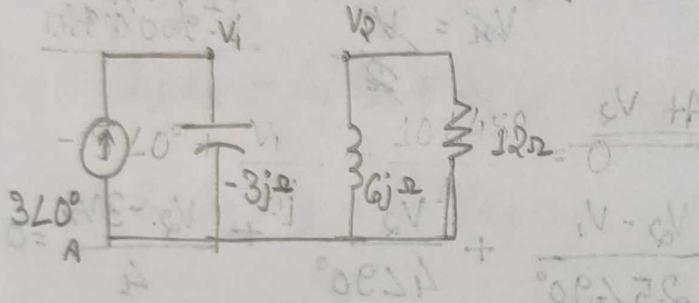

Applying KCL ⇒

$$-3L0^\circ + \frac{V_1}{-3j} + \frac{V_2}{6j} + \frac{V_2}{12} = 0$$
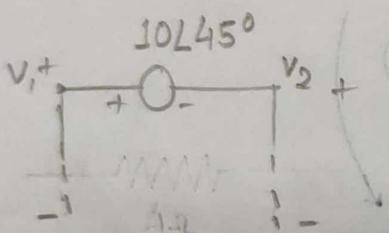
$$\left(\frac{1}{3}\right)V_1 + \left(\frac{-j}{6} + \frac{1}{12}\right)V_2 = 3L0^\circ - 0$$



Applying KVL ⇒

$$V_1 - 10L45^\circ - V_2 = 0$$

$$\begin{bmatrix} \frac{j}{3} & \frac{-j}{6} + \frac{1}{12} \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3L0^\circ \\ 10L45^\circ \end{bmatrix}$$


$$V_1 = \frac{\Delta_1}{\Delta} = \frac{ED - FC}{AD - BC} = 25.78 \angle -70.48^\circ$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{AF - CE}{AD - BC} = 31.4 \angle -87.18^\circ$$





Ques.2}

Find $V_o(t)$ using superposition theorem.

04/Sept/24

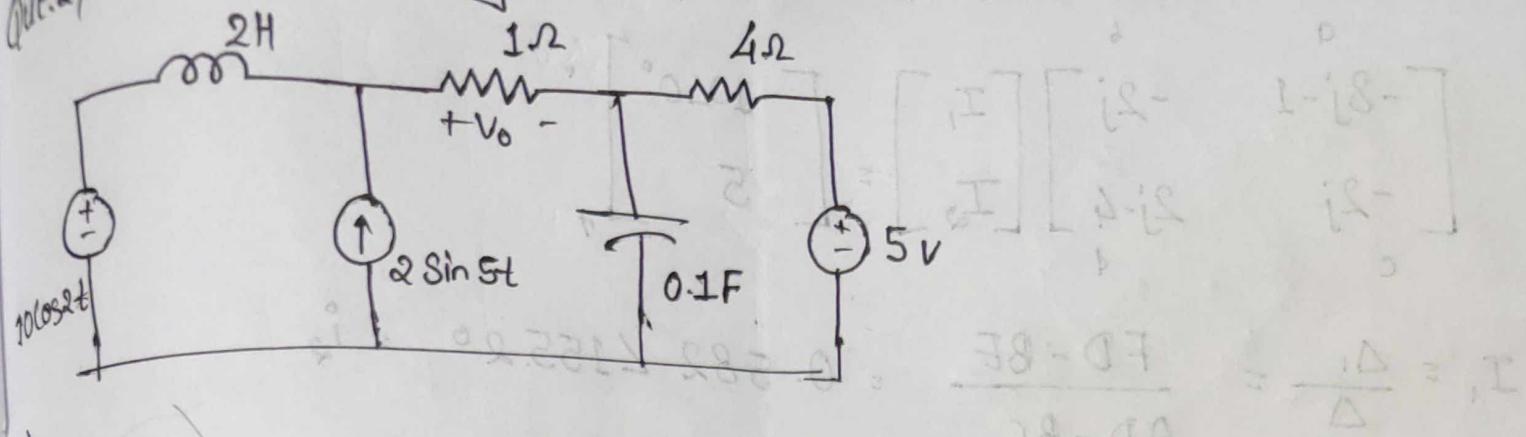


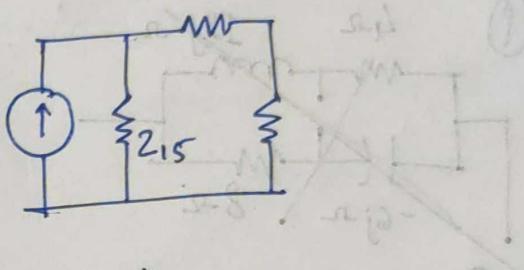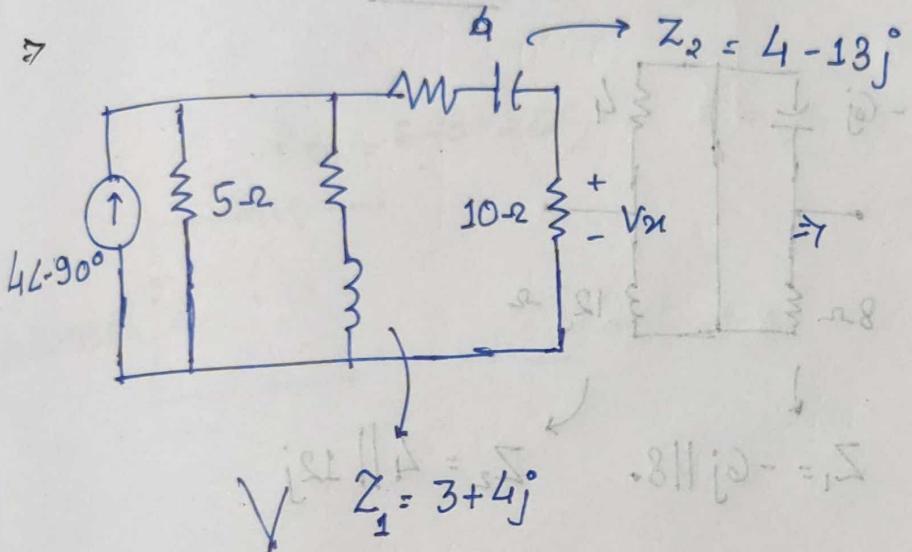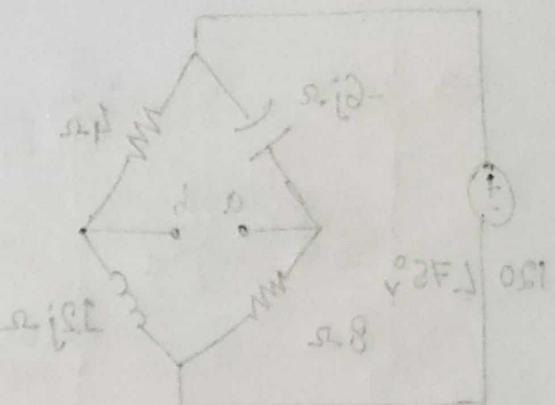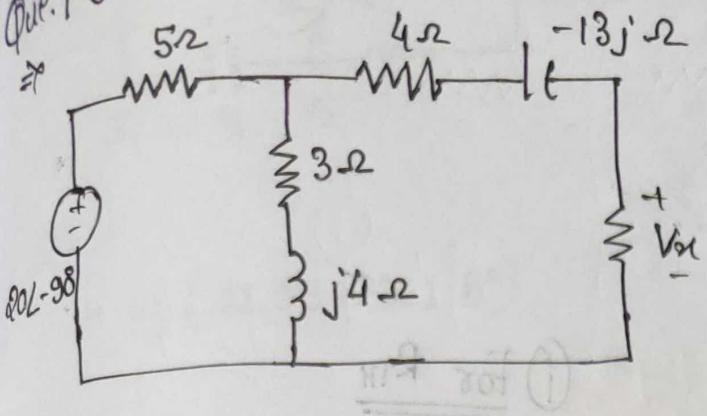Ques. Calculate V_x in the ckt, using Source Transformation 06/Sept/24



$$Z_{15} = \frac{15 + 25 \angle 53.1^\circ}{8.94 \angle 26.56^\circ}$$

$$Z_{15} = 2.796 \angle 26.54^\circ$$

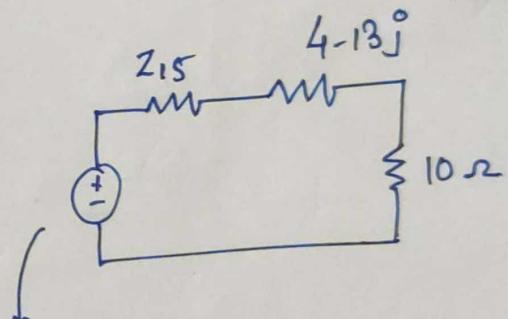

$$11.184 \angle -63.46^\circ \text{ V}$$

$$I = \frac{11.184 \angle -63.46^\circ}{j2.15 + j4 + j10}$$

$$I = 0.552 \angle -28^\circ$$



$$V_x = 0.552 \angle -28^\circ \Rightarrow V_x = 4.874 - 2.59j$$

~~$$V_x = 48.74 - 25.9j$$~~



~~$$(80\angle 0 + 0.552\angle -28^\circ) \times 8I$$~~

~~$$48.74 + 25.9j$$~~

(Ques.) Obtain the thevinin's Eqn. Ckt

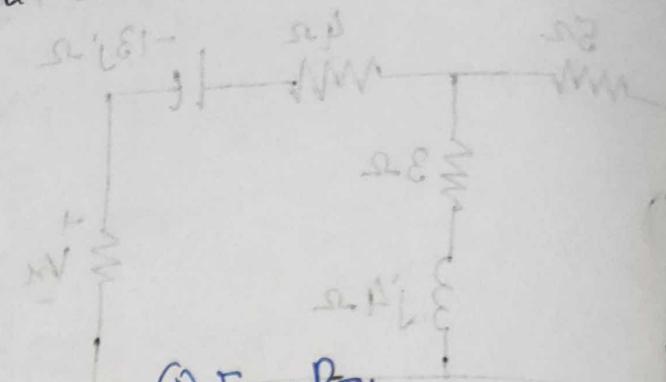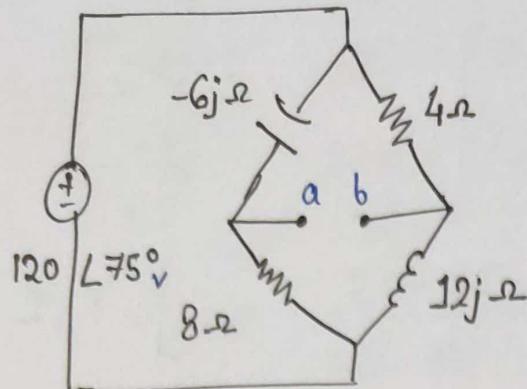

(i) For R_{TH}

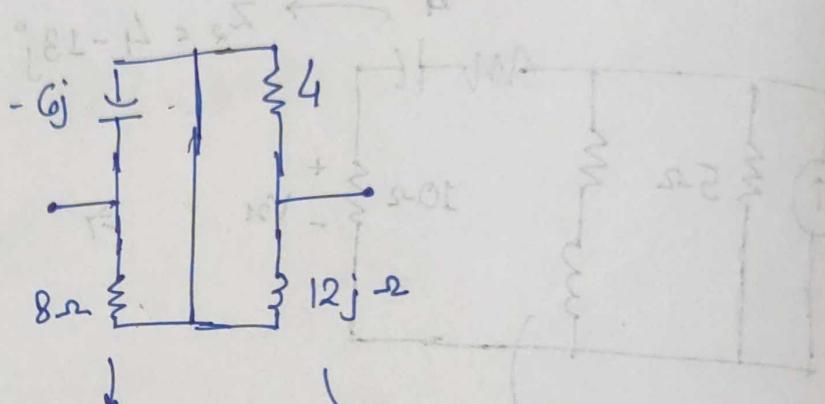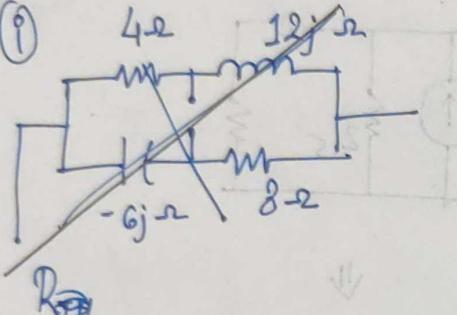

$$Z_1 = -6j \parallel 8 \quad Z_2 = 4 \parallel 12j$$

$$Z_{TH} = Z_1 + Z_2$$

$$Z_{TH} = 2.88 - 3.84j + 3.6 + 1.2j$$

$$Z_{TH} = 6.48 - 2.64j$$

(ii) For V_{TH}

$$I_1 = \frac{4+12j}{12+6j} \times I$$

$$V_a = \frac{-6j}{8-6j} \times 120 \angle 75^\circ$$

$$I_1 = \frac{120 \angle 75^\circ}{8+6j}$$

$$I = \frac{120 \angle 75^\circ}{4+12j \parallel 8-6j}$$


$$I_2 = \frac{120 \angle 75^\circ}{4+12j}$$

$$I_1 = -4.47 + 11.13j$$

$$I_1 = 11.99 \angle 111.8^\circ$$

$$I_2 = 9.469 + 0.568j$$

$$9.48 \angle 3.43^\circ$$

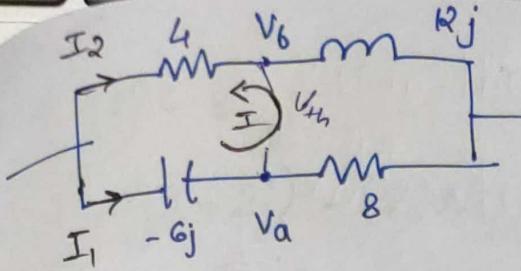


$$\text{KVL} \quad -6j(11.99 \angle 111.8^\circ)$$

$$V_{TH} + (-6j)i_1 - 4i_2 = 0$$


$$V_{TH} = 4i_2 + 6j i_1$$

$$V_{TH} = 37.8 \angle -139.8^\circ$$

$$R_{TH} = 6.48 - 2.64j$$


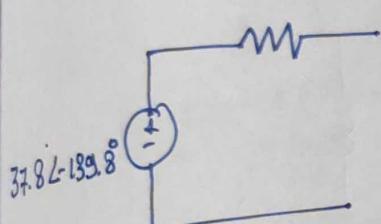


$$Z = R + jX$$

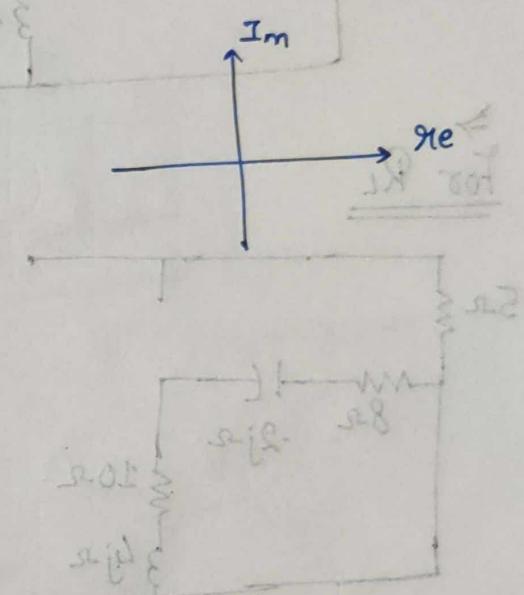

solución de la red

sección 9 potencia y potencia útil

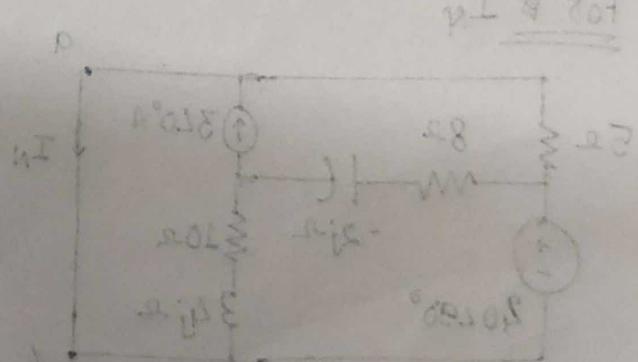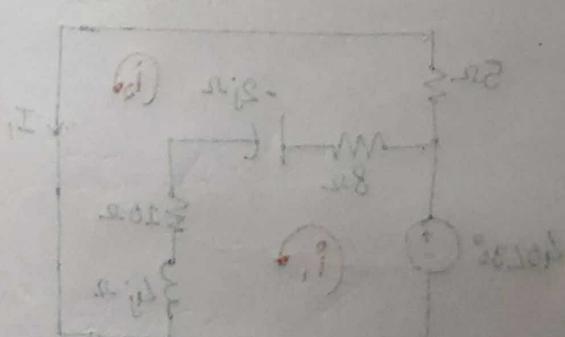


$$0 = (sL - jI)(jC + s) - 37.8 \angle -139.8^\circ$$

$$sI(C(jL + s)) + jI(jC + s) = 37.8 \angle -139.8^\circ$$


$$0 = (sL - jI)(jC + s) - 37.8 \angle -139.8^\circ$$

$$0 = \frac{-37.8 \angle -139.8^\circ}{jL + s} = sL - jI$$

Q.4) obtain i_o using Norton's Theorem.

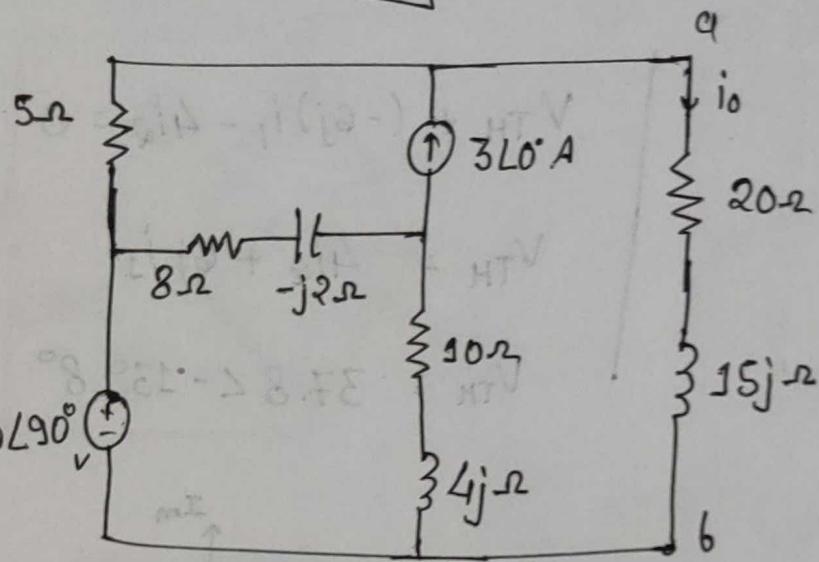


\Rightarrow
For R_L

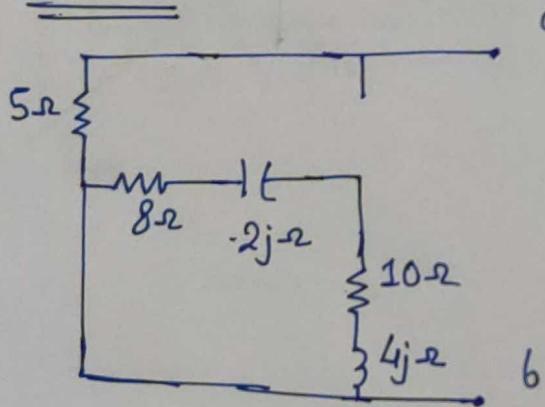

$$R_N = 5\Omega$$

Maximum Power Transfer

Linear CKt

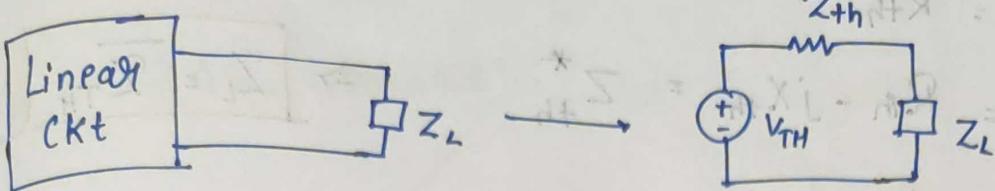

$$Z_{th} = R_{th} + jX_{th} \quad , \quad Z_L = R_L + jX_L$$

Current through the load = $I_L = \frac{V_{th}}{Z_{th} + Z_L} = \frac{V_{th}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}}$

Average power delivered to load, $P = \frac{1}{2} I^2 R_L$

$$= \frac{|V_{th}|^2 R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$

For max Power,

$$\frac{\partial P}{\partial X_L} = \frac{-(V_{th})^2 \cdot R_L \cdot (X_{th} + X_L)}{[(R_{th} + R_L)^2 + (X_{th} + X_L)^2]^2}$$

$$\frac{\partial P}{\partial R_L} = \frac{(V_{th})^2 [(R_{th} + R_L)^2 + (X_{th} + X_L)^2 - (2R_L(R_{th} + R_L))]}{2[(R_{th} + R_L)^2 + (X_{th} + X_L)^2]^2}$$

$$\frac{\partial P}{\partial X_L} = 0 \Rightarrow X_L = -X_{th} \quad \text{--- (1)}$$

$$\frac{\partial P}{\partial R_L} = 0 \Rightarrow R_L = \sqrt{R_{th}^2 + (X_{th} + X_L)^2} \quad \text{--- (2)}$$

from ① & ②, for max. Power transfer


$$X_L = -X_{th}, \quad R_L = R_{th}$$

$$Z_L = R_L + jX_L = R_{th} - jX_{th} = Z_{th}^* \Rightarrow Z_L = \overline{Z}_{th}$$


$$P_{max} = \frac{|V_{th}|^2}{8R_{th}}$$

Condition for max Power

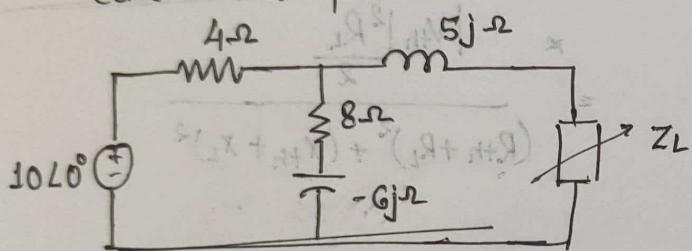Ques.1) Determine the load impedance for max. Power
Calc. Max power



For $Z_{th} \Rightarrow$

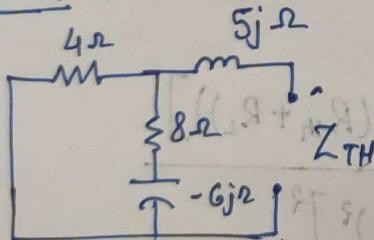


$$2.98 \angle 0.179$$

$$Z_{th} = 5.343 \angle 0.989$$

$$Z_{th} = 5.343 \angle 56.7^\circ$$

For $V_{th} \Rightarrow$

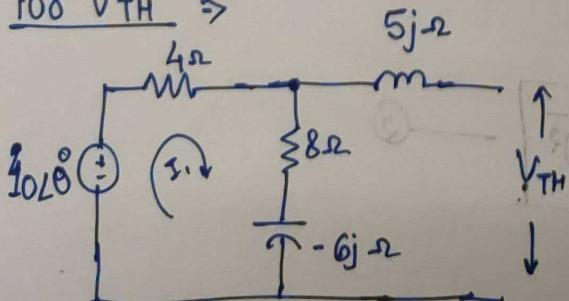

$$V_{th} =$$

$$10 \angle 0^\circ - 4I_1 - 8I_1 + 6jI_1 = 0$$

$$I_1 = \frac{10 \angle 0^\circ}{12 - 6j}$$

$$I_1 = 0.745 \angle -46.5^\circ$$

$$\angle 26.56^\circ$$

$$(8 - 6j)(0.745 \angle 0.463^\circ)$$

$$V_{TH} = 7.45 \angle -0.179^\circ - 10.30^\circ$$

$$P_{max} = \frac{(7.45 \angle -0.179^\circ)^2}{8(5.343 \angle 0.989^\circ)}$$

$$P_{max} = 1.299 \angle -1.348^\circ$$

$$V_{TH} = (8 - 6j)(0.745 \angle 26.56^\circ)$$


$$V_{TH} = 7.45 \angle -10.3^\circ$$

$$P_{max} = \frac{|V_{TH}|^2}{8 R_{TH}} = \frac{(7.45)^2}{8 \times 2.933}$$

$$P_{max} = 2.365 \text{ W}$$

$$0 = V \left(\frac{1}{j0.1} + \frac{1}{j0.8} \right) + IV \left(\frac{1}{j0.1} \right) \quad \left| \begin{array}{l} 0 = V \left(\frac{1}{j0.1} + \frac{1}{j0.8} \right) + IV \left(\frac{1}{j0.1} \right) \\ 0 = V \left(\frac{1}{j0.1} + \frac{1}{j0.8} \right) + IV \left(\frac{1}{j0.1} + \frac{1}{j0.8} \right) \end{array} \right.$$
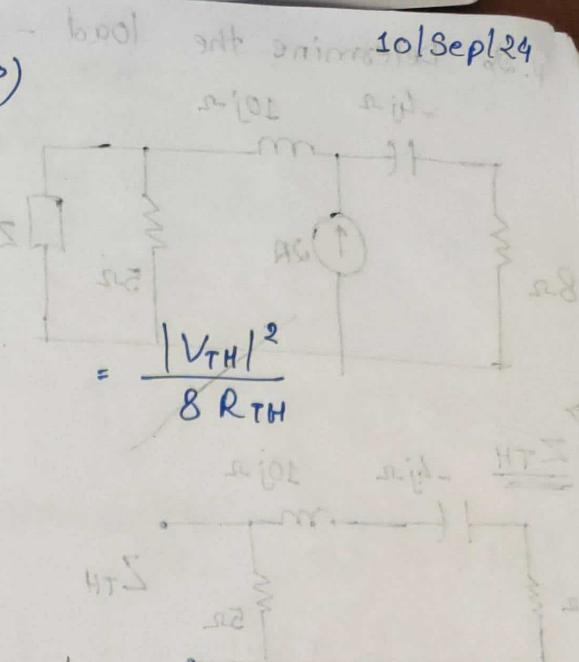
$$\begin{bmatrix} 0 \\ I \end{bmatrix} = \begin{bmatrix} V \\ IV \end{bmatrix} \begin{bmatrix} \frac{1}{j0.1} & \frac{1}{j0.1} + \frac{1}{j0.8} \\ \frac{1}{j0.1} + \frac{1}{j0.8} & \frac{1}{j0.8} \end{bmatrix}$$





$$Z_{TH} = 2.933 + 4.465j$$

$$Z_L = 2.933 - 4.465j$$


$$0 = \frac{5V - IV}{j0.1} + (I) + \frac{0 - IV}{j0.8}$$

$$\frac{3V - 3A}{j0.1} = jV$$

Q. 2p Determine the load

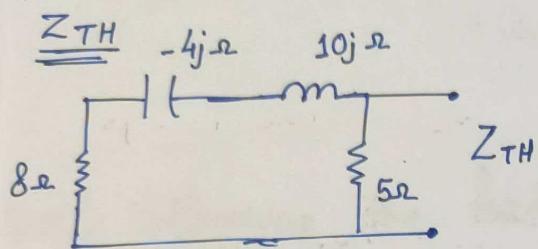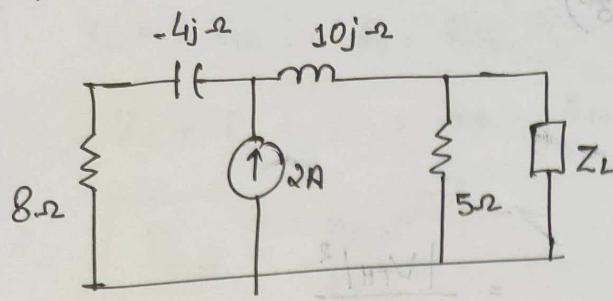

$$Z_{TH} = 3.49 \angle 12.09^\circ$$

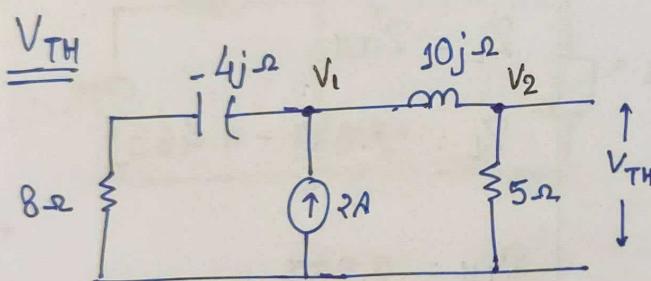

$$\frac{V_1 - 0}{8 - 4j} + (-2) + \frac{V_1 - V_2}{10j} = 0 \quad \left| \begin{array}{l} \frac{V_2 - V_1}{10j} + \frac{V_2}{5} = 0 \\ \left(\frac{1}{8 - 4j} + \frac{1}{10j} \right) V_1 + \left(-\frac{1}{10j} \right) V_2 = 2 \end{array} \right. \quad \text{--- (1)}$$

$$\left(\frac{1}{8 - 4j} + \frac{1}{10j} \right) V_1 + \left(-\frac{1}{10j} \right) V_2 = 2 \quad \left| \begin{array}{l} \left(-\frac{1}{10j} \right) V_1 + \left(\frac{1}{5} + \frac{1}{10j} \right) V_2 = 0 \end{array} \right.$$

$$\begin{bmatrix} \frac{1}{8 - 4j} + \frac{1}{10j} & -\frac{1}{10j} \\ -\frac{1}{10j} & \frac{1}{5} + \frac{1}{10j} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

$$V_2 = \frac{AF - CE}{AD - BC} =$$

10/Sept/24

$$I_5 = \frac{Z_2}{Z_1 + Z_2} \times I = \frac{(8 - 4j)}{(5 + 10j + 8 - 4j)} \times 2 = \frac{10}{13 + 6j} = \frac{10}{\sqrt{169 + 36}} = \frac{10}{\sqrt{205}} = HTV$$

$$I_{5a} = 1.249 \angle -51.34^\circ$$

$$V_{TH} = 5 I_5$$

$$V_{TH} = 6.247 \angle -51.34^\circ$$


$$P_{max} = \frac{(V_{TH})^2}{8 R_{TH}} \Rightarrow P_{max} = 0.223 \angle -127.8^\circ$$

$$P_{max} = \frac{(6.247)^2}{8 \times 3.412}$$


$$P_{max} = 1.43 W$$

$$Z_L = Z_{TH}^* = 3.412 - 0.731j$$

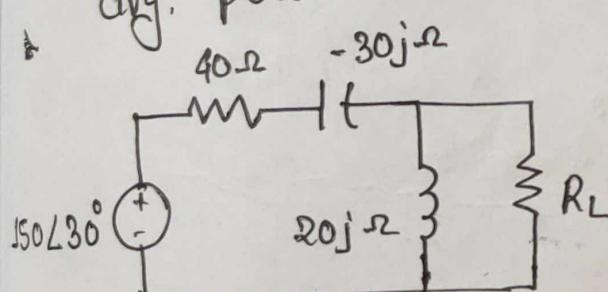Ques.3) Find the value of R_L that will absorb the max. avg. power.



For Z_{TH}

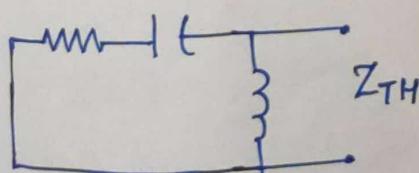

$$Z_{TH} = \frac{(40 - 30j) 20j}{40 - 10j}$$

$$Z_{TH} = 24.25 \angle 67.16^\circ$$

$$= 9.41 + 22.35j$$

For V_{TH}

$$V_{TH} = \frac{20j}{40 - 10j} \times 150 \angle 30^\circ$$

$$V_{TH} = 72.76 \angle 134^\circ \text{ V}$$

$$x_L = 0 \Rightarrow R_L = |Z_{TH}|$$

$$\left| \begin{array}{l} Z_L = Z_{TH}^* \\ R_L = R_{TH} - X_{TH} j \end{array} \right.$$

$$R_L = \sqrt{(9.41)^2 + (22.35)^2}$$


$$R_L = 24.25 \Omega$$

$$P_{max} = \frac{|V_{TH}|^2}{8R_L}$$


$$= 27.288 \text{ W}$$

$$P_{max} = \frac{1}{2} I_L^2 R_L = \frac{1}{2} \times \left(\frac{V_{TH}}{R_L + Z_{TH}} \right)^2 \times R_L$$
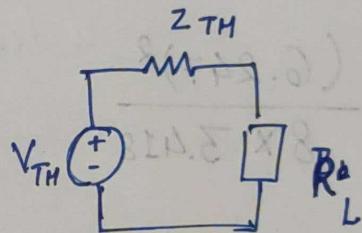
$$= \frac{1}{2} \times \left(\frac{72.76 \angle 134^\circ}{24.25 + (9.41 + 22.35j)} \right)^2 \times 24.25$$



$$\checkmark P_{max} = 39.31 \text{ W}$$

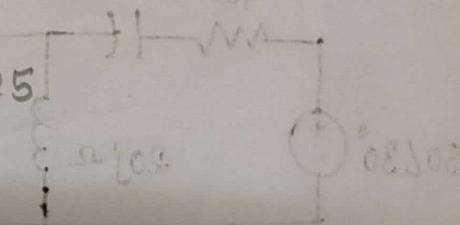


Q.L.F.D $\Delta 22.48$

$\{ 23.22 + 14.9 \text{ } \}$

11 Sep 24


Frequency Response \Rightarrow

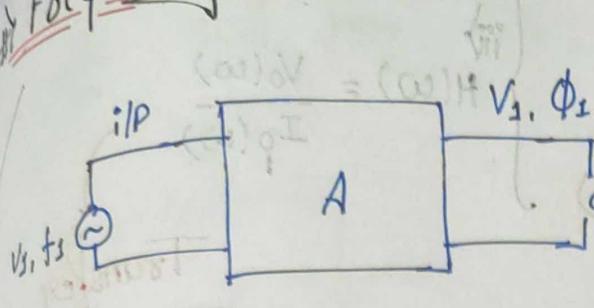

when i/p is freq.

changed how the o/p v or ϕ changes

(more option)

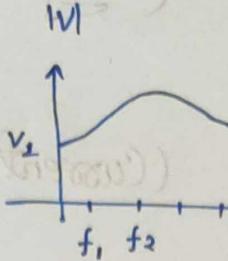

$$(\omega)v = (\omega)H$$

$$(\omega)v = (\omega)H$$

$$(\omega)\phi = (\omega)H$$

$$(\omega)\phi = (\omega)H$$

$$\frac{(\omega)v}{(\omega)v} = (\omega)H$$

$$(\omega)v = (\omega)H$$

$$(\omega)\phi = (\omega)H$$


$$(\omega)\phi = (\omega)H$$

If the amp. of sinusoidal source remains const. & vary the freq. we obtain the ckt frequency response.

The frequency response of the ckt is the variation in h/s behaviour with change in signal freq.

The transfer function also called as Newtowr functn is a useful analytical tool for finding a frequency response of ckt.

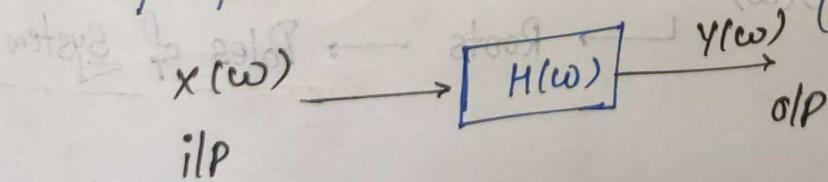The transfer functn of the Circuit is the frequency dependent ratio of phasor o/p $y(\omega)$ to phasor i/p $x(\omega)$.



$x(\omega)$ $y(\omega)$ (x & y can be either Voltage or Current)

$$H(\omega) = \frac{y(\omega)}{x(\omega)}$$

Transfer functn
Network functn

Voltage Gain

Current Gain

Transfer Impedance

$$\text{i} H(\omega) = \frac{V_o(\omega)}{V_i(\omega)}$$

$$\text{ii} H(\omega) = \frac{I_o(\omega)}{I_i(\omega)}$$

$$\text{iii} H(\omega) = \frac{V_o(\omega)}{I_o(\omega)}$$

$$\text{iv} H(\omega) = \frac{I_o(\omega)}{V_i(\omega)}$$

Time Domain Freq. Domain

$R \longleftrightarrow R$

$$L \xrightarrow{j\omega L}$$

$$C \xrightarrow{\frac{1}{j\omega C}}$$


$H(\omega) = \frac{N(\omega)}{D(\omega)}$ $N(\omega) = 0$ Roots of Numerator polynomial
 if ω is a root of $N(\omega) = 0$ then it is called Zeroes of System

$D(\omega) = 0$ Roots \rightarrow Poles of System


$$\frac{(a_1Y)}{(a_0X)} = \frac{(a_3Y)}{(a_2X)}$$

For the RC Ckt. obtain the transfer functn and freq. Response

11/Sep/24

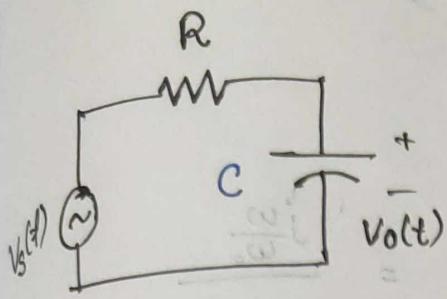

Freq. Equivalent

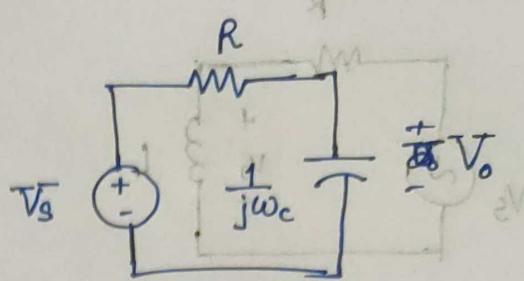

$$H(\omega) = \frac{V_o}{V_s} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

$$H = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}} \quad \boxed{\tan^{-1}(\frac{\omega}{\omega_0})}$$


$$\text{where, } \omega_0 = \frac{1}{RC}$$

To plot $|H|$ & ϕ


$$\omega = 0, |H| = 1, \phi = 0$$

$$\omega = \infty, |H| = 0, \phi = -90^\circ$$


$$\omega = \omega_0, |H| = \frac{1}{\sqrt{2}}, \phi = -45^\circ$$

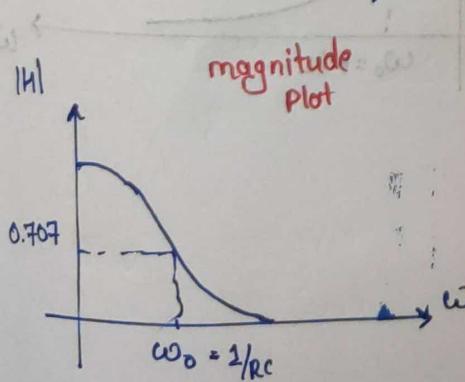

Phase Plot

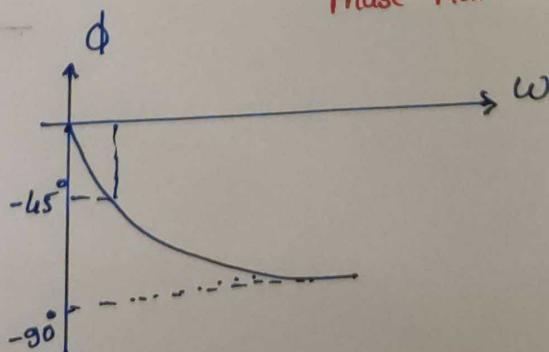


Transfer function of RL Ckt.

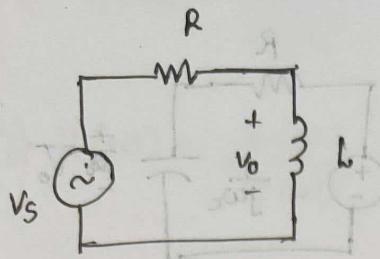

$$V_o = \frac{j\omega L}{R + j\omega L} V_s$$
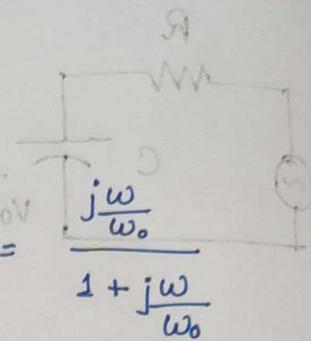
$$\frac{V_o}{V_s} = \frac{j\omega L / R}{1 + j\omega L / R}$$






$$H(\omega) = \frac{\omega}{\omega_0} e^{j\phi} \quad \text{where } \phi = \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$\text{where, } \omega_0 = \frac{R}{L}$$



$$\text{when, } \omega = 0, |H| = 0, \phi = 90^\circ$$

$$\omega = \infty, |H| = 1, \phi = 0$$

$$\omega = \omega_0, |H| = \frac{1}{\sqrt{2}}, \phi = 45^\circ$$

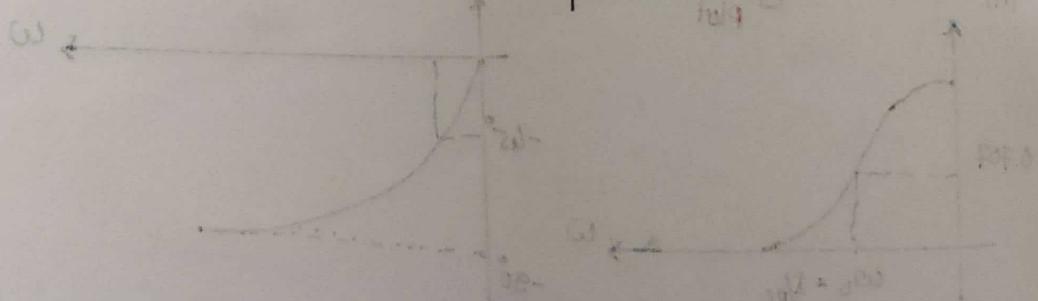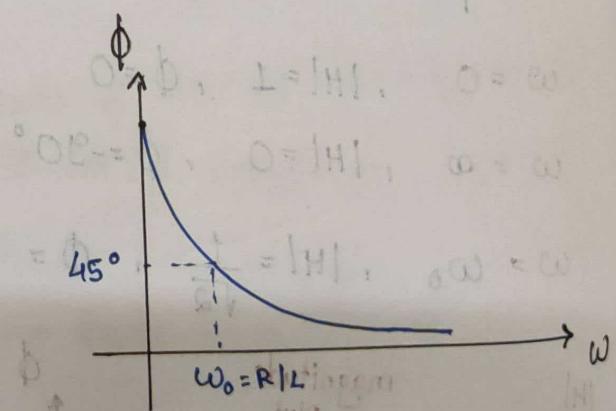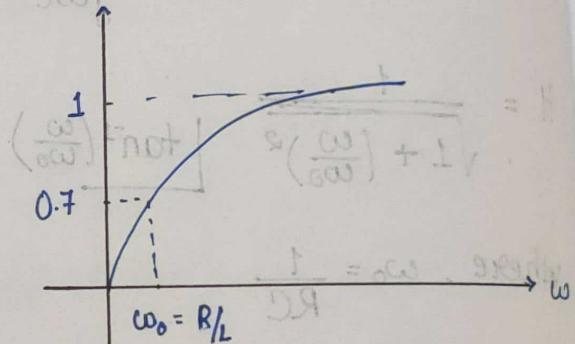

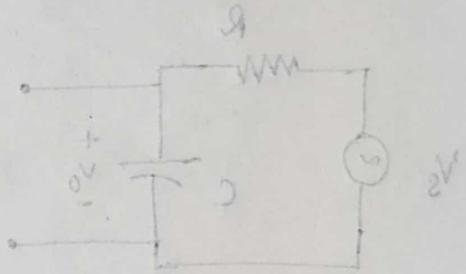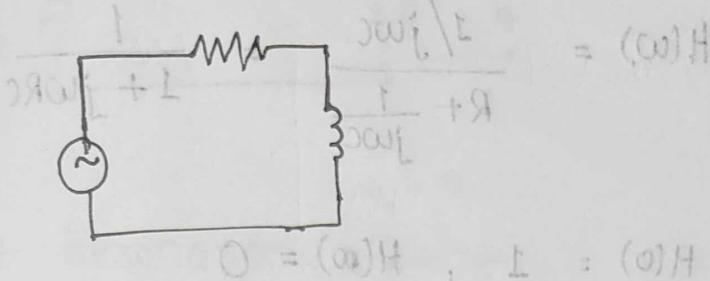Q.1) Transfer functⁿ of R-L ckt. 20/Sept/24




⇒ Passive Filter ⇒


It is a ckt that is designed to pass the signals with desired freq. & attenuate (or Reject) others.

- A filter is a passive filter if it consists of ^{only} passive elements (R, L, C)
- Active filter consists of OP-Amp, transistors, etc.


Q.2) \star) LPE (Low Pass Filter) :-

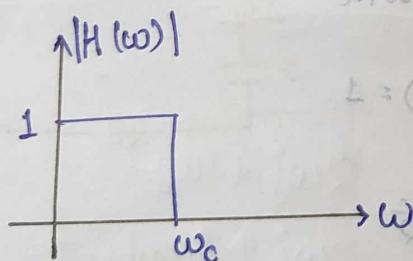

\star) BPF :-

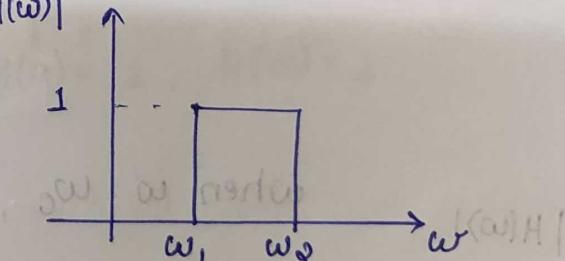


\star) High Pass filter (HPF) :-

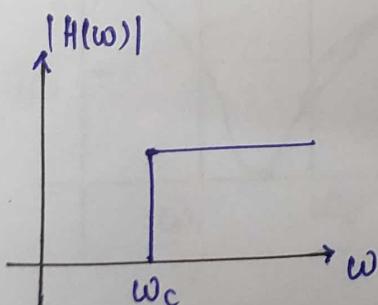


$|H(\omega)|$

BSF
(Band Stop F)
(Notch filter)

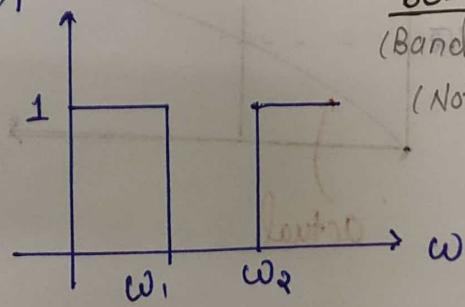

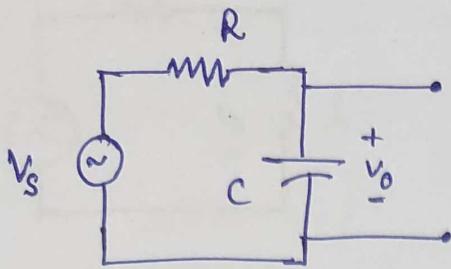
- LPF is formed when the o/p of RC-ckt is taken off the Capacitor




$$H(\omega) = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

$$H(0) = 1, \quad H(\infty) = 0$$

$$|H(\omega)| = \frac{1}{\sqrt{2}}$$

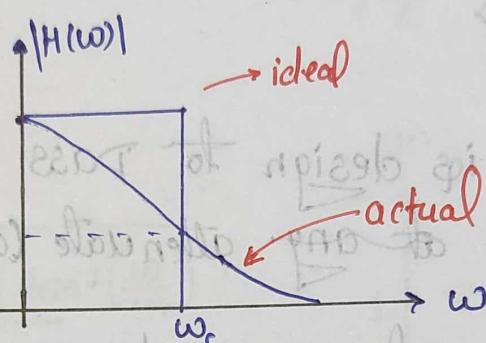

- HPF \Rightarrow

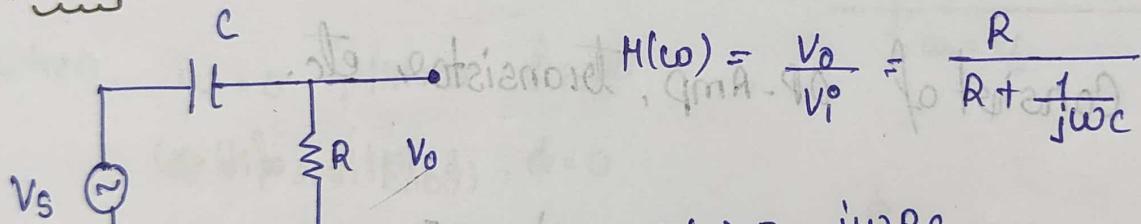


$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$


$$H(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

$$H(0) = 0, \quad H(\infty) = 1$$

$$|H(\omega)| \text{ when } \omega = \omega_c, \quad |H(\omega_c)| = \frac{1}{\sqrt{2}}$$

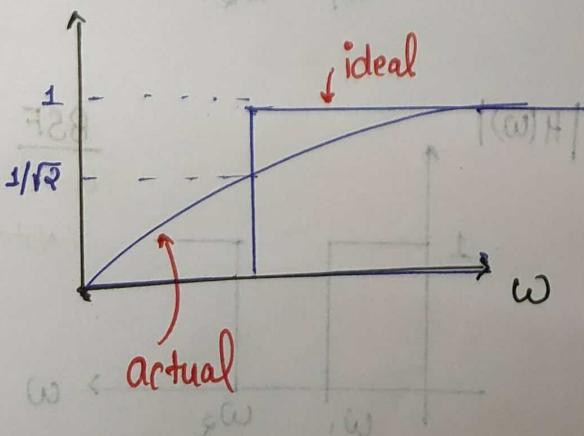

20 Sep/24

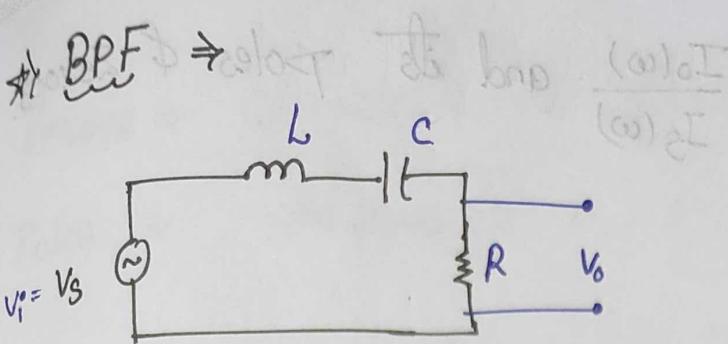

$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}}$$


$$H(0) = 0, H(\infty) = 0$$

$$x_L = x_C$$

At Resonance, $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

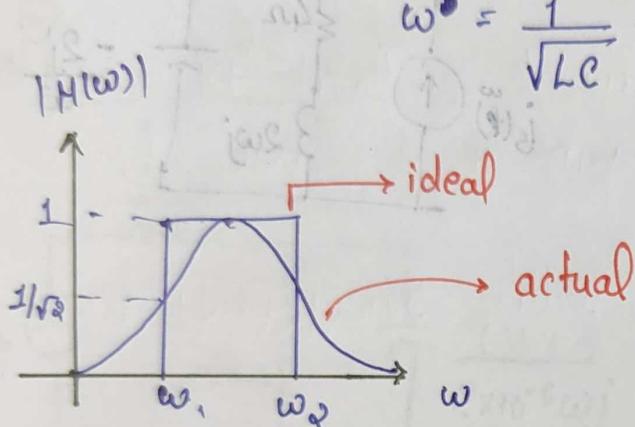

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

* BSF \Rightarrow

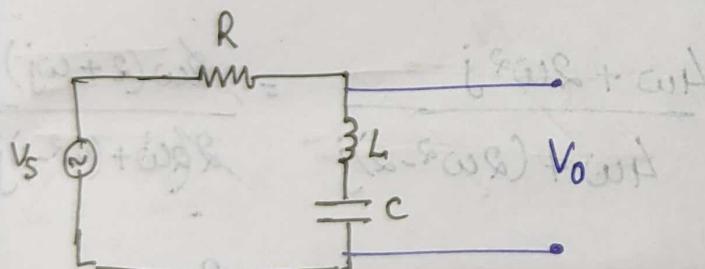

$$H(\omega) = \frac{V_o}{V_i} = \frac{j(\omega L - \frac{1}{\omega C})}{\omega(i\omega R + 1)}$$

$$H(0) = 1, H(\infty) = 1$$

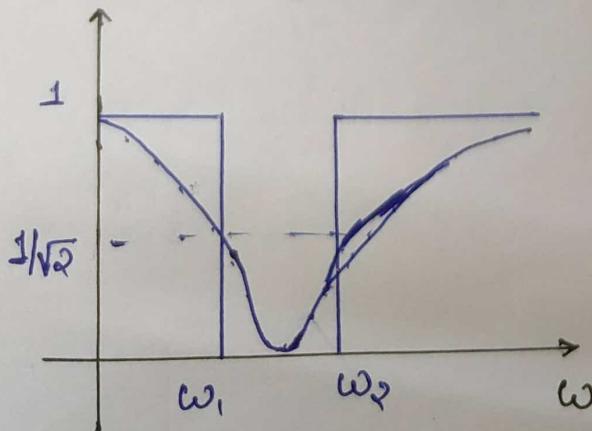


$$\omega = \omega_1 \Leftrightarrow \omega_0 / \sqrt{2}$$

$$\frac{(s+\omega_0)^2}{s^2 + 2s\omega_0 + \omega_0^2} = \frac{(\omega_0 I)^2}{\omega_0^2 L^2}$$


24/sep/24

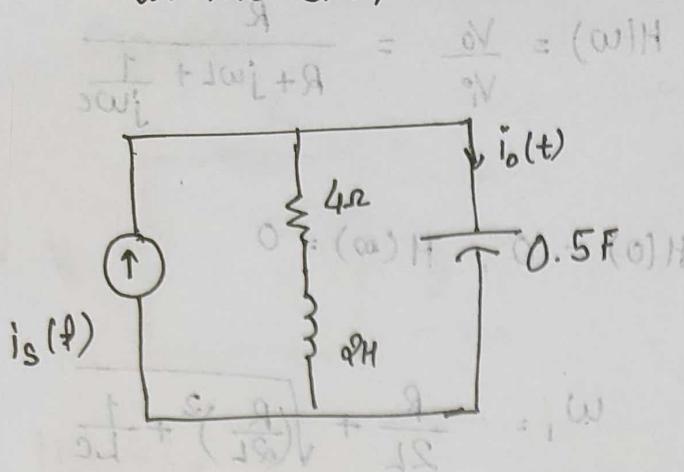Q.1} For the ckt, Calc. the T/F $\frac{I_o(\omega)}{I_s(\omega)}$ and its Poles & Zeros



$$\Rightarrow \frac{1}{X_C} = \frac{1}{j\omega C} + \frac{1}{j\omega L} = X_L = 2\omega j$$
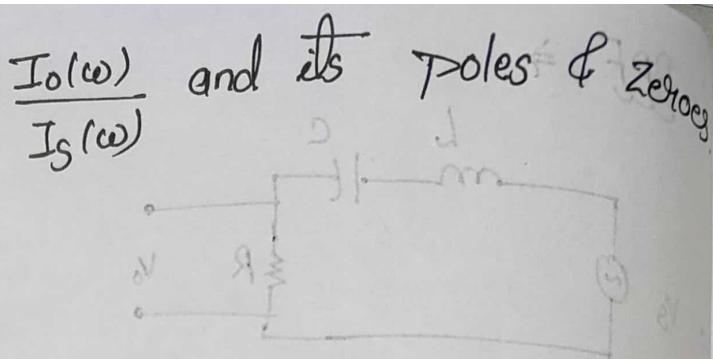
$$= -\frac{j\omega}{\omega} = -\frac{2j}{\omega}$$




$$i_o(\omega) = \left(\frac{4+2\omega j}{4+2\omega j - \frac{2j}{\omega}} \right) \times i_s$$

$$\frac{i_o(\omega)}{i_s(\omega)} = \frac{(4+2\omega j)\omega}{4\omega + 2\omega^2 j} = \frac{4\omega + 2\omega^2 j}{4\omega + (2\omega^2 - 2)j} = \frac{2\omega(2+\omega)}{2\omega + (\omega^2 - 1)}$$

for poles $\Rightarrow 2\omega + (\omega^2 - 1) = 0 \Rightarrow H(\omega) = \frac{2\omega j + (\omega j)^2}{2\omega j + 2(\omega j)^2 + 1}$

Replace $\Rightarrow j\omega = s$
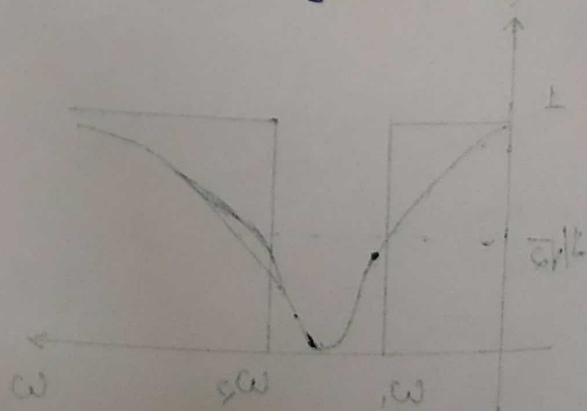
$$\frac{I_o(s)}{I_s} = \frac{s(s+2)}{s^2 + 2s + 1}$$



24/sep/24


$$\text{Zeroes} \Rightarrow s(s+2) = 0 \Rightarrow s = 0, -2$$

$$\text{Poles} \Rightarrow s^2 + 2s + 1 = 0 \Rightarrow s = -1, -1$$

$$1 = |(\omega)H|$$

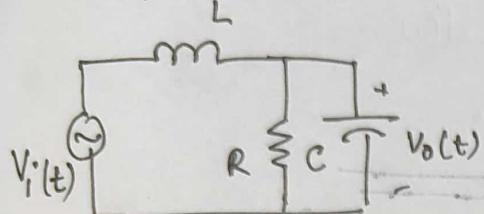Q2) Determine the type of filter, and calculate the corner freq.

Cut-off freq. $R = 2\text{ k}\Omega$, $L = 2\text{ H}$, $C = 2\mu\text{F}$



$$\Rightarrow$$

$$V_o = \frac{Z}{Z + 2\omega j} \times V_i$$

$$V_o = \frac{2 \times 10^3 / (4 \times 10^{-3} \omega j + 1)}{\omega^2 + 4 \times 10^{-3} \omega j + 1} \times V_i$$


$$Z = \frac{2K \left(\frac{1}{2\mu F \omega j} \right)}{2K\omega + \frac{1}{2\mu F \omega j}}$$

$$Z = \frac{2 \times 10^3}{2 \times 10^{-6} \omega j} = \frac{2 \times 10^3}{2 \times 10^3 + \frac{1}{2 \times 10^{-6} \omega j}}$$


$$Z = \frac{2 \times 10^3}{4 \times 10^{-3} \omega j + 1}$$

$$H(\omega) = \frac{V_o}{V_i} = \frac{10^3}{10^3 + 4 \times 10^{-3} (\omega j)^2 + \omega j}$$

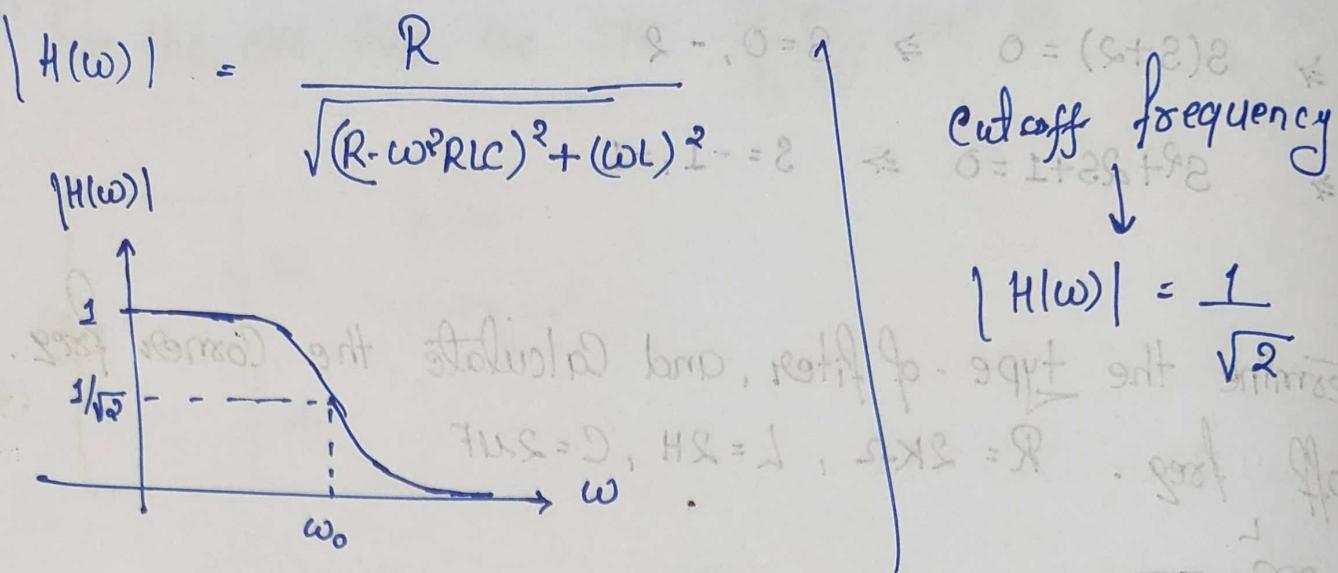
$$\left. \begin{array}{l} \omega = 0 \Rightarrow H(0) = 1 \\ \omega = \infty \Rightarrow H(\infty) = 0 \end{array} \right\} \text{Low Pass filter}$$


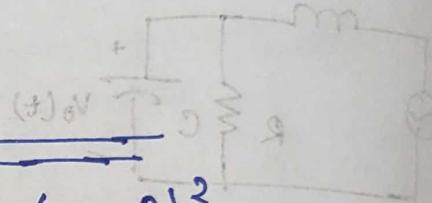
$$\frac{1}{\sqrt{2}} = \frac{2 \times 10^3}{\sqrt{(2 \times 10^{-3} - \omega^2 \times 2 \times 10^3 \times 2 \times 2 \times 10^{-6})^2 + (\omega \times 2)^2}}$$


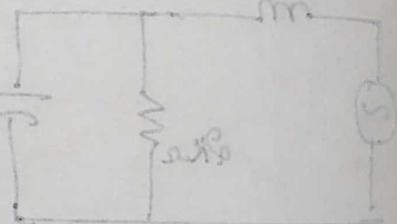
$$(2 \times 10^{-3} - \omega^2 \times 2 \times 10^3 \times 2 \times 2 \times 10^{-6})^2 + 4\omega^2 = \frac{8 \times 10^6}{(\omega^2 \times 2 \times 10^{-3})}$$



$$16\omega_c^4 - 7\omega_c^2 - 1 = 0$$

$$\frac{(j\omega \times 2 \times 10^{-3}) \times 2 \times 10^{-6}}{j\omega^2 \times 2 \times 10^{-3}} = 5$$

$$\omega = 489.52 \text{ rad/sec}$$

$$\omega = 0.742 \text{ K rad/sec}$$

$$= \frac{1}{j\omega^2 \times 2 \times 10^{-3}} \times 8 \times 10^6 = 8$$

$$\omega = 742 \text{ rad/sec}$$


$$\frac{j\omega + 8(j\omega) \times 2 \times 10^{-3} + 8 \times 10^6}{j\omega^2 \times 2 \times 10^{-3}} = \frac{8 \times 10^6}{j\omega^2 \times 2 \times 10^{-3}} = (j\omega)H$$

resonance

$$\left. \begin{array}{l} \omega = 0H \Leftrightarrow \omega = 0 \\ \omega = \infty H \Leftrightarrow \omega = \omega_0 \end{array} \right\}$$

$$\frac{8 \times 10^6}{1 + j\omega \times 2 \times 10^{-3}} = 8$$

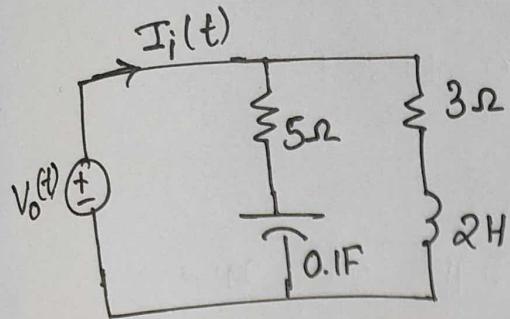Q3) Find $\frac{V_o(\omega)}{I_o(\omega)}$ obtain poles & zeroes.




$$H = \frac{5(s+2)(s+1.5)}{s^2 + 4s + 5}$$

08 Oct 124

Transient Analysis


Statistic Analysis $\Rightarrow t \rightarrow \infty$

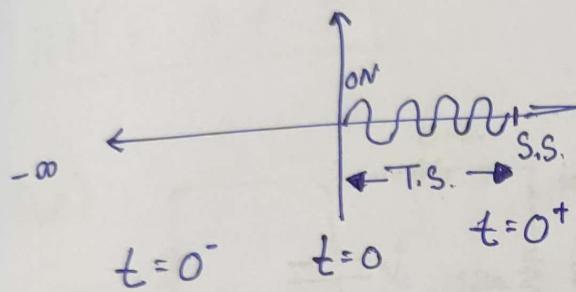T.S. \rightarrow time $t=0$ to $t=t$
 (Switch ON) Steady State




$\hookleftarrow t \rightarrow 0$

$V = (0)V$

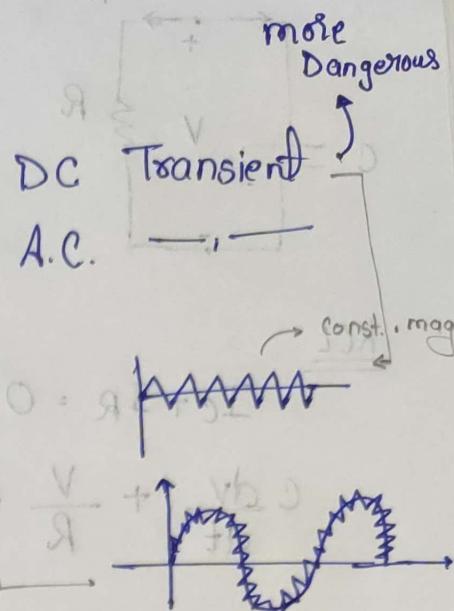


$$V = \frac{V}{R} + \frac{\sqrt{V}}{R} e^{\frac{-t}{RC}}$$



i) source free circuit \rightarrow

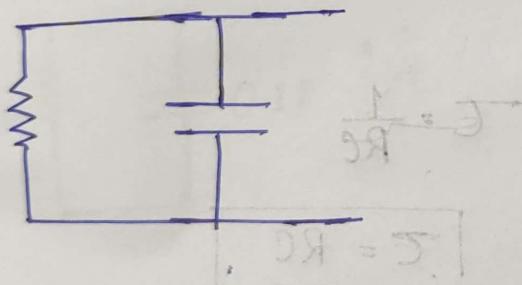

ii) Source Circuit \rightarrow

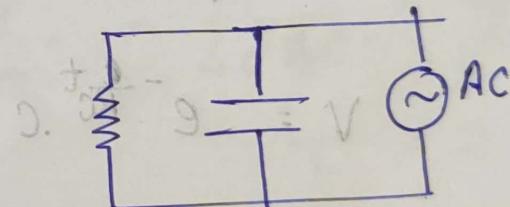


iii) Dependent Source ckt \rightarrow

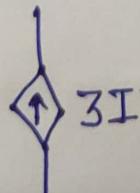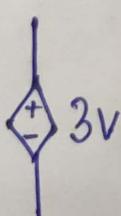

$$3V = V$$

RC source free ckt

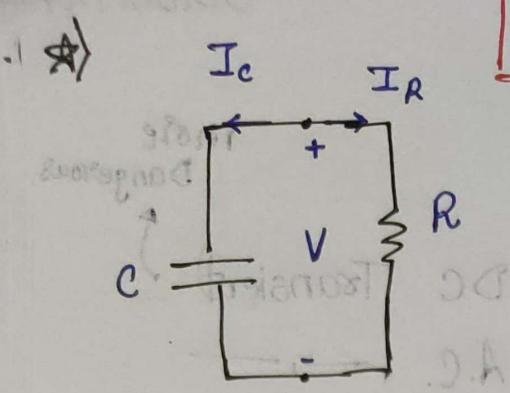

KCL

$$I_C + I_R = 0$$

$$C \frac{dV}{dt} + \frac{V}{R} = 0$$

$$\frac{dV}{dt} + \left(\frac{1}{CR}\right)V = 0$$

$$\text{I.F.} = e^{\int \frac{1}{RC} dt} = e^{\frac{1}{RC} t}$$

$$V \cdot e^{\frac{1}{RC} t} = \int 0 \cdot dt + C$$

$$V = e^{-\frac{1}{RC} t} \cdot C$$



$$V(t) = A e^{-t/\tau}$$

$$V = A \cdot e^{-t/\tau}$$


$$V = V_0 e^{-t/\tau}$$

$$\tau = \frac{1}{RC}$$

$$\tau = RC$$

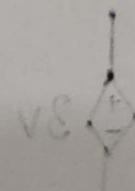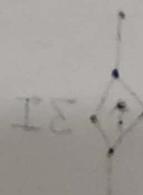

for RL

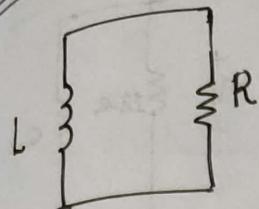


$$H(t) = A \cdot e^{-\frac{Lt}{R}}$$


$$\tau = \frac{L}{R} \quad \tau = \frac{R}{L} \cdot \frac{L}{R}$$

$$i(t) = A \cdot e^{-t/\tau}$$

Ques.

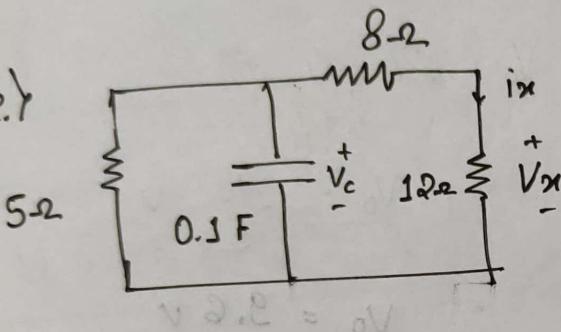

\Rightarrow

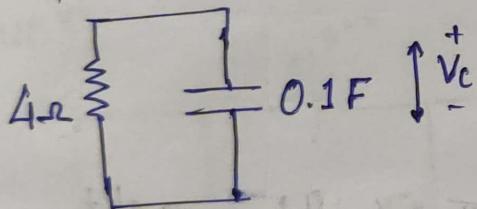

$$V(t) = V_0 e^{-t/\tau}$$

$$V(t) = 15 e^{-2.5t}$$

* Time & Const. \Rightarrow

$$T.C. \Rightarrow C = \frac{1}{F} \quad \frac{1}{F} = C$$

$$\tau = \frac{1}{RC_{eq}} = \frac{1}{4}$$

$$C = \frac{1}{F} \quad F = \frac{1}{C} \quad R = \frac{2}{F} \Rightarrow$$

$$C_{eq} = \frac{1 \times 1}{1+1} = \frac{1}{2} F$$

$$\tau = \frac{1}{RC_{eq}} = \frac{1}{R \cdot \frac{1}{2}} = \frac{1}{\frac{R}{2}}$$

$$R = 5 \Omega$$


$$V_C(0) = 15V$$

find V_C, V_X, i_X

$$\tau = \frac{1}{R_{eq} C} = \frac{1}{4 \times 0.1} = \frac{5}{2}$$

$$\tau = 2.5 \text{ sec}^{-1}$$



$$i_X = \frac{V_X}{12}, \quad V_X = ?$$

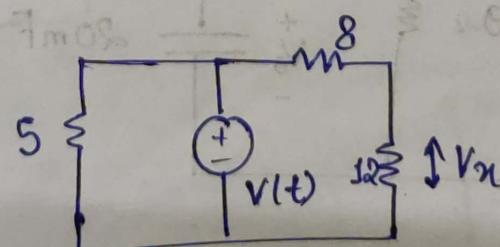

$$V_X = \frac{V(t) \times 12}{20}$$

10 OCT 24

Q.1)

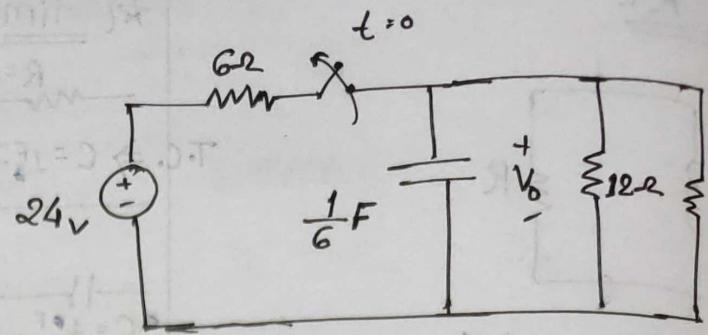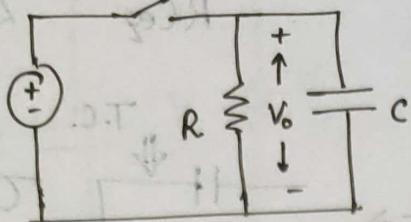

$$V_C = V_0 e^{-t/\tau}$$

$$V_C = 9.6 e^{-t/\tau}$$


$$t \geq 0$$

$$\tau = RC$$

$$\tau = R_{eq}C$$

$$R_{eq} = 4$$
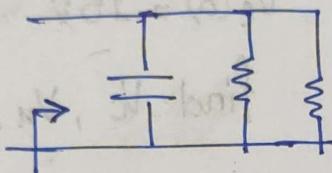
$$\tau = 4 \times \frac{1}{6} = \frac{2}{3}$$



+ DC Source

$$X_C = \infty \Omega$$


$$V_0 = \frac{24 \times 4}{6+4}$$

$$V_0 = \frac{48}{10} V$$

$$V_0 = 9.6 V$$

$$\checkmark V_C = 9.6 e^{-\frac{3t}{2}} \quad \text{Ans}$$

Que.2)

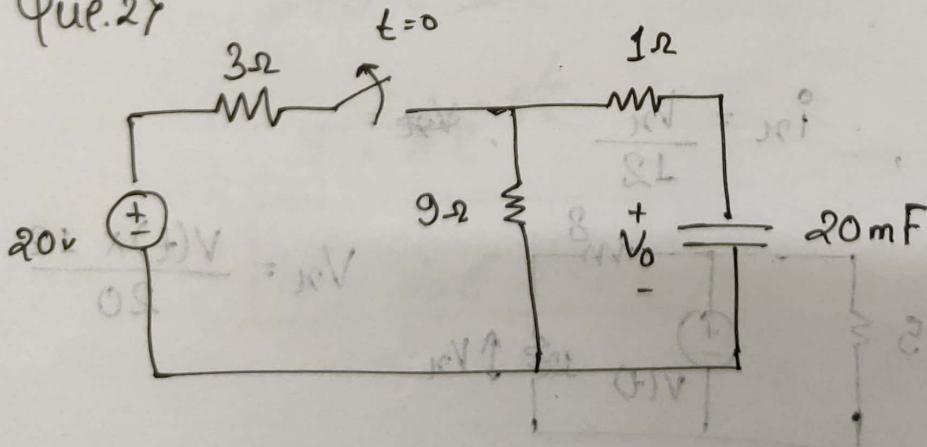

The switch in a ckt has been close for long time at $t=0$

Switch is open.

Find V_t at $t \geq 0$.

& calculate initial Energy.

DC source

$$X_C = \infty$$

$$V_0 = \frac{20 \times 9}{12}$$

$$V_0 = 15V$$

$$V_t = V_0 e^{-t/\tau}$$

$$\tau = R_{eq} C$$


$$R_{eq} = \frac{9 \times 1}{9+1} = \frac{9}{10}$$

$$\tau = \frac{9}{10} \times 20 \times 10^{-3}$$

$$\tau = 18 \times 10^{-3}$$

$$V_t = 15 e^{-\frac{10^3 t}{18}}$$

For R_{eq}

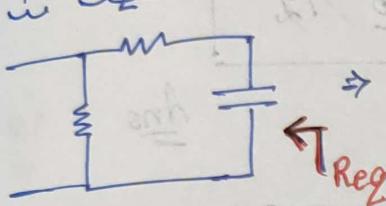

$$R_{eq} = 10$$



$$\tau = R_{eq} C$$

$$= 10 \times 20 \times 10^{-3}$$

$$\tau = \frac{2}{10}$$


$$V_t = 15 \cdot e^{-\frac{10t}{2}} \text{ Ans}$$



Que.3)

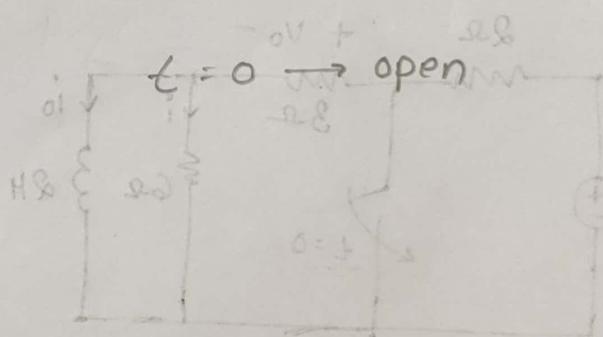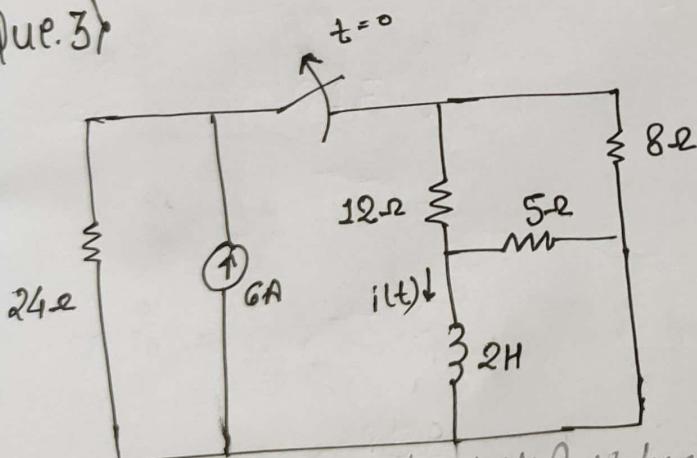

for initial value

DC Source
 $X_L = 0$

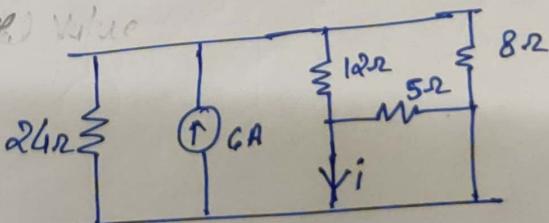

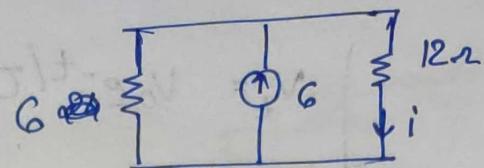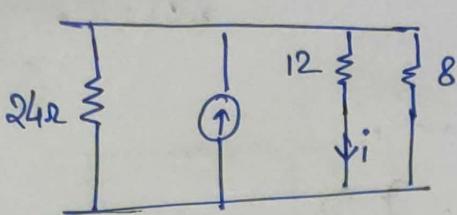


$$i = 6 \times \frac{6}{6+12} = 2 \text{ Amp}$$

$$i = i_0 e^{-t/\tau}$$

$$\tau = \frac{R_{eq}}{\frac{L}{R_{eq}}} \quad t=0 \text{ (open switch)}$$

for R_{eq}

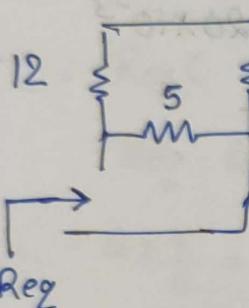

$$R_{eq} = 5 // 20 =$$

$$R_{eq} = 4$$

$$\tau = \frac{4}{2} = 2$$

$$\tau = \frac{2}{4} = 0.5$$




$$i(t) = 2e^{-t/2}$$

Ans

$$i(t) = 2e^{-2t}$$

Ans

Q.4)

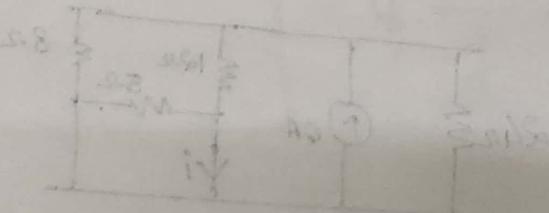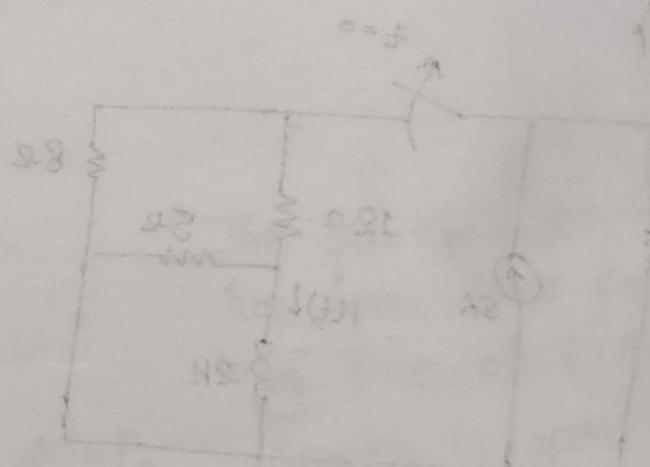
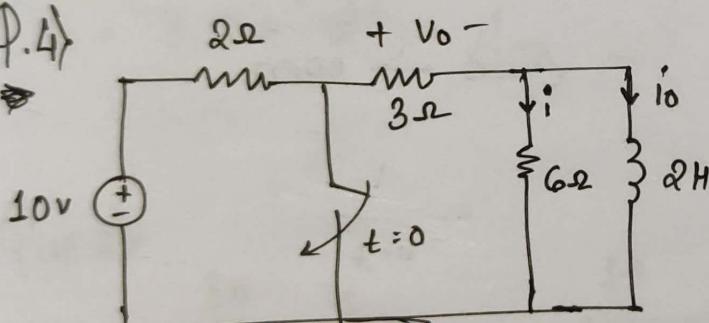


DC Po ar cis


$i = 0$

11 Oct 124

Q1)

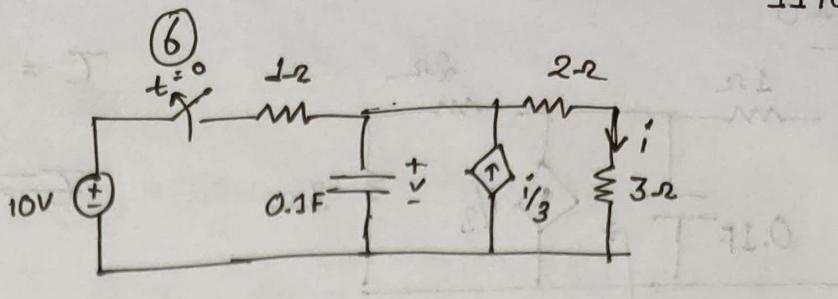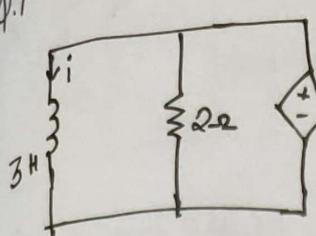

C)

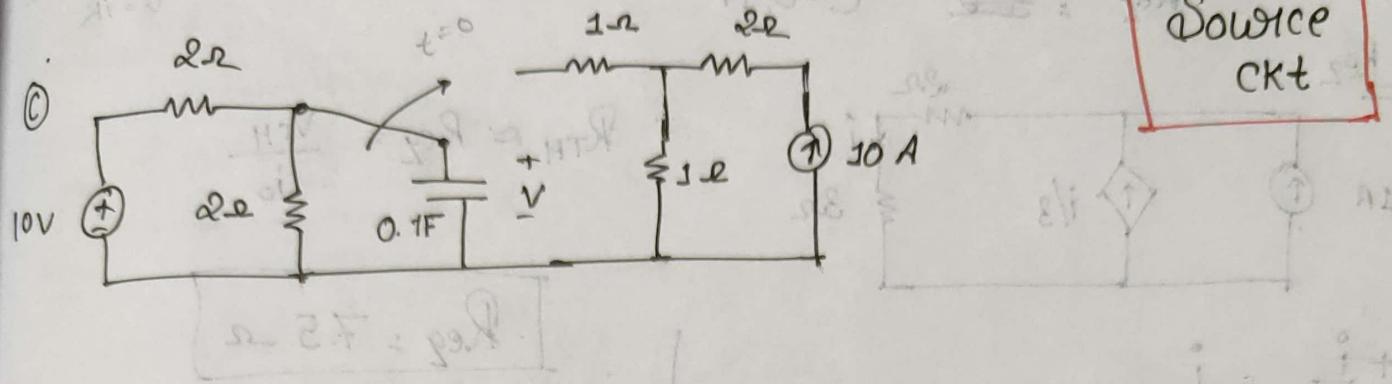


b)

$t=0 \rightarrow$ Switch open \rightarrow T.S.
 $t < 0 \rightarrow$ --, close \rightarrow S.S.

$$A.C.L = \frac{\epsilon}{R} = \frac{i}{\frac{1}{C}} = i$$

For initial Value $\xrightarrow{i_0}$

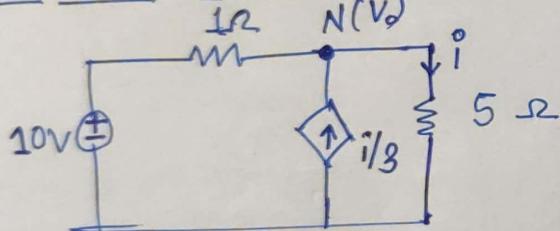

$$i_0 = \frac{V_0}{5}$$

$$i_0 = \frac{150}{5 \times 17} = 1.765 \text{ Amp}$$

$$\frac{V-10}{1} + \left(-\frac{i}{3}\right) + \frac{V_0}{5} = 0$$


$$V-10 - \frac{V_0}{15} + \frac{V_0}{5} = 0$$

$$\frac{17}{15} V_0 = 10$$

$$V_0 = \frac{150}{17}$$

$$V_0 = 8.824$$

for $t \geq 0$

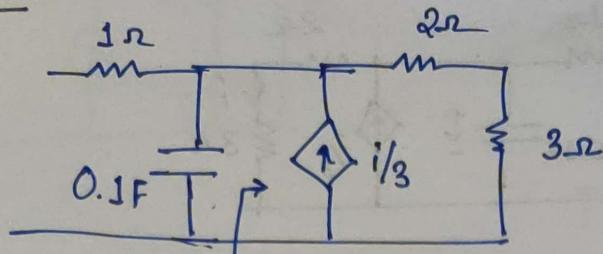


$$\tau = R_{eq} C$$

$$\tau = 0.5$$

$$R_{eq} = 5 \Omega \quad C = 0.1 F$$

$$V = iR$$

For R_{eq}

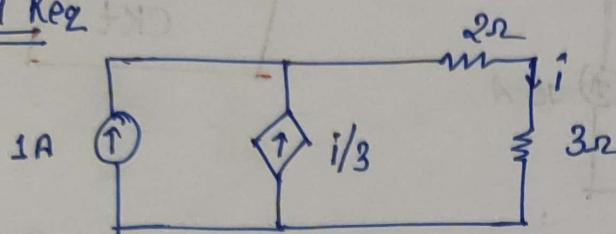

$$R_{TH} \approx R_{eq} = \frac{V_{TH}}{i_0}$$

$$R_{eq} = 7.5 \Omega$$

$$1 + \frac{i}{3} = i$$

$$i = \frac{1}{1 - \frac{1}{3}} = \frac{3}{2} = 1.5 A$$

$$V_{TH} = 3 \times i$$


$$V_{TH} = 7.5 \Omega$$

$$\tau = R_{eq} C$$


$$\tau = 0.75$$

$$V(t) = V_0 e^{-t/\tau}$$

$$V(t) = 8.824 e^{-t/0.75}$$

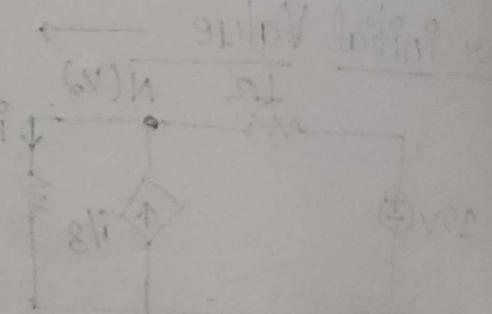

11/0ct/24

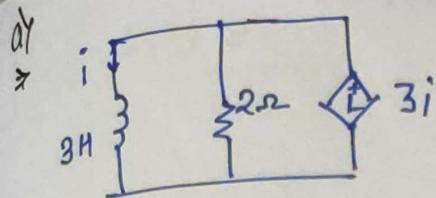


36

Initial Value Method

for initial value \rightarrow

For Req

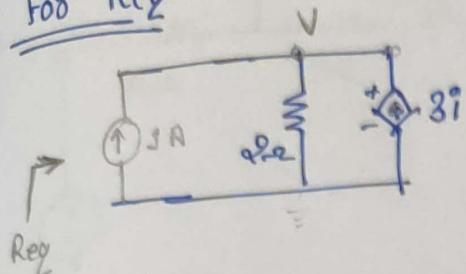


Req

$$-3 + \frac{V - 3i}{2} = 0$$

$$i = \frac{V}{3}$$

$$V = 3i = 2$$

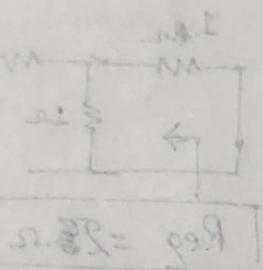

$$i_0 = 1A$$

$$Req = \frac{V}{I_0} = 2\Omega$$

$$i_0 = 1A$$


$$\tau = \frac{3}{2}$$

$$RC = C$$


$$2.0 = 3$$

$$72.0 = 0$$

Req $(0 = ?)$

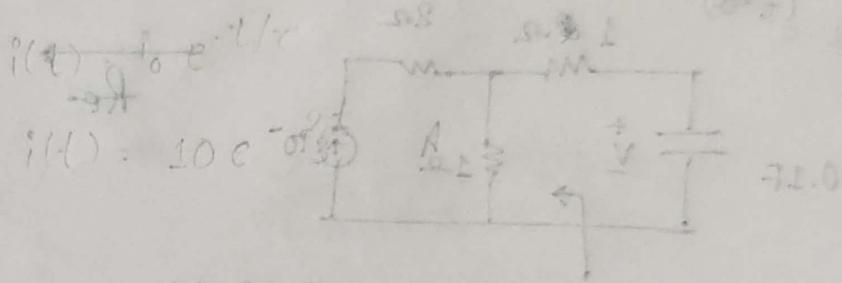

c) for $V(\infty) \Rightarrow$

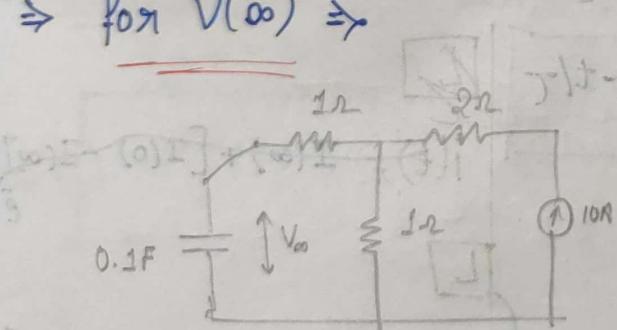

$$12 - 3.2 = (\pm)V \Rightarrow (\pm)V$$

$$8.0 - 9.2 = (\pm)V$$


v

$$8.0 - 9.2 = (\pm)V$$

$$9.2 - 9.2 = (\pm)V$$

$$9.2 - 9.2 = (\pm)V$$
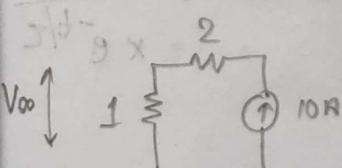
$$[(\infty)i - 12] + (\infty)i = (\pm)i$$





$$V_{\infty} = 10V$$

$$9.2 - (0.1 - 2) + 0.1 = (\pm)V$$

$$9.2 - 9.2 - 0.1 = (\pm)V$$


C) \rightarrow for $V_0 \rightarrow$

for initial value

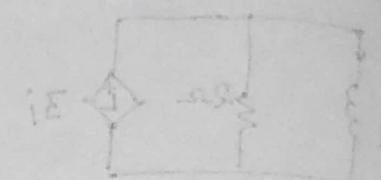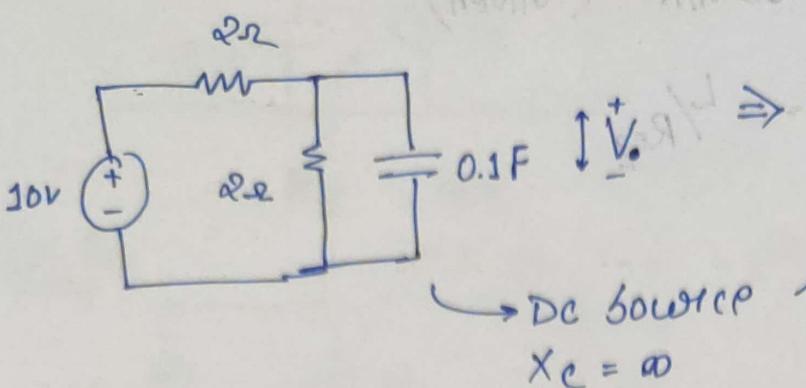


$$V_0 = 5V$$

for $R_{eq} \rightarrow$

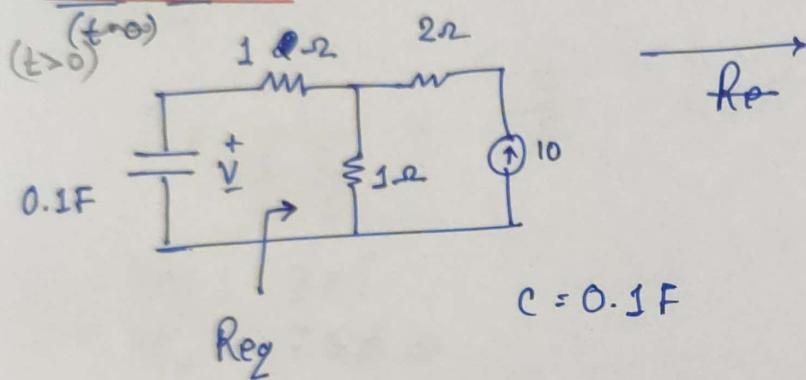

$$C = 0.1F$$

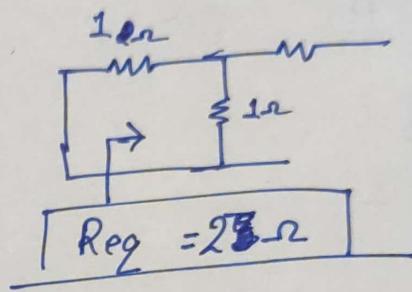

$$R_{eq} = 2\Omega$$

$$\tau = RC$$

$$\tau = 0.2$$

$$V(t) = V_0 e^{-t/\tau}$$

$$V(t) = 5e^{-t/0.2} V$$

$$V(t) = 5e^{-5t} V$$

C

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$

L

$$i(t) = I(\infty) + [I(0) - I(\infty)] e^{-t/\tau}$$

After S.S.

Before S.



$$V(t) = 10 + (5 - 10) e^{-5t}$$

$$V(t) = 10 - 5e^{-5t} V$$

L

$$i(t) = I(\infty) + [I(0) - I(\infty)] e^{-t/\tau}$$
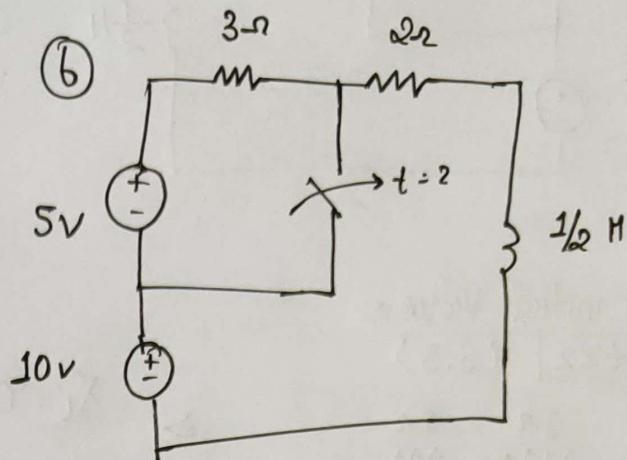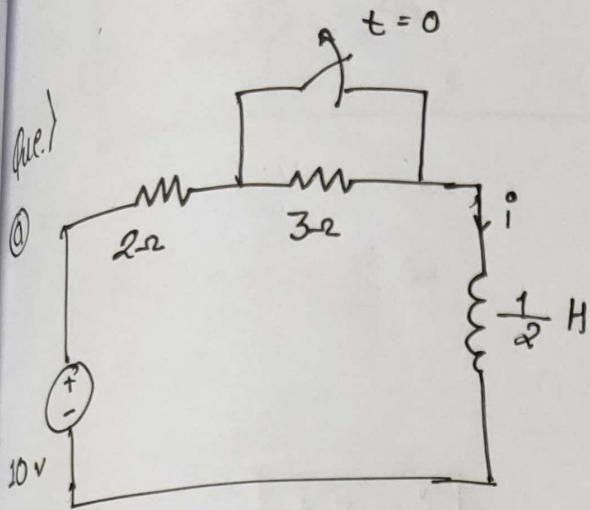
$$i(t) = I(\infty) + [I(0) - I(\infty)] e^{-t/\tau}$$



$\frac{t < 0}{2}$

$X_L = 0 \quad (\text{DC source})$

$i_0 = \frac{10}{2} = 5 \text{ A}$

$i(0) = 5 \text{ A}$

$\frac{\text{for Reg}}{} \quad (t > 0) \quad (\text{T.S.})$

$Req = 5 \Omega$

$\frac{\text{for } i(\infty)}{2\Omega \text{--} 3\Omega}$

$i(\infty) = \frac{10}{5} = 2 \text{ A}$

$i(\infty) = 2 \text{ A}$


$$\tau = \frac{L}{Req}$$

$$\tau = \frac{1}{2 \times 5} = \frac{1}{10}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$


$$i(t) = 2 + (5 - 2) e^{-t/10} \Rightarrow i(t) = 2 + 3 e^{-10t} \text{ A}$$

6

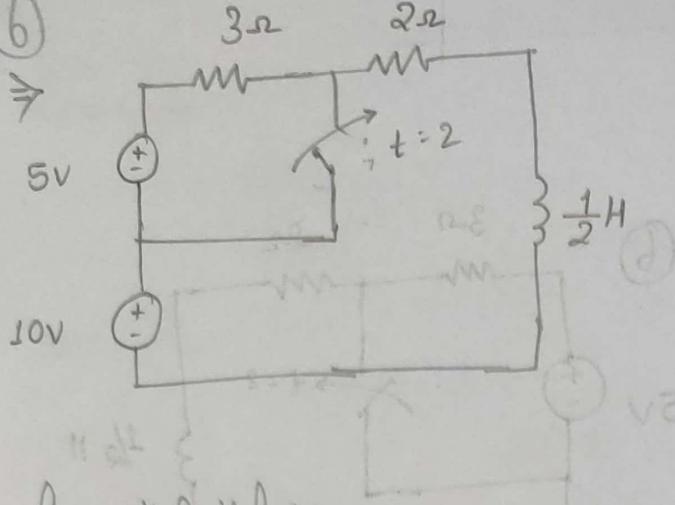


for initial value \Rightarrow

$$t < 2 \text{ (S.S.)}$$

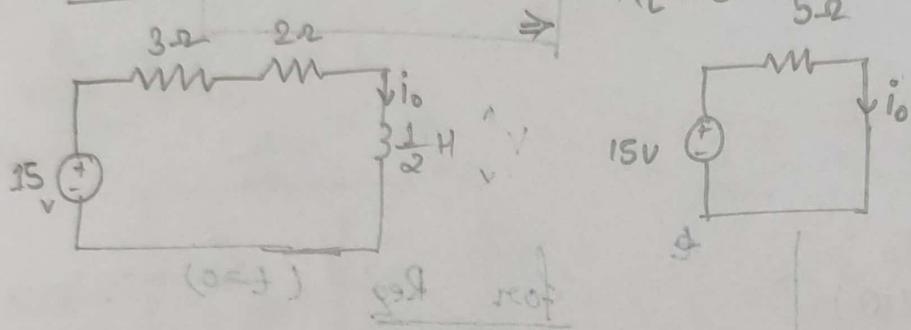


$$X_L = 0$$

$$5\Omega$$

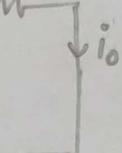


$$i_0 = 3A$$

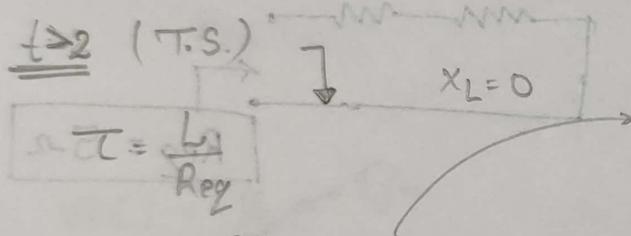

$$A_2 = \frac{O_L}{S} = j$$

$$A_2 = (j)i$$

$$R_{eq} = 2\Omega$$

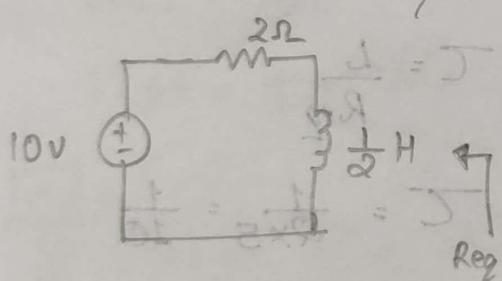


$$\frac{1}{C} = \frac{1}{(0.2)} = \frac{1}{4}$$

$$i(t) = i_0 e^{-\frac{t}{C}}$$

$$i(t) = 3 e^{-4t}$$

$$t = 0$$

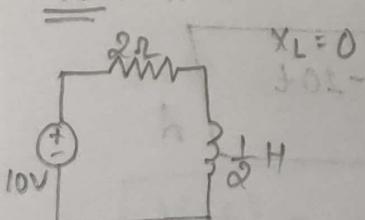

$$i(\infty) = 5A$$







$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-\frac{(t-2)}{C}}$$

$$= (5) + [3 - 5] (e^{-\frac{4(t-2)}{4}})$$







$$i(t) = 5 - 2 e^{-4(t-2)} A$$

15 Oct 24


No initial value →
 $I_0(0)$ or $V_0(0)$

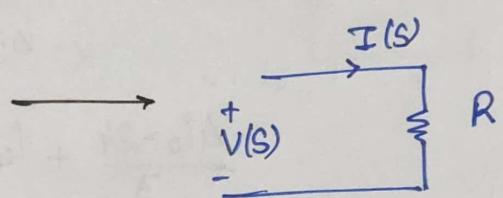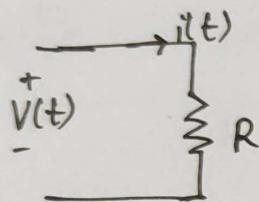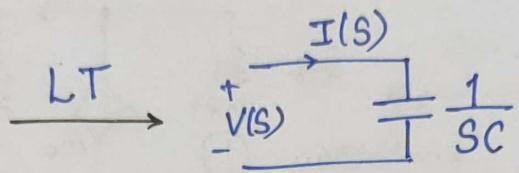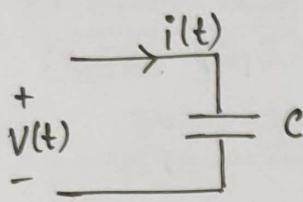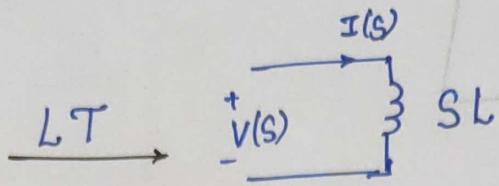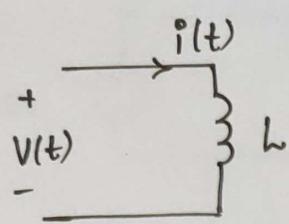

With $I_0(0)$ or $V_0(0)$ →

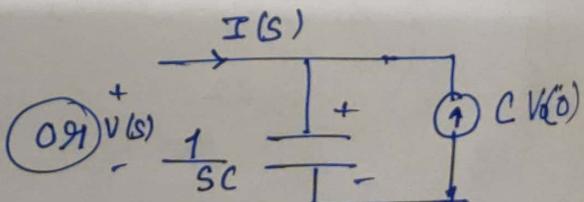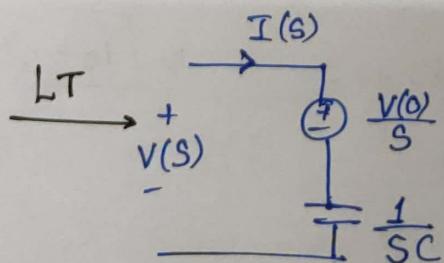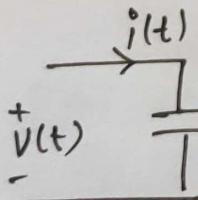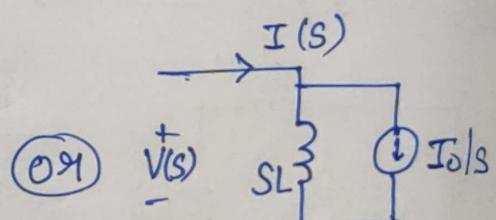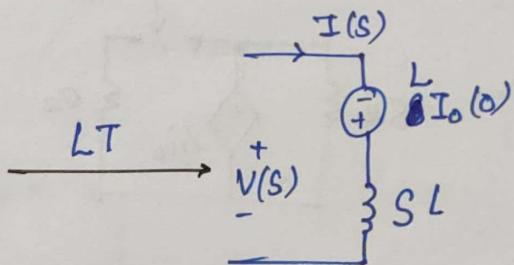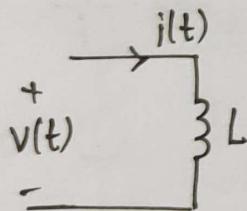


Ques)

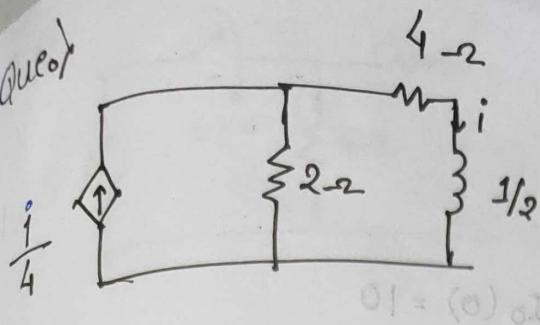


$$I(0) = 10, \text{ find } i(t) = ?$$

KO
15 Oct 24

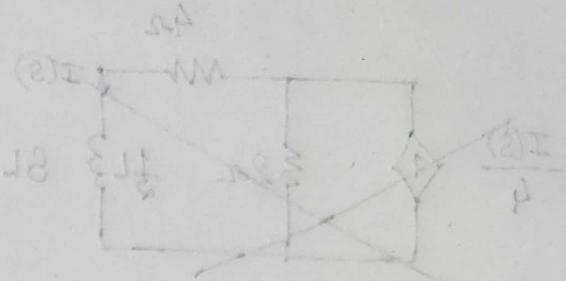

$$\tau = \frac{L}{R_{\text{eq}}}$$

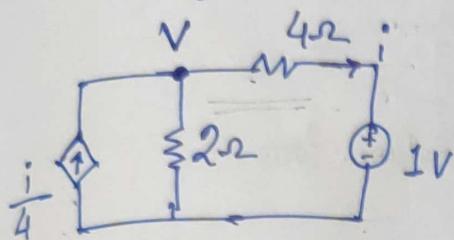

Nodal Analysis \rightarrow

$$-\frac{i}{4} + \frac{V}{2} + \frac{V-1}{4} = 0 \quad | \quad V = 4i + 1$$

$$-\frac{i}{4} + \frac{4i+1}{4} + \frac{4i}{4} = 0$$

$$R_{\text{eq}} = \frac{1}{i_{\infty}} = \frac{1}{\frac{7}{11}} = \frac{11}{7} \Omega$$

$$R_{\text{eq}} = 7 \Omega$$

$$I = \frac{V}{R_{\text{eq}}} = \frac{11}{7} \text{ A}$$

$$\tau = \frac{1}{14}$$

$t = \infty$

$$\tau = \frac{L}{R} = \frac{1}{11}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$


$$i(0) = \frac{8 \times 2}{2+11} = \frac{16}{13} = I$$

$$i(t) = 10 e^{-\frac{11t}{14}}$$



$$i(t) = 10 e^{-\frac{11t}{14}}$$

$$-\frac{1}{4} + \frac{1}{2} \left[10 e^{-\frac{11t}{14}} - 10 \right] = I$$

By frequency domain

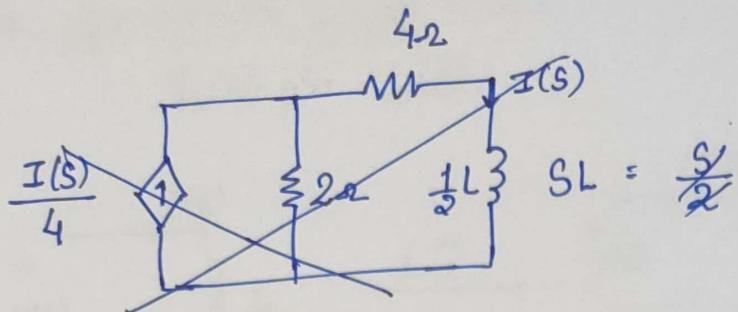

$$I_0(0) = 10$$

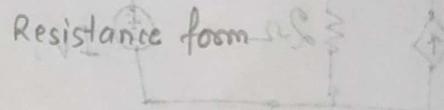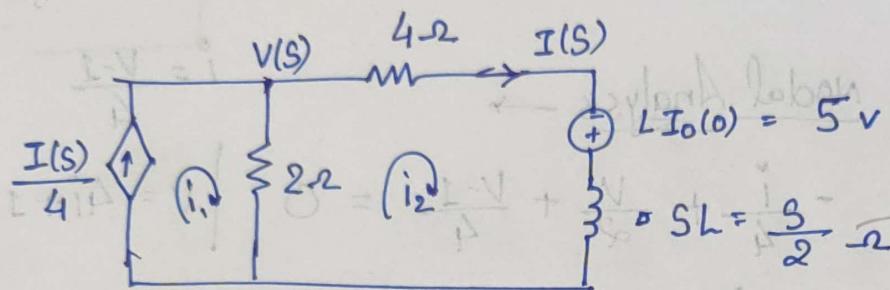

$$i_1 = \frac{I(s)}{4}, \quad -2(I(s) i_2 - i_1) - 4(i_2) + 5 - \frac{S}{2} i_2 = 0$$

$$-2\left(I(s) - \frac{I}{4}\right) - 4I + 5 - \frac{S}{2}I = 0$$

$$-2 \times \frac{3I}{4} - 4I + 5 - \frac{S}{2}I = 0$$



$$\left(\frac{S}{2} + 4 + \frac{3}{2}\right) I = 5$$

$$I = \frac{5 \times 2}{11 + S} = \frac{10}{11 + S}$$

$$\frac{1}{S-a} = e^{at}$$



$$I = 10 \times \frac{1}{S - (-11)}$$

$$I(t) = 10e^{-11t}$$

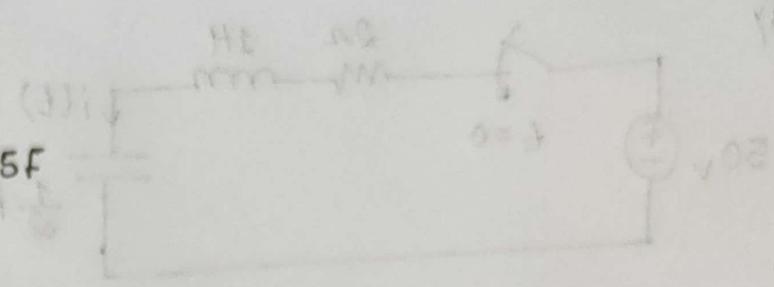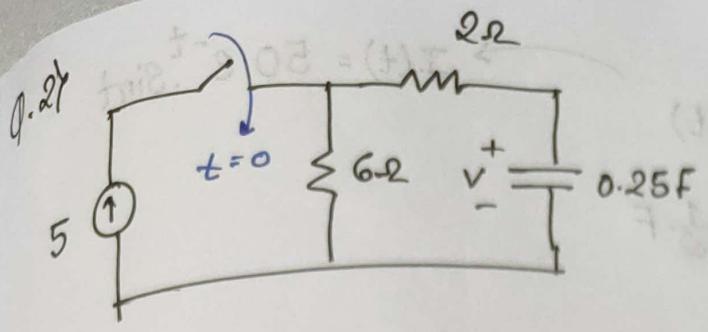



7

18.0

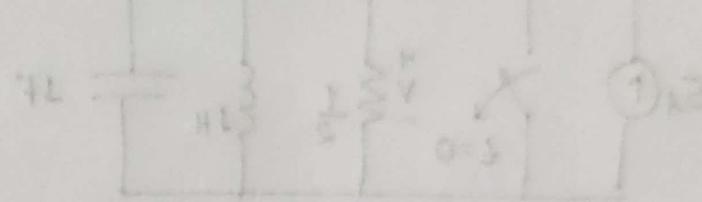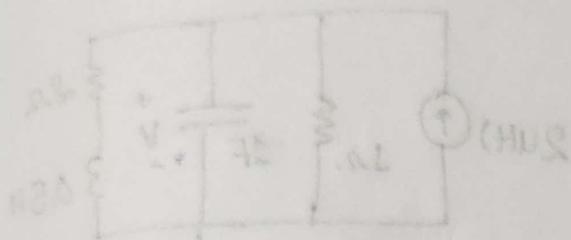


$$E_{18.0} + \frac{1}{2}I_1 2\Omega - (1)V \frac{1}{2} = (1)V$$



$$(1)V^2 - 332 = (1)V$$

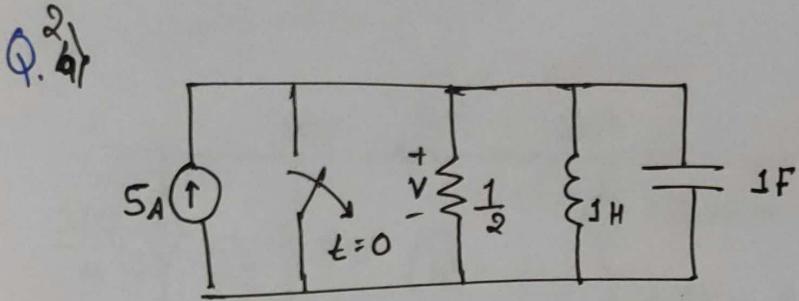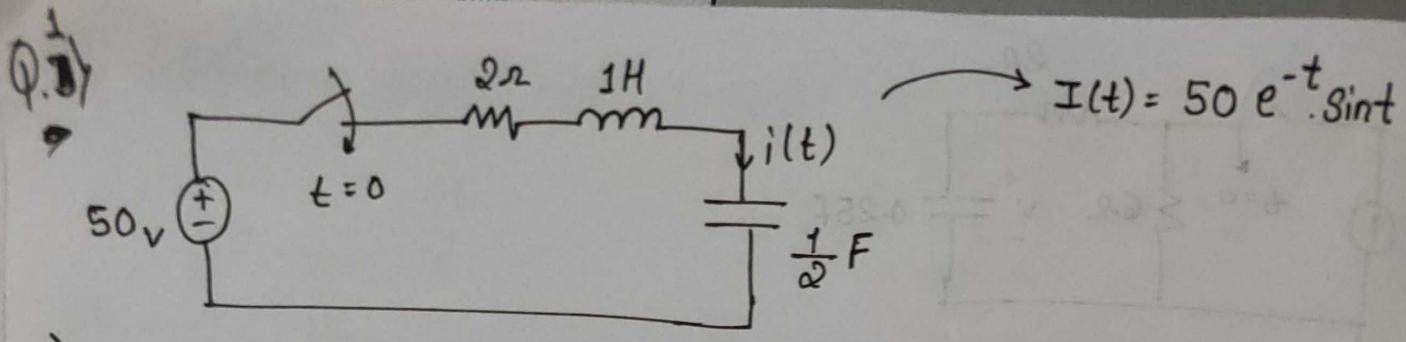


$$v(t) = 5t e^{-t} u(t)$$

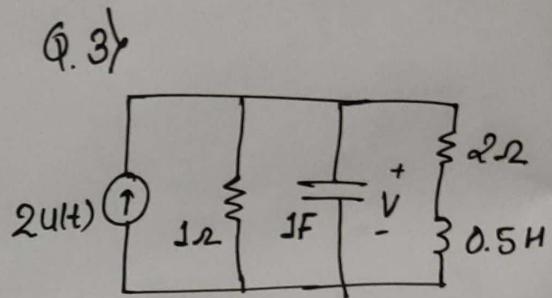

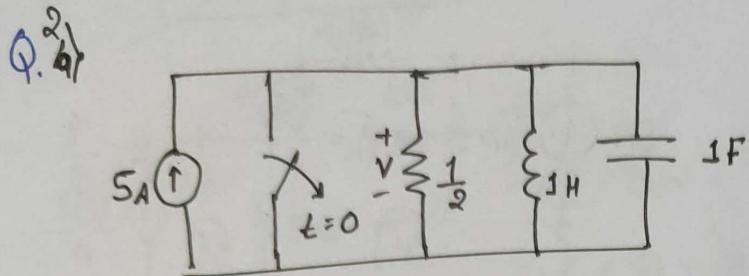
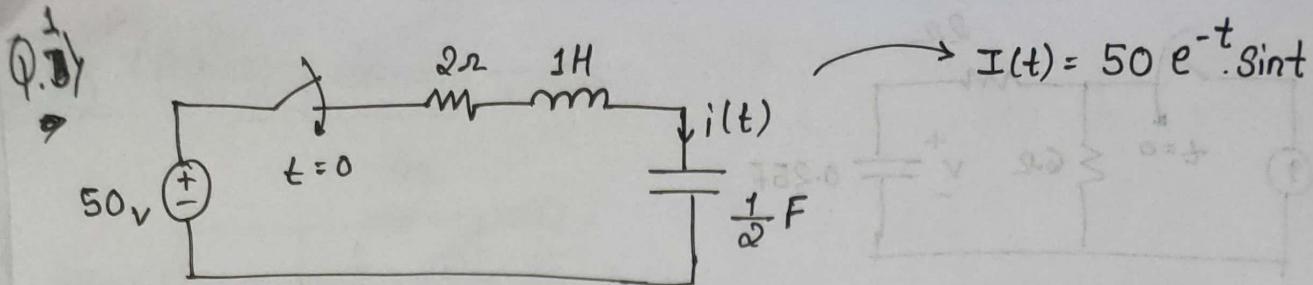
$$v(t) = \frac{4}{3} u(t) - 2e^{-2t} + \frac{2}{3} e^{-3t}$$



$$V(t) = 5t e^{-t} u(t)$$

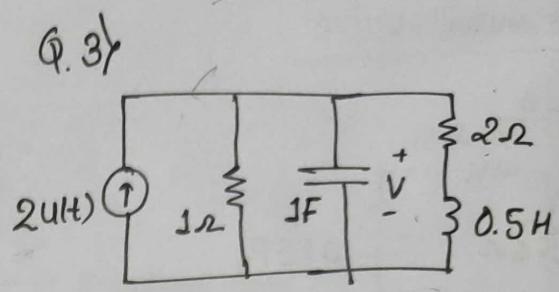
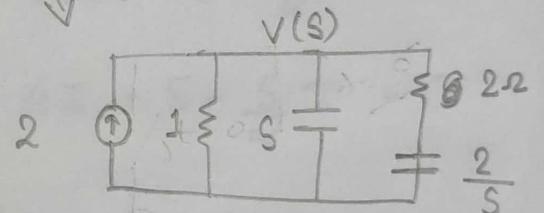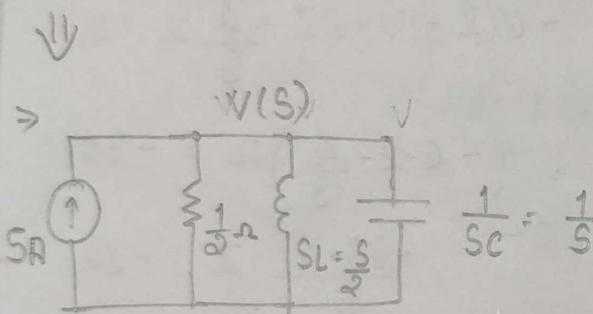
$$V(t) = \frac{4}{3} u(t) - 2e^{-2t} + \frac{2}{3} e^{-3t}$$



$$-2 + V(s) + \frac{V(s)}{S} + \frac{V(s)}{2 + \frac{2}{S}} = 0$$


$$\left(1 + \frac{1}{5} + \frac{S}{2S+2}\right) V(s) = 2$$

$$-5 + 2V(s) + \frac{2V(s)}{S} + 3V(s) = 0$$

$$\left(2 + \frac{2}{S} + S\right) V(s) = 5$$

$$V(s) = \frac{5}{(S+2) + \frac{2}{S}}$$


$$V(s) = \frac{5S}{S^2 + 2S + 2}$$

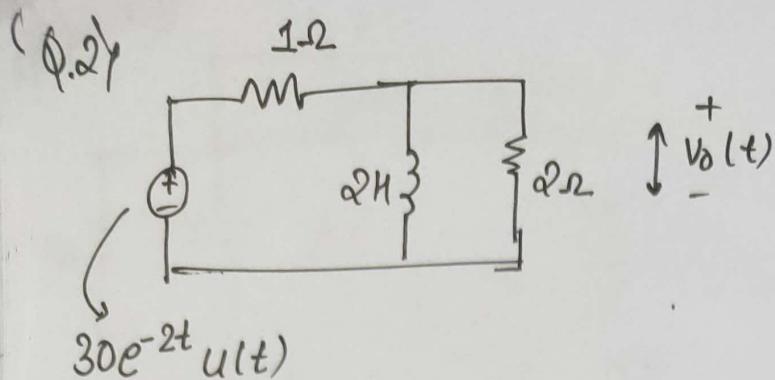

$$v_o(t) = ?$$

$$i_{\text{cap}}(0) = 0$$

⇒ frequency domain →

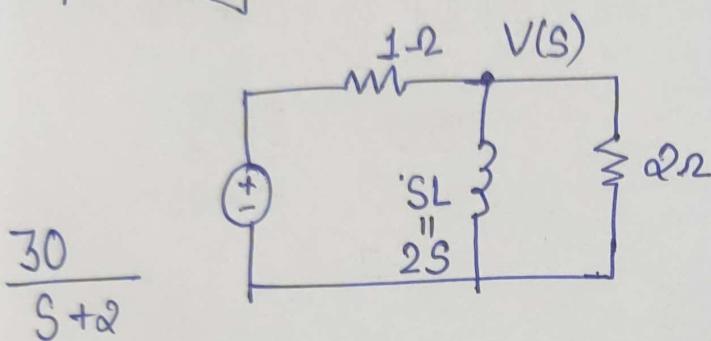

Nodal Analysis

$$\frac{V(s) - 30}{s+2} + \frac{V(s)}{2s} + \frac{V(s)}{\omega}$$

$$\left(1 + \frac{1}{2s} + \frac{1}{\omega}\right) V(s) = \frac{30}{s+2}$$

$$\frac{V(s)}{2(s+1)} = \frac{30}{s+2}$$

$$\left(\frac{3}{\omega} + \frac{1}{2s}\right) V(s) = \frac{30}{s+2}$$

$$\longleftrightarrow V(s) = \frac{60s}{(s+2)(3s+1)}$$

$$\frac{s}{(s+2)(s+1/3)} = \frac{A}{s+2} + \frac{B}{s+1/3}$$

$$V(s) = \frac{20s}{(s+2)(s+1/3)}$$

$$s = A(s + \frac{1}{3}) + B(s+2)$$

$$s = (A+B)s + \frac{A}{3} + 2B$$

$$A+B=1, \quad \frac{A}{3}+2B=0 \Rightarrow B = -\frac{A}{6}$$

$$A - \frac{A}{6} = 1$$

$$A = \frac{6}{5}$$


$$B = -\frac{1}{5}$$

$$\frac{S}{(S+2)(S+3)} = \frac{6}{5(S+2)} + \frac{-1}{5(S+3)}$$

16/10/24


$$V(t) = 20 \left[\frac{6}{5} e^{-2t} - \frac{1}{5} e^{-t/3} \right]$$
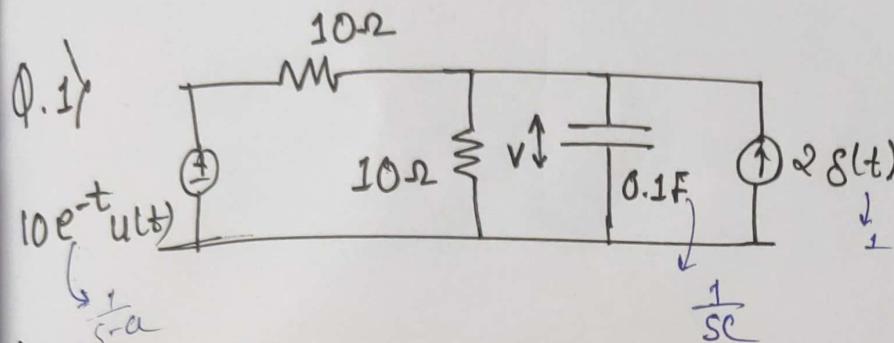
$$\checkmark V(t) = (24e^{-2t} - 4e^{-t/3}) u(t) \quad \underline{\text{Ans}}$$



$$V_o(0) = 5v$$

find $V(t) = ?$

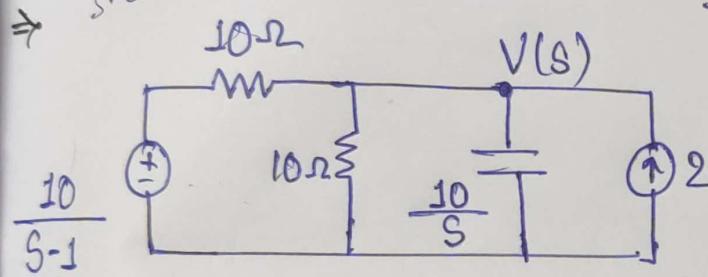


$$\frac{V(s) - \frac{10}{s-1}}{10} + \frac{V(s)}{10} + \frac{sV(s)}{10} - 2 = 0$$

$$\text{Hence } (1+1+s)V(s) - \frac{10}{s-1} = 20$$

$$(2+s)V(s) = 20 + \frac{10}{s-1}$$


$$V(s) = \frac{20s-10}{(s-1)(s+2)} = \frac{10(2s-1)}{(s-1)(s+2)}$$
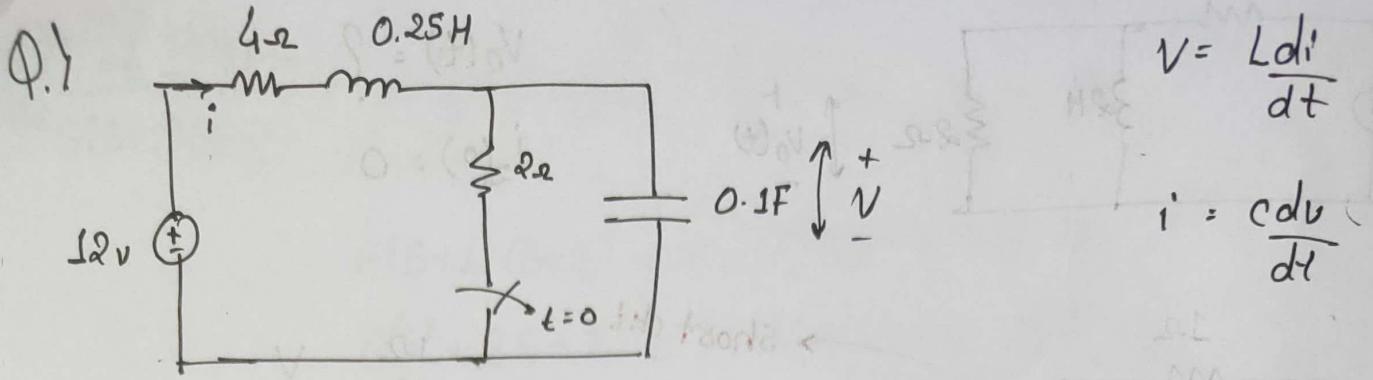
$$V(t) = \frac{10}{3}e^t + \frac{50}{3}e^{-2t} \quad \underline{\text{Ans}}$$



S.S. {
 (a) $i(0^+), V(0^+)$
 (b) $i(\infty), V(\infty)$

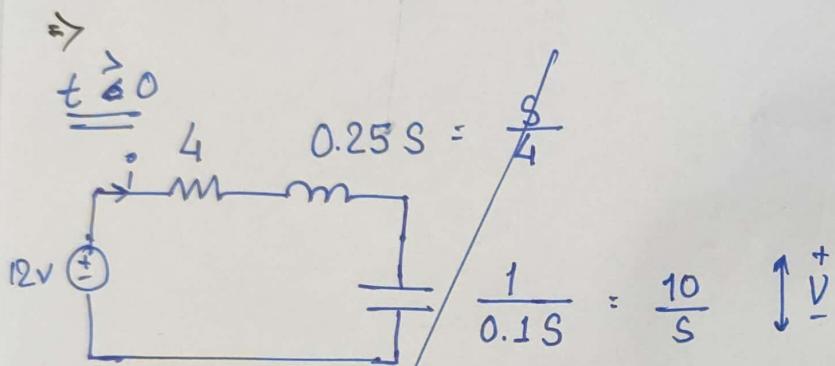T.S (c) $\frac{di(0^+)}{dt}, \frac{dV(0^+)}{dt}$




$$12 - 4I - \frac{1}{4}I - \frac{10}{s}I = 0$$

$$\left(4 + \frac{1}{4} + \frac{10}{s}\right)I = 12$$

$$I = \frac{12(4s)}{16s + s^2 + 40} = \frac{48s}{s^2 + 16s + 40}$$

(a) $\frac{0s}{(s+2)(\frac{1}{s}+2)}$

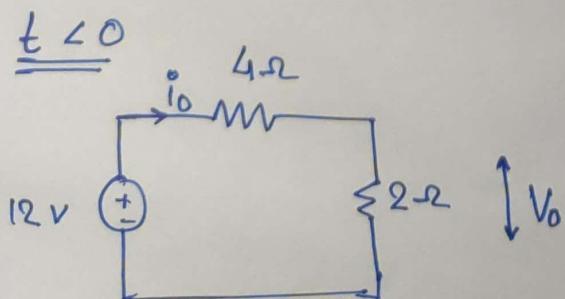


$$V_0 = \frac{12 \times 2}{6}$$

$$\boxed{V_0 = 4V}$$


$$i_0 = \frac{12}{6} \Rightarrow \boxed{i_0 = 2V}$$

$$i(0^+) = 2V, V(0^+) = 4V$$

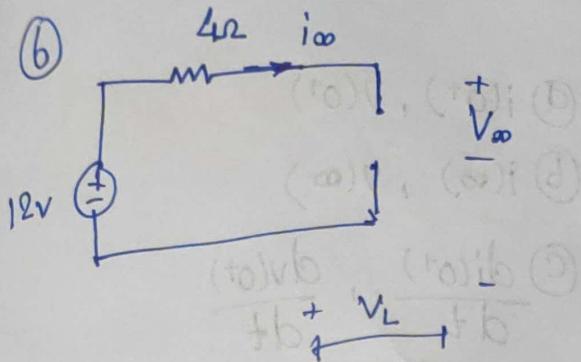

$$i(\infty) = 0 \text{ A}$$

$$V(\infty) = 12 \text{ V}$$

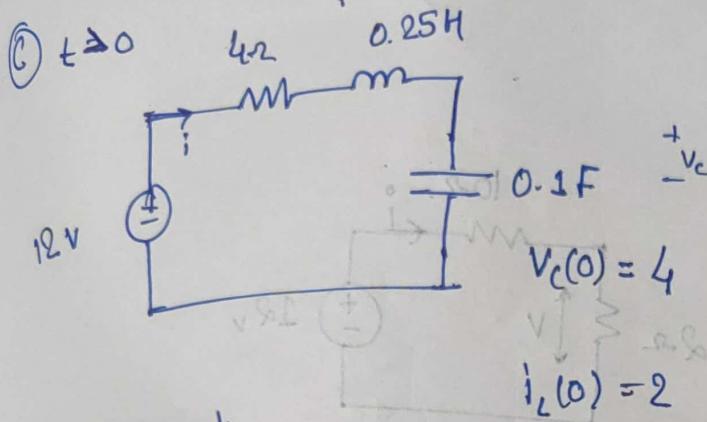

$$\dot{i} = \frac{C}{L} \frac{dv}{dt}$$

$$\frac{dv(0^+)}{dt} = \frac{i_c(0)}{C} = \frac{2}{0.1}$$


$$\frac{dv(0^+)}{dt} = 20 \text{ V/sec}$$

$$12 - 4i_L(0) - V_L - 4 = 0$$

$$V_L = 0$$

$$\checkmark \frac{di(0^+)}{dt} = 0 \text{ A}$$

Q.1

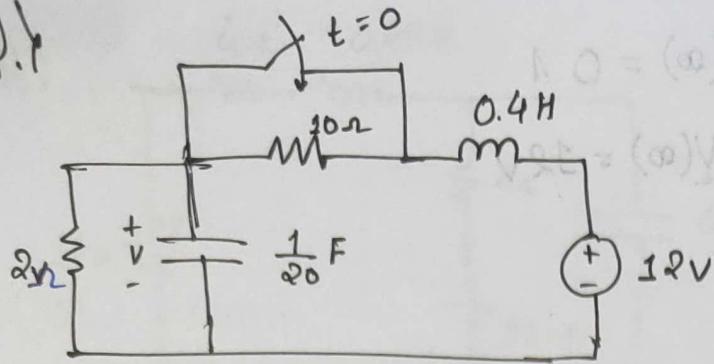


(a) $i(0^+), V(0^+)$

(b) $i(\infty), V(\infty)$

(c) $\frac{di(0^+)}{dt}, \frac{dv(0^+)}{dt}$


Ans

(a) at $t < 0$

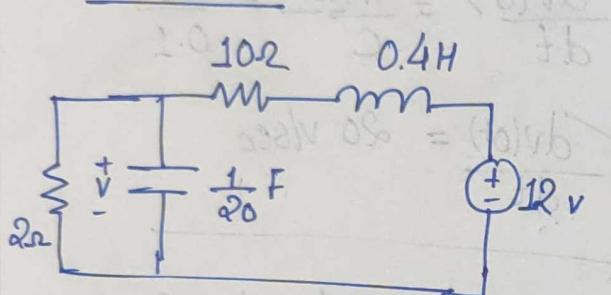

$$0 = 12 - iV - (0)V - 8I$$

$$0 = iV$$

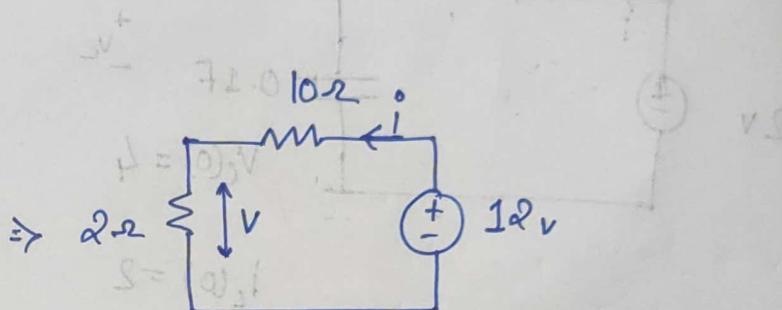


$$i(0^+) = \frac{12}{12} = 1A$$

$$V(0^+) = \frac{12 \times 2}{12} = \frac{12}{6} = 2V$$

22/0ct/24


Two Port

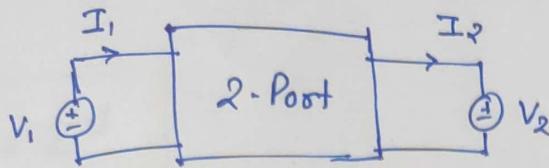

$$sI_{21}S + sI_{12}S = V$$

$$sI_{22}S + sI_{11}S = sV$$
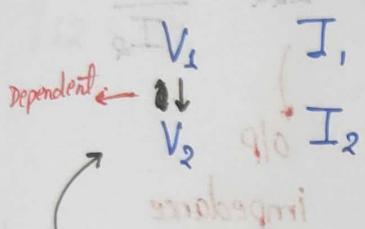
$$C_2 = 6 \rightarrow Z, Y, h, g \Leftrightarrow A, B, C, D \text{ or } a, b, c, d$$



Z parameter
(Impedance)

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Y Parameter
(Admittance)

h-Parameter (Hybrid Parameters)

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = [h_{21}I_1 + h_{22}V_2]$$

Dependent

$$V_1 \quad I_1$$

$$V_2 \quad I_2$$

$$V_1 = f(I_1, V_2)$$

$$I_2 = f(I_1, V_2)$$

g-Parameter

(inverse hybrid Parameters)

$$I_1 = g_{11}V_1 + g_{12}I_2$$


$$V_2 = g_{21}V_1 + g_{22}I_2$$

$$V_1 \xrightarrow{ABCD} I_1$$

$$V_2 \xrightarrow{abcd} I_2$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

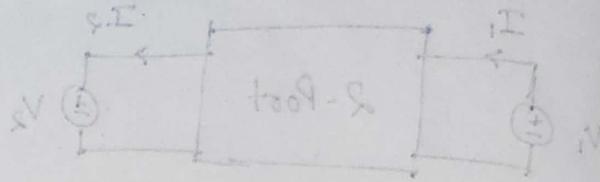

$$I_2 = 0$$

$$Z_{11} = \frac{V_1}{I_1}$$

input impedance

$$Z_{21} = \frac{V_2}{I_1}$$

$$Z_{12} = \frac{V_1}{I_2}$$


$$Z_{22} = \frac{V_2}{I_2}$$

Transfer impedance

open circuit impedance

$$\rightarrow Z_{11} = Z_{22} \rightarrow \text{Symmetrical Parameter}$$
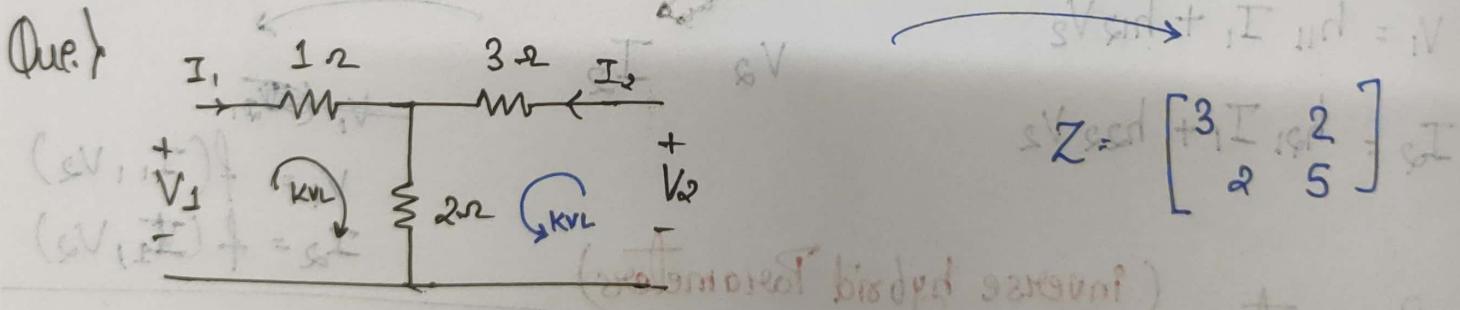
$$\rightarrow Z_{12} = Z_{21} \rightarrow \text{Reciprocal}$$



On Comparing,

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$Z_{11} = 3, Z_{12} = 2$$

$$Z_{21} = 2, Z_{22} = 5$$

\Rightarrow System is reciprocal

22/0ct/24

~~Ans~~ If dependent source is present, then we can not find Symmetrical / Reciprocal Parameter.

$$\boxed{Y = Z^{-1}}$$

$$Y_{11} = \frac{1}{3}, \quad Y_{21} = \frac{1}{2}$$

$$Y_{12} = \frac{1}{2}, \quad Y_{22} = \frac{1}{5}$$

Y_{11} = short-ckt o/p admittance

Y_{12} = short-ckt transfer admittance
from port 2 to 1

Y_{21} = —, —
from port 1 to 2.

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

Y_{22} = short-ckt o/p admittance

T(ABCD)

(Transmission Parameters)

$$SV = (SOL)S + I8 + SIP$$


$$SIP + IOL = SV$$

$$\begin{bmatrix} S & I \\ I & P \end{bmatrix} = X$$

$$\begin{bmatrix} S & I \\ I & P \end{bmatrix} = Y$$

Ques.1) calculate Z-parameters

for Z parameter
apply KVL

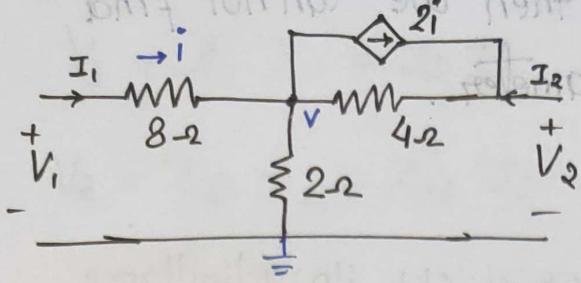


$$\Rightarrow 8I_1 + 2(I_1 + I_2) = V_1$$

$$V_1 = 10I_1 + 2I_2$$

$$I_1 = \frac{1}{8} V_1$$

$$\frac{1}{2} = 2.5$$

$$\frac{1}{4} = 0.25$$

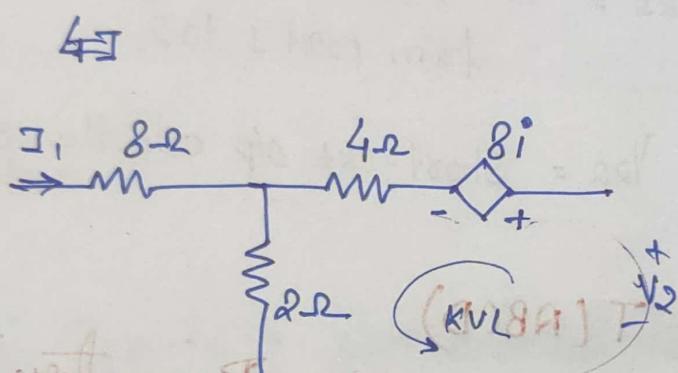

$$4I_2 + 8I_1 + 2(I_1 + I_2) = V_2$$

$$V = IR$$


$$j = I_1$$

$$\left. \begin{array}{l} 8I_2 + 8VA = V \\ CA_2 + DA_1 = I_2 \end{array} \right\}$$

$$V_2 = 10I_1 + 6I_2$$

$$Z = \begin{bmatrix} 10 & 2 \\ 10 & 6 \end{bmatrix}$$
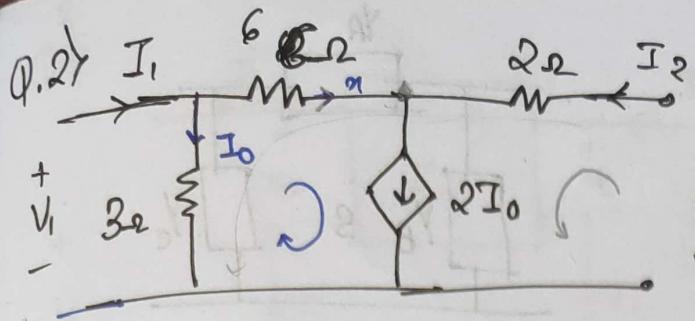
$$Y = \begin{bmatrix} 6 & -2 \\ -10 & 10 \end{bmatrix}$$



22/Oct/24
Y Parameters

$$\Rightarrow I_1 = \alpha + I_0 \quad | \quad V_1 = +3I_0$$

$$\alpha = I_1 - I_0$$

$$-6\alpha + 2I_0 + 3I_0$$

$$I_0 = ?$$

$$V_1 = ?$$

$$V_1 = -3I_0 - 3\alpha$$

$$V_1 = -I_1 - I_2 - ①$$

$$V_2 - 2I_2 \\ \alpha + I_2 = 2I_0$$

$$I_1 - I_0 + I_2 = 2I_0 \\ I_1 + I_2 = 3I_0 \\ I_0 = \frac{I_1 + I_2}{3}$$

$$V_2 - 2I_2 + 6\alpha - 3I_0 = 0$$

$$V_2 = 2I_2 - 6\alpha + 3I_0 = 0$$

$$V_2 = 2I_2 - 6(I_1 - I_0) + 3I_0$$

$$V_2 = 2I_2 - 6I_1 + 6I_0 + 3I_0$$

$$V_2 = -6I_1 + 2I_2 + 9I_0$$


$$V_2 = -3I_1 + 5I_2$$

$$Z_{11} = -1$$

$$Z_{12} = -1$$

$$Z_{21} = -3$$

$$Z_{22} = 5$$

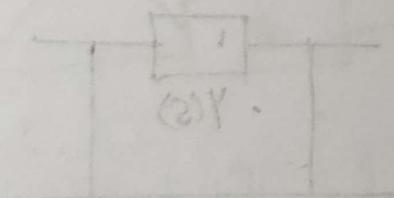

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = Y$$



$$+Y = 5$$

Do you like?

$$\begin{bmatrix} 5 & -3 \\ -1 & 5 \end{bmatrix} = Y$$

$$+Y = 5$$

Do you like?

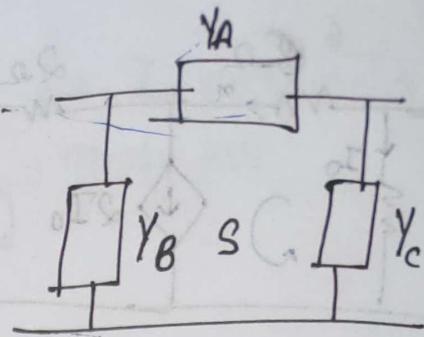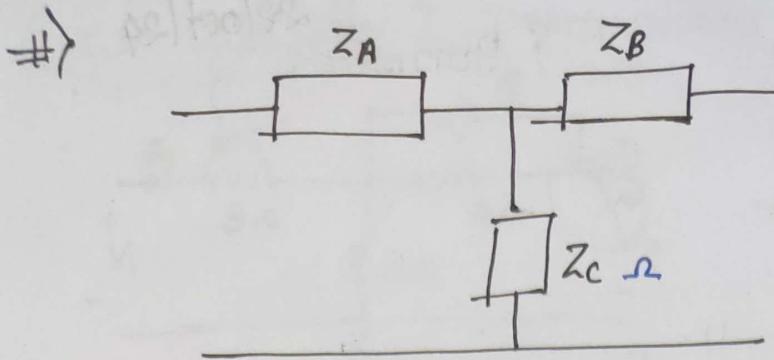

$$Z = \begin{bmatrix} Z_A + Z_C & Z_C \\ Z_C & Z_B + Z_C \end{bmatrix}$$

$$Y = \begin{bmatrix} Y_A + Y_B & -Y_A \\ -Y_A & Y_A + Y_C \end{bmatrix}$$

↳ when there is
no dependent
source is
present

$$Z = Y^{-1}$$

$$h = g^{-1}$$

$$Z_A = Z_{11} - Z_{12}$$

$$Y_A = -Y_{12} = -Y_{21}$$


$$Z_B = Z_{22} - Z_{21}$$

$$Y_B = Y_{11} + Y_{12}$$


$$Z_C = Z_{12} = Z_{21}$$

$$Y_C = Y_{22} + Y_{21}$$

Q.1)

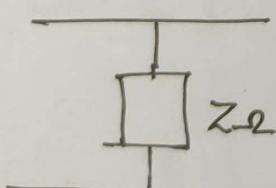

$$Y = ?$$

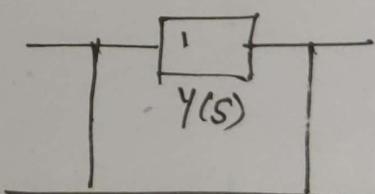

$$Z = ?$$

* $Z = \begin{bmatrix} z & z \\ z & z \end{bmatrix}$


$$Y = Z^{-1}$$

$Y = \text{Not Exist}$

$$Z = Y^{-1}$$

↓
Do not exist

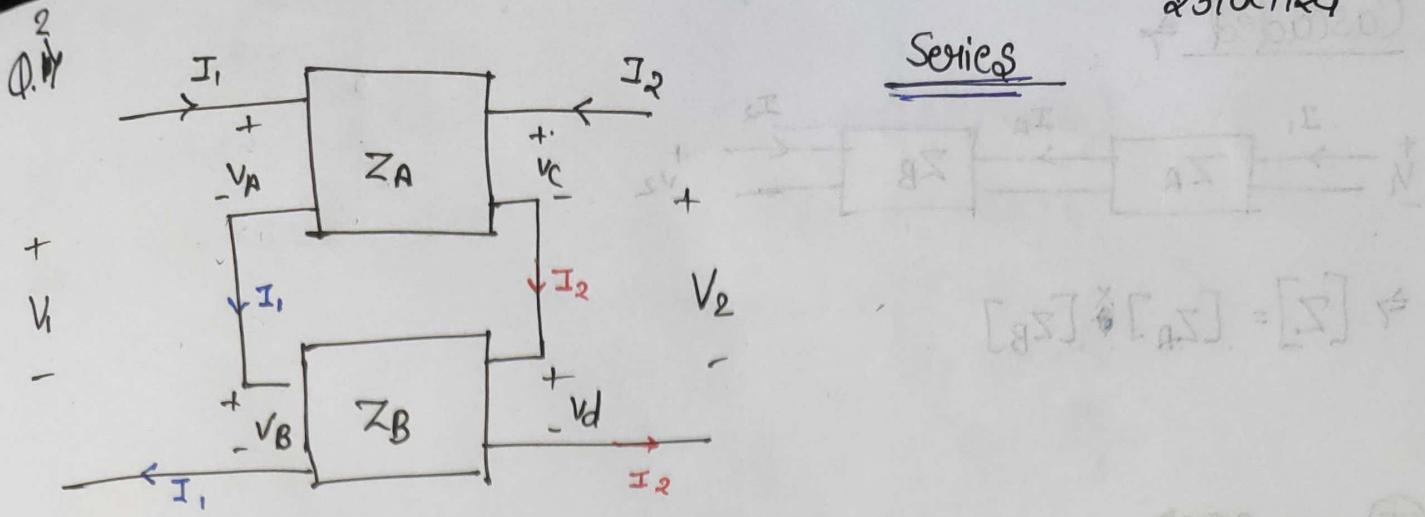
$$Y = \begin{bmatrix} y & -y \\ -y & y \end{bmatrix}$$




$$[Z]_f = [Z_A] + [Z_B]$$

23/10/24
P.D. 2020


$$[Z]_f = [Z_A] + [Z_B]$$

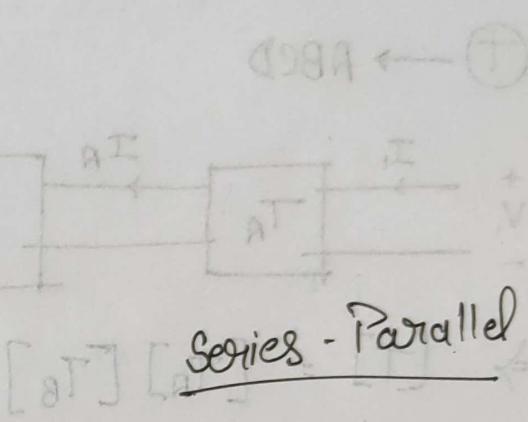

Q. 3) Parallel

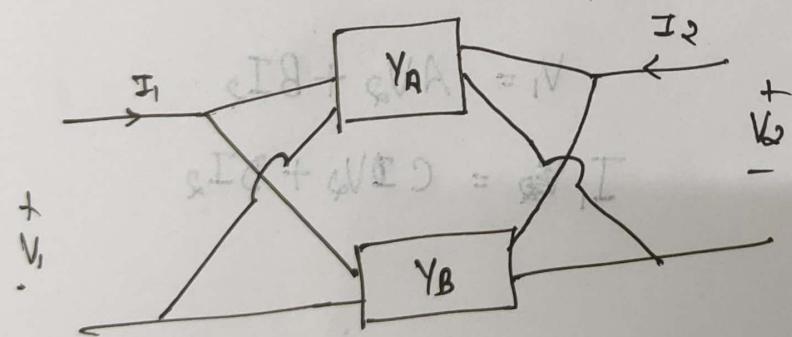

$$Y = [Y_A] + [Y_B]$$

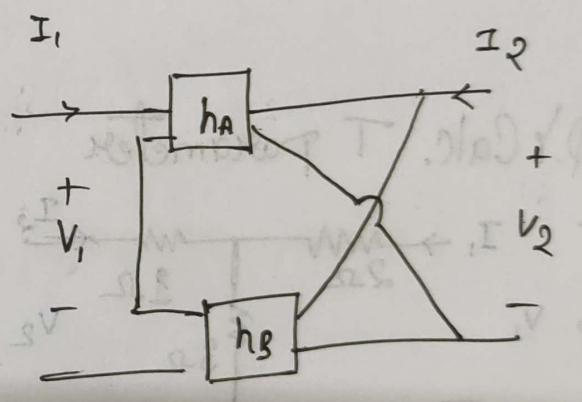


$$[g]_f = [g_A] + [g_B]$$


Parallel Series

$$[g] = [g_A] + [g_B]$$


Cascaded \Rightarrow

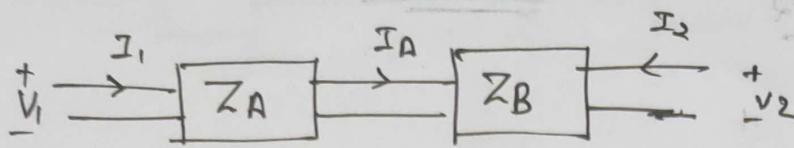
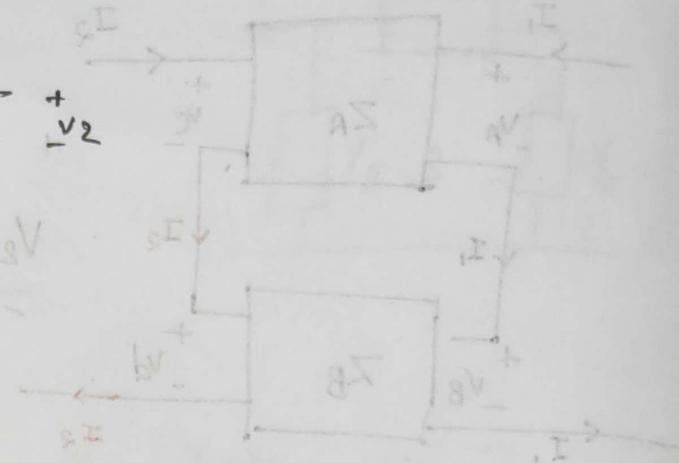
$$\Rightarrow [Z] = [Z_A] \otimes [Z_B]$$




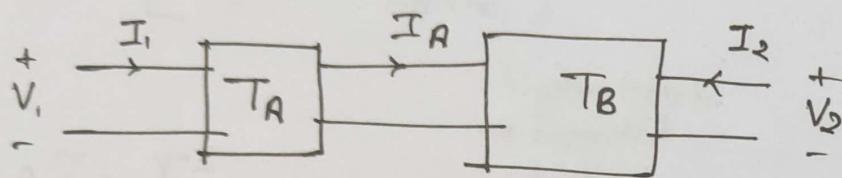$\textcircled{T} \rightarrow \text{ABCD}$



$$\Rightarrow [T] = [T_A] [T_B]$$

Q) Calc. T parameter

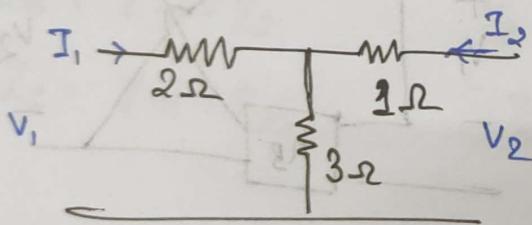

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

$$[Z] = \begin{bmatrix} 5 & 3 \\ 3 & 4 \end{bmatrix}$$

$$V_1 = 5I_1 + 3I_2$$

$$V_2 = 3I_1 + 4I_2$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\text{Put } I_2 = 0 \Rightarrow Z_{11} \checkmark$$

$$\text{Put } I_1 = 0 \Rightarrow Z_{12} \checkmark$$

$$\text{Ans} \quad V_1 = AV_2 + BI_2$$

$$= A(3I_1 + 4I_2) + BI_2 = 5I_1 + 3I_2$$

$$3AI_1 + (4A+B)I_2 = 5I_1 + 3I_2$$

On Comparing

$$A = 5/3$$

$$B = -11/3$$

23 Oct / 24

$$Y = \begin{bmatrix} 4 & -3 \\ -3 & 5 \end{bmatrix}$$

$$I_1 = 4V_1 - 3V_2 \quad \text{--- (1)}$$

$$I_2 = -3V_1 + 5V_2$$

$$I_1 = CV_2 + DI_2$$

$$4V_1 - 3V_2 = CV_2 + D(-3V_1 + 5V_2)$$

$$4V_1 - 3DV_1 = -3DV_1 + (C+5D)V_2$$


On comparing with (1)

$$-3D = 4, \quad C + 5D = 5$$

$$D = -\frac{4}{3}, \quad C = \frac{35}{3}$$

$$0 = xi\delta - iE - V$$

Q. 20

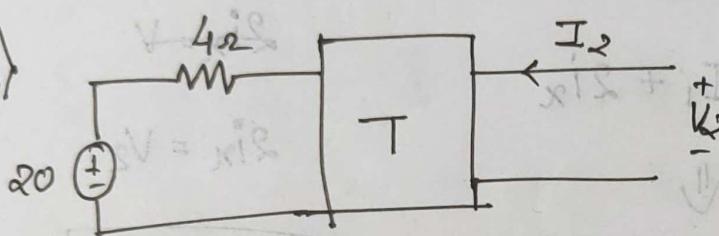

$$i_1 I_2 = 5V$$

$$i_2 E = 1V$$

$$0 = xi\delta + xi\delta - id\delta -$$


$$0 = 0i$$

$$xi = iE$$

⇒

$$T = \begin{bmatrix} 5/3 & -11/3 \\ 1/3 & -4/3 \end{bmatrix}$$

Ques.

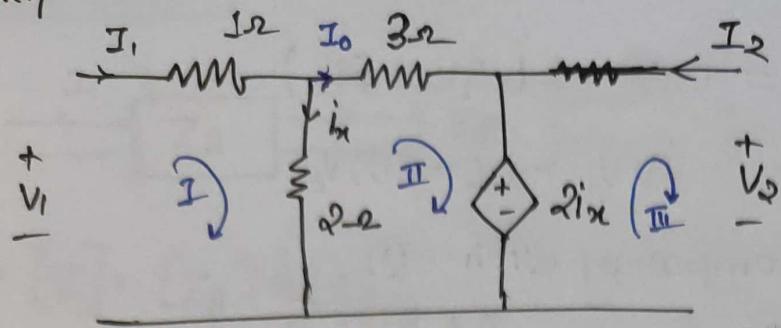

⇒

I

$$I_1 = i_x + i_0$$

$$V_1 - I_1 - 2i_x = 0$$

$$i_0 = I_1 - i_x$$

$$V_1 = I_1 + 2i_x$$

III

$$2i_x = V$$

$$2i_x = V_2$$

II

$$-3i_0 - 2i_x + 2i_x = 0$$

$$\boxed{i_0 = 0}$$


$$\boxed{I_1 = i_x}$$

$$\boxed{V_1 = 3I_1}$$

$$\boxed{V_2 = 2I_1}$$

$$\begin{bmatrix} 3 & 1 \\ 1 & 2 \end{bmatrix} \cdot T$$

Que)

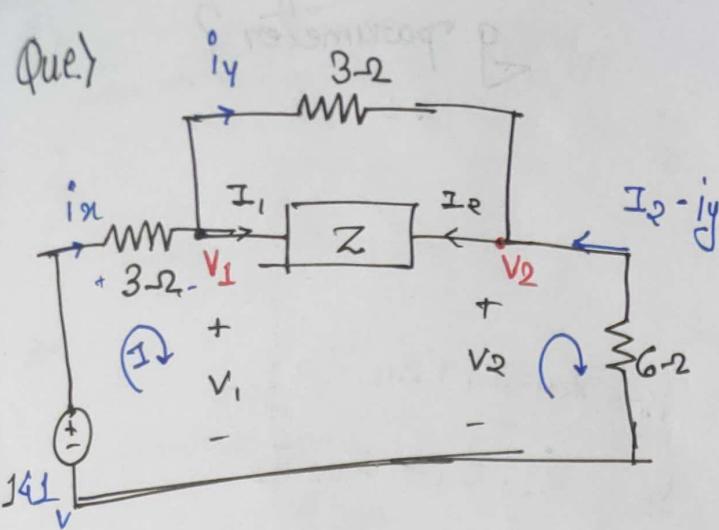

$$Z = \begin{bmatrix} 2 & 1 \\ 1 & 4 \end{bmatrix}$$

23/0ct/24

find I_1 & I_2

$$\Rightarrow i_x = i_y + I_1 \quad \textcircled{3}$$

$$V_1 = 2I_1 + 1I_2 \quad \textcircled{1}$$

$$i_y = \frac{V_1 - V_2}{3} \quad \textcircled{4}$$

$$i_y = \frac{sI_{SSB} + IV_{nB}}{3} = sV \quad \textcircled{5}$$

$$i_y = \frac{+I_1 - 3I_2}{3} \quad \textcircled{5}$$

$$\underline{\text{KVL - I}} \quad sI\left(\frac{1}{1+2}\right) + sV\left(\frac{1}{1+2}\right) = sI \quad \text{from } \textcircled{3}, \textcircled{4}, \textcircled{5} = sV$$

$$141 - 3i_x = V_1 \quad (\text{Substitute } V_1)$$

$$141 - 2I_1 - I_2 = \frac{I_1 - 3I_2}{3} + I_1$$

$$i_x = \frac{141 - 2I_1 - I_2}{3} \quad \text{from } \textcircled{1}$$

$$\text{from } \textcircled{3}, \textcircled{5}$$

$$i_x = \frac{4I_1 - 3I_2}{3}$$

KVL - II

$$V_2 + 6(I_2 - iy) = 0$$

$$\text{from } \textcircled{4} \& \textcircled{6}$$

$$iy = \frac{1}{6}(V_2 + 6I_2)$$

$$6I_1 - 2I_2 = 141$$

$$iy = \frac{1}{6}(I_1 + 10I_2) \quad \textcircled{7}$$

$$\text{from } \textcircled{3} \& \textcircled{7}$$


$$I_1 - 16I_2 = 0$$

$$I_1 = 24$$


$$I_2 = 1.5$$

Ans

Ques.)

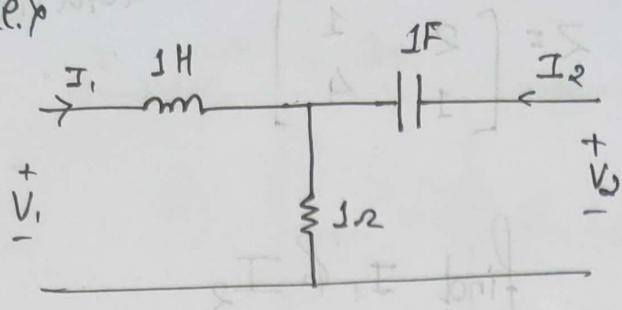

g parameter?

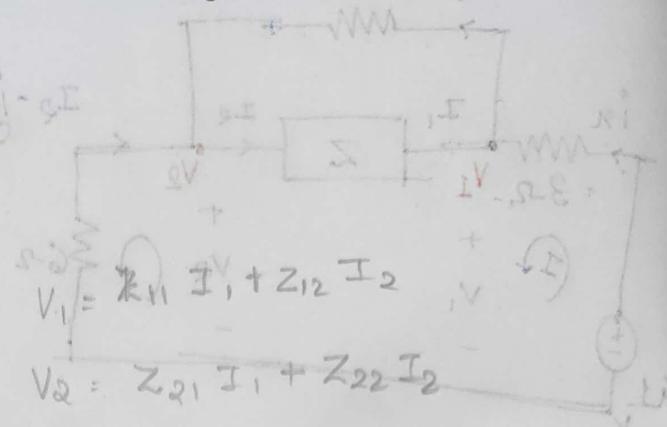

$$1H \rightarrow SL = S - 2$$

$$1F \rightarrow \frac{1}{SC} = \frac{1}{S} - 2$$

$$Z = \begin{bmatrix} S+1 & 1 \\ 1 & \frac{1}{S} + 1 \end{bmatrix}$$

(V₁, V₂)

$$V_1 = (S+1)I_1 + I_2 \quad \rightarrow \quad I_1 = \left(\frac{1}{S+1}\right)V_1 + \left(-\frac{1}{S+1}\right)I_2 \quad (1)$$


$$V_2 = I_1 + \left(\frac{S+1}{S}\right)I_2$$

$$V_2 = \left(\frac{1}{S+1}\right)V_1 + \left(-\frac{1}{S+1}\right)I_2 + \left(\frac{S+1}{S}\right)I_2$$

$$V_2 = \left(\frac{1}{S+1}\right)V_1 + \left(\frac{S^2+S+1}{S(S+1)}\right)I_2 \quad (2)$$

On comparing (1) & (3), (2) & (4)


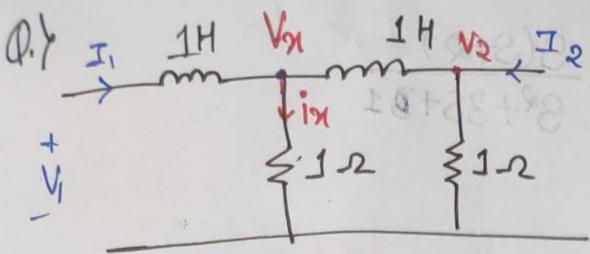
$$g = \begin{bmatrix} \frac{1}{S+1} & \frac{-1}{S+1} \\ \frac{1}{S+1} & \frac{S^2+S+1}{S(S+1)} \end{bmatrix}$$



23/0ct/24

Q. 8 g?

★ Apply Nodal / Mesh

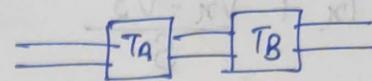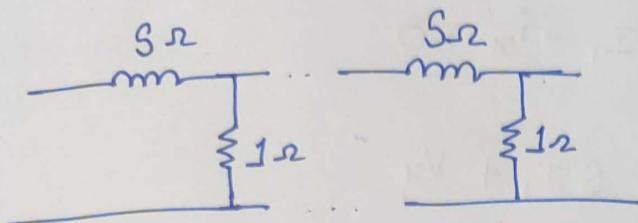

$$[T] = [T_A] \cdot [T_B]$$

Nodal

Nodal

$$\frac{V_X - V_1}{S} + \frac{V_X}{1} + \frac{V_X - V_2}{S} = 0$$

$$\left(\frac{1}{S} + 1 + \frac{1}{S}\right) V_X = \frac{V_1}{S} + \frac{V_2}{S}$$

$$S + \left(\frac{S+2}{S}\right) V_X = \frac{V_1 + V_2}{S}$$

$$V_X = \frac{V_1 + V_2}{S+2}$$

$$\frac{V_2 - V_X}{S} + \frac{V_2}{1} + (-I_2) = 0$$

$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

$$I_2 = \frac{V_2 - V_X}{S} + \frac{V_2}{1} = \frac{V_2}{S} - \frac{V_1 + V_2}{S(S+2)} + \frac{V_2}{S}$$

$$I_2 = \left(\frac{1}{S} + \frac{1}{S(S+2)} + 1\right) V_2 - \frac{V_1}{S(S+2)}$$

$$V_2 = \left(I_2 + \frac{V_1}{S(S+2)}\right) \times \frac{1}{\left(\frac{1}{S} + \frac{1}{S(S+2)} + 1\right)}$$

$$V_2 = \left(\frac{S^2 + 3S + 3}{S(S+2)}\right) I_2 + \left(\frac{1}{S^2 + 3S + 3}\right) V_1$$

$$\frac{S+2 + 1 + S(S+2)}{S(S+2)} \\ \frac{S^2 + 3S + 3}{S(S+2)}$$

$$\check{g}_{11} = \frac{1}{S^2 + 3S + 1}, \quad \check{g}_{22} = \frac{S(S+2)}{S^2 + 3S + 1}$$

debt \rightarrow debt \rightarrow \star

$$i_x = \frac{V_x}{1}$$

~~$$I_1 = i_x + \frac{V_x - V_2}{S}$$~~

$$V_1 - S I_1 - i_x = 0$$

~~$$I_1 = \frac{V_x}{1} + \frac{V_x - V_2}{S}$$~~

$$V_1 = S I_1 + V_x$$

$$J_1 = V_x + V_2 - I_2$$

$$V_1 = S I_1 + \frac{V_1 + V_2}{S+2}$$

$$0 = (S+1) + \frac{S\sqrt{2}}{1} + \frac{\pi V \cdot \sqrt{2}}{2}$$

$$S I_1 = 0 = \frac{V_1 - S\sqrt{V_1 + V_2}}{S+2} - \frac{\pi V}{1} + \frac{\pi V \cdot \pi V}{2}$$

$$S I_1 = \frac{(S+1)V_1 - V_2}{S+2} = \pi V \left(-\frac{1}{8} + L + \frac{1}{2} \right)$$

$$I_1 = \frac{S+1}{S(S+2)} V_1 - \frac{1}{S(S+2)} V_2$$

$$I_1 = \frac{S+1}{S(S+2)} V_1 - \frac{1}{S(S+2)} \left[\frac{S(S+2)}{S^2 + 3S + 1} I_2 + \frac{1}{S+2} V_1 \right]$$

$$I_1 = \left(\frac{S+1}{S(S+2)} V_1 + \frac{1}{S(S+2)(S^2 + 3S + 1)} I_2 \right) V_1 + \left(\frac{-1}{S^2 + 3S + 1} \right) I_2 = S I$$

$$I_1 = \frac{S(S+2)^2}{S(S+2)(S^2 + 3S + 1)} V_1 + \left(\frac{-1}{S^2 + 3S + 1} \right) I_2 = S I$$


$$I_1 = \left(\frac{S+2}{S^2 + 3S + 1} \right) V_1 + \left(\frac{-1}{S^2 + 3S + 1} \right) I_2 = S I$$

$$\check{g}_{11} = \frac{S+2}{S^2 + 3S + 1}$$

$$\check{g}_{12} = \frac{-1}{S^2 + 3S + 1}$$

Ans


Que. >

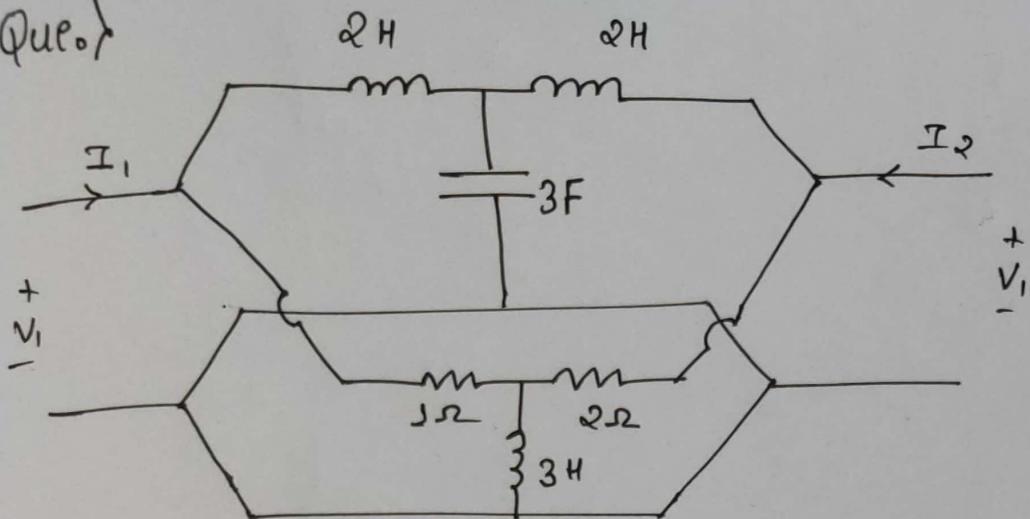

=>

05/NOV/24

Ques 1

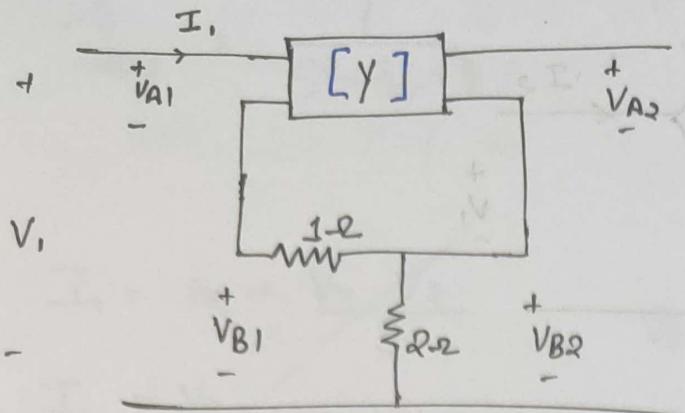
Calc. Ψ parameter

$$[Y] = \begin{bmatrix} 2 & 1 \\ 2 & 4 \end{bmatrix}$$

⇒

$$[Z_1] = [Y]^{-1}$$

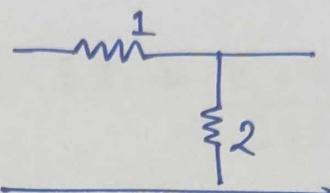
$$[Z_1] = \begin{bmatrix} 4 & -1 \\ -2 & 2 \end{bmatrix}$$



$$[Z_2] = \begin{bmatrix} 3 & 2 \\ 2 & 2 \end{bmatrix}$$


$$Z = Z_1 + Z_2 = \begin{bmatrix} 7 & -1 \\ 0 & 4 \end{bmatrix} \quad \underline{\text{Ans}}$$

Ques. 2

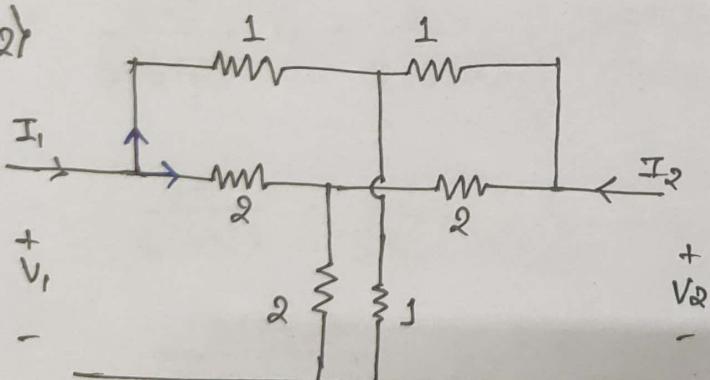
find $[Y]$?

→ Parallel

⇒

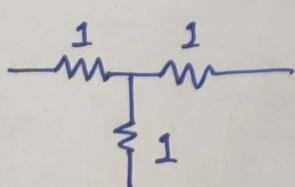
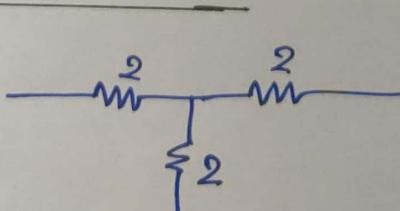
$$Z_1 = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}$$




$$Z_2 = \begin{bmatrix} 4 & 2 \\ 2 & 4 \end{bmatrix}$$



$$\Rightarrow Y = Y_1 + Y_2$$

$$Y = \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix} + \begin{bmatrix} 4 & 2 \\ 2 & 4 \end{bmatrix}$$

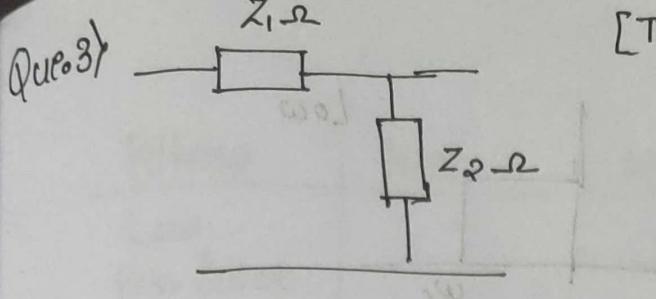
$$Y = \begin{bmatrix} 6 & -3 \\ -3 & 6 \end{bmatrix} \quad \underline{\text{Ans}}$$



[T] ?

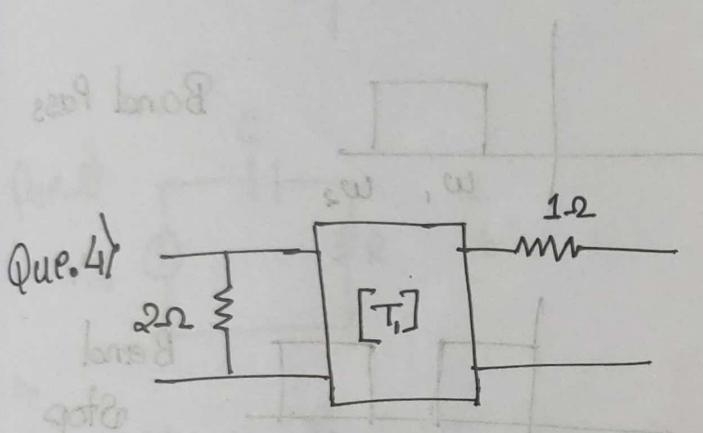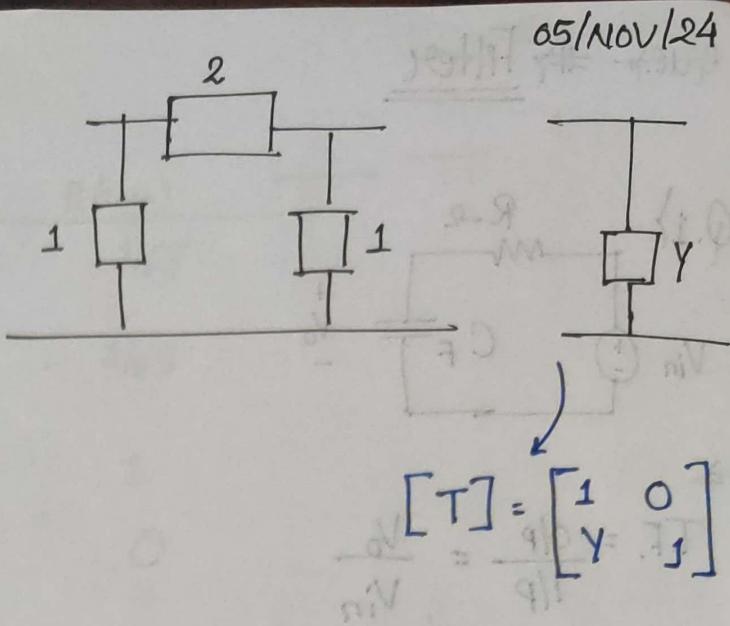
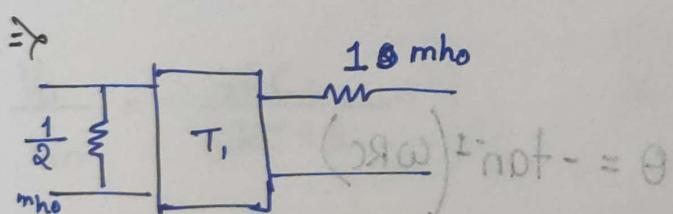
$$[T_1] = \begin{bmatrix} 3 & 4 \\ 2 & 3 \end{bmatrix} \quad T?$$



$$[T] = \begin{bmatrix} 1 & 0 \\ 1/2 & 1 \end{bmatrix} \begin{bmatrix} 3 & 4 \\ 2 & 3 \end{bmatrix} \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix}$$

$$0 = (\omega)H$$

$$\frac{1}{s^2(2R\omega) + L} = H(T)$$

$$\frac{1}{s^2(2R\omega) + L} = H(T)$$



$$\frac{1}{s^2(2R\omega) + L} = |(\omega)H|$$

$$\frac{1}{s^2(2R\omega) + L} = H(T)$$

$$s^2(2R\omega) + L = \omega^2$$

$$\frac{1}{s^2(2R\omega) + L} = \omega^2$$

Ques. # Filter

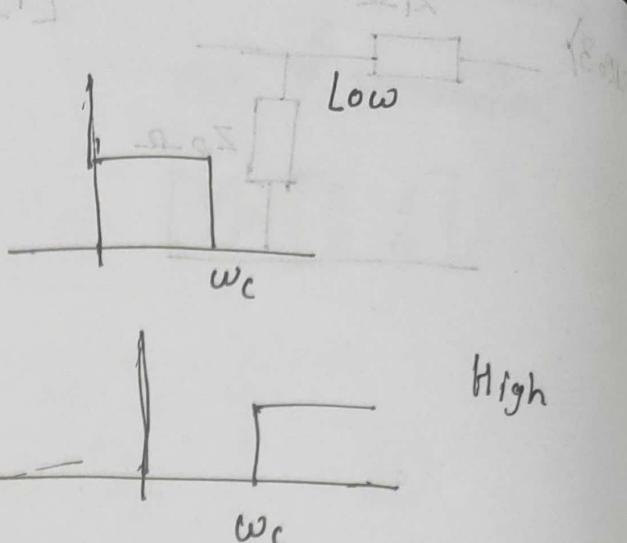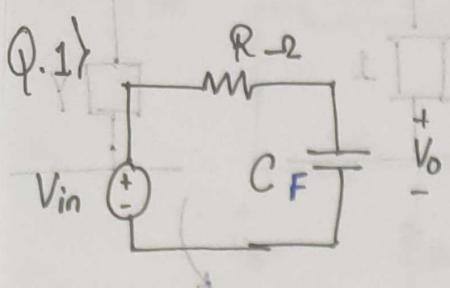

$$\Rightarrow T.F. = \frac{O/P}{I/P} = \frac{V_o}{V_{in}}$$

$V_{in} =$

$$V_o = V_{in} \times \frac{\frac{1}{SC}}{\frac{1}{SC} + R}$$


$$\frac{V_o}{V_{in}} = \frac{1}{1 + SRC}$$

$$\frac{V_o}{V_{in}} = \frac{1}{1 + j\omega RC} = H(\omega)$$

$$|TF| = \frac{1 - j\omega RC}{1 + (\omega RC)^2}$$

$$|TF| = \frac{\sqrt{1 + (\omega RC)^2}}{1 + (\omega RC)^2}$$

$$|TF| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

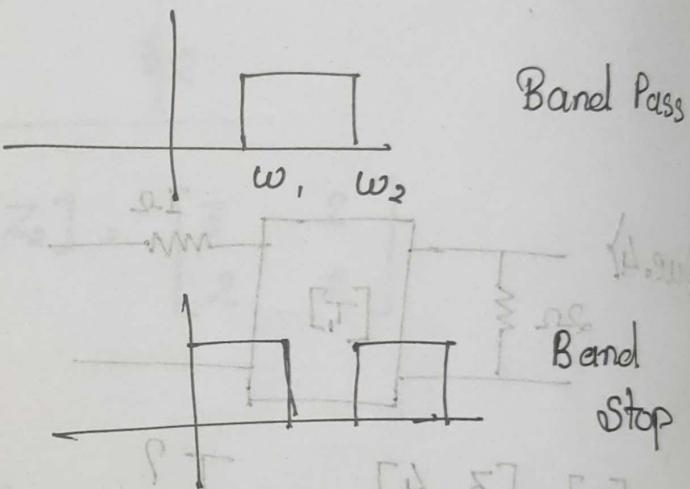




$$\Theta = -\tan^{-1}(\omega RC)$$



$$\begin{aligned} H(0) &= 1 \\ H(\infty) &= 0 \end{aligned} \quad \left. \right\} \text{Low Pass filter}$$

$$|H(\omega)| = \frac{1}{\sqrt{2}}$$

$$1 + (\omega_c RC)^2 = 2$$

$$\boxed{\omega_c = \pm \frac{1}{RC}}$$

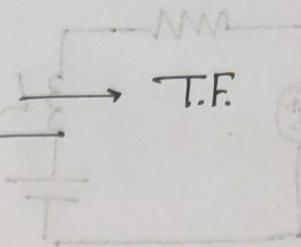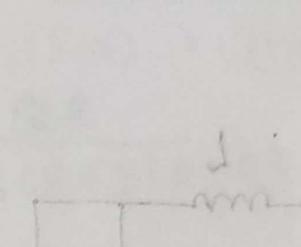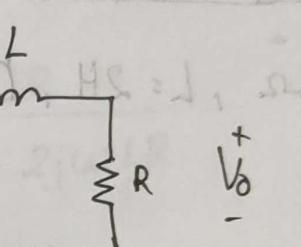Filter	$H(0)$	$H(\infty)$	$H(\omega_c)$	T.F.
Low Pass filter	1	0	$\frac{1}{\sqrt{2}}$	
High	0	1	$\frac{1}{\sqrt{2}}$	
Band Pass	0	0	1	
Band Stop	1	1	0	

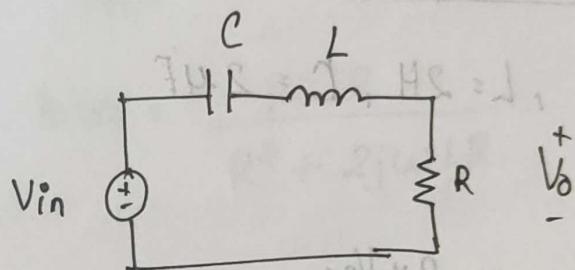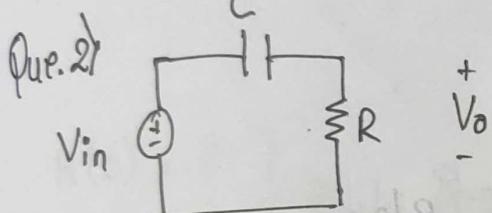

$$\frac{V_o}{V_{in}} = \frac{\frac{1}{SRC} + \frac{R}{R + \frac{1}{SC}}}{SRL + \frac{R}{R + \frac{1}{SC}}} = \frac{\frac{R}{R + \frac{1}{SC}}}{SRL + \frac{R}{R + \frac{1}{SC}}} = \frac{R}{R + \frac{1}{SC} + SRC}$$

$$V_o = V_{in} \times \frac{R}{R + \frac{1}{SC} + SRC}$$

$$\frac{V_o}{V_{in}} = \frac{SRC}{SRC + 1 + S^2CL}$$

$$H(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

$$H(\omega) = \frac{j\omega RC}{1 - \omega^2 CL + j\omega RC}$$


$$|H(\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

$$|H(\omega)| = \frac{\omega RC}{\sqrt{(1 - \omega^2 CL)^2 + (\omega RC)^2}}$$


$$\left. \begin{array}{l} H(0) = 0 \\ H(\infty) = 1 \end{array} \right\} \text{High Pass}$$

$$\left. \begin{array}{l} H(0) = 0 \\ H(\infty) = 0 \end{array} \right\} \text{Band Pass}$$

Que. 3

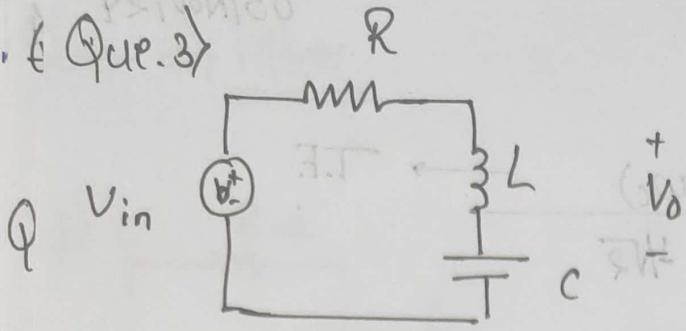


Que. 4

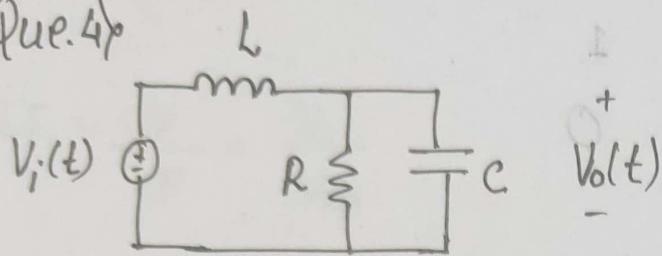

Find Type of filter & cut off freq.

$$R = 2\text{k}\Omega, L = 2\text{H}, C = 2\mu\text{F}$$

\Rightarrow

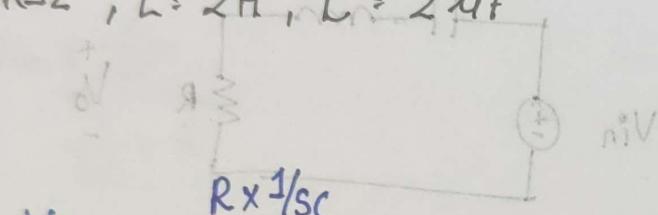

$$V_o = V_i \times \frac{\frac{R \times 1/SC}{R + \frac{1}{SC}}}{\frac{SL + \frac{R \times 1}{SC}}{R + \frac{1}{SC}}} = 0\text{V}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{\frac{R/SC}{SRL + R/SC + \frac{L}{C}}}{\frac{R}{S^2 RLC + R + SL}}$$

$$H(\omega) = \frac{R \omega i}{SRL + R - \omega^2 RLC + j\omega L} = (j\omega)H$$

$$H(0) = +1^\circ \quad \left. \right\} \text{Low Pass}$$

$$H(\infty) = 0$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}}$$

$$\frac{R^2}{\sqrt{(R - \omega^2 RLC)^2 + (\omega L)^2}} = \frac{1}{\sqrt{2}}$$

$$2R^2 = R^2 + \omega^4 R^2 L^2 C^2 - 2\omega^2 R^2 L C + \omega^2 L^2$$

$$\Rightarrow (R^2 L^2 C^2) \omega_c^4 + (L^2 - 2R^2 L C) \omega_c^2 - R^2 = 0$$

Q.5) ~~Find ω_c~~



$$\omega_c = ?$$

$$(j\omega + j_0 \omega n) \text{ rad} \sum_{\text{L+R}} + j_0 D = (j) +$$

$$R_1 = R_2 = 100, L = 2 \text{ mH}$$

$$8 \text{ rad/sec} \times 8 \text{ rad/sec} = (8+A) \text{ rad/sec}$$

\Rightarrow

$$V_o = V_{in} \times \frac{\frac{SLR}{SL+R}}{\frac{SLR}{SL+R} + R} \Rightarrow \frac{V_o}{V_{in}} = \frac{SLR}{SLR + SLR + R^2} = \frac{SLR}{R^2 + 2SLR}$$

~~$(j_0 \omega n) \text{ rad/sec} = j_0 D$~~

~~$(j_0 \omega n) \text{ rad/sec} = j_0 D$~~

$$H(j\omega) = \frac{j\omega LR}{R^2 + 2j\omega LR}$$

$$\left. \begin{array}{l} H(0) = 0 \\ H(\infty) = 1 \end{array} \right\} \text{High Pass}$$

$$(j_0 \omega n) \text{ rad/sec} + j_0 D = (j) +$$

$$|H(j\omega)| = \frac{\omega LR}{\sqrt{R^4 + (2\omega LR)^2}}$$

$$\frac{jD + j_0 D}{2} = 1 \text{ rad/sec}$$

$$\left(\frac{jD}{j_0 D} \right)^2 \text{ rad/sec} = j_0 \phi$$

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} \left(\frac{jD}{j_0 D} \right)^2 \text{ rad/sec}$$

$$\frac{jD + j_0 D}{2} = j_0 \phi \Rightarrow |A|$$

$$2\omega_c^2 L^2 R^2 = R^4 + 4\omega_c^2 L^2 R^2$$

$$2\omega_c^2 L^2 R^2 = R^4$$

$$\omega_c = \frac{R}{L\sqrt{2}} = \frac{100}{2 \times 10^{-3} \times \sqrt{2}} = 100 \text{ rad/sec}$$

$$(j_0 \omega n) \text{ rad/sec} = j_0 D$$

$$\omega_c = 35.35 \times 10^3 \text{ rad/sec}$$

06/Nov/24

→ Fourier Series

$$f(t) = a_0 + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t + \phi_n)$$

$$\cos(A+B) = \cos A \cos B - \sin A \sin B$$

$$= [A_n \cos(n\omega_0 t)] \cos \phi_n - [A_n \sin(n\omega_0 t)] \sin \phi_n$$

$$= a_n \cos \phi_n + b_n \sin \phi_n$$

~~$$a_n = A_n \cos(n\omega_0 t)$$~~

~~$$b_n = -A_n \sin(n\omega_0 t)$$~~

$$f(t) = a_0 + \sum_{n=0}^{\infty} (a_n \cos \phi_n + b_n \sin \phi_n)$$

$$|A_n| = \sqrt{a_n^2 + b_n^2}$$


$$\phi_n = -\tan^{-1}\left(\frac{b_n}{a_n}\right)$$

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t))$$

$$|A_n| \angle \phi_n = \sqrt{a_n^2 + b_n^2} \quad \left[-\tan^{-1}\left(\frac{b_n}{a_n}\right) \right] \frac{1}{\sqrt{2}} = |(\omega)H|$$

$$a_n = A_n \cos(\phi_n)$$

$$b_n = -A_n \sin(\phi_n)$$

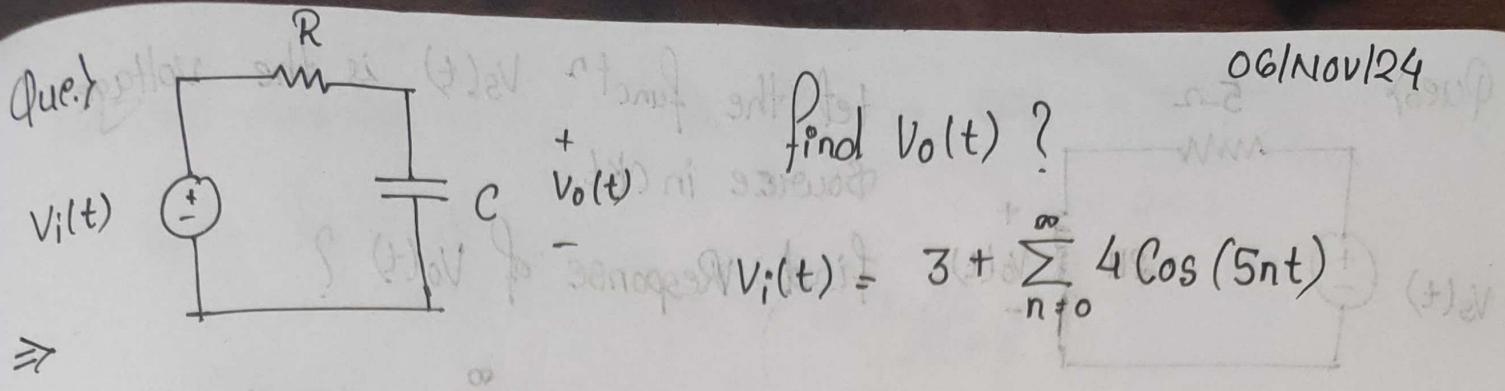

$$V_o(s) = \frac{1/sC}{R + 1/sC} \times V_i(s) = \boxed{a_0 = 3}$$

$$|A_n| = 4 = \sqrt{a_n^2 + b_n^2}$$

$$a_n^2 + b_n^2 = 16 \quad \text{--- (1)}$$

$$\phi_n = 0 = -\tan^{-1}\left(\frac{b_n}{a_n}\right)$$

$$\frac{b_n}{a_n} = 0 \Rightarrow \boxed{b_n = 0}$$


$$\boxed{a_n = 4}$$

$$\omega = 5n$$

$$|A_n| = 4 \quad \phi_n = 0$$

$$v(t) = 3 + \sum_{n=0}^{\infty} 4 \cos(5nt)$$

Ques

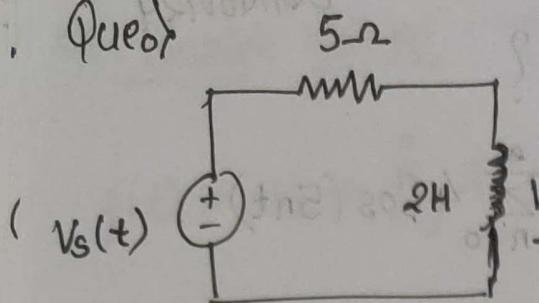

Let the funct'n $V_s(t)$ is the voltage source in ckt.
find Response of $V_o(t)$?

$$V_s(t) = \underbrace{\frac{1}{2}}_{DC} + \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{1}{n} \sin(n\pi t)$$

$$\Rightarrow \underline{s_0} + \underline{s_0 D} = P = 1 \quad \omega_n = 0$$

$$\textcircled{1} \rightarrow \underline{s_0} = \underline{s_0} + \underline{s_0 D}$$

$$s = j\omega$$

$$n = 2K-1$$

$$\omega_n = n\pi$$

$$\omega_1 = \pi$$

for DC $\rightarrow \omega_n = 0$

$$V_o = V_s \times \frac{2S}{2S+5}$$

$$S = j\omega$$

$$S = 0$$

$$V_o = \frac{1}{2} \times \frac{0}{0+5}$$

$$V_o = 0$$

For AC $\rightarrow \omega_n = n\pi$


$$n = 2K-1$$

$$V_o = V_s \times \frac{2S}{2S+5}$$

$$V_s = \frac{2}{\pi} \sum_{k=1}^{\infty} \frac{1}{n} \sin(n\pi t)$$

$$\angle -90^\circ$$

$$\cos(-90^\circ) + j \sin(-90^\circ)$$

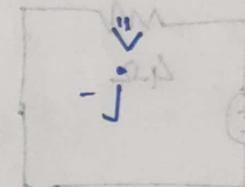

$$S = j\omega$$

$$S = j\pi n$$

$$\begin{aligned} & \frac{1}{n} \sin(n\pi t) \\ & \frac{1}{n} \cos(n\pi t - 90^\circ) \\ & \phi = -90^\circ \\ & = -j \end{aligned}$$

Conversion to
Phasor domain

$$V_s = -\frac{2j}{\pi n}$$

$$V_o = \frac{-2j}{\pi n} \times \frac{2j\pi n}{2j\pi n + 5}$$

$$= \frac{+4}{(2\pi n)j + 5}$$

$$|V_o| = \frac{4}{\sqrt{4\pi^2 n^2 + 25}} \angle \tan^{-1}\left(\frac{2\pi n}{5}\right)$$

Phase domain

$$|V_o| = \frac{4}{\sqrt{4\pi^2 n^2 + 25}} \cos\left(n\pi t - \tan^{-1}\left(\frac{2\pi n}{5}\right)\right)$$

Time domain

$$V_o(t) = 0 + \sum_{k=1}^{\infty} \frac{4}{\sqrt{4\pi^2 n^2 + 25}} \cos\left(n\pi t - \tan^{-1}\left(\frac{2\pi n}{5}\right)\right)$$

Ques.)

$V(t)$

$i(t)$

$i_o(t)$

$\frac{4}{2} = n\omega \leftarrow 2\Omega \text{ at } 30^\circ$

$1 - X_C = 5\Omega$

$\frac{3}{2} + 2\Omega \times 2V$

$\frac{2}{2+2\Omega}$

$\frac{2\Omega}{2+2\Omega} \times i_o(t)$

find Response of $i_o(t)$

$\omega_l = 2$

$0 = 0$

$\frac{2\Omega}{2+2\Omega} \times \frac{i_o(t)}{2\Omega} = 0$

$i_o(t) = 0$

$V(t) = 1 + \sum_{n=1}^{\infty} \frac{2(-1)^n}{1+n^2} (\cos nt - n \sin nt)$

$\downarrow \text{DC}$

$\downarrow \text{AC}$

\Rightarrow

$$i_o(s) = i(t) \times \frac{4}{4+2s}$$

$\left| \begin{array}{l} \text{Z} = \frac{1}{(s+1)} + \frac{1}{s+2} = (s+1) \\ \text{Z} = 4 + (4||2s) = 4 + \frac{8s}{4+2s} \\ \text{Z} = \frac{16+16s}{4+2s} \\ \text{Z} = \frac{8(s+1)}{s+2} \end{array} \right.$

$$i(t) = \frac{V}{Z} = \frac{(s+2)V}{8(s+1)}$$

$$i_o(t) = \frac{V(s+2)}{8(s+1)} \cdot \frac{2}{s+2}$$

$$i_o(s) = \frac{V}{4(s+1)}$$

$$i_o = \frac{V}{4(1+j\omega_n)} \Rightarrow |i_o| = \frac{V}{4\sqrt{1+n^2}} \angle \tan^{-1}(n)$$

$$i_o = 0 \text{ for } \omega_n = 0 \text{ or } n = 0$$

$$V = 1 \Rightarrow i_o = \frac{1}{4}$$

17.7

$$V(t) = 1 + \sum_{n=1}^{\infty} \frac{2(-1)^n}{1+n^2} (\cos nt - n \sin nt)$$

$$V(t) = 1 + \sum_{n=1}^{\infty} \frac{2(-1)^n}{1+n^2} \underbrace{A_n \cos(-nt)}_{\text{Amplitude}}$$

$$a_n = 1$$

$$A_n = \sqrt{1+n^2}$$

$$b_n = -n$$

$$\phi = -\tan^{-1}(-n) = \tan^{-1}(n)$$

$$V(t) = 1 + \sum_{n=1}^{\infty} \frac{2(-1)^n}{\sqrt{1+n^2}} \cos(nt + \tan^{-1}(n))$$

$$i_0 = \frac{V}{4\sqrt{1+n^2}} \angle \tan^{-1}(n)$$

$$\omega_n = n$$

$$DC \geq \omega_n \Rightarrow \omega_n = 0 \Rightarrow n = 0$$

$$i_0 = \frac{1}{4}$$

$$AC \geq$$

$$V = \frac{2(-1)^n}{\sqrt{1+n^2}} \angle \phi \quad \begin{matrix} n > 1 \\ \phi = \tan^{-1} n \end{matrix}$$

$$V = \frac{2(-1)^n}{\sqrt{1+n^2}} \angle \tan^{-1}(n)$$

for n^{th} harmonic,

$$\frac{L(-)nS_0}{S_0 + 1} = n\theta$$

$$V = \frac{2(-1)^n}{\sqrt{1+n^2}} \angle \tan^{-1}(n)$$

$$I_0 = \frac{1}{4\sqrt{1+n^2}} \angle \tan^{-1}(n) \times \frac{2(-1)^n}{\sqrt{1+n^2}} \angle \tan^{-1}(n)$$

$$I_0 = \frac{(-1)^n}{2(1+n^2)} = n\phi$$

$$i_0(t) = \frac{1}{4} + \sum_{n=1}^{\infty} \frac{(-1)^n}{2(1+n^2)} \cos(nt)$$

$$\frac{2S+\Delta}{2S+\Delta} = (2S||\Delta) + \Delta = \Sigma$$

$$\frac{2S+2\Delta}{2S+\Delta} = \Sigma$$

$$\frac{(1+2)S}{S+\Delta} = \Sigma$$

$$\frac{V(S+\Delta)}{(1+2)S} \times \frac{V}{5}$$

$$S \cdot (S+\Delta)V$$