


Bipolar Junction Transistor

* BJT is a 3-terminal device.



p-type is sandwiched
b/w 2 n types

Width $\rightarrow C > E > B$

Doping $\rightarrow E > C > B$

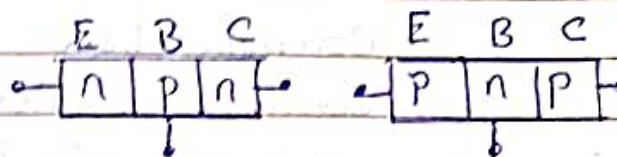

n type is
sandwiched b/w
2 p-types.

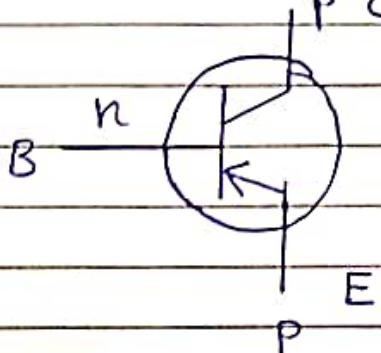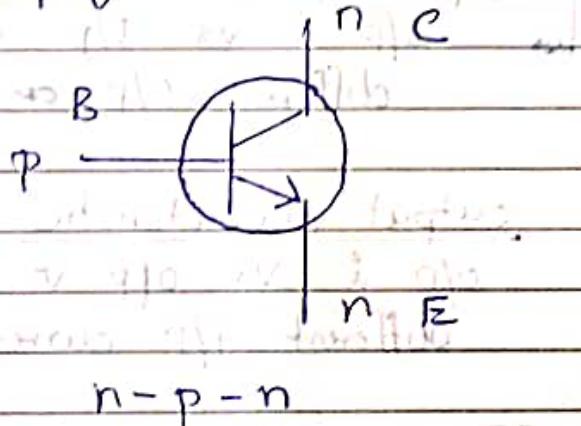

Bipolar Junction \rightarrow holes, electrons
 \leftrightarrow Two junctions

E-B $\leftarrow J_1$ & $J_2 \rightarrow C-B$

Transistor \rightarrow Transfer resistance

BJT \rightarrow amplified
 \rightarrow switching device

E-B	C-B	Region of operation	Application
J_1	J_2	Active region	Amplifier
F.B	R.B	Saturation region	Digital ON
F.B	F.B	Cutoff region	Digital OFF
R.B	R.B	Never used	Never used
R.B	F.B	Inverter	Inverter

BJT can be used in those configuration.


- i) Common - base
- ii) Common - emitter
- iii) Common - collector

Transfer Characteristics


→ Input characteristics
 I/P i vs I/P V for different O/P ∞ voltage

Output characteristic

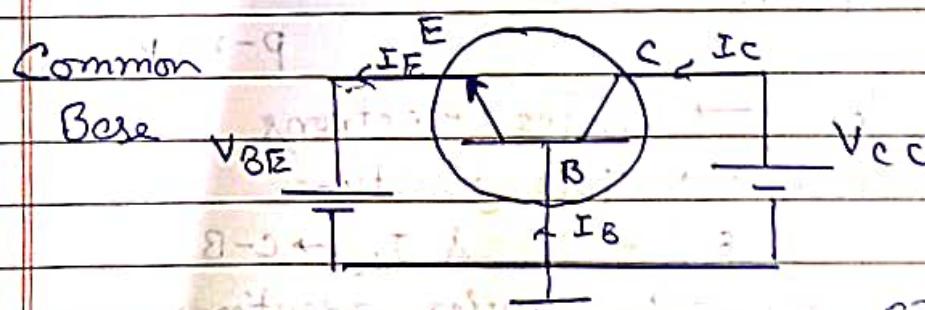O/P i vs O/P V for different I/P current.



$$\left\{ \begin{array}{l} I_E = I_C + I_B \\ I_C = \alpha I_E + I_{CBO} \end{array} \right. \rightarrow \begin{array}{c} I_E \\ I_C \end{array} = \begin{array}{|c|c|c|} \hline & - & + & - \\ \hline - & | & | & | \\ \hline - & + & - & - \\ \hline \end{array} \rightarrow I_C = \alpha I_E$$

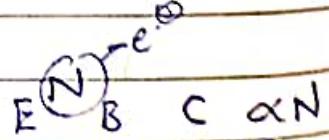

$$I_C = \alpha I_E$$


Recombination

Reverse saturation current

Collector current which flows when emitter ckt is open. I_{CBO}

$$I_C = \alpha I_E + I_{CBO}$$

negligible value

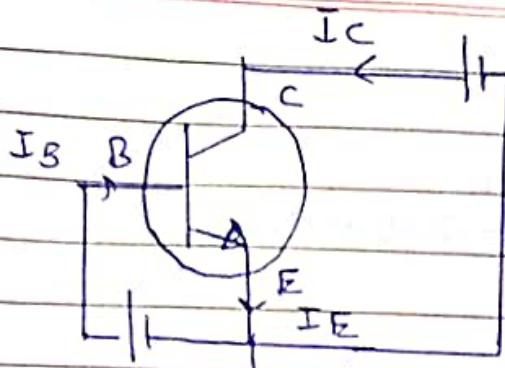


Common
Emitter

Used as amplifier

$$= \begin{cases} \text{i/p} & I_B \\ \text{o/p} & I_C \end{cases}$$
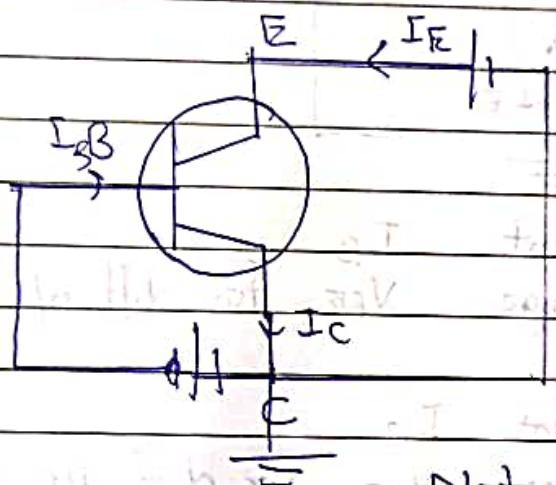
$$\beta = \frac{I_C}{I_B} \quad \beta = \{50 - 400\}$$




F.B. \rightarrow low resistance
R.B. \rightarrow high resistance



High input resistance
low output resistance

Not used for amplification purposes.

$$Q_0 I + (a_1 I + a_2) \approx -I$$

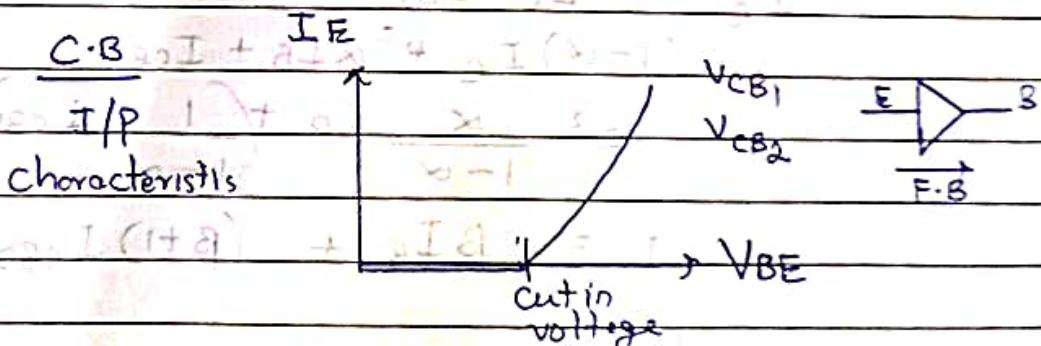

O/P characteristics

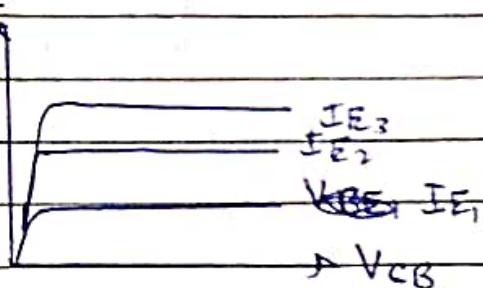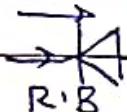

$$I_{BZ} = I_C + I_B$$


$$I_C = \alpha I_B + I_{CBO}$$

$$\therefore I_C \approx 0.95 \text{ to } 0.98$$

$$\frac{I_C}{I_{BE}}$$

Common Emitter Configuration

Emitter is common for base and collector

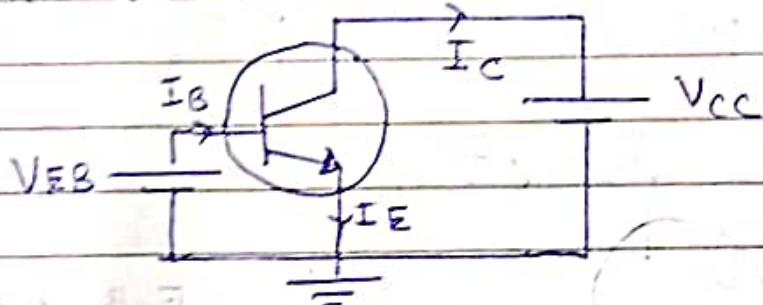

Input current I_B

Input voltage V_{BE} for diff o/p voltage V_{CE}

Output current I_C

Output voltage V_{CE} for diff i/p current I_B

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$



$$\therefore (1-\alpha) I_C = \alpha I_B + I_{CBO}$$

$$I_C = \frac{\alpha}{1-\alpha} I_B + \left(\frac{1}{1-\alpha} I_{CBO} \right) \rightarrow I_{CBO}$$

$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$

$$[I_C = \beta (I_B + I_{CBO}) + I_{CBO}]$$

$$\left\{ \beta = \frac{I_C}{I_B} \right\}$$

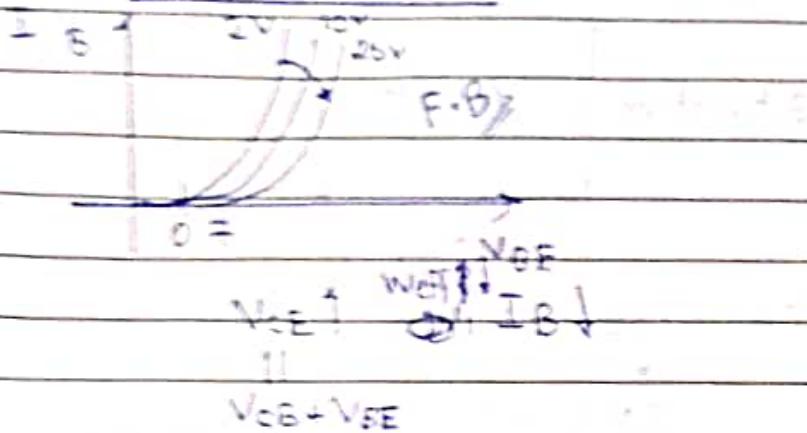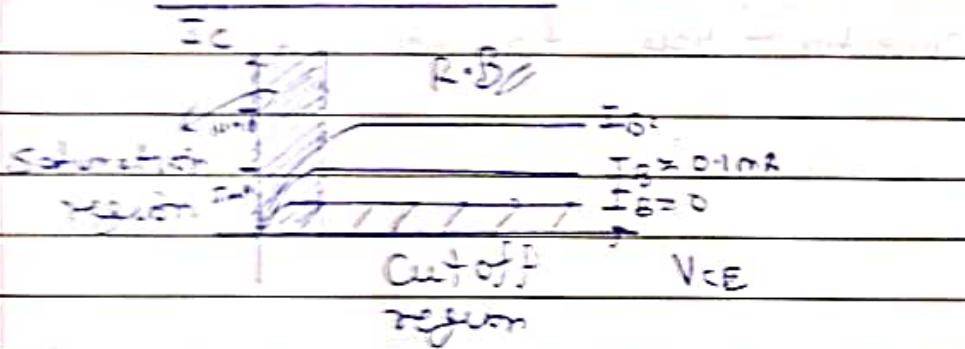i/p characteristicsO/p characteristics

Early effect:


$$V_{CE} = V_{BE} + V_{CB}$$

\downarrow
constant
in forward
bias

depletion width b/w collector & base increases
so base current decreases

Ques: In ~~CB~~ CB configuration i/p characteristic

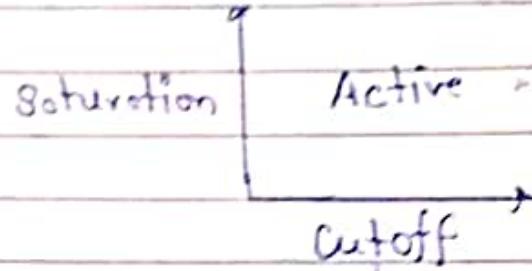I_E vs V_{BE} which was F-B diode characteristic
how will that i/p characteristic vary with
output voltage V_{CE} ? increase or decreases
& why?




$$V_{CE} = V_{BE} + V_{CB}$$

\downarrow
fired (0.7V)

initially $V_{CE} < 0.7V$ at that pt. $V_{CB} < 0$
Collector - base forward bias.


DC Biasing of BJT

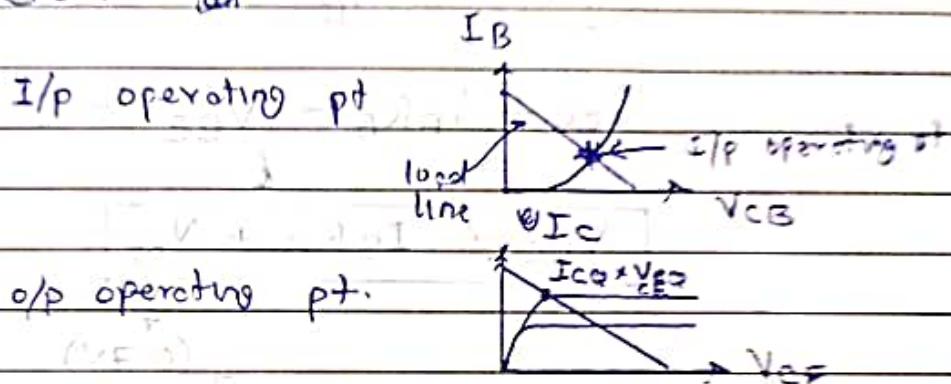
Biasing of the BJT is application of appropriate external DC voltage to establish an operating point of the circuit. When a ~~weak~~ signal is applied to the BJT at this ~~weak~~ operating point then we get an amplified signal at the output. Input operating point is the intersection of load line with the input characteristic of the BJT.



- * Load lines keeps on changing as per V_{CE}
- * operating pt in Active region so that we can amplify the weak AC signal.

Fixed Bias Configuration

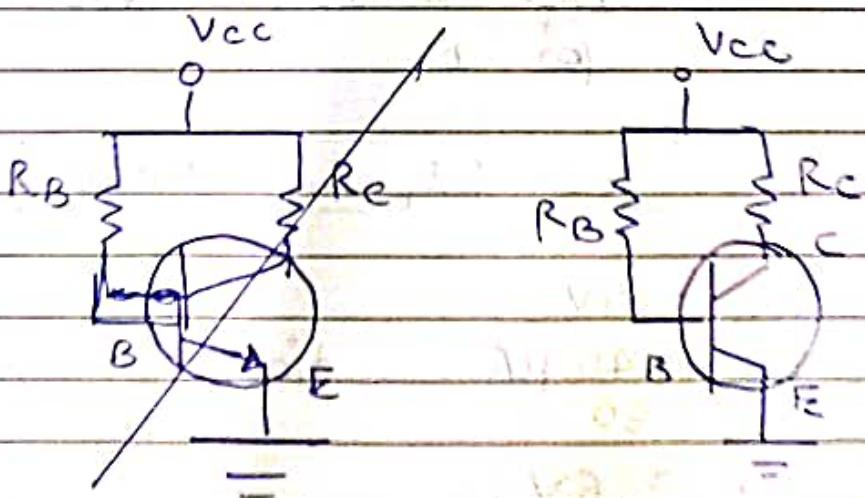

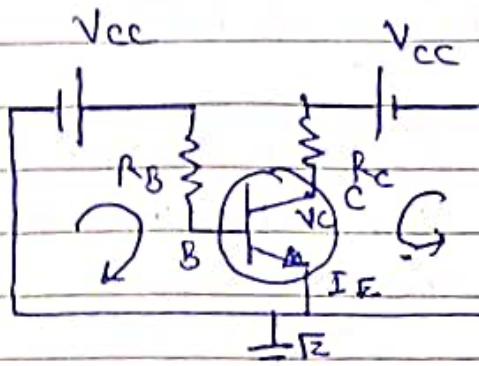

Base emitter \rightarrow i/p ckt

Collector emitter \rightarrow o/p ckt

KVL in i/p ckt

$$V_{cc} - i_B R_B - V_{BE} = 0$$

$$V_{cc} = I_B R_B + V_{BE}$$

(0.7V)

$$I_B = \frac{V_{cc} - V_{BE}}{R_B}$$

$$V_{cc} - i_C R_C - V_{CE} = 0$$

$$V_{cc} - i_C R_C - (V_{CB} + V_{BE}) = 0$$

$$I_C = \beta \cdot I_B \quad V_{CE}$$

$$V_{cc} - \beta I_B \cdot R_C = V_{CE} \varphi$$

let $V_{cc} = 14V$

$$I_B = 40 \mu A$$

$$\beta = 80$$

$$V_{CE} = 6V$$

find I_C, R_C, R_B

$$\& V_C$$

$$\beta = \frac{I_C}{I_E}$$

$$I_C = 85 / 40$$

$$= 2.125 \mu A$$

$$= 3.2 mA$$

$$V_{CE} = I_C R_B - V_{BE} = 0$$

$$14 - (40 \mu A)(V_B) = 0 \Rightarrow V_B = 0.7 V$$

$$R_B = \frac{12.3 V}{40 \mu A} = 320 \Omega \approx 320 \times 10^3 \Omega$$

$$V_{CE} = I_C R_C = V_{CC} = 0$$

$$R_C = \frac{14 - 6 V}{3.2 mA}$$

$$= 2.5 k\Omega$$

$$\text{Q} \quad [V_{CE} = V_C]$$

$$V_{CEQ} = \{V_C = 0\}$$

Reference Books:

- DC biasing is required to establish proper region operation for ac amplification.
- Lower doping of base increases resistance by limiting number of "free" carriers.
- Bipolar $\xrightarrow{\text{electrons}} \xrightarrow{\text{holes}}$ participates in ac charge carriers.
- $I_C = I_{C\text{majority}} + I_{C0}$
 - $I_{C\text{majority}}$ ← minority charge carrier current
 - I_{C0} ← leakage current
- $I_{C\text{sat}}/I_{C0}$ increases rapidly with temperature
- C-B configuration $I_E \rightarrow$ input $I_C \rightarrow$ output
- At cutoff region $I_C = 0$
- At saturation region $V_{CB} = 0$
- $V_{BE} = 0.7V \rightarrow$ constant in active region.
- ΔV_{CB} has negligible effect on I_C

$$\alpha_{dc} = \frac{\Delta I_C}{I_E} \quad |$$

$$I_C = \alpha I_E + I_{C0}$$

$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E} \quad |$$

common
base, short-ckt,
amplification factor
 $V_{CB} = \text{const}$

- In an n-p-n transistor n-p is F-B if p-n is reverse biased. This means transistor has low input resistance and

high output resistance. Thus voltage is amplified since $V = i \times R$ and R_{output} is high.

(Transferring current from low R to high R)

CE-configuration: $\text{BE} \rightarrow \text{FB}$ $I_B \rightarrow \text{input}$
 $\text{CE} \rightarrow \text{RB}$ $I_C \rightarrow \text{output}$

$I_C \neq 0$ when $I_B = 0$

$$I_C = \frac{\alpha I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha} \quad \text{when } I_B = 0$$

$$I_C = \frac{1}{1 - \alpha} I_{CBO} = I_{CEO} \neq 0 \quad \begin{matrix} \text{distortion in} \\ \text{signal} \end{matrix}$$

+ collector current drawn by

For least distortion, $I_C = I_{CEO}$ $\Rightarrow I_B = 0$

$\therefore I_B < 0$ is avoided

cutoff $I_B = 0$ $I_C = I_{CEO}$

$$\beta_{dc} = \frac{I_C}{I_B}$$

$$B_{dc} = \left| \frac{\Delta I_C}{\Delta I_B} \right|$$

$V_{CE} = \text{constant}$

$$\alpha = \frac{\beta}{1 + \beta} \quad \left\{ \begin{matrix} \beta \approx \frac{I_{CEO}}{I_{CBO}} \\ \text{or} \\ \beta = \frac{I_C}{I_B} \end{matrix} \right.$$

$$A_V = \frac{V_L}{V_i}$$


Common collector \rightarrow Input is same for CE & CC configuration

$\{ V_C > V_B \wedge V_B > V_E \}$ Active region condition

$\{ V_B > V_C > V_E \}$ saturation region

$\{ V_B < V_C \wedge V_B < V_E \}$ cut off region

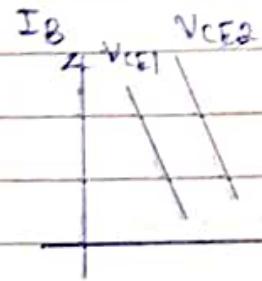BJT \rightarrow current controlled device




$$r = \frac{V_{CE}}{I_c}$$

$$[r = \beta + 1]$$


$$r = \beta + 1 = \frac{1}{1 - \alpha}$$

$\alpha \cdot r = \beta$

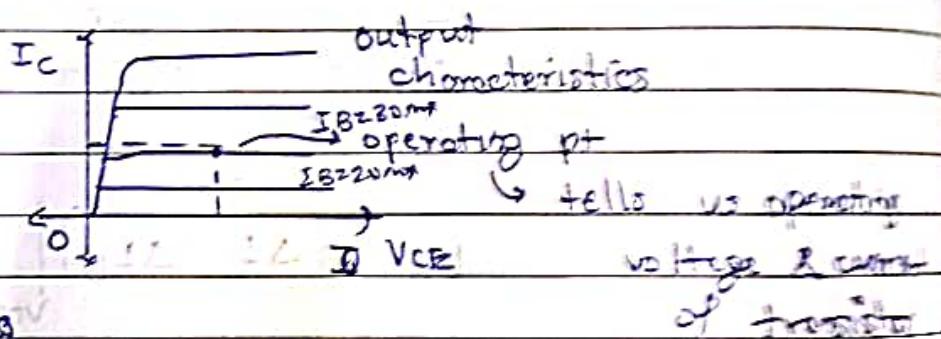operating point / Q-point ← a fixed point on O/P/I/P characteristics of transistor



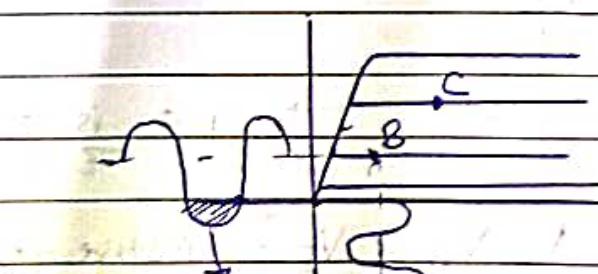Q-point → inside active region for amplification.



At C gain is best for amplifiers

current cannot go below


OA so B point is not suitable

causes non-linear distortion in output waveform

→ Temperature changes B , I_{CBO}

Stability factor (S) prevents change in operation of BJT

$$\frac{V_{CC}}{R_C1/R_C2}$$

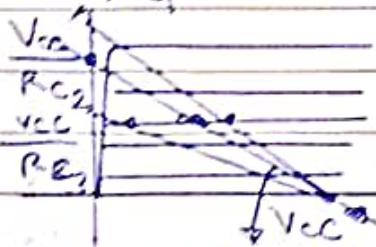

load line

change in this causes
 $(i_B) = \frac{V_{BB} - V_{BE}}{R_B}$ change in Q-point


$$R_{C3} > R_{C2} > R_{C1}$$

As V_{CC} ↑ load line shifts

towards left same for R_{C3}

In fixed bias configuration even if base current is fixed external factor change the Q-point.

with respect to load voltage

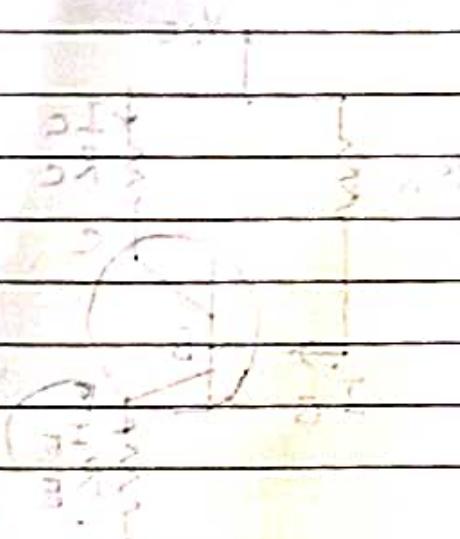


$$V_{CC} = 12V$$

$$R_B = 290k\Omega$$

$$R_C = 2.2k\Omega$$

$$\beta = 50$$

$$I_{CQ}, V_{CEQ}$$

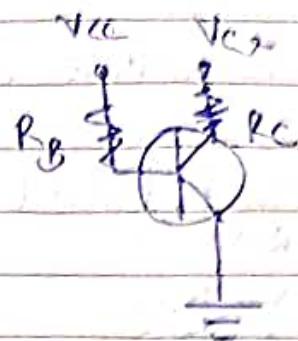

$$V_{CC} - i_B R_B - 0.7 \approx 0$$

$$12 - i_B R_B - 0.7 \approx 0$$

$$i_B R_B \approx 11.3V$$

$$i_B = \frac{11.3}{290k\Omega} \approx 0.047mA$$

$$\beta = \frac{i_C}{i_B}$$

$$i_B$$

$$[i_C \approx 2.35mA]$$


$$V_{CC} - i_C R_C \approx 0$$

$$12 - 0.047mA \times 2.2k\Omega \approx 0$$

Biasing Techniques

- Fixed Bias
- Emitter follower Feedback Bias
- Collector feedback Bias
- Voltage divider bias

Emitter Feedback Bias Configuration

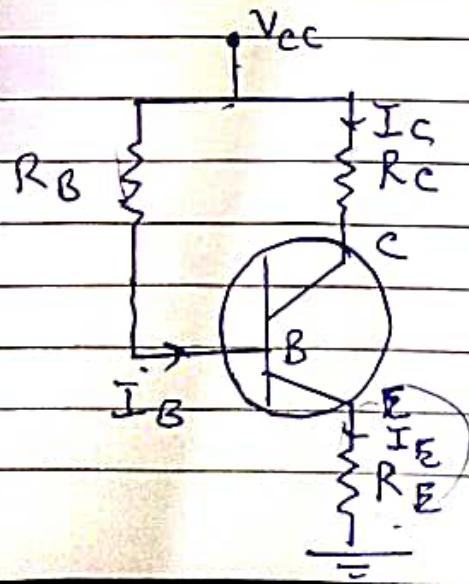

$$V_{cc} - i_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = (\beta + 1) i_B$$

$$V_{cc} - i_B R_B - V_{BE} - (\beta + 1) i_B \cdot R_E = 0$$

~~V_{cc} - i_BR_B~~

$$\boxed{i_B = \frac{V_{cc} - V_{BE}}{R_B + (\beta + 1) R_E}}$$

$$I_C = \beta \times i_B$$

$$V_{cc} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{cc} - \beta i_B R_C -$$

$$(I_C \approx I_E)$$

$$V_{CE} = V_{cc} - I_C (R_E + R_C)$$

$$V_{cc} = 12V$$

$$R_B = 2k\Omega$$

for emitter bias configuration if

$$V_C = 7.6V \quad I_C = 3mA$$

$$V_C = 7.6V$$

$$\textcircled{1} \quad V_E = 2.4V \quad \beta = \frac{I_C}{I_B}$$


$$\beta = 80 \quad I_B = 0.0375$$

Find $R_C, R_B, R_E?$ $i_E = (\beta + 1) i_B = 3.037$

$$V_{cc} - i_B R_B - 0.7 - i_E R_E = 0$$

$$12 - \cancel{0.0375} R_B - 0.7 - \cancel{3.037} R_E = 0$$
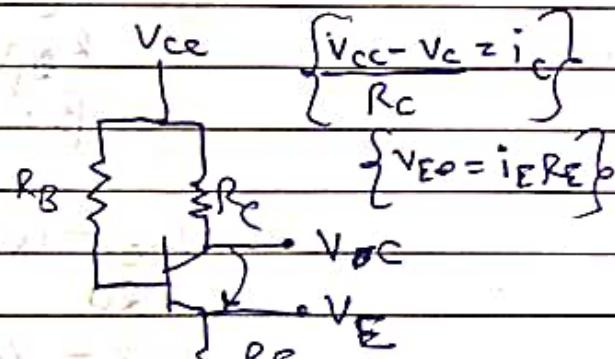
$$0.0375 R_B + 3.037 R_E = 11.3 \quad \text{--- (1)}$$



ii)

$$V_{CC} = R_C i_C = V_{CE} - i_E R_E = 0$$

$$12 - 3R_C - 5.2 - 3.037 R_E = 0$$

$$6.8 = 3R_C + 3.037 R_E \quad \text{--- (2)}$$

$$V_E = i_E R_E$$

$$i_E = 0.8 \quad R_E = 800$$

$$R_E = 800 \text{ k}\Omega \quad 2 \text{ k}\Omega$$

~~1.558 k\Omega~~

$$6.8 = 3R_C + 2.1259$$

$$R_C = 1.558 \text{ k}\Omega \quad 237.6$$

$$[R_B = 237.6 \text{ k}\Omega]$$

~~0.0005 A~~

$$\text{Q) } V_{CC} = 20V$$

$$R_B = 430 \text{ k}\Omega$$

$$R_C = 2 \text{ k}\Omega$$

$$R_E = 1 \text{ k}\Omega$$

$$\beta = 50$$



$$V_{CC} - i_B R_B - 0.7 - i_E R_E = 0$$

~~20~~

$$19.3 = 430 i_B + 5 i_E \quad \text{--- (1)}$$

$$V_{CC} - i_C R_C - V_{CE} - i_E R_E = 0$$



$$20 - 2i_C - V_{CE} - i_E = 0 \quad \text{--- (2)}$$

$$\beta = 50 i_B = i_C \quad \text{--- (3)}$$

$$i_E = 51 - i_B \quad \text{--- (4)}$$

$$\left\{ \begin{array}{l} 19.3 = (430 + s^1) i_B \\ i_B = 0.04 \text{ mA} \\ i_C = 2 \text{ mA} \\ i_E = 2.04 \text{ mA} \end{array} \right.$$

$$V_{CEO} [V_{CE} = 13.96 \text{ V}]$$

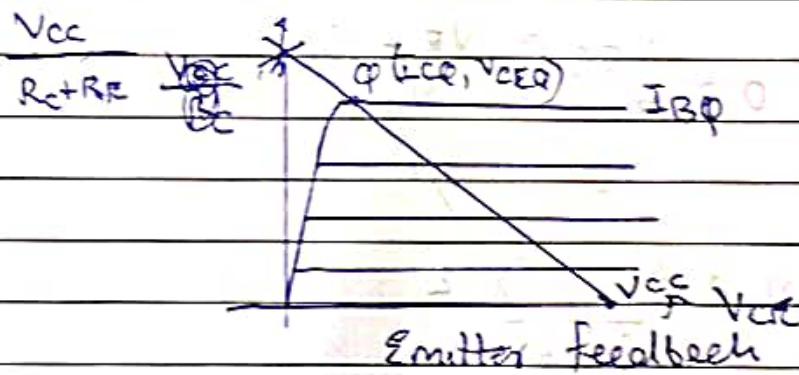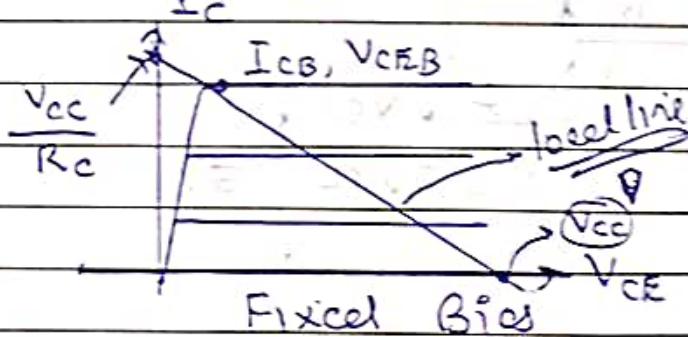

$$I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E} = 1.3 \text{ mA}$$

$$A_{C1} = \frac{V_{CEQ}}{V_{CEQ} - V_{CE}} = 100 \text{ dB}$$

$$F_T = \frac{1}{2\pi f_L C_{EB}}$$

C-BC-E

- Input impedance - $\frac{\Delta V_{EB}}{\Delta I_E}$, V_{EB} is constant $\frac{\Delta V_{EB}}{\Delta I_B}$, I_E is constant
- Output admittance - $\frac{\Delta I_C}{\Delta V_{CB}}$, I_E is constant $\frac{\Delta I_C}{\Delta V_{CE}}$, I_E is constant
- Forward current gain = $\frac{\Delta I_C}{\Delta I_E}$, V_{CB} is constant, $\frac{\Delta I_E}{\Delta I_B}$

Reverse voltage gain $\approx \frac{\Delta V_{EB}}{\Delta V_{CB}}$, I_E is constant $\frac{\Delta V_{EB}}{\Delta V_{CB}}$

$$\alpha = \Delta I_C / \Delta I_E$$

$$\beta = \Delta I_C / \Delta I_B$$

$$\gamma = \Delta I_E / \Delta I_B$$

$$\gamma = \frac{1}{1-\alpha} = \beta + i$$

$$A_V = \frac{V_L}{V_i}$$

$$I'_{CBO} = I_{CBO} 2^{(T_2-T_1)/10}$$

$$V_{CC} = 12V$$

(P)

$$I_C = \beta I_B$$

$$3 = 80 I_B$$

$$I_B = 3/80 mA$$

$$I_E = (\beta + 1) I_B$$

$$I_E = \frac{81 \times 3}{80} = \frac{243}{80} mA$$

$$\beta = 800 \quad I_C = 3mA$$

$$V_E = 7.6V$$

$$0.7V$$

$$\leq$$

$$R_E$$


$$2.4$$

$$\frac{V_E}{I_E} = R_E \quad V_{CC} - 10.7$$

$$\frac{V_{CC} - V_C}{R_C} = R_C$$

$$\frac{i_B}{R_R}$$

Collector Bias or Self Bias

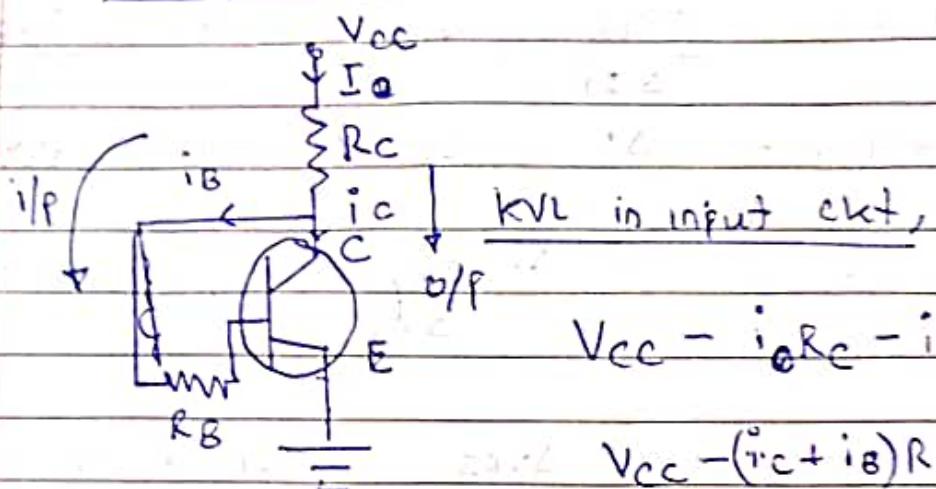

$$V_{CC} = i_C R_C - i_B R_B - V_{CE}$$

$$V_{CC} - (i_C + i_B) R_C - i_B R_B = 0$$

$$V_{CC} - \beta i_B R_C - i_B (R_B + R_C) = 0$$

$$V_{CC} = i_C R_C -$$

$$\text{KVL in output ckt}$$

$$i_B = \frac{V_{CC} - V_{CE}}{R_B + R_C}$$

$$V_{CC} - i_C R_C - V_{CE} = 0$$

$$V_{CC} - i_B R_C - i_B R_C - V_{CE} = 0$$


$$V_{CC} - i_B R_C - \beta i_B R_C - V_{CE} = 0$$

$$\cancel{i_B} = \frac{V_{CC} - V_{CE}}{(\beta + 1) R_C}$$

$$i_C = \beta \left[\frac{V_{CC} - V_{CE}}{R_B + R_C (\beta + 1)} \right]$$

$$V_{CE} = V_{CC} - i_B R_C (\beta + 1)$$

B

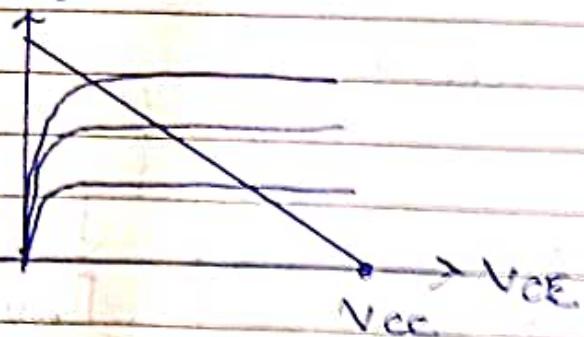

HW

for $V_{CC} = 20V$

Collector bias with
emitter resistor only

$$R_C = 1k\Omega$$

$$R_B = 100k\Omega$$

$$\beta = 100$$

$$R_E = 1k\Omega$$

$$V_{CC} - iR_C - i_B R_B - 0.7 = 0$$

$$20 - \beta(Bi_B + i_B)R_C - i_B R_B - 0.7 = 0$$


$$19.3 = \cancel{100} (100i_B + i_B) + 100i_B$$

$$\boxed{\begin{array}{l} B = 119.3 \text{ mA} \\ \cancel{100} 20 \end{array}}$$

$$i_B = 0.096 \text{ mA}$$

$$i_C = 9.6 \text{ mA}$$

Collector bias with emitter resistor

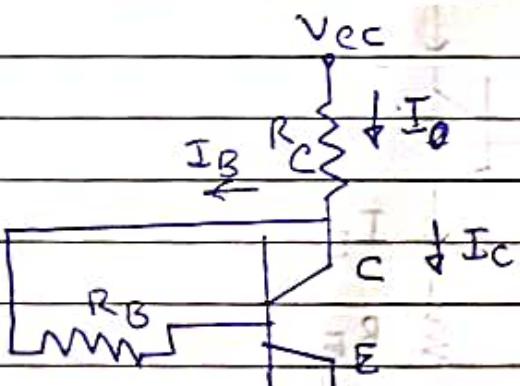

$$V_{CC} - (i_C + i_B)R_C - i_B R_B - V_{BE} - i_E R_E = 0$$

$$V_{CC} - \beta i_B R_C - i_B R_C - i_B R_B - V_{BE} - (\beta + 1)i_B R_E = 0$$

$$= \left[\frac{V_{CC} - V_{BE}}{(\beta + 1)R_C + R_B + (\beta + 1)R_E} \right] = i_B$$

$$i_B = \frac{V_{CC} - V_{BE}}{(\beta + 1)[R_C + R_E] + R_B}$$

$$V_{CC} - (i_C + i_B) R_C - V_{CE} - i_E R_E = 0$$

$$V_{CC} - (\beta i_B + i_B) R_C - (\beta + 1) i_B R_E \approx V_{CE}$$


$$V_{CC} - i_B + (\beta + 1) R_C - (\beta + 1) i_B R_E \approx V_{CE}$$

$$\boxed{V_{CC} - i_B (\beta + 1) (R_C + R_E) \approx V_{CE}}$$

V_{CC}




Voltage divider Bias ckt

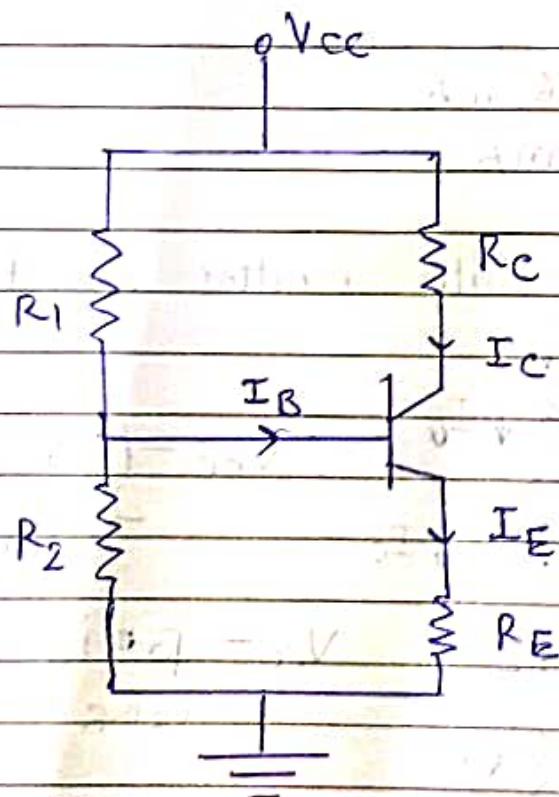

Thevenin equivalent circuit

Thevenin equivalent circuit can be found out for a linear ~~bipolar~~ ~~bipolar~~ bidirectional 2-terminal network by replacing with an equivalent Thevenin circuit consisting of an equivalent voltage source, V_{th} , connected in series with an equivalent resistance, R_{th} , where $V_{th} \rightarrow$ open circuit voltage across the terminals

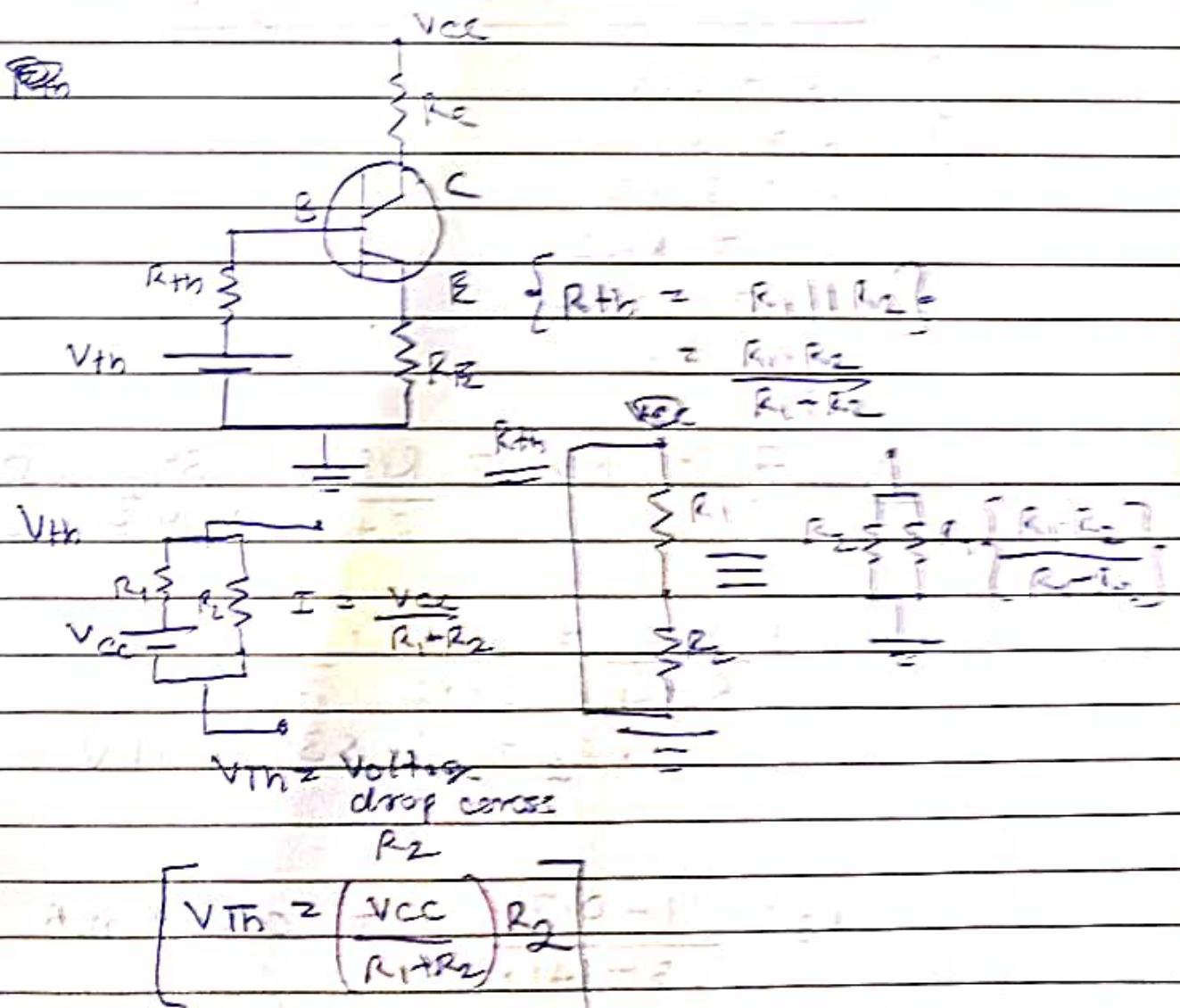$R_{th} \rightarrow$ equivalent resistance when voltage sources are turned off.



$$V_{Th} - i_B R_{Th} - V_{BE} - i_E R_E = 0$$

$$V_{Th} - i_B R_{Th} - V_{BE} - (B+1)i_E R_E = 0$$

$$i_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (B+1)R_E}$$

$$V_{CC} - i_C R_C - V_{CE} - i_E R_E = 0$$

$$V_{CC} - B i_B R_C - (B+1) i_E R_E = V_{CE}$$

$$V_{CE} = V_{CC} - [B R_C + (B+1) R_E] i_E$$

(Q) $V_{CC} = 22V$
 $R_1 = 39k\Omega$
 $R_2 = 39k\Omega$
 $R_C = 10k\Omega$
 $R_E = 1.5k\Omega$
 $B = 140$

$$V_{Th} \approx R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{39 \times 2}{39 + 2} = 19.5 k\Omega$$

$$i = \frac{V_{CC}}{R_1 + R_2} = \frac{22}{39 \times 2} = \frac{11}{39}$$

$$V_{Th} \approx i_C \times R_2 = \frac{11 \times 39}{39} = 11V$$

$$i_B = \frac{11 - 0.7}{19.5 + 141 \times 1.5} = 0.044 mA$$

$$i_C = 6.242 mA \quad i_E = 6.286 mA$$

$$V_{CE} = 3.454V - 48.906V$$

$$[V_{CE} = 6.53V]$$

(P)

$$V_{CC} = 20V$$

~~8.2 k R₁~~R_C 2.7 k

$$-i_R P \leftarrow V_m$$

~~5.2 k R₂~~R_E 1.8 k

$$V_{Th} = i_R R_2 - V_{EE}$$

~~gmp~~

$$V_{EE} = -20V$$

R_{Hb}

of only magnitude?

$$R_{Th} = 1.73 k\Omega$$

$$I_{Th} = V_{CC} / (R_1 + R_2) = 1.92 mA$$

$$V_{Th} = i_{Th} \times R_2 = 4.23V$$




V_{CC}
R_C

$$i_{Th} = 20 + 20 = 3.84 mA$$

$$V_{Th} - i_{Th} R_{Hb} - V_{BE} - i_E R_E = 0$$

$$V_{Th} - V_{BE} = i_B (R_{Hb} + R_E)$$

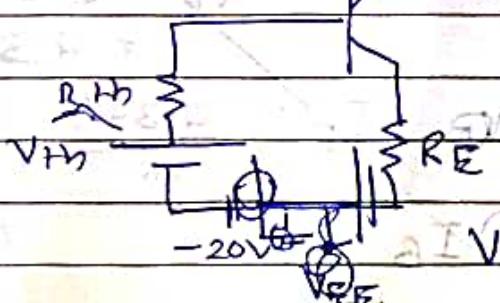


$$V_{Th} = i_{Th} R_2 - V_{EE}$$

$$= 28.46V$$

$$V_{Th} = i_R R_2 - V_{EE}$$

$$= -11.53V$$

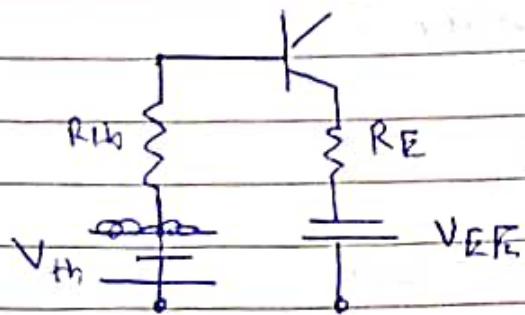


$$V_{TH} - \frac{iR_{BH}}{B} - V_{BE} - \frac{iR_E}{E} + V_{EF} = 0$$

$$i_B = \frac{-V_{TH} - V_{BE} + V_{EF}}{(R_{BH} + (B+1)R_E)}$$

$$= 0.035 \text{ mA}$$

$$i_C = 4.24 \text{ mA}$$

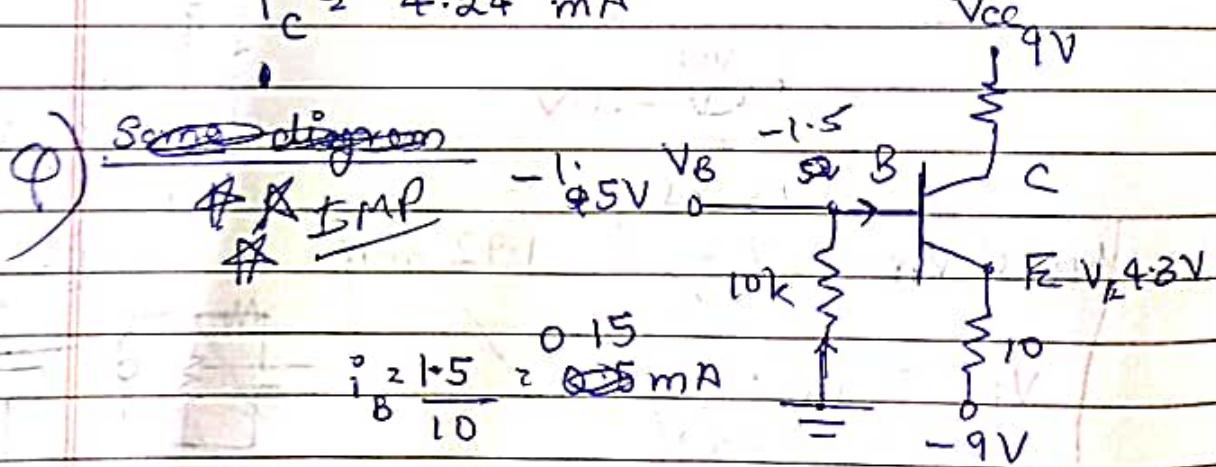

Calculate B

$$V_{BE}^{EB} = V_{BE} - V_{EF}$$

$$V_B + 0.7 = 5 - V_E$$

$$V_E =$$

$$V_{BE} = V_B - V_E$$

$$V_E = 0.7 - 4.3 = -3.6$$

$$V_B = 4.3 + 9 = 13.3$$

~~$$B^2 - I_E = (\beta + 1) I_B$$~~

$$21.33$$

$$\begin{cases} V_{EB} = V_E - V_B \\ 0.7 = V_F + 1.5 \end{cases}$$

$$\begin{aligned} V_{BE} &= V_B - V_E \\ 0.7 &= -1.5 - V_E \end{aligned}$$

$$V_E = -2.2 \text{ V}$$


$$i_E = \frac{-2.2 + 9}{10} = 0.68 \text{ mA}$$

$$\beta \rightarrow (\beta + 1) = \frac{i_E}{I_R}$$

$$[\beta = 3.53]$$

+15V

P)

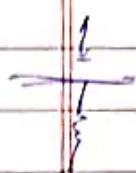


330Ω

B = 20

$$i_C = 4.739$$

$$i_E = 4.76 \text{ mA}$$

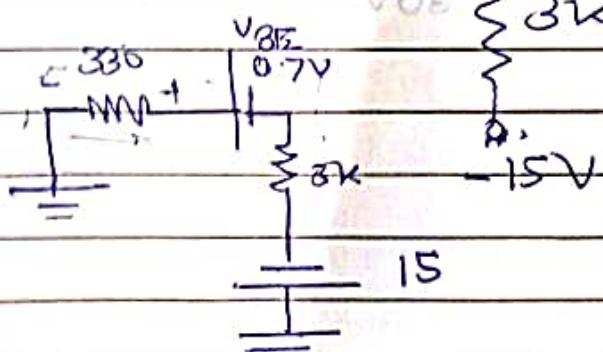


$$\begin{aligned} i_B &= 2.155 \times 10^{-3} \times 10^{-2} \\ &\approx 0.021 \text{ mA} \end{aligned}$$

$$i_B = \frac{14.3}{3000 \times (B+1) + 330}$$


$$-i_B(330) - 0.7 - 3000(B+1)i_B + 15 = 0$$

$$-3300i_B - 0.7 - 3000B + 15 = 0$$

$$i_B = \frac{14.3 - 3000B}{3300}$$

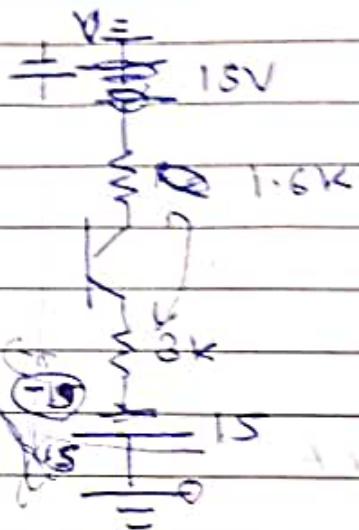
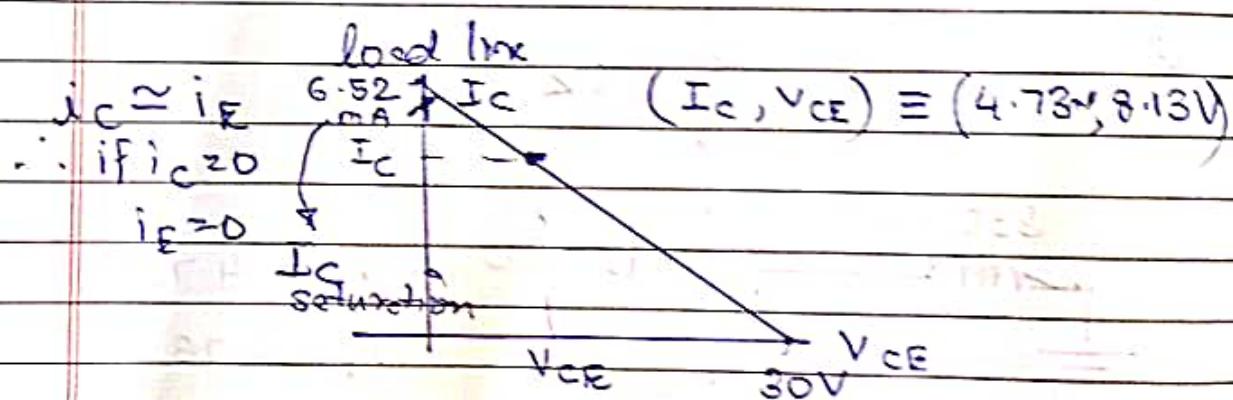
$$15 - 1.6 \times i_C - 3 \times i_E + 15 = V_{CE}$$
 ~~$i_E = 0$~~
 $V_{CE} = 8.13 \text{ V}$




$$i_C = 30$$

$$4.6$$

Boylemester

eg 4.14)

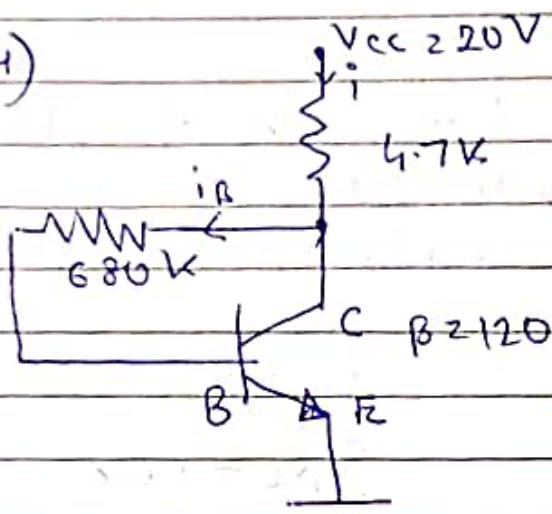

$$V_{CC} - i(4.7) - i_B(680) - V_{BE} = 0$$


$$V_{BE} \approx 0.7 \text{ V}$$

$$V_{CC} - (i_B + \beta i_B)^{(4.7)} - i_B(680) - 0.7 = 0$$

$$i_B = \frac{V_{CC} - 0.7}{4.7(1+\beta) + 680} = 0.015 \text{ mA}$$

$$i_C = 1.8 \text{ mA}$$

4.15)

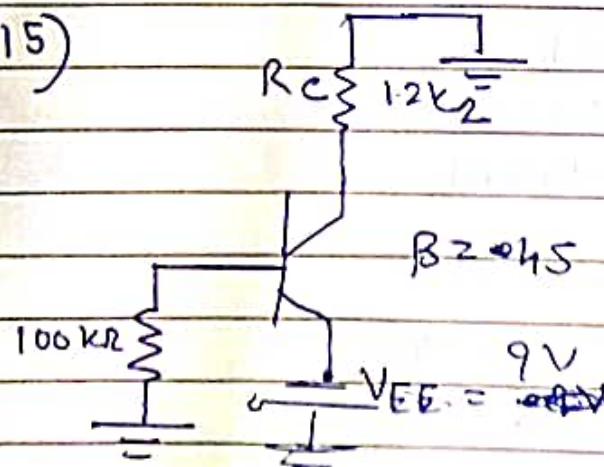

$$-100 \text{ k}\Omega \parallel 100 \text{ pF} + 37 \text{ V}$$

$$100 \text{ pF} = 33 \text{ }\mu\text{F}$$

$$100 \text{ pF} \parallel 33 \text{ }\mu\text{F}$$

$$100 \text{ pF} \parallel 33 \text{ }\mu\text{F}$$

$$100 \text{ pF} \parallel 33 \text{ }\mu\text{F}$$

$$-20 \text{ k}\Omega \parallel -100 \text{ pF} = V_{C2} + 37 \text{ V}$$


$$9 - 3733/137 \cdot V_{C2} = 4518 \text{ V}$$

$$V_{C2} = V_{C1} = 4518 \text{ V}$$

$$V_{C2} = 4518 \text{ V}$$

$$V_{C2} = 4518 \text{ V}$$

Q3 (4.15)

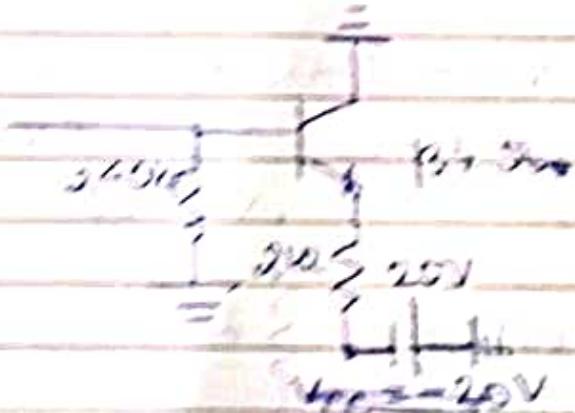

$$-10,1240 - V_{C2} = 0.12 \cdot 20 + 0$$


$$i_2 = \frac{0.12 - 120}{200 + (R_1 + R_2)} = 0.006 \text{ mA}$$

$$i_2 = 0.006 \text{ mA}$$

$$i_{C2} = 0.006 \text{ mA}$$

$$-V_{C2} = 0.12 + 20 + 0$$

$$0.006 \cdot 120 = 14.42 \text{ V}$$

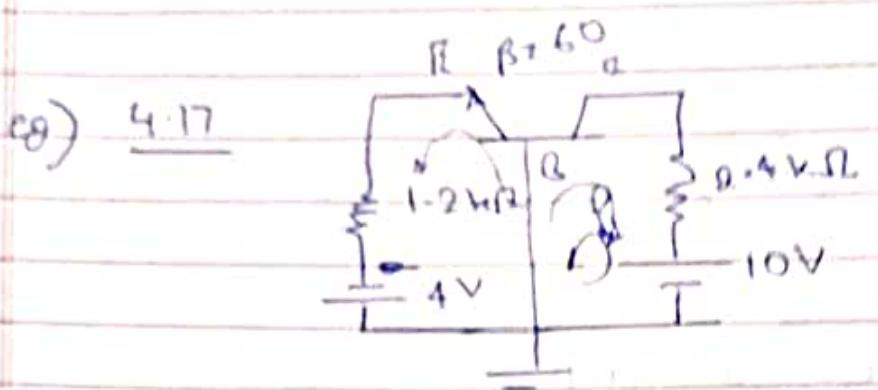

$$V_{BE} - V_{BE} = 1.2i_E + 4 = 0$$

$$\frac{3.3}{1.2} \approx i_E = 0.275 \text{ mA}$$

$$i_E = 2.75 \text{ mA}$$


$$i_B = \frac{i_E}{(\beta + 1)} = 0.045 \text{ mA}$$

$$i_C = 2.704 \text{ mA}$$

$$- V_{CB} - 2.4i_C + 10 = 0$$


$$- V_{CB} \approx - 3.5 \text{ V}$$

eg 4.18

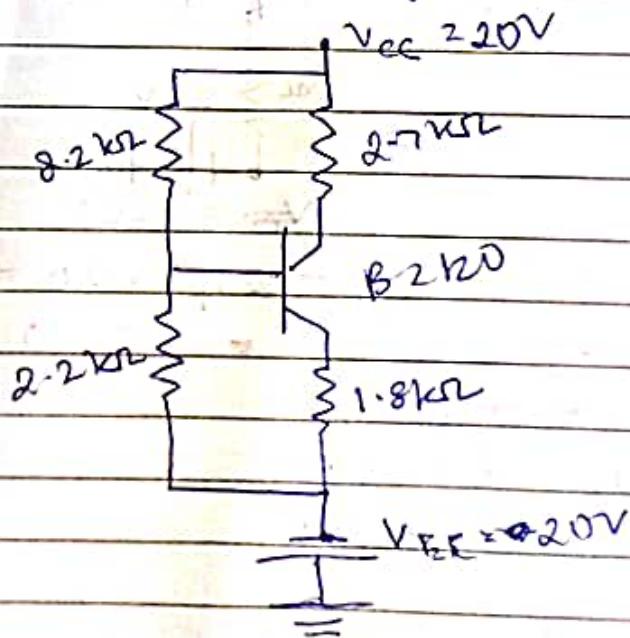

for FEV should be to minimize

$$R_M = 1.73 \Omega$$

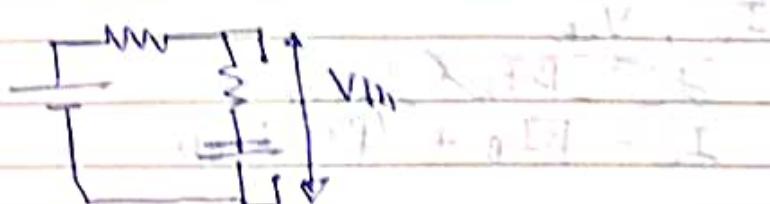

$$V_{CC} - i(8.2 + 2.2) + 2.0 = 0 \text{ for collector}$$

$$\text{Derivative } 40 = 3.84 \text{ mA } V_{CE} \text{ right now}$$

so $V_{CE} = 8.2 + 2.2 = 10 \text{ VDC} \text{ from eqn}$

$$\text{Derivative } 2.0 \text{ } V_{RE} = i_E(2.2) + 2.0 = 0 \text{ remains eqn}$$

$$\text{Derivative } 2.0 = V_{RE} = -11.55 \text{ VDC } \text{ so current is}$$

therefore it is around V_{CC} half solution removed

$$\text{so current in } 2.2 \text{ k} \text{ is } 9.98 \text{ mA}$$

$$V_{CE} = 11.55 - 2.2i_B - V_{BE} - 1.8i_E + 2.0$$

$$11.55 - 2.2 \times 0.035 - 0.7 & 2.2 + (\beta+1) 1.8 = i_E$$

$$i_B = 0.035 \text{ mA}$$

$$i_E = 4.92 \text{ mA}$$

$$i_F = 4.26 \text{ mA}$$

$$\text{saturation} = 8.38 \text{ V}$$

$$V_{CC} - i_C(2.7) - V_{BE} - 1.8i_E + 2.0 = 0$$

$$40 - i_C(2.7) - 0.7 - 1.8i_E = V_{CE}$$

$$\text{saturation} = 1.9 \text{ VDC}$$

$$V_{CC} = 20.938 \text{ V}$$



saturation 8.38 V
is available in form

Stabilization of DC biasing BJT ckt

I_c, V_{CE}

$$(I_c = B I_B + I_{CBO})$$

$$I_c = B I_B + (B+1) I_{CBO}$$

Flow of collector current I_c produces heat and this will increase the temperature of the circuit. With the increase in temperature the reverse saturation current I_{CBO} increases. This forms a chain reaction. The circuit becomes unstable. This is also known as the runaway. With increase in temperature V_{BE} & B also varies.

If $V_{BE} \uparrow$ varies $I_B \uparrow$ B changes by Temp. Stability factor is rate of change of collector current I_c wrt ΔI_{CBO} & constant V_{BE} & B .

$$S = \frac{\partial I_c}{\partial I_{CBO}}$$

$V_{BE}, B \Rightarrow$ constants

$$S' = \frac{\partial I_c}{\partial \Delta V_{BE}}$$

$B, I_{CBO} \Rightarrow$ constant

$$S'' \approx \frac{\partial I_c}{\partial B}$$

$V_{BE}, I_{CBO} \Rightarrow$ constant

very complex
not in syllabus

Fixed bias

and bias

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + R_E}$$

$$\therefore I_C = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right) + (\beta + 1) I_{CBO}$$

$$S = \frac{\partial I_C}{\partial I_{CBO}} = \frac{\beta}{\beta + 1}$$

Emitter bias, Collector bias, Fixed bias

$$i_B = \frac{V_{CE} - V_{BE}}{R_B + (\beta + 1) R_E} \quad i_B = \frac{V_{CE} - V_{BE}}{R_B + (\beta + 1) R_C}$$

$$S = \frac{\beta i_B + (\beta + 1) i_{CBO}}{\partial I_{CBO}}$$

$$S = \frac{\beta (V_{CC} - V_{BE}) + (\beta + 1) I_{CBO}}{R_B + (\beta + 1) R_C}$$

Voltage divider bias

$$i_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E}$$

$$S = \frac{\beta i_B + (\beta + 1) i_{CBO}}{\partial i_{CBO}}$$

$$S = \frac{\beta I_B (1 + \beta)}{R_{TH} + (\beta + 1) R_E} = \frac{\beta + 1}{\beta + 1 + R_E / R_{TH}}$$

Fixed bias

$$S' = \frac{\partial I_C}{\partial V_{BE}} = -\frac{\beta}{R_B}$$

• Emitter bias

$$S' = \frac{\partial I_C}{\partial V_{BE}} = \frac{-\beta}{R_B + (\beta+1)R_E}$$

X ∫ can't directly
use formula

Collector bias

$$S' = \frac{\partial I_C}{\partial V_{BE}} = -\frac{\beta}{R_B + (\beta+1)R_C}$$

Voltage divider bias

$$S' = \frac{\partial I_C}{\partial V_{BE}} \rightarrow -\frac{\beta}{R_{th} + (\beta+1)R_E}$$

Emitter bias

$$I_C = \beta I_B + (B+1) I_{CBO}$$

$$I_B = \frac{V_{CC} - V_{BE} - I_C R_E}{R_B + R_E} \quad (I_C \approx I_E)$$

$$I_C = \beta I_B + I_{CBO} (B+1)$$

$$\frac{\partial I_C}{\partial I_C} = \frac{\beta}{R_B + R_E} \frac{\partial}{\partial V_{BE}} \left(\frac{V_{CC} - V_{BE} - I_C R_E}{R_B + R_E} \right) + 0$$

$$I = \frac{B}{R_E + R_B} \frac{(-R_E) + (B+1)}{S}$$

$$S = \frac{B+1}{1 + \frac{B R_E}{R_B + R_E}}$$

Collector Loop

$$V_{CE} - V_{BE} = \beta (I_C - I_S)$$

$$V_{CE} - (I_C + I_S) R_E - \beta I_C R_E - V_{BE} = 0$$

$$\beta I_C^2 - V_{CE} - V_{BE} - \frac{\beta I_C R_E}{R_E + R_B} = 0$$

$$I_C = \frac{\beta (V_{CE} - V_{BE} - I_S R_E) + (B+1) I_{DSS}}{R_E + R_B}$$

$$I_C = \frac{\beta I_S}{\beta R_E + R_B} \frac{(-R_E) + (B+1) - 1}{S}$$

blocking current $I_S = \frac{\beta I_D}{\beta R_E + R_B}$

$$S = \frac{\beta + 1}{1 + \frac{\beta R_E}{R_B + R_E}}$$

$$I_C = \frac{(V_{CE} - V_{BE} - I_S R_E) + (B+1) I_{DSS}}{R_B + R_E} = \frac{(V_{CE} - V_{BE} - I_S R_E) + (B+1) I_{DSS}}{R_B + R_E}$$

S' (for saturation)

~~$\rightarrow (B+1) I_{DSS}$~~ ON

$$I_C = \frac{V_{CE} - V_{BE} - I_S R_E + (B+1) I_{DSS}}{R_B + R_E + R_E} = S' = -R_E B$$

$$S' = \frac{B}{R_B + R_E + R_E} \frac{(-R_E) + (B+1) I_{DSS}}{S} = \frac{B R_E - B R_E}{B R_E + B R_E} = 1$$

$$\left\{ \begin{array}{l} S' = \frac{1}{R_B + R_E} \\ \quad \quad \quad \end{array} \right.$$

$$I = \frac{\beta}{R_B + R_E} \left(0 - \frac{1/S'}{1/S' + 1} - R_E \right) + 0$$

$$R_B + R_E = -\frac{\beta S'}{S' + 1} = R_E \beta$$

$$R_E (\beta + 1) + R_B = -\beta \frac{1}{S'}$$

$$\left\{ \begin{array}{l} S' = -\frac{\beta}{R_E (\beta + 1) + R_B} \\ \quad \quad \quad \end{array} \right.$$

Collector bias

$$V_C = \frac{(-\beta + 1)}{2} \cdot 16 = -6$$

Q) Why do we include emitter feedback resistance in our ckt?

→ stability S' with respect to V_{BE} is equal to $-\frac{1}{(R_E(\beta+1)+R_B)}$.

design the ckt such that emitter res R_E is much greater than R_B . Then S' can be approximated as $-\beta$.

$$1 - \frac{1}{(R_E(\beta+1)+R_B)} \approx 1 - \frac{1}{\beta R_E} = \frac{1}{\beta+1} R_E$$

Further approximation of $B+1 \approx B$ make the stability
 $\Rightarrow \frac{V_{BE}}{R_E}$: Thus the ckt. becomes stable

with respect to V_{BE} with change in temperature.

Stability of system is measure of sensitivity of
 a network to variation in parameters.


$$B \uparrow T \uparrow$$

$$V_{BE} + T \uparrow$$

$$I_{CBO} + T \uparrow$$

~~Practise~~

Fixed Bias

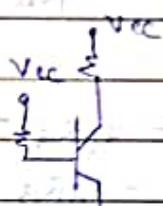

$$\frac{V_{CC} - V_{BE}}{RB} = I_c = B i_B + (B+1) i_{CBO}$$

$$I_c = B i_B + (B+1) i_{CBO}$$


$$I_c = B i_B + (B+1) \frac{i_{CBO}}{B+1}$$

$$I_c = B i_B + (B+1)$$

$$I_c = B i_B + (B+1)$$

$$I_c = B i_B + (B+1)$$

Emitter bias

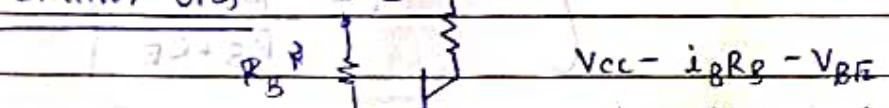

$$V_{CC} - i_B R_B - V_{BE} - i_C R_E = 0$$

$$V_{CC} - V_{BE} = i_B R_B - i_C R_E$$

$$V_{CC} - V_{BE} = i_B R_B - i_C R_E$$

$$V_{CC} - V_{BE} = i_B R_B - i_C R_E$$

$$i_C = \frac{\beta}{R_B} (V_{CC} - V_{BE} + i_C R_E) \rightarrow (\beta+1) i_C R_B$$

$$I = -\frac{\beta}{R_B} (R_E) + (\beta+1) \frac{1}{S}$$

$$R_B = -\beta R_E + \frac{R_B(\beta+1)}{S}$$

$$R_B = \frac{\beta R_E}{S} + \frac{R_B(\beta+1)}{S}$$

$$S > \frac{R_B(\beta+1)}{R_B - \beta R_E}$$

$$\textcircled{X} \quad \Rightarrow \quad \frac{\beta+1}{1 - \frac{\beta R_E}{R_B}}$$

$$V_{CC} - V_{BE} - I_B R_E = -(\beta+1) I_B R_E = 0$$

$$V_{CC} - V_{BE} - I_B R_E - I_B R_E - \beta I_C R_E = 0$$

$$i_E = \frac{1}{R_E + R_B} (V_{CC} - V_{BE} - I_C R_E)$$

$$i_E = \frac{\beta}{R_E + R_B} (V_{CC} - V_{BE} - i_C R_E) + \beta i_C R_E (\beta+1)$$

$$I = \frac{\beta}{R_E + R_B} (-R_E) + \frac{\beta+1}{S}$$

$$1 + \frac{\beta R_E}{R_E + R_B} = \frac{\beta+1}{S}$$

$$\left\{ \begin{array}{l} S > \frac{\beta+1}{1 + \frac{\beta R_E}{R_E + R_B}} \\ 1 + \frac{\beta R_E}{R_E + R_B} \end{array} \right\}$$

level one
one

$$= \frac{P_0}{P_0 + P_1}$$

$$= \frac{P_0}{P_0 + P_1}$$

P_0

$$(P_0) \left(1 + \frac{P_1}{P_0} \right)$$

$$\left[\frac{P_0 + P_1}{P_0} = 1 + \frac{P_1}{P_0} \right]$$

P_0 in multiplying
 P_0

$$(P_0) \left(1 + \frac{P_1}{P_0} \right) = 3.1$$

$$P_0 / P_1$$

$$P_0 = 11$$

P_1

$$3.1 - 11 = -8$$

{ lowest
level }

$$11 - 8 = 3$$

$$11 - 3 = \frac{8}{8} = \frac{1}{1}$$

$$8 - 3 = \frac{5}{5} = \frac{1}{1}$$

$$5 - 3 = 2$$

$$2 - 2 = 0$$

$$\frac{0}{0} = 1$$

Molt imp

$$S = \frac{\partial I_c}{\partial I_{cBO}}$$

$$S' = \frac{\partial I_c}{\partial V_{BE}}$$

$$\beta'' = \frac{\partial I_c}{\partial I_B}$$

Fixed
Bias

$$\beta + 1$$

$$-\beta / R_B$$

Emitter
Bias

$$\frac{(\beta+1)(R_B + R_E)}{R_B + (\beta+1)R_E}$$

$$-\frac{\beta}{R_B + (\beta+1)R_E}$$

Collector
Bias

$$\frac{(\beta+1)(R_B + R_C)}{R_B + (\beta+1)R_C}$$

$$-\frac{\beta}{R_B + (\beta+1)R_C}$$

Voltage
Divided
Bias

$$\frac{(\beta+1)(R_{Th} + R_E)}{R_{Th} + (\beta+1)R_E}$$

$$-\frac{\beta}{R_{Th} + (\beta+1)R_E}$$

General form

$$I_c = (\beta+1) I_{cBO} + \beta I_B$$

$$\frac{\partial I_c}{\partial I_c} = \beta \frac{\partial I_B}{\partial I_c} + (\beta+1) \frac{\partial I_{cBO}}{\partial I_c}$$

$$1 = \beta \frac{\partial I_B}{\partial I_c} + (\beta+1) \frac{1}{8}$$

$$S = \frac{\beta+1}{1 - \beta \frac{\partial I_B}{\partial I_c}}$$

(Q) For an emitter feedback ckt if $V_{cc} = 10V$, $R_c = 1.5k$, $R_B = 270k$, $R_E = 1k$ and $\beta = 50$. Find the operating point and the stability factor S of the ckt.

$$V_{cc} - i_B R_B - V_{BE} - R_E (\beta + 1) i_B = 0$$

$$i_B = \frac{V_{cc} - V_{BE}}{R_B + (\beta + 1) R_E} = 0.028 \text{ mA}$$

$$R_E = 10k \quad i_B = 0.028 \text{ mA}$$

$$i_C = 1.448 \text{ mA}$$

$$i_E = 1.476 \text{ mA}$$

$$V_{cc} - i_C R_c - V_{CE} - i_E R_E \approx 0$$

$$V_{CEQ} = 6.352 \text{ V}$$

$$Q \equiv (1.448 \text{ mA}, 6.352 \text{ V}, 1.448 \text{ mA})$$

$$S = \frac{(\beta + 1)(R_B + R_E)}{R_B + (\beta + 1) R_E}$$

$$= 43.05$$

$$(1 + \beta + R_E)(1 + \beta) = 3$$


(Q) A voltage divider bias ckt is to be designed for stability ($S \geq 12$) if supply voltage is 16V

$\therefore R_c = 1.5k$, $\beta = 50$. The germanium transistor is to be used having $V_{BE} = 0.2V$


The ckt has an operating point $V_{CE} = 8V$ and $i_C = 48 \text{ mA}$. Design the ckt.

$$16V - 8V = 18V$$

$$\{ 52 \times 0.5 = 11.9 \}$$

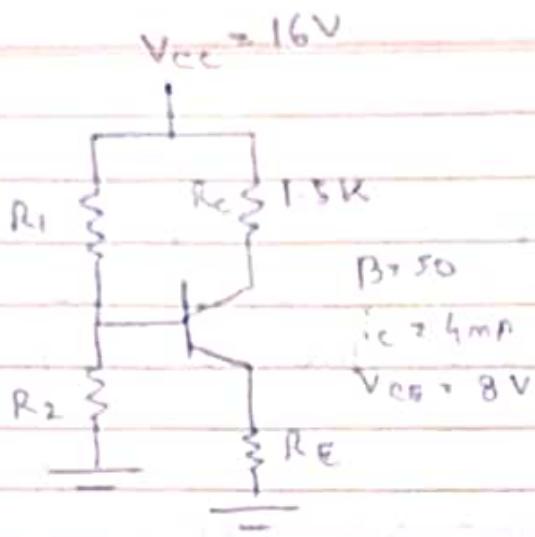

$$R_{th} = R_1 \parallel R_2$$

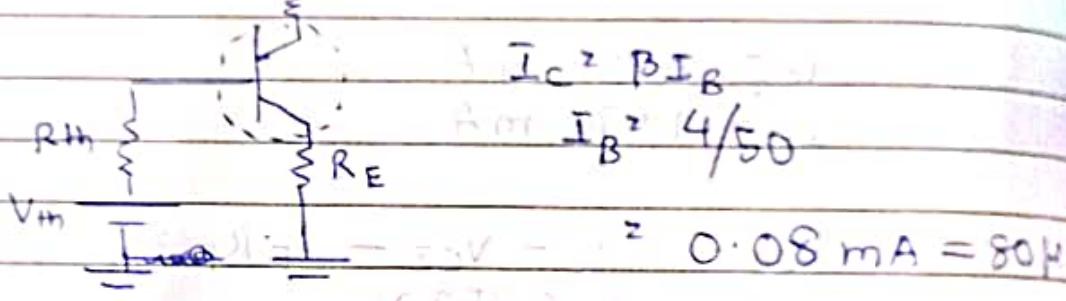

$$I_E = 0.08 + 4$$

$$= 4.08 \text{ mA}$$

$$V_{cc} - i_c R_c - (V_{ce} - i_E R_E) = 0$$

$$16 - V_{ce} - R_E = 0.49 \text{ k}\Omega$$

$$S = (\beta + 1)(R_{th} + R_E)$$

$$12 = 51 \left(R_{th} + 0.49 \right)$$

$$R_{th} + 51 = 24.99$$

$$299.8 + 12 R_{th} = 51 R_{th} + 24.99$$

$$274.81 = 39 R_{th}$$

$$\{ R_{th} = 7.046 \Omega \}$$



$$R_1 R_2 = 7.046 \quad \text{---} \quad (1)$$

$$R_1 + R_2$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{7.046} \quad (1)$$

$$V_{Th} - \frac{iR_{Th}}{B} - V_{BE} - iEPE = 0$$
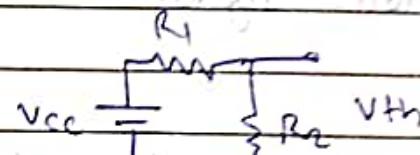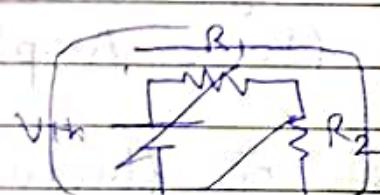
$$V_{Th} = 2.76 \text{ } \Omega \text{ } V$$



$$V_{Th} = \left(\frac{V_{cc}^2}{R_1 + R_2} \right) \cdot R_2$$

$$2.76 = \frac{16R_2}{R_1 + R_2}$$

$$2.76 = \frac{16R_2}{R_1 + R_2} \quad | \cdot (R_1 + R_2)$$

$$2.76(R_1 + R_2) = 16R_2 \quad | : 2.76$$

$$R_1 + R_2 = 4.79 R_2$$

$$\frac{(4.79) R_2}{(4.76 + 1) R_2} = 7.046$$

$$(4.76 + 1) R_2$$

$$R_2 = \frac{7.046 \times 5.76}{4.79}$$

$$= 8.47 \Omega$$

$$R_1 = 40.58 \Omega$$

Small Signal Analysis

In small signal analysis of BJT we find AC response of the transistor using different models.

Hybrid Model

P_e model

→ Two types of analysis are :


(1) Small signal

(2) Large signal

(Power Amplifier)

→ In small signal analysis the fluctuation in source voltage V_S is small so the base current will not change much and there won't be much change in collector current I_C . So operating point i_0 will not shift.

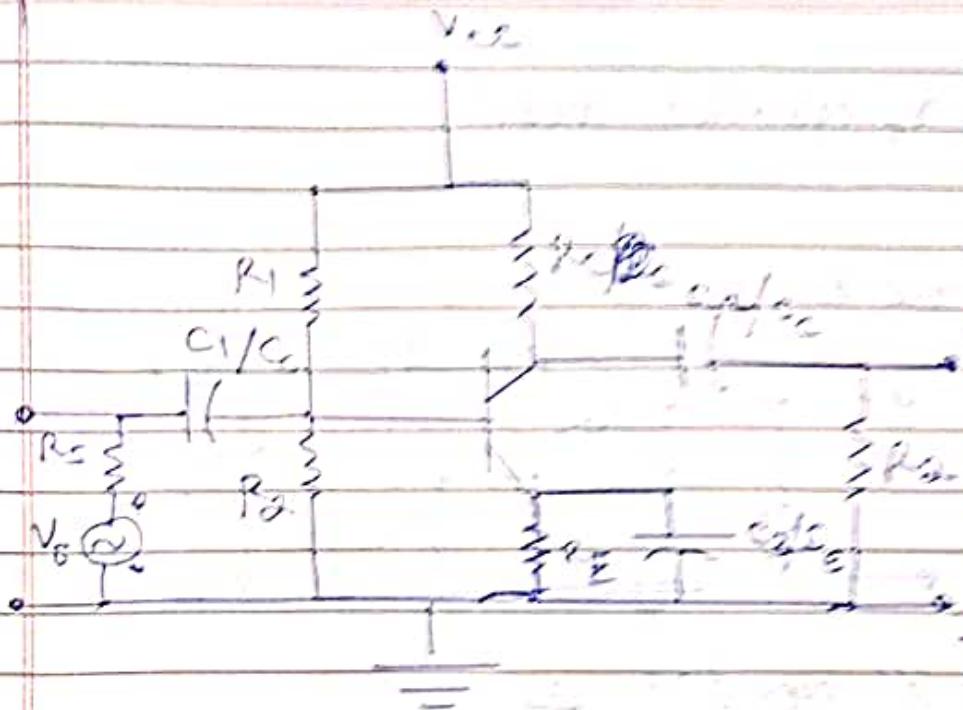Small signal analysis means the AC signal is sufficiently small to keep the region of operation in active region of the transistor where the transistor behaves like an amplifier.



C_1 , C_2 & C_3 capacitors are short circuit for AC signal and open circuit for DC signal.

$$f_{X_C} = \frac{1}{2\pi f C}$$

in de $f = 0$:

$$\text{so } X_C = \infty$$

so open circ

in ac $f = \text{large value}$

so $X_C = \text{small}$

so direct \Rightarrow

\Rightarrow short circ

C_1 and C_2 are known as coupling capacitors while C_3 is known as emitter bypass capacitor.


To find the AC response of the circuit:

Steps-


- 1) Draw the AC equivalent circuit by removing all DC sources
- 2) Short all the capacitors
- 3) Re-draw the circuit with elements removed (h-parameter)
- 4) Replace the transistor with hybrid equivalent model [OR]

b) π equivalent model

i) i) Remove the dc source

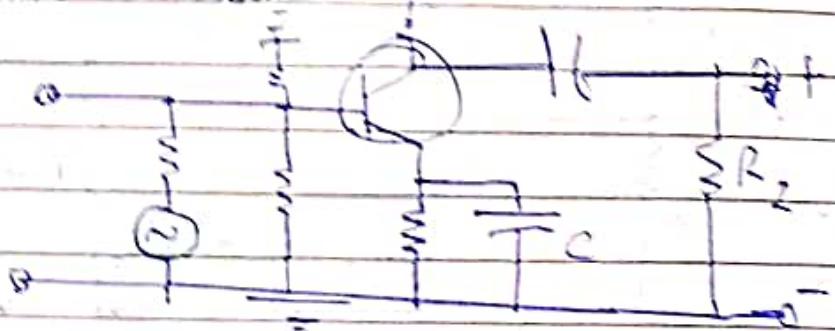


ii) Short all capacitors

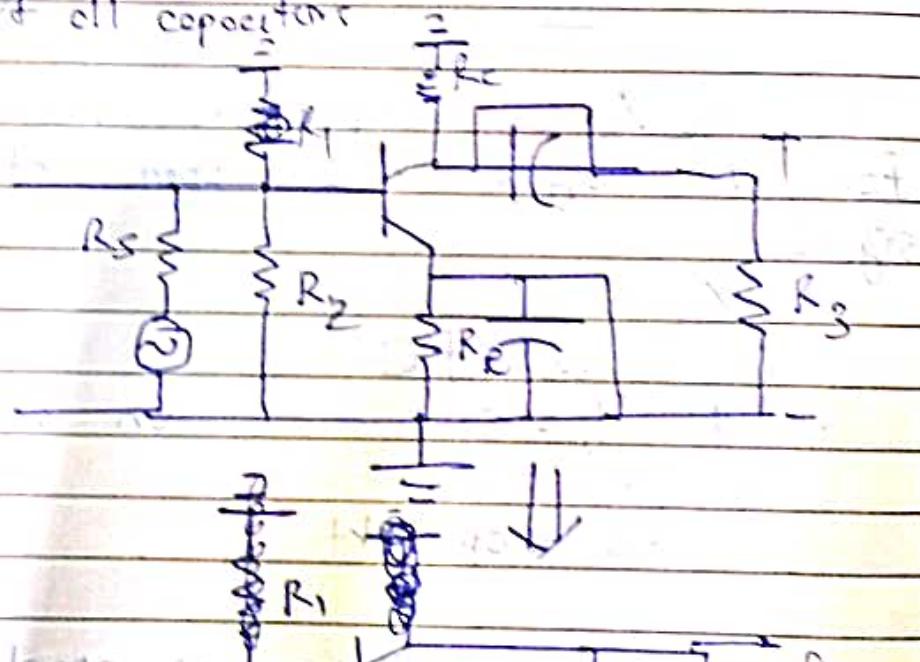

$$m_{AB} = \beta$$

$$m_{AC} = \alpha$$


$$m_{BC} = \gamma$$

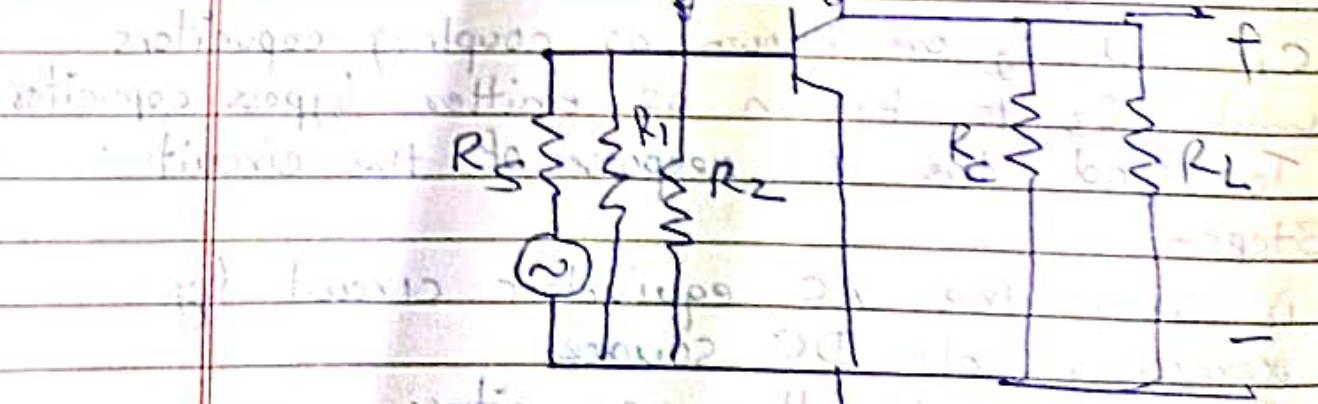

(returning)

Kelvin's bridge that rotates with angle θ (left)


$$R_{AC} = R_C \parallel R_L$$

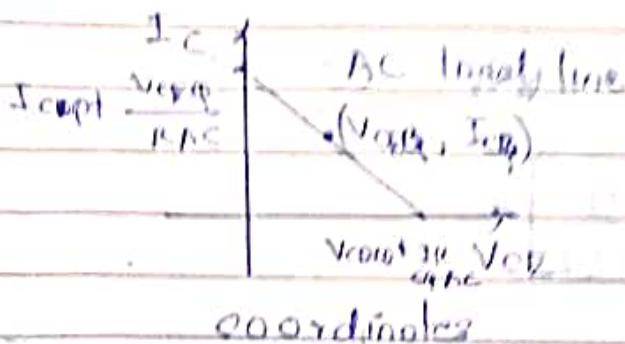

(ii)

Hybrid Model

Calculation of n-parameters

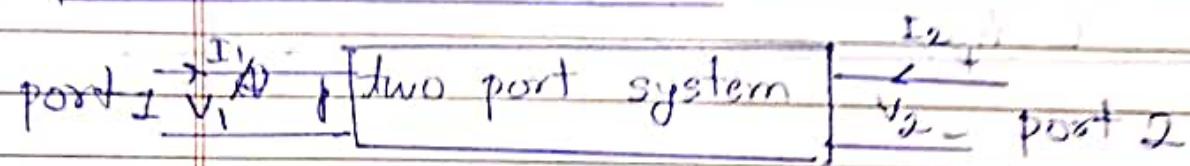

For analysis

two terminals together V_1 and I_2 are independent parameters

and terminals I_1 and V_2 are independent parameters

substituting

$$I_2 = f_1(V_2, I_2)$$

$$V_{21} = f_2(V_2, I_2)$$

(iii) substitution

The small change in V_1 ,

$$\frac{dV_1}{dI_1} = \frac{\partial V_1}{\partial I_1} \cdot \frac{\partial I_1}{\partial I_2} \cdot \frac{\partial I_2}{\partial I_1}$$

also it is given $\frac{\partial V_1}{\partial I_1} = \frac{\partial V_1}{\partial I_1} + \frac{\partial V_1}{\partial I_2} \frac{\partial I_2}{\partial I_1}$

so $\frac{dV_1}{dI_1} = \frac{\partial V_1}{\partial I_1} + \frac{\partial V_1}{\partial I_2} \frac{\partial I_2}{\partial I_1}$

$$i_2 (1 + h_o R_L) = h_f i_1$$

$$\frac{i_2}{i_1} = \frac{h_f}{1 + h_o R_L}$$

$$[A_i^o = \frac{-i_2}{i_1} = \frac{-h_f}{1 + h_o R_L}]$$

~~$$v_1 = h_{ii} + h_r v_2$$~~

$$v_1 = h_{ii} - h_r (i_2 R_L)$$

~~$$Z_i^o = \frac{v_1}{i_1}$$~~

~~$$v_1 = h_{ii} + h_r v_2$$~~

$$= h_{ii} - h_r i_2 R_L$$

$$Z_i^o = h_i^o - h_r R_L \left(\frac{i_2}{i_1} \right)$$

$$Z_i^o = h_i^o + h_r R_L \left(A_i^o \right)$$

$$\left\{ Z_i^o = h_i^o - \frac{h_r h_f}{h_o + 1/R_L} \right\}$$

$$(i_1^o)^2 = i_{1d}^o + i_{1u}^o$$

$$i_{1d}^o = i_{2d}^o + \alpha_{21}$$

Writing again Voltage Gain A = $\frac{V_2}{V_1}$

$$\therefore A_d \times \frac{V_2}{V_1} = - \frac{i_2 R_L}{i_1 R_L} = - \frac{A_d \times i_1 \times R_L}{V_1}$$

$$= - h_f \times \frac{R_L}{1 + h_o R_L}$$

$$= - \frac{h_f}{1 + h_o R_L} \times \frac{R_L}{R_L}$$

$$= \frac{h_f}{h_o + 1/R_L}$$

$$= \frac{h_f}{h_o + 1/R_L}$$

~~$$83. \frac{h_f}{1 + h_o R_L} = \frac{h_o R_L + A}{h_o R_L}$$~~

~~$$h_f = \frac{h_o R_L + h_i}{R_L} - h_o h_f$$~~

$$+ P_{PPH} = 2 \times - h_f \times \frac{R_L}{R_L} = 2 \times A$$

~~$$2 \times h_o R_L + h_i - h_o h_f - h_{PPH}$$~~

$$2 \times - R_L h_f = 2 \times - R_L h_f$$
~~$$\frac{h_o R_L + h_i - h_{PPH}}{h_i + \Delta h R_L}$$~~

$$\begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_i & h_r \\ h_f & h_o \end{bmatrix} \begin{bmatrix} i_2 \\ V_2 \end{bmatrix}$$

h

Q) A common emitter amplifier has the following parameters
 $h_{ie} = 1100 \Omega$ $h_{re} = 2.5 \times 10^4$
 $h_{fe} = 50$ $h_{oe} = 25 \text{ mAmperes per } \mu\text{A}$
 $R_S^2 R_L = 1 \text{ k}\Omega$

Find: A_i , A_v , Z_i

$$A_i = \frac{-h_f}{1+h_0R_L} = \frac{-50}{1+25 \times 10^3}$$

$$= -Z_i / f$$

$$A_i^2 = \frac{-h_f}{1+h_0R_L} = -48.78$$

$$\therefore Z_i = id + 1/h_0R_L$$

$$A_v^2 = \frac{-R_L h_f id}{h_i + R_L(h_{i0} - h_f h_r)} = -44.94$$

$$Z_i = h_i + h_{re} R_L / A_i$$

$$\{ Z_i^2 = 1087.805 \Omega \}$$

~~Q4*~~ Table

$$\left\{ \begin{array}{l} i) v_1 = h_{11}^o + h_{12} v_2 \\ ii) i_2 = h_{21}^o + h_{22} v_2 \end{array} \right.$$

a) Current gain $A_i = \frac{-h_f}{1 + h_{21} R_L}$

b) Voltage gain $A_v = \frac{-h_f R_L}{h_1^o + \Delta h_f R_L} = \frac{A_i \times R_L}{Z_i}$

c) Power gain = $A_i^o \times A_v$

$$= \frac{h_f^2 R_L}{(h_1^o + \Delta h_f R_L)(h_1^o + h_{21} R_L)}$$

d) Input impedance $= h_1^o - \frac{h_{21} h_f}{1 + h_{21}} = h_1^o h_{21} R_L$

e) $\cancel{A/V} = A_i^o \times \frac{R}{Z_i}$



Output impedance Z_o

$$= \frac{R_S + h_1^o}{\Delta h + h_2^o R_S}$$

$$\left\{ \begin{array}{l} v_1/i_1 = h_1^o = \text{input impedance} \\ i_2/v_2 = h_{22} = \text{output impedance} \\ v_1/v_2 = h_{21} = \text{reverse current gain} \\ i_2/i_1 = h_f = \text{forward current gain} \end{array} \right.$$

f) Overall current gain $A_{IS} = \frac{A_i^o \times R_S}{R_S + Z_i}$

g) Overall voltage gain $A_{VS} = A_v \times \frac{Z_i}{Z_i + R_S}$

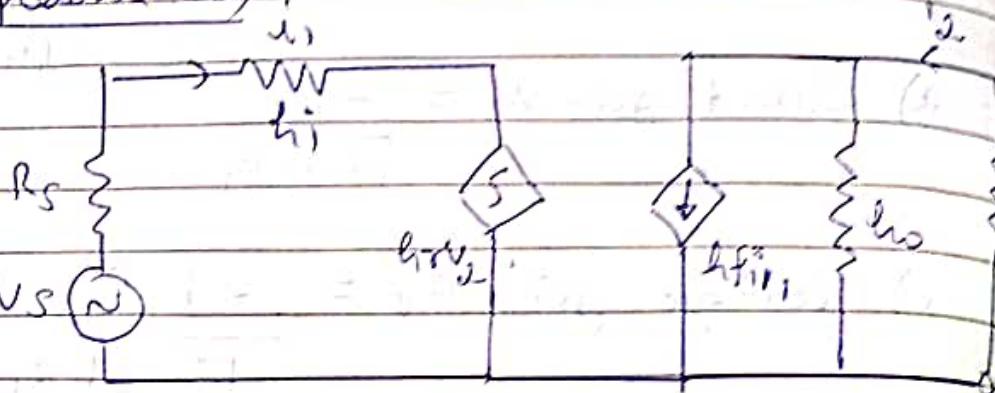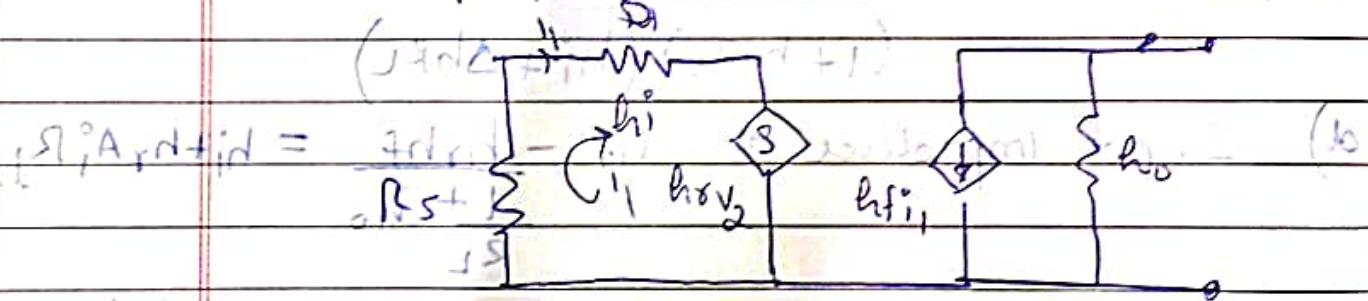Output impedance Z_o)* Short ckt + the voltage ($V_s = 0$)* Open ckt + load resistance R_L ($R_L = \infty$)

$$i_d = i_{fd} = 1 \text{ A}$$

$$i_d = Z_o^2 \frac{V_2}{h_{fi} + h_{rv2}}$$

$$-iR_s - i_1 h_i - h_r v_2 = 0$$

$$i_1 = \frac{-h_r v_2}{R_s + h_i}$$

$$= \frac{V_2}{h_f \left(\frac{-h_r v_2}{R_s + h_i} \right) + h_{rv2}} = \frac{R_s + h_i}{h_o R_s + h_{oh} - h_f h_r}$$

$$Z_o = \frac{R_s + h_{ie}}{h_{oe} R_s + \Delta h}$$

(Q) A common emitter amplifier ckt has following measurements when output is short circuited i.e. $V_{CE} = 0$, $i_b = 15 \mu A$, $i_c = 1.5 \text{ mA}$, $V_{be} = 15 \text{ mV}$.

when input is open $V_{be} = 1 \text{ mV}$, $i_c = 90 \mu A$, $V_{cc} = 1.5 \text{ V}$
Find out the h-factors?

h_{ie} , h_{re} , h_{fe} & h_{oe} ?

$$h_{ie} = \frac{V_1}{i_1} = \frac{V_{be}}{i_b} = \frac{15 \text{ mV}}{15 \mu \text{A}} \approx 1000$$


$$h_{fe} = h_{fe} = \beta = \frac{i_c}{i_b} = \frac{1.5 \text{ mA}}{15 \mu \text{A}} = 100$$

$$h_{re} = \frac{V_{21}}{V_2} = \frac{1 \text{ mV}}{1.5 \text{ V}} = 0.002 \times 1000^{\text{--}}$$

$$i_b = 0$$



$$= 0.667 \times 10^{-3}$$
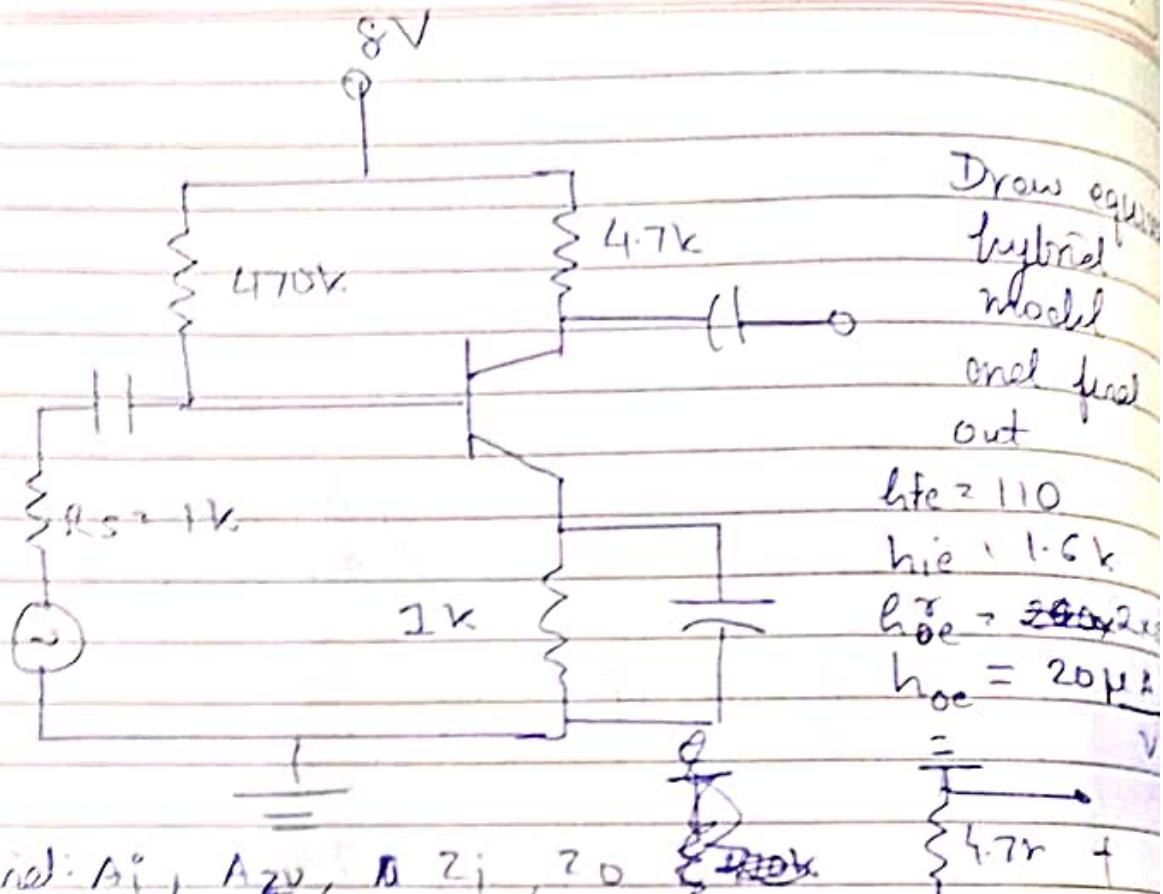
$$h_{oe} = i_2 / V_2 = \frac{90 \mu \text{A}}{1.5} = 60 \times 10^{-3} \text{ mho} = 60 \text{ microh}$$



$$\rightarrow A_i^o = \frac{h_{fe}}{h_{ie} R_2}$$

~~200HD~~
Eq. ckt

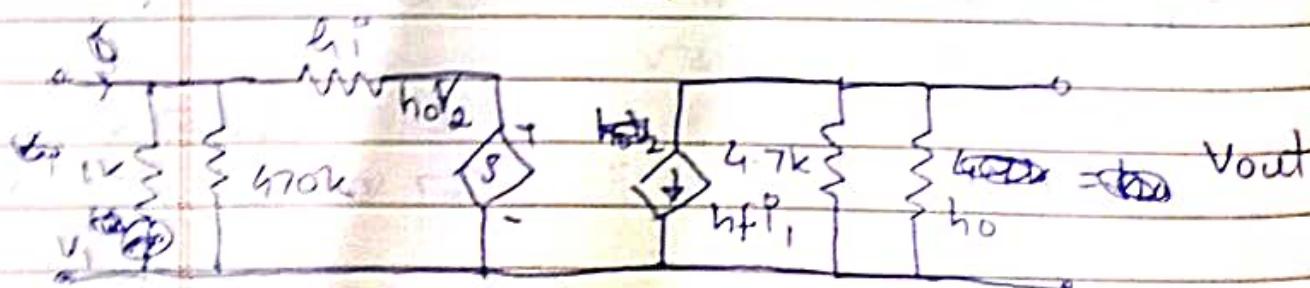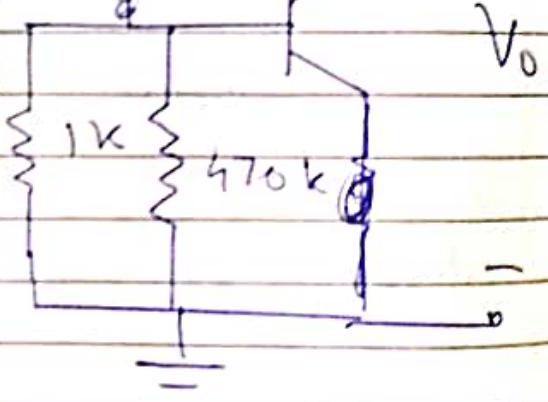

$$A_i = \frac{-h_f}{1+h_0 R_L}$$

$$= -\frac{110}{1+20 \times 4.7 \times 10^3 \times 10^6}$$

$$= -100.58$$

$$A_v = \frac{-h_f R_L}{h_i + \Delta h R_L} = -\frac{110 \times 4.7 \times 10^3}{1.6 \times 10^3 + (h_i - h_f) (L \cdot 7 \times 10^3)}$$

$$= -313.9$$

~~$$Z_o = \frac{A_i \times R_L}{Z_i} = A_v$$~~

$$Z_i = 1505.97 \Omega$$

$$Z_o = \frac{R_s + h_i}{\Delta h + h_0 R_s}$$

$$R_s = 2 k \approx 2 k$$

$$= 86666.67 \Omega$$

$$\approx 86.67 k\Omega$$

Note: If the ~~no~~ ^{h_{o0}} ~~no~~ output is given as $50k$
 then $h_0 = 1/k$. If it is

given as $20 \mu A/V$ then $k = 20 \Omega$

$$\begin{aligned}
 A_{V2} &= \frac{V_2}{V_S} + \frac{V_2}{V_S} \times \frac{V_1}{V_1} + \frac{V_2}{V_1} \times \frac{V_1}{V_S} \\
 &= A_V \times \frac{V_1}{V_S} \\
 &= \left[A_V \times \frac{Z_i}{R_S + Z_2} \right]
 \end{aligned}$$

$$\frac{V_1}{V_S} = \frac{Z_i}{Z_i + R_f}$$

Overall current gain

$$A_{is} = i_L / i_S = \frac{i_2}{i_S} \times \frac{i_1}{i_1} = A_i \times \frac{i_1}{i_S}$$

$$A_{is} = A_i \times \frac{R_S}{R_S + Z_i}$$


$$i_1 = i_S \times \frac{R_S}{R_S + R_2}$$

$$\frac{i_1}{i_S} = \frac{R_S}{R_S + R_2}$$

$$A_{VS} = A_V \times \frac{Z_i}{R_S + Z_i}$$

$$A_{is} = \frac{A_i \times R_S}{R_S + Z_i}$$

CE configuration

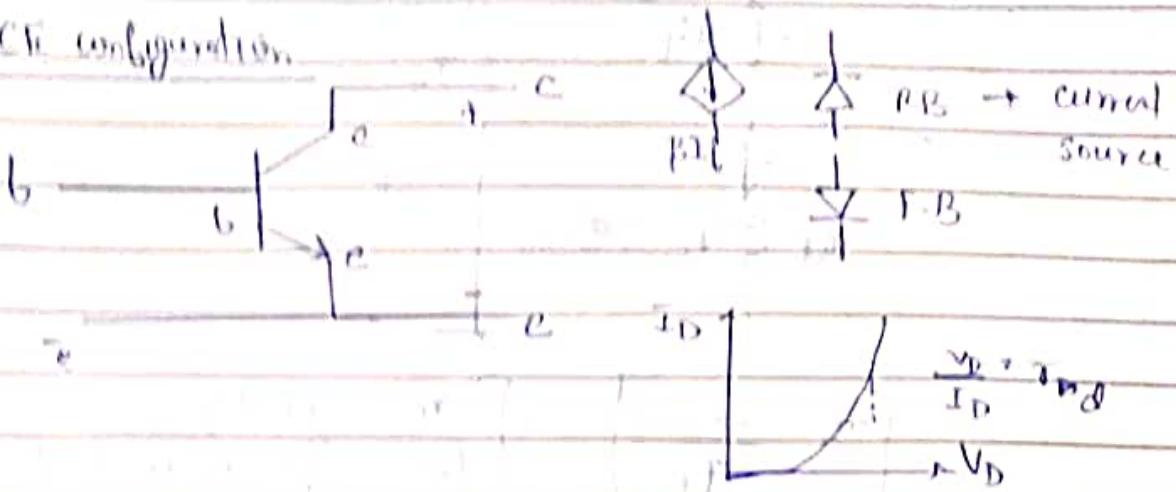

dynamic resistance r_{dl}

$$I_D \geq I_S \left(e^{\frac{kV_D}{T_K}} - 1 \right)$$

Temperature in Kelvin
reverse saturation current

$$\frac{dI_{dl}}{dV_{dl}} = I_S \frac{\frac{kV_D}{T_K} + \frac{V_D}{kV_D}}{T_K}$$


$$= \frac{k}{T_K} \left(e^{\frac{kV_D}{T_K}} \right) \cdot I_S$$

$$= \frac{k}{T_K} \left(\frac{I_D}{I_S} + 1 \right) \cdot I_S$$

$$= \frac{k}{T_K} (I_D + I_S)$$

$$\frac{1}{r_{dl}} \approx \frac{k}{T_K} I_D \quad (I_D \gg I_S)$$
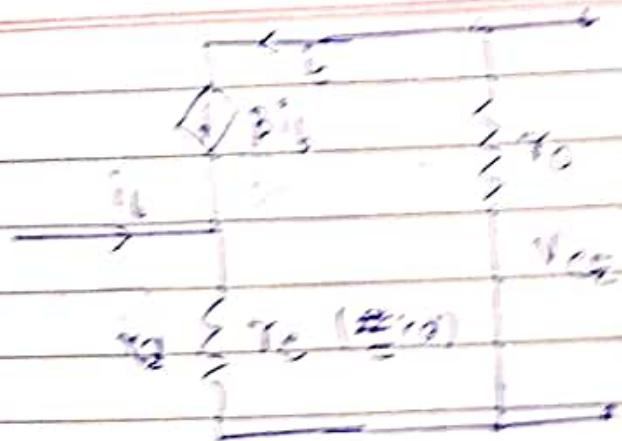
$$\left\{ r_{dl} \approx 26 \text{ mV} \right\}$$



$$\left[Z_2 = \frac{26 \text{ mV}}{I_o} \right]$$


Z_0 is ideally or
probably Z_0 is high value

voltage drop across $Z_2 = 101.30$




$$\Rightarrow (B+1)Z_0$$

{
↳ reflected impedances
of b2o side has a
value of $(B+1)Z_0$

$$Z_{2\text{ref}} = 161.30 \text{ mV}$$

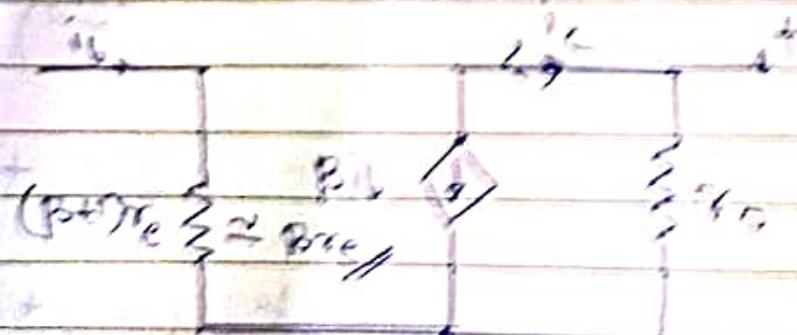

Dynamic load model = $\frac{R_L}{B+1}$

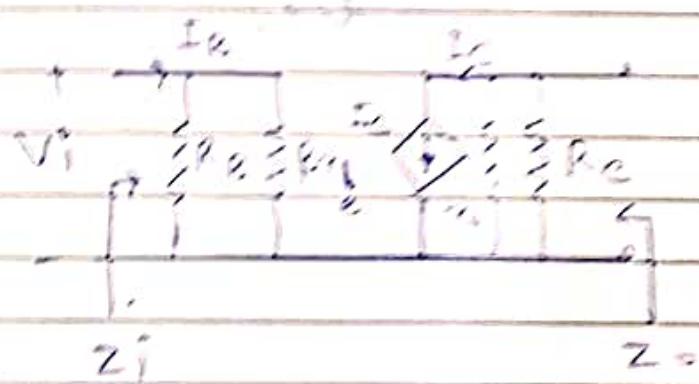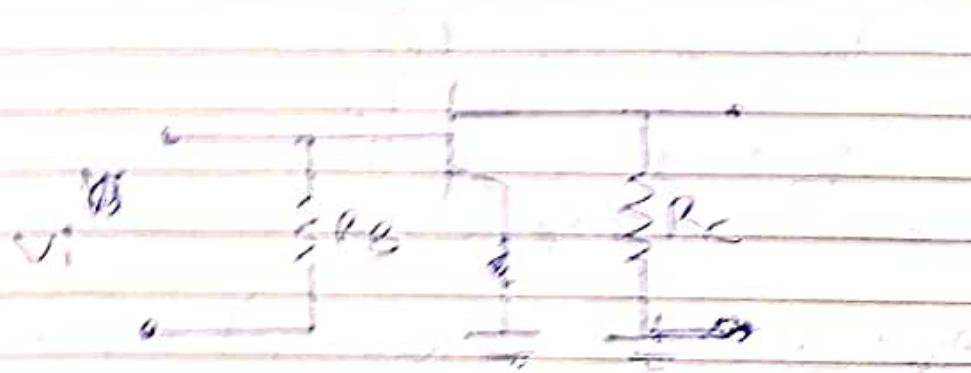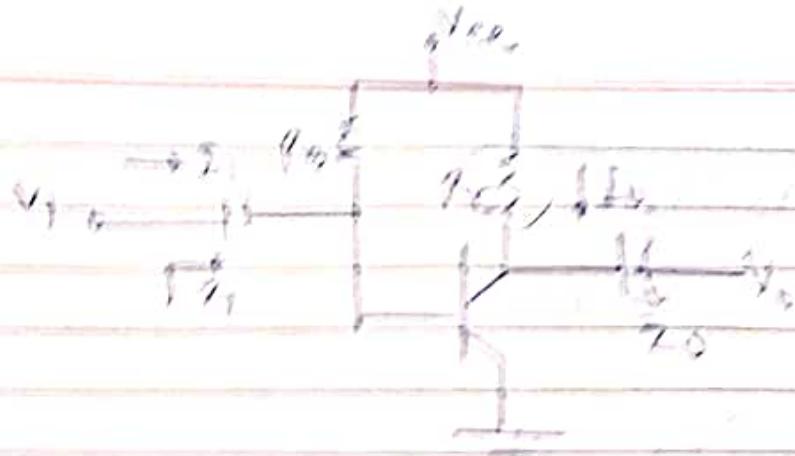

$$Z_i = R_s \parallel R_{eq}$$

$$\therefore R_{eq} = 10 \parallel R_{load}$$

$$Z_i = \frac{R_s \cdot R_{load}}{R_s + R_{load}} \approx R_{load}$$

$$Z_0 \approx r_0 \parallel r_L$$

if $r_0 \gg 10R_C$

$$(Z_0 = R_C)$$


$$V_o \approx i_B \times (R_C \parallel R_S)$$

$$\approx -i_C \times (R_C \parallel R_S)$$


$$V_o = -\beta \frac{V_i}{R_C + r_e} (R_C \parallel r_o)$$

$$A_{V2} \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{R_C + r_e} \approx \boxed{\sim \frac{r_o}{R_C}}$$

(P)

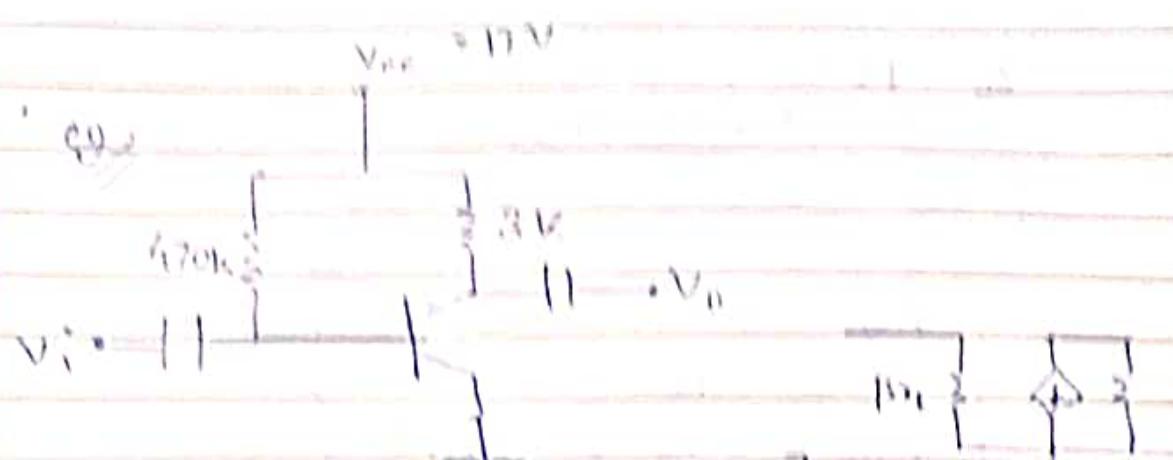

Find r_e , Z_i , β_0 , A_v {P.T.O}

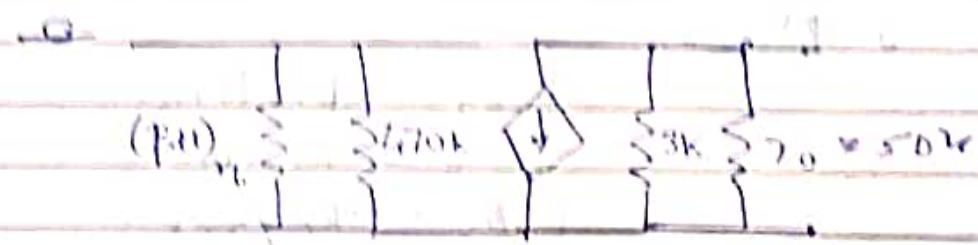

$$i_B = \frac{V_{CC} - V_{CE}}{R_B} = \frac{17 - 0.7}{470k} = 0.024 \text{ mA}$$

$$i_C = 0.404 \text{ mA}$$

$$r_{eQ} = \frac{26 \text{ mV}}{0.404 \text{ mA}} = 10.71 \Omega$$

$$Z_i = \beta r_{eQ} \| 470k$$

~~$$= 1.0045 \text{ k}\Omega \approx 1.0 \text{ k}\Omega$$~~

$$\approx 10.68 \text{ k}\Omega \approx \beta r_{eQ}$$

$Z_i = \beta r_{eQ}$

$$R_B \geq \beta r_{eQ}$$

$$Z_b = 1G \parallel 13k$$

$$\approx 2.83 \text{ k}\Omega$$

$$Z_0 = R_C$$

$$A_V = -\frac{R_C || R_o}{R_E} \rightarrow -264.24$$

$$A_V = -\frac{R_C}{r_{ce}} = -280.11$$



~~for AF~~
summary

$$Z_1^o = B_r e || r_B$$

$$Z_b = R_C || r_E$$

$$A_V = -R_C / r_{ce}$$

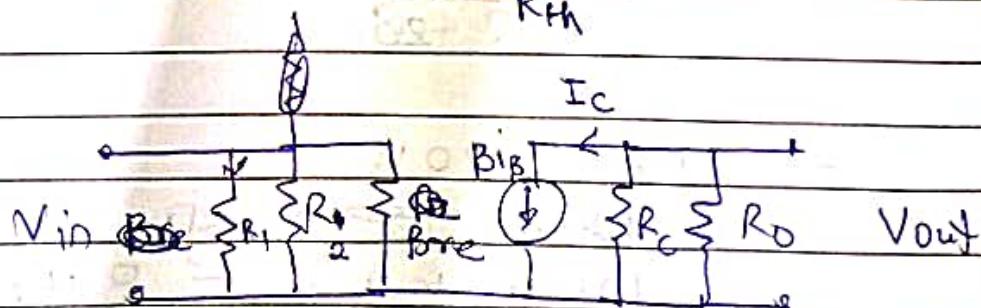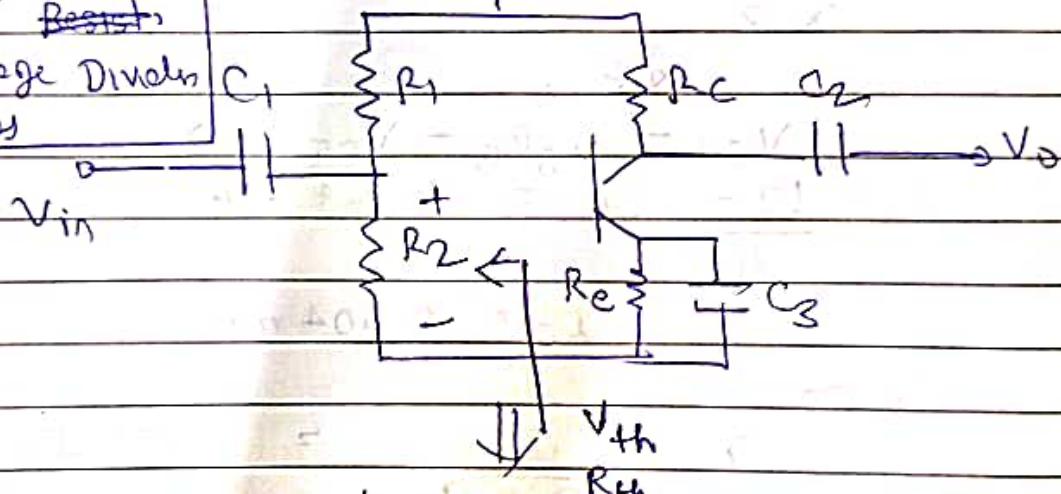RE Model
for ~~Bias~~
Voltage Dividers
Bias



$$Z_i = B_{re} = R_B \parallel B_{re}$$

$$Z_o = R_C = r_o \parallel R_C$$

$$A_V = -R_C/r_e = -\frac{R_C r_o}{r_e}$$

$$R_1 = 56k$$

$$R_C = 6.8k$$


$$R_E = 1.5k$$

$$R_2 = 8.2k$$

$$\beta = 90$$

$$V_{CE} = 22V$$

$$R_{Th} = 7.153k$$

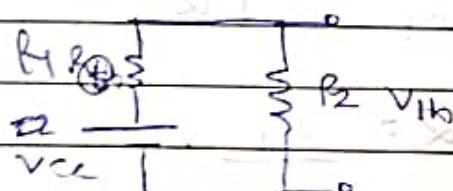


$$V_{Th} = \frac{R_2 \times 22V}{R_1 + R_2} = \frac{8.2}{56 + 8.2} \times 22$$

$$22 - i(7.153) - i(8.2) = 0$$

$$i = 1.4356$$

$$V_{Th} = 2.81V$$

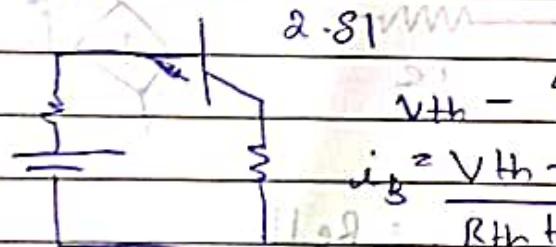

$$i_B = \frac{V_{Th} - V_{Bh}}{R_{Th} + (\beta + 1)R_E} = 0.014$$

$$i_B = 0.014mA$$

$$i_C = 0.014 \times 907mA = 1.335$$

$$I_E = 0.014 \times 983mA$$

$$\gamma_e = \frac{26mV}{1.335 \times 983mA} = \frac{19.47}{1.335 \times 983mA}$$

$$Z_i = B_{re} = 236.53 \Omega \quad r_{Th} = 7.15$$


$$1752.8011 \times 1407.7 \Omega = 2447.598k\Omega$$

$$Z_o \approx R_C = 6.8k\Omega$$

$$A_V = -R_C/r_e = 349.25$$

Common Base

(Configuration)


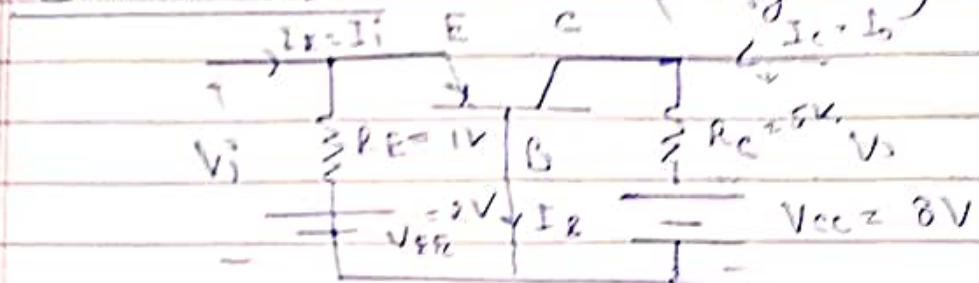


$$V_{BE} - (\beta + 1)I_B R_E - V_{FB} = 0$$

$$j_E \rightarrow \frac{9 - 0.7}{(\cancel{\beta+1})R_E} \frac{2.13}{1k} = 1.3 \text{ mA}$$

$$\alpha \approx \frac{I_C}{I_E}$$

$$r_o = \frac{20mV}{I_E} = 20.5 \Omega$$

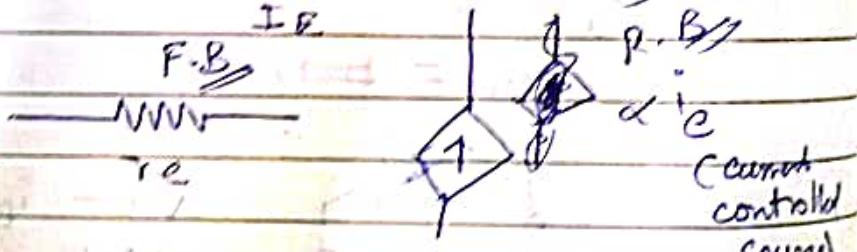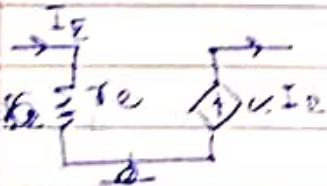

$$Z_i = R_E // r_e$$

$$= 19.61 \Omega$$


$$Z_o = 5k\Omega \text{ (R}_C\text{)}$$

$$\left\{ \begin{array}{l} A_V = \frac{V_o}{V_i} = \frac{i_C R_C}{i_E r_e} = \frac{r_C}{r_e} \\ r_o = \frac{V_o}{i_E} = \frac{V_o}{i_C} \times \frac{1}{r_e} = \frac{r_C}{r_e} \end{array} \right.$$

$$= 245$$

Emitter Forward Follower

OR,

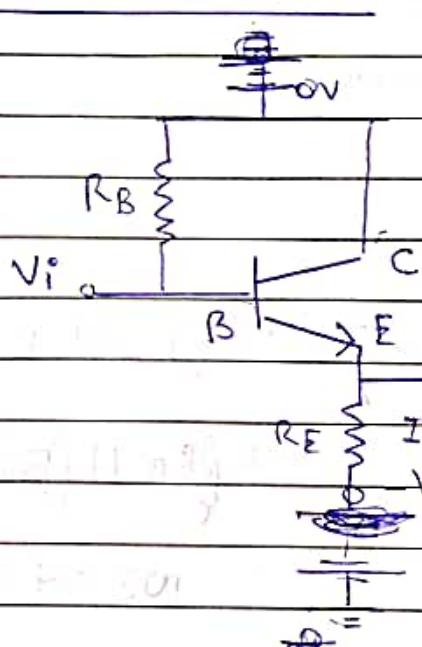Common Collector

In emitter follower circuit the output is taken from the emitter terminal of the circuit

$$V_{00} = V_0 - 0.7$$

The voltage gain of an emitter follower circuit is approximately equal to 1 because $V_{out} \approx (V_{in} - 0.7)V$

~~Q17~~

$$-i_B R_B - 0.7 = i_E R_E + V_{EE}$$


$$i_B = \frac{V_{EE} - 0.7}{R_B + (\beta + 1) R_E}$$

$$i_E = (\beta + 1) \left[\frac{V_{EE} - 0.7}{R_B + (\beta + 1) R_E} \right]$$

$$R_B = 240k, R_E = 2k, V_{EE} = -20V, \beta = 90$$

$$i_B = 0.046 \text{ mA}$$

$$i_E = 4.162 \text{ mA}$$

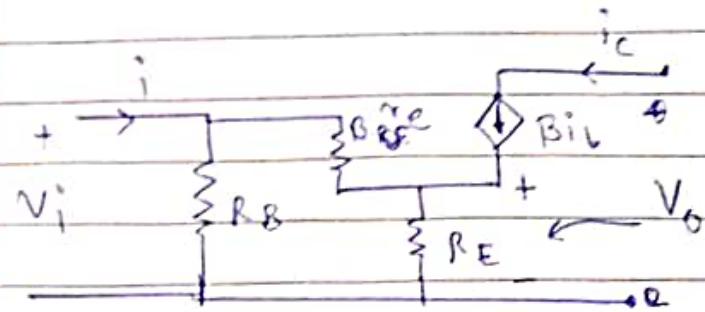

re model

$$\begin{cases} i_B \\ R_{BE} \end{cases}$$

$$\begin{cases} i_E = (\beta + 1)i_B \\ R_E \end{cases}$$

$$\begin{cases} i_B \\ i_E = (\beta + 1)R_E \end{cases}$$

$$\therefore Z_i = \frac{1}{R_B} || (\beta r_e + (\beta + 1)R_E)$$

$$= 103.04 \text{ k}\Omega$$

Applying KVL in input ckt

We short ckt the V_i

KVL in input ckt

$$i_B = \frac{V_i}{\beta(r_e + R_E)}$$

$$i_E = \frac{V_i}{r_e + R_E}$$

$$Z_o = R_E || r_e = 6.23 \Omega$$

$$V_o = i_E R_E$$

$$= \left(\frac{V_i}{r_e + R_E} \right) R_E$$

Q


$$\left(\frac{V_o}{V_i} = \frac{R_E}{R_E + R_L} \right)$$

$$= \frac{2k}{6.25 + 2k} \approx 1 \text{ (in phm)}$$

$$\therefore [A_v = 1]$$

In CE we get 180°

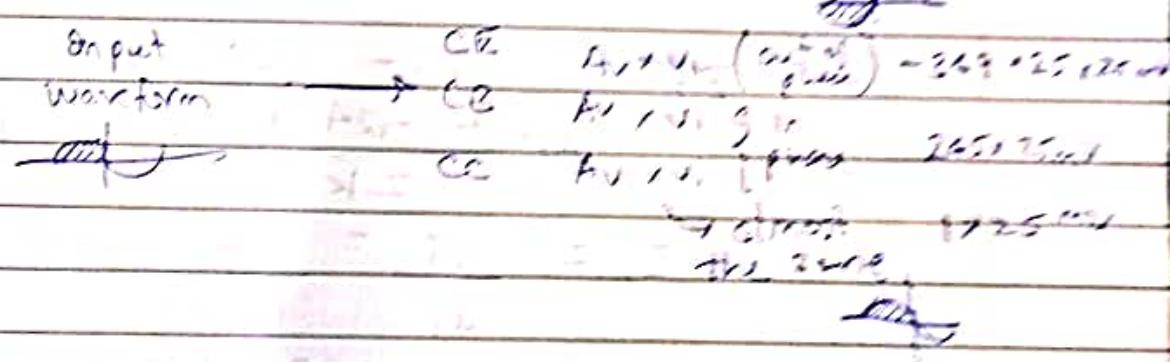In CB & CC \Rightarrow output is in phase with input.



Effect of R_S and R_L

$$A_v = \frac{V_o}{V_i}$$

Once we add the load resistance R_L in the circuit the equivalent output resistance changes from $R_E \parallel R_C$ to $R_E \parallel R_L$.

$$A_{vL} = \left(\frac{Z_i}{Z_o + R_S} \right) A_v$$

(Q) A BJT amplifier has a voltage gain of 320. Source voltage of 40 mV is given for a source resistance of 1.2 k. The amplifier is used in common emitter configuration; calculate the value of V_i^o , Z_i and I_o . $V_o = -7.68 \text{ V}$

$$A_v = \frac{V_o}{V_i^o}$$

~~$$V_o = 40 \times 320$$~~

$$V_i^o = 0.024 \text{ V}$$

$$= 24 \text{ mV}$$

~~$$V_s - (1.2) i_i^o - 24 = 0$$~~


$$i_i^o = \frac{40 - 24}{1.2 \text{ k}} = 13.33 \mu\text{A}$$

$$Z_i = \frac{V_i^o}{i_i^o} = \frac{24}{13.33} \times 10^3$$


$$= 1.8 \text{ k}\Omega$$

Small Signal Analysis Miscellaneous

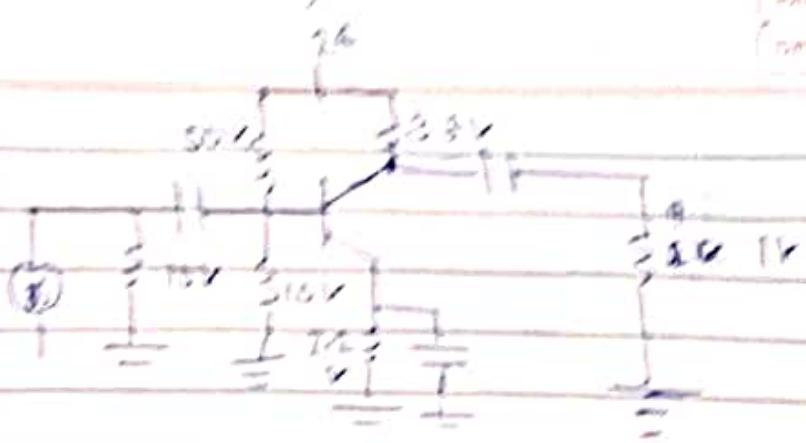1) On an RC coupled amplifier shown below, the BJT has an $h_{fe} = 50$. All bypass's and capacitance capacitors are assumed to have zero reactance at signal frequency. Find quiescent condition and draw the small signal equivalence model. Find Z_i , A_v , Z_o .



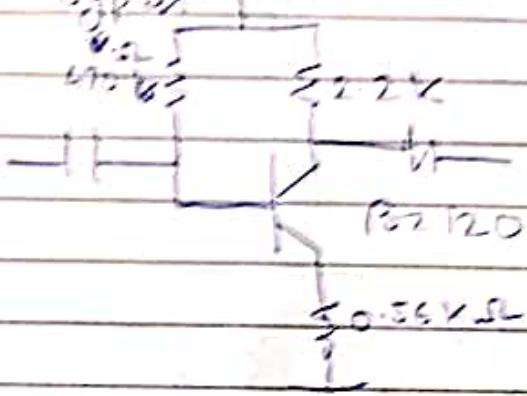3) The following one is a CE configuration with emitter bypass -




Forward
current

$I_1 = 277, 298,$

$299 (\text{B}_\text{E} \approx 0.7 \text{V})$


Small Signal Analysis

Y_{E} model

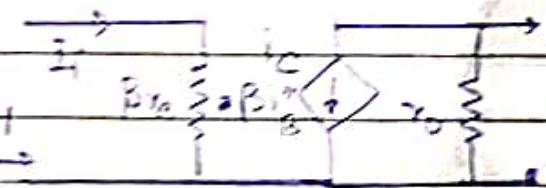

Z_{in} Source follower \rightarrow Emitter
CE emitter follower \rightarrow collector

Approximate
Hybrid model

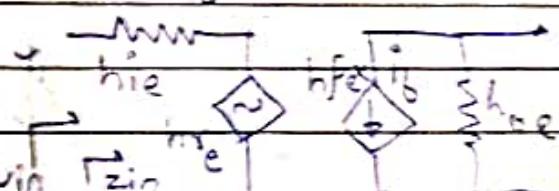

Replace $V_{\text{out}} = 0$

$$h_{\text{FE}} = \frac{V_{\text{in}}}{V_{\text{D}}} = \text{short ckt.}$$

$= V_{\text{small}}$

≈ 0

$$\beta_{re} = h_{fe}$$

$$\beta = h_{fe}$$

$$m^+ \frac{1}{h_{oe} \cdot \alpha}$$

{ As there is zero voltage drop due to $h_{re} = 0$ }


(Q) $I_B = 2.5 \text{ mA}$

$$h_{fe} = 146$$

$$h_{oe} = 20 (\mu\text{mho})$$

Draw the β_B re and hybrid model.

~~re model~~

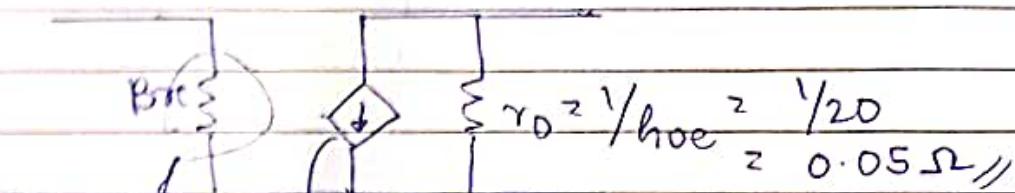


$$r_e = \frac{26 \text{ mV}}{I_B} \quad B1B1 = h_{fe} \left(\frac{I_B}{h_{fe} + 1} \right)$$

$$= 10.45 \Omega \quad = 2.48 \text{ mA}$$



~~B1B1 model~~

$$B1B1 = 1456 \Omega$$

$$= 1.45 \text{ k}\Omega$$

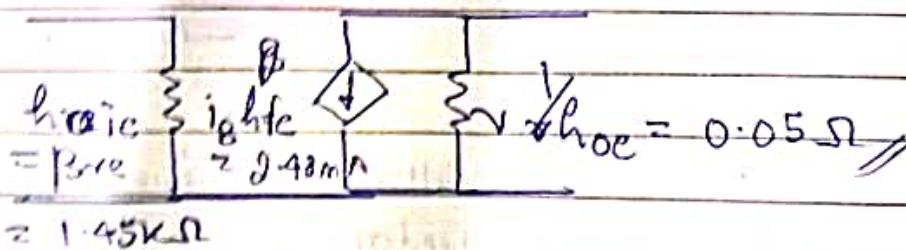

Fixed Bias

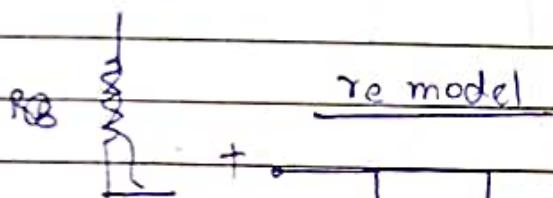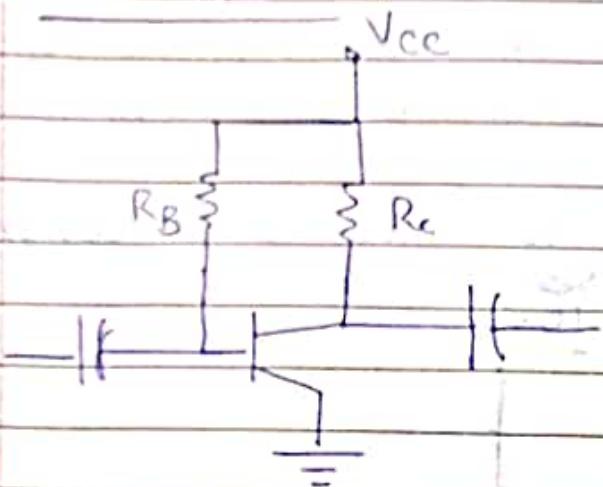

For AC models

Short ckt.


cap.

+ DC volt +

source = 0

$$z_i = V_i \quad A_v = -\left(R_C || r_o \right) \quad z_o$$

Appox. h-model

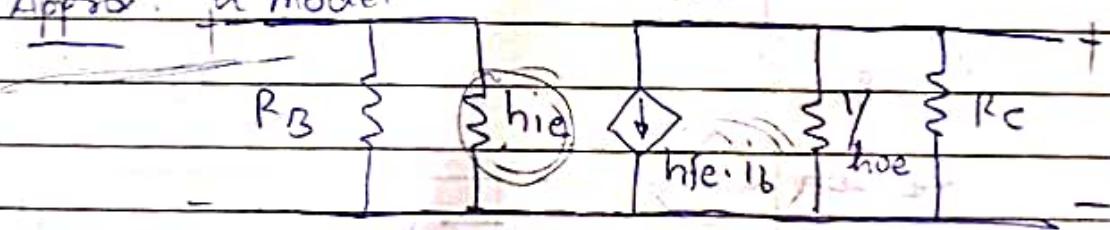

$$z_i = R_B || h_{ie}$$

$$z_o = \frac{1}{h_{oe}} || R_C$$

$$A_v = -\left(\frac{R_C || \frac{1}{h_{oe}}}{h_{ie}} \right)$$



$$= -\left(\frac{R_C || \frac{1}{h_{oe}}}{h_{ie}} \right) h_{fe}$$

$$\left\{ z_o = \frac{1}{h_{oe}} \right\} \quad \left\{ z_o = \frac{1}{h_{oe}} \right\}$$

HW

For voltage divider circuit find expression of Z_i and A_v in terms of h-parameters.

$\{$ Emitter follower circuit is also called common collector $\}$

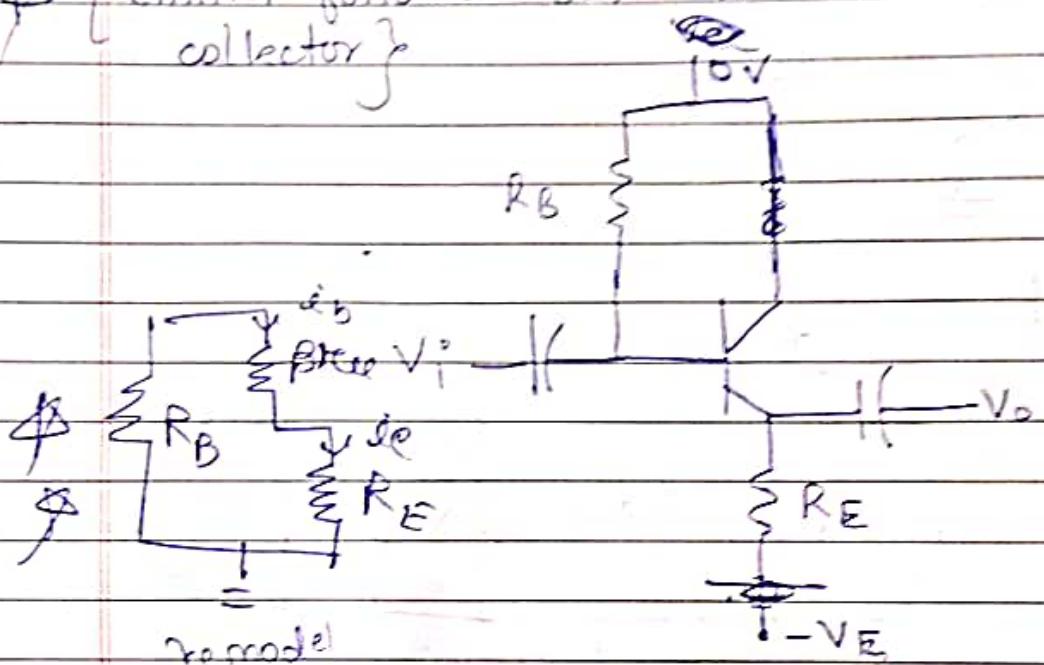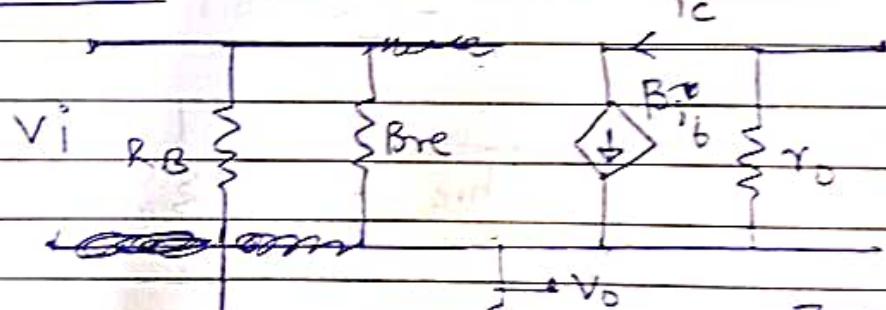
remodel

$$Z_i = R_B + B_r r_e + R_L \parallel r_o$$

$$Z_o = R_L \parallel r_o$$



Approximate hybrid model

$$A_v \approx 1$$

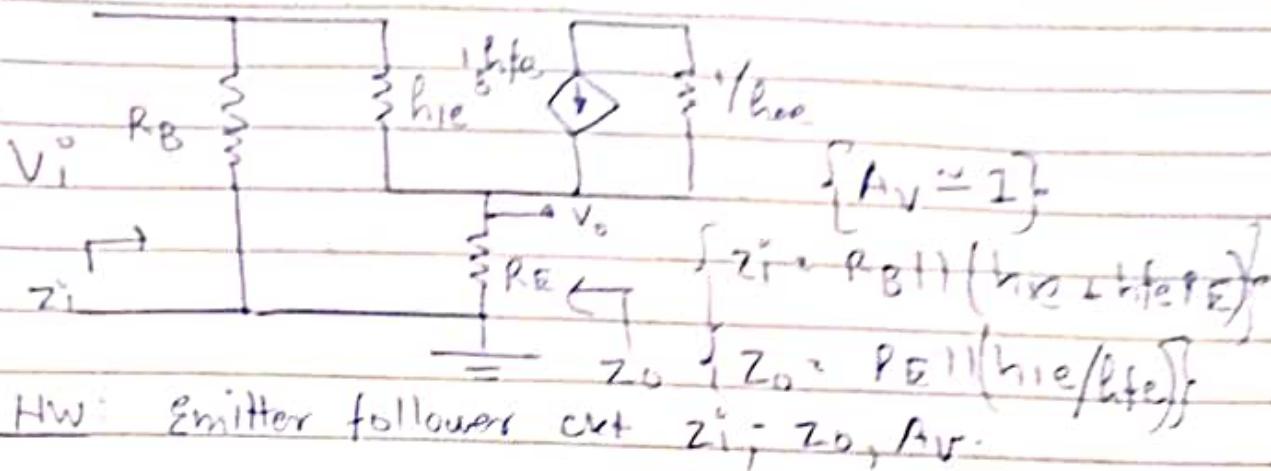


* Every ckt in small signal model, marks where we are taking input : v_i , i_i , z_i & output : v_o , i_o , z_o . Should be clearly marked }

Common base

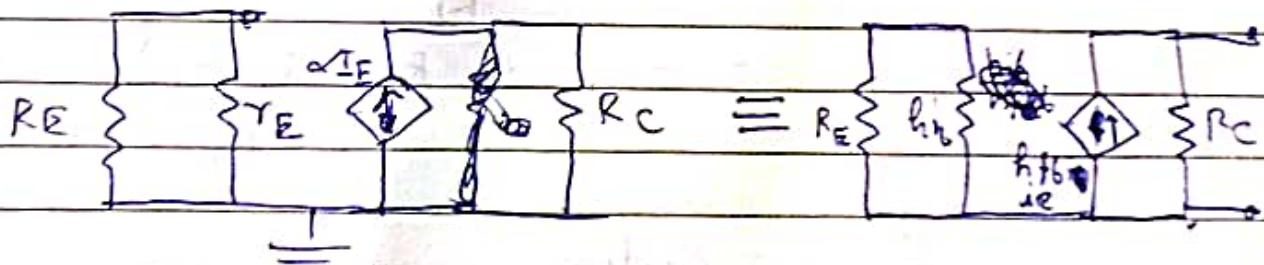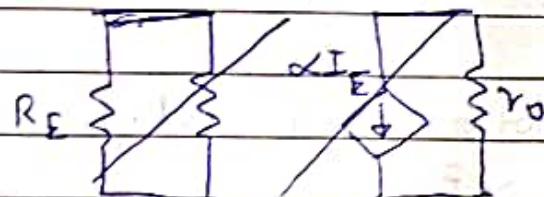

$$\begin{cases} h_{FE} = r_e \\ \alpha h_{FE} = \alpha \approx 1 \end{cases}$$

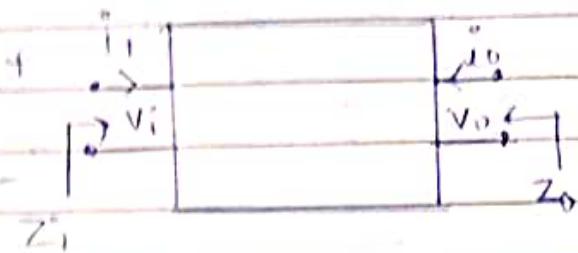Cascade System of Transistors1) Effect of loading R_L

$$A_{vL} = \frac{R_L}{R_L + Z_0} \times A_{vM2}$$

2) Effect of loading R_S

$$A_{vS} = \frac{Z_i}{Z_i + R_S} \times A_{vM2}$$


3) Effect of both R_S and R_L

$$A_{vS} = \frac{Z_i}{Z_i + R_S} \times \frac{R_L}{R_L + Z_0} \times A_{vNL}$$

4) Current gain relation with voltage gain


$$A_{iL} = -A_{vL} \times \frac{Z_i}{R_L}$$

$$\approx -A_{vS} \times \frac{R_S}{R_L} \left(\frac{R_S + Z_i}{R_L} \right)$$

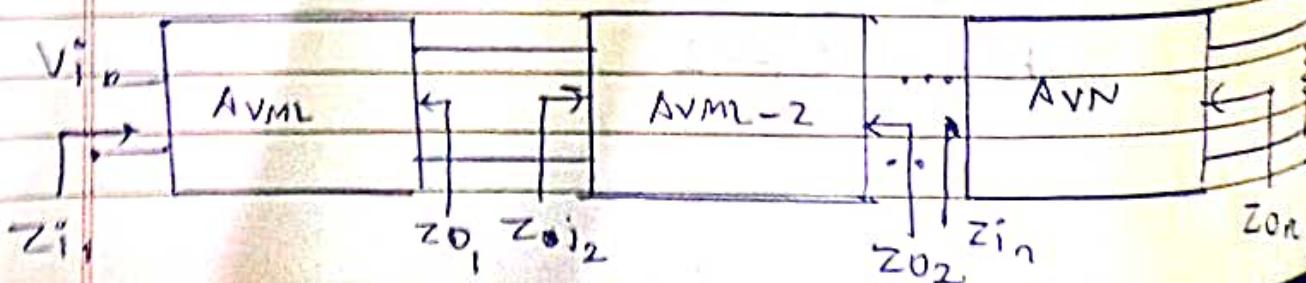Cascade System

$$[A_{VT} = A_{VL1} \times A_{VL2} \times A_{VL3} \times \dots \times A_{VLn}]$$

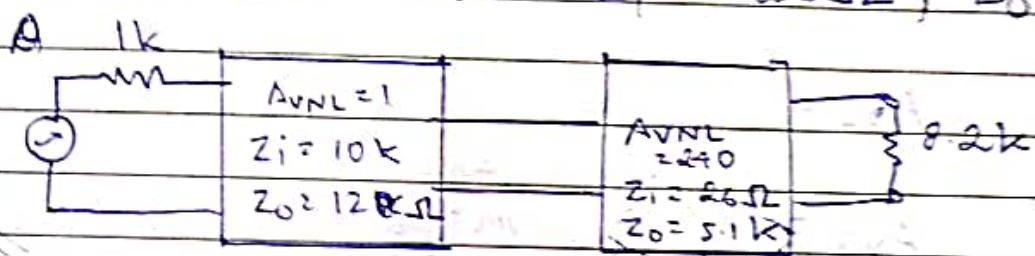- (q) A two stage system employs a two stage amplifier system employing an emitter follower followed by a common base configuration. No local voltage gain of common base is 240, no local voltage gain of emitter follower is 2. The input impedance Z_i of emitter follower is $10k\Omega$. $Z_{out} = 12k\Omega$ in common base. $Z_i = 26\Omega$, $Z_o = 5.1k\Omega$



Find :

- 1) Localized gain of each stage
- 2) Total gain of overall system

Solⁿ

$$1) A_{VL} = \frac{R_L}{R_L + Z_o} \times A_{VNL}$$

$$\therefore R_L = Z_{i2} = 26\Omega$$

$$\therefore A_{VL} = \frac{26}{26 + 5.1} \times 240 = 0.684 \times 240 = 164.16$$

$$2) A_{VL} = \frac{R_L}{R_L + Z_o} \times A_{VNL}$$

$$= \frac{240 \times 8.2}{8.2 + 5.1} = 147.97$$

Total gain

$$= A_{V1} \times A_{V2}$$

//

$$\approx 101.21$$

//

$$A_{VS\ Total} = A_{VT} \times \frac{Z_i}{Z_i + R_S}$$

//

$$\approx 92$$

//

- ① If we remove the first stage of amplifier
 then find out what will be A_{VL} , A_{VS} ??

$$A_{VL} = \frac{R_L}{R_L + Z_0} \times A_{VN1}$$

$$A_{VS} = \frac{Z_i \times A_{VN1}}{Z_i + R_S} = \frac{26}{26 + 1000} = 0.025$$

7 Variation -


- ① Gain of amplifier can be given in dB
 ② In that case convert the gain to absolute value and then do the calculations.

- ② $A_{VN2(\text{dB})} = 10 \log_{10} A_{VN2}$ (convert to absolute value then convert back)

If gain is given in dB then the total gain should also be given in dB.

[Page 10]
[Date: 11/11/2023]

Darlington Pair

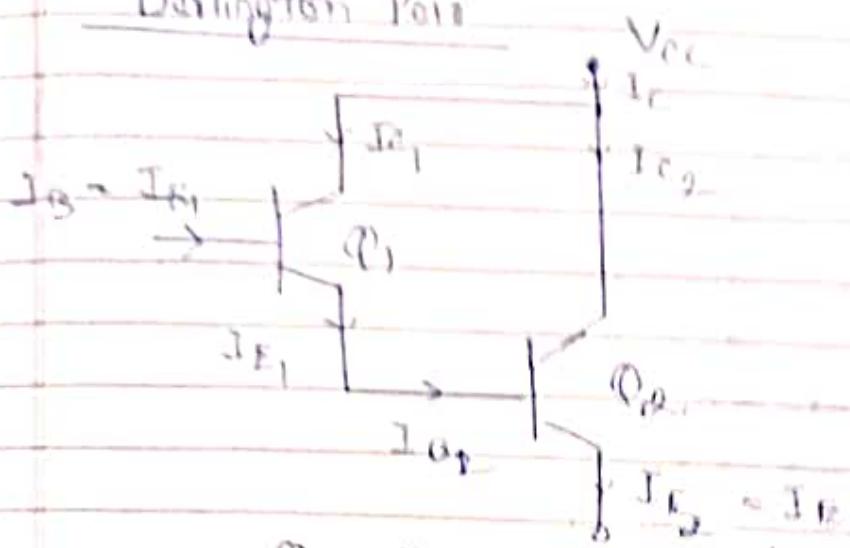

Overall current gain / β ?

$$\beta = \frac{I_E}{I_B} \rightarrow \frac{I_E_2}{I_B}$$

$$= \frac{I_E_2}{I_B} \cdot \frac{(\beta_2 + 1) I_{E_1}}{I_{E_1}}$$


$$= (\beta_2 + 1)(\beta_1 + 1) I_{E_1}$$

$$\boxed{\beta \approx \beta_2 \cdot \beta_1}$$

~~I_E~~ $\Rightarrow \beta_2$ Super β Transistor

$$V_{BE} = V_{BF_1} + V_{BF_2}$$

Voltage drop has increased

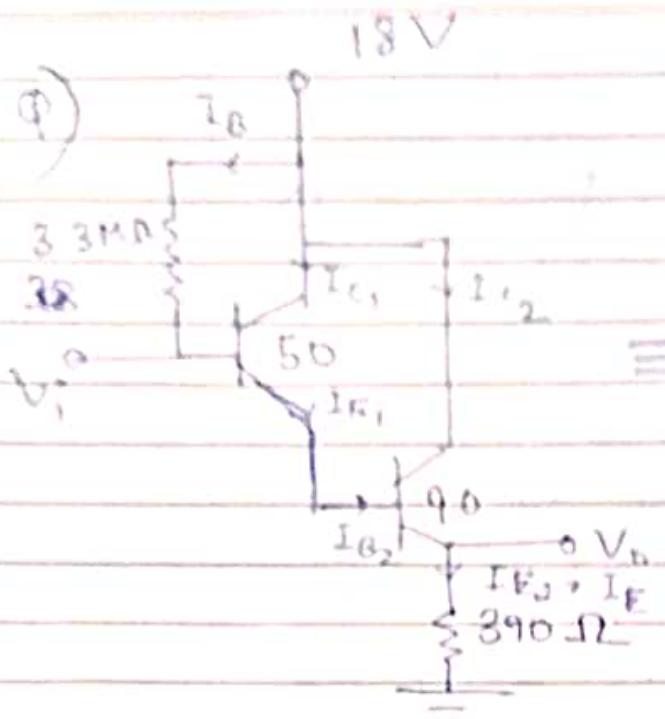

Calculate the value of β_D , i_B , i_{C_2} , V_{E_2} , V_{CE_2}


$$\beta_D = \frac{90 \times 50}{4500} \approx 1$$

$$18 - 0.7 \\ \beta_D$$

$$I_{C_2} \approx I_{E_2}$$

$$I_{B_2} = I_{E_1}$$

$$18V - I_{C_1} \approx I_{E_1}$$

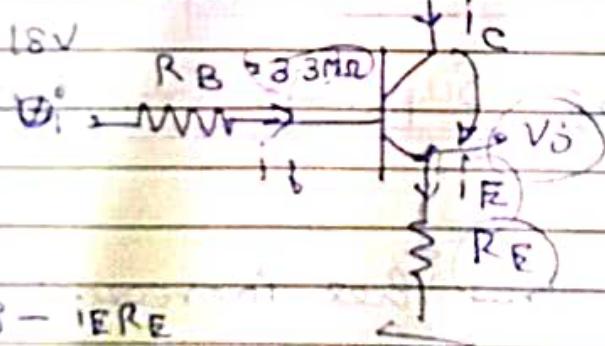

$$18 - 0.7 \\ (\beta + 1)R_E + R_B = 13$$

$$i_B = 3.4 \text{ mA}$$

$$i_C = 14.77 \text{ mA}$$

$$i_E = 14.77 \text{ mA}$$


$$V_o = i_E \times R_E$$

$$\approx 5.762 \text{ kV}$$


Voltage Regulator

**Series
Regulator**

**Shunt
Regulator**

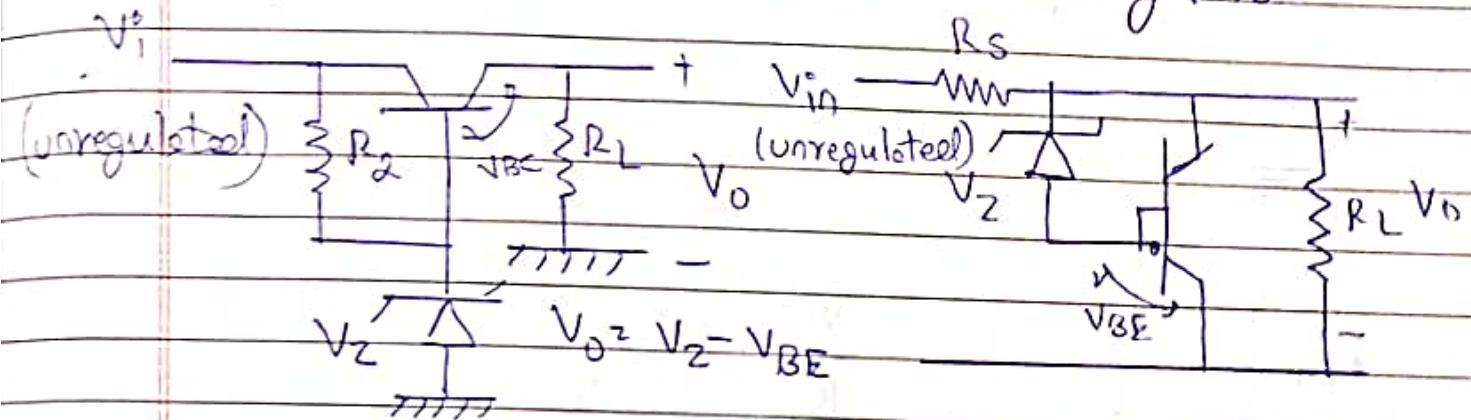

$$V_o = V_Z + V_{BE}$$

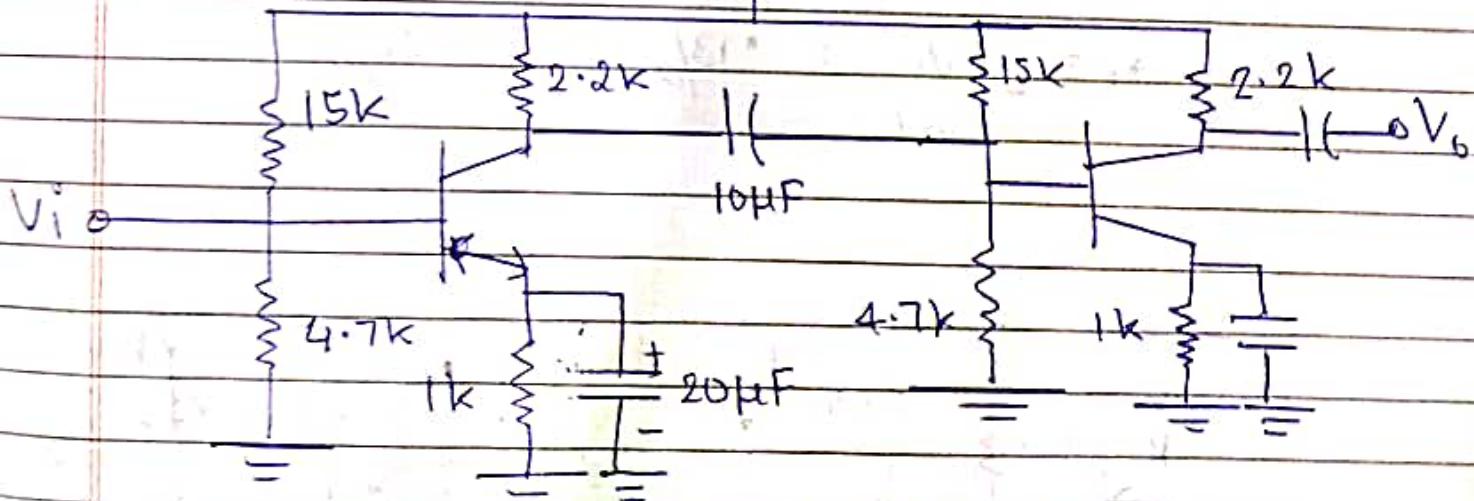


RC coupled BJT

DC analysis capacitor becomes open
 AC analysis capacitor is shorted.

DC analysis to calculate i_e

i_{in}

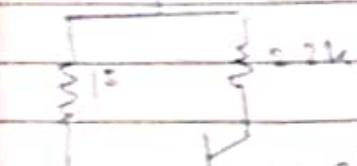

$$\beta = 200 \quad r_{th} = 3.578 \text{ k}\Omega$$


$$V_{th} = \frac{4.7}{4.7+15} \times V_{cc}$$

$$= 4.771 \text{ V}$$

$$i_e = \frac{i_{in}}{R_E} \quad j_S = \frac{V_{th} - V_{BE}}{R_H + (B+1)R_E} = 0.0198 \text{ mA}$$

$$i_e = 3.999 \approx 4 \text{ mA}$$
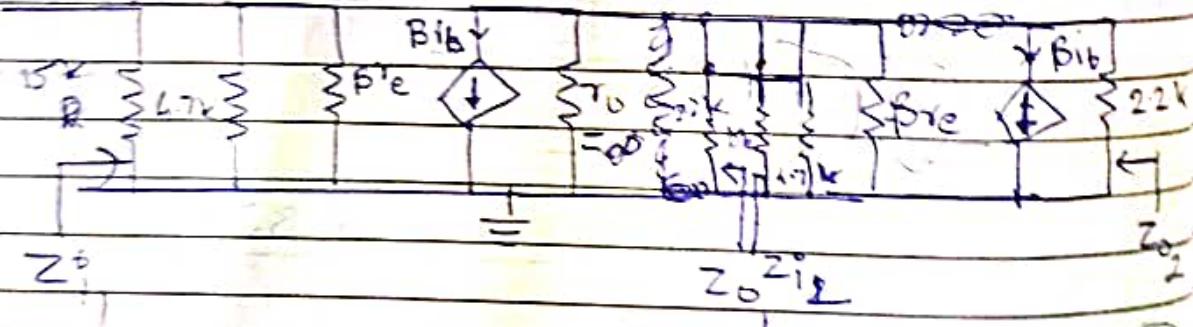
$$g_o = \frac{26 \text{ mV}}{4 \text{ mA}} = 13/2 = 6.5 \text{ }\Omega$$



$$Z_{i1} = 15k || 4.7k || Brce$$

$$Z_o = R_c = 2.2k$$

$$A_{V1} = \frac{R_c || R_L}{r_e}$$

$$A_{V2} = R_c/r_e$$

$$\left\{ A_{o1} = A_{V1} \times A_{V2} \right\}$$

$A_{v2} = \frac{1.3524 \times 10^3}{6.5}$ $= -209.6$	$A_{v2} = \frac{1.0223 \times 10^3}{6.5}$ $= -156.4$
$A_{ov} = 30$	$A_{ov} = 3.4 \times 10^4$

Revision :

- * DC biasing \rightarrow fixed self E.D common base {Revise all numericals done in class & tut}
- * T_a model \rightarrow Emiss. follower
- * approx. hybrid model
- * Darlington Pair
- can ask to draw ckts (DC, remodel, approx. hybrid)


{No AC analysis of Darlington} / Only DC Analysis

* Voltage shunt/series regulator (ckt diagram)
(2 or 3 mks)

* Exact hybrid model . (Formula based)

Field effect Transistor

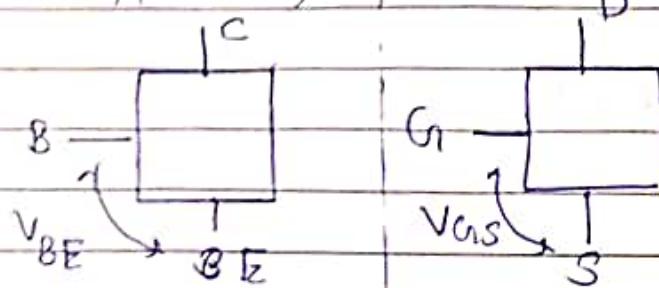Bipolar \rightarrow BJT current controlled devices
 Unipolar \rightarrow FET voltage controlled devices
 (n-channel, p-channel)



Base, Collector,
Emitter

Gate, Drain, Source

FET

JFET
Junction
Field effect
Transistor

$\{ V_{GS} \rightarrow I_D \}$


MOSFET


Metal - oxide (SiO_2)
Semiconductor
field effect
Transistor

JFET { n - channel
p - channel

→ enhancement
type

→ Depletion type

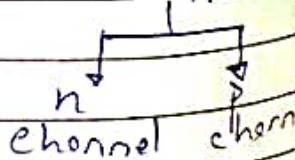

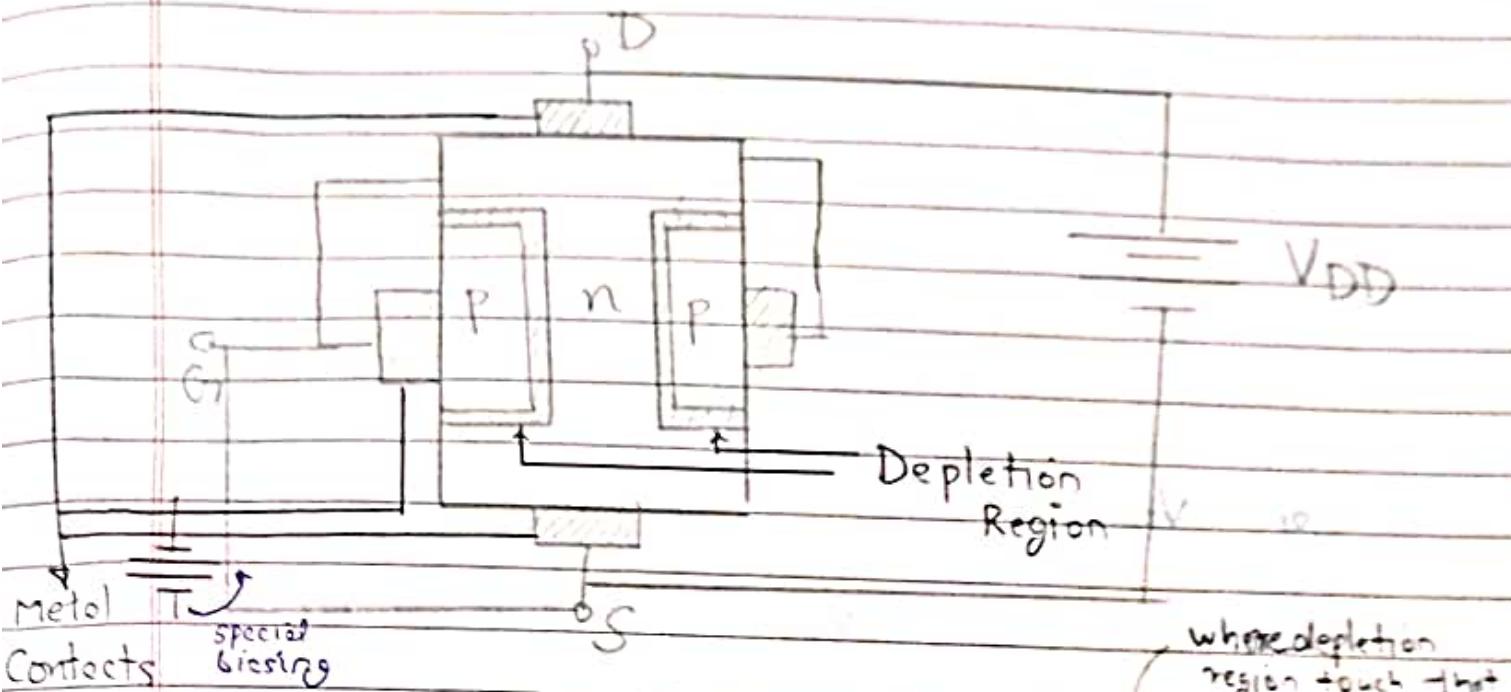JFETn-channel JFET


Cases :

- ① $V_{GS} = 0 \text{ V}$
- ② $V_{DS} = V_{DD}$

[As $V_{DS} \uparrow$, I_D reaches saturation & becomes constant] {★ $I_{Dr} = 0$ (always) some $\star \approx V_{EE}$ in BTI }

when depletion region touch that point \rightarrow called pinch off voltage

* { $I_D = I_S$ }

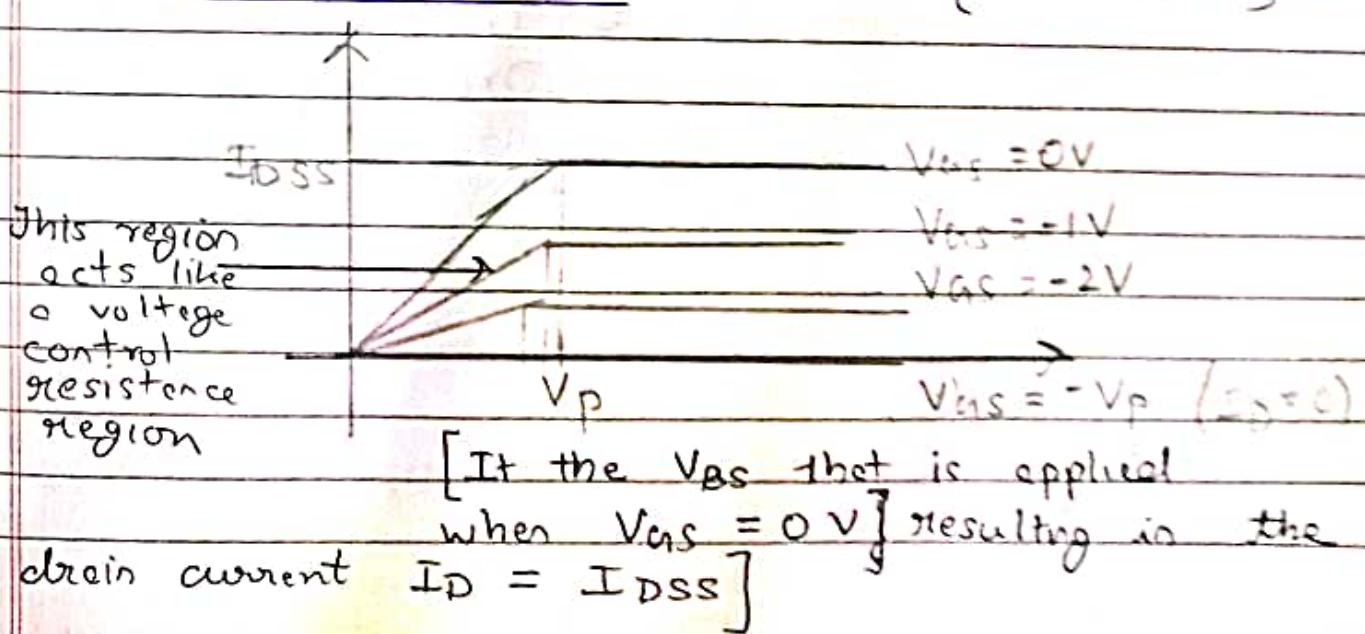Drain Characteristics

Current
Drain to Source gate shorted

If a battery is applied between gate and source then saturation occurs at a lower I_D

The effect of applying 've' bias between gate and source is that we achieve the same depletion region as $V_{GS} = 0$ V, but at a lower value of V_{DS} .

When we apply $V_{GS} = V_p$ drain current = 0.

$I_D = 0$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 \quad (\text{Standard Relation})$$


(fig. 10) $\alpha = 1 - \frac{V_{GS}}{V_p} \Rightarrow$ gate to source voltage
 $V_p \Rightarrow$ pinch off voltage
 $I_{DD} \Rightarrow I_{DSS} \quad (\text{Drain to Source})$

Drain characteristic \Rightarrow Transfer characteristic

Transfer
characteristics

I_D

Drain characteristics
n-channel

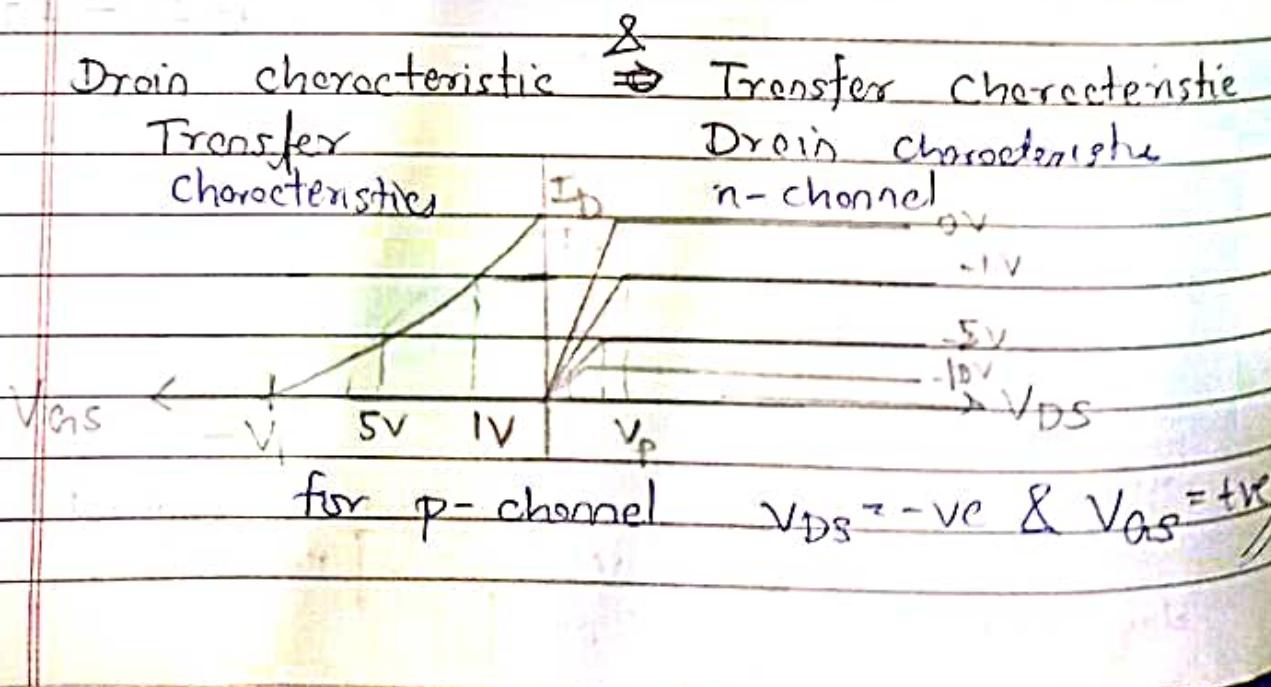

$$I_{DS} = \left[1 - \frac{V_D}{V_T} \sqrt{\frac{2D_S}{3V_T}} \right] V_D$$

Draw the transfer characteristic for a JFET having relation when $D_{SS} = 12 \text{ mV}$ and $V_F = 6V$


i) $I_D = D_{SS} \left(1 - \frac{V_{DS}}{V_F} \right)^2$

when $V_{DS} > 0$

$$I_D > D_{SS} > 12 \text{ mV}$$

ii) when $V_{DS} < -V_F = -6V$

$$I_D = 0$$

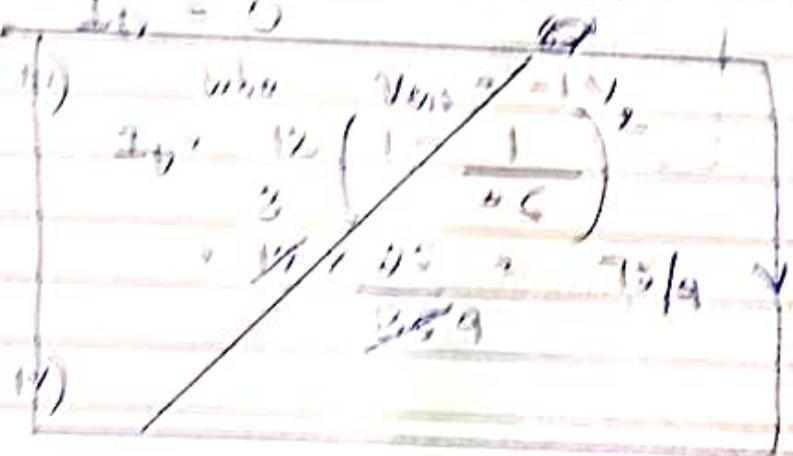


iii) when $V_{DS} > \frac{V_F}{2}$

$$I_D = D_{SS} \left(1 - \frac{1}{2} \right)^2 = \frac{D_{SS}}{4}$$

iv) when $|V_{DS}| > |D_{SS}|/2$


$$\frac{D_{SS}}{2} > I_{DS} \left(1 - \frac{V_{DS}}{V_F} \right)^2$$

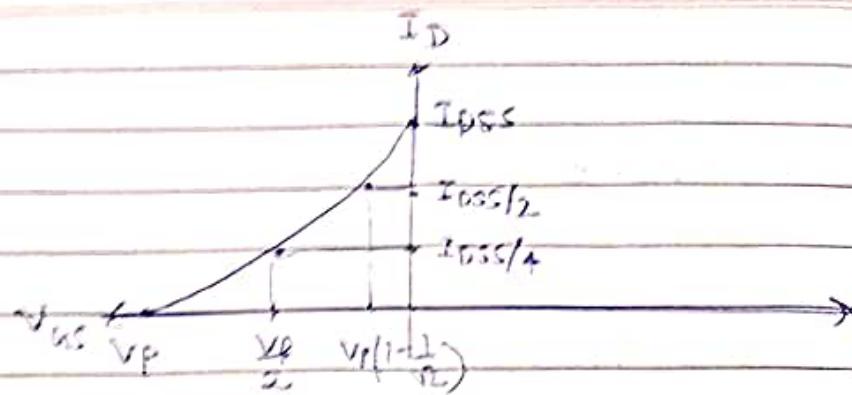
$$V_{DS} > V_F \left(1 - \frac{1}{2} \right)$$



V_{DS}	I_D	Generalized Table
0	I_{DD}	
V_P	0	
$V_D/2$	$I_{DS}/2$	
$V_P(1 - \frac{1}{\sqrt{2}})$	$I_{DS}/2$	

Depletion Type MOSFET

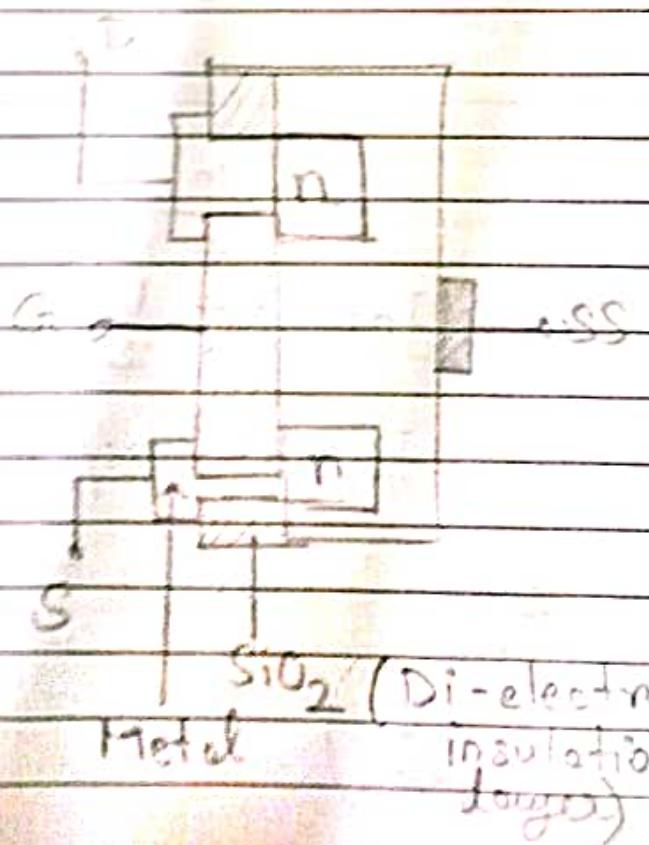

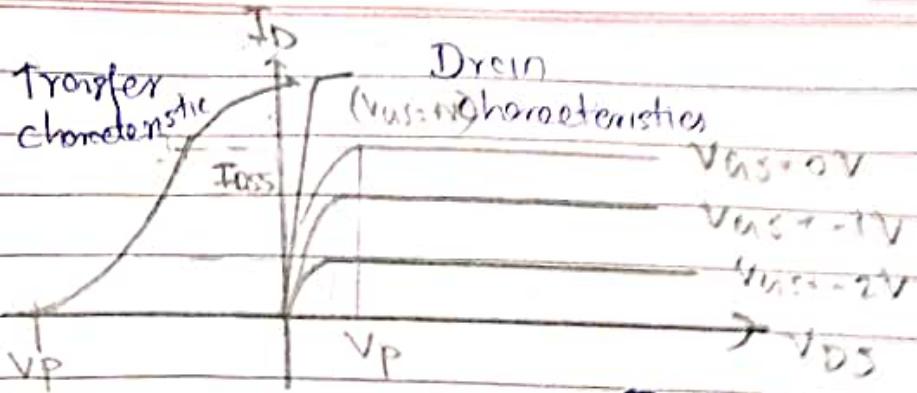

1) $V_{GS} = 0$
 $V_{DS} = +ve$

2) $V_{GS} = -ve$
 $V_{DS} = +ve$

3) $V_{GS} = +ve$
 $V_{DS} = +ve$

$V_{DS} = +ve$
 $V_{GS} = -ve$

1) Free electrons in n-channel will establish \rightarrow current just like J-FET.

2) The saturation is achieved at a lower voltage just like JFET.

3) When gate is made +ve, it will attract electrons from the p-substrate and the accelerating particle establishes new free electrons by collision.

drain

Thus the current increases drastically. So we have to ensure that it does not exceeds the maximum power rating of the device.

In MOSFET the transfer characteristic has both depletion region & enhancement region.

Draw the transfer characteristic for n-channel depletion MOSFET having $I_{DSS} = 10 \text{ mA}$ and $V_P = -4 \text{ V}$

$$\begin{array}{c} I_D \\ \text{---} \\ 0 \end{array} \quad \begin{array}{c} V_{GS} \\ \text{---} \\ 0 \end{array} \quad \begin{array}{c} I_D \\ \text{---} \\ I_{DSS} \end{array}$$

$$\begin{array}{c} V_P \\ \text{---} \\ 0 \end{array}$$

$$\begin{array}{c} V_P \\ \text{---} \\ \frac{V_P}{2} \end{array} \quad \begin{array}{c} I_{DSS}/4 \\ \text{---} \\ - \end{array}$$

$$\frac{I_{DSS} \cdot I_{DSS}(-V_P)^2}{2} = \frac{V_{GS}^2}{V_P}$$

$$V_P \left(1 - \frac{1}{\sqrt{2}}\right) \leq \frac{V_P}{2}$$

$$I_{DSS}/2$$


V_{GS}	I_D
0	I_{DSS}
V_P	0
$V_P/2$	$I_{DSS}/4$
$V_P(1 - 1/\sqrt{2})$	$I_{DSS}/2$

$$V_{GS} = +ve$$


$$\begin{aligned} I_D &= I_{DSS} \left(1 + \frac{V_{GS}}{V_P}\right)^2 \\ &= 10 \left(1 + \frac{1}{4}\right)^2 \end{aligned}$$

$$\frac{25}{16} \times 10^2 = 15.625 \text{ mA}$$

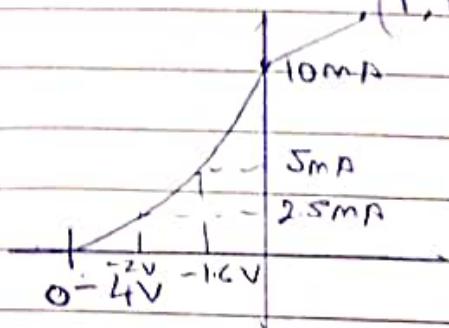[All eqn of JFET are valid for depletion n MOSFET]
(1, 15.55)



Enhancement Type MOSFET

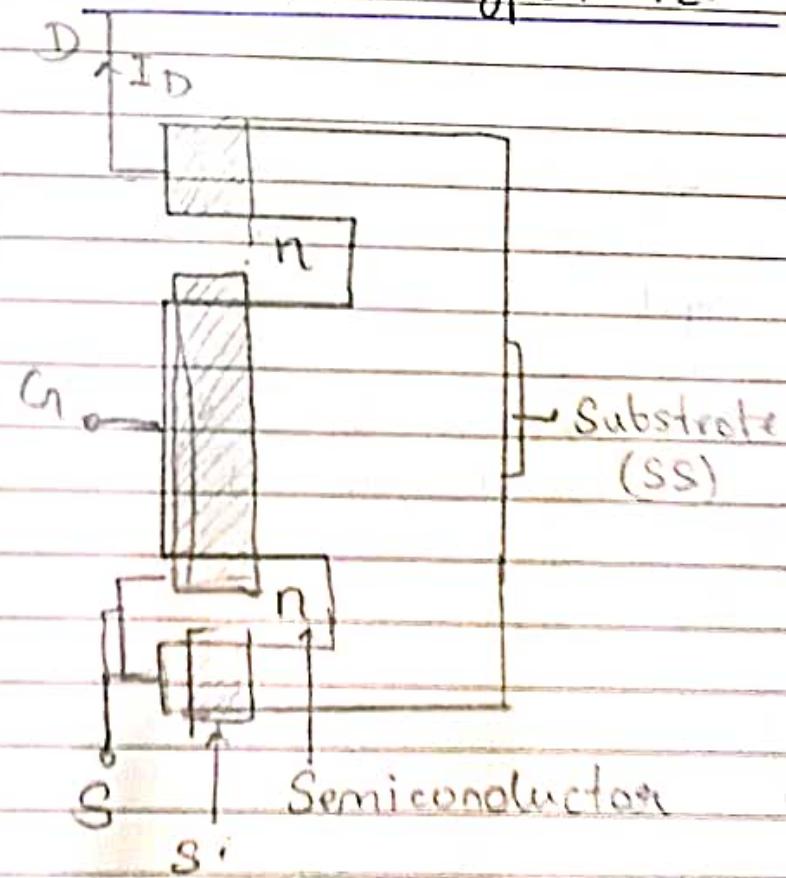

1) Shockley eqn do not hold in Enhancement type MOSFET.

2) $V_{GS} = 0V$

$V_{DS} = +V_C$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

When $V_{GS} = 0$ & $V_{DS} = +ve$ the absence of n channel between drain and source will not allow any electrons to flow.


$$V_{GS} = 0V$$

2) $I_D = 0$ (absence of n channel)
 $V_{DS} > +ve$

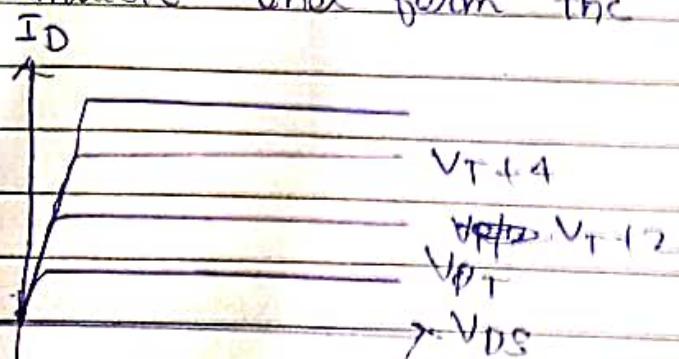3) $V_{GS} = +ve$ ($V_{threshold}$)
 $V_{DS} = +ve$ (enhancement)

* When gate is made +ve with respect to source it attracts electrons from p substrate and repels the holes.

* When the V_{GS} voltage is increased to a threshold value V_P sufficient electrons accumulate and form the channel.



The current flow is enhanced by applying +ve V_{GS} , so it is called as enhancement type MOSFET.

iv) $V_{GS} = \text{constant}$ and $\geq V_T$

The behaviour is like JFET and depletion type ~~MOSFET~~ JFET and $V_{DS} = -V_D$.

The drain current equation is,

$$I_D = k(V_{GS} - V_T)^2$$

$$V_{DS, \text{sat}} = V_{GS} - V_T$$

Draw the transfer characteristic of an enhancement type MOSFET if $V_P = 2V$ and $V_{GS} = 3V$.
 $I_D = 10 \text{ mA}$.

$$\textcircled{1} I_D = 0$$


$$V_{GS} = V_T$$

$$\textcircled{2} V_{GS} = V_T \quad I_D = 10 \text{ mA}$$




$$k > \frac{10}{5/18}^2 = 0.277 \text{ mA/V}^2$$

$$\textcircled{3} I_D = \frac{V_{GS} - V_T}{2}$$


~~Q~~ ~~Q~~

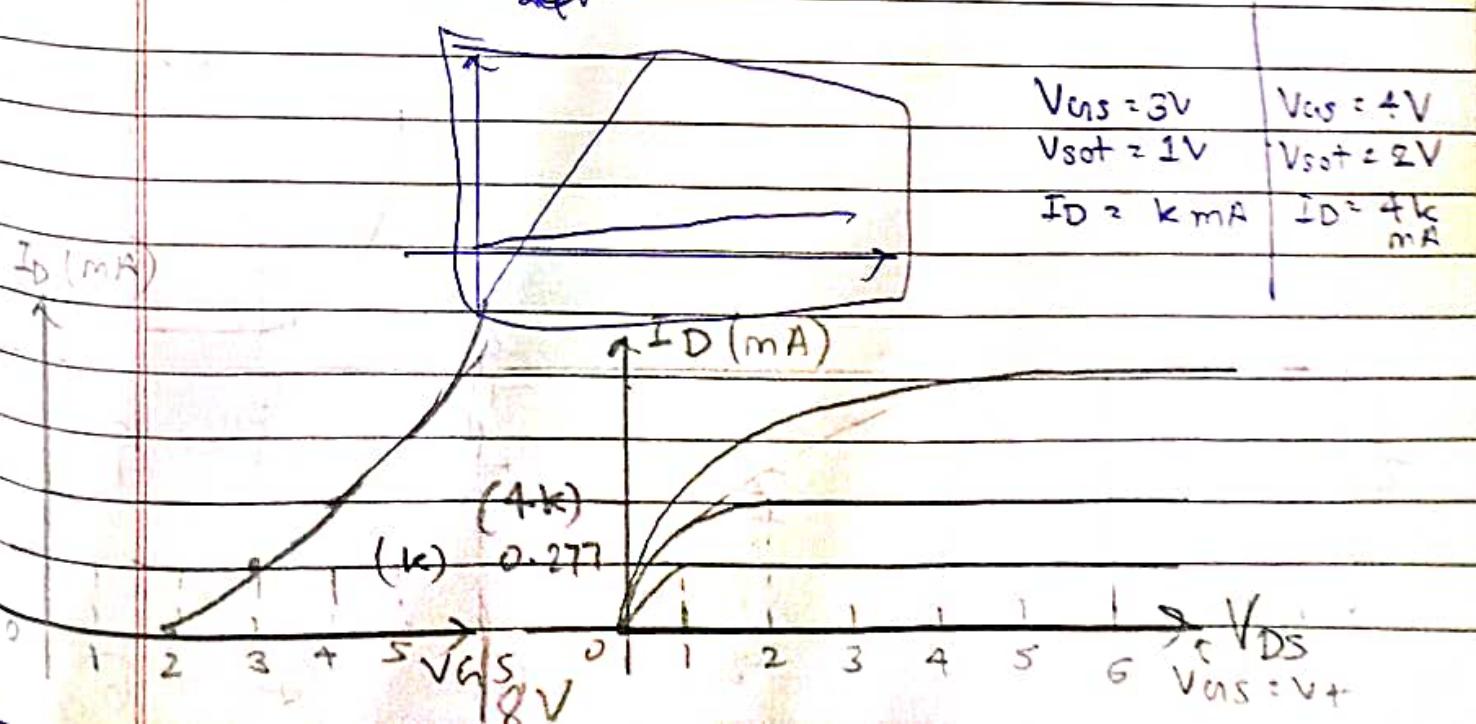


n channel JFET

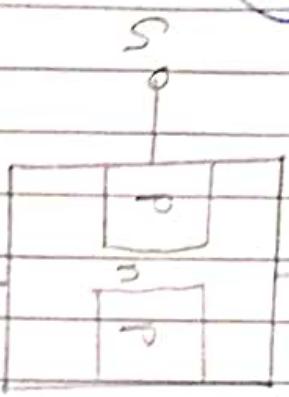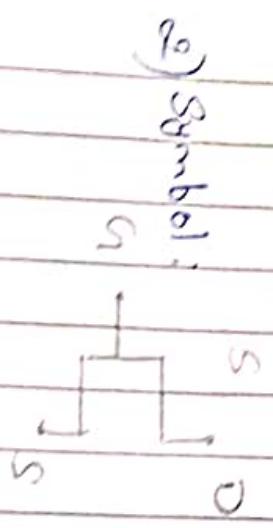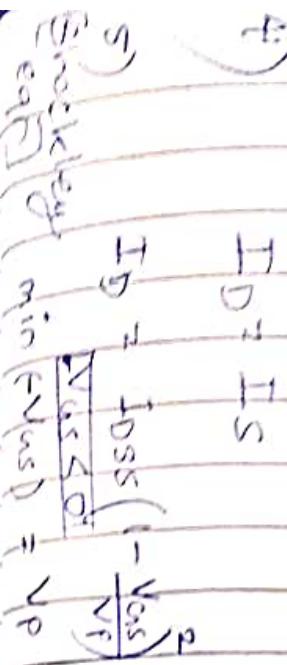

n channel depletion MOSFET

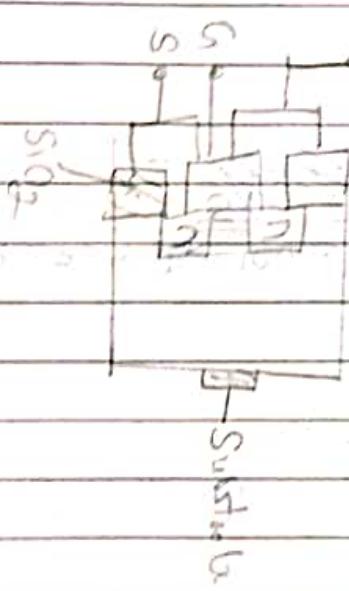

n channel enhancement MOSFET

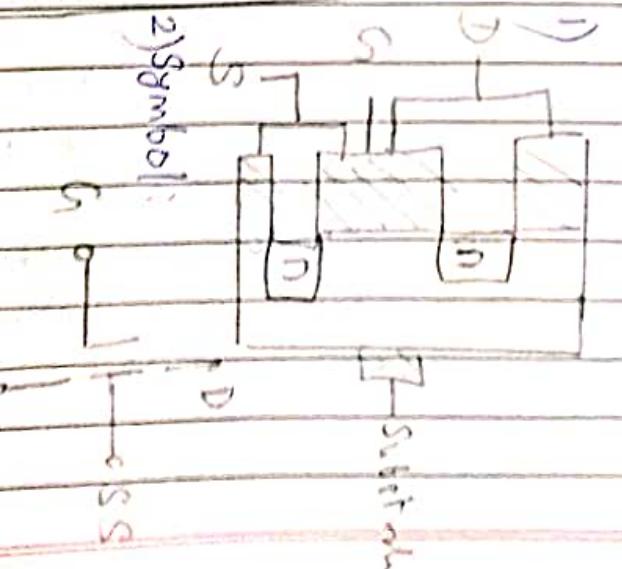

(1) $I_D = I_{DS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$

(2) $I_D = I_S \left(1 - \frac{V_{GS}}{V_P} \right)^2$

(3) $I_D = I_S \left(1 - \frac{V_{GS}}{V_P} \right)^2$

(4) $I_D = I_S \left(1 - \frac{V_{GS}}{V_P} \right)^2$


(5) Smockley eqn places hole

$I_D = k(V_{GS} - V_T)^2$

$V_{GS} = V_{GS}^* + V_T$

Fixed Bias

I_C bias working out
from I_{CQ}

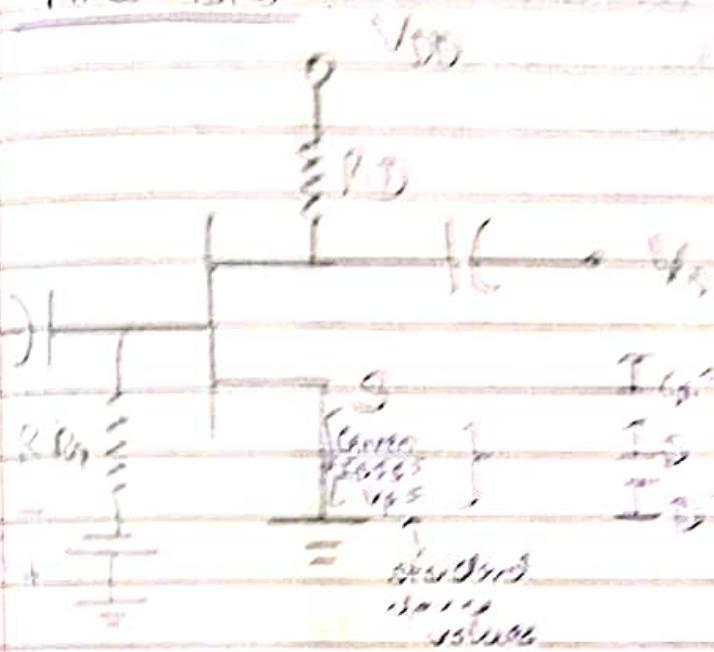


Steps:

i.) O.C all capacitors.

ii.) $I_C = 0$

iii.) $V_{CE} = I_{CQ} R_E = 0$

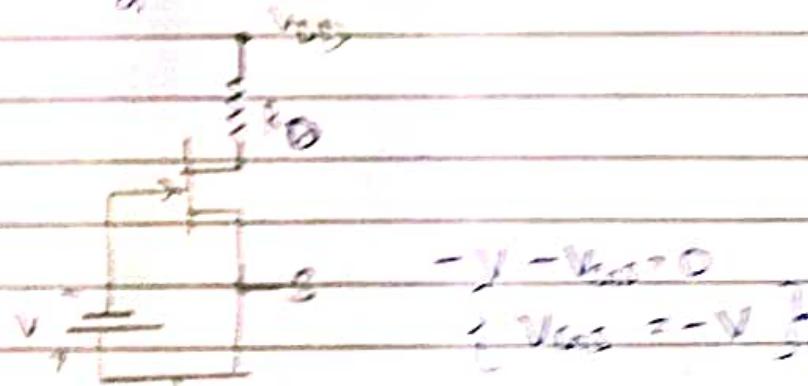

$$V_{CE} - I_{CQ} R_E = 0 \quad I_{CQ} = I_{CQ} \left(\frac{V_{CC} - V_{BE}}{R_E} \right)$$

$$I_{CQ} = I_{CQ} \left(\frac{V_{CC} - V}{R_E} \right)$$

For a fixed bias configuration, $V_D = 16V$, $R_D = 2k\Omega$,
 $V_{GS} = 2V$, $R_{in} = 1k\Omega$. Draw transfer characteristic
 & load line. $I_{DSS} = 10mA$ & $V_P = -8V$.

$$V_{GS} = -V_{GD}$$


$$= -2V$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$= 10 \left(1 - \frac{-2}{-8} \right)^2 = 10 \times \frac{9}{16}$$

$$= 10 \left(\frac{3}{4} \right)^2 = \frac{75}{5.625} mA$$

$$\varphi = (-2V, 7.5mA)$$

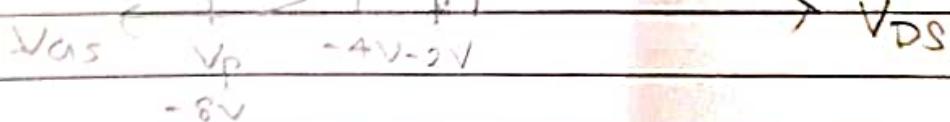 I_D $I_{DSS} = 10mA$ $5.625mA$ $2.5mA$ $1mA$ $500\mu A$ 

$$V_{RD} = 2 \times 5.625$$




$$= 11.250 mA$$

$$V_{DS} = 16 - 11.250$$

$$= 4.75 V$$

$$V_D = 4.75V$$

$$V_S = 0V$$

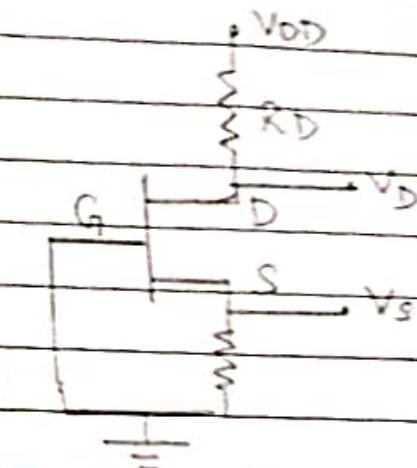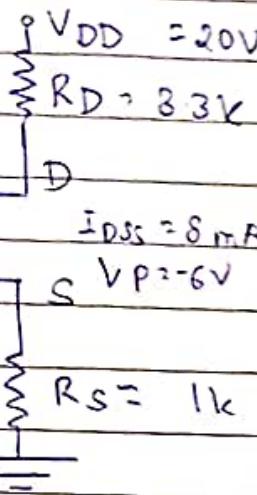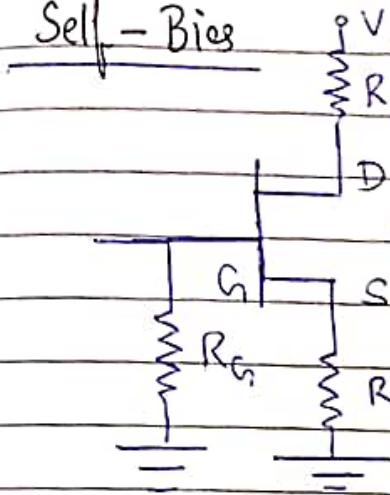Self-Bias

$$I_G = 0 \text{ mA}, V_{RG} = 0 \text{ V}, I_S = I_D$$

$$-V_{GS} - I_S R_S = 0$$

$$\left\{ V_{GS}^2 - I_S R_S \right\} - \textcircled{1}$$

$$I_D^2 = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 - \textcircled{2}$$


→ Analytical Method
→ Graphical Method

$I_D \Rightarrow$ Q. Quadratic equation

$$V_{DS} = V_{DD} - I_D R_D$$

$$- I_D R_S$$

$$V_S = I_D R_S$$

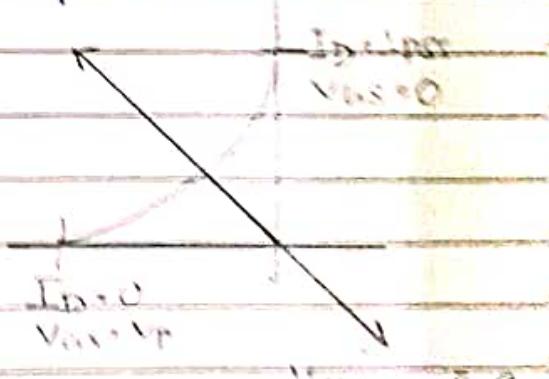

~~V_{GS} → -V_P~~

$$I_D^2 = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\Rightarrow 8 \left(1 + \frac{V_{GS}}{V_P} \right)^2$$

$$\frac{V_{GS}}{R_S} = \frac{8}{36} (G + V_{GS})^2$$

~~V_{GS} = -I_SR_S~~
~~[from eq. of straight line]~~

$$\frac{-V_{DS}}{1} = \frac{8}{36} (36 + V_{DS}^2 + 12V_{DS})$$

$$-\frac{36V_{DS}}{8} = 36 + V_{DS}^2 + 12V_{DS}$$

$$V_{DS}^2 + 16.5V_{DS} + 36 = 0$$


$$V_{DS} = -2.5876 \text{ V}$$

$\Rightarrow -13.9123 \text{ V}$ // Not possible


$$\therefore V_{DS} = -2.5876 \text{ V}$$

$$I_D = I_S = -\frac{V_{DS}}{R_S}$$

$$2.5876 \text{ mA}$$

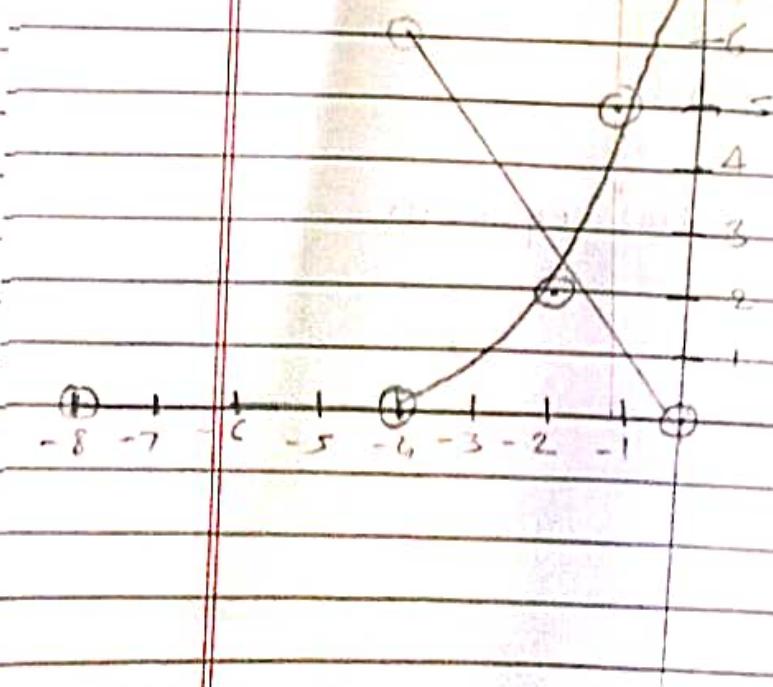

Voltage Divider Bias

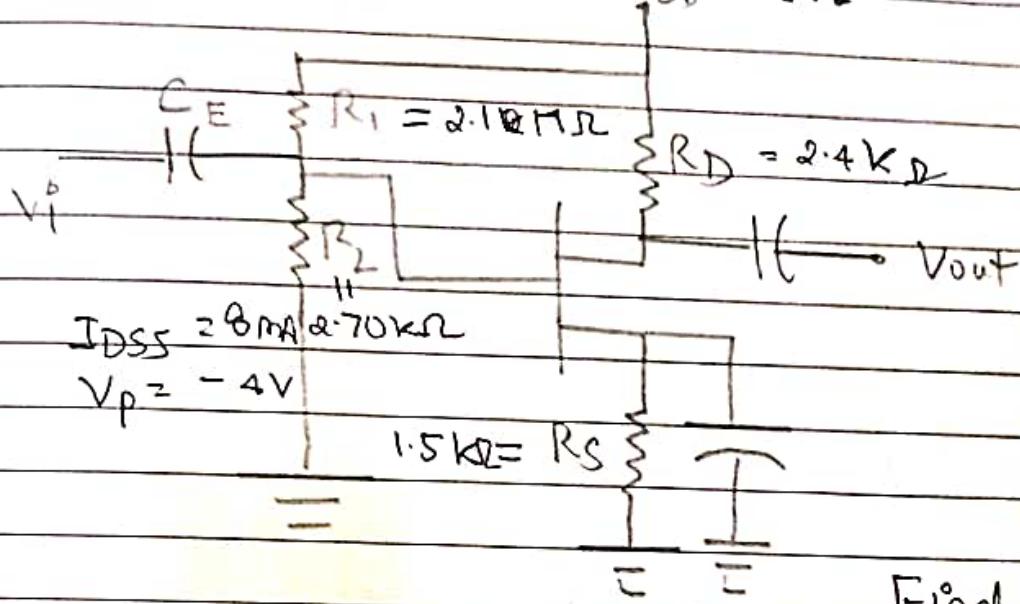


Find

I_{DQ} , V_{GSQ} ,
 V_{D1} , V_S , T , V_{DS}

$$R_{Th} = R_p = \frac{R_1 R_2}{R_1 + R_2}$$

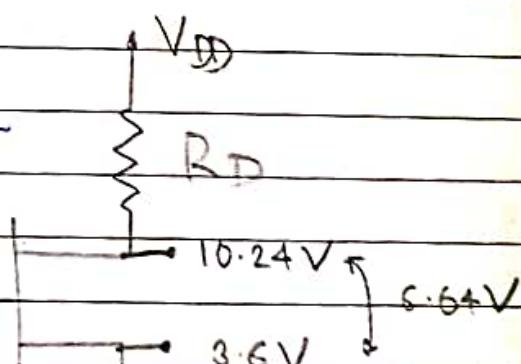
$$V_{Th} = \frac{V_{DD}}{R_1 + R_2} \cdot R_2$$



No $\rightarrow R_{Th}$

voltage
 drop
 across
 R_{Th} .

$\{I_{Ch} = 0\}$

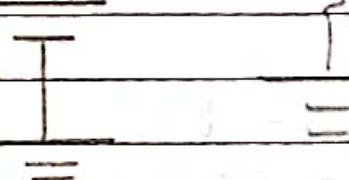

$$V_{Th} = \frac{16 \times 2.70}{270 + 2100}$$

$$V_{Th} - V_{GS} - I_D R_S = 0$$


$$V_{GS} ? \quad V_{Th} - I_D R_S =$$

$$= \frac{0.022}{1.822}$$

$$V_{GS} = 1.82 - I_D (1.5)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

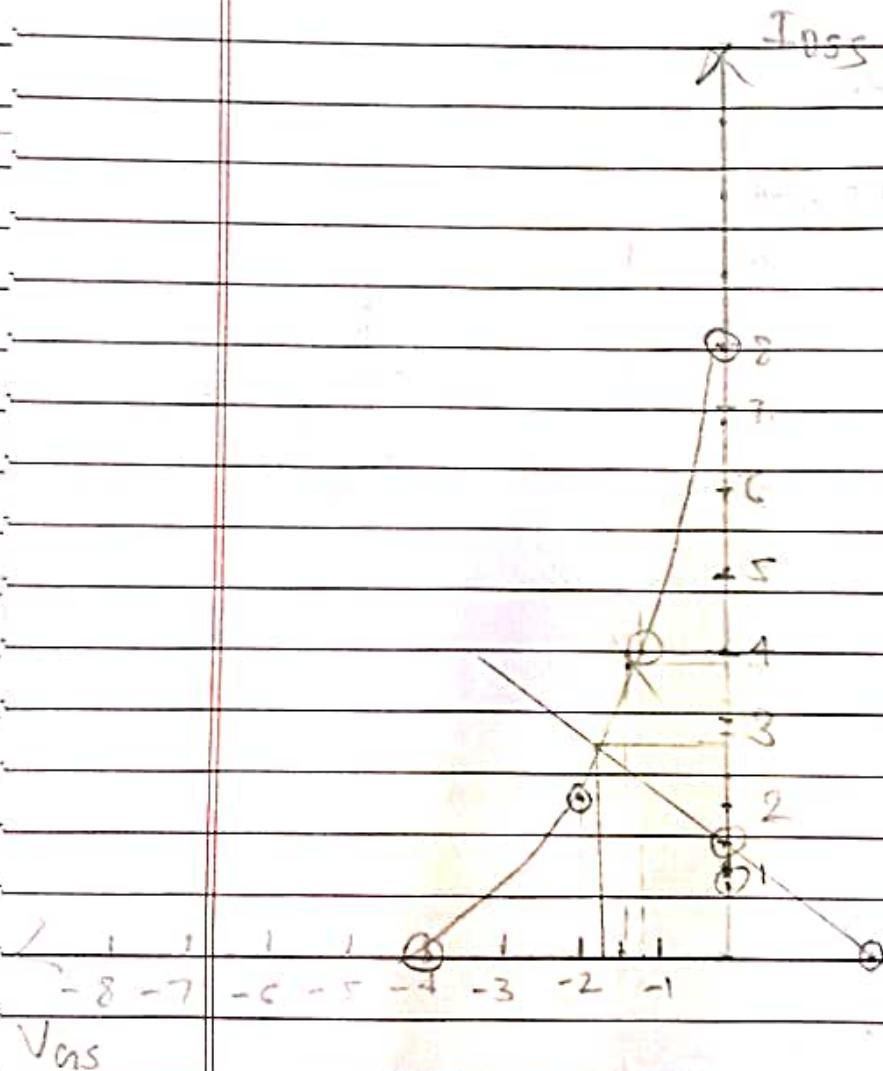
$$= 8 \left(1 - \frac{V_{GS}}{V_P}\right)^2$$



$$V_{GS} = -1.8 \text{ V}$$

$$I_D = 2.7 \text{ mA}$$
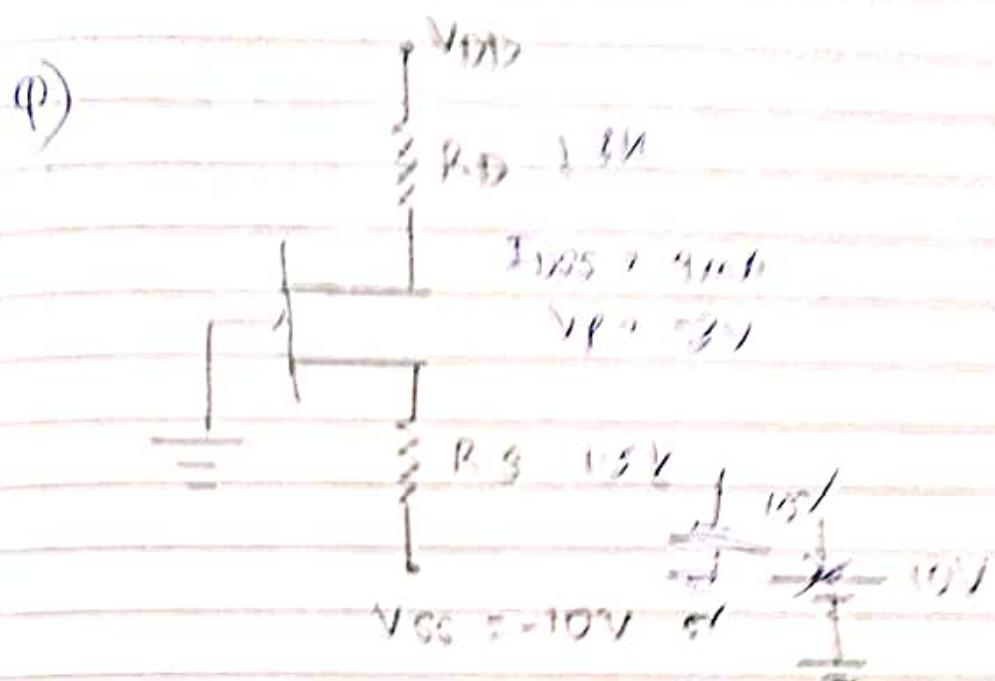
$$2.75 \Omega + 20 \frac{\text{V}}{\text{A}}$$




Find I_{DSQ} , V_{DSQ} , V_{GS} , V_{DS} , V_c

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_F} \right)^2$$

$$-V_{GS} = I_D R_S = 10 \text{ mV}$$

$$V_{GS} = I_D R_S = 10 \text{ mV}$$

$$V_{GS}^2 = 10^2 = 100 \text{ mV}^2$$

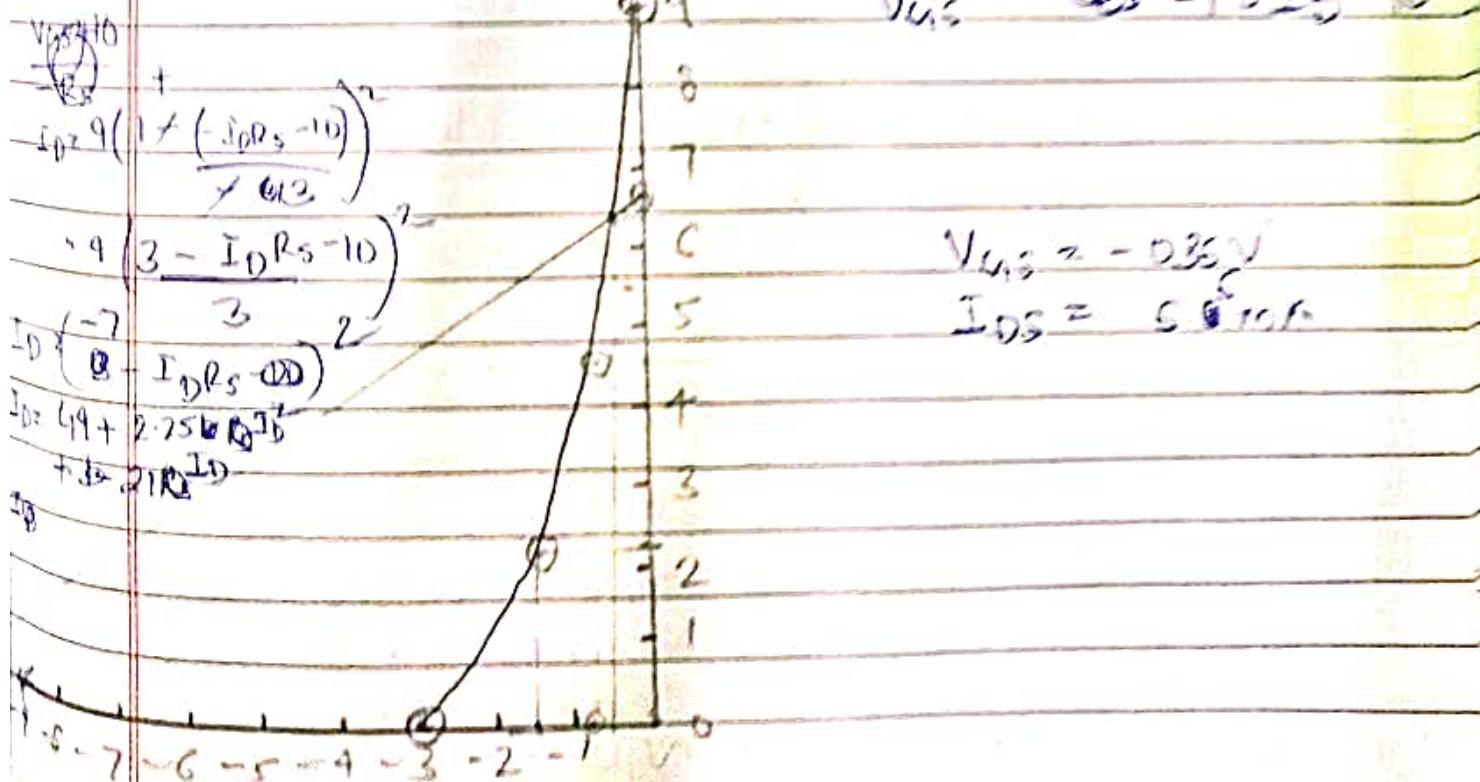


$$V_{DS} = -0.3 \text{ V}$$


$$I_{DS} = 5 \text{ mA}$$

1) Depletion MOSFET is like JFET it has both enhancement & depletion region.

2) Symbol changes

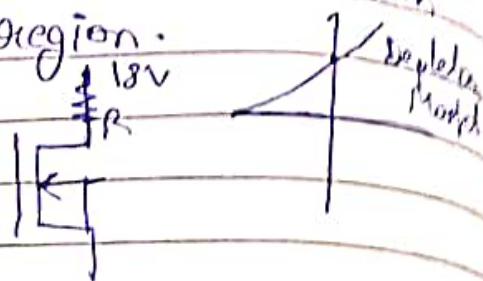

(Q)

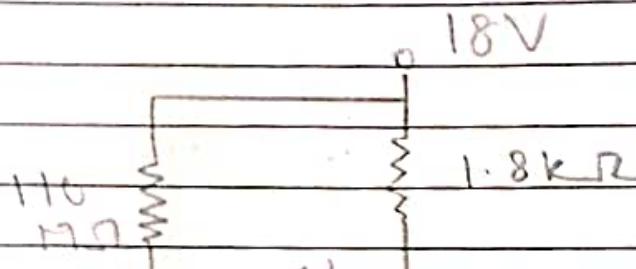

$$V_p = -3V$$


$$I_{Dss} = 6mA$$

$\approx 750\ \Omega$

Final
operating
point & load
line.

$$R_{th} = 9.167\ M\Omega \Rightarrow 9167\ k\Omega$$

$$V_{Th} = 1.5\ V$$

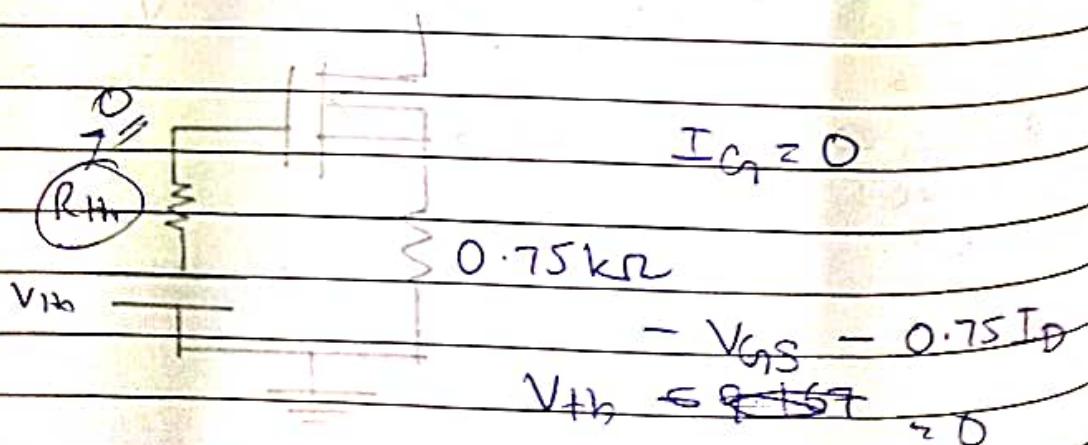

$$9.5 = V_{Th} = V_{GS} + 0.75 I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{DS}}{V_F} \right)^2$$

$$I_D = \frac{6}{3} \left(1 + \frac{V_{GS}}{3} \right)^2$$

$$I_D = 6 \left(3 + 1.5 - 0.75 I_D \right)^2$$

$$I_D = \frac{2}{3} \left(4.5 - 0.75 I_D \right)^2$$

$$1.5 I_D = 20.25 + 0.5625 I_D^2 - 6.75 I_D$$

$$0.5625 I_D^2 - 8.25 I_D + 20.25 = 0$$


$$I_D = 11.549 \text{ or } 3.116 \text{ mA}$$

A


$$V_{GS} = -7.161 \text{ V or } -0.837 \text{ V}$$

not possible
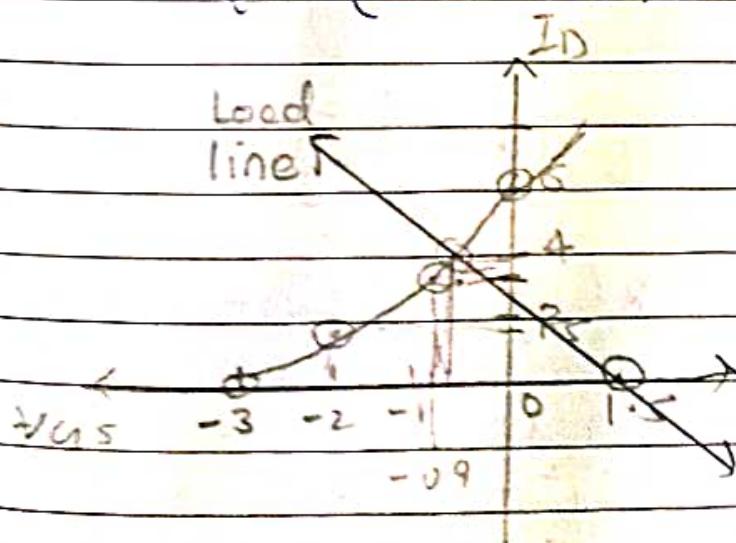
$$Q \in (-0.837 \text{ V}, 3.116 \text{ mA})$$



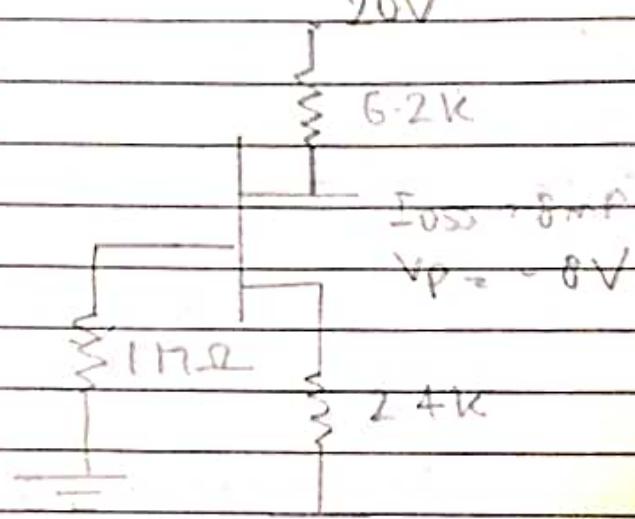Q) For a self bias ckt using depletion MOSFET
find the operating point if $\kappa_d = 6.2 \text{ k}$
 $\kappa_s = 2.4 \text{ k}$, $r_{dg} = 1 \text{ M}\Omega$, $I_{DSS} = 8 \text{ mA}$
 $V_{G_S} = -8 \text{ V}$, $V_{D_S} = 20 \text{ V}$



$$-V_{G_S} - I_D (2.4) = 0 \quad V_{G_S} = -I_D (2.4)$$

$$I_{D_S} = I_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{G_S}}{V_P} \right)^2$$

$$\Rightarrow 8 \left(1 + \frac{V_{G_S}}{8} \right)^2$$

$$= 8 \left(1 - \frac{24 I_D}{8} \right)^2$$

$$I_D = 8 \left(1 + 0.09 I_D^2 - 0.6 I_D \right)$$

$$0.125 I_D = 1 + 0.09 I_D^2 - 0.6 I_D$$

$$0.09 I_D^2 - 0.725 I_D + 1 = 0$$


$$I_D = 6.288 \text{ mA}$$

$$I_{D2} = 1.766 \text{ mA}$$

$$V_{G_S} = -15.09 \text{ V} \quad \text{X}$$

$$V_{G_S} = -4.238 \text{ V}$$

$$\Phi = (-4.238V, 1.706mA)$$

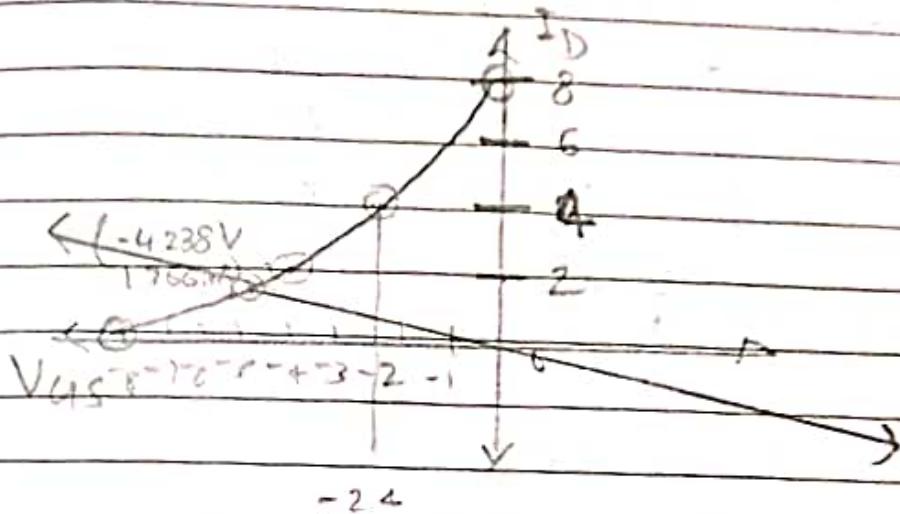


$$V_S = 4.2V$$

~~$V_D = 20V$~~

$$20 - V_D = 6.2 \times I_D$$

$$V_D = 9.0508V$$

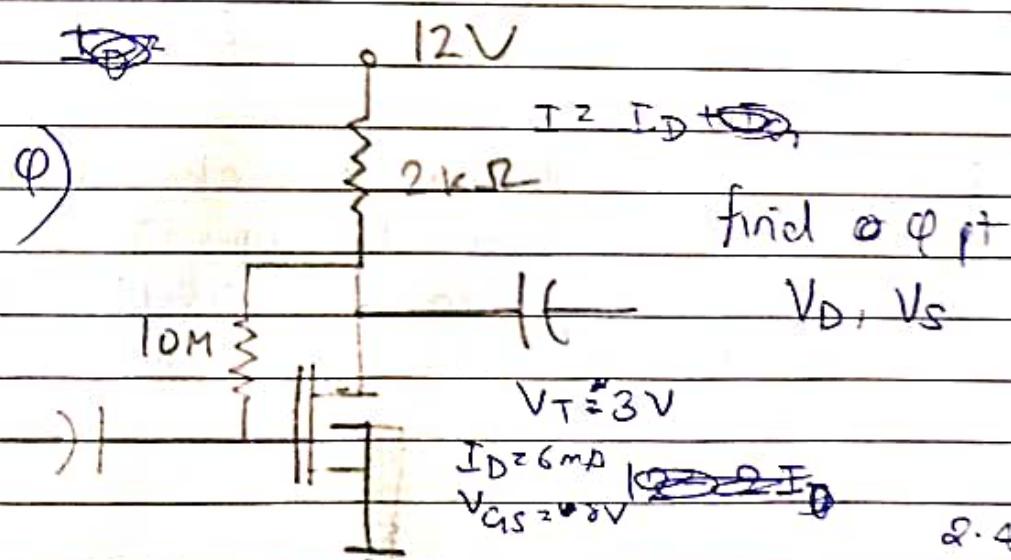

$$12 - I_D(2) - V_{GS} = 0$$

$$12 - V_{GS}$$

$$= 12 - 2I_D - V_{DS}$$

$$I_D = k(V_{DS})^2$$

$$k = \frac{I_D}{(V_{DS})^2}$$

$$= -11.4$$

$$I_D V = k V_{DS}^2$$

$$I_D = k (10 - d I_D - 3)^2$$

$$= k (9 - d I_D)^2 \quad 2000$$


$$\Rightarrow 4 \cdot 10^{-4} \cdot 1000 (9 - d I_D)^2$$

$$4166.67 I_D^2 - 81 + 4 I_D^2 - 86 I_D$$

$$360000000$$

$$4000 I_D^2 - 4000 I_D + 81 = 0$$

$$I_D = 10.5063$$

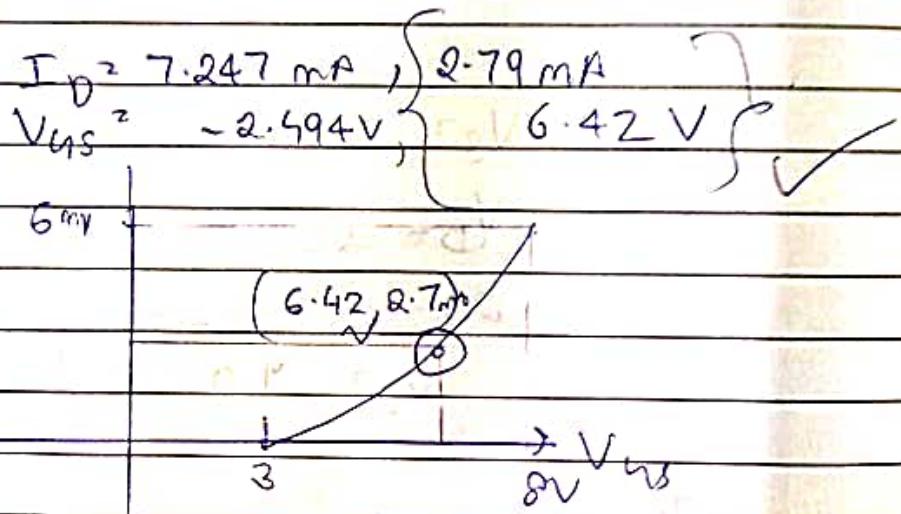

Q) For a voltage divider bias ckt. using enhancement type MOSFET find the operating point V_{DS} , V_D , V_S & draw load line & transfer characteristic for the following parameters.

$$V_{DD} = 40 \text{ V}$$

$$R_1 = 22 \text{ M}\Omega$$

$$R_2 = 18 \text{ M}\Omega$$

$$R_D = 3 \text{ k}\Omega$$

$$R_S = 0.82 \text{ k}\Omega$$

$$I_{D(on)} = 3 \text{ mA}$$

$$V_{DQ10M} = 10 \text{ V}$$

$$V_{GS(\text{threshold})} = 5 \text{ V}$$

Small Signal A.C analysis

BJT


$$I_{E_C} = f(I_B)$$

CE



FET

$$I_D = f(V_{GS})$$

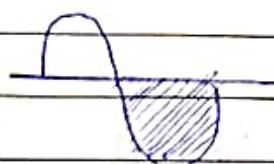~~common~~

common source


CC (Emitter follower)
transistor

Gain = 1 {Source follower}

CB




C (D)

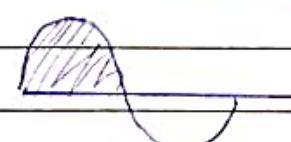


common gate

B(G)

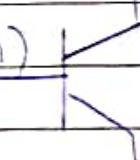

E (S)

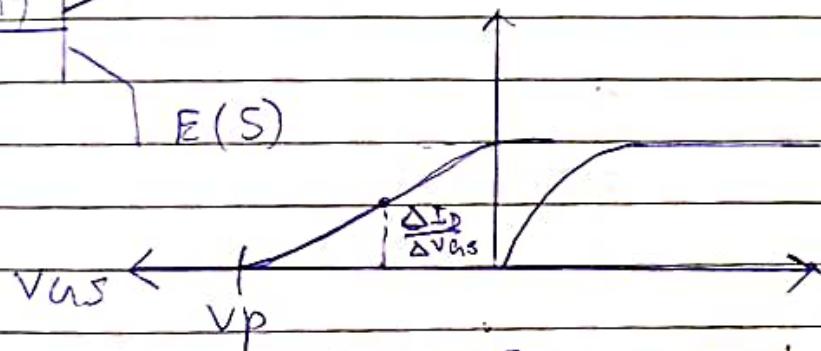 $g_m = \text{Transconductance}$

$$= \frac{\Delta I_D}{\Delta V_{DS}} \quad (\text{Siemens})$$

Transconductance is the slope of point of operation in the transfer characteristics

$$g_m = \frac{\partial I_D}{\partial V_{DS}} = \frac{\partial}{\partial V_{DS}} \left[I_{DSS} \left(1 - \frac{V_{DS}}{V_r} \right)^2 \right]$$

$$= - \frac{I_{DSS}}{V_r} = -2 I_{DSS} \left(1 - \frac{V_{DS}}{V_r} \right) \left(\frac{1}{V_r} \right)$$

$$= \frac{2 I_{DSS}}{V_r} \left(1 - \frac{V_{DS}}{V_r} \right)$$

Final form of magnet

$$\frac{d^2y}{dx^2} = 0$$

$$2x^2 - 2x + 1 = 0$$

II

Blue

Yellow

Green Blue

Enter solution
now

Now \Rightarrow $\frac{dy}{dx}$

II

Blue

Green Blue

Blue

Yellow

III

Blue

Blue

Yellow

$E_0 = \text{magnetic field}$

$\frac{dy}{dx} = \text{Slope}$

$\frac{dy}{dx} \propto 3$

Transverse is the slope of first 3 section
in the graph shown

$$E_0 = \frac{\Delta y}{\Delta x} = \frac{3 E_0}{3 R_0} = E_0$$

$\frac{dy}{dx}$

$\frac{dy}{dx} = \frac{2 E_0}{2 R_0} = E_0$

$$= \frac{2 E_0}{2 R_0} = \frac{E_0}{R_0}$$

Calculate the transconductance value if

$$I_{DSS} = 8 \text{ mA}$$

$$V_P = -4 \text{ V}$$


$$V_{GS} = -0.5 \text{ V}$$

$$g_m = \left| \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P} \right) \right|$$

$$= \frac{2 \times 8 \times 2}{4} \left(1 - \frac{1}{8} \right)$$

$$= \frac{4}{2} \left(\frac{7}{8} \right) = 3.5 \text{ mS}$$
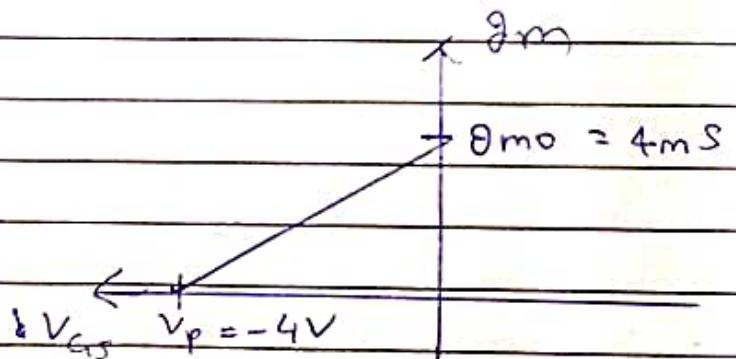
$$g_{mo} = \frac{8 \times 2}{14} = 4 \text{ mS}$$




when $V_{GS} = 0$

$$g_m = \frac{2I_{DSS}}{|V_P|} = g_{mo} \quad \{ \text{fixed value} \}$$

$$\therefore g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_P} \right)$$


$$g_m = g_{mo} \sqrt{\frac{I_D}{I_{DSS}}}$$

point 1
point 2

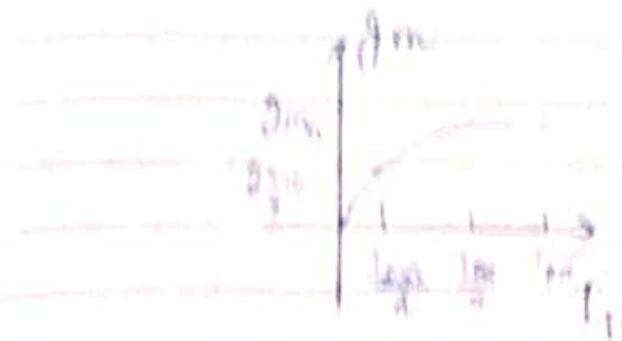

$$g_m \cdot I_f$$

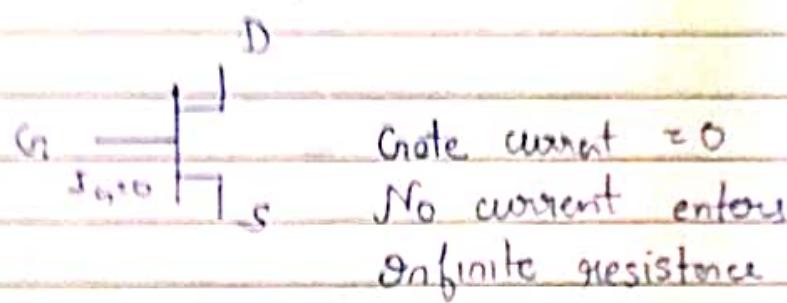In some specification sheets the transconductance parameter g_m is also denoted by y_{fs} , where f stands for forward source.



$$Z_i = \infty$$

$$Z_o = R_o$$

$$R_o = \frac{1}{y_{os}} = \frac{\Delta V_{DS}}{\Delta I_D}$$

$$g_i$$

$$V_{DS}$$

$$8mV_{AS}$$

$$\text{S}$$

$$y_o$$

$$V_{DS}$$

$$R_D$$

$$V_{DD}$$

$$800\Omega$$


$$g_m V_{AS}$$

$$R_G$$

$$V_{out}$$

$$R_B$$

$$y_o$$

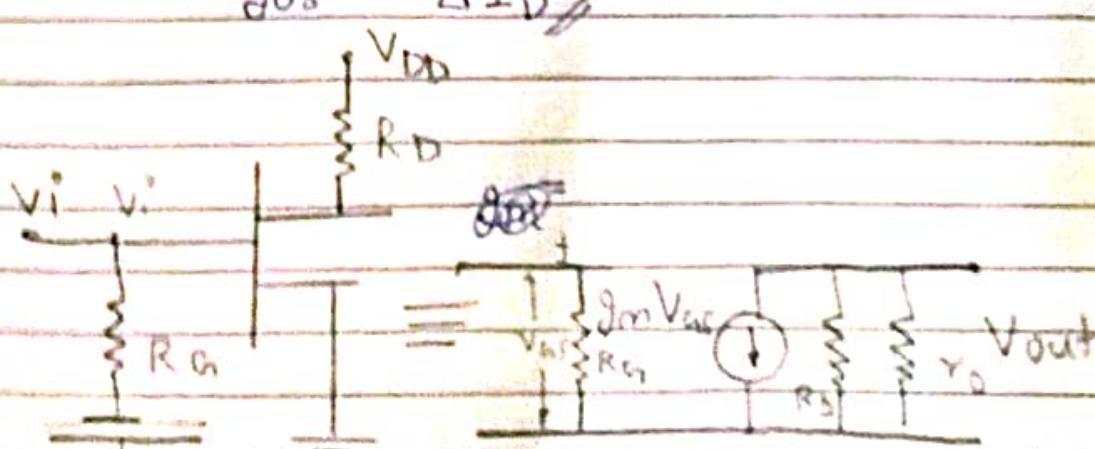

$$Z_i = R_B$$

$$Z_o = R_D || y_o$$

Q) A fixed bias configuration has an operating point defined by $V_{GS0} = -2V$, $I_{D0} = 5.625V$, $I_{DS0} = 10mA$, $V_P = -8V$. The value of $Y_{OS} = 40 \mu S$. Calculate g_{m0} , g_m , z_0 .

$$g_{m0} = \frac{2I_{DS0}}{|V_P|}$$

$$= \frac{2 \times 10}{8} = 2.5 \text{ mS}$$


$$g_m = g_{m0} \left(1 - \frac{V_{GS0}}{V_P}\right)$$

$$= 2.5 \left(1 - \frac{2}{8}\right)$$

$$= 2.5 \times \frac{3}{4} = \frac{7.5}{4} = 1.875 \text{ mS}$$

$$z_0 = \frac{1}{Y_{OS}} = \frac{1}{40} \times 10^6 \times 10^4$$
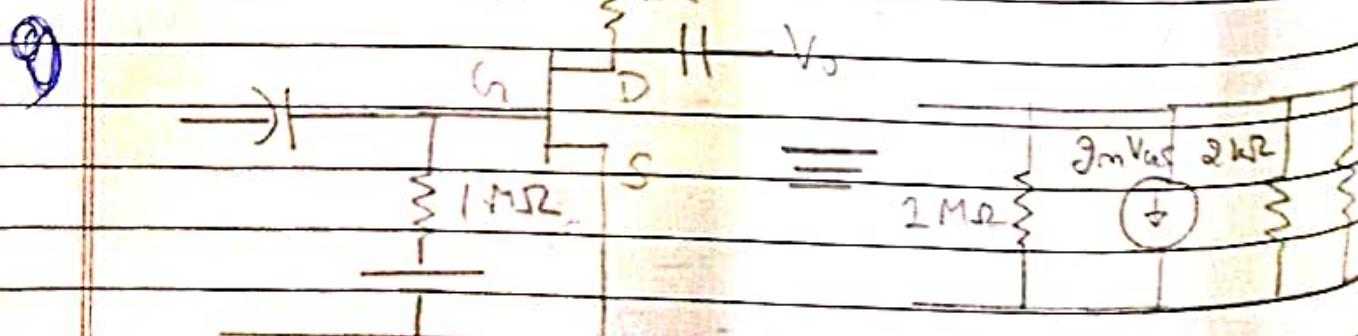
$$\frac{20V}{2.5 \times 10^4 \Omega} = 8 \text{ k}\Omega$$




$$Z_i = 1 \text{ M}\Omega$$

$$Z_o = \frac{2.5 \times 2}{27} = 50/27 \text{ k}\Omega$$

$$= 1.851 \text{ k}\Omega$$

A)

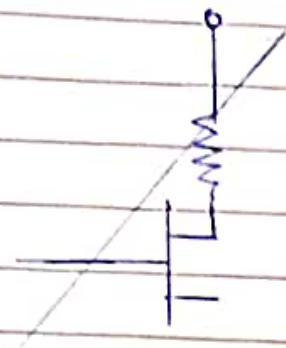



$$A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_i} \text{ Yes}$$

$$A_v = \frac{R_f}{R_i}$$

$$A_v = -1.875 \quad \text{Ans} \\ 2-3.471$$

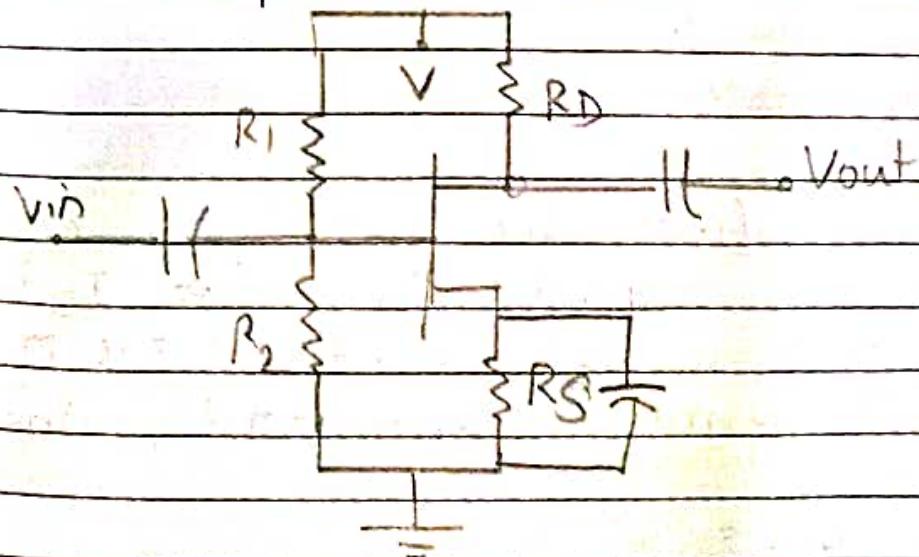* The output voltage is 180° out of phase with the input voltage with respect to



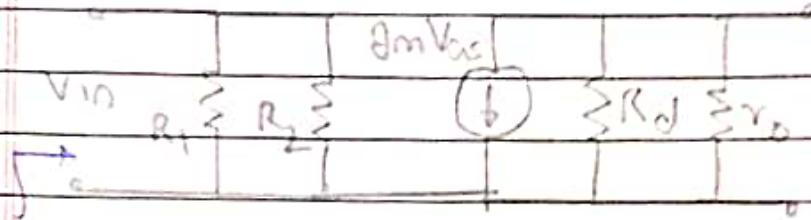

$$Z_{in} = R_1 \parallel R_2$$

$$Z_o = R_L \parallel r_o$$

$$A_v = -\frac{g_m V_{be}}{R_L \parallel r_o}$$

$$= g_m (R_L \parallel r_o)$$

(Q) For a voltage divider bias ckt, $V_{DD} = 10V$, $R_D = 2k\Omega$

μ (v) $R_1 = 220k\Omega$

$$R_2 = 1M\Omega$$

$$R_S = 22k\Omega$$

$$I_{DSS} = 10mA$$

$$V_P = -8V$$

(Q) Design a fixed bias ckt having a gain of 10 and operating point at $I_D = I_{DSS}$

(Q) given gate resistance $= 10M\Omega$, $I_{DSS} = 10mA$, $V_P = -4V$, $Y_{OS} = 20\mu S$

$$Y_{OS} = \frac{1}{r_o}$$

$$r_o = 50k\Omega$$

A_{o2}

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$g_{m0} = \frac{2I_{DSS}}{V_P} = \frac{2 \times 10}{4.2} \approx 5 \text{ mS}$$



$$= 5 \left(1 - 0 \right) = 5 \text{ mS} \quad \left\{ \begin{array}{l} \text{at } I_{DSS} \\ V_{GS} = 0 \end{array} \right.$$

$$A_v = \underline{g_m (R_D || r_o)}$$

$$10 = 5 \times 10^3 \left(\frac{R_D \times 50 \times 10^3}{R_D + 50 \times 10^3} \right)$$

$$\frac{10R_D + 500 \times 10^3}{R_D} = 250R_D$$

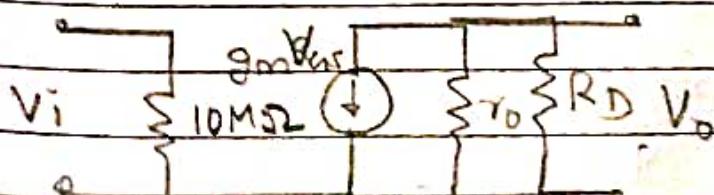
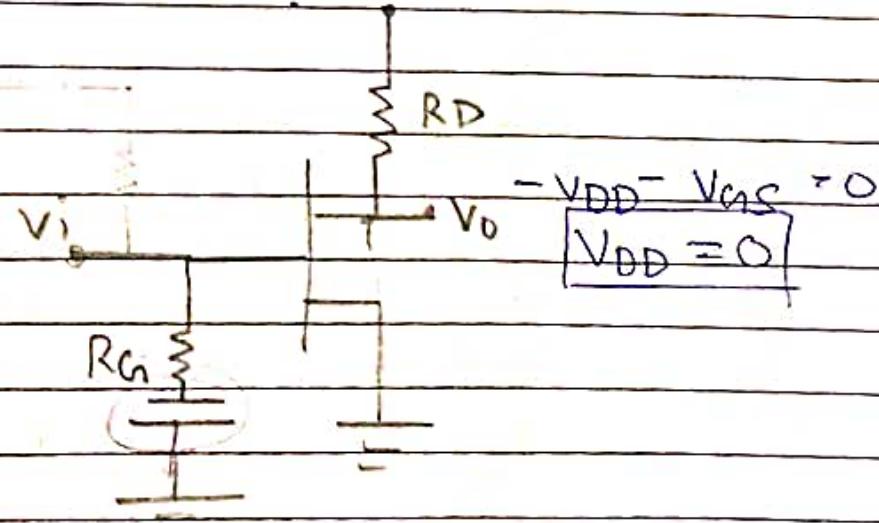
$$R_D = \frac{500 \times 10^3}{248} = 2.083 \text{ k}\Omega$$



Depletion Mosfet

In depletion type MOSFET the Schokley's equation of JFET is applicable here. So the gm model of JFET is valid here. The only difference is V_{AS} can be +ve in depletiony MOSFET whereas it is not possible n channel n channel JFET.

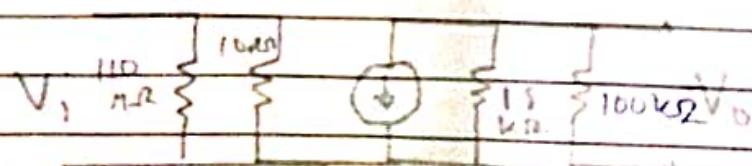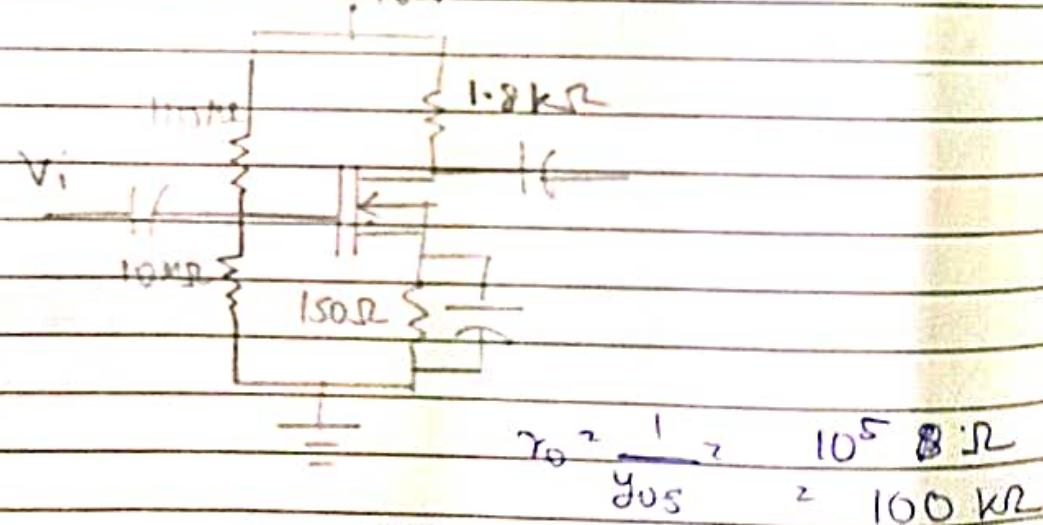- (i) Draw a voltage divider bias ckt with depletion with $V_{DD} = 18 \text{ V}$, $R_D = 1.8 \text{ k}\Omega$, $R_I = 110 \text{ M}\Omega$, $R_2 = 10 \text{ M}\Omega$, $R_S = 150 \Omega$. $I_{DSS} = 6 \text{ mA}$, $V_{GP} = -3 \text{ V}$, $y_{OS} = 10 \mu\text{s}$, $V_{ASG} = 0.35 \text{ V}$, $I_{DO} = 7.6 \text{ mA}$.



$$Z_i = 9.167 \text{ M}\Omega$$

$$Z_o = 1.768 \text{ k}\Omega$$

$$g_m = \frac{2 \times 6^2}{8} = 4 \text{ mS}$$

$$g_m = 4 \left(1 + \frac{0.35}{3} \right)$$

46

$$g_m = 4.20 \text{ mS}$$

$$A_v^2 = \frac{g_m V_{ds} (1768)}{V_{GS}} = -7897$$

$$= -\frac{g_m}{2}$$

Enhancement Type MOSFET

$$I_D = k(V_{GS} - V_{TH})^2$$


$$k = \frac{I_D}{(V_{GS(on)} - V_{TH})^2}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$


$$g_m = 2k(V_{GS} - V_{TH})$$

$$g_m = \frac{2I_D}{V_{GS(on)} - V_{TH}}$$

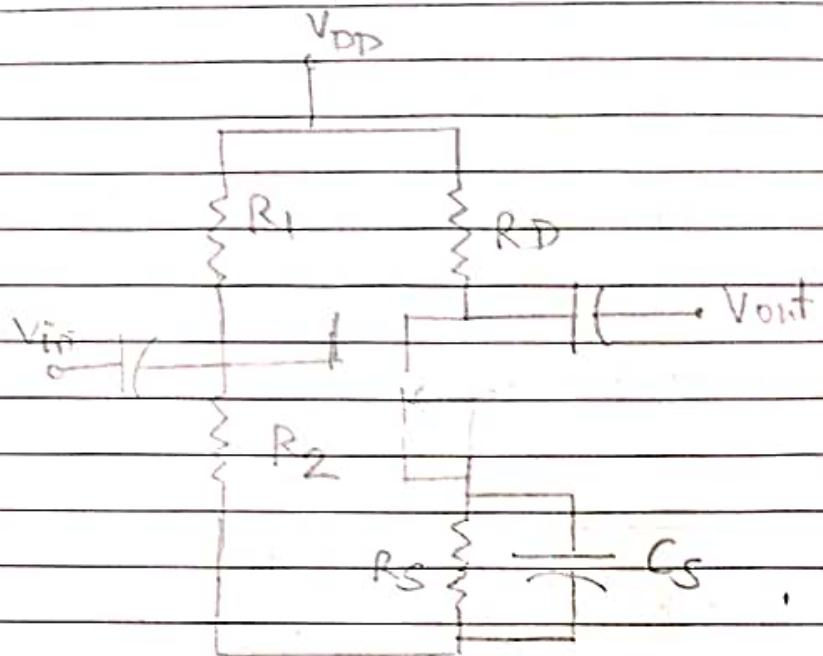The small signal model of enhancement type MOSFET is same as depletion type MOSFET & JFET.
Only the expression for g_m is different in this case.



Draw the small signal model


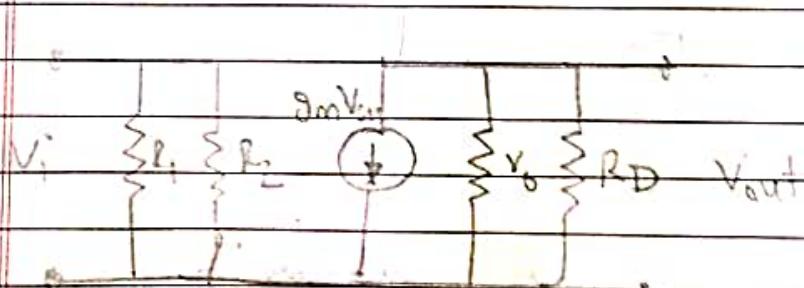


$$Z_i = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad \star \left\{ \text{Output is } 180^\circ \text{ shift w.r.t. input} \right\}$$

$$Z_o = \frac{r_D \cdot R_D}{r_D + R_D}$$

$$A_V = - \frac{\partial m V_{AS} \cdot (R_D || r_o)}{V_{AS}}$$

$$\Rightarrow - \partial m (R_D || r_o)$$

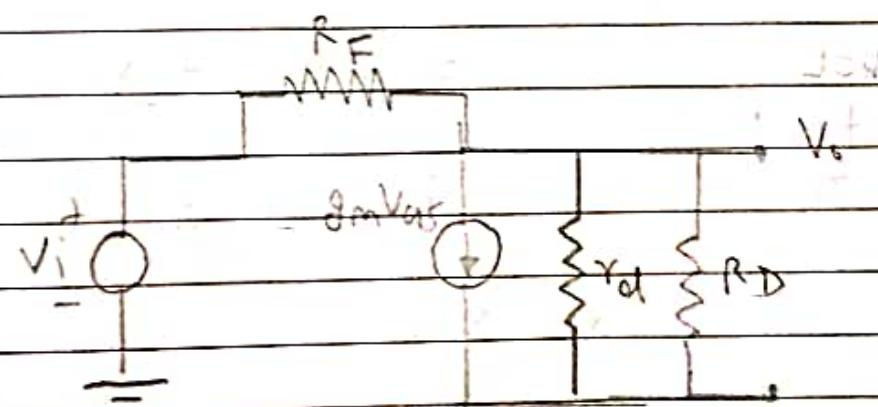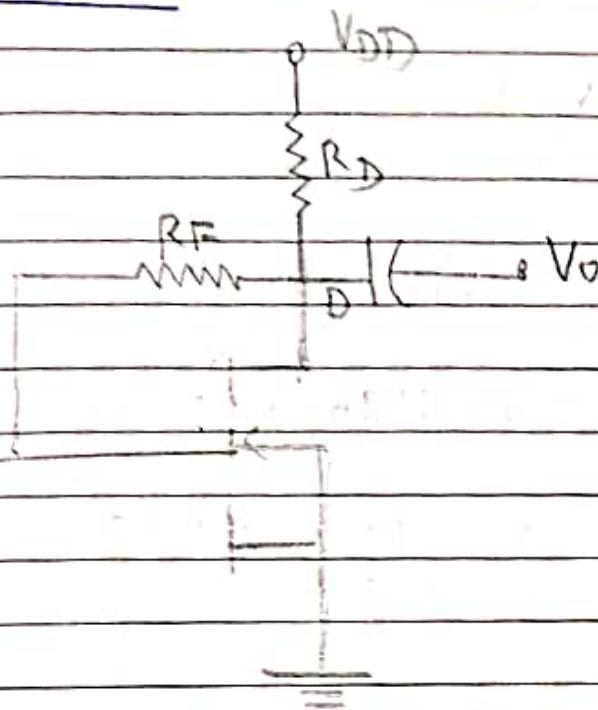Drain Feedback

Z_i :- Applying KCL at node D

$$I_i = g_m V_{GDS} + \frac{V_o}{r_d || R_D}$$

$$V_{GDS} \approx V_Z$$

$$I_Z = g_m V_i + \frac{V_o}{r_d || R_D}$$

$$I_Z = g_m V_i = \frac{V_o}{r_d || R_D}$$

$$v_o = (\gamma_d || R_D) (\bar{I}_z - g_m v_i)$$

$$I_i = \frac{V_i - V_o}{R_F}$$

$$\bar{I}_i = V_i - (\gamma_d || R_D) I_i + (\gamma_d || R_D) g_m v_i$$

$$\bar{I}_i (R_F + (\gamma_d || R_D)) = v_i (1 + g_m (\gamma_d || R_D))$$

$$\left\{ \begin{array}{l} Z_i = \frac{V_i}{I_i} = \frac{R_F + (\gamma_d || R_D)}{1 + g_m (\gamma_d || R_D)} \end{array} \right.$$

A_v = voltage gain

KCL at node

$$I_i = g_m v_{o\text{ref}} + \frac{V_o}{\gamma_d || R_D}$$

D_i

$$I_i = \frac{V_i - V_o}{R_F}$$

$$v_{gs} = V_i$$

$$\frac{V_i - V_o}{R_F} = g_m v_{o\text{ref}} + \frac{V_o}{\gamma_d || R_D}$$

$$V_o \left[\frac{1}{\gamma_d || R_D} + \frac{1}{R_F} \right] = V_i \left[\frac{1}{R_F} - g_m \right]$$

$$A_v = \frac{V_o}{V_i} = \left[\frac{1}{R_F - g_m} \right]$$

$$\left[\frac{1}{\gamma_d || R_D} + \frac{1}{R_F} \right]$$


$e_{rd} \gg i_{rd}$
 $R_F \gg r_{oHID}$

$$\boxed{A_V = -g_m R_D} \quad \left\{ \begin{array}{l} \text{Output is } 180^\circ \text{ out of phase} \\ \text{w.r.t input} \end{array} \right\}$$


A₂₂:

- i) An enhancement type MOSFET was connected in drain feedback configuration. The parameters of the MOSFET are $k = 0.24 \times 10^3 \text{ A/V}^2$, $V_{DSsat} = 6.4 \text{ V}$ & $I_{DSS} = 2.75 \text{ mA}$. Supply voltage = 12V, drain resistance is $2 \text{ k}\Omega$, feedback resistance = $10 \text{ M}\Omega$, $g_{os} = 20 \mu\text{S}$, $V_{TH} = 3 \text{ V}$. ii) Coupling capacitor or $1 \mu\text{F}$

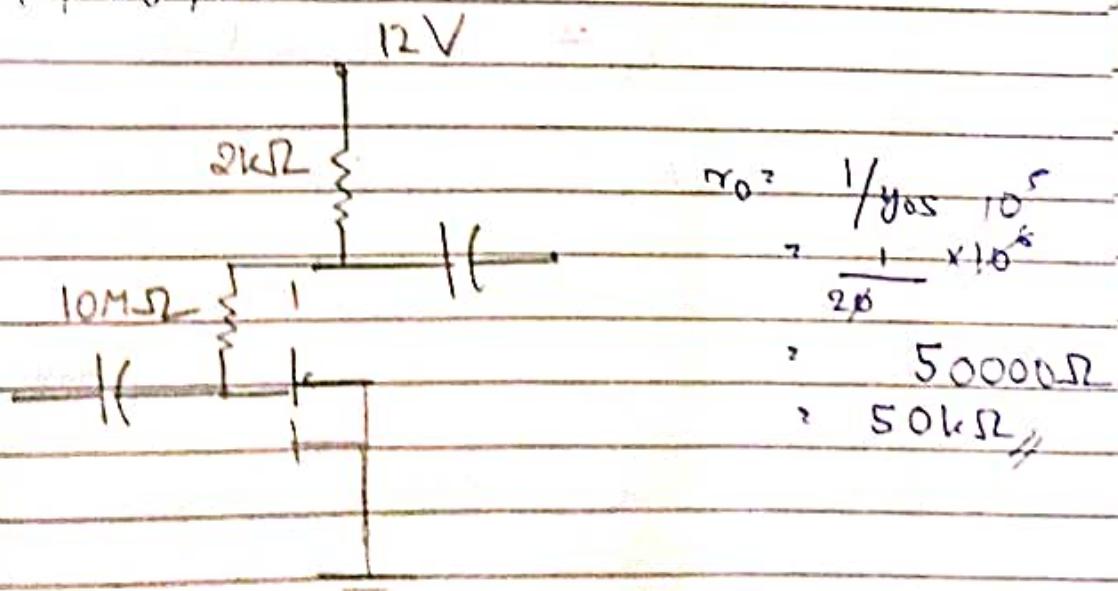- i) Draw circuit diagram
- ii) Small signal model
- iii) Z_i , Z_o , A_V



$$S_D = k(V_{DS} - V_{TH})$$

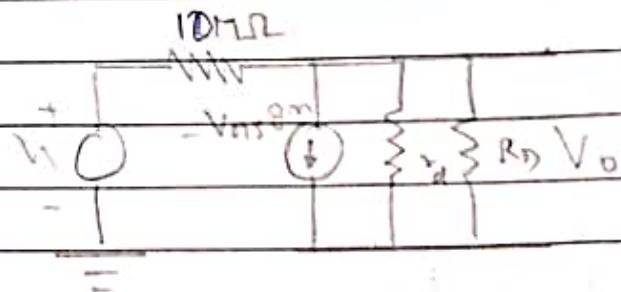

$$Z_i = R_I +$$

$$g_m^2 = 2k(V_{AS} - V_{TH})$$

$$\approx 2 \times 0.24 \times 10^{-3} (6.4 - 3)$$

$$\approx 6.8 \times 0.24 \times 10^{-3}$$

$$\approx 1.632 \text{ mS}$$


$$Z_i = \frac{V_i}{I_i} = \frac{R_I + (r_d || R_D)}{1 + g_m(r_d || R_D)}$$

$$= \frac{24083.49 \cdot 193}{2.408 \text{ M}\Omega} \approx 1.922$$

$$Z_0 \approx R_D = 2k\Omega$$


$$A_V = -g_m R_D$$

$$\approx -3.264$$

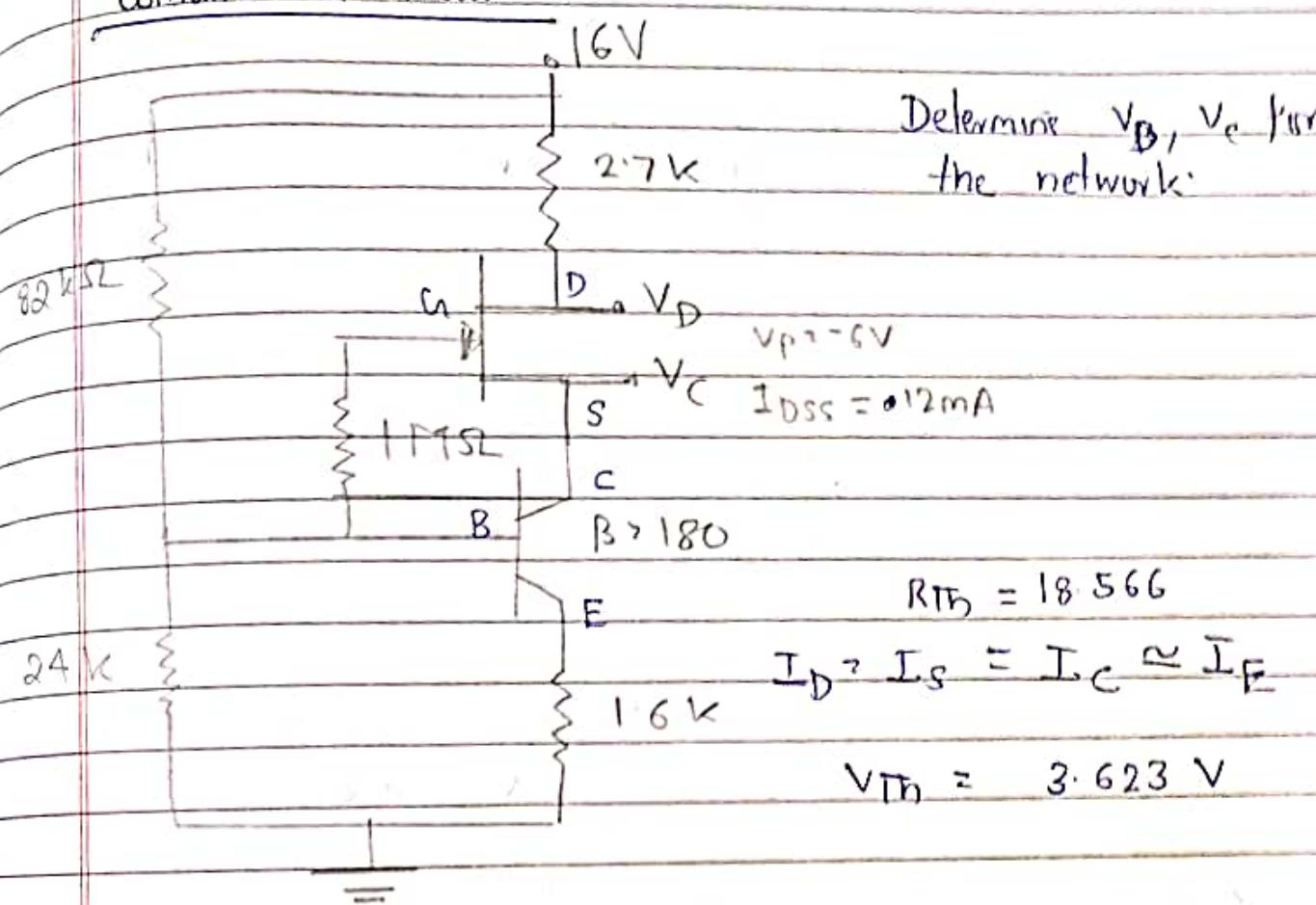Combinational Circuit

$$V_D = 16 - I_D \cdot 2.7 \quad \text{--- (1)}$$
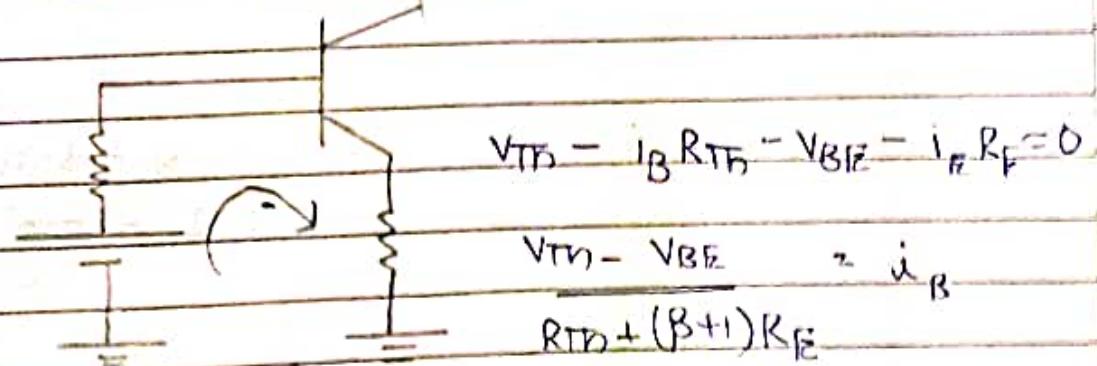
$$V_D = I_D = I_{DS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$




$$V_D = 16 - I_D R_D$$

$$= 11.3911 \text{ V}$$

$$V_{DD} = 10V$$

Q)

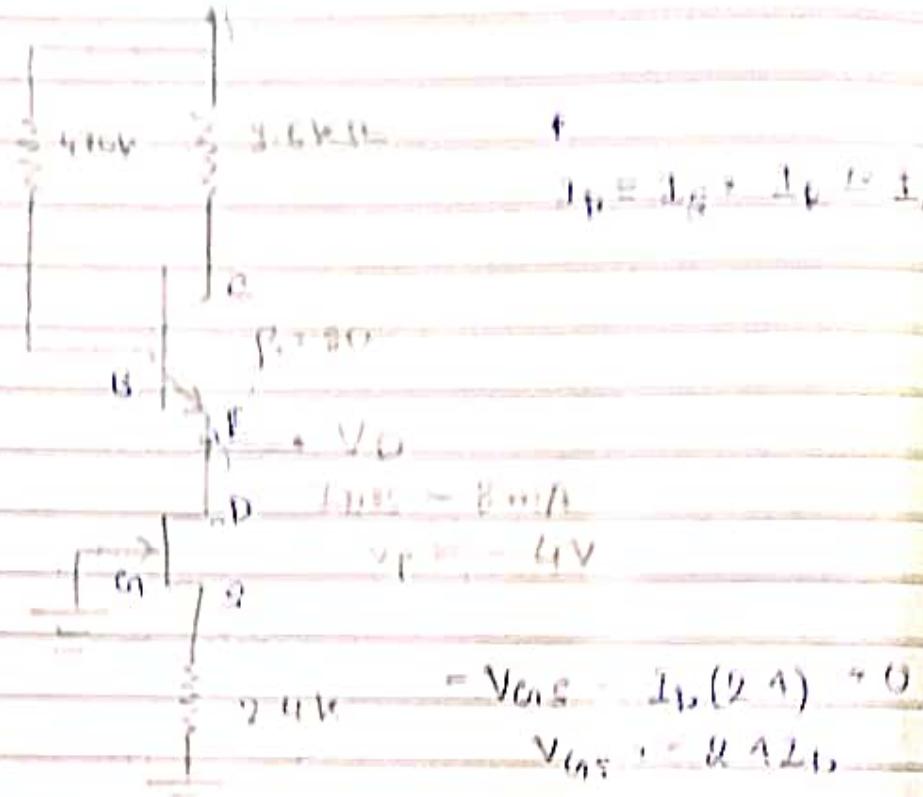

$$= V_{O, S} - I_B (2.4) \approx 0$$

$$V_{O, S} = 0.12 I_B$$

$$I_D = I_{DSS} \left(1 - \frac{V_{DS}}{V_P} \right)^2$$

$$I_D = 8 \left(1 - \frac{2.4}{0.12} \right)^2$$

$$I_D = 8 \left(0.12 + 5.76 \right)^2$$

$$= 0.12 I_D$$

$$2 I_D = 1.6 + 5.76 I_D = \frac{19.2}{4.8} I_D$$

$$5.76 I_D = 4.8 I_D + 0.12$$

$$I_D = 1.22 \text{ mA}$$

$$I_D = 0.12 \text{ mA}$$

$$5.76 I_D^2 = 2.12 I_D + 1.6 \approx 0$$

$$I_D = 2.62 \text{ mA} \times \text{neglected}$$


$$I_D = 1.65 \text{ mA} \quad V_{DS} = -2.52V$$

$$I_B = \frac{1.65}{B} = \frac{1.65}{0.01325} = 124$$


$$V_{CC} - I_B(470) - V_{BR} = V_D$$

$$V_D = 9.0725 \text{ V}$$

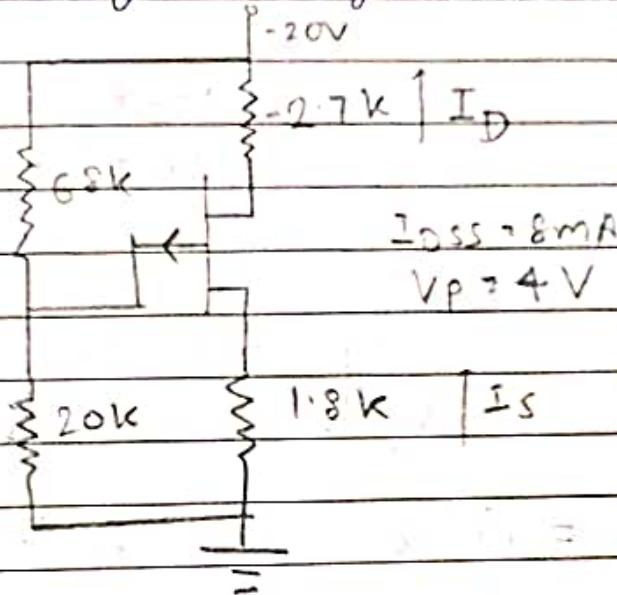- (Q) Determine the Q-point for a p-channel JFET which is used in the given voltage divider configuration.


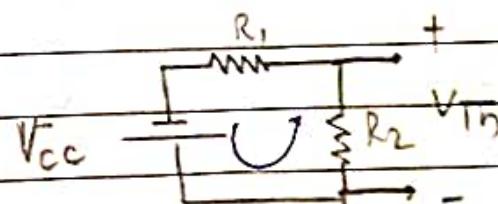
$$\therefore R_{TH} = 15.45 \text{ k}\Omega$$



~~$$V_{CC} + iR_1 - iR_2 = 0$$~~


~~$$R_2 \quad i =$$~~

-20V

$$V_{TH} = -\frac{V_{CC} \cdot R_2}{R_1 + R_2}$$

$$V_{CC} - i_2 R_2 - i_1 R_1$$

$$i_1 = \frac{V_{CC}}{R_1 + R_2}$$

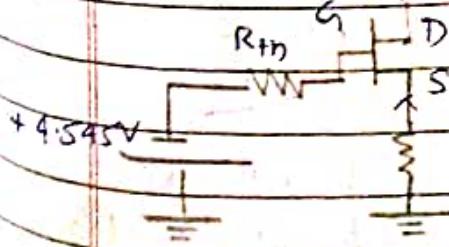

$$-4.545 \text{ V}$$

$$-V_{TH} = V_{BS} + I_{DS} R_S = 0$$

$$V_{BS} = V_{TH} + I_{DS} R_S$$

$$-4.545 + I_D (1.8)$$

$$I_D^2 = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$= 8 \left(1 - (4.545 + 1.3I_D) \right)^2$$

$$I_D^2 = \frac{8}{16} (4.545 + 1.3I_D)^2$$

~~$$2I_D = (4.545 + 1.8I_D)^2$$~~

~~$$2I_D = 3.24 I_D^2 + 91.107 + 34.362 I_D$$~~

~~$$3.24 I_D^2 + 32.362 I_D + 91.107 = 0$$~~

~~$$8 \left(1 - (1.8I_D - 4.54) \right)$$~~

~~$$= 10^{-3} \times 8 \left(1 - \frac{(1.8 \times 10^3 I_D - 4.54)}{4} \right)^2$$~~

~~$$I_D^2 = \frac{8 \times 10^{-3}}{1.8} \left[4 - 1.8 \times 10^3 I_D + 4.54 \right]^2$$~~

~~$$2I_D \times 10^3 = (8.54 - 1.8 \times 10^3 I_D)^2$$~~

$$I_D^2 = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



$$I_D^2 = \frac{8}{2^{1/2}} (8.545 - 1.3I_D)^2$$

$$2I_D = 3.24 I_D^2 + 73.017 - 30.762$$

$$3.24 I_D^2 - 32.762 I_D + 73.017 = 0$$

$$I_D = 6.795 \text{ mA } \times$$

$$I_D = 3.31 \text{ mA } 1.418$$

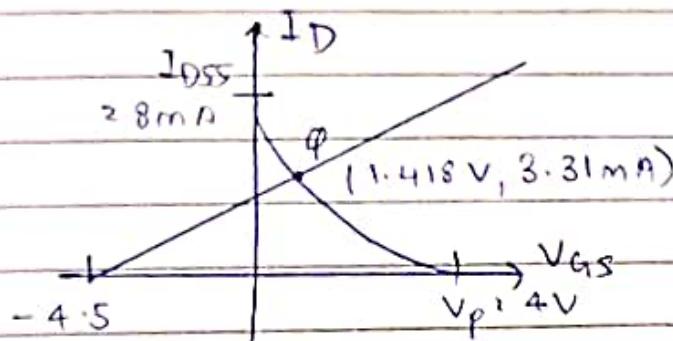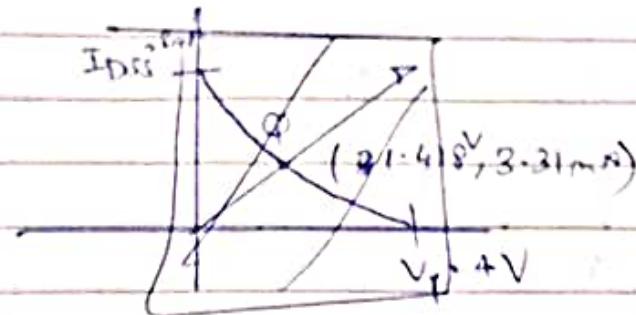

Frequency Response of BJT & FET

$$1) \quad A_P = \frac{P_2}{P_1} \quad \text{Gain (dB)} = 10 \log_{10} \frac{P_2}{P_1}$$

$$2) \quad A_V = \frac{V_2}{V_1} \quad \text{Gain (dB)} = 20 \log_{10} \frac{V_2}{V_1}$$

$$A = A_{V1} \times A_{V2} \times A_{V3} \times \dots$$

$$\text{Gain} = G_1 + G_2 + G_3 \dots$$

$$P = V^2/R$$

$$P_2 = 10 \text{ kW}$$

$$V_2 = 1 \text{ kV}$$



$$P_0 = 500 \text{ W}$$

$$Z_0 = 20 \Omega$$

$$G_P = 10 \log \left(\frac{10 \times 10^3 \Omega}{500 \Omega} \right) = 10 \log \left(\frac{1}{50} \right) = -13 \text{ dB}$$

$$C_s = 20 \text{ pF}$$
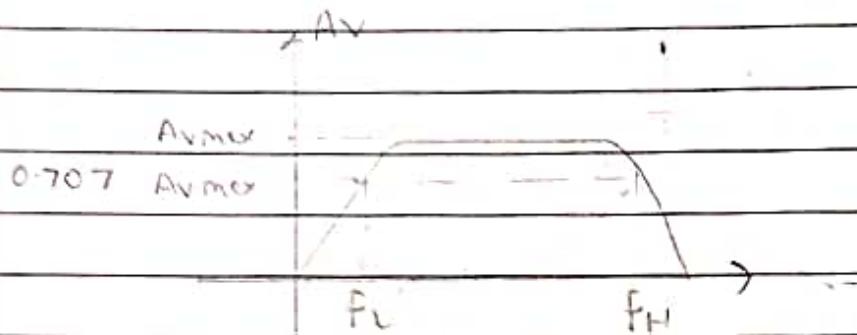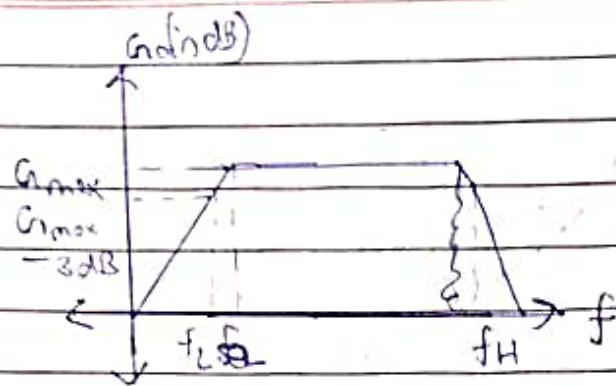
$$V_{DD} = \sqrt{PR} = \sqrt{20 \times 10^3 \text{ W} \times 500 \Omega} = 100 \text{ V}$$



$$P_i^o = \frac{A_v \times V_i^2}{R}$$


$$P_{o, \text{half}} = \frac{P_i^o}{2}$$

$$\frac{1}{2} = \frac{V_o^2 R}{R \cdot V_i^2}$$

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{2}}$$

$$A_v^2 \frac{1}{\sqrt{2}} = 0.707$$

C

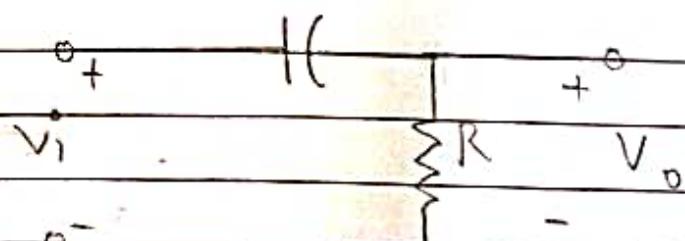

$$X_C^2 = \frac{1}{\omega C}$$

$$\omega = 0$$

$$\omega = \infty$$

$$X_C = \infty$$

$$X_C = 0$$

$$V_o = \left(\frac{R}{R - jX_C} \right) \cdot V_i$$

when $R = jX_C$

$$V_o = \infty$$

when $X_C = R$,


$$|V_o| = V_i \times \frac{R}{\sqrt{R^2 + X_C^2}}$$

$$|V_o| = V_i$$

$$\sqrt{2}$$

$$[|V_o| = 0.707 V_i]$$

$$f = \frac{1}{2\pi RC}$$

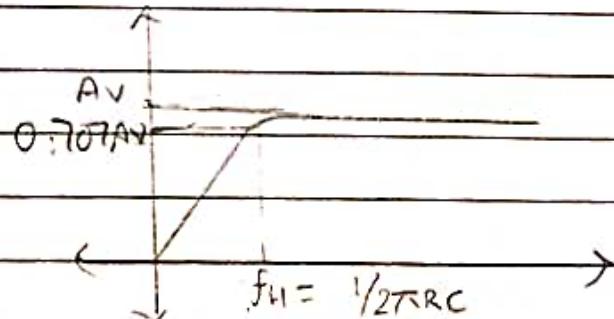

$$\frac{V_o}{V_i} = \frac{R}{R - jX_C}$$

$$\frac{V_o}{V_i} = \frac{R}{\sqrt{R^2 + X_C^2}} \cdot \frac{\sqrt{R^2 + X_C^2}}{R} \cdot \frac{1}{\omega^2 C^2}$$


$$\frac{V_o}{V_i} = \frac{R}{R - jX_C}$$

$$= \frac{R}{R - \frac{j}{2\pi f C}}$$


$$= \frac{1}{1 - \frac{j}{2\pi f C R}}$$

$$A_v = \frac{1}{1 - \frac{f_c j}{f}}$$
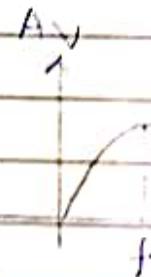
$$= \frac{1}{\sqrt{1 + f_c^2/f^2}} \cdot \tan^{-1} \left(\frac{f_c}{f} \right)$$



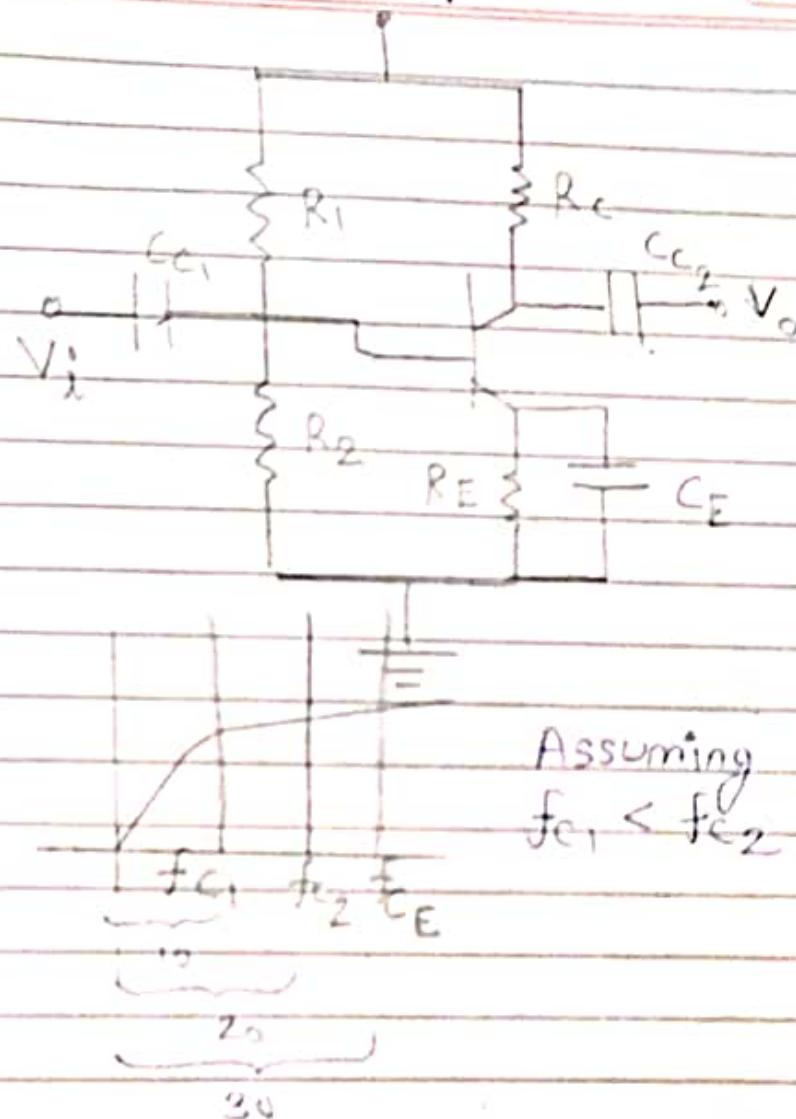In BJT, we have 3 capacitors i.e. C_C i.e. coupling capacitor at input and output and ~~emitter~~ bypass capacitor i.e. C_E . Corresponding to this we'll have 3 frequencies.



$$f_{C_0} = \max(f_{C_1}, f_{C_2}, f_{C_E})$$

$$C_0 \Rightarrow f_{C_0} = \max(f_{C_1}, f_{C_2}, f_{C_E})$$

$$f_{CC_1} = \frac{1}{2\pi R_{eq} C_{C_1}}$$

$$f_{CC_2} = \frac{1}{2\pi R_{eq} C_{C_2}}$$

$$f_{CE} = \frac{1}{2\pi R_{eq} C_E}$$

Using r_e equivalent model,

$$f_{C_E} = \frac{1}{2\pi(R_1 + R_2 + R_{E'})C_E}$$

$$f_{C_E} = \frac{1}{2\pi(R_C + r_s)C_E}$$

$$f_{C_E} = \frac{1}{2\pi(R_3' + R_C)C_E}$$

when $R_{eq} = R_2 + \frac{R_3' + R_C}{R_3' + R_C + R_2}$

$$R_3' = R_1 + R_2$$

(Q) Find the lower cutoff frequency for a bridge divided network having

$$C_{E1} = 10 \mu F$$

$$C_{E2} = 1 \mu F$$

$$C_E = 20 \mu F$$

$$R_1 = 40k$$

$$R_2 = 10k$$

$$R_E = 2k$$

$$R_C = 4k$$

$$\beta = 100$$

$$V_{ee} = 20V$$

$$r_e = 26$$


$$j\omega$$

f_{CC1}

$$R_m = 8 \text{ k}\Omega$$

$$V_{TH} = \frac{210}{50} \times 20$$

$$= 4 \text{ V}$$

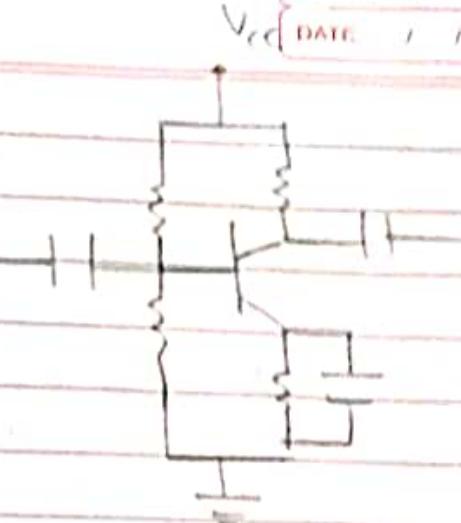


$$i_B = \frac{V_{TH} - V_{BE}}{R_m + (\beta+1)R_E}$$

$$= 0.0157 \text{ mA}$$

$$i_E = 1.587 \text{ mA}$$

$$r_e = 16.38 \text{ }\Omega$$

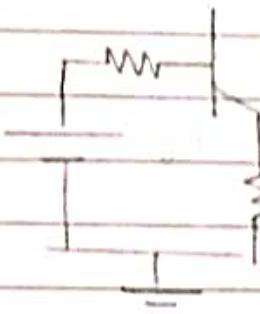

$$f_{CC1} = \frac{1}{2\pi (R_1 || R_2 || \beta r_e) C_{C1}}$$

$$= \frac{1}{2\pi (1.35 \text{ k}\Omega) C_{C1}}$$

$$= 11.789 \text{ kHz}$$

$$\emptyset f_{CC2} = \frac{1}{2\pi R_C \cdot C_{C2}} = 39.788 \text{ kHz}$$

$$f_{CR} = \frac{1}{2\pi R_{eq} C_{Fe}}$$

$$R_{eq} = R_B || (0.01 C_{38})$$


$$= 0.065 \text{ k}\Omega$$

$$R_B f_{CR} = 86.35$$


$$f_{max} f_C = 86.35 \text{ kHz}$$


Power Amplifiers / Large Signal Amplifiers

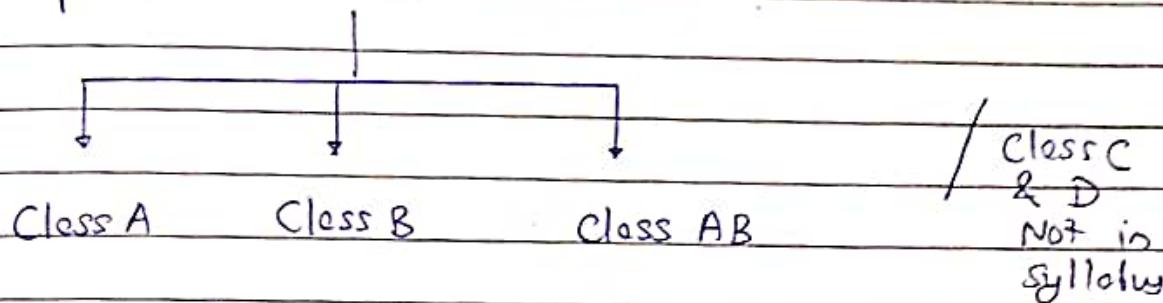Power amplifier signals are used to provide power to an output load such as a speaker or a power device.



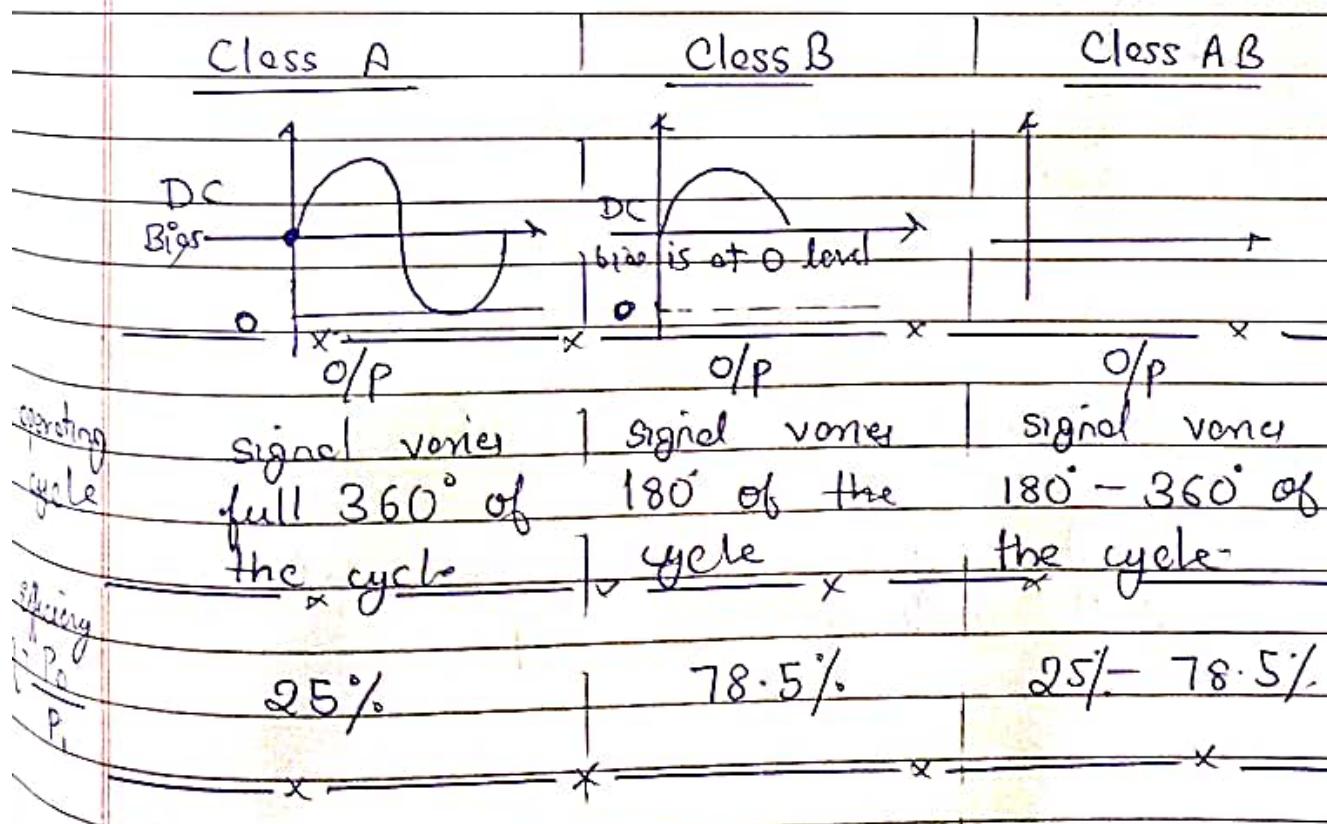Power amplifiers are categorized on the basis of the amount of output signal variation over 1 cycle of operation for a full cycle of input signal.




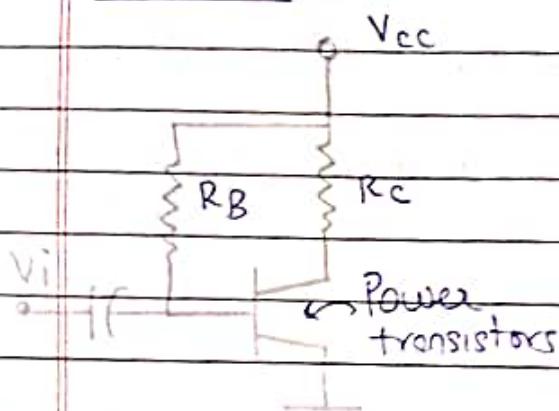Class A

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_{CQ} = \beta \cdot \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$
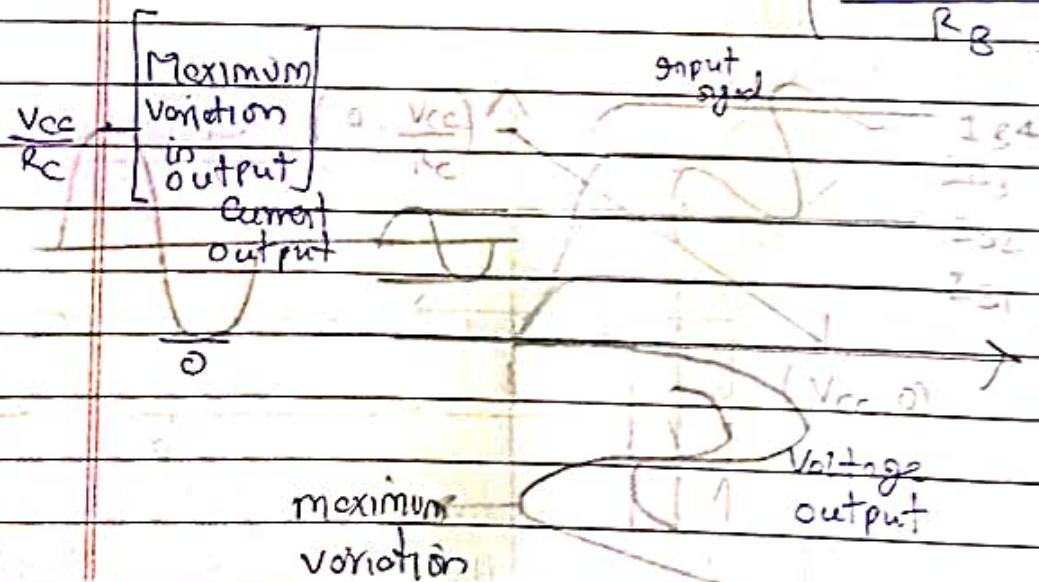
$$V_{CEQ} = V_{CC} - \beta \cdot R_C \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$



operating point is such that output conduct full cycle of the i/p.

$\frac{o/p \text{ current } V_{cc}}{R_c} \text{ to } 0$

$o/p \text{ voltage } V_{cc} \text{ to } 0$

$$V_{cc} \times I_{cp} = P_{\text{input}} - P_i(\text{dc})$$

The output power ~~and~~ H_i is derived from the output voltage and current varying around the biased point.

~~$P_o = V_{rms} \times I_{rms}$~~

V_{rms}	RMS	Peak	Peak to Peak
Power output	V_{rms}	V_p	V_{pp}
$P_o(VI)$	$V_{rms} I_{rms}$	$\frac{V_p \cdot I_p}{2}$	$\frac{V_{pp} \cdot I_{pp}}{8}$
(I)	$I_{rms}^2 R_c$	$\frac{I_p^2 R_c}{2}$	$\frac{I_{pp}^2 R_c}{8}$
(V)	$\frac{V_{rms}}{R_c}$	$\frac{V_p^2}{2 R_c}$	$\frac{V_{pp}^2}{8 R_c}$

Maximum η : Maximum $V_{CE}(\text{p.p.}) = V_{cc}$

Maximum $I_c(\text{p.p.}) = \frac{V_{cc}}{R_c}$

$$P_o = V_{cc} \times \frac{V_{cc} \times I}{R_c \times 8}$$

$$I_{CQ} = \frac{V_{CC}}{R_C}$$

input power

Maximum efficiency, : $P_i = V_{CC} \times \frac{V_{CE}}{2 R_C}$

$$\eta = \frac{P_o}{P_i} = \frac{\frac{V_{CC}^2}{8 R_C}}{\frac{V_{CC}^2}{2 R_C}}$$


$$\eta = \frac{P_o}{P_i} = \frac{1}{4} = 0.25$$

$$\frac{V_{CC}^2}{2 R_C}$$

$\therefore \eta = 25\%$

$$V_{CC} = 20V$$

e.g. :

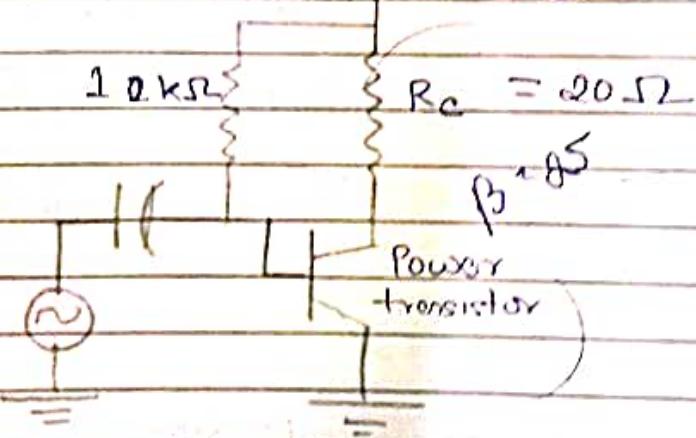

Draw the

DC

load

line

and


calculate

the maximum

efficiency.

Calculate the

for a base current
peak of 10mA.

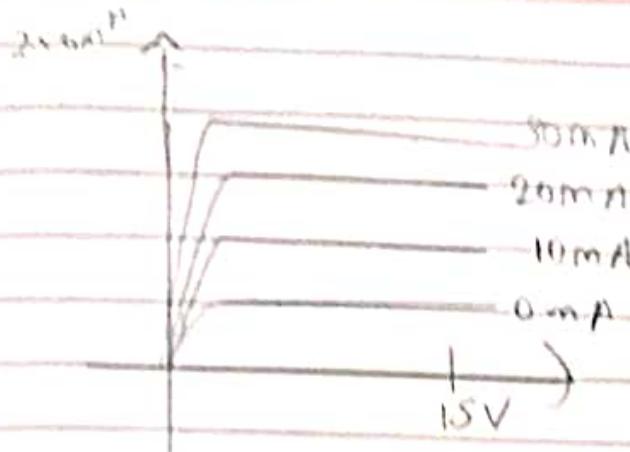


$$\begin{aligned} I_c &= \beta i_B \\ &= 25 \times 10 \\ &= 250 \text{ mA} \end{aligned}$$

$$V_{CEQ} = 15 \text{ V}$$

$$\begin{aligned} R_C &= \frac{20 - 0.7}{1000 + 25 \times 20} \\ &= \frac{19.3}{1000 + 500} \\ &= \frac{19.3}{1500} \text{ m}\Omega \\ &= 0.0128 \text{ m}\Omega \\ i_C &= 0.321 \text{ mA} \\ V_{CEQ} &= V_{CC} - i_C R_C \end{aligned}$$

$$\begin{aligned} i_B &= 0.0128 \text{ mA} \\ i_{CQ} &= 0.321 \text{ mA} \\ V_{CEQ} &= 19.3 \text{ V} \end{aligned}$$

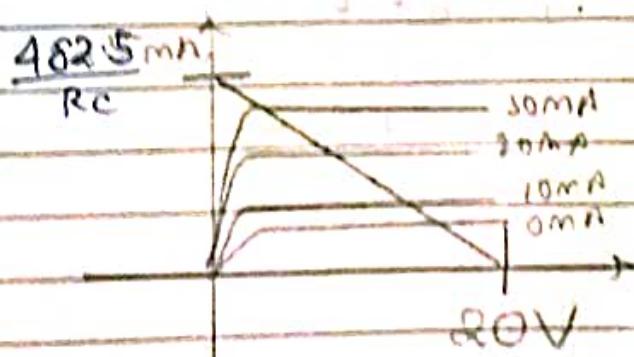
$$\begin{aligned} i_B &= 19.3 \text{ mA} \\ i_C &= 482.5 \text{ mA} \\ V_{CEQ} &= 10.35 \text{ V} \end{aligned}$$



$$\begin{aligned} P_i &= V_{CEQ} \times I_{CQ} \\ &= 9.6 \text{ W} \end{aligned}$$

$$P_o = \frac{V_{PP} \times I_{PP}}{8}$$

Transformer coupled
class A
amplifier

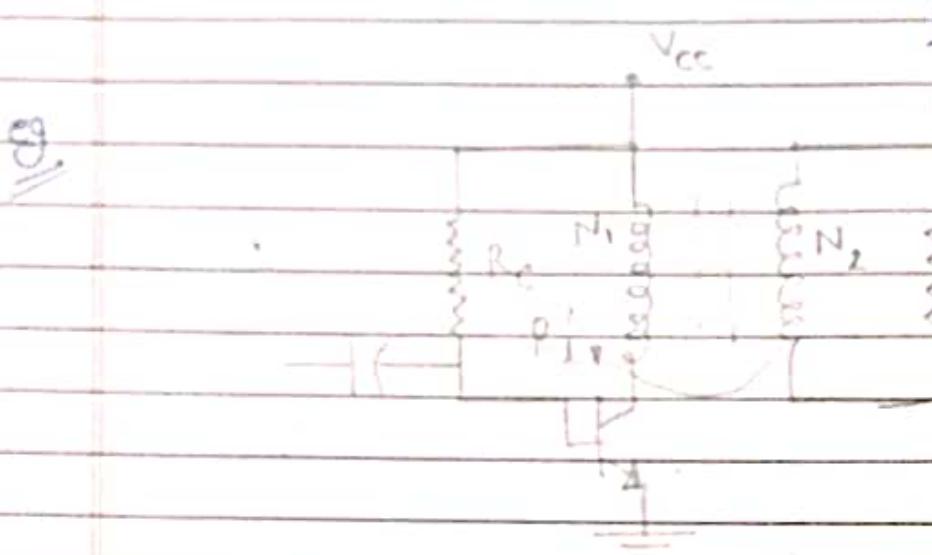

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2}$$

$$R'_1 = R_2 \times \left(\frac{N_1}{N_2} \right)^2$$

Q 15:1 Transformer. Calculate effective resistance seen from the primary side of a transformer (15:1) connected to a 8Ω load.

$$\begin{aligned} R'_1 &= 8 \times 15^2 \\ &= 1800 \Omega \\ &= 1.8 \text{ k} \end{aligned}$$